

EE394V Homework Assignment #5

Due date: 11/27/2013

For all questions elaborate some few conclusions or comments about the results. For all questions you are free to make further, but logical, assumptions you consider necessary

- 1) Consider a buck-boost converter with $L = 500 \mu\text{H}$, $C = 1 \text{ mF}$, $R = 10 \Omega$, $E = 30 \text{ V}$. Simulate an hysteresis control that achieves a voltage output of 40 V with a current ripple of 1 Amp . Plot the state variables in time domain and on a phase portrait.
- 2) Now, try regulating the output with a PI controller. For the PI controller choose some suitable gains and simulate the resulting system. Plot the state variables in time domain and on a phase portrait.
- 3) Consider a buck converter with $L=500 \mu\text{H}$, $C= 1000 \mu\text{F}$, $E = 24\text{V}$, and a resistive load with $R = 12.96 \Omega$. Plot the state variables in time domain when a converter of the form

$$d = 0.7 + .1 \int e dt + 0.001e$$

is used to regulate the output voltage to 18 V . In the last equation, e is the error signal that results from the difference between the desired output voltage and the actual output voltage.

- 4) Now replace the resistive load by a constant power load of 25 W and repeat the simulation showing the same plots. Finally, repeat once again the simulation but now add a differential term to the above controller with a gain $k_d=0.0001$.