


Invertors

Note Title

11/2/2008

Understanding the switching function is essential for analyzing invertors behavior.

For $f(t)$ as:

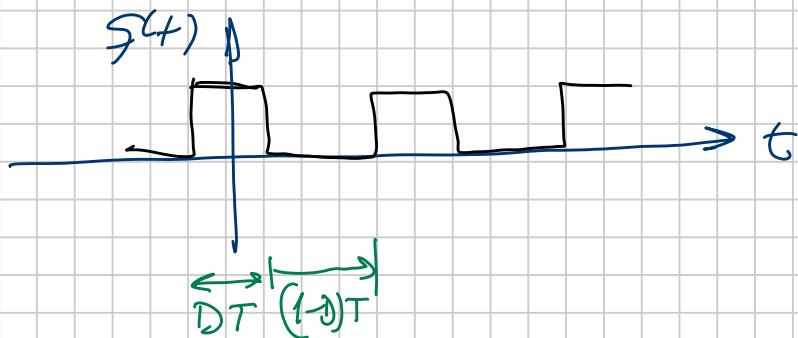


$$f(t) = D + \frac{1}{\pi} \sum_{n=1}^{\infty} \frac{\sin(n\pi D)}{n} \cos(\omega_0 t - n\phi_0)$$


↳ average value

$$|f(t)|_{avg} = \sqrt{D}$$

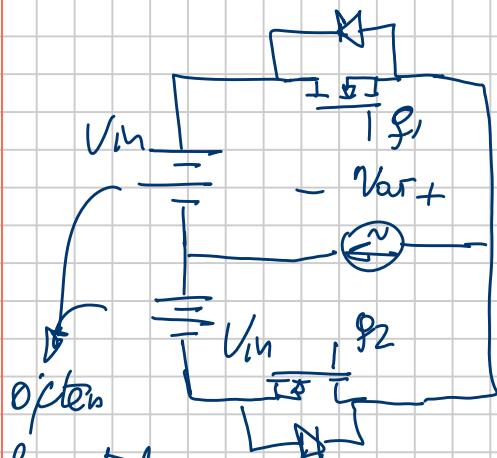Like we did with the rectifiers let's assume first a single-phase output half bridge inverter



Implemented

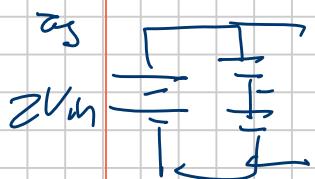

From LOVL $g_1 + g_2$ cannot be more than 1

From KCL $f_1 + f_2$ cannot be less than 1

∴ Hence, $f_1 + f_2 = 1$

When $f_1 = 1$, $V_{out} = V_h$ $\left\{ \begin{array}{l} V_{out} = g_1(+)V_h - g_2(+)V_h \\ V_{out} = g_1(-)V_h - g_2(+)V_h \end{array} \right.$

When $f_2 = 1$, $V_{out} = -V_h$

$$V_{out} = (2g_1 - 1)V_h$$

$$\langle V_{out} \rangle = \underbrace{(2D_1 - 1)}_{\text{average}} V_h$$

So if the load is inductive which requires $(N_L) = 0$,
then $\langle V_{out} \rangle = 0 \Rightarrow 2D_1 = 1$


$$D_1 = \frac{1}{2}$$

and since $f_1 + f_2 = 1 \rightarrow D_1 + D_2 = 1$

$$D_2 = D_1 = \frac{1}{2}$$

Since we want an ac output, then let's assume that
 $D_1 = D_2$ regardless of whether or not the load is
inductive.

Then ↴

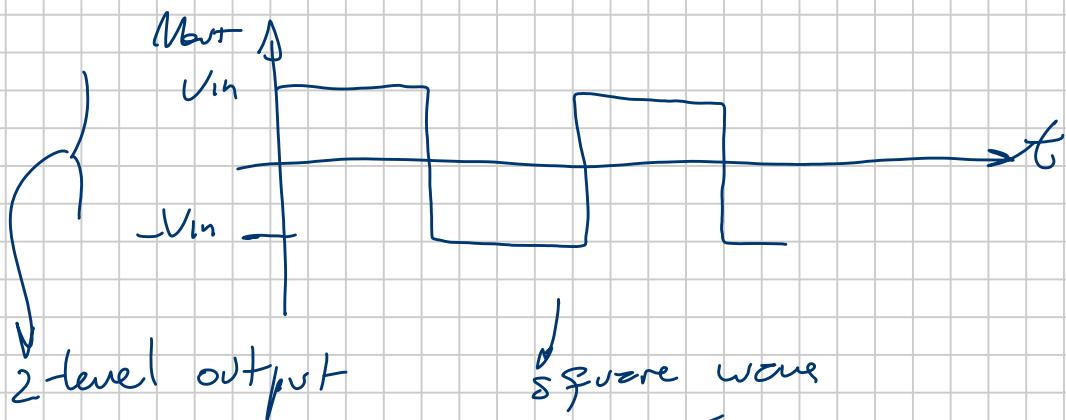

$$V_{out} = \frac{4V_{in}}{\pi} \sum_{n=1}^{\infty} \frac{\sin(n\pi/2)}{n} \cos(n\omega_{sw}t - n\phi)$$

it is obtained from $V_{out} = (2g_1 - 1)V_{in}$


$$\text{and } g_1(t) = \frac{1}{2} + \frac{2}{\pi} \sum_{n=1}^{\infty} \frac{\sin(\frac{1}{2}\pi n)}{n} \cos(n\omega t - n\phi_0)$$

$\underbrace{D}_{\frac{1}{2}}$

Usually we are mostly concerned with the fundamental



$$V_{out} = \frac{4V_{in}}{\pi}$$

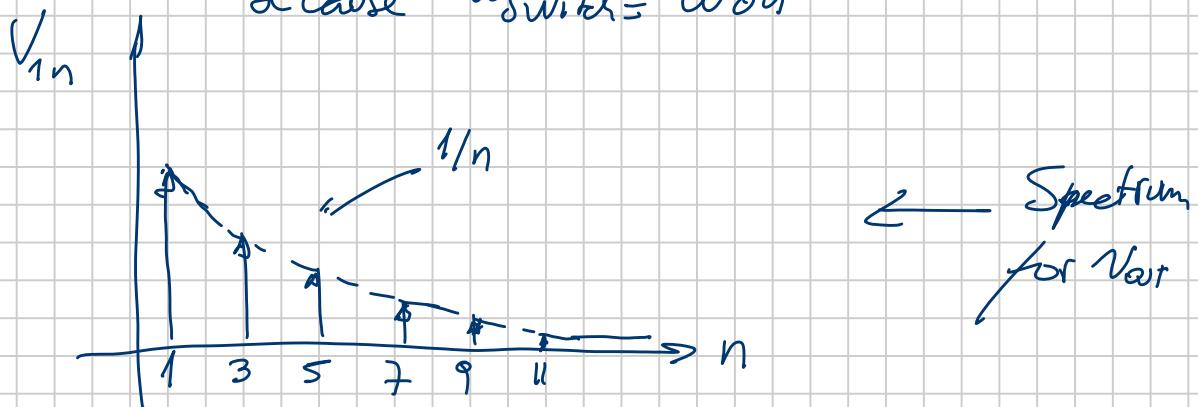- Issues:
- 1) Output is fixed \rightarrow No voltage regulation
 - 2) Harmonics too close to fundamental. And fundamental frequency is usually low because $\omega_{switch} = \omega_{out}$



How can we have output voltage regulation?

One solution is the following one:

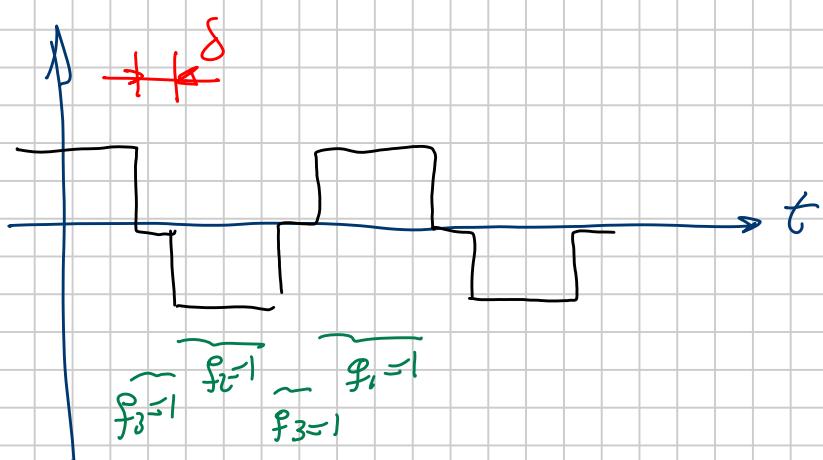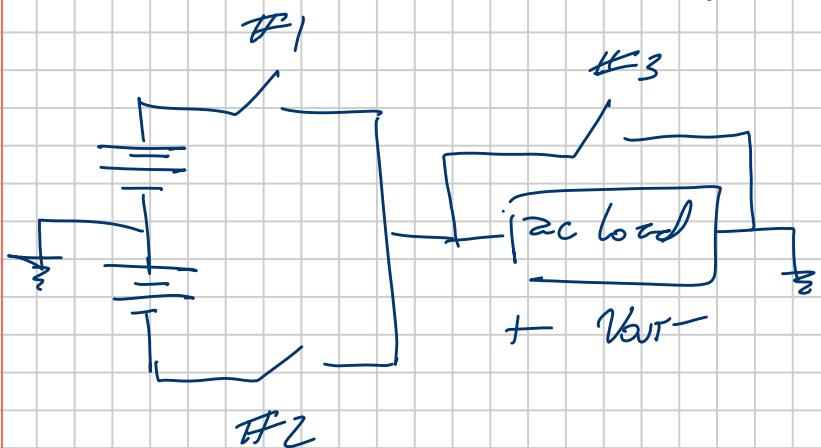


$$V_{out} = \frac{2V_{ib}}{\pi} \sum_{n=1}^{\infty} \frac{\sin(n\pi/2)}{n} \left[\cos(nwsut) + \cos(nwsut - n\delta) \right]$$

The fundamental component is

$$V_{out_1} = \underbrace{\frac{4V_{ib}}{\pi} \cos \frac{\delta}{2} \cos \left(wsut - \frac{\delta}{2} \right)}_{V_{out_1}}$$

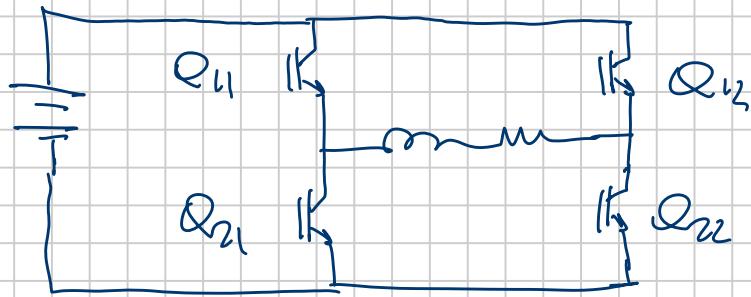I can achieve the same behavior with a full bridge inverter :



From KVL & KCL:


$$\left. \begin{array}{l} f_{11} + f_{21} = 1 \\ f_{12} + f_{22} = 1 \end{array} \right\}$$

If Q_{11} and Q_{21} or Q_{12} and Q_{22} are simultaneously on I have short-thru

$$\left. \begin{array}{l} Q_{11}, Q_{22} \text{ ON} \rightarrow V_{out} = V_m \\ Q_{12}, Q_{21} \text{ ON} \rightarrow V_{out} = -V_m \\ Q_{11}, Q_{12} \text{ ON} \rightarrow V_{out} = 0 \\ Q_{21}, Q_{22} \text{ ON} \rightarrow V_{out} = 0 \end{array} \right.$$

$$\left. \begin{array}{l} V_{out} = f_{11} V_m - f_{12} V_m = \\ = (f_{11} - f_{12}) V_m = \\ = (f_{11} + f_{22} - 1) V_m \end{array} \right.$$

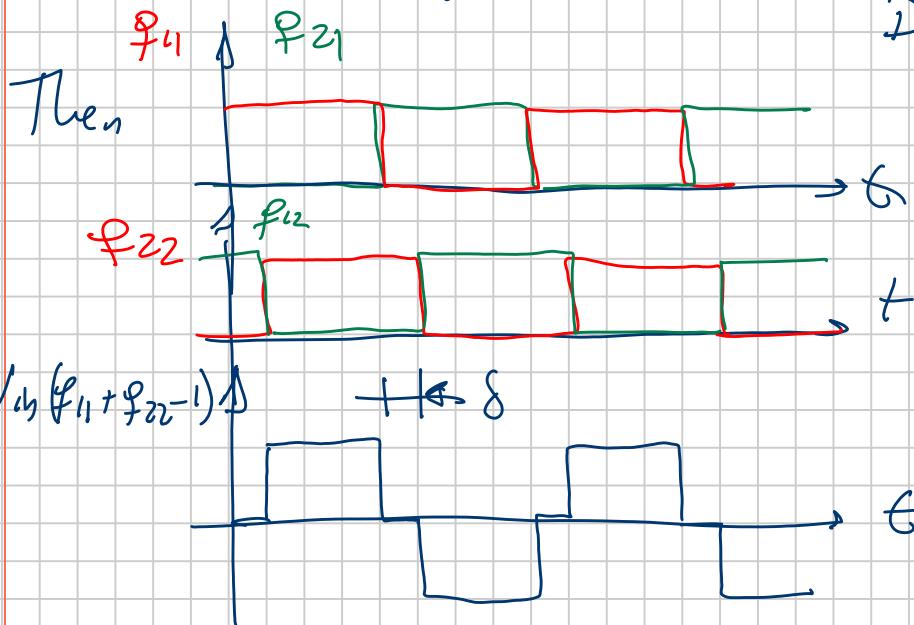
To avoid having dc we need $D_{11} = D_{21} = 1/2$
 $D_{12} = D_{22} = 1/2$



So I have addressed issue #1 above. But this approach does not address issue #2. Can I address both simultaneously? Yes, with pulse-width modulation (PWM).

PWM

Let's consider the inverter seen before

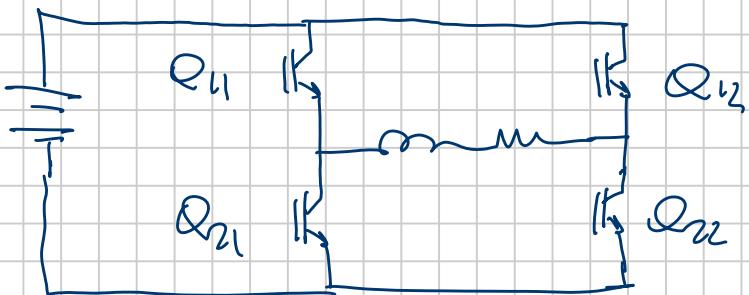

and let's operate it only with the following 2 states.

- { State1: Q_{11} ON and Q_{22} ON $\rightarrow V_{out} = V_{in}$
- State2: Q_{12} ON and Q_{21} ON $\rightarrow V_{out} = -V_{in}$

S_1 last for dT_S and S_2 lasts for $(1-d)T_S$ where d is the duty cycle for a given switching period and T_S is the switching period.

Although d stays fixed during each switching period it can change from switching period to switching period

My goal is to obtain an ac output in which the fundamental has a frequency of $\omega_b = 2\pi f_0 = \frac{2\pi}{T_0}$

So let's define k as

$$k = \frac{T_o}{T_s} \longrightarrow k \gg 1$$

Let's consider now one switching interval $\widehat{T_s}$.

During that particular switching interval d , is fixed and equals:

$$d = D | \widehat{T_s}$$

Then, the average output voltage for that switching interval $\widehat{T_s}$ is:

$$\langle V_{out} \rangle | \widehat{T_s} = D | \widehat{T_s} V_{th} + (1-D) | \widehat{T_s} (-V_{in}) = \\ = V_{th} (2D | \widehat{T_s} - 1)$$



This expression comes from $V_{out} = (g_{11} + g_{22} - 1) V_{in}$. If $g_{11} = g_{22}$ then

$$\overbrace{V_{out} = (2g_{11} - 1) V_{in}}^{\text{average}} \quad (1)$$

$$\langle V_{out} \rangle = (2D_{av} - 1) V_{th}$$

So from $\langle V_{out} \rangle | \widehat{T_s} = V_{th}(2D | \widehat{T_s} - 1)$ let's assume, as I said before, that the duty cycle changes' from switching cycle to switching cycle in the following particular way:

$$d(t) = \frac{1}{2} + \frac{1}{2} m(t)$$

where $m(t) = m \cos(\omega_0 t)$

modulator
Signal

modulation
index

desired
↑ fundamental
explosive

$$m \triangleq \frac{V_{\text{out}}}{V_{\text{ch}}}$$

where $m \leq 1 \quad \forall t \quad \text{so } |m(t)| \leq 1 \quad \text{and}$

$$|d(t)| \leq \frac{1}{2} \quad \forall t$$

so

$$d(t) = \frac{1}{2} + \frac{1}{2} m \cos(\omega_0 t)$$

and

$$\langle V_{\text{out}} \rangle(t) = V_{\text{ch}} m \cos(\omega_0 t)$$

The problem here is that I said

Although d stays fixed during each switching period it can change from switching period to switching period

And in the above equation d changes continuously with time. So the correct form is

$$D|_{T_s} = \frac{1}{2} + \frac{1}{2} m \cos(\omega_0 t(nT_s))$$

As $T_s \rightarrow 0$ ($f_{\text{sw}} \rightarrow \infty$) then $D|_{T_s} \rightarrow d(t)$

and $t(nT_s) \rightarrow t$.


So, how do I take $t(nT_s)$. In other words, how

do I sample the modulation signal?

There are 2 main approaches for sampling $m(t)$.

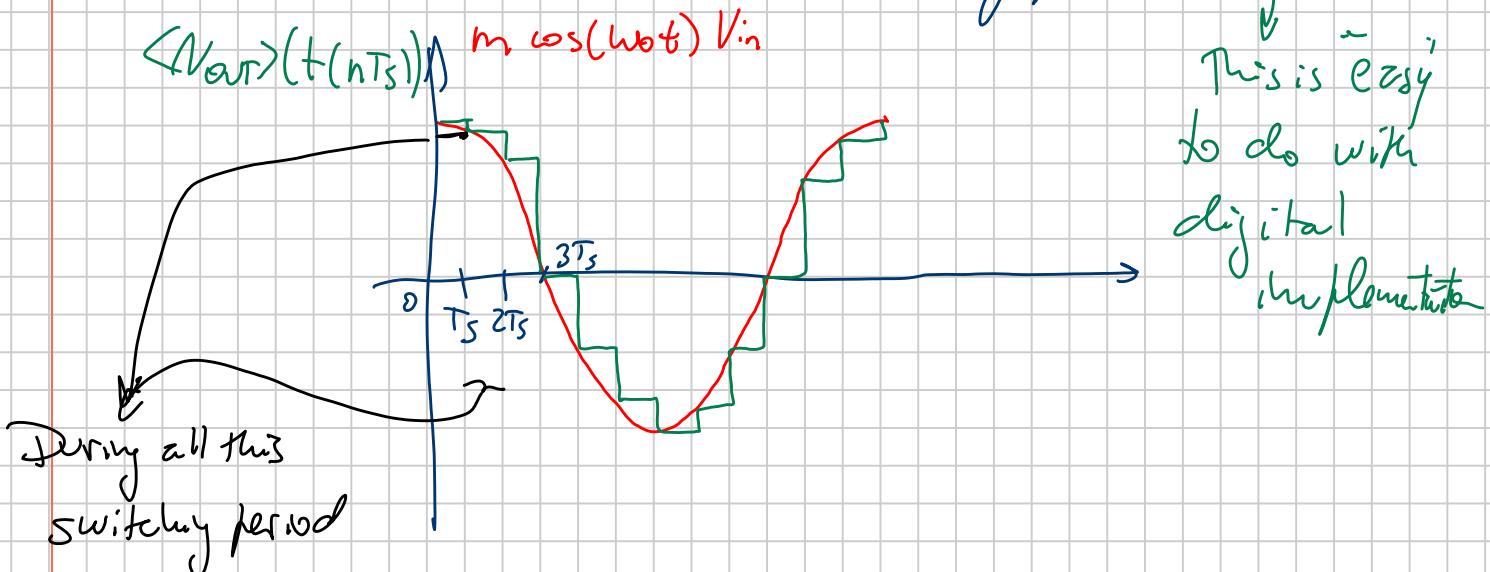
1) Uniform PWM (Upwm)

I sample every T_s seconds, usually at the start of each switching period.



$$D|_{T_s} = \frac{1}{2} + \frac{1}{2} m \cos(w_b T_s)$$

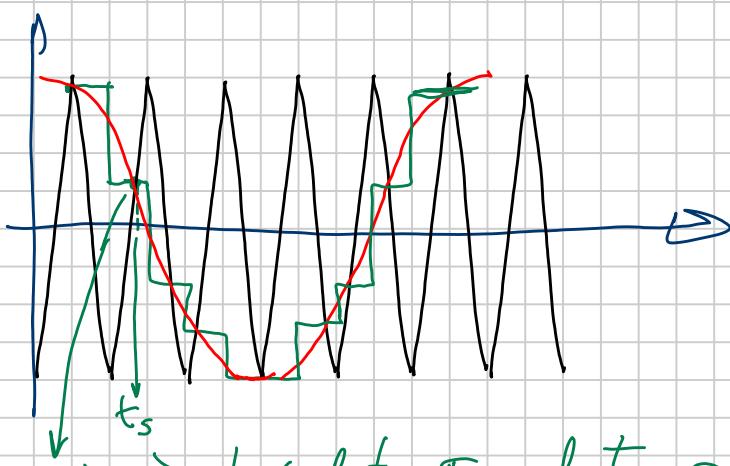
2) Natural PWM (NPWM) \rightarrow Sample is given by a triangle waveform




to find t_s I need to solve the transcendental equation $f_{t_s}(t_s) = m(t_s)$

This is difficult when it is implemented digitally

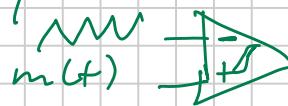
but it is easy when it is implemented
analogically



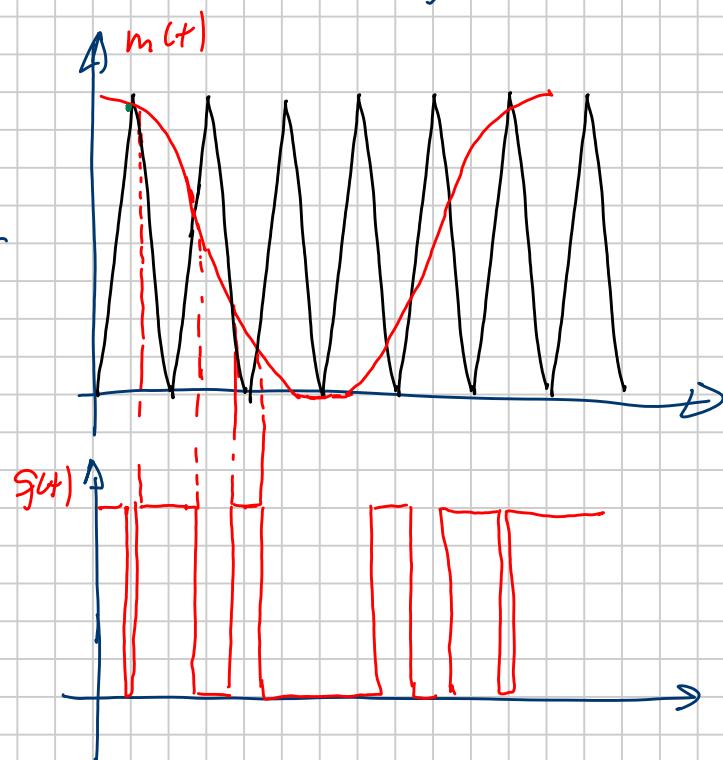$m(t)$ has, in fact, an offset of $1/2$ with respect to the red curve above. So $g(t)$ looks something like the following.




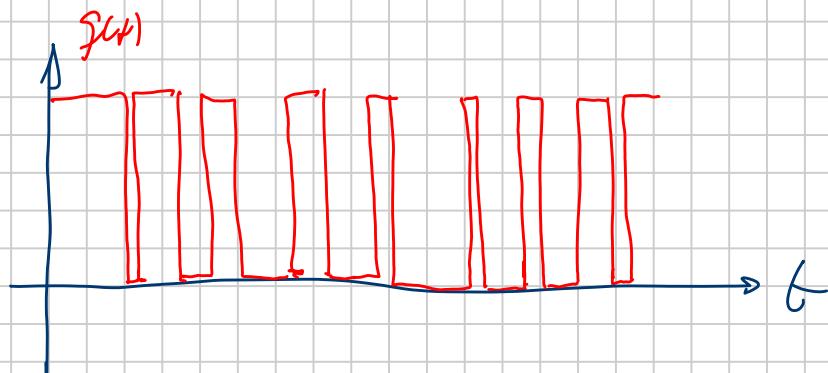Typically $T_s \ll T_0$ so $g(t)$ looks closer to the following



$$\text{And since } \text{Nbr} = (2g_{\text{in}}(t) - 1)V_{\text{in}}$$
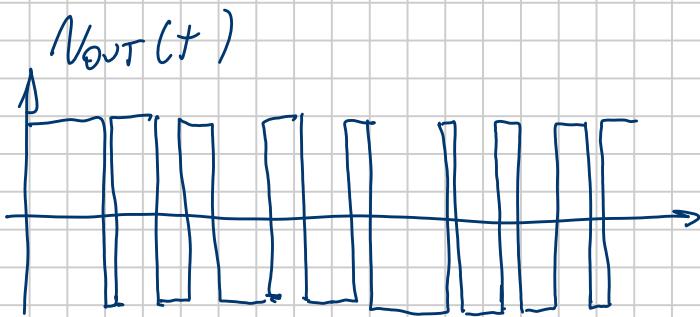
$$\text{if } d_{11}(t) = \frac{1}{2} + \frac{1}{2}m(t)$$



$$V_{out}(t) = \underbrace{\left(2 \frac{d}{T_S} - 1\right) V_{in} + \frac{4V_{in}}{T_S}}_{\langle V_{out} \rangle |_{T_S}(t)} \sum_{n=1}^{\infty} \frac{\sin(n\pi d/T_S)}{n} \cos(n\omega_{sw} t)$$

If $T_S \rightarrow 0$ then

$$V_{out}(t) = \left(2d_{11} - 1\right) V_{in} + \frac{4V_{in}}{T_S} \sum_{n=1}^{\infty} \frac{\sin(n\pi d_{11})}{n} \cos(n\omega_{sw} t)$$


$$V_{out}(t) = m(t) V_{in} + \frac{4V_{in}}{T_S} \sum_{n=1}^{\infty} \frac{\sin\left(n\pi\left(\frac{1}{2} + \frac{m(t)}{2}\right)\right)}{n} \cos(n\omega_{sw} t)$$


Fundamental



$$V_{out,1}(t) = m V_{in} \cos \omega_{sw} t$$


harmonic content

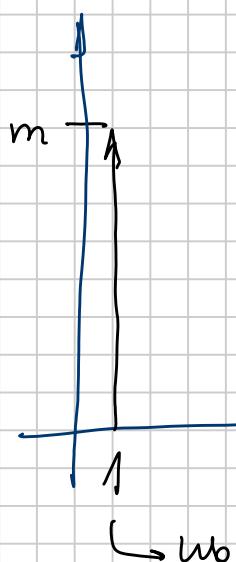For T_S small (h large) both NPWM and UPWM yields the same spectrum for V_{out}




Spectrum for V_{out}

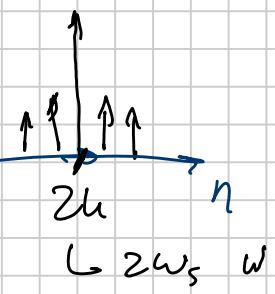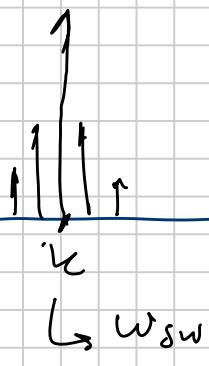

In reality \rightarrow NPWN \rightarrow it is more difficult to implement
but doesn't have harmonics around the fundamental (ω_0)

\rightarrow UPW \rightarrow it's easier to implement but for low L it yields harmonics around ω_0

How do I filter the unwanted harmonics?

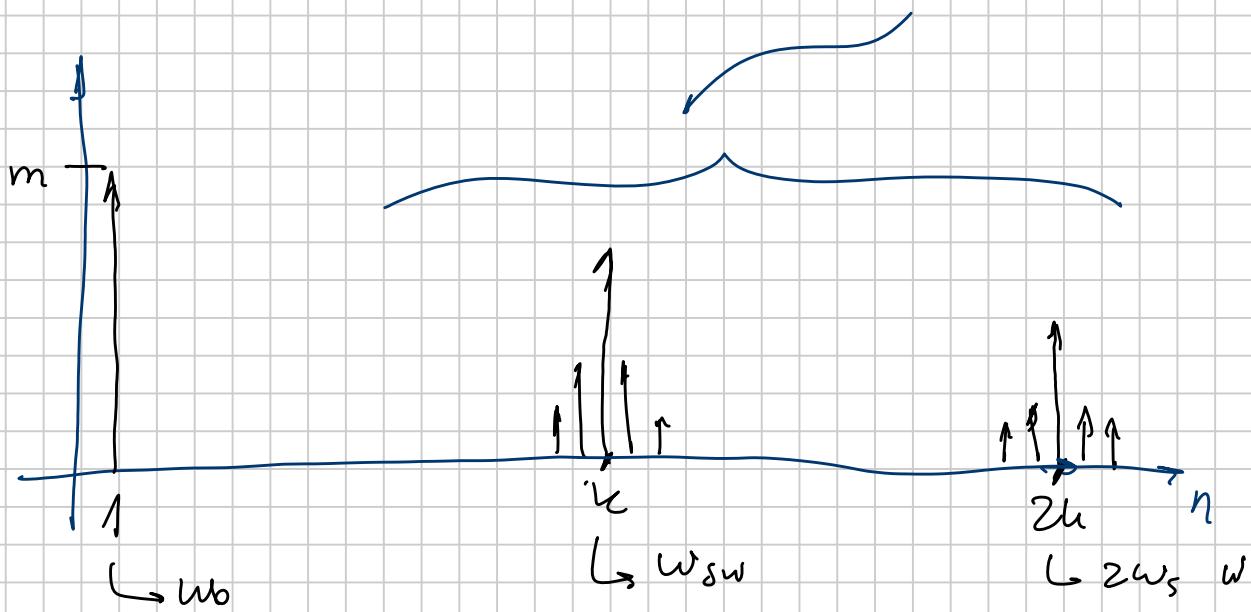


Answer: I use a low-pass filter:




The advantage is that ω_{sw} is away from ω_0 , so I can reduce the size of my filter components by choosing a higher corner frequency.

So the filter looks something like this.

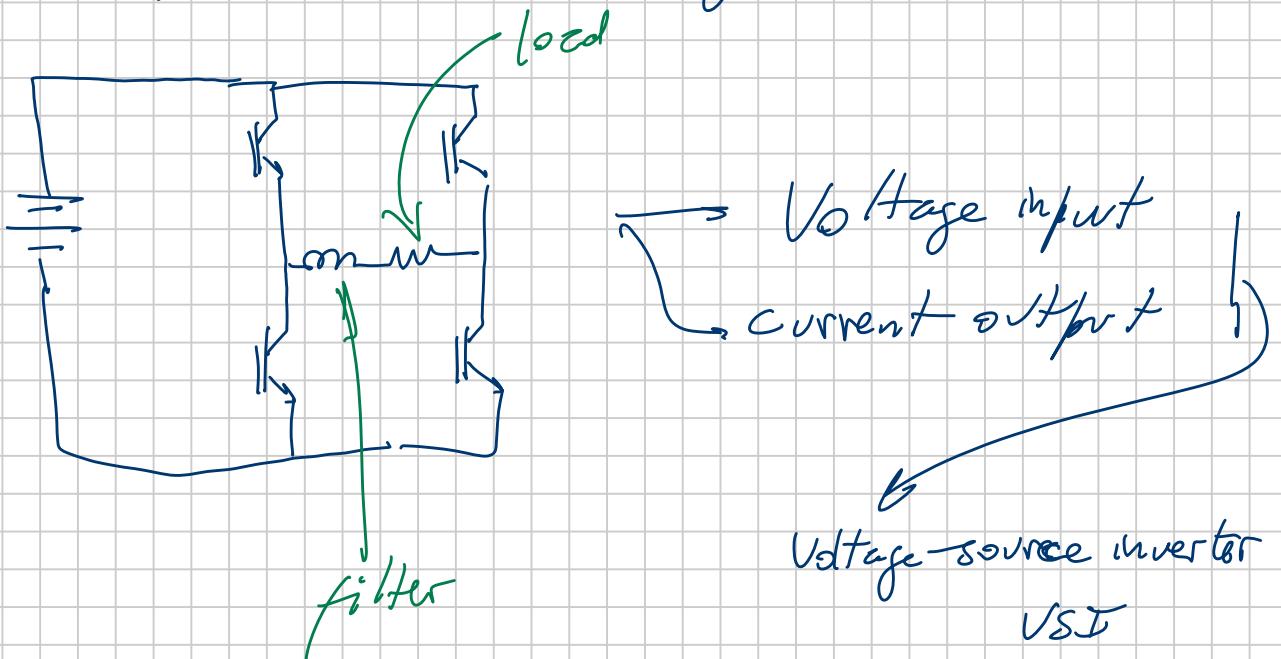

3-phase VSI:

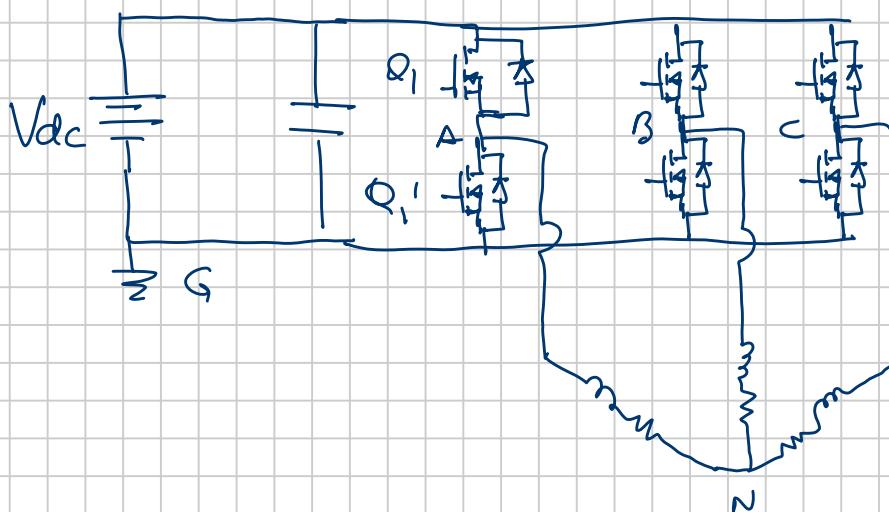

If Q_1 and Q_1' are simultaneously on I have short-through

I need to add standby time

Possible voltages $V_{Aa}, V_{Bb}, V_{Cc} = \begin{cases} V_{dc} \\ 0 \end{cases}$

$$V_{AB}, V_{BC}, V_{CA} = \begin{cases} +V_{dc} \\ -V_{dc} \\ 0 \end{cases}$$

$$V_{AN}, V_{BN}, V_{CN} = \begin{cases} 2/3 V_{dc} \\ +1/3 V_{dc} \\ -1/3 V_{dc} \\ 2/3 V_{dc} \end{cases}$$

$$V_{AS} = \begin{cases} V_{dc} & \text{with } Q_1 = \text{on} \\ 0 & \text{with } Q_1 = \text{off} \end{cases}$$

$$V_{AS \text{ fund}}(t) = f_{11}(t) V_{dc} = \left(\frac{1}{2} + \frac{1}{2} m_a(t) \right) V_{dc}$$

↳ fundamental

In 3 phase systems: $m_a(t) = m \cos \omega_0 t$

$$m_b(t) = m \cos(\omega_0 t - \frac{2\pi}{3})$$

$$m_c(t) = m \cos(\omega_0 t + \frac{2\pi}{3})$$

$$V_{AB \text{ fund}} = V_{A \text{ fund}} - V_{B \text{ fund}} = \left\{ \frac{1}{2} [m_a(t) - m_b(t)] \right\} V_{dc} =$$

\uparrow
line voltage

$$= \left\{ \frac{1}{2} m \left[\cos \omega_0 t - \cos \left(\omega_0 t - \frac{2\pi}{3} \right) \right] \right\} \frac{V_{dc}}{\sqrt{3}}$$

$$= \frac{1}{2} m V_{dc} \sqrt{3} \cos \left(\omega_0 t + \frac{\pi}{6} \right)$$

$$V_{AB \text{ fund peak}} = \frac{\sqrt{3}}{2} m V_{dc} \quad \Rightarrow \quad m = \frac{V_{AB \text{ fund peak}}}{\sqrt{3} \frac{V_{dc}}{2}}$$

$$m = \frac{V_{AB \text{ fund peak}}}{\sqrt{3} \frac{V_{dc}}{2}} = \frac{-\sqrt{2} V_{AB \text{ fund rms}}}{\sqrt{3} \frac{V_{dc}}{2}} = \frac{\sqrt{2} V_{AB \text{ fund rms}}}{\frac{V_{dc}}{2}}$$


$$m = \frac{V_{AB \text{ fund peak}}}{\frac{V_{dc}}{2}}$$

→ half the gain
than a 1-phase
converter

Still we have a VSI \Rightarrow Voltage input, current output

Other topologies are:

- Current source interface (CSI)

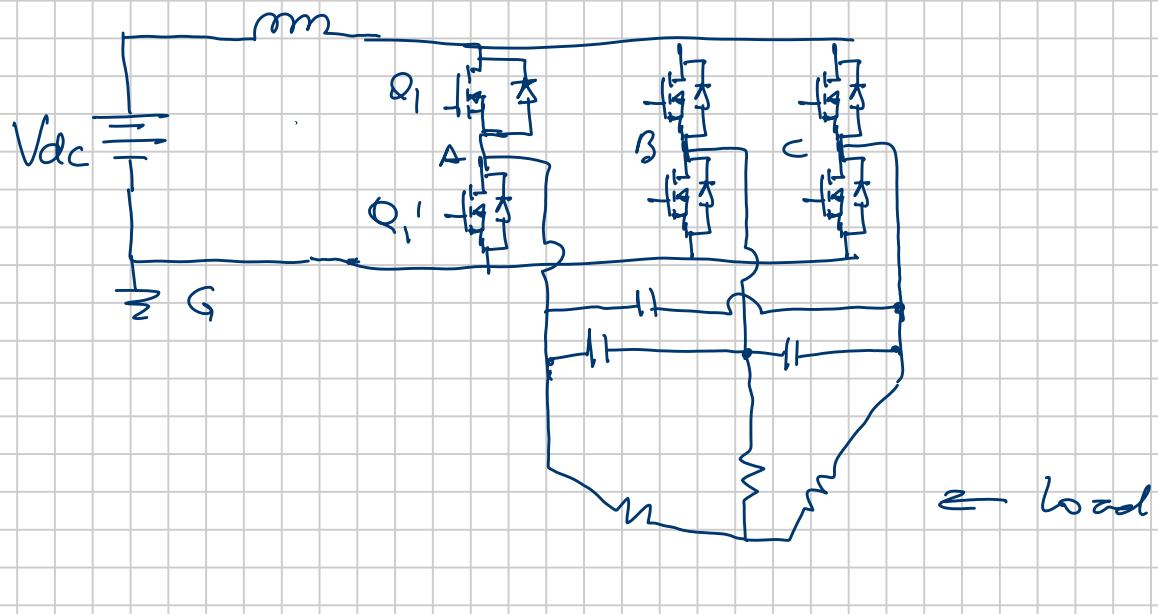

504

IEEE TRANSACTIONS ON INDUSTRY APPLICATIONS, VOL. 39, NO. 2, MARCH/APRIL 2003

Z-Source Inverter

Fang Zheng Peng, Senior Member, IEEE

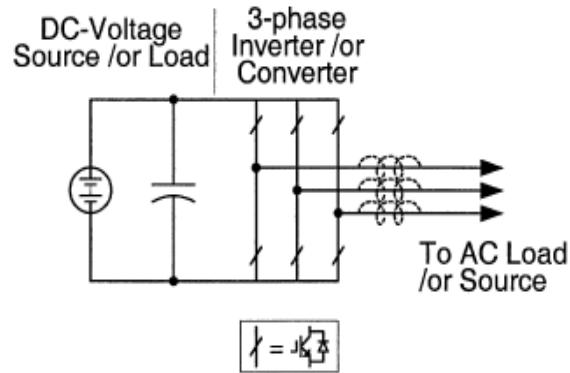


Fig. 1. Traditional V-source converter.

→ only reduces the input voltage

→ inconvenient output filter

→ only boost input voltage

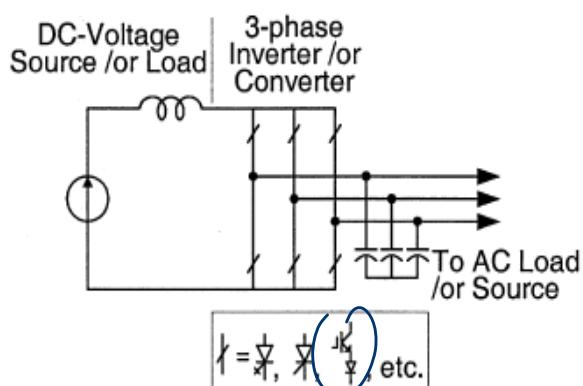


Fig. 2. Traditional I-source converter.

→ requires additional diode to block

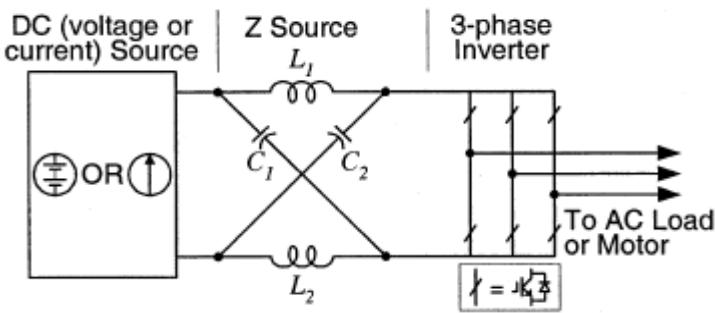


Fig. 4. Z-source converter structure using the antiparallel combination of switching device and diode.

Impedance source converter
→ ZSI

Can both buck and boost voltage

Boost factor → depends on the ratio between shoot-through and non-shoot-through states

$$V_{out \text{ fund freq ph}} = mB \frac{V_{dc}}{2}$$

mod index

$$mB = B_3$$

Buck-Boost factor

Can vary between 0.1

2:1 range

in fuel cells

typical dc link voltage

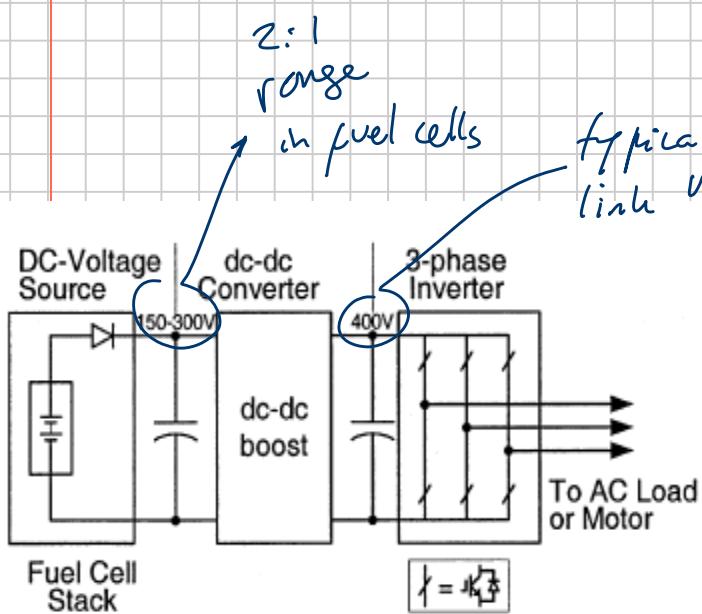


Fig. 6. Traditional two-stage power conversion for fuel-cell applications.

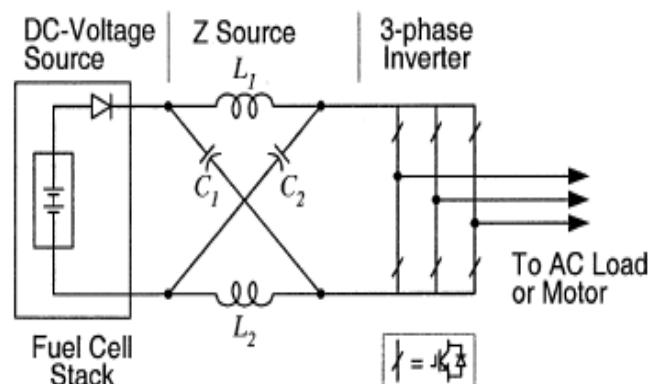


Fig. 7. Z-source inverter for fuel-cell applications.

