


MPP

Note Title

11/6/2011


The maximum power point (MPP) problem in PV applications

Consider the following:

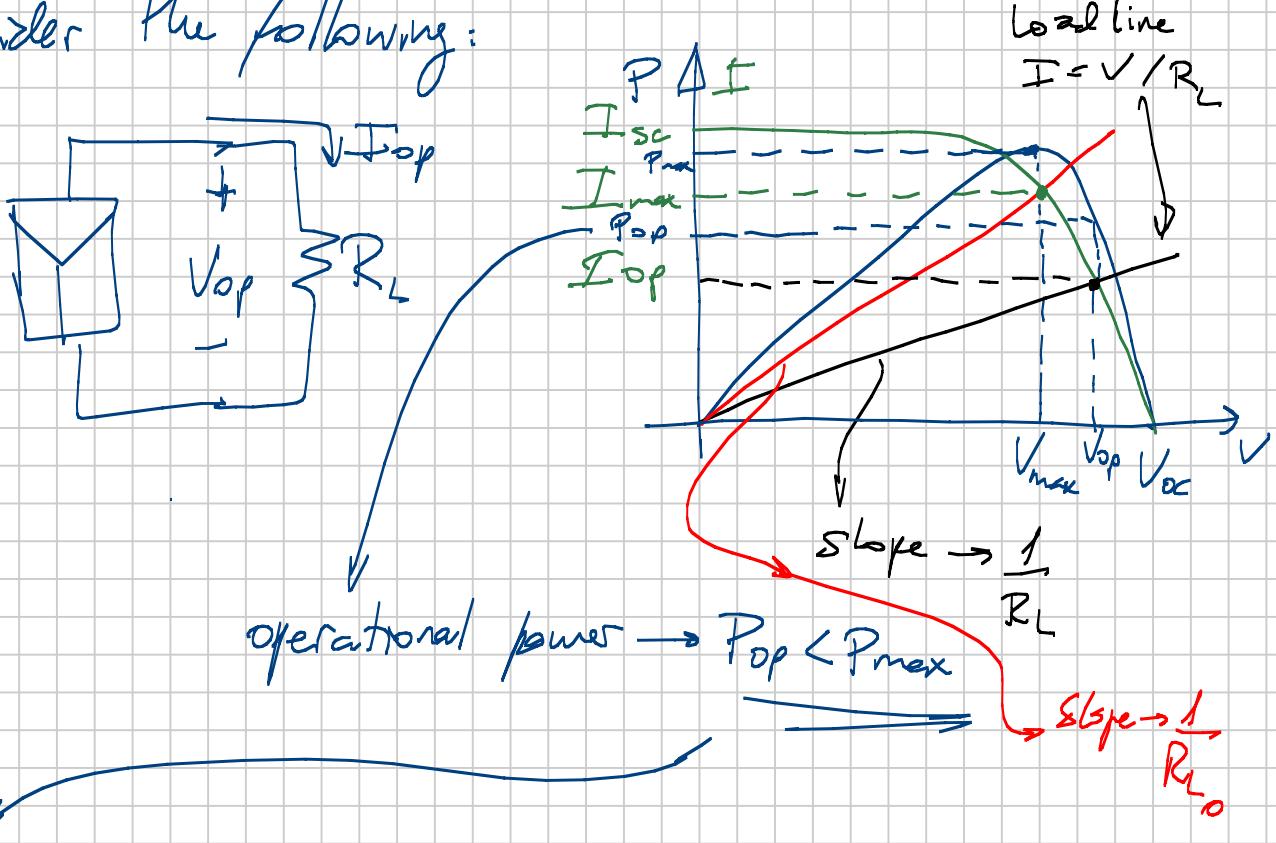

But I want to operate the PV panel at its maximum.

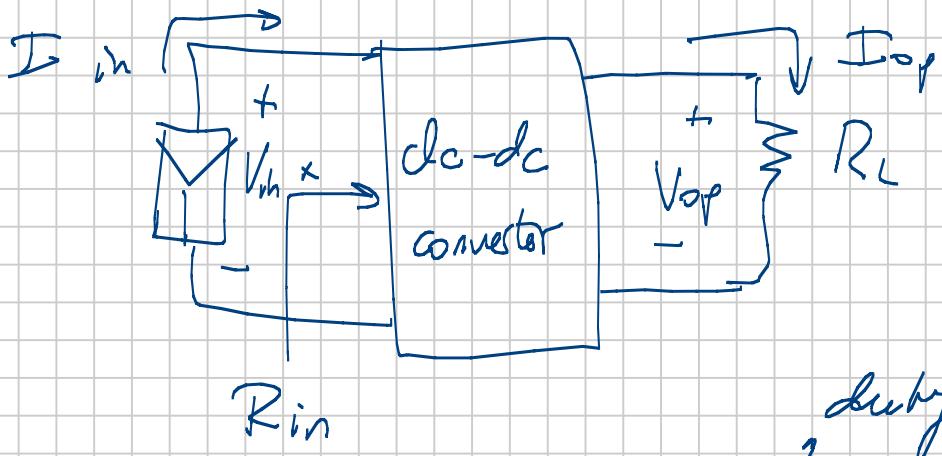So I use a dc-dc converter to "trick" the PV panel into believing it has a load resistance R_{L0} connected to its terminal instead of the actual load resistance R_L .



Since $R_{in} = f(R_L \text{ and } d)$ The idea is to find the duty cycle that makes $R_{in} = R_{L0}$

So consider a buck converter

$$\left. \begin{array}{l} V_{out} = V_{in} D \\ I_{out} = \frac{I_{in}}{D} \end{array} \right\} R_L = \frac{V_{out}}{I_{out}}$$

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{V_{out}}{D} \frac{1}{I_{out} D} = \frac{R_L}{D^2}$$


$$\text{For } R_{in} = R_{L0} = \frac{V_{max}}{I_{max}} \rightarrow D_0 = \sqrt{\frac{R_L}{R_{L0}}}$$

Since $0 < D < 1$ and $R_L = R_{L0} D_0^2$


$$R_L < R_{L0}$$

So a buck converter can only achieve the MPP for $R_{L0} > R_L$

Another problem of such converters

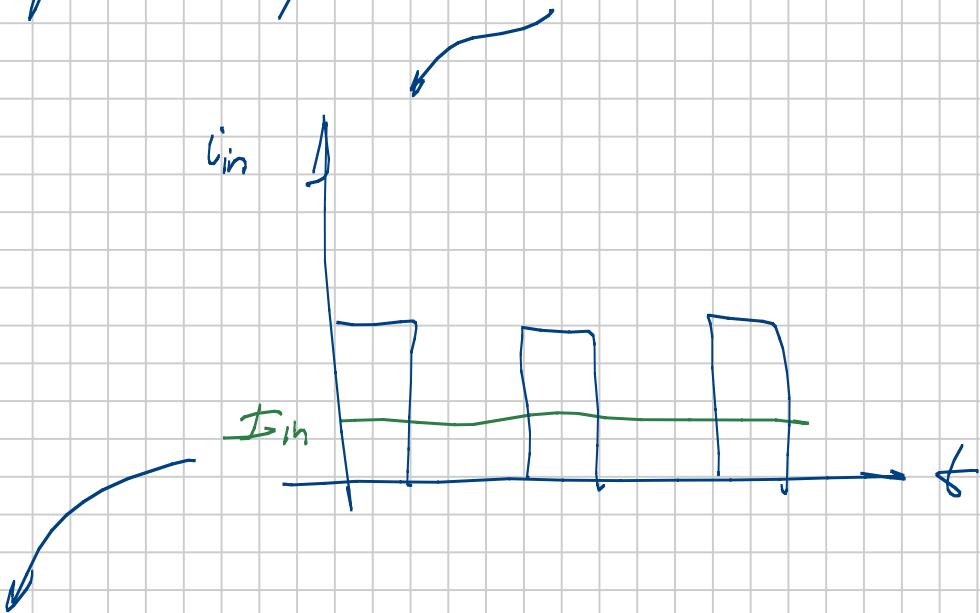

It can only achieve the MIP in average

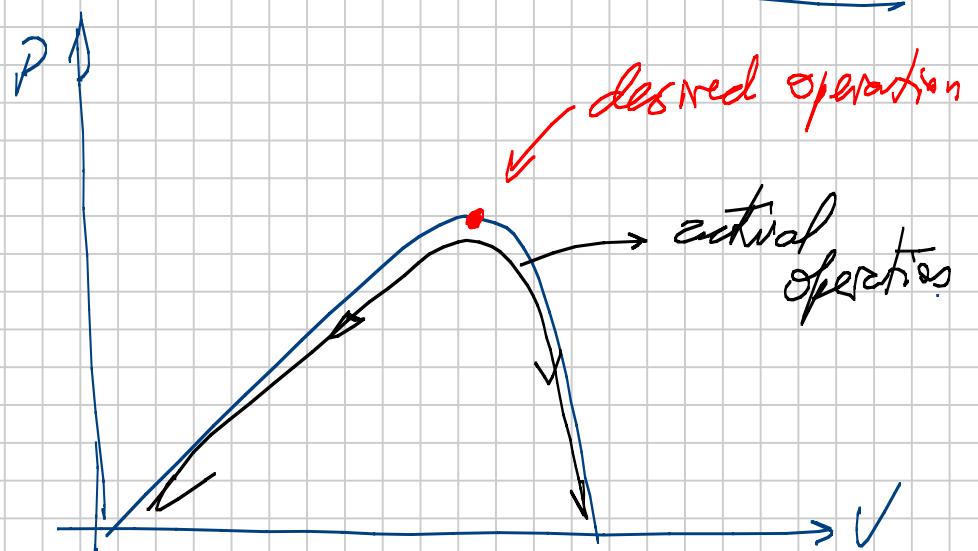

Consider now a boost converter.

$$V_{out} = \frac{V_{in}}{1-D}$$

$$I_{out} = I_{in}(1-D)$$

$$\left\{ R_L = \frac{V_{out}}{I_{out}}$$

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{V_{out}(1-D)}{I_{out}(1-D)} = R_L (1-D)^2$$

$$\text{For } R_{in} = R_{Lo} \longrightarrow R_{Lo} = R_L (1-D)^2$$



$$\text{Since } 0 < D < 1$$



$$0 < (1-D) < 1$$

So the boost converter can only achieve the MLI
for $R_L > R_{Lo}$

At least the boost converter input current is
not switched so the the MLI is achieved
almost exactly

- Consider the static, Cuk or buck-boost converters

$$V_{out} = \frac{D V_{in}}{1-D}$$

$$I_{out} = \frac{(1-D) I_{in}}{D}$$

$$R_{Lo} = \frac{V_{out}}{I_{out}}$$

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{(1-D)^2}{D^2} \frac{V_{out}}{I_{out}} = \frac{(1-D)^2}{D^2} R_L$$

For $R_{in} = R_{out} \rightarrow D = \bar{D}$

$$R_{out} = \frac{(1-D)^2}{D^2} R_L$$

So, ideally, the SEPIC, Cuk or buck-boost converters can achieve the MPP for all R_L between 0 and ∞ . (can R_L be, actually, 0 or ∞ ? Do we have other constraints?)

Although the three of them seem equivalent, they are not \rightarrow the buck-boost have switched input current so often only achieve the MPP in average

The output of a Cuk converter is inverted.

Additional discussion on limitations when implementing MPPT can be gathered from:

Maximum Power Point Tracking Feasibility in Photovoltaic Energy-Conversion Systems

So the question now is how do we control the dc-dc converter to achieve the MPP?

There are several methods for this. First, let's explore the problem from a classical mathematical approach. That is, if I am looking for the maximum power point then I am looking for the point where $\frac{dP}{dV} = 0$

For the next discussion I am considering the paper:

Analysis of Classical Root Finding Methods Applied to Digital Maximum Power Point Tracking for Sustainable Photovoltaic Energy Generation

Seunghyun Chun, Student member, IEEE, and Alexis Kwasinski, Member, IEEE¹

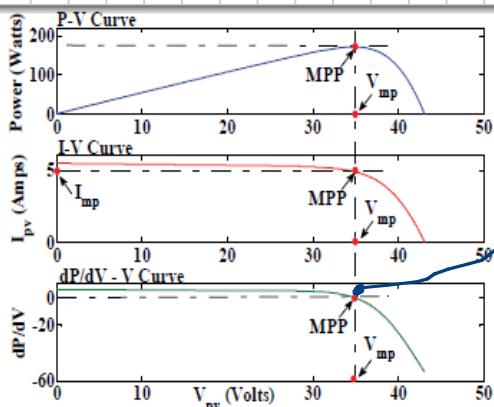


Figure 6: Maximum Power Point for different curves of a PV module.
Figure 7: Irradiance effect on P-V Characteristic at Constant Temperature(25°C).

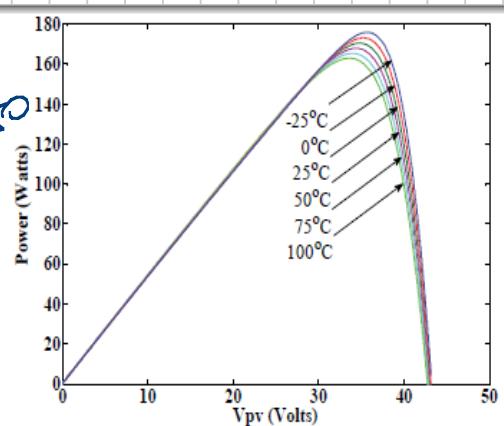


Figure 4: Temperature Effect on P-V Characteristic at constant irradiance (1000W/m²).

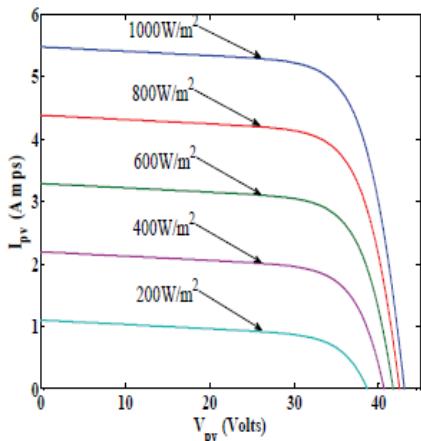


Figure 3: Irradiance effect on I-V Characteristic at Constant Temperature (25°C).

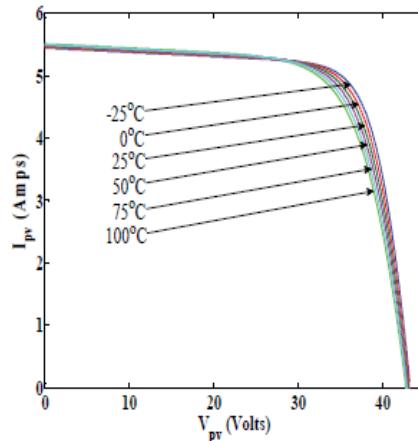


Figure 5: Temperature Effect on I-V Characteristic at constant irradiance (1000W/m²).

$$\frac{dP}{dT}$$

If we need to find the point where $\frac{df}{dx} = 0$, then

The MPP controller just need to find a root:

Some methods to finding a root:

2) Newton-Raphson

Let $f(v) = \frac{df}{dv}$ and v^* be the voltage at the MPP

then we perform iterations of

$$v_{n+1} = v_n - \frac{f(v_n)}{f'(v)}$$


until

$$|f(v_i)| < \epsilon$$


↓
↳ tolerance

then v_i is considered to be v^*

In graphic way:

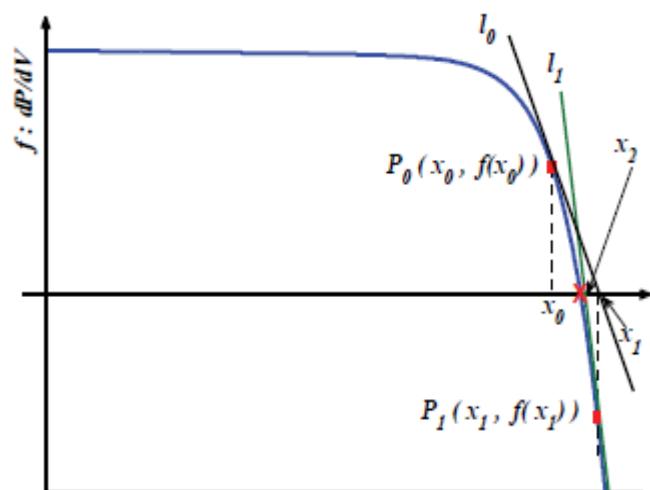

Problem \rightarrow convergence

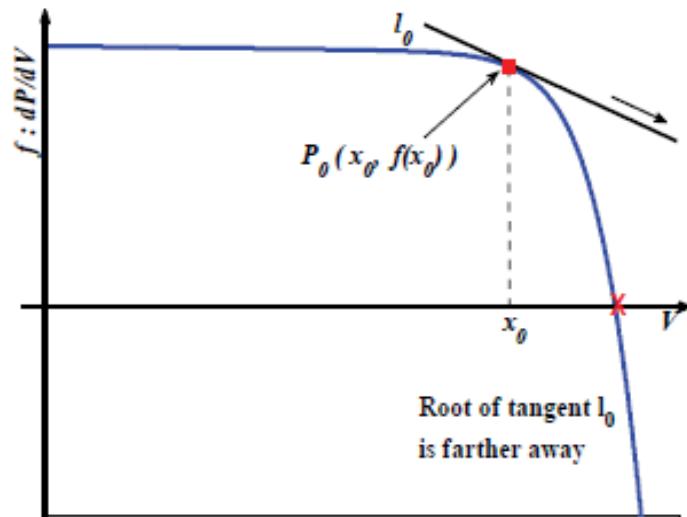

b) Secant Method

The algorithm is now:

$$V_{n+1} = V_n - \frac{f(V_n)}{f(V_n) - f(V_{n-1})} \left(\frac{V_n - V_{n-1}}{f(V_n) - f(V_{n-1})} \right)$$

So I consider 2 steps now

So convergence is faster

But it is not ensured

c) Bisection method



(i) Given a well-defined function $f(x)$, choose a lower value x_l and an upper value x_u . These two points define an interval $[x_l, x_u]$ that must include the root x^* of $f(x)$. That is, $f(x)$ has opposing signs in x_l and x_u , e.g. $f(x_l)f(x_u) < 0$.


(ii) Approximate the root to the midpoint x_m of the interval $[x_l, x_u]$. That is

$$x_m = \frac{x_u + x_l}{2} \quad (6)$$

(iii) If $f(x_l)f(x_m) < 0$ then set $x_u = x_m$ and repeat the previous step. If $f(x_l)f(x_m) > 0$ then set $x_l = x_m$ and repeat the previous step. If $|f(x_m)| \leq \varepsilon$ (where ε is the tolerance) then take x_m as the root or approximation.


The BSM convergence rate is slower than the SM. Yet, with the BSM root convergence is guaranteed.

\rightarrow Secant method

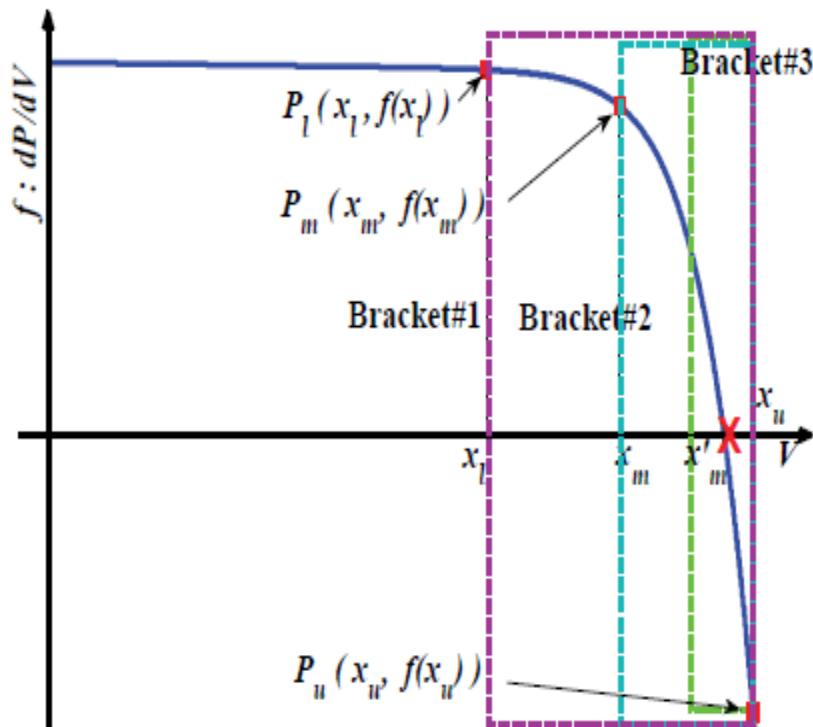

d) Regula Falsi:

- (i) Given a continuous function $f(x)$ find initial points x_l and x_u , such that $x_l \neq x_u$ and $f(x_l) \cdot f(x_u) < 0$. Hence, according to the intermediate value theorem the root of $f(x)$ is located inside the interval $[x_l, x_u]$.
- (ii) Calculate the approximate value for the root c_i with (7)
- (iii) If $|f(c_i)| \leq \varepsilon$ (where ε is the tolerance) then it is considered that the root have been reached and that c_i is the root. Else, if $f(c_i) \cdot f(x_u) < 0$ then let $x_l = c_i$, else if $f(c_i) \cdot f(x_l) < 0$ then let $x_u = c_i$. These changes yield a smaller interval.
- (iv) Iterate steps (ii) and (iii) until the root is reached.

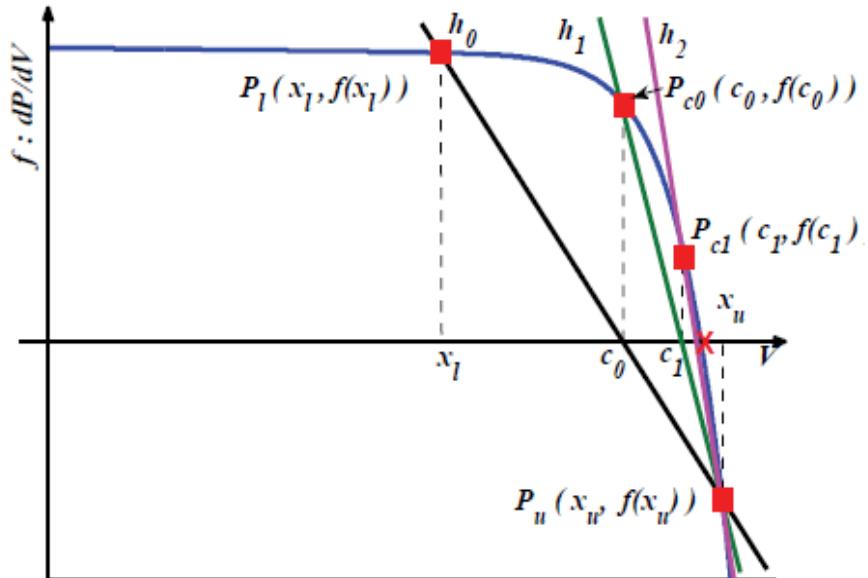

e) Modified Regula Falsi:


We replace in method (d) step (ii) by:

- (ii) If $f(x_l) \cdot f(x_u) < 0$ and $f(x_l) > 0$ then $f(x_u)$ is replaced in (7) by $f_p(x_u) = \frac{f(x_u) + f(x_l)}{2}$ and $f_p(x_l) = f(x_l)$

$$c_i = \frac{x_l \cdot f_p(x_u) - x_u \cdot f_p(x_l)}{f_p(x_u) - f_p(x_l)} = \frac{x_l \cdot f(x_u) \cdot 0.5 - x_u \cdot f(x_l)}{0.5 \cdot f(x_u) - f(x_l)}, \quad (8)$$

If $f(x_l) \cdot f(x_u) < 0$ and $f(x_l) < 0$ then $f(x_l)$ is replaced in (7) by $f_p(x_l) = \underline{f(x_l)/2}$ and $f_p(x_u) = f(x_u)$
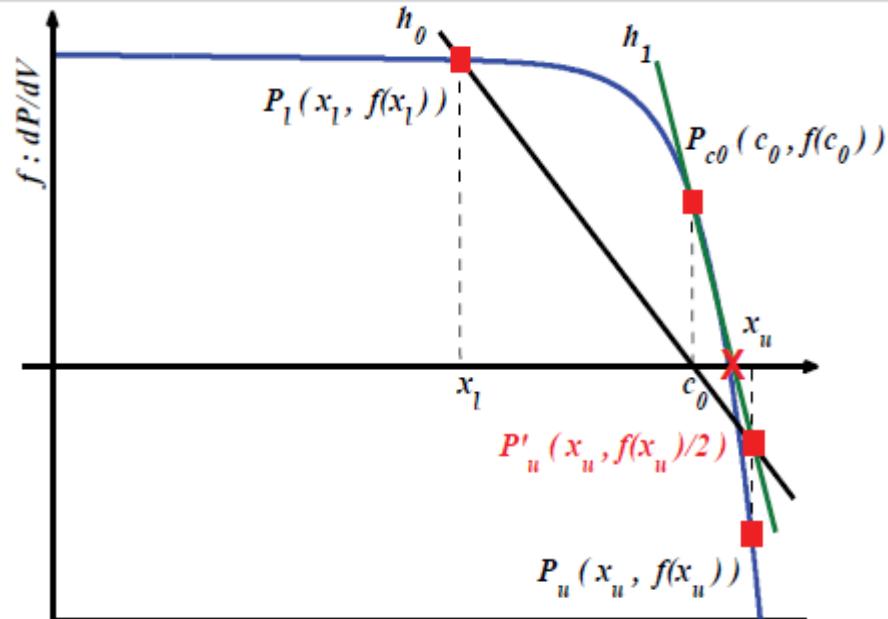
$$c_i = \frac{x_l \cdot f_p(x_u) - x_u \cdot f_p(x_l)}{f_p(x_u) - f_p(x_l)} = \frac{x_l \cdot f(x_u) - x_u \cdot f(x_l) \cdot 0.5}{f(x_u) - 0.5 \cdot f(x_l)}, \quad (9)$$



How do we implement all these methods → digitally.

Other methods.

Several methods are summarized here.


Comparison of Photovoltaic Array Maximum Power Point Tracking Techniques

Trishan Esram, *Student Member, IEEE*, and Patrick L. Chapman, *Senior Member, IEEE*

TABLE III
MAJOR CHARACTERISTICS OF MPPT TECHNIQUES

MPPT Technique	PV Array Dependent?	True MPPT?	Analog or Digital?	Periodic Tuning?	Convergence Speed	Implementation Complexity	Sensed Parameters
Hill-climbing/P&O	No	Yes	Both	No	Varies	Low	Voltage, Current
InCond	No	Yes	Digital	No	Varies	Medium	Voltage, Current
Fractional V_{OC}	Yes	No	Both	Yes	Medium	Low	Voltage
Fractional I_{SC}	Yes	No	Both	Yes	Medium	Medium	Current
Fuzzy Logic Control	Yes	Yes	Digital	Yes	Fast	High	Varies
Neural Network	Yes	Yes	Digital	Yes	Fast	High	Varies
RCC	No	Yes	Analog	No	Fast	Low	Voltage, Current
Current Sweep	Yes	Yes	Digital	Yes	Slow	High	Voltage, Current
DC Link Capacitor Droop Control	No	No	Both	No	Medium	Low	Voltage
Load I or V Maximization	No	No	Analog	No	Fast	Low	Voltage, Current
dP/dV or dP/dI Feedback Control	No	Yes	Digital	No	Fast	Medium	Voltage, Current
Array Reconfiguration	Yes	No	Digital	Yes	Slow	High	Voltage, Current
Linear Current Control	Yes	No	Digital	Yes	Fast	Medium	Irradiance
I_{MPP} & V_{MPP} Computation	Yes	Yes	Digital	Yes	N/A	Medium	Irradiance, Temperature
State-based MPPT	Yes	Yes	Both	Yes	Fast	High	Voltage, Current
OCC MPPT	Yes	No	Both	Yes	Fast	Medium	Current
BFV	Yes	No	Both	Yes	N/A	Low	None
LRCM	Yes	No	Digital	No	N/A	High	Voltage, Current
Slide Control	No	Yes	Digital	No	Fast	Medium	Voltage, Current

= Hill climbing and Perturb and observe

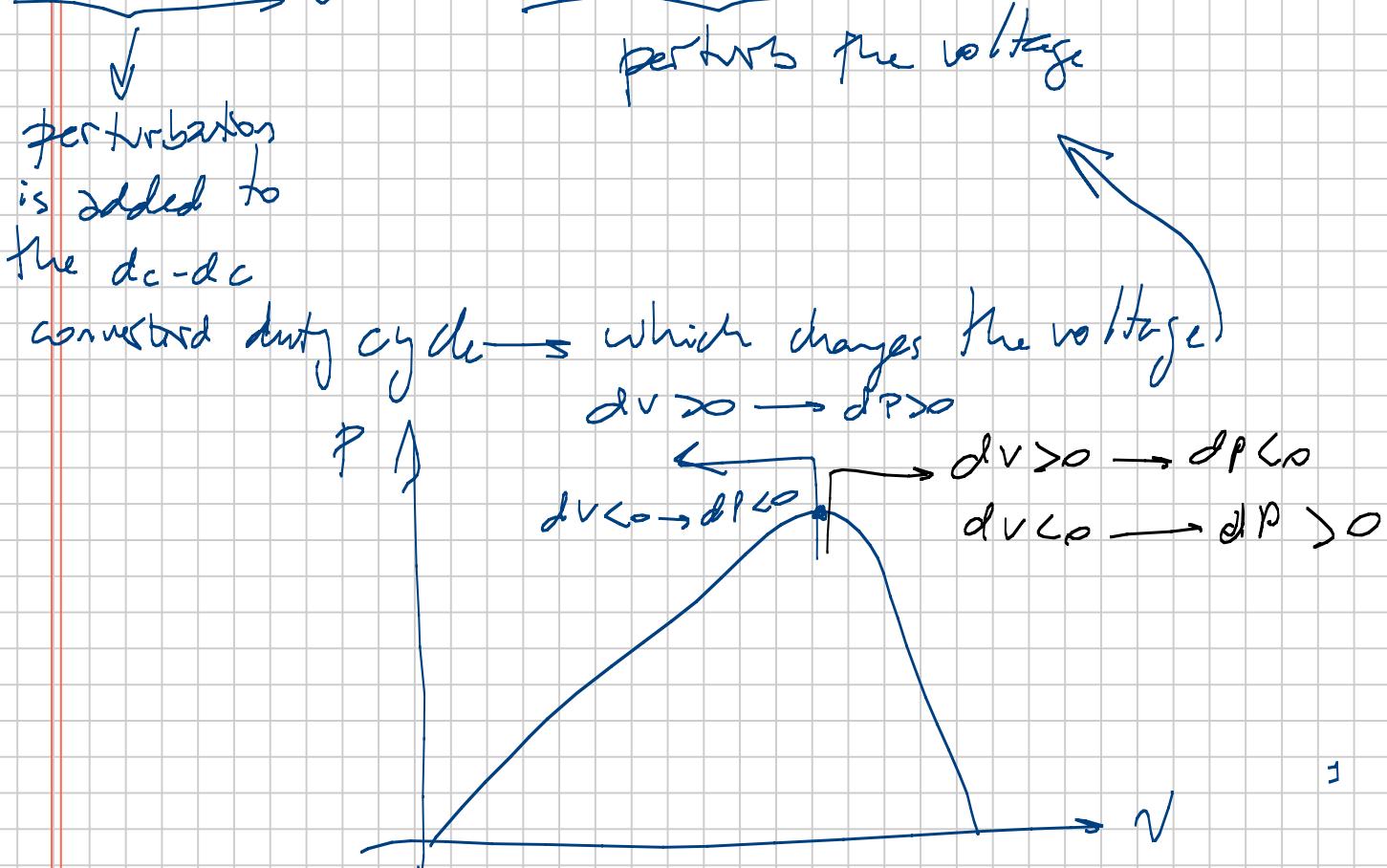

Process:

Whenever $dP > 0 \rightarrow$ perturbation is kept the same

$dP_{\text{Lo}} \rightarrow \dots$ is reversed


Process is repeated until reaching MPP

Problem: oscillates around MPP

Solution \rightarrow choose a smaller step size (\leq smaller perturbation)

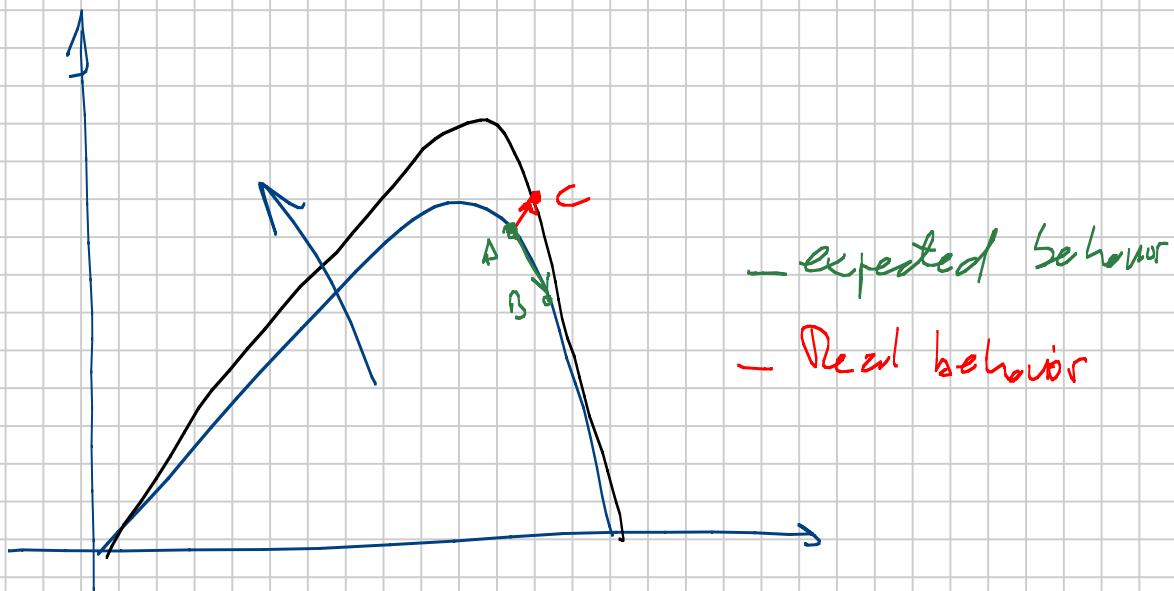Problem \rightarrow smaller step size means slower convergence.

Another problem \rightarrow can fail in rapidly changing weather conditions



— expected behavior $\rightarrow dV > 0 \rightarrow dP_{\text{Lo}}$ so perturbation is reversed

— Actual necessary behavior $\rightarrow dV > 0 \rightarrow dP > 0$ so

perturbation is kept the same

that is $dV \neq 0$

↓
So it moves away
from MPP

— Incremental conductance

Notice that:

$$\left\{ \begin{array}{ll} dP/dV = 0 & \text{at MPP} \\ dP/dV < 0 & \text{right of MPP} \\ dP/dV > 0 & \text{left of MPP} \end{array} \right.$$

$$\text{Now: } \frac{dI}{dV} = \frac{d(IV)}{dV} = I + V \frac{dI}{dV} \approx I + V \frac{\Delta I}{\Delta V}$$

So


$$\left\{ \begin{array}{ll} \Delta I / \Delta V = -I/V & \text{at MPP} \\ \Delta I / \Delta V < -I/V & \text{right of MPP} \\ \Delta I / \Delta V > -I/V & \text{left of MPP} \end{array} \right.$$

Approach #1:

Consider $e = \frac{I}{V} + \frac{dI}{dV}$

$\Delta I / \Delta V \approx 0 \rightarrow$ so we can use
a PI controller to make
 $e = 0$


Approach #2

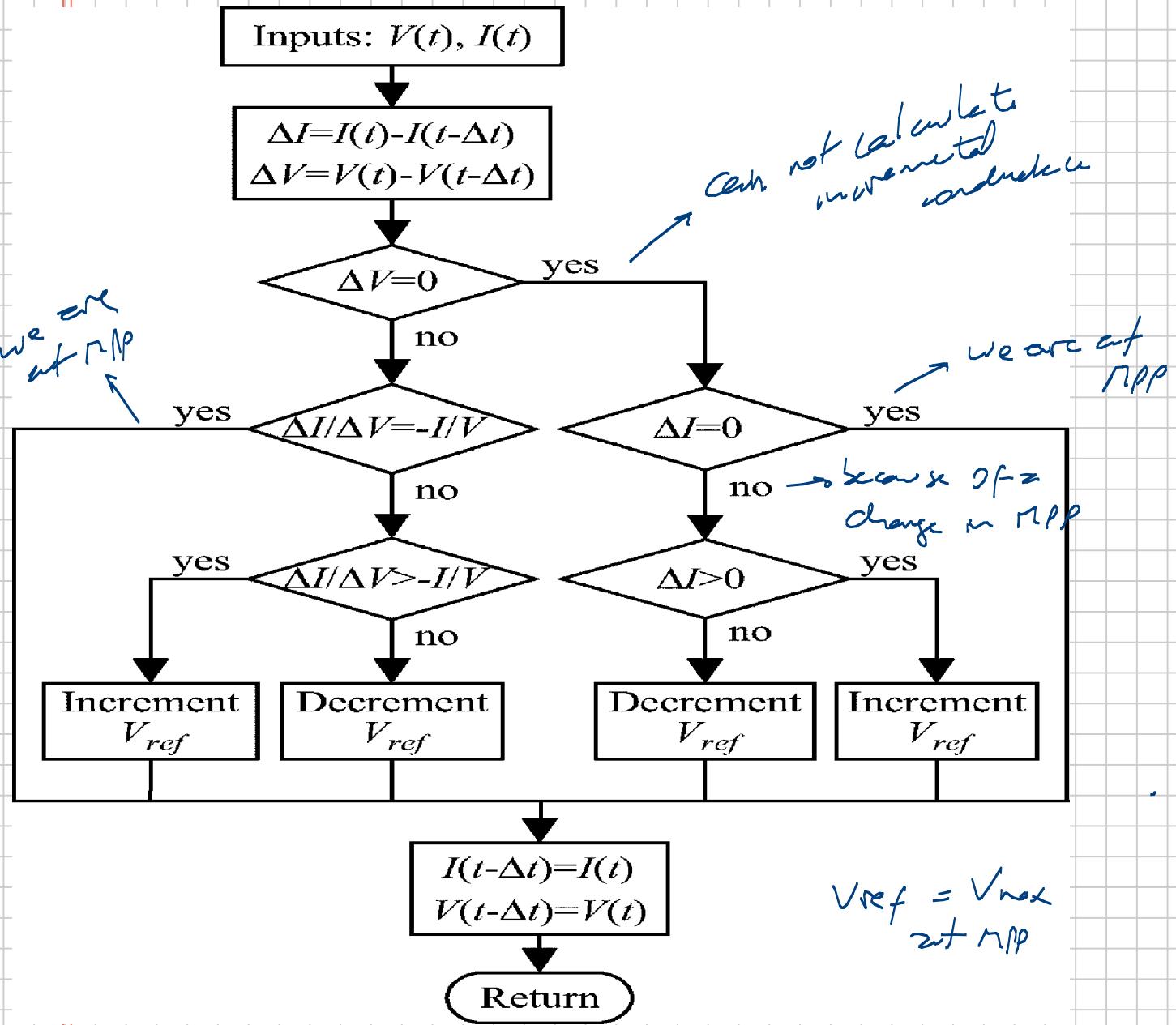


Ripple cancellation control!

i/n to the da-da converter always has some ripple

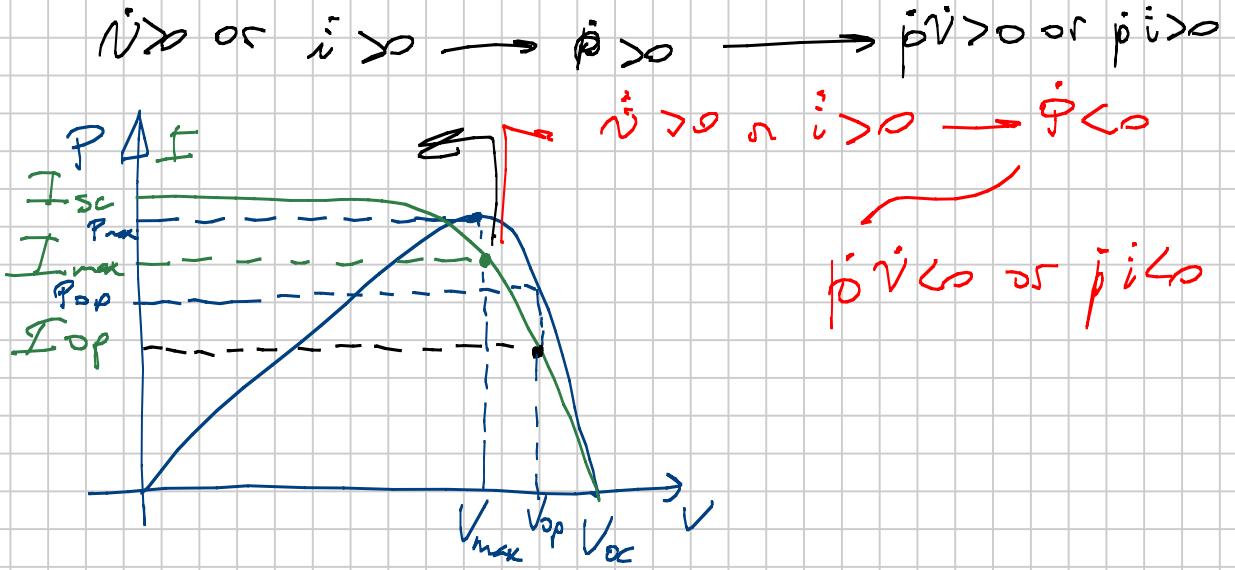this ripple is used to drive the converter
to the PV module MPP



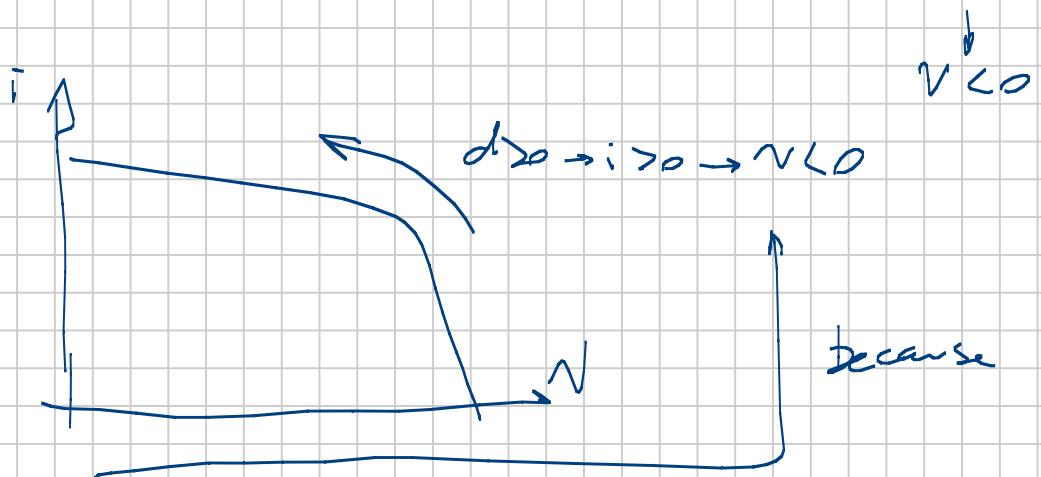Consider a boost converter \rightarrow When $d > 0 \rightarrow i > 0$



So $d(t) = \underbrace{k \int \dot{p}v dt}_{\text{like error signal}} \rightarrow \dot{p}v = 0$

at MPP
because
 $\dot{p} = 0$ at
MPP

or $d(t) = k \int \dot{p}i dt$