


Power electronic circuits modeling

Note Title


8/27/2011

- Switched model

Switching function $\tilde{g}(t)$:

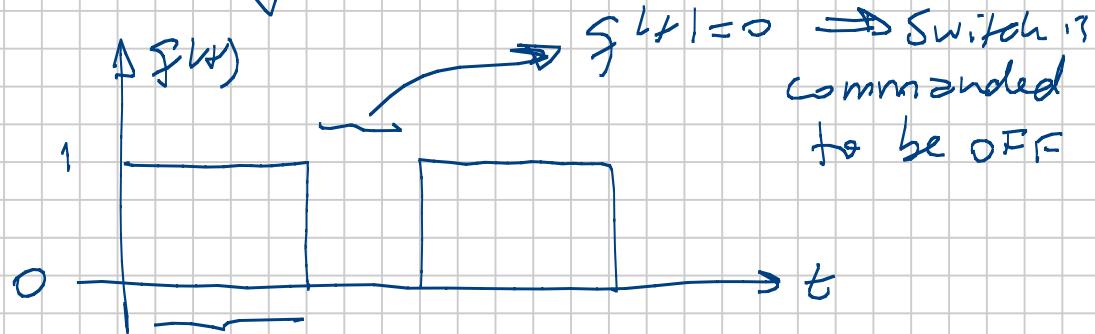

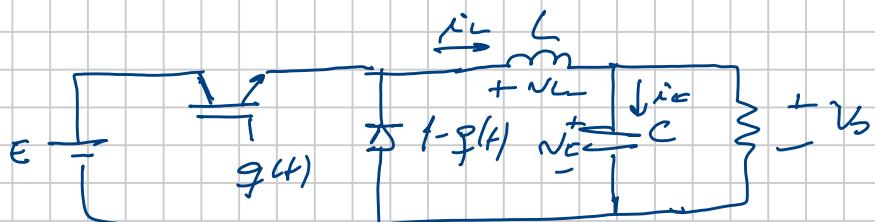
- Consider a buck converter operating in continuous conduction mode (CCM) \rightarrow i.e., $i_L(t) > 0 \forall t \geq 0$



$$i_L = \dot{x}_1$$


$$V_C = x_2$$

\rightarrow I assume ideal components

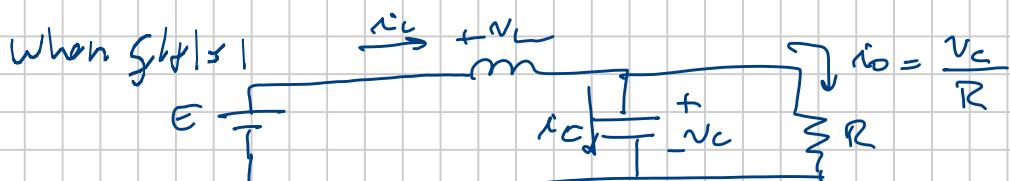

$$\begin{cases} L \dot{x}_1 = E - x_2 \\ C \dot{x}_2 = x_1 - x_2/R \end{cases}$$

when $\tilde{g}(t) = 0$

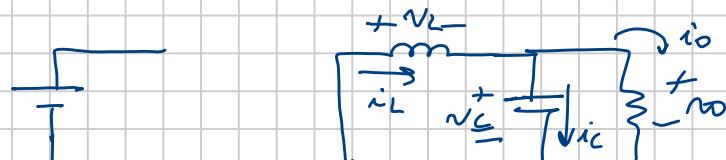


$$\begin{cases} L \dot{x}_1 = -x_2 \\ C \dot{x}_2 = x_1 - x_2/R \end{cases}$$

Hence

$$\begin{cases} L \dot{x}_1 = f(t) \varepsilon - x_2 \\ C \dot{x}_2 = x_1 - \frac{x_2}{R} \end{cases}$$

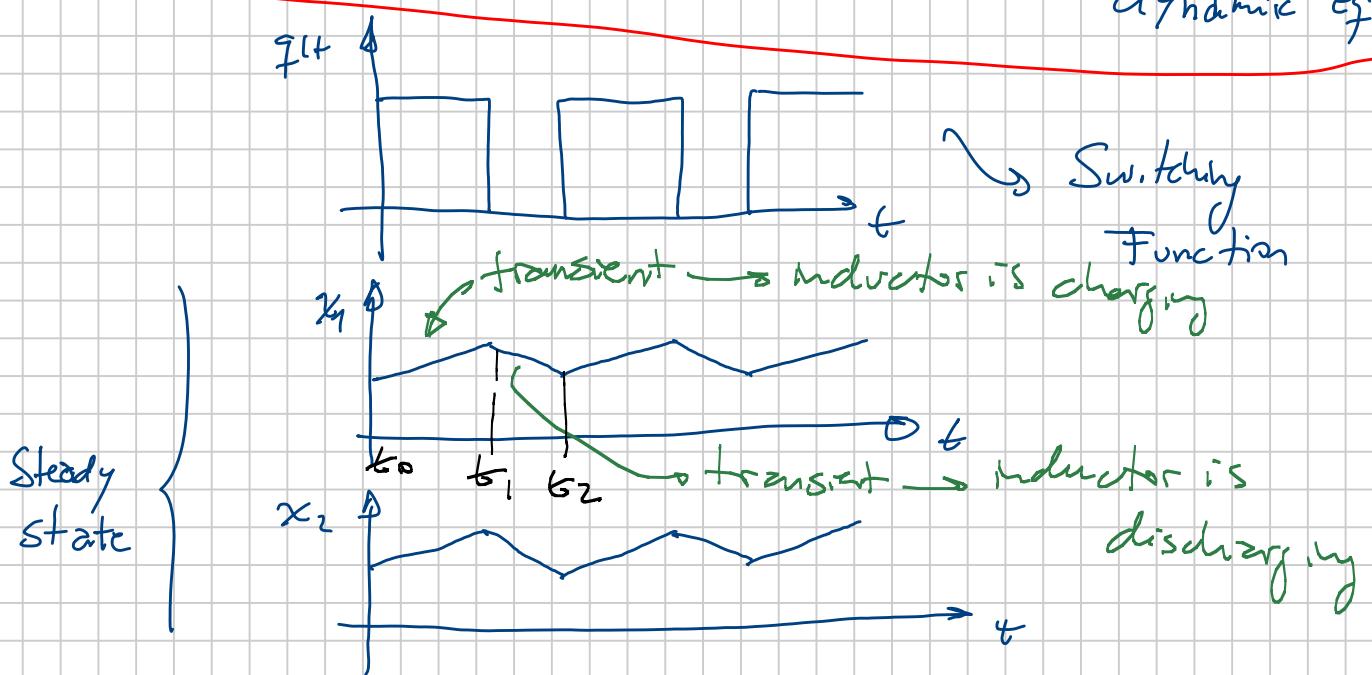(1) \rightarrow Switched system dynamic eqs.



Note that $f(t)$ is non linear. So power electronics circuits are non linear circuits. Because of $f(t)$ in (1) I cannot use Fourier, Laplace or identify impedances.

Steady state is a succession of transient states

That is $x_1(t_0) \neq x_1(t_1)$ and $x_2(t_1) \neq x_2(t_2)$ but
 $x_1(t_0) = x_1(t_2)$
Steady state

Equilibrium points \rightarrow are those points where $\dot{x}_1 = 0$ and $\dot{x}_2 = 0$ (e.g. "velocity" \dot{x} is zero)

$$\text{For } g(t)=1 \rightarrow \begin{cases} 0 = E - x_2 \rightarrow x_{2,0} = E \\ 0 = x_1 - x_2/R \rightarrow x_{1,0} = E/R \end{cases}$$

$$\text{For } g(t)=0 \rightarrow \begin{cases} 0 = -x_2 \rightarrow x_{2,0} = 0 \\ 0 = x_1 - x_2/R \rightarrow x_{1,0} = 0 \end{cases}$$

In matrix form (1) & (2) can be written as:

$$(1) \quad \begin{cases} L\dot{x}_1 = g(t)E - x_2 \\ C\dot{x}_2 = x_1 - \frac{x_2}{R} \end{cases} \rightarrow \mathbf{\Gamma}_0 \dot{\mathbf{x}} = \mathbf{A}\mathbf{x} + \mathbf{B}\mathbf{u}$$


Circuit structure

"inertia" $\leftarrow \mathbf{\Gamma}_0 = \begin{pmatrix} L & 0 \\ 0 & C \end{pmatrix}, \mathbf{A} = \begin{pmatrix} 0 & -1 \\ 1 & -1/R \end{pmatrix}$

$$\text{Based on control input} \rightarrow \mathbf{B} = \begin{pmatrix} E \\ 0 \end{pmatrix}, \mathbf{u} = g(t)$$

$$\text{Based on power input} \rightarrow \mathbf{B} = \begin{pmatrix} g(t) \\ 0 \end{pmatrix}, \mathbf{u} = E$$

- For a boost converter:

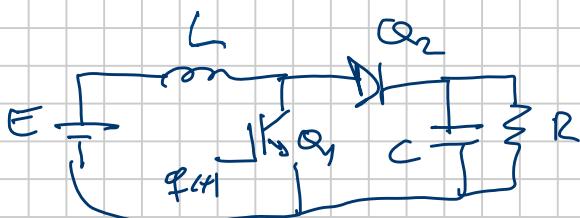

$$g'(t) = 1 - g(t)$$

$$g(t)=1 \quad \begin{cases} L\dot{x}_1 = E \\ C\dot{x}_2 = -\frac{x_2}{R} \end{cases}$$

$$g(t)=0 \quad \begin{cases} L\dot{x}_1 = E - x_2 \\ C\dot{x}_2 = x_1 - \frac{x_2}{R} \end{cases}$$

$$\left\{ \begin{array}{l} L\dot{x}_1 = E - g'(t)x_2 \\ C\dot{x}_2 = g'(t)x_1 - \frac{x_2}{R} \end{array} \right.$$

switched model






Equilibrium points:

$$f(t+)=1 \rightarrow \begin{cases} 0 = E (?) \rightarrow \text{There is no equilibrium} \\ 0 = -\frac{x_2}{R} \end{cases}$$

If I leave the switch closed $x_1 \rightarrow \infty$

$$f(t+)=0 \rightarrow \begin{cases} 0 = E - x_2 \rightarrow x_{z_{02}} = E \\ 0 = x_1 - \frac{x_2}{R} \rightarrow x_{1_{z_{02}}} = \frac{E}{R} \end{cases}$$

Buck-boost converter

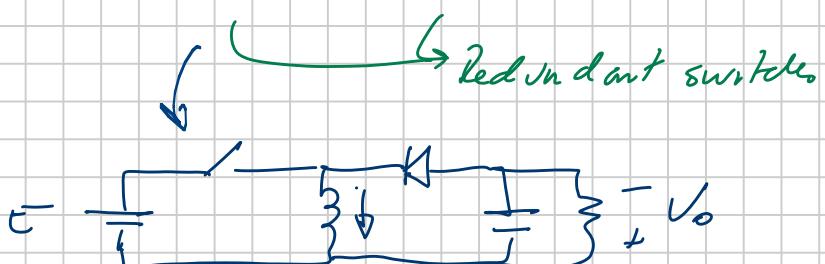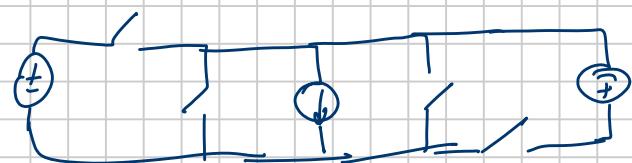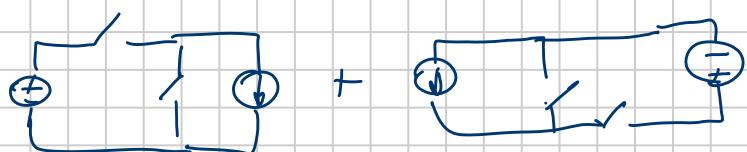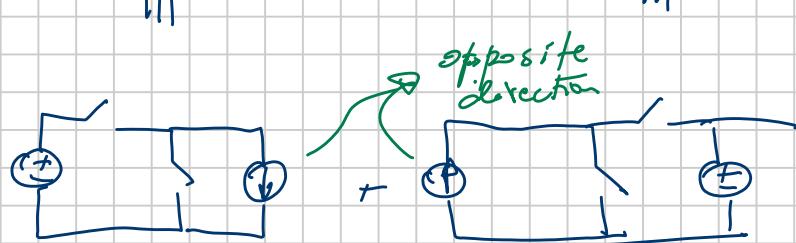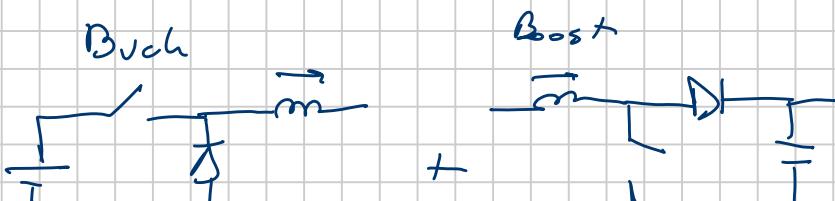

$$\begin{cases} L \dot{x}_1 = g^1(t) E - g^1(t) x_2 \\ C \dot{x}_2 = g^2(t) x_1 - \frac{x_2}{R} \end{cases}$$

Equilibrium points:


$$g^1(t) = 0 \rightarrow \begin{cases} 0 = E \quad (?) \\ x_{201} = 0 \end{cases}$$

Analogous to the same condition in the boost converter

$$g^2(t) = 0 \rightarrow \begin{cases} 0 = -x_2 \rightarrow x_{202} = 0 \\ 0 = x_1 - \frac{x_2}{R} \rightarrow x_{102} = 0 \end{cases}$$

Fly back converter

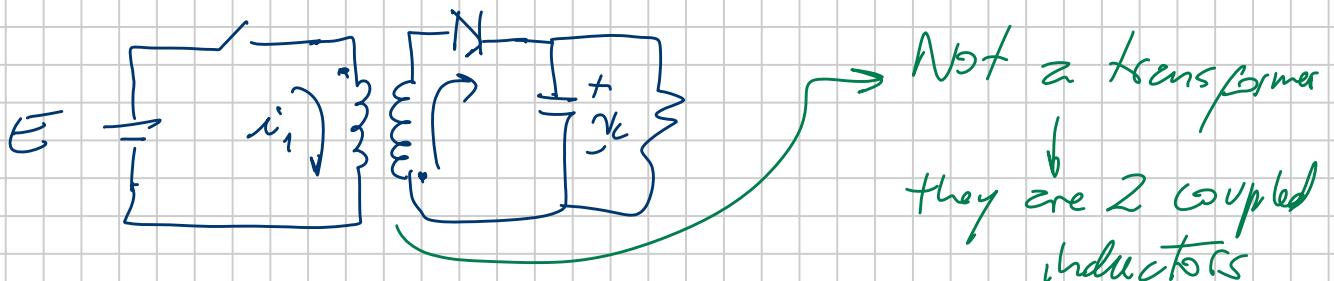From the buck-boost converter let's split the inductor in two coupled inductors



$$\frac{d\phi}{dt} = \frac{V_1}{N_1} = \frac{V_2}{N_2}$$

$$\phi = A_L (i_1 N_1 + i_2 N_2) \quad \text{general form}$$

permeance

$$A_L = \frac{l}{R} \quad \text{Reductance}$$

$$\phi l = I$$

$\hookrightarrow N_i$

\hookrightarrow ohm's law for a magnetic circuit

So ϕ plays the role of an inductor current $\phi R = Ni$

$$\frac{d\phi}{dt} = \frac{gE}{N_1} - g' \frac{V_C}{N_2}$$

$$Cd\frac{V_C}{dt} = \frac{g'\phi}{A_L N_2} - \frac{1}{R} V_C$$

$i_2 \neq 0$ when $i_1 = 0$

This is why it can't be considered a transformer

So when the diode is conducting we have that

$$\phi = A_L i_2 N_2 \rightarrow i_2 = \frac{\phi}{A_L N_2}$$

otherwise the general form should be valid.

$$\text{If } \phi = x_1 \text{ and } V_C = x_2 \rightarrow$$

$$\begin{cases} \dot{x}_1 = \frac{gE}{N_1} - \frac{g'x_2}{N_2} \\ \dot{x}_2 = \frac{g'x_1}{A_L N_2} - \frac{x_2}{R} \end{cases}$$

Fast average model

Fast average operator $\bar{f}(t) = \frac{1}{T_{sw}} \int_t^{t+T_{sw}} f(y) dt$

$$\boxed{\bar{f}(t) = \frac{1}{T_{sw}} \int_t^{t+T_{sw}} f(y) dt}$$

this is a linear

An operator is a machine

operator

What kind of machine is this?

If I apply zplane transform on both sides I obtain that $\bar{F}(s)$ is proportional to $\frac{F}{s}$

- Since $\frac{F}{S}$ is indicative of a low-pass filter
 the fast average operator acts as a low-pass filter

So when I apply the fast average operator to the switching function I obtain the instantaneous duty cycle $\bar{d}(t)$

$$g(t) \longrightarrow \bar{d}(t) = \frac{1}{T_{sw}} \int_t^{t+T_{sw}} g(t) dt$$




From (1)



$$\begin{cases} L \dot{x}_1 = g(t) E - x_2 \\ C \dot{x}_2 = x_1 - \frac{x_2}{R} \end{cases}$$

Fast average
operator
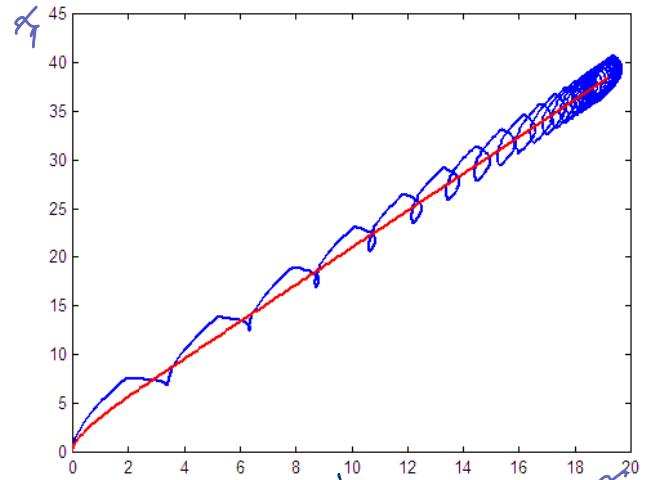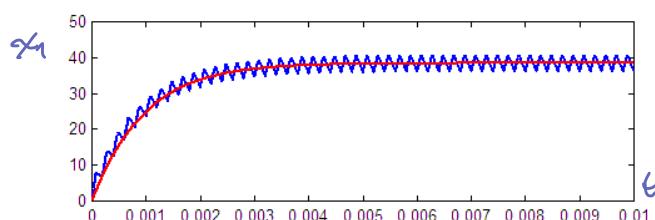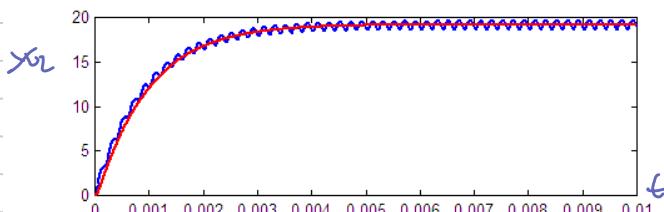
$$\begin{cases} L \dot{\bar{x}}_1 = \bar{d}(t) E - \bar{x}_2 \\ C \dot{\bar{x}}_2 = \bar{x}_1 - \frac{\bar{x}_2}{R} \end{cases} \quad (2)$$



↓
time domain

↓
state space

(phase portrait)

Blue → switched model


Red → Fast average model

Simulations performed with Simulink with a buck converter with $E = 48V$, $R = 0.5\Omega$, $L = 50\mu H$, $C = 100\mu F$

Note that in order to realize the switching function we sample on the instantaneous duty cycle signal with linear transitions that do not add distortion

$$\bar{d}(t) = \frac{1}{T} \int_{t_0}^{t_0+T} g(t') dt'$$

generated with
PWM from

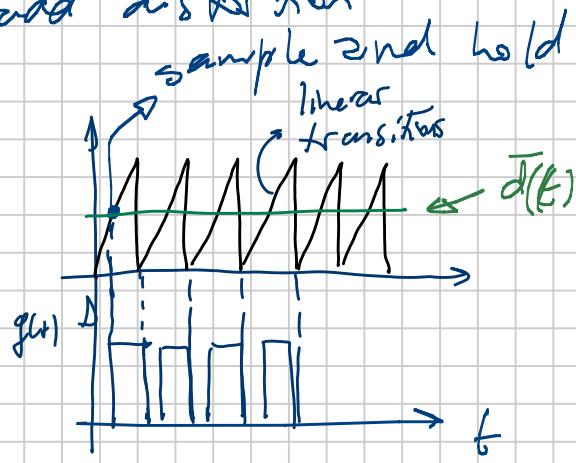

Like earlier I can represent the fast average model in a matrix form.

$$(2) \begin{cases} L \dot{\bar{x}}_1 = \bar{d}(t)E - \bar{x}_2 \\ C \dot{\bar{x}}_2 = \bar{x}_1 - \frac{\bar{x}_2}{R} \end{cases} \rightarrow \boxed{L \dot{\bar{x}} = A \bar{x} + B \bar{u}}$$


↓

If $\bar{d}(t)$ is constant and equal to D , then

$$\begin{cases} L \dot{\bar{x}}_1 = D E - \bar{x}_2 \\ C \dot{\bar{x}}_2 = \bar{x}_1 - \frac{\bar{x}_2}{R} \end{cases}$$

$$\xrightarrow{\text{eq. point}} \begin{cases} \dot{\bar{x}}_1 = 0 \\ \dot{\bar{x}}_2 = 0 \end{cases} \quad \begin{cases} 0 = D E - V_o \\ 0 = I_L - \frac{V_o}{R} \end{cases}$$

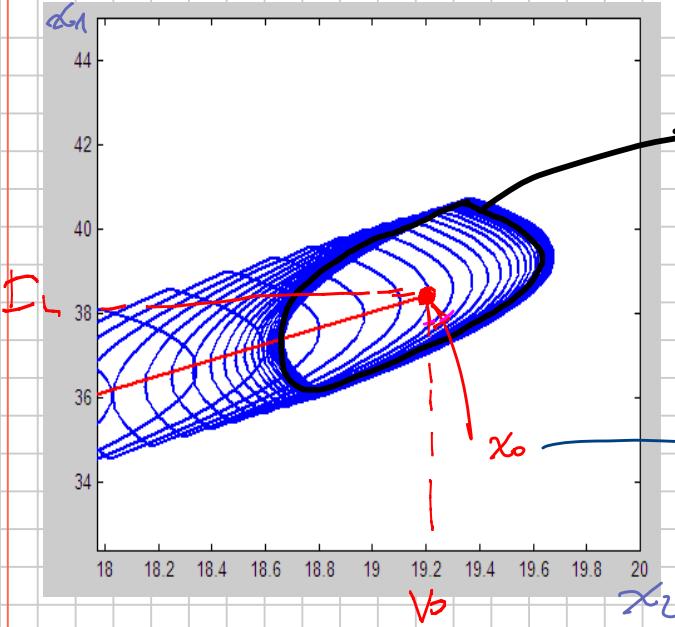eg. point $\rightarrow x_0 = \begin{pmatrix} I_L \\ V_o \end{pmatrix} = \begin{pmatrix} D E / R \\ D E \end{pmatrix}$




Limit cycle

(1) does not lead to an equilibrium point

Equilibrium point only achieved in a weighted average sense

$$\bar{x}_e = \begin{pmatrix} DE/R \\ DE \end{pmatrix} = x_{e_{01}} D + (1-D) x_{e_{02}} \begin{pmatrix} E/R \\ E \end{pmatrix} \begin{pmatrix} \rho \\ 0 \end{pmatrix}$$

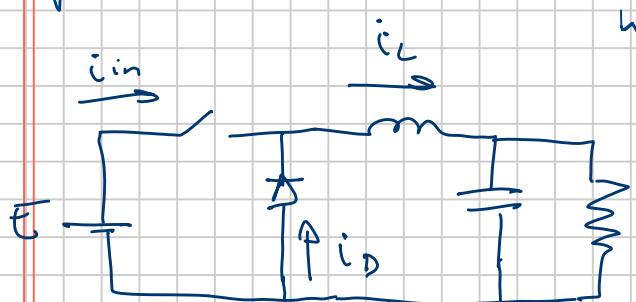What if we are not in con and $i_L=0$ for part of the period (we are in discontinuous conduction mode - DCM)



When $Q_1 = \text{ON}$,


$$V_L = V_{in} - V_{out} = L \frac{di}{dt} = L \frac{i_{peak}}{D_1 T}$$

$$\text{Then } i_{peak} = \frac{D_1 T}{L} (E - V_{out})$$

Also

$$P_{in} = \frac{1}{T} \int_0^T V_{in} i_{in} dt =$$
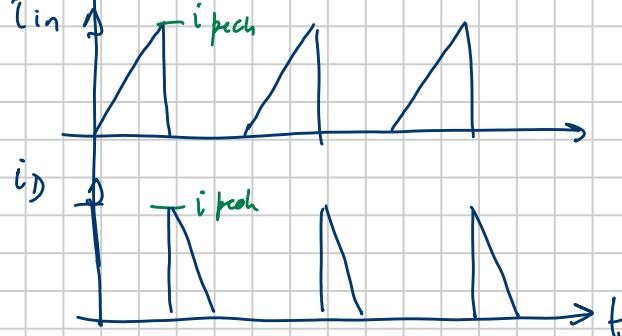
$$= E \frac{1}{T} \int_0^T i_{in} dt \underbrace{\quad}_{\langle i_{in} \rangle}$$



Now,

$$\langle i_{in} \rangle = \frac{1}{T} \frac{D_1 T i_{peak}}{Z} = \frac{D_1 i_{peak}}{Z}$$

\hookrightarrow Area of triangle

$$\text{And, since } P_{in} = P_{out} \rightarrow E(i_{in}) = \frac{V_{out}^2}{R}$$

\downarrow in (**) and (***)

$$\frac{D_i^2 T}{2L} (E - V_{out}) V_{in} = \frac{V_{out}^2}{R}$$



$$V_{out} = -\frac{D_i^2 E R T}{4L} + D E \sqrt{\frac{R T}{2L} + \frac{R^2 T^2 D_i^2}{16L^2}}$$

A complete average model for a buck converter in DCM is

$$L \dot{x}_1 = \bar{E} - \frac{L_2 \bar{x}_1 \bar{x}_2}{\bar{d} T (E - \bar{x}_1)}$$

$$C \dot{x}_2 = \bar{x}_1 - \frac{\bar{x}_2}{R}$$

For the boost converter:

$$\begin{cases} \dot{x}_1 = \bar{E} - f'(t) x_2 \\ C \dot{x}_2 = f''(t) x_1 - \frac{x_2}{R} \end{cases}$$

\downarrow But I cannot replace $f(t)$ by $\bar{f}(t)$ as I did with the buck converter without some clarification:

$$\text{Fast average issue} \rightarrow \frac{1}{T_{sw}} \int_t^{t+T_{sw}} f'(t) x_i dt \neq \frac{1}{T_{sw}} \int_t^{t+T_{sw}} f'(t) dt / \bar{x}_i$$

$\overbrace{d(t)}^{\bar{d}(t)} \quad \overbrace{\bar{x}}^{\bar{x}}$

That is, the fast average operator applied to $f'(t) x_i$ is not necessarily $\bar{f}'(t) \bar{x}$

e.g.

Since in the switched model the state variables follow linear transitions consider that

$$x_i = \alpha t$$

Then

$$\overline{x_i g(t)} = \frac{1}{T_{sw}} \int_t^{t+T_{sw}} \Delta t \cdot g(t) dt = \frac{A}{2} D \left(2t + \overline{T_{sw}} \right)$$

→ Fast average of the product $x_i g(t)$

Now consider

$$\bar{x}_i dA = \left(\frac{1}{T_{sw}} \int_t^{t+T_{sw}} A t \right) \left(\frac{1}{T_{sw}} \int_t^{t+T_{sw}} g(t) dt \right) = \frac{D A}{2} \left(2t + \overline{T_{sw}} \right)$$

This is the only difference

For T_{sw} very small there is no problem

So, for high switching frequency ($f_{sw} = \frac{1}{T_{sw}}$) .

$$\begin{cases} L \dot{x}_1 = E - \bar{d}' \bar{x}_2 \\ C \dot{x}_2 = \bar{d}' \bar{x}_1 - \frac{\bar{x}_2}{R} \end{cases}$$


But how "high" is a "high" switching frequency?

Consider a switched linear system

$$\dot{x} = (A_1 g(t) + A_2 (1-g(t)) x$$

|||
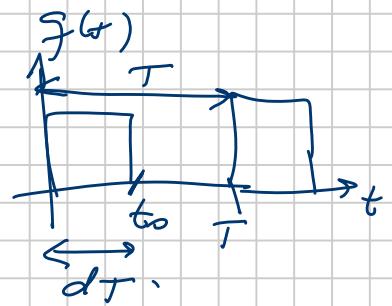
$$\dot{x} = \begin{cases} f_1(t) = A_1 x, & t \in [0, t_0] \\ f_2(t) = A_2 x, & t \in [t_0, T] \end{cases}$$



The exact solutions for $f_1(t)$ and $f_2(t)$ are

A_1 and A_2 are matrices so this function is the exponential of a matrix

$$x(t) = e^{A_1 t} x(0) \quad t \in [0, t_0]$$

$$x(t) = e^{A_2(t-t_0)} x(t_0) \quad t \in [t_0, T]$$

which is calculated as $e^{A_0} = \sum_{k=0}^{\infty} \frac{1}{k!} A_0^k$

$$\Rightarrow x(T) = e^{A_2(T-t_0)} x(t_0) = e^{A_2(T-dT)} x(t_0)$$

Since $x(t)$ is continuous at t_0 ($x(t_0^-) = x(t_0^+)$) then

$$x(T) = e^{A_2(T-dT)} x(t_0) = e^{A_2(1-d)T} e^{A_1 dT} x(0)$$

$$x(t_0) = e^{A_1 t_0} x(0)$$

Now let's call $A_2(1-d)T = A_2$ (it's a matrix) and

$A_1 dT = A_1$ (another matrix)

$$\text{So } x(T) = e^{A_2} e^{A_1} (3)$$

Before continuing let's see some useful properties of the function of the exponential of 2 matrix.

$$e^0 = I$$

$$e^{ab} e^{ba} = e^{(a+b)b}$$

$$e^b e^{-b} = I$$

$$\text{If } \beta \text{ is invertible then } \rightarrow e^{B\beta \beta^{-1}} = \beta e^b \beta^{-1}$$

$$\det(e^{\beta}) = e^{\text{tr}(\beta)}$$

\hookrightarrow trace of $\beta \longrightarrow \text{tr}(\beta) = \sum_{j=1}^n \alpha_{jj}$

$$e^{\beta^T} = (e^\beta)^T$$

If β and γ commute (i.e., $\beta\gamma = \gamma\beta$) then $e^{\beta+\gamma} = e^\beta e^\gamma$

If β and γ do not commute we can use Baker-Campbell-Hausdorff formula

$$\hookrightarrow \text{If } e^C = e^\beta e^\gamma$$

$$\text{then } C = \beta + \gamma + \frac{1}{2} [\beta, \gamma] + \frac{1}{12} ([\beta, [\beta, \gamma]] + [[\beta, \gamma], \gamma]) + \dots$$

$$\overbrace{\text{commutator}} \rightarrow [\beta, \gamma] = \beta\gamma - \gamma\beta$$

$$\hookrightarrow \text{So if they commute } [\beta, \gamma] = 0$$

and

$$e^C = e^{\beta+\gamma}$$

$$\text{So let's go back to (3)} \longrightarrow x(T) = e^{\beta_2} e^{\beta_1}$$

Since β_1 and β_2 do not necessarily commute then from (2)

$$\beta = AT = \beta_1 + \beta_2 + \frac{1}{2} [\beta_1, \beta_2] =$$

$$dI = 1-d \leftarrow = (dA_1 + d'A_2)T + dd'(A_1 A_2 - A_2 A_1)T^2 + \dots$$

Now, if T is small (i.e., few large) then $T^2 \ll T$ and

$$AT \approx (dA_1 + d'A_2)T$$

$$\text{and } x(T) = e^{AT} x(0) \approx e^{(dA_1 + d'A_2)T} x(0) \quad (4)$$

$$\text{solution to } \dot{x} = \underbrace{(dA_1 + d'A_2)}_{\text{weighted average of }} x \quad \left. \begin{array}{l} \dot{x} = A_1 x \\ \dot{x} = A_2 x \end{array} \right\}$$

So the fast average model is a good approximation for the switched model if T is small (or few is large) so the following approximation is valid

$$e^{t_0} = \sum_{k=0}^{\infty} \frac{1}{k!} A_0^k \tilde{I} + A_0 \rightarrow \begin{cases} e^{dA_1 T} \tilde{I} + dA_1 T \\ e^{d'A_2 T} \tilde{I} + d'A_2 T \end{cases}$$

so let's go back to the buck converter for a quick example



Switched system


$$\begin{cases} L \dot{x}_1 = f(t) E - x_2 \\ C \dot{x}_2 = x_1 - \frac{x_2}{R} \end{cases} . \quad x(0) = x_0$$

equilibrium

$$\text{For } f(t)=0 \rightarrow x_2=0, x_1=0$$

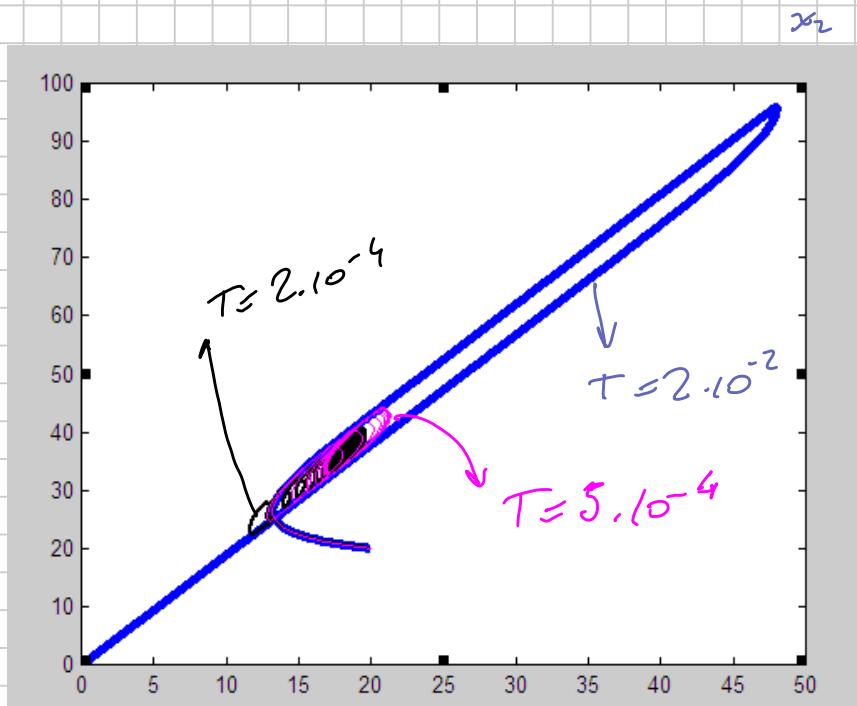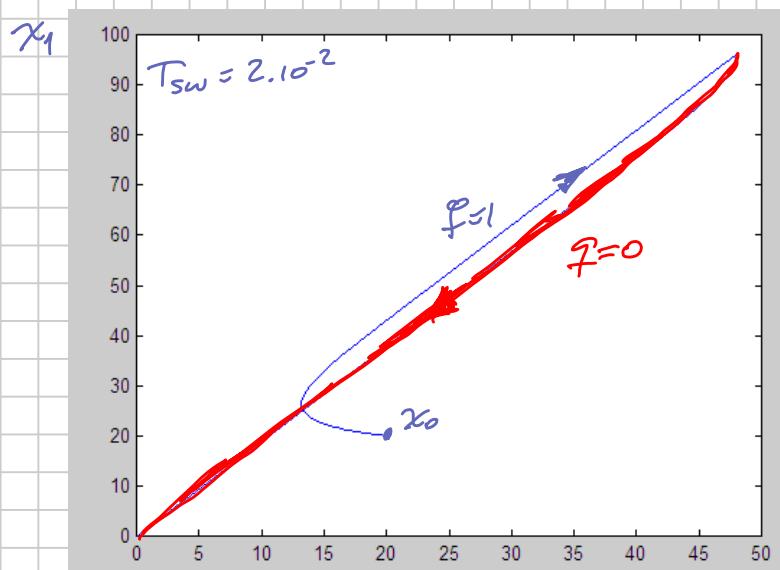
$$\text{For } f(t)=1 \rightarrow x_2=E, x_1=\frac{E}{R}$$



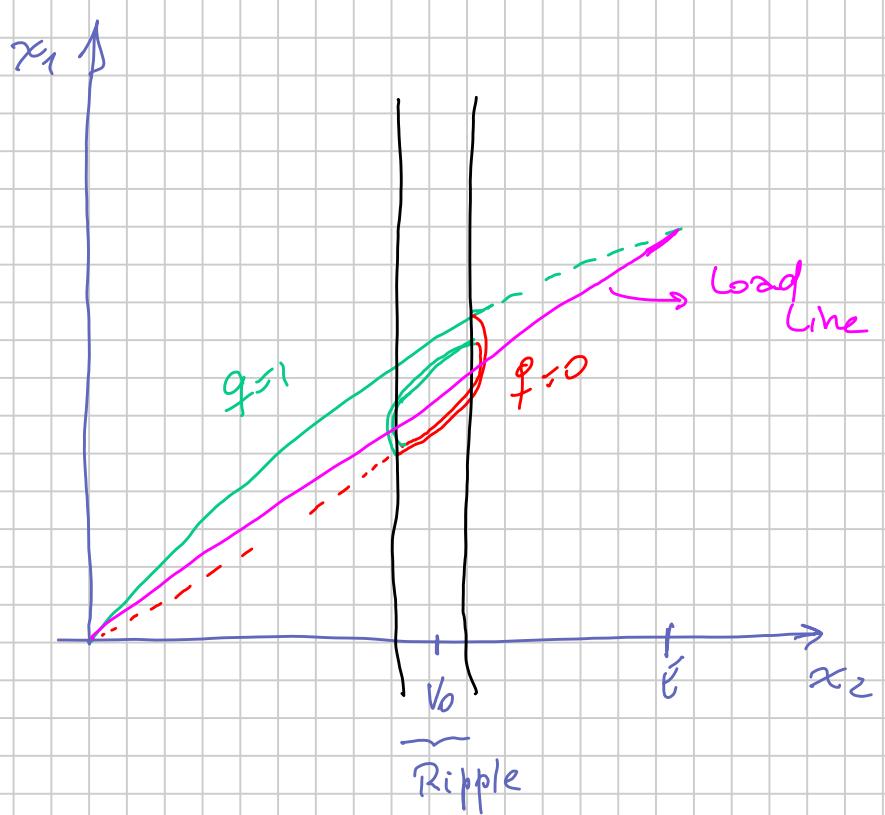

Small signal model

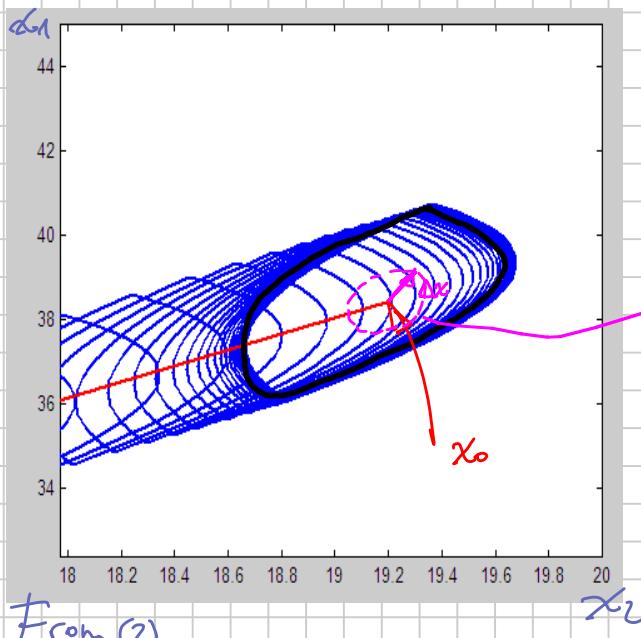let's consider once again the buck converter



Let's represent the converter behavior in a small region close around the equilibrium point x_0

From (2)

$$\begin{cases} L \frac{\dot{x}_1}{x_1} = \bar{J}(t)E - \bar{x}_2 \\ C \frac{\dot{x}_2}{x_2} = \bar{x}_1 - \frac{\bar{x}_2}{R} \end{cases}$$

Consider the linear operator Δ that is defined as

$\Delta(f) = f - f_0 \rightarrow$ so it just calculates the difference with respect to a point f_0 .

$$\text{So } \delta_{\bar{x}_1} = \Delta(\bar{x}_1) = \bar{x}_1 - \bar{x}_{10} \rightarrow (\delta \bar{x}_1) = \dot{\bar{x}}_1 \\ \text{↳ coordinate in } x_1 \text{ of the equilibrium point.}$$

Let $r_1 = x_1, r_2 = x_2$ then

$$L \delta \dot{\bar{x}}_1 = E \bar{\delta}_d - \delta \bar{x}_2$$

$$\text{In the same way } C \delta \dot{\bar{x}}_2 = \delta \bar{x}_1 - \frac{\delta \bar{x}_2}{R}$$

thus,

$$L \delta \dot{\bar{x}}_1 = E \bar{\delta}_d - \delta \bar{x}_2$$

$$C \delta \dot{\bar{x}}_2 = \delta \bar{x}_1 - \frac{\delta \bar{x}_2}{R}$$

→ Model valid in
a small neighborhood
around the equilibrium
point x_0

If the input voltage E is allowed to vary then:

$$\left. \begin{array}{l} L \delta \dot{\bar{x}}_1 = \underbrace{E \bar{\delta}_d + \delta_E D_0}_{\text{the product of two variables (d and E) becomes two terms}} - \delta \bar{x}_2 \\ C \delta \dot{\bar{x}}_2 = \delta \bar{x}_1 - \frac{\delta \bar{x}_2}{R} \end{array} \right.$$

So I can now do standard linear analysis. For example I can calculate the transfer functions from

$$\rightarrow \begin{pmatrix} \dot{\delta x_1} \\ \dot{\delta x_2} \end{pmatrix} = \underbrace{\begin{pmatrix} 0 & -1/L \\ 1/C & -1/R \end{pmatrix}}_A \underbrace{\begin{pmatrix} \delta x_1 \\ \delta x_2 \end{pmatrix}}_{\delta x} + \underbrace{\begin{pmatrix} E/L & D_o/L \\ 0 & 0 \end{pmatrix}}_B \underbrace{\begin{pmatrix} \delta d \\ \delta e \end{pmatrix}}_{\delta u}$$

Notice that δx_2 is controlled through δx_1

$$\delta y = \delta x_2$$

Using Laplace

$$\mathcal{L}(\dot{\delta x}_1) = S \Delta x_1(s) \dots$$

$$\left. \begin{array}{l} L S \Delta x_1(s) = - \Delta x_2(s) + E \Delta_d(s) + D_o \Delta_e(s) \\ C S \Delta x_2(s) = \Delta x_1(s) - \frac{\Delta x_2(s)}{R} \end{array} \right.$$

$$G(s) = \frac{\Delta x_2(s)}{\Delta_d(s)} \rightarrow \frac{\text{output}}{\text{control input}}$$

transfer function

$$L S \Delta x_1(s) = L S \left(C S \Delta x_2(s) + \frac{\Delta x_2(s)}{R} \right) = - \Delta x_2(s) + E \Delta_d(s) + D_o \Delta_e(s)$$

$$\Delta x_2(s) \left(L C S^2 + \frac{L}{R} S + 1 \right) = E \Delta_d(s)$$

$$G(s) = \frac{E R}{L C R S^2 + L S + R}$$

When calculating the transfer function with respect to the control input, it is considered that the power input is fixed $\Rightarrow \Delta_e(s) = 0$

for the boost converter:

Linearization:

$$\text{From } \Delta f \approx \frac{\partial f}{\partial r_1} \Big|_{r_0} \Delta r_1 + \frac{\partial f}{\partial r_2} \Big|_{r_0} \Delta r_2$$

$$\text{If } f = \bar{x}_i$$

$$\text{then } \delta_f = X_{i0} \delta_d + D_0 \delta \bar{x}_i$$


thus,

$$\begin{cases} L \dot{\bar{x}}_1 = X_{20} \delta_d - (1-D_0) \delta x_2 \\ C \dot{\bar{x}}_2 = -X_{10} \delta_d + (1-D_0) \delta x_1 - \frac{\delta x_2}{R} \end{cases}$$

Equivalent circuit based on the first average model

— Buck converter

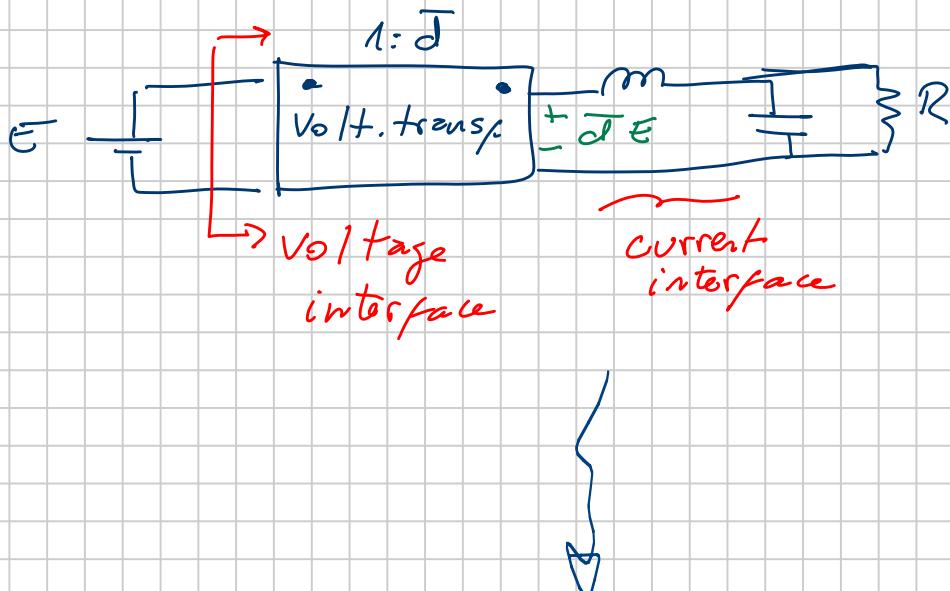
$$\begin{cases} L \dot{\bar{x}}_1 = \bar{J}(t) E - \bar{x}_2 \\ C \dot{\bar{x}}_2 = \bar{x}_1 - \frac{\bar{x}_2}{R} \end{cases}$$



- Boost converter

$$\bar{d}' = 1 - d$$

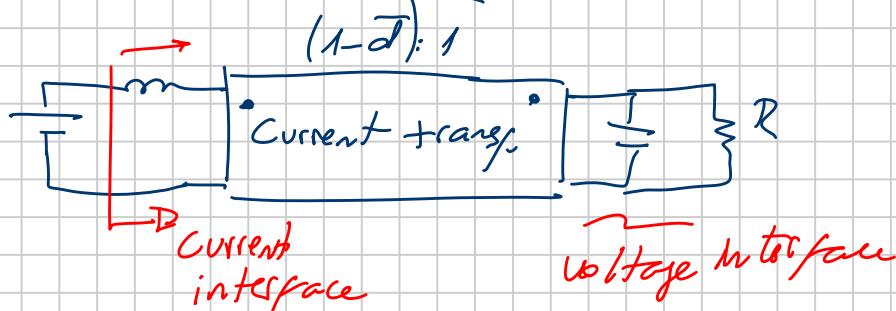
$$\begin{cases} L \dot{\bar{x}}_1 = E - \bar{d}'(t) \bar{x}_2 \\ C \dot{\bar{x}}_2 = \bar{d}' \bar{x}_1 - \frac{\bar{x}_2}{R} \end{cases}$$



- Fly Back

$$\begin{cases} \dot{\bar{\phi}} = \frac{\bar{d}E}{N_1} - \frac{\bar{d}'}{N_2} \bar{x}_2 \\ C \dot{\bar{x}}_2 = \frac{\bar{d}'}{N_2} \bar{x}_1 - \frac{\bar{x}_2}{R} \end{cases} \rightarrow \begin{cases} \frac{d\bar{\phi}}{dt} = \bar{d}E - \frac{N_1 \bar{d}'}{N_2} \bar{v}_c \\ C \frac{d\bar{v}_c}{dt} = \bar{d}' \frac{N_2}{N_1} \bar{i}_1 - \frac{V_c}{R} \end{cases}$$
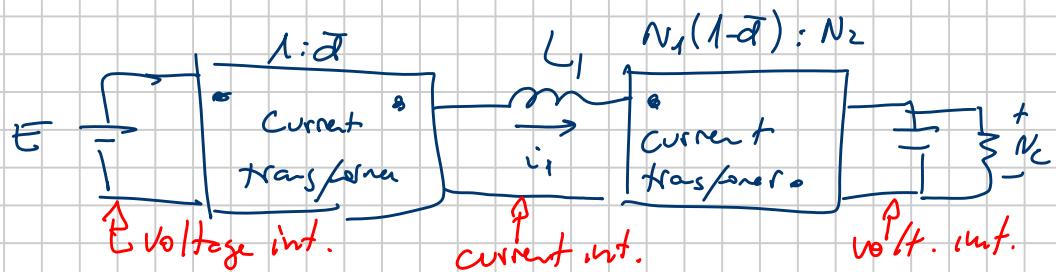
$$\frac{\dot{\bar{\phi}}}{\Delta_{CN_2}} = \frac{\dot{\bar{\phi}}}{N_2} = \bar{\phi} \frac{N_2}{L_2} = \frac{N_1}{N_2^2} \bar{i}_1$$



Some good papers for reference:

Small-Signal Modeling of Pulse-Width Modulated Switched-Mode Power Converters

R. D. MIDDLEBROOK, FELLOW, IEEE

On the Use of Averaging for the Analysis of Power Electronic Systems

PHILIP T. KREIN, MEMBER, IEEE, JOSEPH BENTSMAN, MEMBER, IEEE,
RICHARD M. BASS, STUDENT MEMBER, IEEE,
AND BERNARD L. LESIEUTRE

LARGE-SIGNAL DESIGN ALTERNATIVES FOR SWITCHING POWER CONVERTER CONTROL

Richard M. Bass¹ and Philip T. Krein²

A GENERAL UNIFIED APPROACH TO MODELLING SWITCHING-CONVERTER POWER STAGES

R. D. Middlebrook and Slobodan Cuk

} → classical paper from
PESL 1976

Modeling of PWM Converters in Discontinuous Conduction Mode - A Reexamination

Jian Sun, Daniel M. Mitchell Matthew F. Greuel, Philip T. Krein and Richard M. Bass

GENERATION, CLASSIFICATION AND ANALYSIS OF SWITCHED-MODE DC-TO-DC CONVERTERS BY THE USE OF CONVERTER CELLS

Richard Tymerski and Vatché Vorpérian