

Power electronics for energy storage

Note Title

11/20/2011

Batteries and ultracaps


↳ 2 Functions for the power electronics interface

↳ Control charge/discharge
↳ Cell equalization

Consider \rightarrow  = 

Non-isolated converters for charge/discharge control

1/2 Bridge (aka boost/buck)

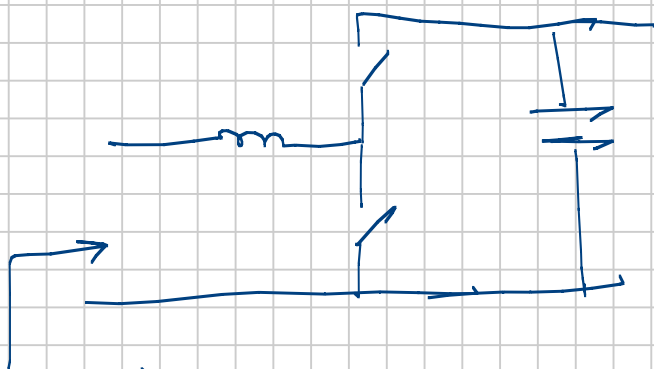


No diodes \rightarrow All active switches

↳ but depending the operational mode may only act as diodes


Boost \leftarrow energy storage on this side because of its low voltage

↑
Also some battery technologies need to have their current controlled when they are being charged
↑
e.g. Li-ion

Cuk

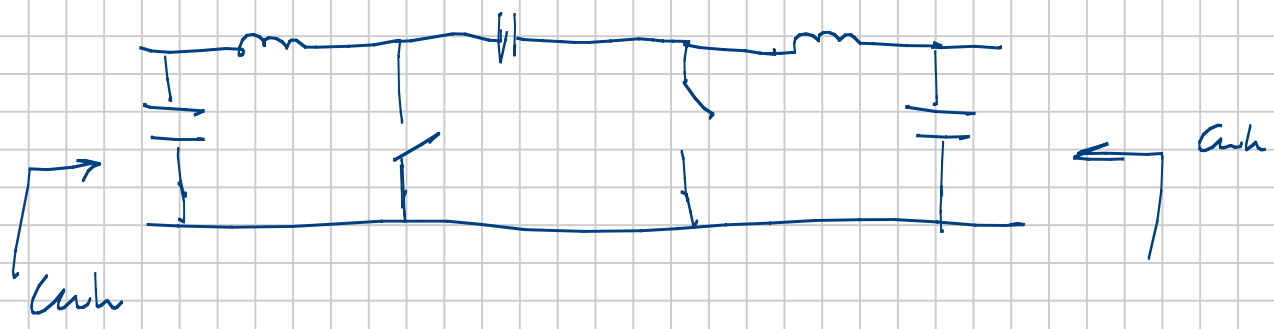

SEPIC

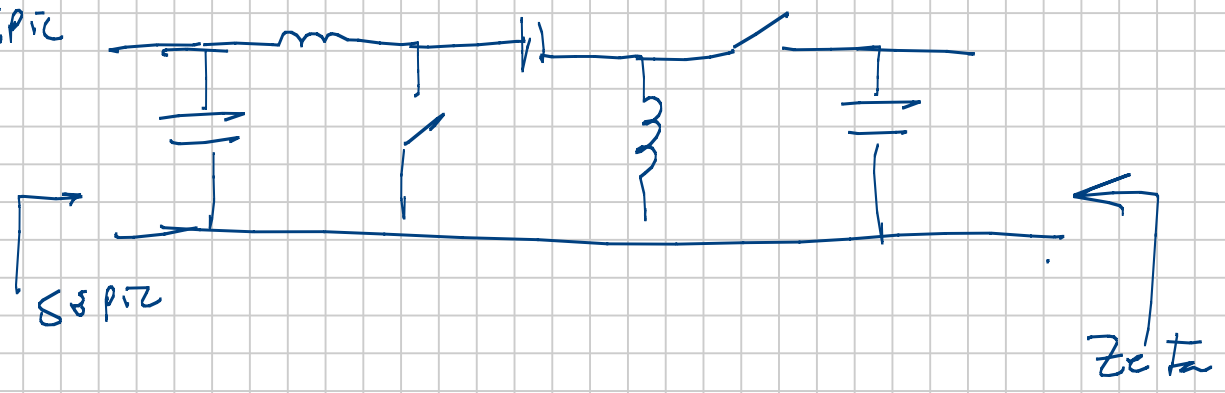

Advantages of non-isolated topologies

- simple
- high efficiency
- low cost
- high reliability


Disadvantage → Max. voltage step-up ratio $\approx 4x$

→ 1/2 Bridge tends to be more efficient and cost less than the other configurations.


→ Isolated converters

→ There is a good summary here

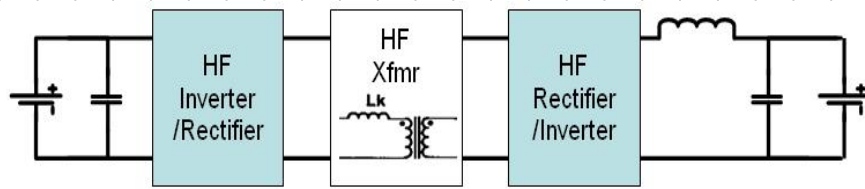
Review of High Power Isolated Bi-directional DC-DC Converters for PHEV/EV DC Charging Infrastructure



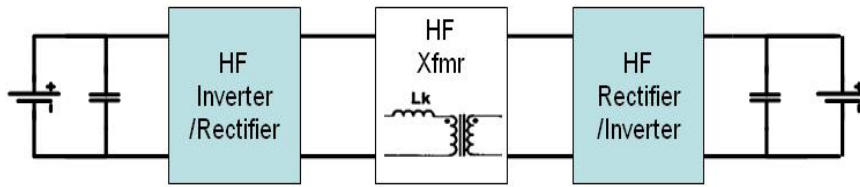One voltage-fed and one current-fed DC side




Two voltage-fed DC sides

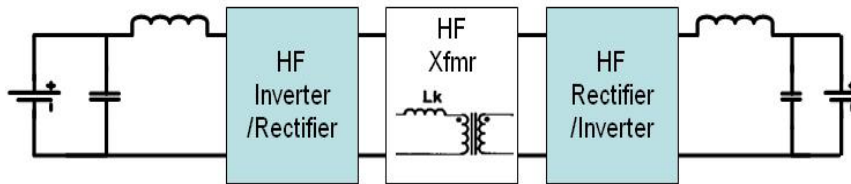


Two current-fed DC sides

inverter →


← *Rectifier*

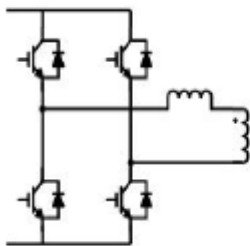


Full-bridge

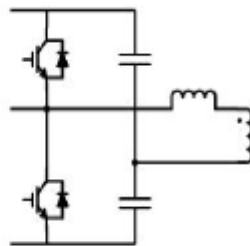


Half-bridge (Symmetric)

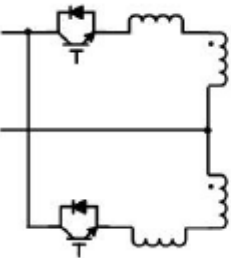


Push-pull

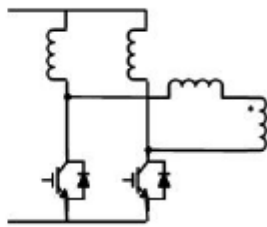


L-type HB (V-fed only)

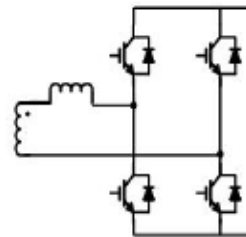


Full-bridge

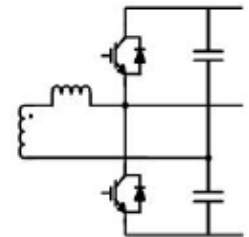

Half-bridge (Voltage Doubler)

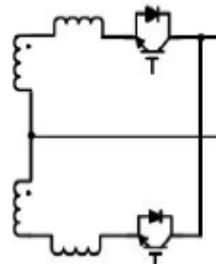

Center-tapped

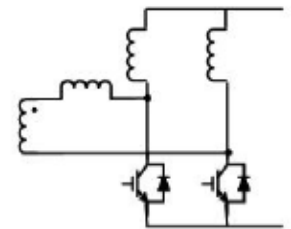

Current Doubler

(a) Major topologies for high frequency inverter

(b) The counterpart topologies for high frequency rectifier

↔
Notice the correspondence

Voltage stress in full bridge = voltage stress in half bridge
 current " " " " = $\frac{1}{2}$ current " " " "

Best of topologies suitable for low voltage and high current application because of stress switches

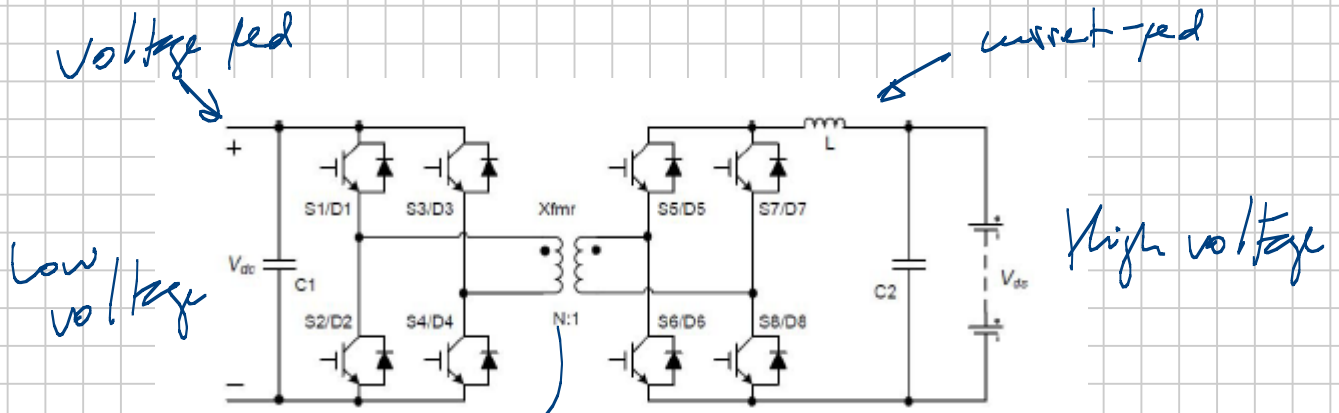



Fig. 4: Bi-directional DC-DC converter based on a voltage-fed full bridge and a current-fed full bridge

Issue in high power applications → leakage inductance

High voltage spikes on switches when switching


Lower efficiency
Possible reliability issues

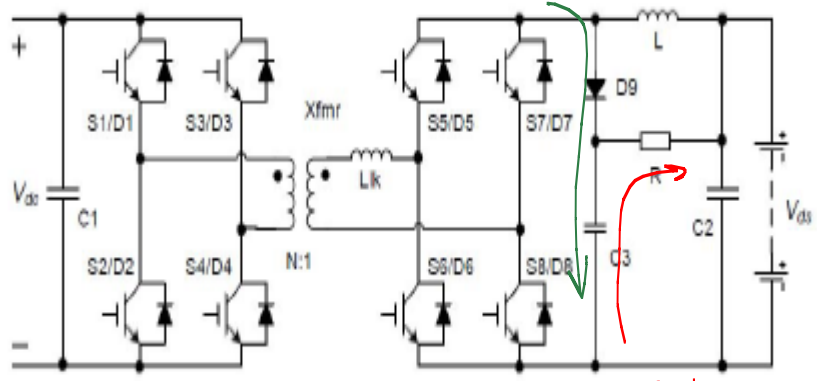Energy of spikes transferred to capacitor which limits the spike




lossy RCD snubber

Extra energy dissipated to resistor

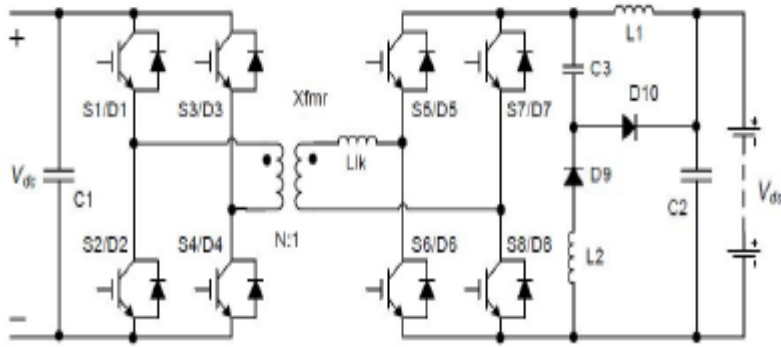

→ lossless but more components

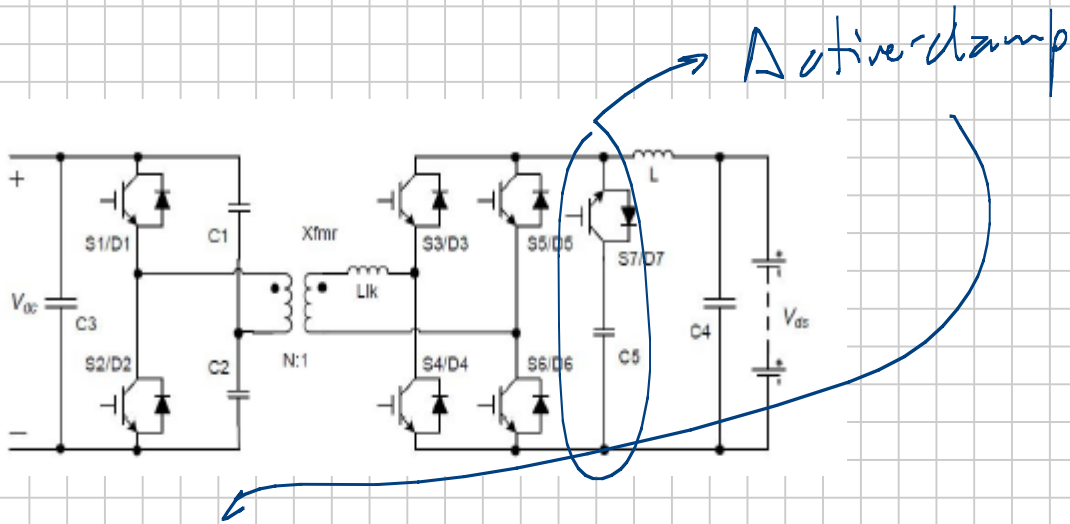




Let's see it in more detail from

A Soft-switching Active-Clamp Scheme for Isolated Full-Bridge Boost Converter

En-Sung Park

Sung Jin Choi, J. Moon Lee and B.H. Cho

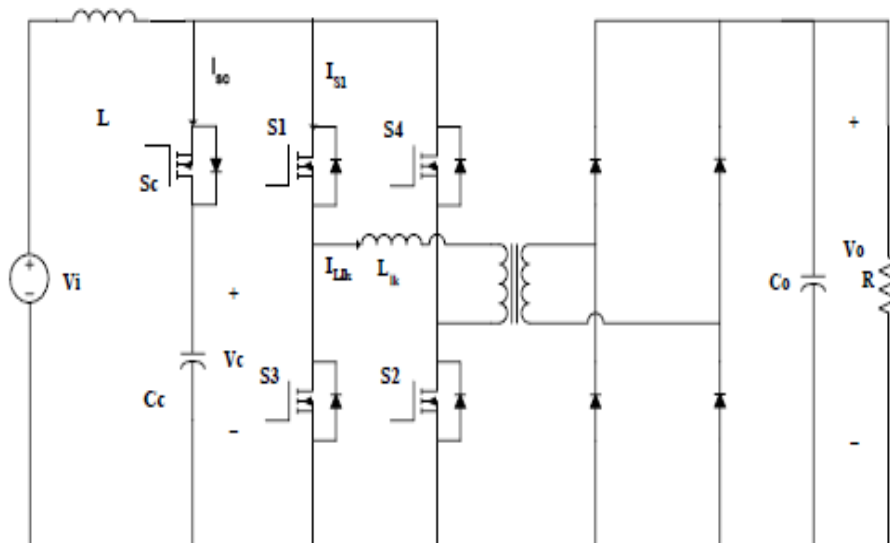

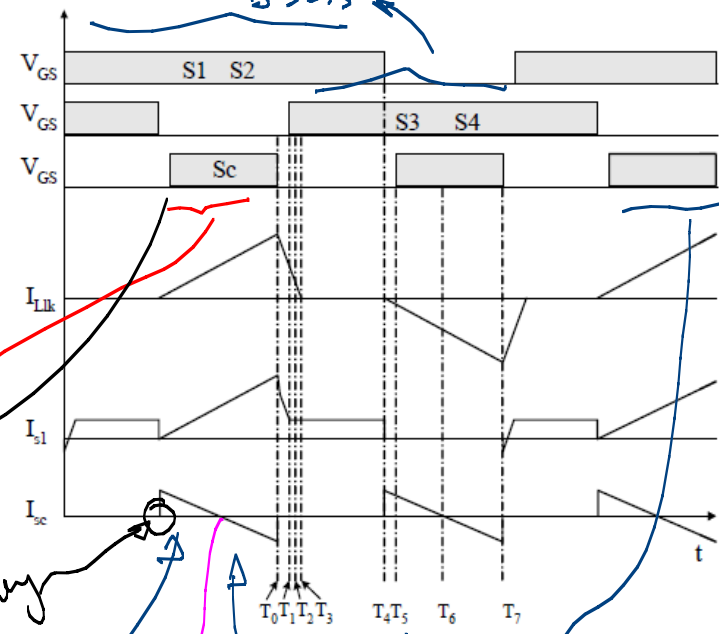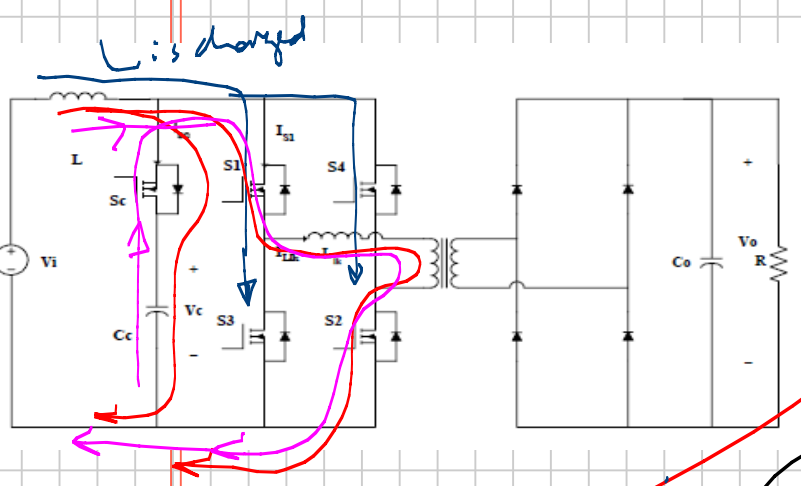

- L is discharged
- L is discharged


Zero current switching
current goes through diode



Cc is charged
Cc is discharged
Switched is switched on
→ 2V_S
L_{rs} discharged

L is charged in T₁ to T₄


When either (S₁, S₂) or (S₃, S₄) are switched off then the diode in S_c starts to conduct and clamps the switch voltage to V_{in}.

Some more details

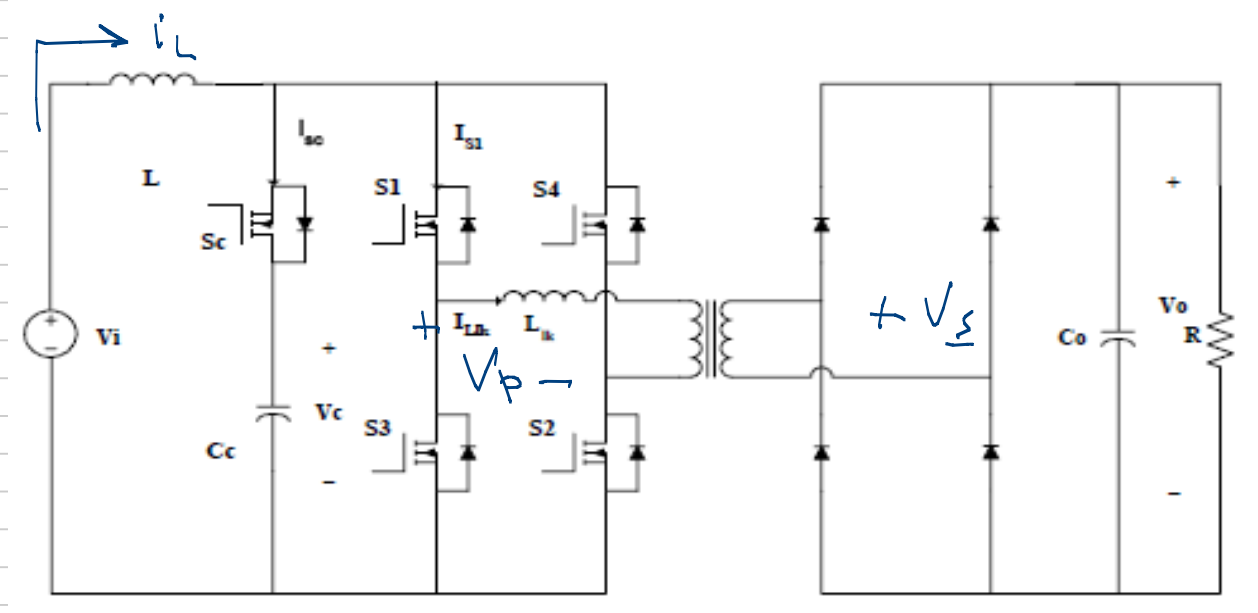

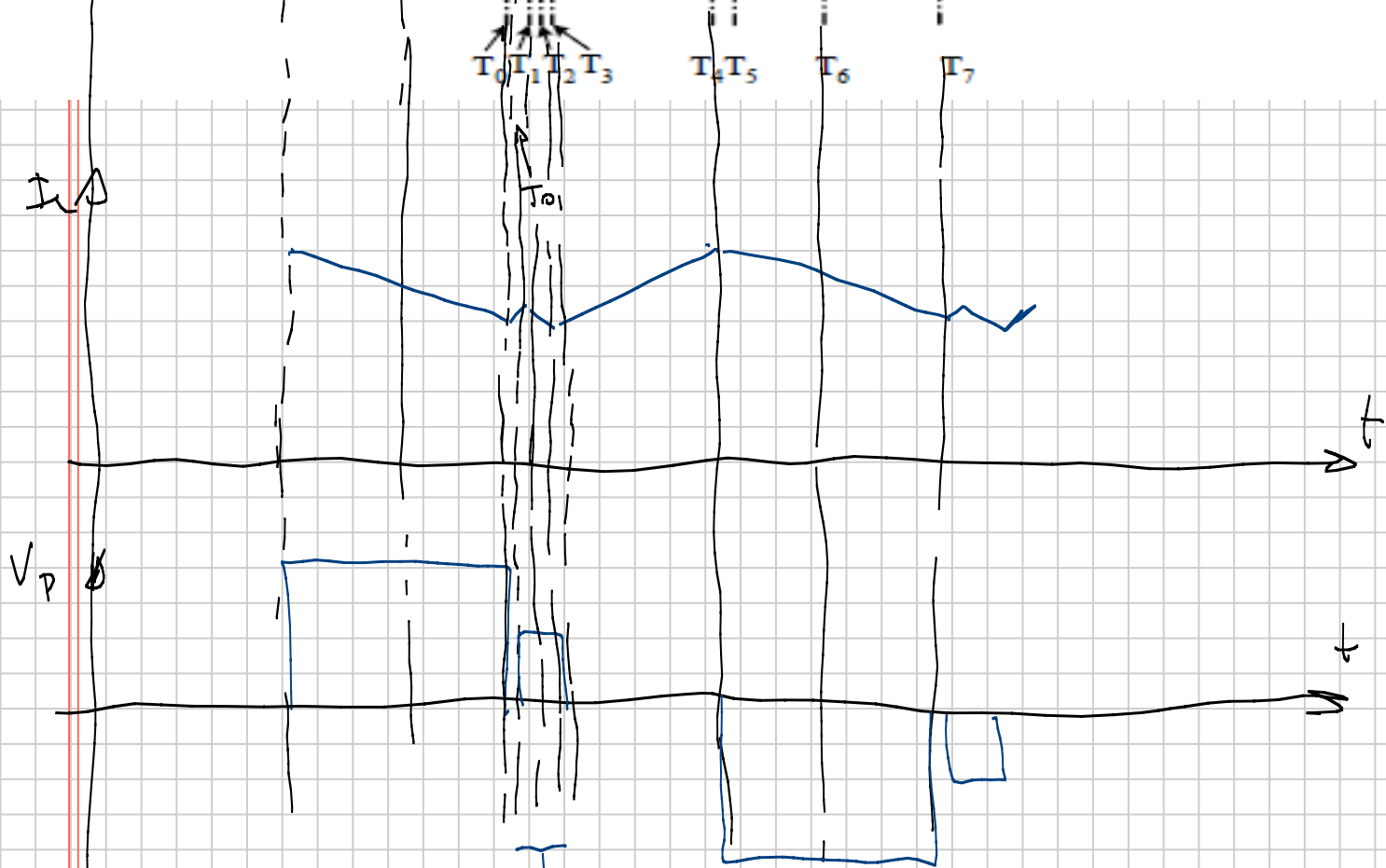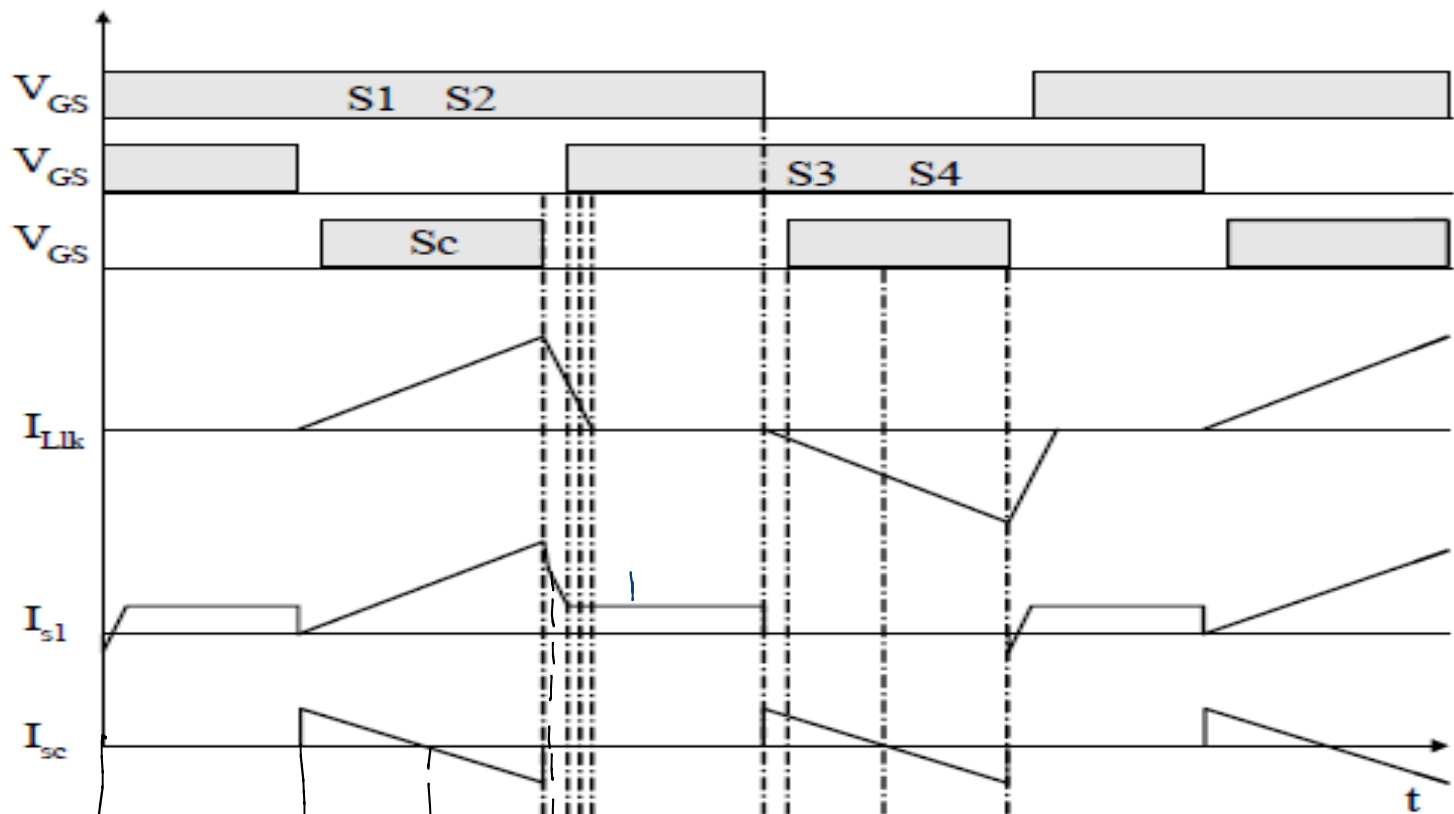

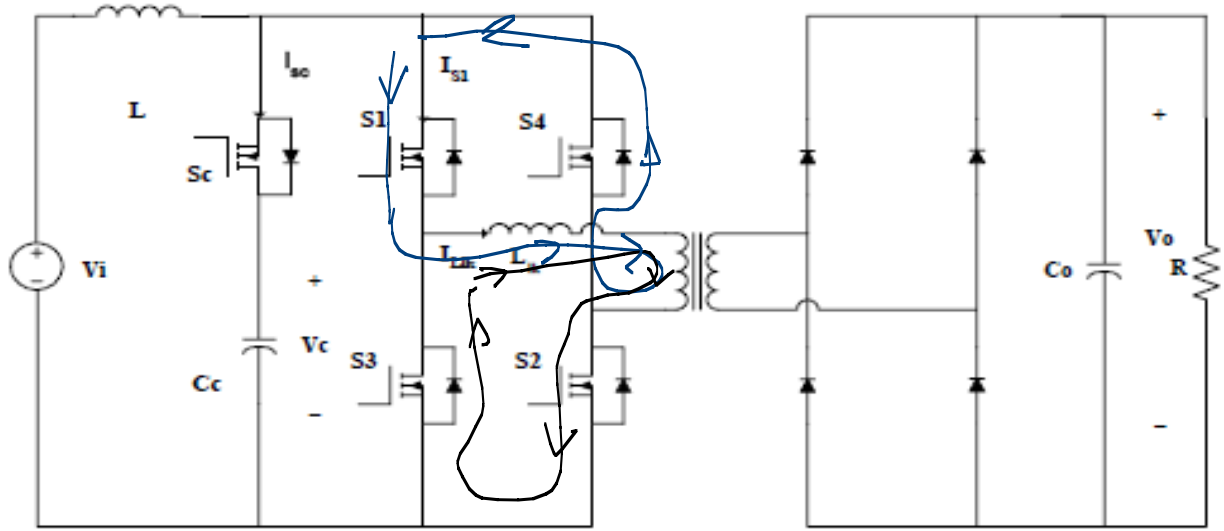leakage
 Inductance energy transferred to secondary
 so it is not lost.



Now, let's continue with the energy storage converters:

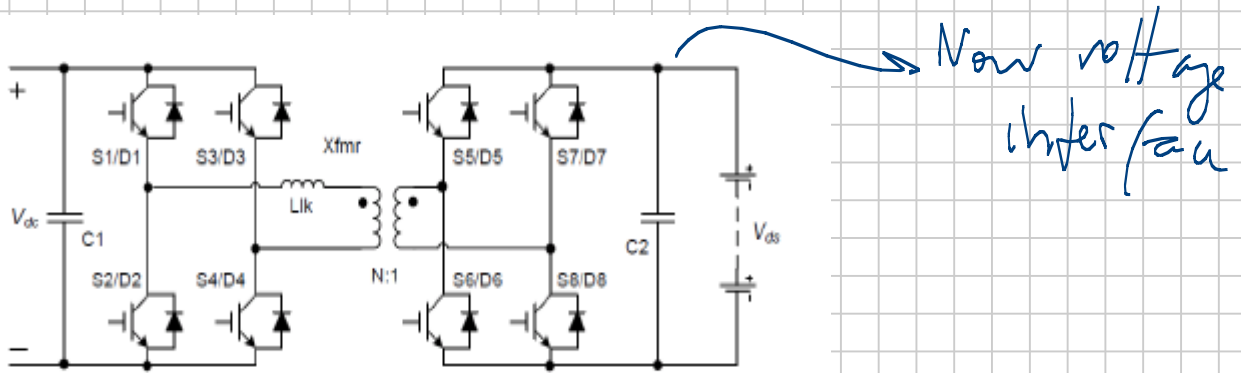


Fig. 10: Bi-directional DC-DC converter based on two voltage-fed full bridges

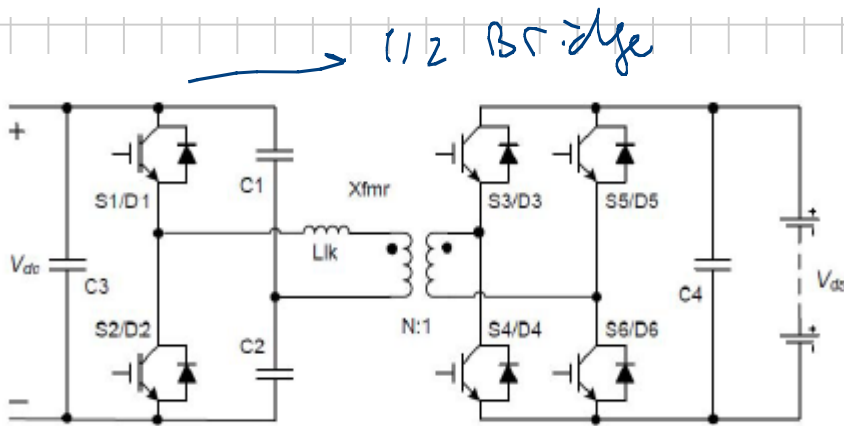


Fig. 11: Bi-directional DC-DC converter based on a voltage-fed half bridge and a voltage-fed full bridge

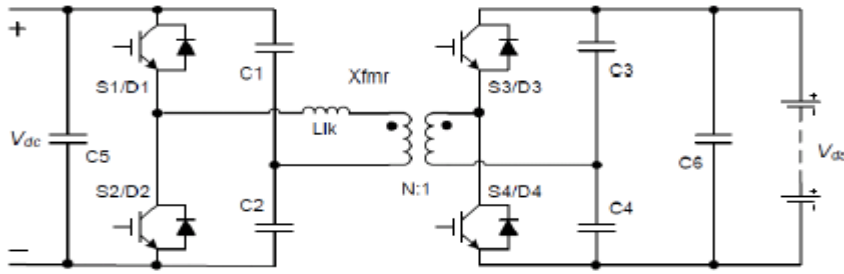



Fig. 12: Bi-directional DC-DC converter based on two voltage-fed half bridges

Advantage \rightarrow potential higher efficiency compared to current source due to \angle stress.

But

Disadvantages \rightarrow Not easy to have high efficiency with light loads
 \rightarrow Narrow voltage range for optimal operation \rightarrow problem when the input voltage is expected to drop due to battery discharge

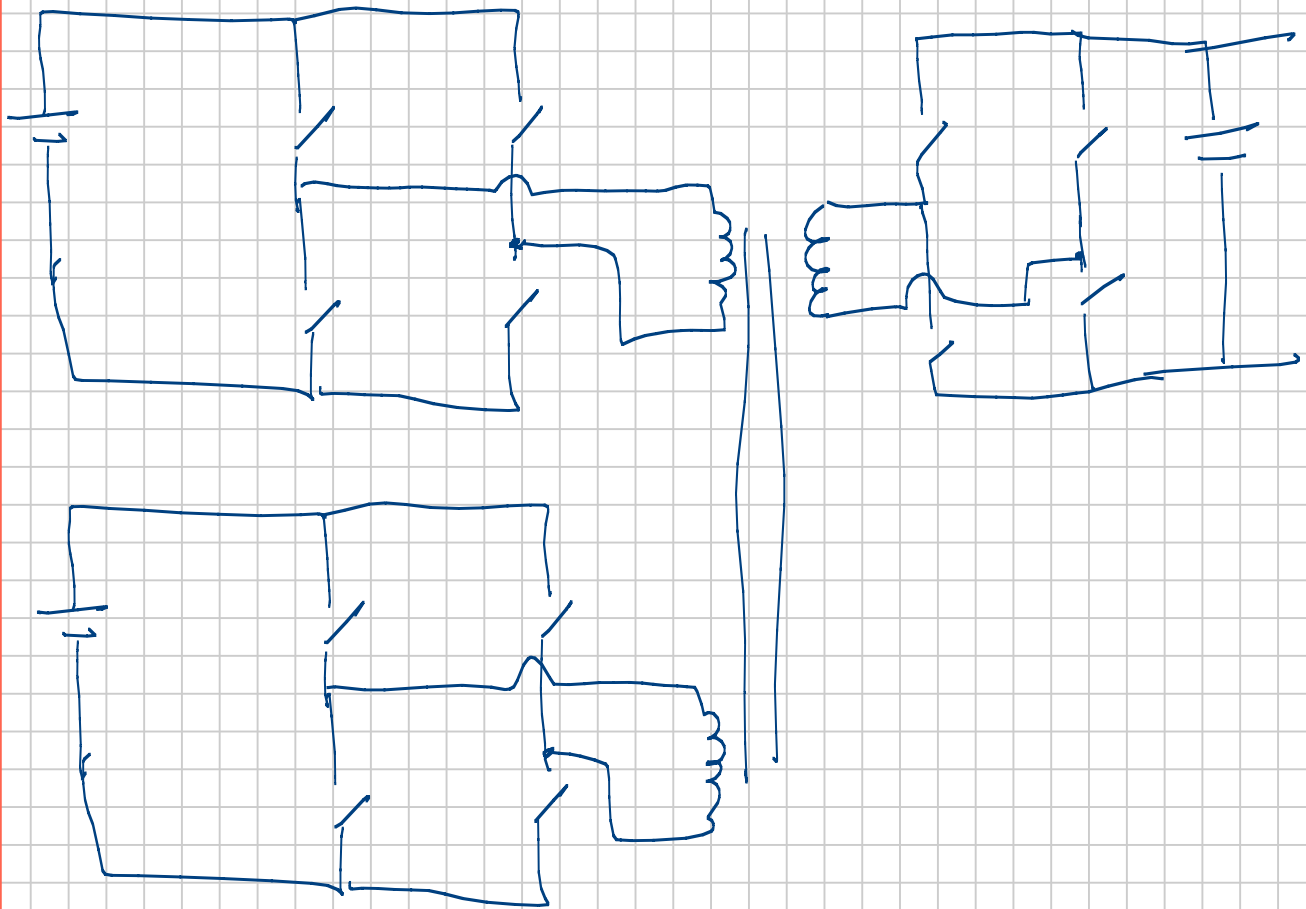
The full bridge can be extended as multiple input configuration




Other bidirectional converters.

Tri-Modal Half-Bridge Converter Topology for Three-Port Interface

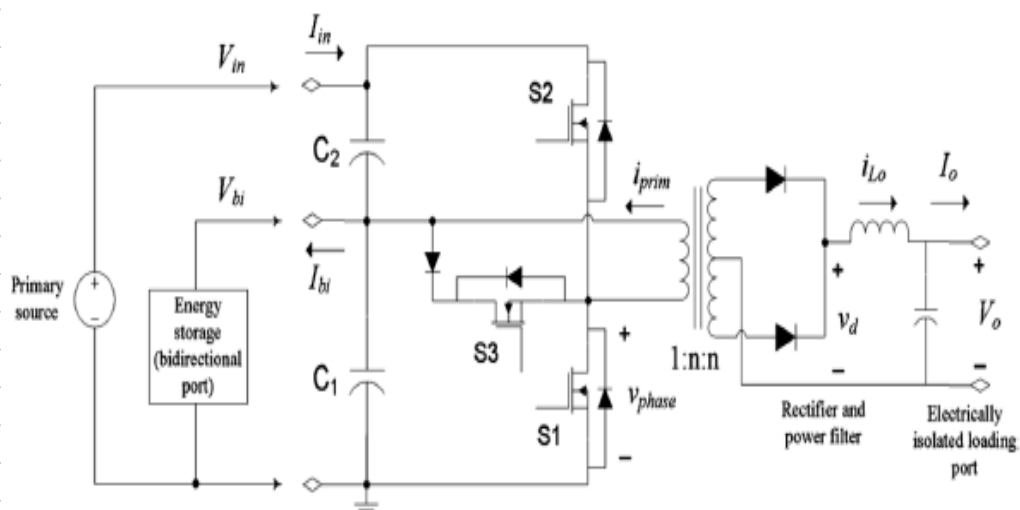Hussam Al-Atrash, *Student Member, IEEE*, Feng Tian, *Student Member, IEEE*, and Issa Batarseh, *Fellow, IEEE*



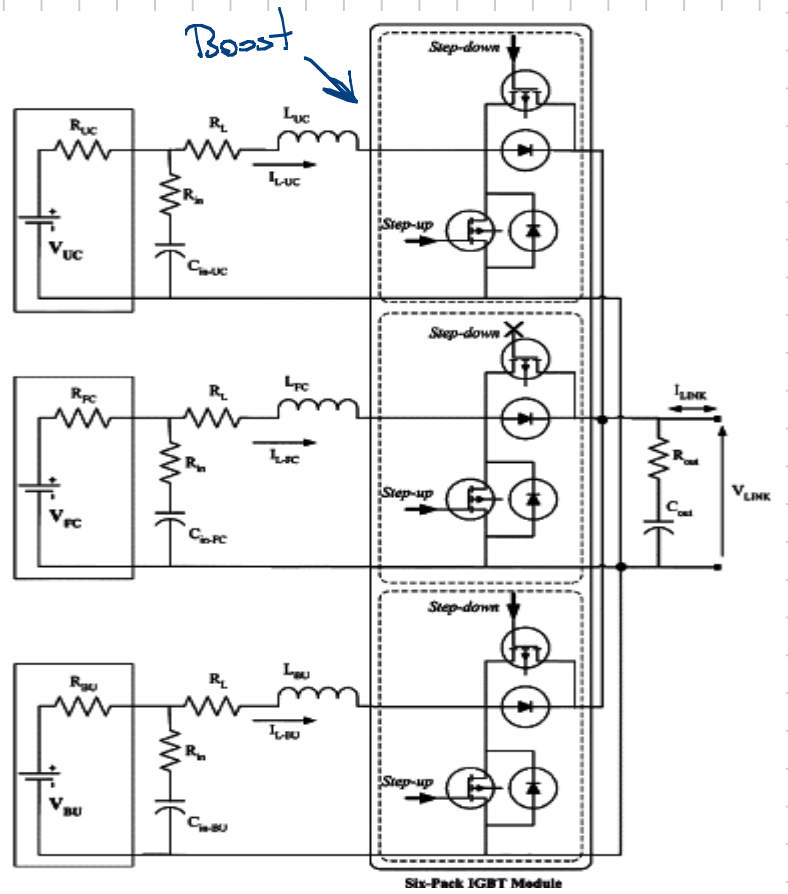


Design of Multiple-Input Power Converter for Hybrid Vehicles


Luca Solero, *Member, IEEE*, Alessandro Lidozzi, *Student Member, IEEE*, and Josè Antenor Pomilio, *Senior Member, IEEE*

A Multiple-Input SEPIC with a Bi-Directional Input for Modular Distributed Generation and Energy Storage Integration


Juyoung Jung

Alexis Kwasinski

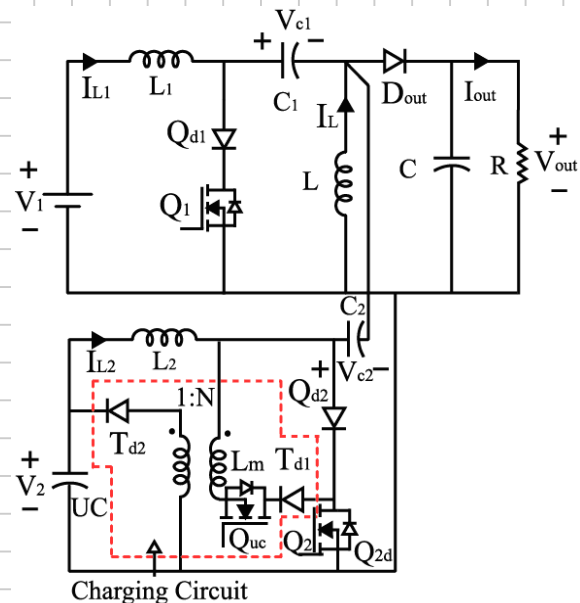


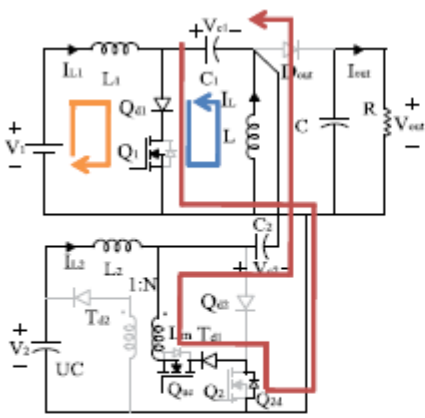

Mode 1 ($q_1(t)=1, q_{uc}(t)=1$)

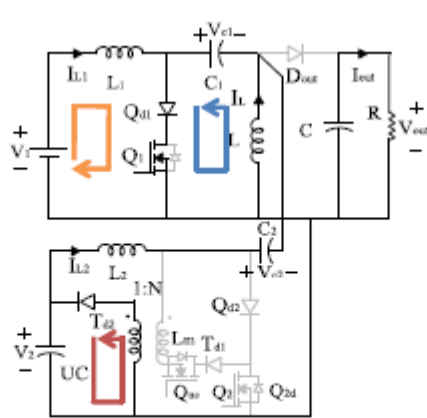


Mode 2 ($q_1(t)=1, q_{uc}(t)=0$)

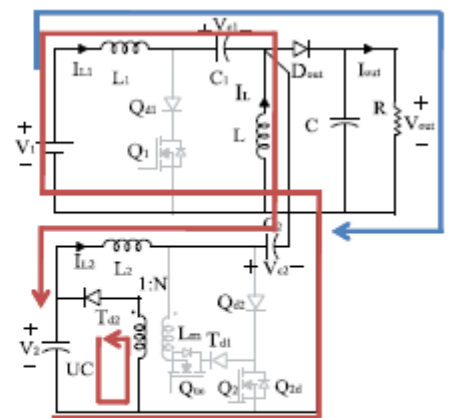


Mode 3 ($q_1(t)=0, q_{uc}(t)=0$)


Charge mode

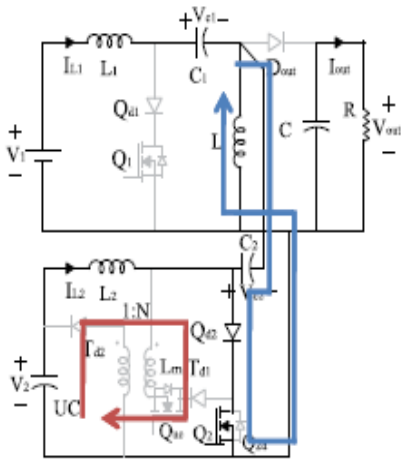

Mode 1 ($q_1(t)=1, q_2(t)=1$)

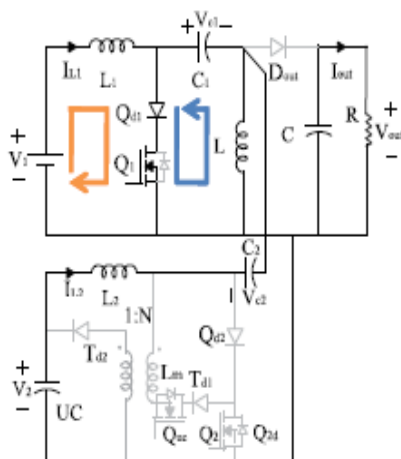


Mode 2 ($q_1(t)=1, q_2(t)=0$)

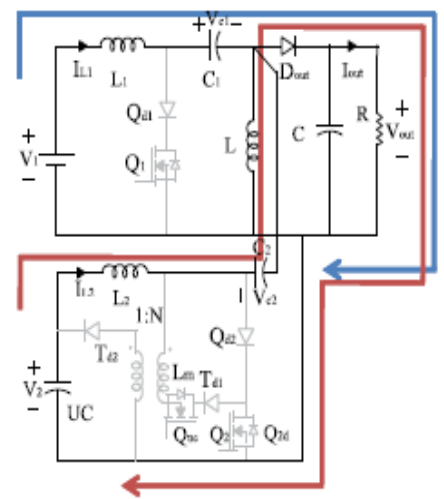

Mode 3 ($q_1(t)=0, q_2(t)=0$)

Discharge mode

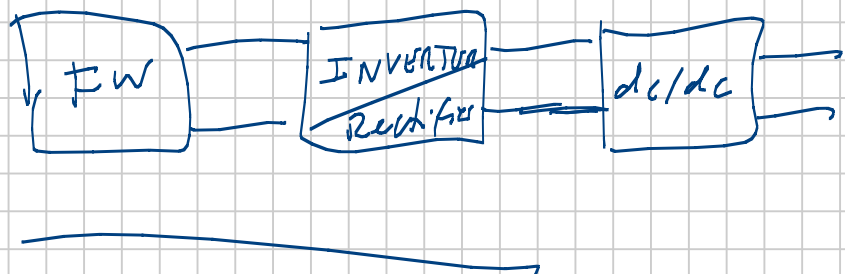For flywheel I need controlled ac as output on one side.



Let's go back to batteries,

another important need is cell balancing.

What's the problem with cell balancing?



All cells need to be kept "floating" at a given voltage.

When they discharge their voltage should not fall below a given value.

With many cells connected in series cells will have a slight voltage difference → eventually due to this voltage difference some cells may have a voltage too low and fail.

So the goal of cell balancing algorithms is to keep all cells at the same voltage.
Reference →

Battery Balancing Methods: A Comprehensive Review

Shunt active balancing → Removes extra energy from overcharged cells and transfers that energy to undercharged cells.

(see paper).