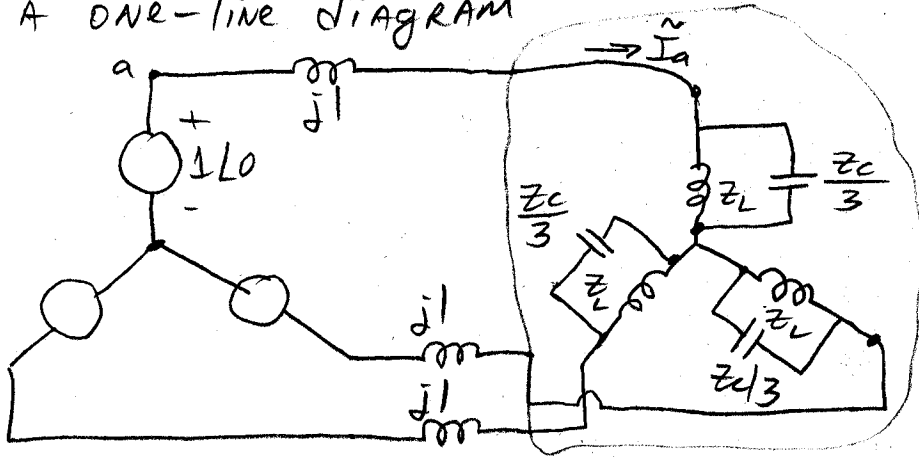



Balanced! So, convert deltas to wyes, AND DRAW A ONE-LINE DIAGRAM



$Z_L = j10$
 $Z_C = -j10$

"The load" (3φ)

One-line

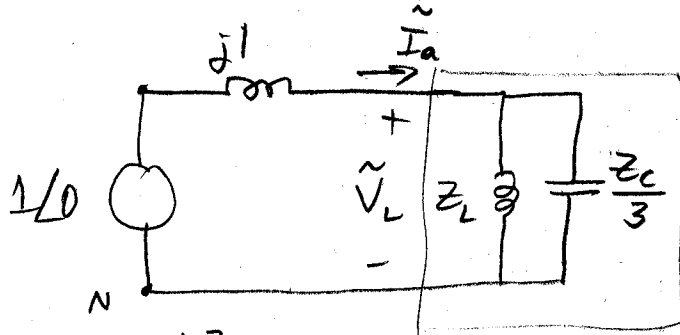

"The load" (one-line)

$$\tilde{V}_L = 1\angle 0 \left[\frac{Z_L \parallel \frac{Z_C}{3}}{j1 + Z_L \parallel \frac{Z_C}{3}} \right]$$

$$Z_L \parallel \frac{Z_C}{3} = (j10) \parallel \left(\frac{-j10}{3} \right)$$

$$= \frac{(j10)(-j10/3)}{j10 - j10/3} = \frac{100/3}{j20/3} = -j5\Omega$$

$$\tilde{V}_L = 1\angle 0 \left[\frac{-j5}{j1 - j5} \right]$$

$$= 1\angle 0 \left[\frac{j5}{-j4} \right] = 1.25\angle 0 \text{ (yes, the voltage can rise when caps ARE in the circuit!)}$$

Now, $\tilde{I}_a = \frac{1\angle 0}{j1 - j5} = \frac{1\angle 0}{-j4} = j0.25 \text{ A}$

So $S_{1\phi \text{ source}} = V_{an} I_a^* = (1\angle 0)(-j0.25) = -j0.25 \text{ VA}$

$S_{3\phi \text{ source}} = 3S_{1\phi \text{ source}} = -j0.75 \text{ VA} = -0.75 \text{ VAR}$ ← supplied by the source

$$\tilde{I}_{\text{CAP } 10} = \frac{\tilde{V}_L}{Z_C/3} = \frac{1.25\angle 0}{-j10/3} = j \frac{3(1.25)}{10} = j0.375 \text{ A}$$

Now, the \tilde{I}_{cap} in the picture is \tilde{I}_{ab} in a delta,
 We solved for \tilde{I}_{an} in a wye. From the three-
 phase phasor diagram, we know that

$$\tilde{I}_{ab} = \frac{\tilde{I}_{an}}{\sqrt{3}} \cdot 1 \angle 30 = \frac{j0.375}{\sqrt{3}} \cdot 1 \angle 30 = 0.217 \angle 120^\circ \text{ A}$$

For the load S,

$$S_{LOAD} = V_{LOAD} I_a^* = (1.25)(-j0.25) = -j0.313 \text{ VA} = -0.313 \text{ VAR}$$

$$S_{3\phi} = 3 S_{1\phi} = -0.939 \text{ VAR}$$

Now, let's check for conservation of P, Q in 1ϕ
 Supplied by source

$$P = 0$$

$$Q = -0.25$$

Consumed by the Load

$$P = 0$$

$$Q = -0.313 \text{ VAR}$$

Consumed by line $j1$

$$Q = I^2 X = (0.25)^2 (1) = 0.0625$$

$$-0.25 \stackrel{?}{=} -0.313 + 0.0625 \quad \text{OK } \checkmark$$