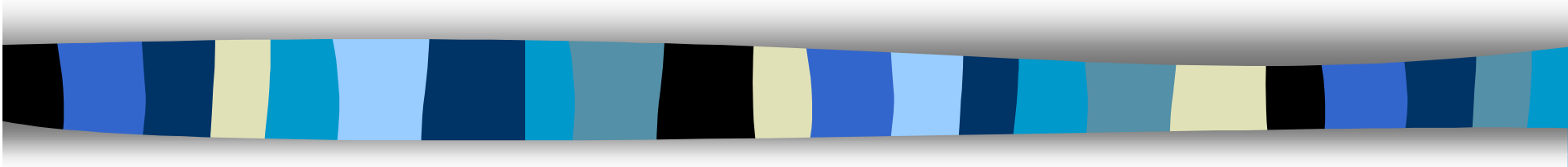


# CycleSim: A Phase-Locked Loop Simulator



Norman James  
Embedded Systems  
November 1999




# Phase-Locked Loop (PLL)


## Primer

- Used for clock generation/distribution in computers
- Capable of frequency multiplication and phase alignment of clocks
- Can be implemented as a separate clock chip or internal to a microprocessor, ASIC, etc.

# Clock Distribution Example

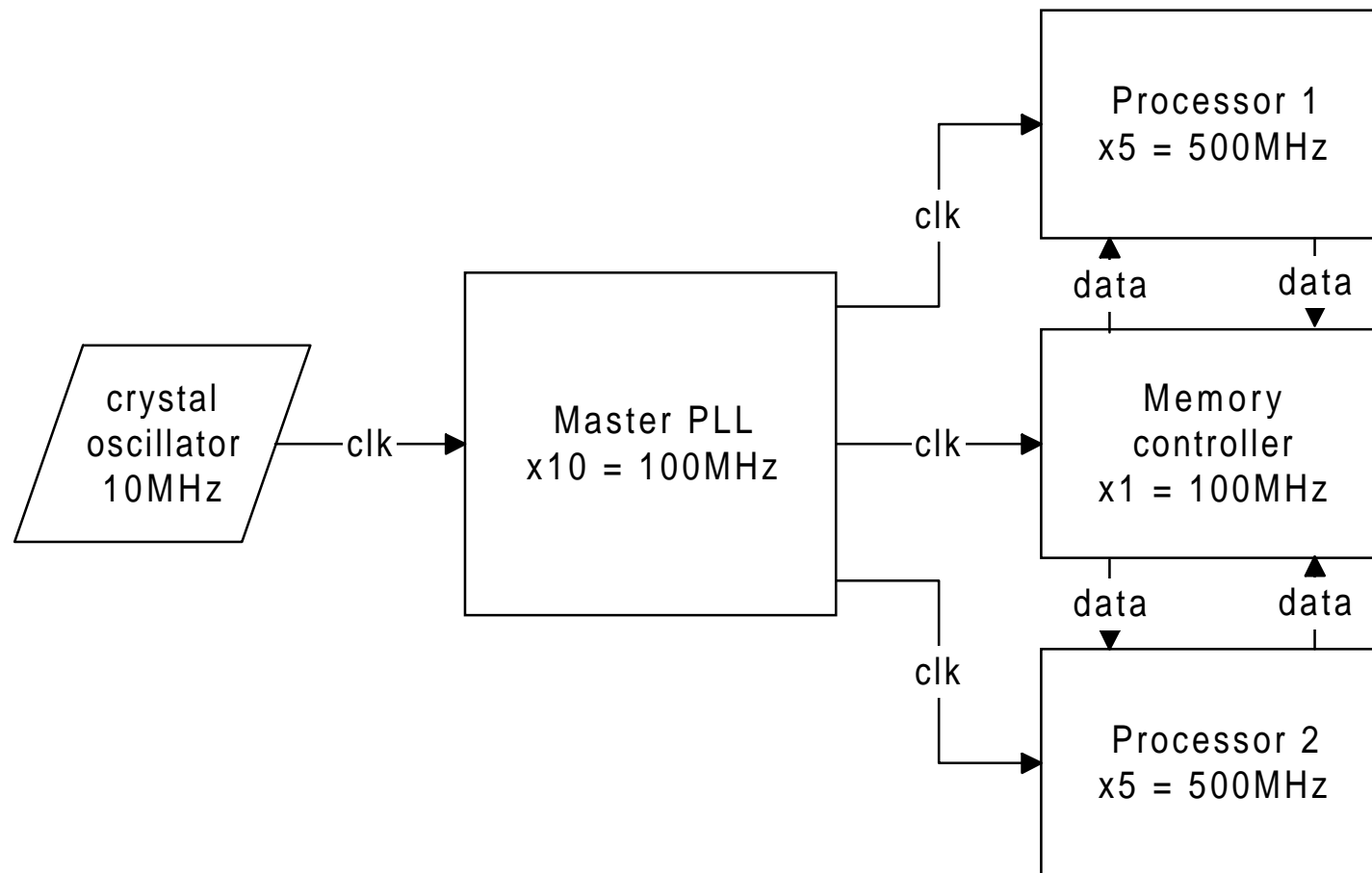

- **PFD (phase-frequency detector) generates up or down pulses depending on whether the feedback is leading or lagging the reference. The pulse is proportional to the phase difference**
- **Charge pump converts the pulses to current and pumps the filter up or down.**
- **The VCO (voltage-controlled oscillator) uses the voltage on the filter to control its frequency**
- **The divider frequency divides the clock**

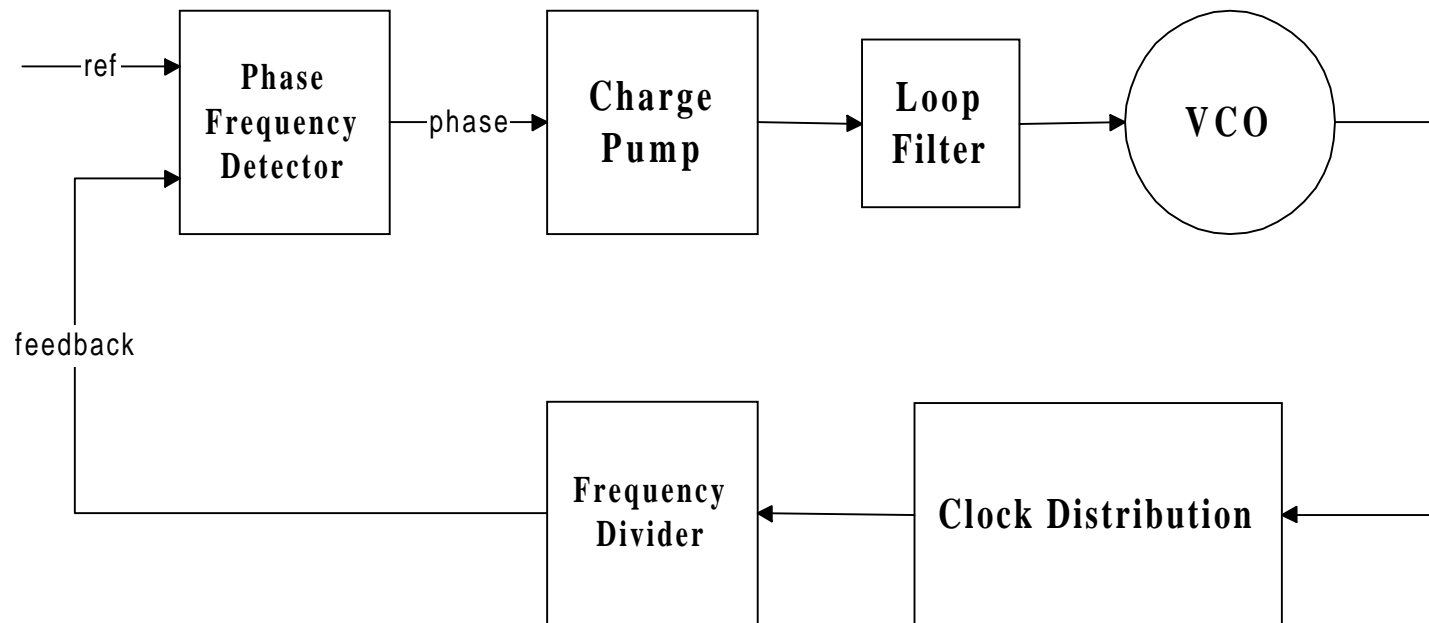



# PLL Performance

- Cycle-to-cycle and period jitter (clock accuracy)
- Long-term jitter
- Loop bandwidth
- Must be independent of multiplier



# Current methods of PLL simulation

Tool	Domain	Pros	Cons
SPICE	time	accurate	slow for PLL sims; too much data
EESof	frequency	fast	accuracy; difficult to model
Analytical	s-domain z-domain time	fast	not accurate

## More on SPICE:


- **PLL's have clock frequencies of  $> 1\text{GHz}$  and loop bandwidths of  $< 5\text{MHz}$**
- **Full loop simulation can take a week and generates files  $> 100\text{MB}$**



# CycleSim

- **The PLL is modeled as DDF (not statically schedulable)**
- **Implemented in C++; each object is a node**
- **Clock sources such as VCO and reference have tokens that represent time tags**
  - **Time tags represent the point in time at which a clock waveform crosses a threshold on a rising edge**
- **Each iteration of the simulation is one cycle of the clock sources**
- **During each iteration the time tags are adjusted accordingly**
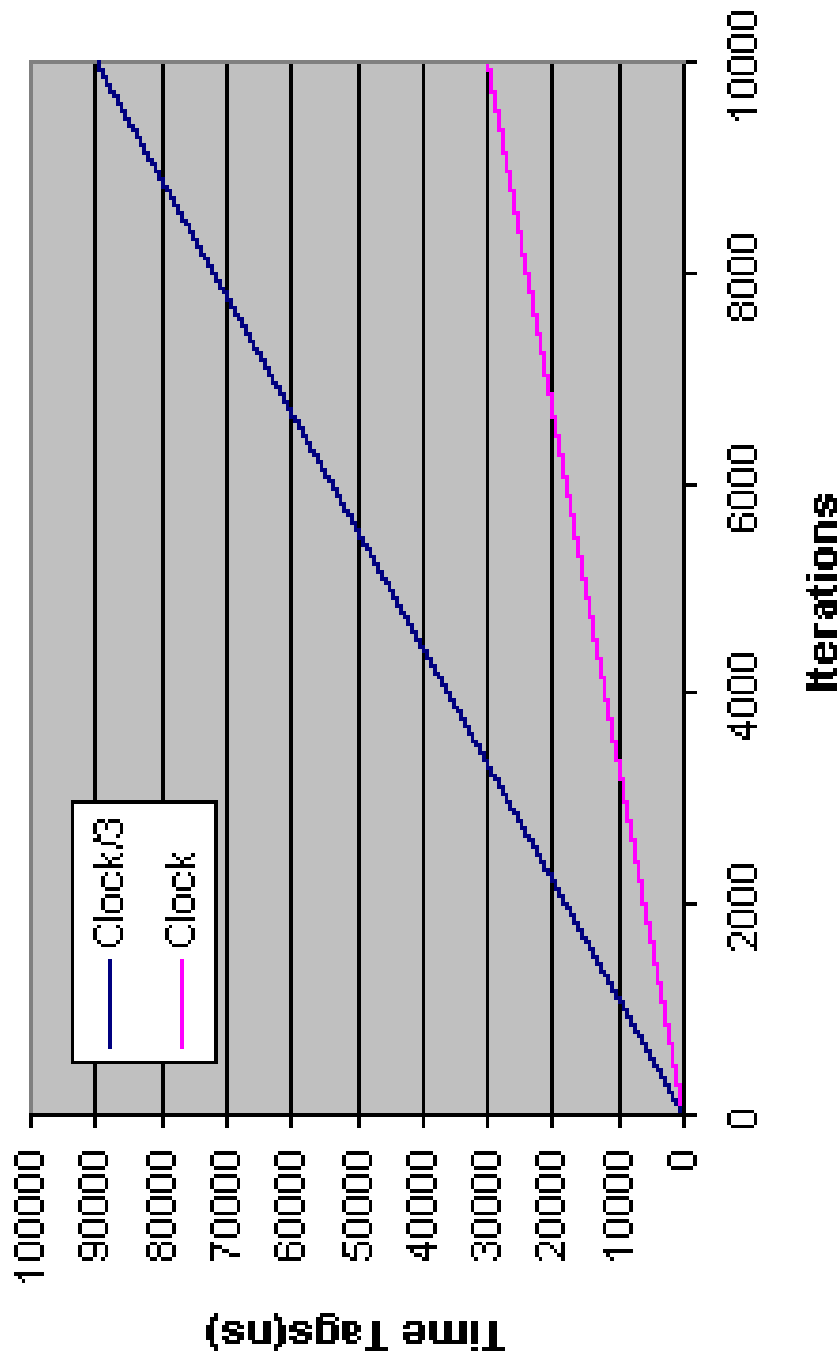
## Time Tags for Clks with 3:1 Frequency Ratio









## CycleSim (part 2)

- Reference clock - produces periodic time tags
- Phase-frequency detector - outputs phase difference between the reference clock and the divider
- Charge pump - integrates current over the phase difference and produces a change in voltage
- Loop filter - accumulates changes in voltage off charge pump
- VCO - uses voltage from loop filter to produce an output time tag

# PLL Lock Sim

 

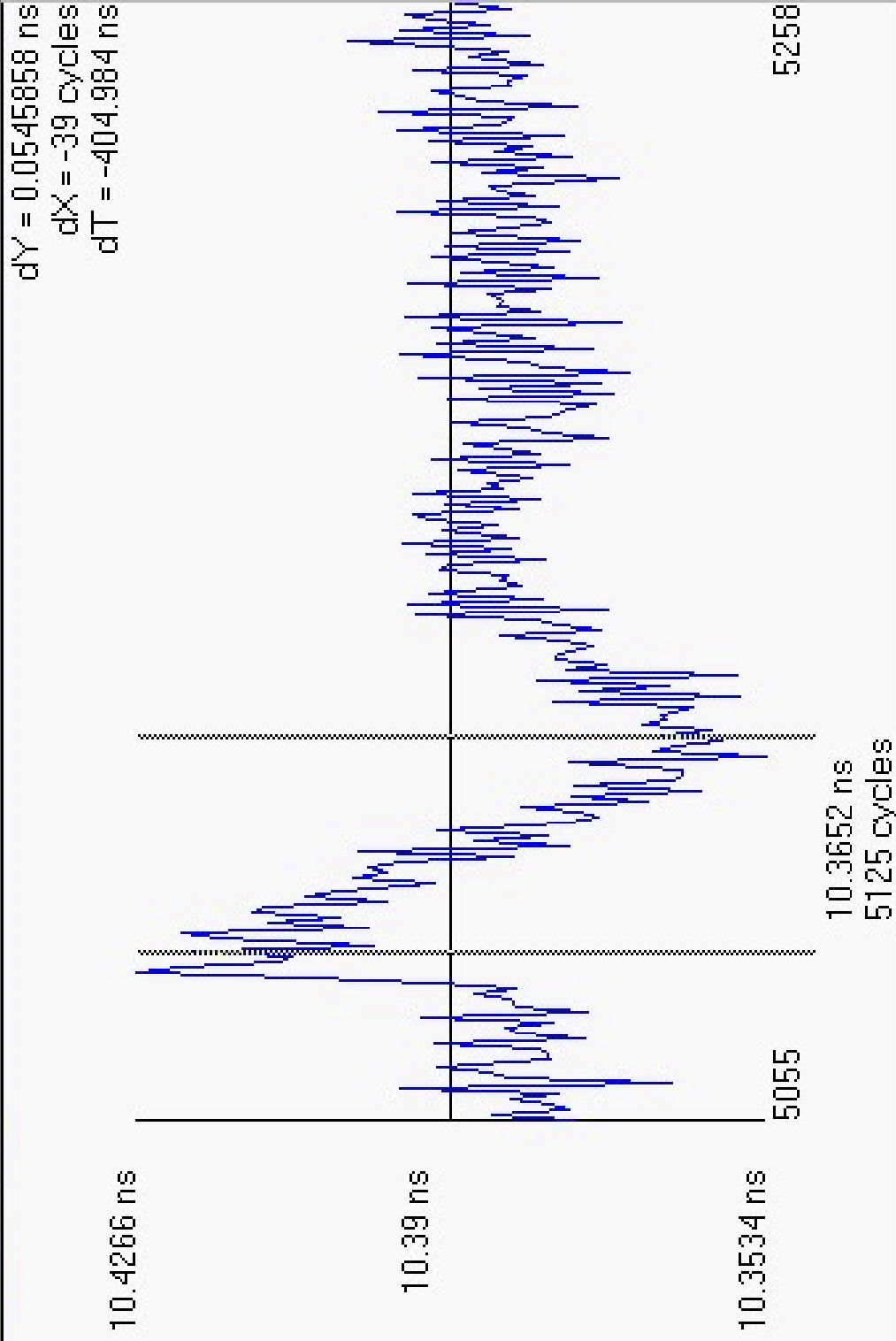

Acquisitions:

1 of 1

Cycles:

5055:5259

Max:

10.427 ns

Min:

10.353 ns

Mean:

10.384 ns


Peak-Peak:

0.073265 ns

Standard Dev:

0.012504 ns

# PLL Tracking a Noise Event on the VCO

 



# Conclusions

- PLL's are mixed signal circuits which makes them difficult to simulate, especially in the time domain
- The cycle domain is more "natural" for describing PLL's as clock sources
- CycleSim is several orders of magnitudes faster than SPICE making it easy to fine tune current designs and explore new ones