

7. Combinational Circuits

- Last module:
 - Delay in logic networks
 - Logical Effort
 - Choosing the best number of stages
- This module:
 - Designing CMOS gate networks
 - Speeding up combinational gates

D. Z. Pan 7. Combinational Circuits 1

Example 1

```

module mux(input s, d0, d1,
           output y);

    assign y = s ? d1 : d0;
endmodule
    
```

1) Sketch a design using AND, OR, and NOT gates.

D. Z. Pan 7. Combinational Circuits 2

Example 2

2) Sketch a design using NAND, NOR, and NOT gates. Assume $\sim S$ is available.

D. Z. Pan 7. Combinational Circuits 3

Bubble Pushing

- Start with network of AND / OR gates
- Convert to NAND / NOR + inverters
- Push bubbles around to simplify logic
 - Use DeMorgan's Law

D. Z. Pan 7. Combinational Circuits 4

Example 3

3) Sketch a design using one compound gate and one NOT gate. Assume $\sim S$ is available.

D. Z. Pan 7. Combinational Circuits 5

Compound Gates


- Logical Effort of compound gates

unit inverter	AOI21	AOI22	Complex AOI
$Y = \overline{A}$	$Y = \overline{A \cdot B + C}$	$Y = \overline{A \cdot B + C \cdot D}$	$Y = \overline{A \cdot (B + C) + D \cdot E}$
$g_A = 3/3$ $p = 3/3$	$g_A = 6/3$ $g_B = 6/3$ $g_C = 5/3$ $p = 7/3$	$g_A = 6/3$ $g_B = 6/3$ $g_C = 6/3$ $g_D = 6/3$ $p = 12/3$	$g_A = 5/3$ $g_B = 8/3$ $g_C = 8/3$ $g_D = 8/3$ $g_E = 8/3$ $p = 16/3$

D. Z. Pan 7. Combinational Circuits 6

 Example 4


- The multiplexer has a maximum input capacitance of 16 units on each input. It must drive a load of 160 units. Estimate the delay of the NAND and compound gate designs.



$H = 160 / 16 = 10$
 $B = 1$
 $N = 2$


NAND Solution

 $P = 2 + 2 = 4$
 $G = (4/3)(4/3) = 16/9$
 $F = GBH = 160/9$
 $\hat{f} = \sqrt[3]{F} = 4.2$
 $D = N\hat{f} + P = 12.4\tau$




Compound Solution

$P = 4 + 1 = 5$
 $G = (6/3)(1) = 2$
 $F = GBH = 20$
 $\hat{f} = \sqrt[3]{F} = 4.5$
 $D = N\hat{f} + P = 14\tau$

 

 Example 5


- Annotate your designs with transistor sizes that achieve this delay.



16 $160 * (4/3) / 4.2 = 50$ 16 $160 * 1 / 4.5 = 36$


Input Order

 - Our parasitic delay model was too simple
 - Calculate parasitic delay for Y falling
 - If A arrives latest? 2τ
 - If B arrives latest? 2.33τ



Inner & Outer Inputs

 
- Inner input is closest to output (A)
- Outer input is closest to rail (B)



- If input arrival time is known
 - Connect latest input to inner terminal

Asymmetric Gates

 - Asymmetric gates favor one **input** over another
- Example: Suppose input A of a NAND gate is most critical
 - Use smaller transistor on A (less capacitance)
 - Boost size of noncritical input
 - So total resistance is same




- $g_A = 10/9$
- $g_B = 2$
- $g_{total} = g_A + g_B = 28/9$
- Asymmetric gate approaches $g = 1$ on critical input
- But total logical effort goes up

D. Z. Pan 7. Combinational Circuits 13

Symmetric Gates


- Inputs can be made perfectly symmetric

 

 D. Z. Pan 7. Combinational Circuits 14

Skewed Gates

- Skewed gates favor one **edge** over another
- Ex: suppose rising output of inverter is most critical
 - Downsize noncritical nMOS transistor



- Calculate logical effort by comparing to unskewed inverter with same effective resistance on that edge.
 - $g_{Hi} = 2.5 / 3 = 5/6$
 - $g_{Lo} = 2.5 / 1.5 = 5/3$


D. Z. Pan 7. Combinational Circuits 15

HI- and LO-Skew

- Logical effort of a skewed gate for a particular transition is the ratio of the input capacitance of that gate to the input capacitance of an unskewed inverter delivering the same output current for the same transition
- Skewed gates reduce size of noncritical transistors
 - HI-skew gates favor rising output (small nMOS)
 - LO-skew gates favor falling output (small pMOS)
- Logical effort is smaller for favored direction
- But larger for the other direction

D. Z. Pan 7. Combinational Circuits 16


Catalog of Skewed Gates

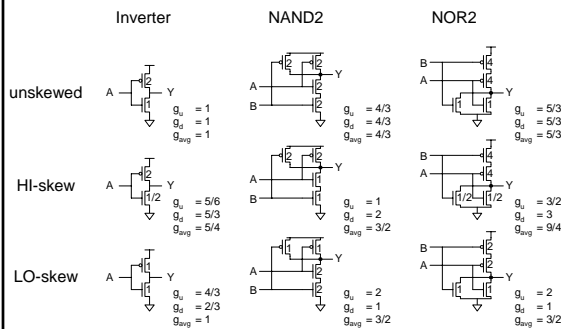

 D. Z. Pan 7. Combinational Circuits 17

Asymmetric Skew

- Combine asymmetric and skewed gates
 - Downsize noncritical transistor on unimportant input
 - Reduces parasitic delay for critical input



D. Z. Pan 7. Combinational Circuits 18

Best P/N Ratio for Least Avg Delay

- We have selected P/N ratio for unit rise and fall resistance ($\mu = 2-3$ for an inverter).
- Alternative: ratio for least average delay
- Ex: inverter
 - Delay driving identical inverter
 - $t_{pdf} = (P+1)$
 - $t_{pdr} = (P+1)(\mu/P)$
 - $t_{pd} = (P+1)(1+\mu/P)/2 = (P + 1 + \mu + \mu/P)/2$
 - Differentiate t_{pd} w.r.t. P
 - Least delay for $P = \sqrt{\mu}$




D. Z. Pan

 7. Combinational Circuits 19

P/N Ratios

- In general, best P/N ratio for lowest avg delay is the square root of that giving equal delay
 - Only improves average delay slightly for inverters
 - But significantly decreases area and power for NOR



- In practice, P/N ratio consideration not really average delay

D. Z. Pan

7. Combinational Circuits 20