

CHAPTER 17

Solutions for Exercises

E17.1 From Equation 17.5, we have

$$B_{\text{gap}} = K i_a(t) \cos(\theta) + K i_b(t) \cos(\theta - 120^\circ) + K i_c(t) \cos(\theta - 240^\circ)$$

Using the expressions given in the Exercise statement for the currents, we have

$$B_{\text{gap}} = K I_m \cos(\omega t) \cos(\theta) + K I_m \cos(\omega t - 240^\circ) \cos(\theta - 120^\circ) \\ + K I_m \cos(\omega t - 120^\circ) \cos(\theta - 240^\circ)$$

Then using the identity for the products of cosines, we obtain

$$B_{\text{gap}} = \frac{1}{2} K I_m [\cos(\omega t - \theta) + \cos(\omega t + \theta) + \cos(\omega t - \theta - 120^\circ) \\ + \cos(\omega t + \theta - 360^\circ) + \cos(\omega t - \theta + 120^\circ) \\ + \cos(\omega t + \theta - 360^\circ)]$$

However we can write

$$\cos(\omega t - \theta) + \cos(\omega t - \theta - 120^\circ) + \cos(\omega t - \theta + 120^\circ) = 0 \\ \cos(\omega t + \theta - 360^\circ) = \cos(\omega t + \theta) \\ \cos(\omega t + \theta - 360^\circ) = \cos(\omega t + \theta)$$

Thus we have

$$B_{\text{gap}} = \frac{3}{2} K I_m \cos(\omega t + \theta)$$

which can be recognized as flux pattern that rotates clockwise.

E17.2 At 60 Hz, synchronous speed for a four-pole machine is:

$$n_s = \frac{120f}{p} = \frac{120(60)}{4} = 1800 \text{ rpm}$$

The slip is given by:

$$s = \frac{n_s - n_m}{n_s} = \frac{1800 - 1750}{1800} = 2.778\%$$

The frequency of the rotor currents is the slip frequency. From Equation

17.17, we have $\omega_{\text{slip}} = s\omega$. For frequencies in the Hz, this becomes:

$$f_{\text{slip}} = sf = 0.02778 \times 60 = 1.667 \text{ Hz}$$


In the normal range of operation, slip is approximately proportional to output power and torque. Thus at half power, we estimate that $s = 2.778/2 = 1.389\%$. This corresponds to a speed of 1775 rpm.

E17.3 Following the solution to Example 17.1, we have:

$$n_s = 1800 \text{ rpm}$$

$$s = \frac{n_s - n_m}{n_s} = \frac{1800 - 1764}{1800} = 0.02$$

The per phase equivalent circuit is:

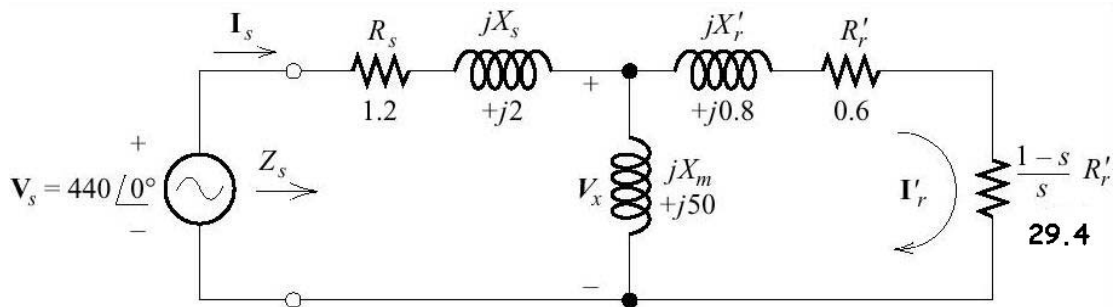

$$\begin{aligned} Z_s &= 1.2 + j2 + \frac{j50(0.6 + 29.4 + j0.8)}{j50 + 0.6 + 29.4 + j0.8} \\ &= 22.75 + j15.51 \\ &= 27.53 \angle 34.29^\circ \end{aligned}$$

$$\text{power factor} = \cos(34.29^\circ) = 82.62\% \text{ lagging}$$

$$\mathbf{I}_s = \frac{\mathbf{V}_s}{Z_s} = \frac{440 \angle 0^\circ}{27.53 \angle 34.29^\circ} = 15.98 \angle -34.29^\circ \text{ A rms}$$

For a delta-connected machine, the magnitude of the line current is

$$I_{\text{line}} = I_s \sqrt{3} = 15.98 \sqrt{3} = 27.68 \text{ A rms}$$

and the input power is

$$P_{\text{in}} = 3I_s V_s \cos \theta = 17.43 \text{ kW}$$

Next, we compute V_x and I_r' .

$$\begin{aligned}V_x &= \mathbf{I}_s \frac{j50(0.6 + 29.4 + j0.8)}{j50 + 0.6 + 29.4 + j0.8} \\&= 406.2 - j15.6 \\&= 406.4 \angle -2.2^\circ \text{ V rms}\end{aligned}$$

$$\begin{aligned}\mathbf{I}_r' &= \frac{V_x}{j0.8 + 0.6 + 29.4} \\&= 13.54 \angle -3.727^\circ \text{ A rms}\end{aligned}$$

The copper losses in the stator and rotor are:

$$\begin{aligned}P_s &= 3R_s I_s^2 \\&= 3(1.2)(15.98)^2 \\&= 919.3 \text{ W}\end{aligned}$$

and

$$\begin{aligned}P_r &= 3R_r'(I_r')^2 \\&= 3(0.6)(13.54)^2 \\&= 330.0 \text{ W}\end{aligned}$$

Finally, the developed power is:

$$\begin{aligned}P_{\text{dev}} &= 3 \times \frac{1-s}{s} R_r'(I_r')^2 \\&= 3(29.4)(13.54)^2 \\&= 16.17 \text{ kW} \\P_{\text{out}} &= P_{\text{dev}} - P_{\text{rot}} = 15.27 \text{ kW}\end{aligned}$$



The output torque is:

$$T_{\text{out}} = \frac{P_{\text{out}}}{\omega_m} = 82.66 \text{ newton meters}$$

The efficiency is:

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\% = 87.61\%$$

E17.4 The equivalent circuit is:

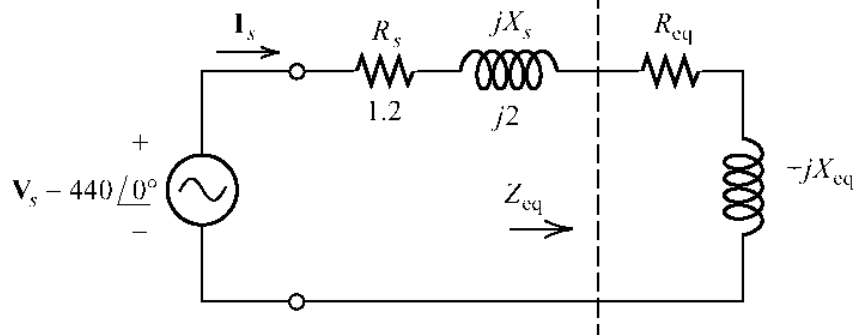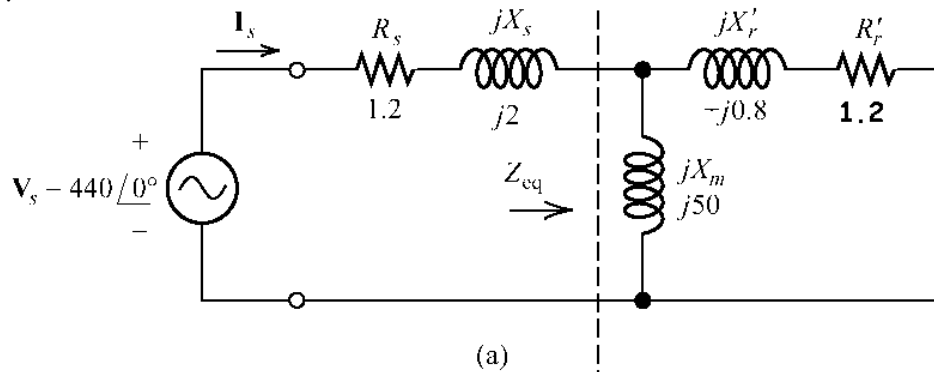

$$Z_{eq} = R_{eq} + jX_{eq} = \frac{j50(1.2 + j0.8)}{j50 + 1.2 + j0.8} = 1.162 + j0.8148$$

The impedance seen by the source is:

$$\begin{aligned} Z_s &= 1.2 + j2 + Z_{eq} \\ &= 1.2 + j2 + 1.162 + j0.8148 \\ &= 3.675 \angle 50.00^\circ \end{aligned}$$

Thus, the starting phase current is

$$I_{s, \text{starting}} = \frac{V_s}{Z_s} = \frac{440 \angle 0^\circ}{3.675 \angle 50.00^\circ}$$

$$I_{s, \text{starting}} = 119.7 \angle -50.00^\circ \text{ A rms}$$

and for a delta connection, the line current is

$$I_{\text{line, starting}} = I_{s, \text{starting}} \sqrt{3} = 119.7 \sqrt{3} = 207.3 \text{ A rms}$$

The power crossing the air gap is (three times) the power delivered to the right of the dashed line in the equivalent circuit shown earlier.

$$P_{ag} = 3R_{eq} (I_{s, \text{starting}})^2 = 49.95 \text{ kW}$$

Finally, the starting torque is found using Equation 17.34.

$$\begin{aligned} T_{\text{dev, starting}} &= \frac{P_{\text{ag}}}{\omega_s} \\ &= \frac{49950}{2\pi 60/2} \\ &= 265.0 \text{ newton meters} \end{aligned}$$

E17.5 This exercise is similar to part (c) of Example 17.4. Thus, we have

$$\begin{aligned} \frac{\sin \delta_3}{\sin \delta_1} &= \frac{P_3}{P_1} \\ \frac{\sin \delta_3}{\sin 4.168^\circ} &= \frac{200}{50} \end{aligned}$$

which yields the new torque angle $\delta_3 = 16.90^\circ$. E_r remains constant in magnitude, thus we have

$$\begin{aligned} \mathbf{E}_{r3} &= 498.9 \angle -16.90^\circ \text{ V rms} \\ \mathbf{I}_{a3} &= \frac{\mathbf{V}_a - \mathbf{E}_{r3}}{jX_s} = \frac{480 - 498.9 \angle -16.90^\circ}{j1.4} = 103.6 \angle -1.045^\circ \text{ A rms} \end{aligned}$$

The power factor is $\cos(-1.045^\circ) = 99.98\%$ lagging.

E17.6 We follow the approach of Example 17.5. Thus as in the example, we have

$$\begin{aligned} I_{a1} &= \frac{P_{\text{dev}}}{3V_a \cos \theta_1} = \frac{74600}{3(240)0.85} = 121.9 \text{ A} \\ \theta_1 &= \cos^{-1}(0.85) = 31.79^\circ \\ \mathbf{I}_{a1} &= 121.9 \angle -31.79^\circ \text{ A rms} \\ \mathbf{E}_{r1} &= \mathbf{V}_a - jX_s \mathbf{I}_{a1} = 416.2 \angle -20.39^\circ \text{ V rms} \end{aligned}$$

The phasor diagram is shown in Figure 17.24a

For 90% leading power factor, the power angle is $\theta_3 = \cos^{-1}(0.9) = 25.84^\circ$.

The new value of the current magnitude is

$$I_{a3} = \frac{P_{\text{dev}}}{3V_{a3} \cos(\theta_3)} = 115.1 \text{ A rms}$$

and the phasor current is

$$\mathbf{I}_{a3} = 115.1 \angle 25.84^\circ \text{ A rms}$$

Thus we have

$$\mathbf{E}_{r3} = \mathbf{V}_a - jX_s \mathbf{I}_{a3} = 569.0 \angle -14.77^\circ \text{ V rms}$$

The magnitude of E_r is proportional to the field current, so we have:

$$I_{f3} = I_{f1} \frac{E_{r3}}{E_{r1}} = 10 \times \frac{569.0}{416.2} = 13.67 \text{ A dc}$$

E17.7 The phasor diagram for $\delta = 90^\circ$ is shown in Figure 17.27. The developed power is given by

$$P_{\max} = 3V_a I_a \cos(\theta)$$

However from the phasor diagram, we see that

$$\cos(\theta) = \frac{E_r}{X_s I_a}$$

Substituting, we have

$$P_{\max} = \frac{3V_a E_r}{X_s}$$

The torque is

$$T_{\max} = \frac{P_{\max}}{\omega_m} = \frac{3V_a E_r}{\omega_m X_s}$$

Answers for Selected Problems


P17.1* $P = 8$ pole motor
 $s = 5.55\%$

P17.7* $f = 86.8$ Hz
 $I = 5.298$ A

P17.10* As frequency is reduced, the reactances X_s , X_m , and X_r' of the machine become smaller. (Recall that $X = \omega L$.) Thus the applied voltage must be reduced to keep the currents from becoming too large, resulting in magnetic saturation and overheating.

P17.13* $B_{\text{four-pole}} = B_m \cos(\omega t - 2\theta)$
 $B_{\text{six-pole}} = B_m \cos(\omega t - 3\theta)$

P17.16*

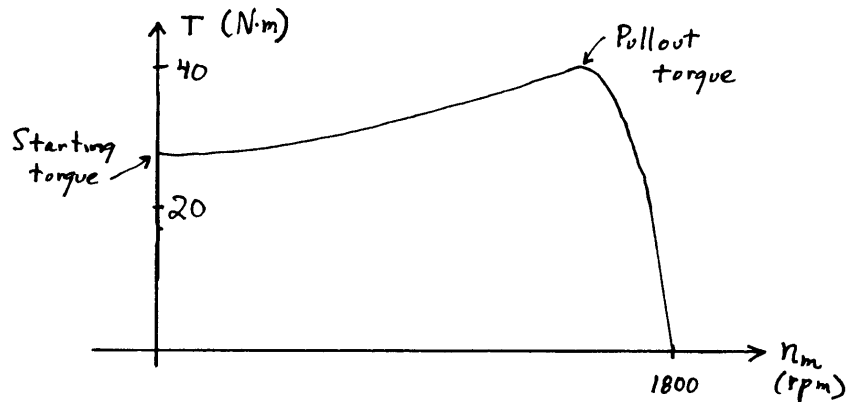

$$I_{line} = 16.3 \text{ A rms}$$

Typically the starting current is 5 to 7 times the full-load current.

P17.20* $I_{line, starting} = 115.0 \text{ A rms}$

$$T_{dev, starting} = 40.8 \text{ newton meters}$$

Comparing these results to those of the example, we see that the starting current is reduced by a factor of 2 and the starting torque is reduced by a factor of 4.

P17.23* Neglecting rotational losses, the slip is zero with no load, and the motor runs at synchronous speed which is 1800 rpm.

The power factor is 2.409%.

$$I_{line} = 10 \text{ A rms}$$

P17.26* The motor runs at synchronous speed which is 1200 rpm.

The power factor is 1.04%.

$$I_{line} = 98.97 \text{ A rms}$$

P17.29* $P_{ag} = 9.893 \text{ kW}$

$$P_{dev} = 9.773 \text{ kW}$$

$$P_{out} = 9.373 \text{ kW}$$


$$\eta = 91.51\%$$

P17.32* $P_{rot} = 76.12 \text{ W}$

- P17.35***
1. Use an electronic system to convert 60-Hz power into three-phase ac of variable frequency. Start with a frequency of one hertz or less and then gradually increase the frequency.
 2. Use a prime mover to bring the motor up to synchronous speed before connecting the source.
 3. Start the motor as an induction motor relying on the amortisseur conductors to produce torque.

- P17.38***
- (a) Field current remains constant. The field circuit is independent of the ac source and the load.
 - (b) Mechanical speed remains constant assuming that the pull-out torque has not been exceeded.
 - (c) Output torque increases by a factor of $1/0.75 = 1.333$.
 - (d) Armature current increases in magnitude.
 - (e) Power factor decreases and becomes lagging.
 - (f) Torque angle increases.


P17.41*

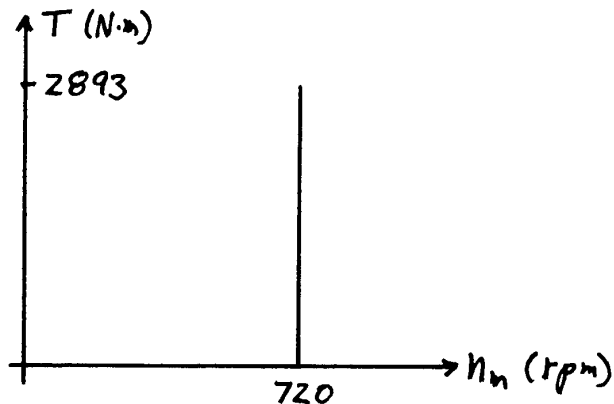

P17.44* $I_{f2} = 5.93 \text{ A}$

P17.47* (a) $f_{\text{gen}} = 50 \text{ Hz}$

(b)

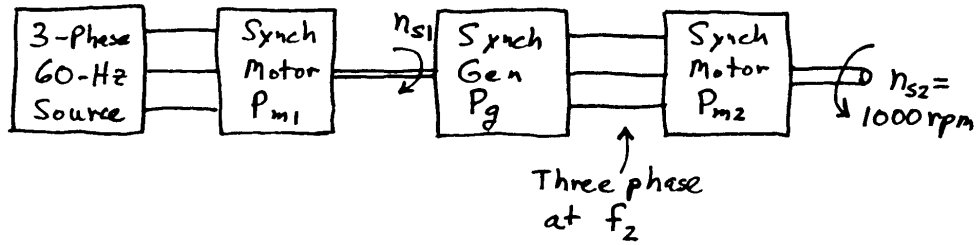

One solution is:

$$P_g = 10 \quad P_{m1} = 12 \quad \text{and} \quad P_{m2} = 6$$

for which $f_2 = 50 \text{ Hz}$.

Another solution is:

$$P_g = 10 \quad P_{m1} = 6 \quad \text{and} \quad P_{m2} = 12$$

for which $f_2 = 100 \text{ Hz}$.

P17.50* (a) power factor = 76.2% lagging

(b) $Z = 11.76 \angle 40.36^\circ \Omega$

(c) Since the motor runs just under 1800 rpm, evidently we have a four-pole motor.

P17.53* The percentage drop in voltage is 7.33%.