

## ECE382M.20: System-on-Chip (SoC) Design

---

### Lecture 7 – High-Level Synthesis

*Sources: Jacob Abraham*

*D. Gajski, S. Abdi, A. Gerstlauer, G. Schirner,  
"Embedded System Design: Modeling, Synthesis, Verification,"  
Chapter 6: Hardware Synthesis, Springer, 2009.*

Andreas Gerstlauer

Electrical and Computer Engineering

The University of Texas at Austin

gerstl@ece.utexas.edu



The University of Texas at Austin

Chandra Department of Electrical  
and Computer Engineering

Cockrell School of Engineering

---

### Lecture 7: Outline


---



- **Introduction**
  - High-level synthesis (HLS)
- **Essential issues**
  - Behavioral specification languages
  - Target architectures
  - Intermediate representation
  - Scheduling/allocation/binding
  - Control generation
- **High-level synthesis flow**
  - Synthesis example


## High Level Synthesis (HLS)

- **Convert a high-level description of a design to a RTL netlist**
  - **Input:**
    - High-level languages (e.g., C)
    - Behavioral hardware description languages (e.g., VHDL)
    - State diagrams / logic networks
  - **Tools:**
    - Parser
    - Library of modules
  - **Constraints:**
    - Area constraints (e.g., # modules of a certain type)
    - Delay constraints (e.g., set of operations should finish in  $\lambda$  clock cycles)
  - **Output:**
    - Operation scheduling (time) and binding (resource)
    - Control generation and detailed interconnections

## High Level Synthesis

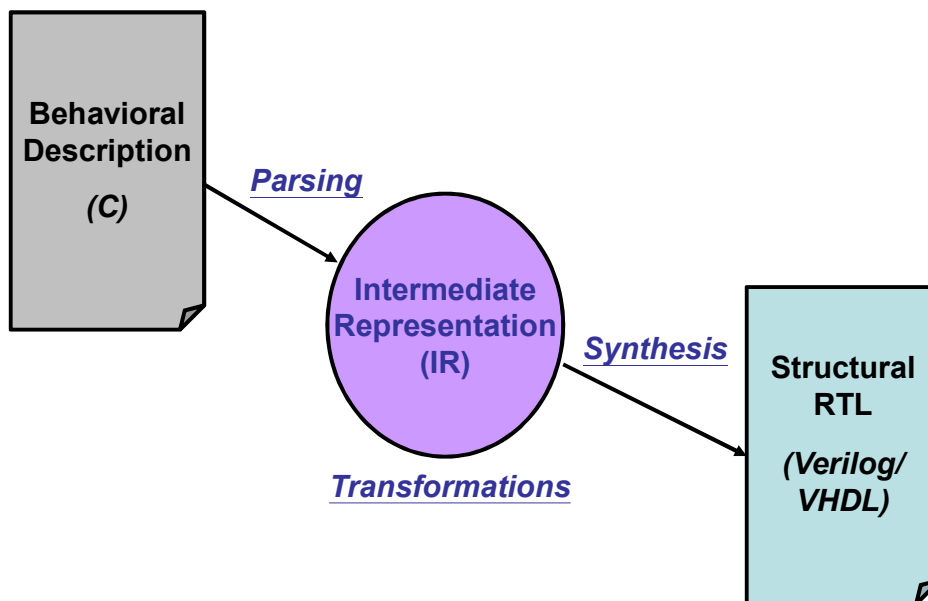

  

 

## Lecture 7: Outline

### ✓ Introduction

✓ High-level synthesis

### • Essential issues

- Behavioral specification languages
- Target architectures
- Intermediate representation
- Scheduling/allocation/binding
- Control generation


### • High-level synthesis flow

- Synthesis example


## Behavioral Specification Languages

- **First HLS approaches (90's)**
  - Popular HDL
    - Verilog, VHDL
  - Synthesis-oriented HDLs
    - UDL/I
- **Recent resurgence (00's)**
  - Popular legacy programming languages
    - C/C++
  - Add hardware-specific constructs to existing languages
    - SystemC


## Target Architecture

 

Finite-State Machine with Data Path

 

## Design Space Exploration

 

ECE382M.20: SoC Design, Lecture 7

© Jacob Abraham, UT Austin

11

## Design Space and Quality Measures


- **Design space**
  - Set of all feasible implementations
- **Quality Measures**
  - Performance
    - Cycle-time
    - Latency
    - Throughput
  - Area cost
  - Power Consumption
  - Testability
  - Reusability

ECE382M.20: SoC Design, Lecture 7

© Jacob Abraham, UT Austin

12

## Intermediate Representation

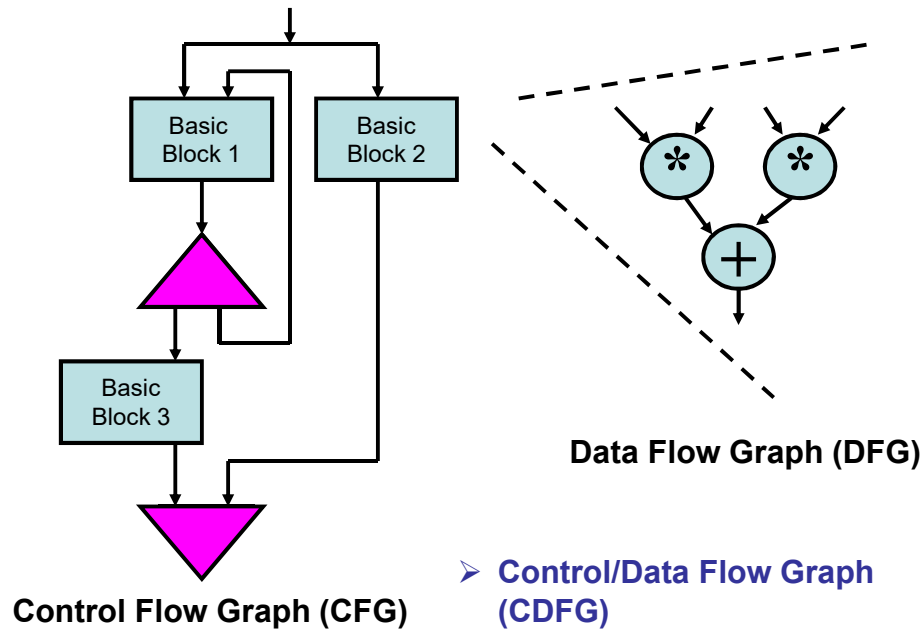

ECE382M.20: SoC Design, Lecture 7

© Jacob Abraham, UT Austin

13

## Data Flow Graph (DFG)


- **Directed acyclic graph (DAG)**
  - Data dependencies, no control/conditionals, no other order

### Original code

```
x = a + b;
y = a * c;
z = x + d;
x = y - d;
x = x + c;
```

### Single assignment form

```
x1 <= a + b;
y <= a * c;
z <= x1 + d;
x2 <= y - d;
x3 <= x2 + c;
```

 



ECE382M.20: SoC Design, Lecture 7

© Jacob Abraham, UT Austin


14
  
## Scheduling

- **Assign operations to clock cycles**
  - Single basic block / data flow graph (DFG) at a time
  - Blocks concatenated according to control flow graph (CFG)
  - Advanced scheduling techniques go beyond single blocks




Schedule A

 

Schedule B


## Scheduling Example

- **One feasible schedule for last DFG**

 




## Allocation/Binding

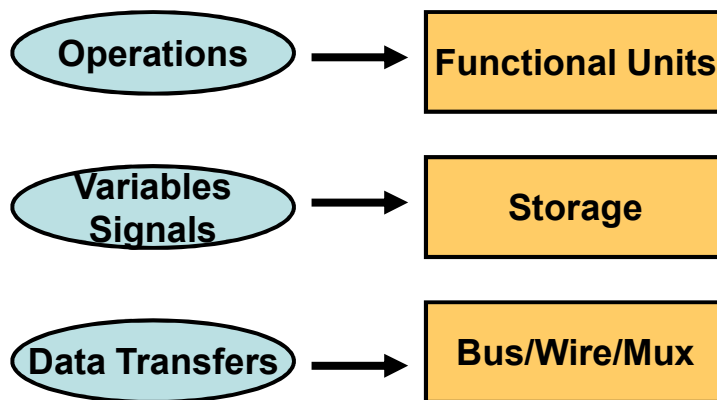


## Datapath

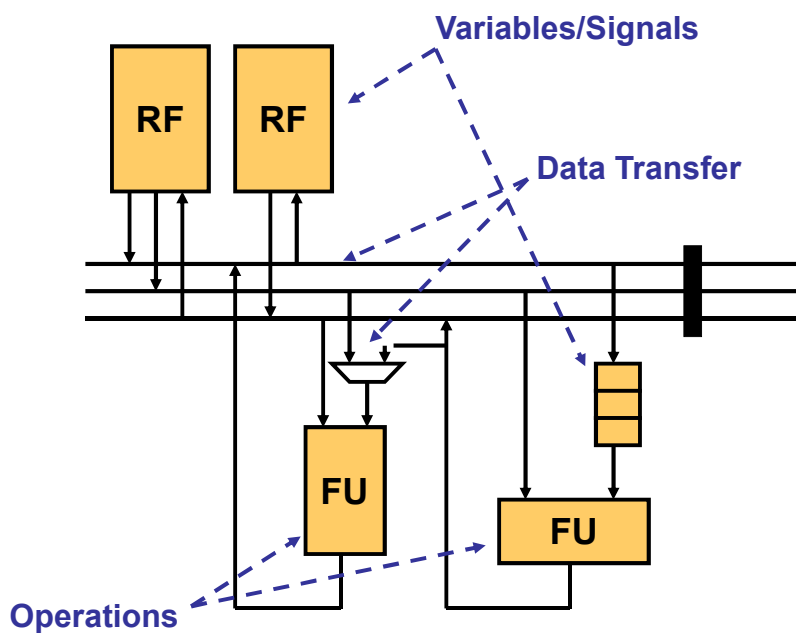

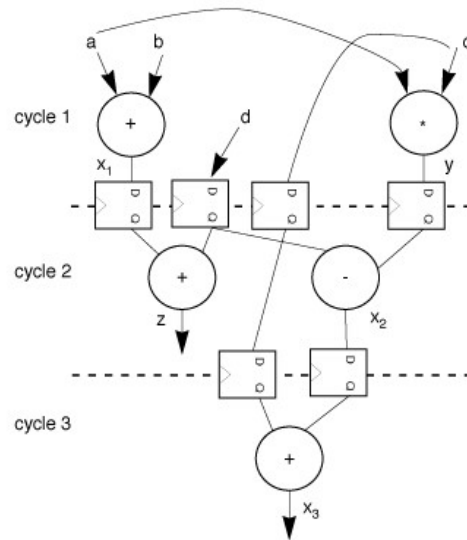
## Binding Values to Registers

- Registers fall on clock cycle boundaries



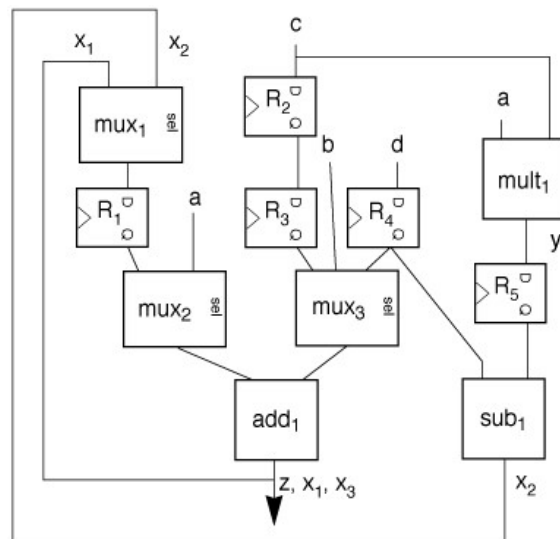
## Binding Operations to Functional Units

- Muxes allow sharing
  - Functional units (FUs) for several operations
  - Registers for several variables




## Controller Generation

 
 
## Building the Sequencer


- **Finite state machine (FSM)**
  - Driving datapath control signals
  - Multiple states/cycles even without conditionals




## Hardware Variations

- **Functional Units**
  - Pipelined
  - Multi-cycle
  - Chained
  - Multi-function
- **Storage**
  - Register, register file
  - Single-/multi-ported RAM, ROM
  - FIFO, Scratchpad
- **Interconnect**
  - Bus-based
  - Mux-based
  - Protocol-based

## Functional Unit Variations

 

## Storage/Interconnect Variations

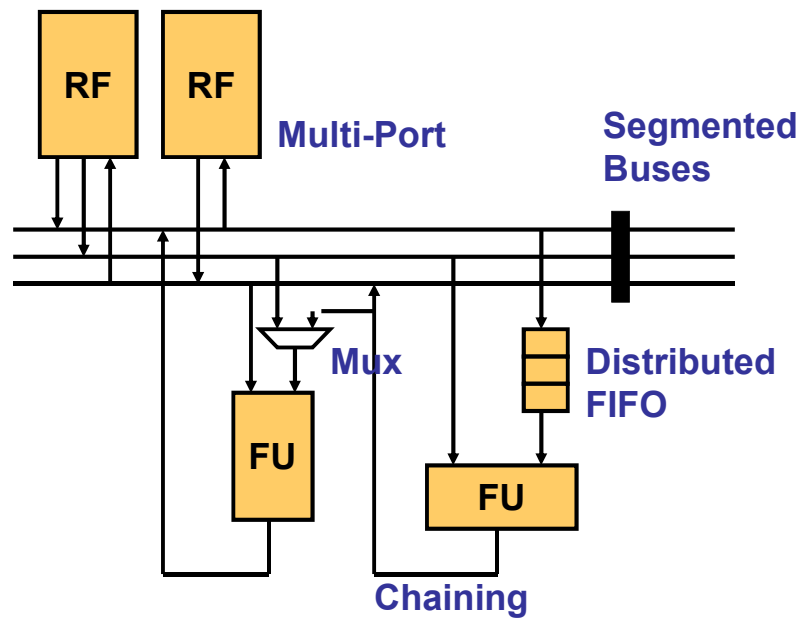


ECE382M.20: SoC Design, Lecture 7

© Jacob Abraham, UT Austin

25

## Architectural Pipelining

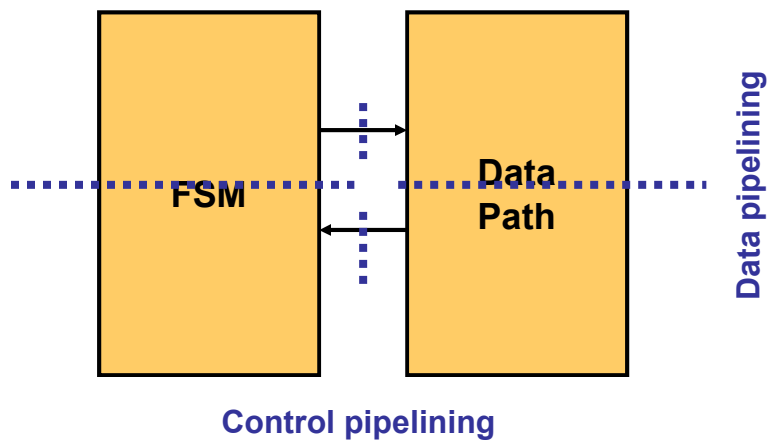

ECE382M.20: SoC Design, Lecture 7

© Jacob Abraham, UT Austin

26

## Lecture 7: Outline

### ✓ Introduction

- ✓ High-level synthesis (HLS)

### ✓ Essential issues

- ✓ Behavioral specification languages
- ✓ Target architectures
- ✓ Intermediate representation
- ✓ Scheduling/allocation/binding
- ✓ Control generation

### • High-level synthesis flow

- Synthesis example

ECE382M.20: SoC Design, Lecture 7

© 2023 A. Gerstlauer

27

## Example 1: C Code for Ones Counter

### • Programming language semantics

- Sequential execution,
- Coding style to minimize coding

### • HW design

- Parallel execution,
- Communication through signals

```

01: int OnesCounter(int Data) {
02:     int Ocount = 0;
03:     int Temp, Mask = 1;
04:     while (Data > 0) {
05:         Temp = Data & Mask;
06:         Ocount = Data + Temp;
07:         Data >>= 1;
08:     }
09:     return Ocount;
10: }

```

Function-based C code

```

01: while(1) {
02:     while (Start == 0);
03:     Done = 0;
04:     Data = Input;
05:     Ocount = 0;
06:     Mask = 1;
07:     while (Data>0) {
08:         Temp = Data & Mask;
09:         Ocount = Ocount + Temp;
10:         Data >>= 1;
11:     }
12:     Output = Ocount;
13:     Done = 1;
14: }

```

RTL-based C code

ECE382M.20: SoC Design, Lecture 7


© 2009 D. Gajski, S. Abdi, A. Gerstlauer, G. Schirner

28


## CDFG for Ones Counter
 
### • Control/Data Flow Graph (CDFG)

- Resembles programming language
  - Loops, ifs, basic blocks (BBs)
- Explicit dependencies
  - Control dependences between BBs
  - Data dependences inside BBs
- Missing dependencies between BBs



## CDFG and FSMD for Ones Counter

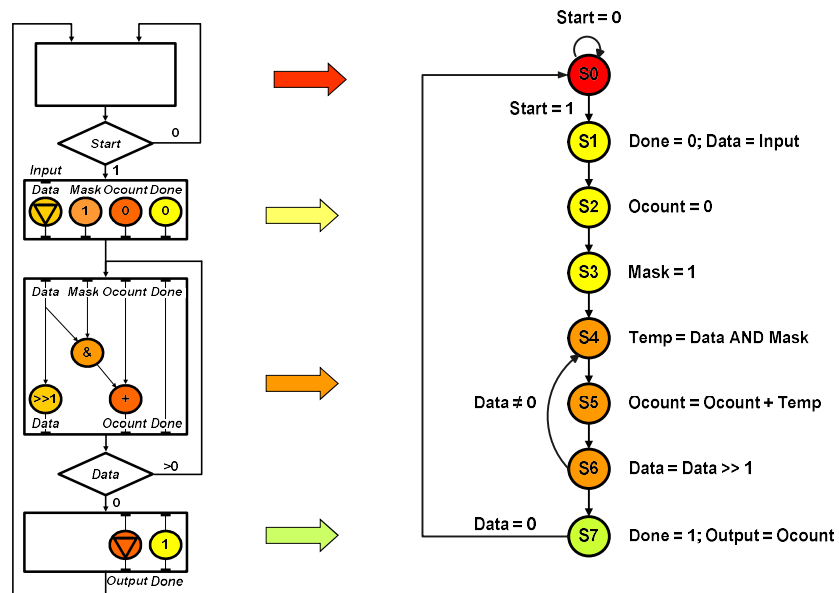


## FSMD for Ones Counter

- **FSMD more detailed than CDFG**


- States may represent clock cycles
- Conditionals and statements executed concurrently
- All statement in each state executed concurrently
- Control signal and variable assignments executed concurrently

- **FSMD includes scheduling**

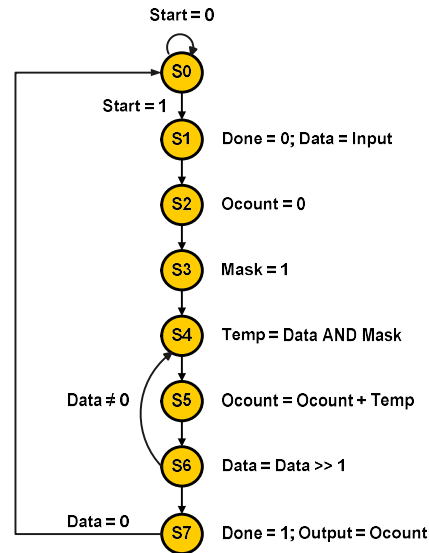- **FSMD doesn't specify binding or connectivity**



## RTL Specification for Ones Counter

 


- **RTL**

- FSM control
- Datapath netlist

Next state logic table

| Present State | Inputs: Start | Data = 0 | Next State | Output: Done |
|---------------|---------------|----------|------------|--------------|
| S0            | 0             | X        | S0         | X            |
| S0            | 1             | X        | S1         | X            |
| S1            | X             | X        | S2         | 0            |
| S2            | X             | X        | S3         | 0            |
| S3            | X             | X        | S4         | 0            |
| S4            | X             | X        | S5         | 0            |
| S5            | X             | X        | S6         | 0            |
| S6            | X             | 0        | S4         | 0            |
| S6            | X             | 1        | S7         | 0            |
| S7            | X             | X        | S0         | 1            |

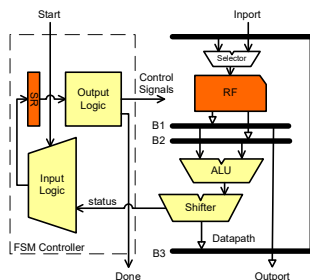

Output logic table

| State | RF Read Port A | RF Read Port B | ALU       | Shifter     | RF selector | RF Write | Output |
|-------|----------------|----------------|-----------|-------------|-------------|----------|--------|
| S0    | X              | X              | X         | X           | X           | X        | Z      |
| S1    | X              | X              | X         | X           | Inport      | RF[0]    | Z      |
| S2    | RF[2]          | RF[2]          | subtract  | pass        | B3          | RF[2]    | Z      |
| S3    | RF[2]          | X              | increment | pass        | B3          | RF[1]    | Z      |
| S4    | RF[0]          | RF[1]          | AND       | pass        | B3          | RF[3]    | Z      |
| S5    | RF[2]          | RF[3]          | add       | pass        | B3          | RF[2]    | Z      |
| S6    | RF[0]          | X              | pass      | shift right | B3          | RF[0]    | Z      |
| S7    | RF[2]          | X              | X         | X           | X           | disable  | enable |

RF[0] = Data, RF[1] = Mask, RF[2] = Ocount, RF[3] = Temp



## HDL description of Ones Counter

### • HDL description

- Same as RTL description
- Several levels of abstraction
  - Variable binding to storage
  - Operation binding to FUs
  - Transfer binding to connections

### • Netlist must be synthesized

- Logic synthesis

```



01: // ...
02: always@(posedge clk)
03: begin : output_logic
04:   case (state)
05:     // ...
06:     S4: begin
07:       B1 = RF[0];
08:       B2 = RF[1];
09:       B3 = alu(B1, B2, 1_and);
10:       RF[3] = B3;
11:       next_state = S5;
12:     end
13:     // ...
14:     S7: begin
15:       B1 = RF[2];
16:       Output <= B1;
17:       done <= 1;
18:       next_state = S0;
19:     end
20:   endcase
21: end
22: endmodule

```



## Example 2: Square-Root Algorithm (SRA)

### • $SQR = \max((0.875x + 0.5y), x)$


- $x = \max(|a|, |b|)$
- $y = \min(|a|, |b|)$

  

### C and CDFG for SRA Algorithm

  


### SRA Scheduling

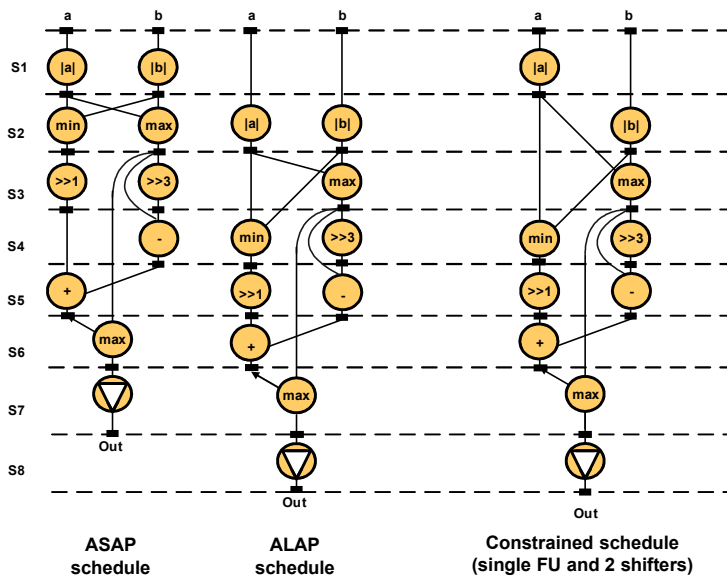

## Resource Sharing

- **Register sharing**
  - Variables with non-overlapping lifetime sharing the same register
- **Functional unit sharing**
  - Non-overlapping (sequential) operations sharing the same unit
- **Interconnect (wire & port) sharing**
  - Non-overlapping transfers sharing busses
  - Non-overlapping register accesses sharing register files

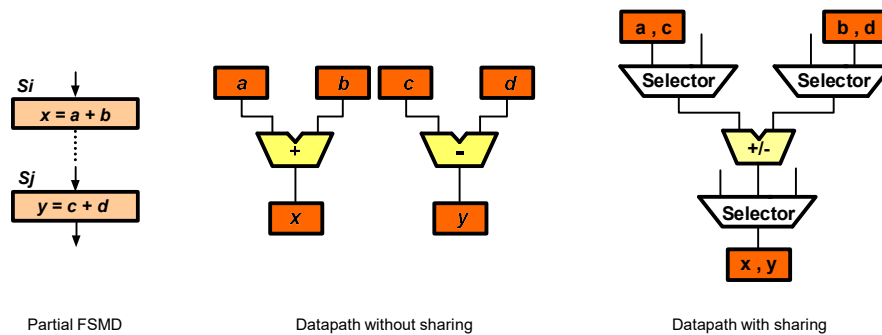

ECE382M.20: SoC Design, Lecture 7


© 2009 D. Gajski, S. Abdi, A. Gerstlauer, G. Schirner

37

## SRA Datapath with Shared Registers

- **Variables combined into registers**
- **One functional unit for each operation**

R1 = [a, t1, x, t7]  
 R2 = [b, t2, y, t3, t5, t6]  
 R3 = [t4]

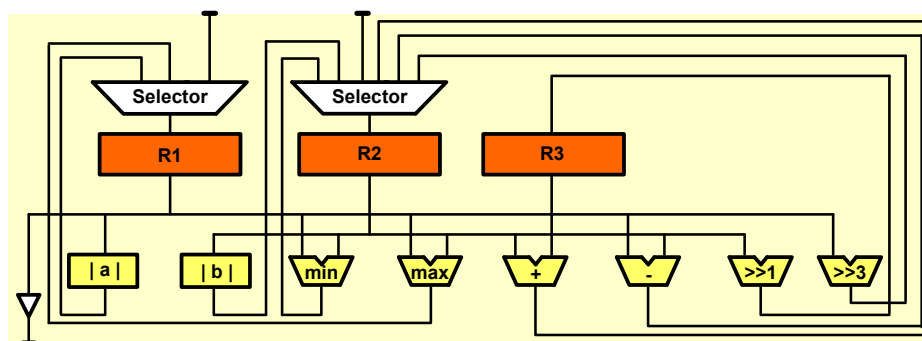


ECE382M.20: SoC Design, Lecture 7

© 2009 D. Gajski, S. Abdi, A. Gerstlauer, G. Schirner

38

## Datapath with Shared Registers and FUs

- Variables combined into registers
- Operations combined into functional units

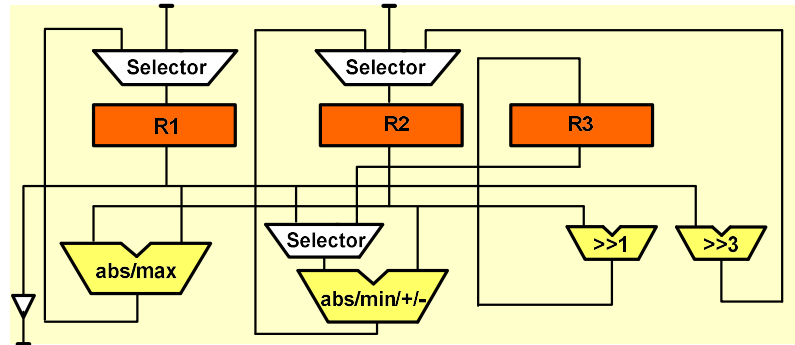

ECE382M.20: SoC Design, Lecture 7


© 2009 D. Gajski, S. Abdi, A. Gerstlauer, G. Schirner

39

## Datapath with Shared Registers, FUs, Buses

- Minimal SRA architecture

- 3 registers
- 4 (2) functional units
- 4 buses

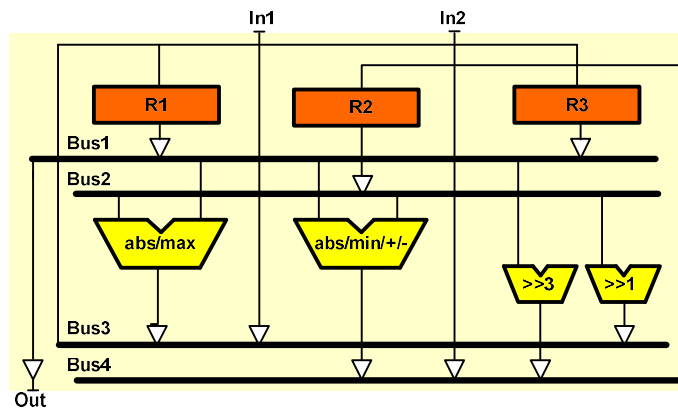


ECE382M.20: SoC Design, Lecture 7

© 2009 D. Gajski, S. Abdi, A. Gerstlauer, G. Schirner

40

## Datapath with Shared RF

- RF minimize connectivity cost by sharing ports

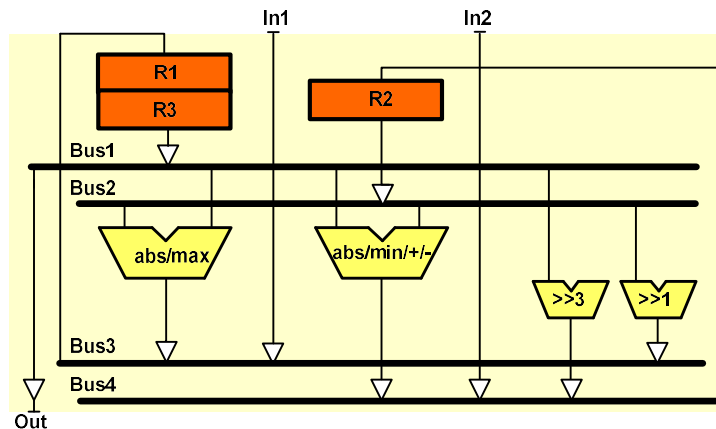


ECE382M.20: SoC Design, Lecture 7

© 2009 D. Gajski, S. Abdi, A. Gerstlauer, G. Schirner

41
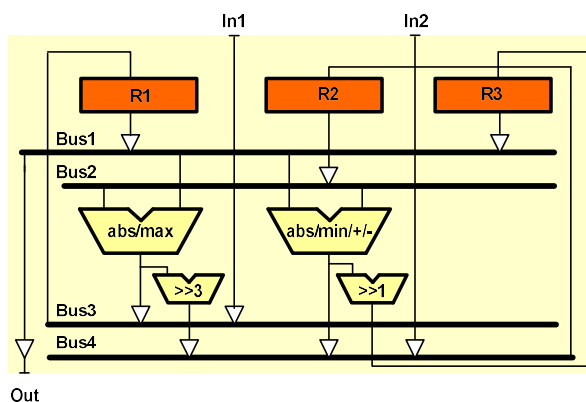
## Datapath with Chaining

- Chaining connects two or more FUs
- Allows execution of two or more operation in a single clock cycle
- Improves performance at no cost




Out

ECE382M.20: SoC Design, Lecture 7

© 2009 D. Gajski, S. Abdi, A. Gerstlauer, G. Schirner



42

 

## Datapath with Chaining and Multi-Cycling

### • Multi-cycling

- Operations that take more than one cycle
- Allows use of slower FUs
- Allows faster clock-cycle

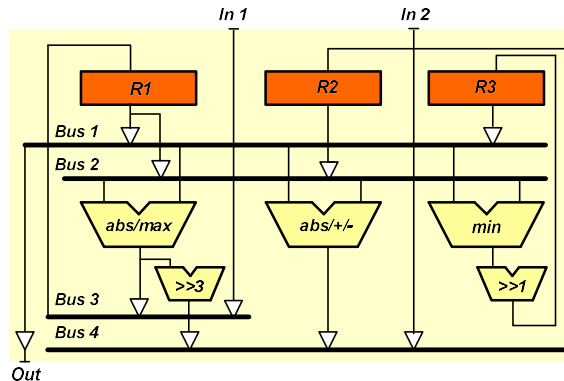 



ECE382M.20: SoC Design, Lecture 7

© 2009 D. Gajski, S. Abdi, A. Gerstlauer, G. Schirner

43

## Functional Unit Pipelining (1)

- Operation delay cut in "half"
- Shorter clock cycle
- Dependencies may delay (stall) some states
- Extra stall states reduce performance gain

 
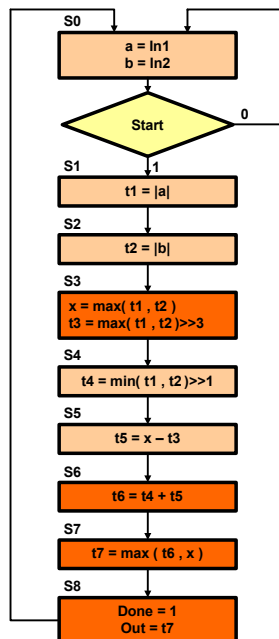


ECE382M.20: SoC Design, Lecture 7

© 2009 D. Gajski, S. Abdi, A. Gerstlauer, G. Schirner

44


## Functional Unit Pipelining (2)

 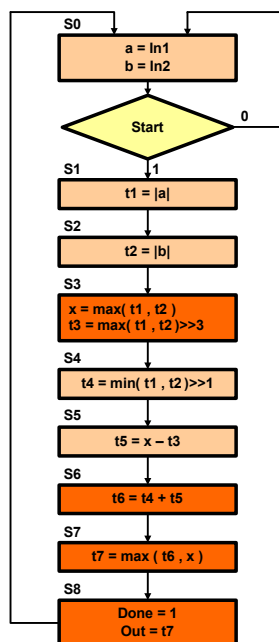


Timing diagram with 4 additional NOP states

|             | S0 | S1 | S2 | NO | S3  | S4  | S5  | NO  | S6 | NO | S7  | NO  | S8 |
|-------------|----|----|----|----|-----|-----|-----|-----|----|----|-----|-----|----|
| Read R1     |    | a  |    |    | t1  | t1  | X   |     |    |    | X   |     | t7 |
| Read R2     |    |    | b  |    | t2  | t2  | t3  |     | t5 |    | t6  |     |    |
| Read R3     |    |    |    |    |     |     |     |     | t4 |    |     |     |    |
| ALU stage 1 |    | a  | b  |    | max | min | -   |     | +  |    | max |     |    |
| ALU stage 2 |    |    | a  | b  |     | max | min | -   |    | +  |     | max |    |
| Shifters    |    |    |    |    |     |     | >>3 | >>1 |    |    |     |     |    |
| Write R1    | a  |    | t1 |    |     | X   |     |     |    |    |     | t7  |    |
| Write R2    |    | b  |    |    | t2  |     | t3  |     | t5 |    | t6  |     |    |
| Write R3    |    |    |    |    |     |     | t4  |     |    | t6 |     |     |    |
| Write Out   |    |    |    |    |     |     |     |     |    |    |     |     | t7 |



## Datapath Pipelining (1)

 

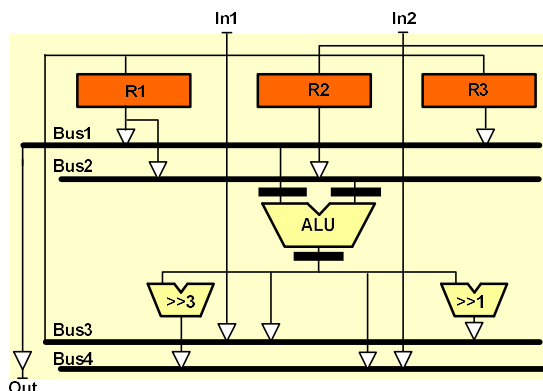- Register-to-register delay cut in "equal" parts
- Much shorter clock cycle
- Dependencies may delay some states
- Extra transfer states reduce performance gain



## Datapath Pipelining (2)

 
 


Timing diagram with additional NOP clock cycles

| Cycles    | 1 | 2 | 3 | 4 | 5  | 6  | 7   | 8   | 9   | 10  | 11 | 12 | 13 | 14 | 15 | 16 | 17  | 18 |
|-----------|---|---|---|---|----|----|-----|-----|-----|-----|----|----|----|----|----|----|-----|----|
| Read R1   |   | a |   |   |    | t1 | t1  |     | x   |     |    |    |    |    | x  |    |     | t7 |
| Read R2   |   |   | b |   |    | t2 | t2  |     | t3  |     |    | t5 |    |    | t6 |    |     |    |
| Read R3   |   |   |   |   |    |    |     |     |     |     |    | t4 |    |    |    |    |     |    |
| ALUIn(L)  |   | a |   |   |    | t1 | t1  |     | x   |     |    | t4 |    |    | x  |    |     |    |
| ALUIn(R)  |   |   | b |   |    | t2 | t2  |     | t3  |     |    | t5 |    |    | t6 |    |     |    |
| ALUOut    |   |   | a | b |    |    | max | min |     |     |    |    | +  |    |    |    | max |    |
| Shifters  |   |   |   |   |    |    |     |     | >>3 | >>1 |    |    |    |    |    |    |     |    |
| Write R1  | a |   |   |   | t1 |    |     |     | x   |     |    |    |    |    |    |    |     | t7 |
| Write R2  |   | b |   |   |    | t2 |     |     | t3  |     |    |    |    | t6 |    |    |     |    |
| Write R3  |   |   |   |   |    |    |     |     |     | t4  |    |    |    |    |    |    |     |    |
| Write Out |   |   |   |   |    |    |     |     |     |     |    |    |    |    |    |    |     |    |
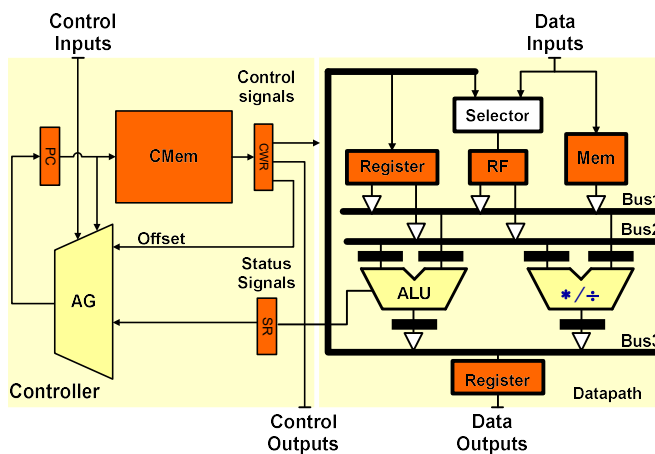 
## Datapath and Control Pipelining (1)


- Fetch delay cut into several parts
- Shorter clock cycle
- Conditionals may delay some states
- Extra NOP states reduce performance gain





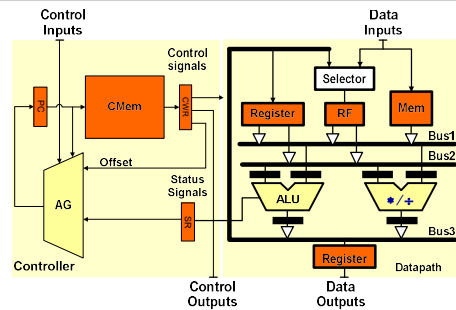
## Datapath and Control Pipelining (2)

- 3 NOP cycles for the branch
- 2 NOP cycles for data dependence



 Timing diagram with additional NOP clock cycles



| Operation      | Cycle | 0  | 1  | 2   | 3     | 4  | 5   | 6  | 7  | 8  | 9   | 10 |
|----------------|-------|----|----|-----|-------|----|-----|----|----|----|-----|----|
| Read PC        |       | 10 | 11 | 12  | 13    | 14 | 15  | 16 | 17 | 18 | 19  | 20 |
| Read CWR       |       |    | S1 | NO  | NO    | NO | S2  | NO | NO | S3 |     |    |
| Read RF(L)     |       |    | a  |     |       |    | c   |    |    | x  |     |    |
| Read RF(R)     |       |    | b  |     |       |    | d   |    |    | 1  |     |    |
| Write ALUIn(L) |       |    | a  |     |       |    | c   |    |    | x  |     |    |
| Write ALUIn(R) |       |    | b  |     |       |    | d   |    |    | 1  |     |    |
| Write ALUOut   |       |    |    |     |       |    | c+d |    |    |    | x-1 |    |
| Write RF       |       |    |    |     |       |    |     | x  |    |    |     | y  |
| Write SR       |       |    |    | a>b |       |    |     |    |    |    |     |    |
| Write PC       |       | 11 | 12 | 13  | 14/17 | 15 | 16  | 17 | 18 | 19 | 20  |    |

ECE382M.20: SoC Design, Lecture 7

© 2009 D. Gajski, S. Abdi, A. Gerstlauer, G. Schirner

49

## Lecture 7: Summary

- **High-level synthesis**
  - Scheduling
    - Resource- or time-constrained
  - Binding and resource sharing
    - Variable merging (storage sharing)
    - Operation merging (FU sharing)
    - Connection merging (bus sharing)
  - Architecture techniques
    - Chaining and multi-cycling
    - FU, datapath and control pipelining
- **Design automation (algorithms)**
  - Formalization / problem definition

ECE382M.20: SoC Design, Lecture 7

© 2023 A. Gerstlauer

50