

# EE445M/EE360L.6

## Embedded and Real-Time Systems/ Real-Time Operating Systems

### Lecture 6: Analog Input, Analog Filters, Analog-to-Digital Conversion


Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

1

## EE445M vs. CS372

THE DIFFERENCE:

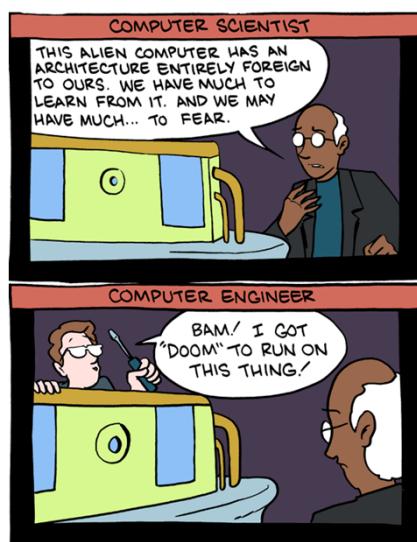
<http://www.smbc-comics.com/index.php?db=comics&id=2158#comic>

Lecture 6

2
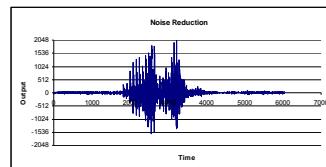
## Class Agenda

- Recap: RTOS Kernel
  - Multi-tasking, context switch, scheduling
  - Synchronization, communication, semaphores
- Outlook: Applications of RTOS
  - Lab 4: Digital scope & spectrum analyzer
    - Analog input and filters
    - Digital filter, FFT
    - Display amplitude vs. time/frequency on LCD




Reference book, Chapter 5

Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

3

## Instrumentation & Control

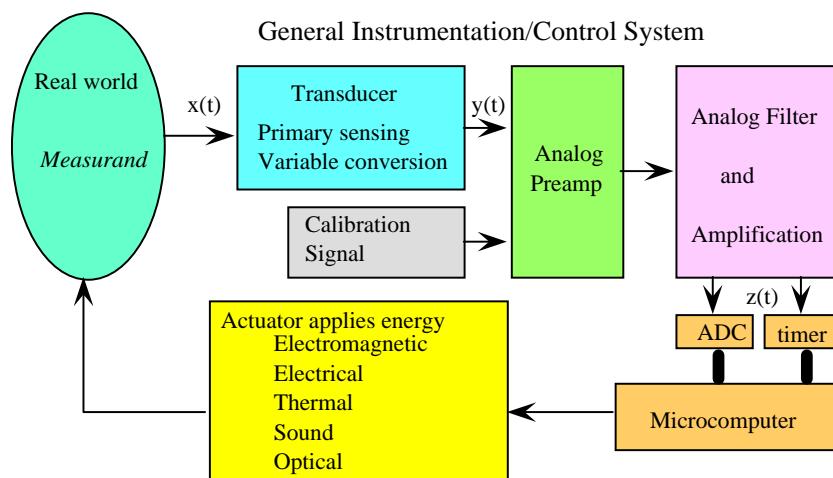

Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

4

## Data Acquisition System (DAS)

- Quantitative (thermometer in EE445L)
  - Range ( $r_x$ )
  - Resolution ( $\Delta x$ )
  - Precision ( $n_x$  in alternatives)
  - Frequencies of interest ( $f_{\min}$  to  $f_{\max}$ )
- Qualitative (sound recording in EE445M)
  - “sounds good”
  - “looks pretty”
  - “feels right”

Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

5

## Data Acquisition System (DAS)

- Other qualitative DAS
  - Detection of events (baby apnea monitor)
    - true positive (TP): stop breathing & monitor alarm
    - false positive (FP): breathing OK, but monitor alarm
    - false negative (FN): stop breathing & no alarm
  - Prevalence =  $(TP + FN) / (TP + TN + FP + FN)$
  - Sensitivity =  $TP / (TP + FN)$
  - Specificity =  $TN / (TN + FP)$
  - PPV =  $TP / (TP + FP)$
  - NPV =  $TN / (TN + FN)$

Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

6

## Analog Signal Processing

- Analog circuit design with single supply
  - MAX494CPD/TLC2274ACN rail to rail op amp
- Instrumentation amps (EE445L)
  - INA122
- Noise measurements and reduction
- Analog sensors
  - Electret microphones (sound)
  - IR distance sensor
- Analog filters



Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

7

## Convert to Single Supply

- $V_{cc} = 3.3V$ , start with design using  $+Vs$   $-Vs$
- Assume ADC range is 0 to  $V_{max}$  (0 to 3V)
- Add an analog reference,  $V_{ref} = \frac{1}{2} V_{max}$
- **Map**
  - $-Vs (-12)$  to **digital ground**
  - **Analog ground** to  **$V_{ref}$  reference**
  - $+Vs (+12)$  to  **$V_{cc}$  supply**


Reference EE345L book, Chapter 5

Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

8

## Inverting Amp

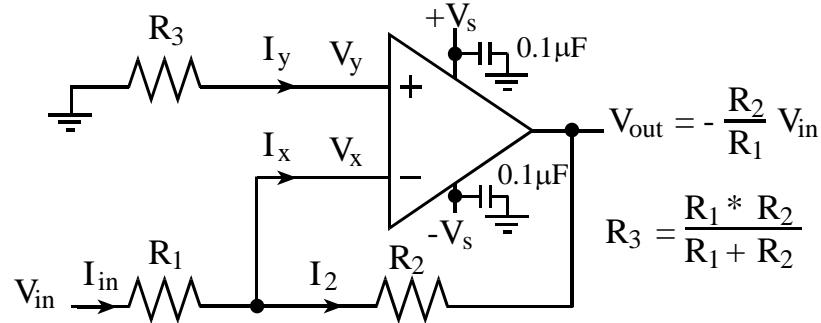

Use a rail-to-rail op-amp and map

- |               |    |                |
|---------------|----|----------------|
| -Vs           | to | digital ground |
| Analog ground | to | Vref reference |
| +Vs           | to | Vcc supply     |

Lecture 6


J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

9

## Original Design

**V<sub>out</sub> = 2V<sub>in</sub>**

**with some LPF**

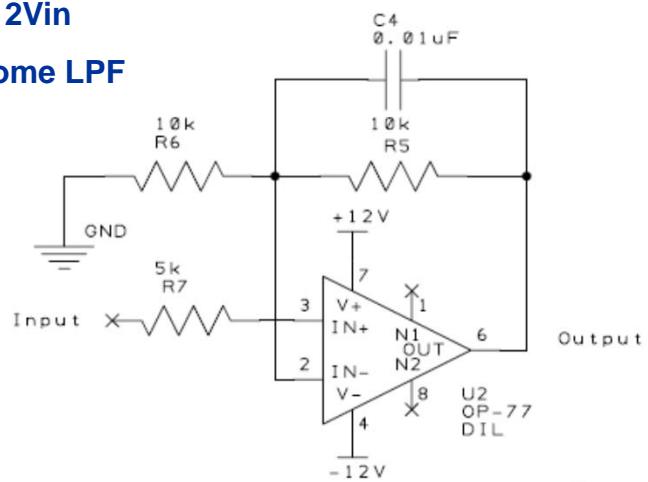

Lecture 6


J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

10

## New Design

$V_{out} = 2V_{in}-V_{ref}$   
 $(V_{ref} = 1.23V)$

with some LPF

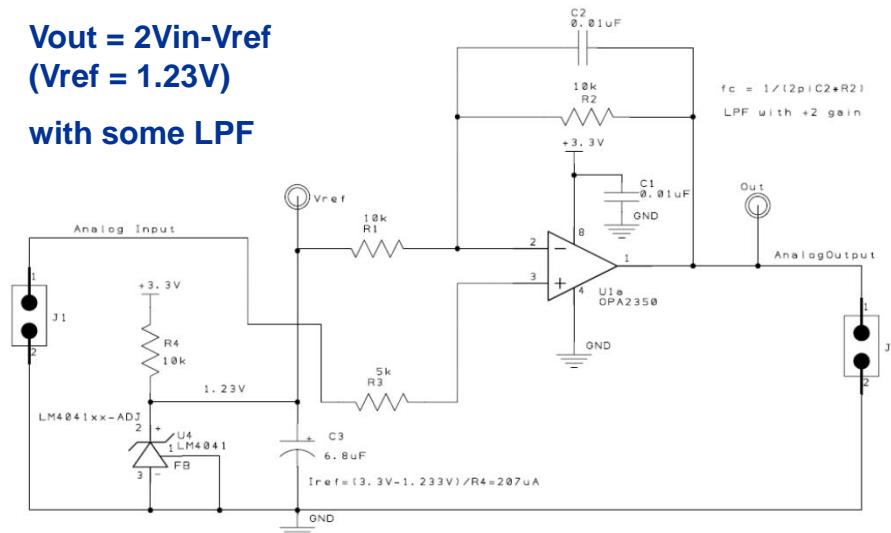

Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

11

## Instrumentation Amp


- Necessary conditions (must be true)
  - Differential input (as in any op-amp)
- Motivation (at least one must be true)
  - Large gain
  - Large input impedance
  - Large common mode rejection ratio (CMRR)
  - Low noise
  - Small package

Lecture 6


J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

12


## Burr-Brown INA122

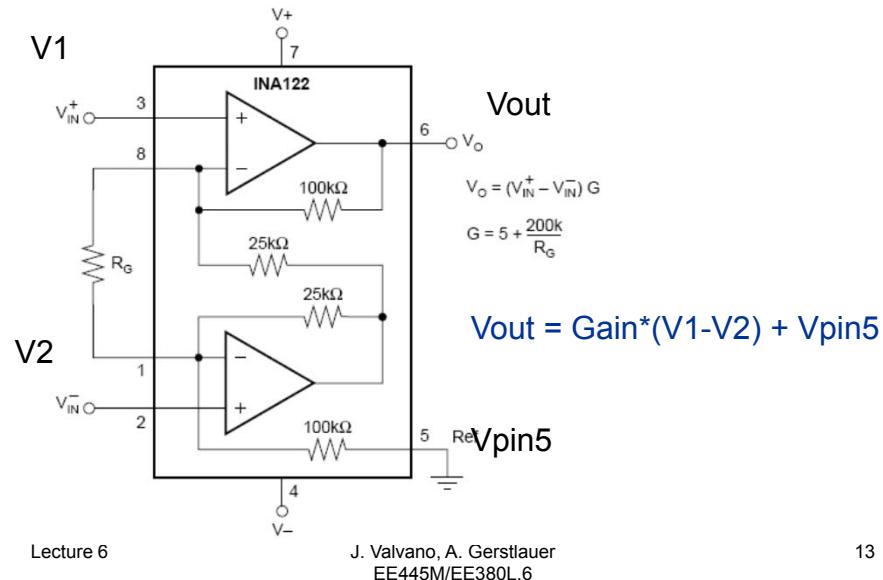

## Magnetic Field Noise

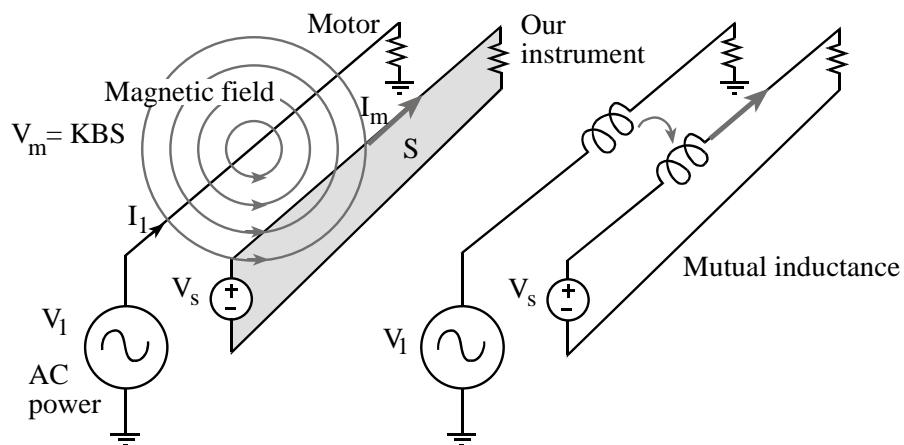

## Electric Field Noise

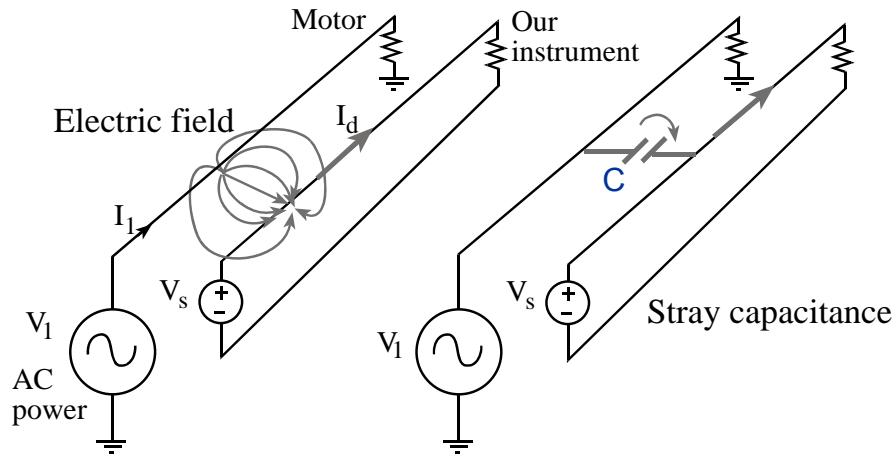

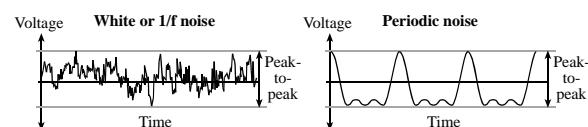
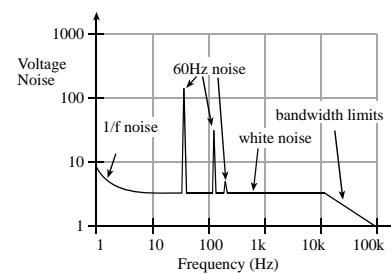
How do you reduce  $C$ ?


Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

15
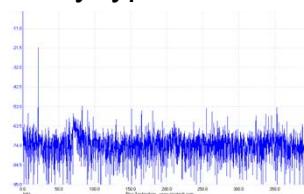
## Noise Measurement


- Digital volt meter (AC mode)
  - Most accurate quantitative noise measure
- Oscilloscope (line trigger)
  - Shape
 
- Spectrum Analyzer
  - Classify type
 



## Noise Reduction (1)

### 1. Reducing noise from the source

- Shielding
  - Enclose noisy sources in a grounded metal box
- Filter noisy signals
- Limit the rise/fall times of noisy signals.
- Limiting the  $di/dt$  in the coil.

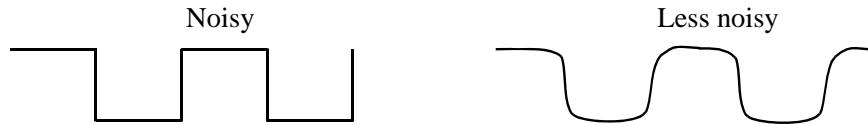

Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

17

## Noise Reduction (2)

### 2. Limiting the coupling between the noise source and instrument


- Maximize the distance from source to instrument
- Cables with noisy signals should be twisted together
- Cables should also be shielded.
- For high frequency signals, use coaxial
- Reduce the length of a cable
- Place the delicate electronics in a grounded case
- Optical or transformer isolation circuits

Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

18

## Limiting the Coupling

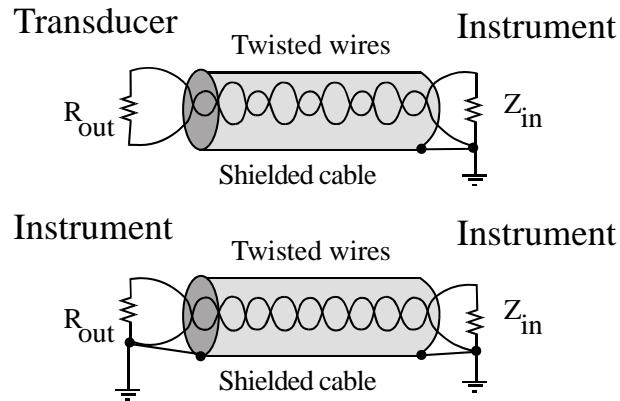


Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

19

## Noise Reduction (3)

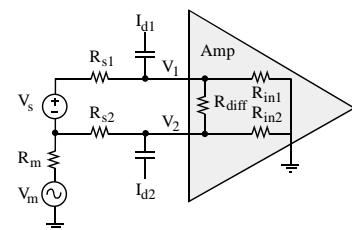3. Reduce the noise at the receiver
  - Bandwidth should be as small as possible.
  - Add frequency-reject digital filters
  - Use power supply decoupling capacitors on each
  - Twisted wires then  $I_{d1}$  should equal  $I_{d2}$ 
    - $V_1 - V_2 = R_{s1} I_{d1} - R_{s2} I_{d2}$



Henry Ott, Noise Reduction Techniques in Electronic Systems, Wiley, 1988.  
 Ralph Morrison, Grounding and Shielding Techniques, Wiley, 1998.

Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

20

## Electret Condenser Microphone




Lecture 6


J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

21

## Cross-Section of Typical ECM

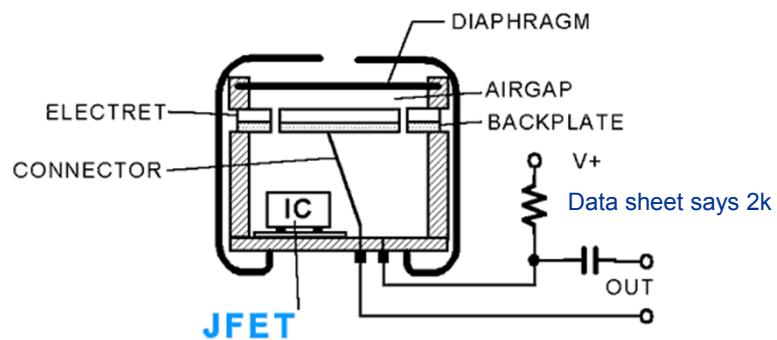

- JFET Buffer
- Phantom Biasing

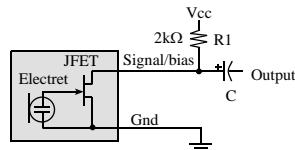


Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

22

## ECM Interface

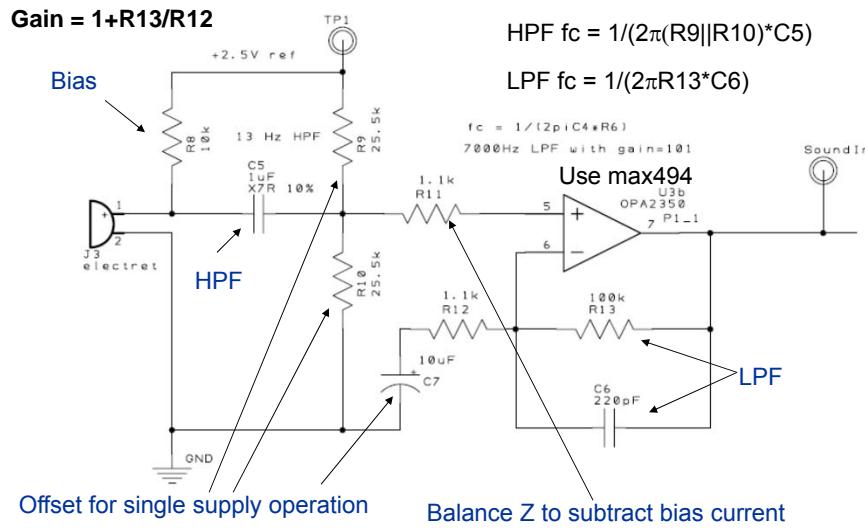

Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

23

## Sharp GP2Y0A21YK

- Infrared distance sensor
  - You will need 5V to power IR sensor
  - Needs analog LPF
    - Reduces noise
  - Analog input protection
  - Needs digital median filter
  - Needs 10 mF or larger +5V to Gnd cap for each sensor




Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

24

## IR Sensor Calibration

d (cm)	1/d	ADC
10	0.100	703
15	0.067	484
20	0.050	380
30	0.033	260

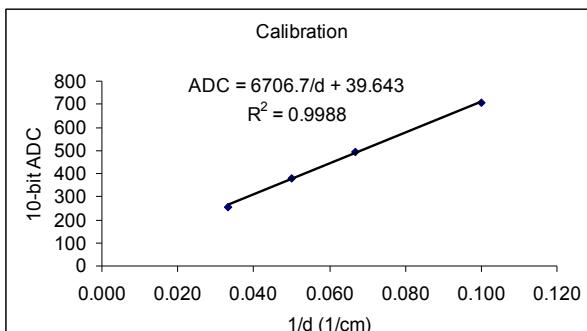

Lecture 6


## Sharp GP2Y0A21YK

- Accuracy => Calibration
- Resolution => Noise

$$\text{ADC} = 6707/d + 40$$

$$d = 6707/(\text{ADC}-40)$$

$$d \text{ (0.01cm)} = 6706700/(\text{ADC}-40)$$

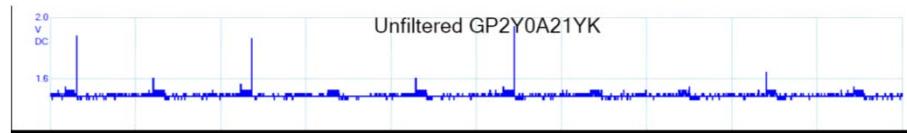


Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

26

# Sampling

- Time & value quantizing
  - Precision  $n_z = 2^n$
- Nyquist theory
  - If sampled at  $f_s$ , digital samples only contain frequency components from 0 to  $\frac{1}{2}f_s$
  - If analog signal contains frequency components larger than  $\frac{1}{2}f_s$ , **aliasing** error
- System design
  - Choice of sampling rate:  $f_s > 2 f_{\max}$
  - Low pass analog filter to remove frequency components above  $0.5f_s$ 
    - A digital filter can not be used to remove aliasing

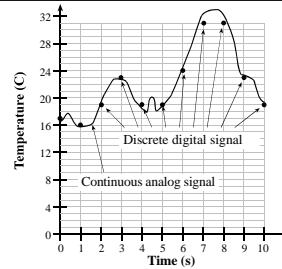


Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

27

# Filter Types

- Analog
  - Low pass filter (LPF)
  - High pass filter (HPF)
  - Band pass filter (BPF)
- Digital
  - Extremely flexible
  - But only available after sampling

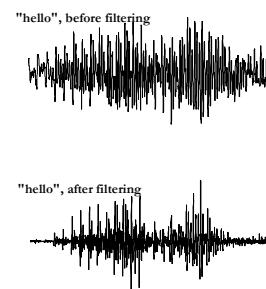



Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

28

## Analog Filters


- Prevent aliasing
  - No signal >  $0.5f_s$
- Band-pass filter

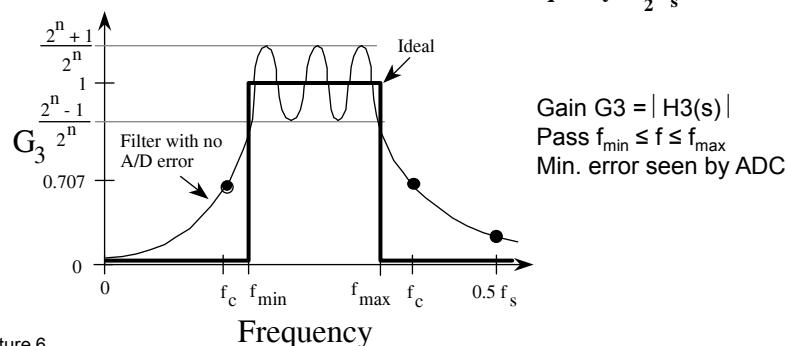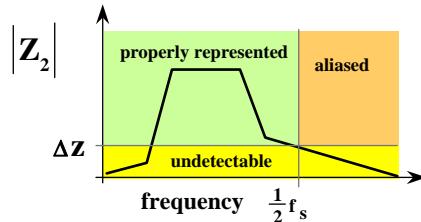

Lecture 6

29

## Butterworth Filters

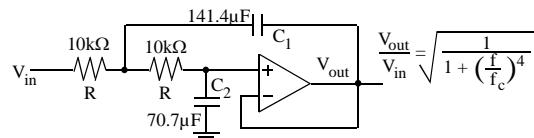

- 2-pole Butterworth filter
  1. Select the cutoff frequency,  $f_c$
  2. Divide the two capacitors by  $2\pi f_c$ 
    - $C_{1A} = 141.4\mu F / 2\pi f_c$
    - $C_{2A} = 70.7\mu F / 2\pi f_c$
  3. Locate two standard value capacitors (with 2/1 ratio) in the same order of magnitude as the desired values
    - $C_{1B} = C_{1A}/x$
    - $C_{2B} = C_{2A}/x$
  4. Adjust the resistors to maintain the cutoff frequency
    - $R = 10k\Omega \cdot x$

lpf.xls

TI FilterPro

Lecture 6

J. Valvano, A. Gerstlauer  
EE445M/EE380L.6

30