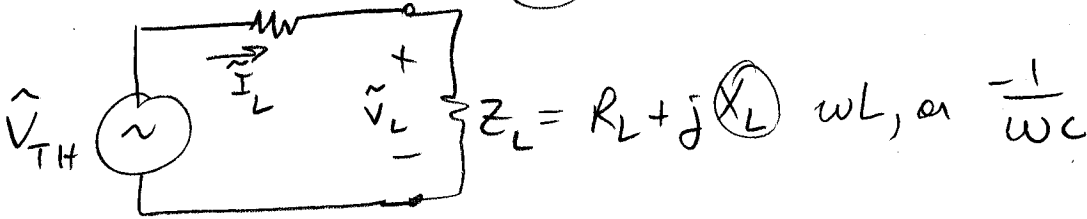


MAX POWER TRANSFER

ωL , or $\frac{1}{\omega C}$

$$Z_{TH} = R_{TH} + jX_{TH}$$



$$S_L = \tilde{V}_L \tilde{I}_L^* = (P_L) + jQ_L, \quad \tilde{I}_L = \frac{\tilde{V}_{TH}}{(R_{TH} + R_L) + (jX_{TH} + jX_L)}$$

WANT to MAX

$$P_L = |\tilde{I}_L|^2 R_L = \frac{|\tilde{V}_{TH}|^2}{(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2} R_L$$

Note: \tilde{I}_L bigger when $X_L = -X_{TH}$

$$= |\tilde{V}_{TH}|^2 R_L \left[(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2 \right]^{-1}$$

$$\frac{\partial P_L}{\partial R_L} = \frac{|\tilde{V}_{TH}|^2}{(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2} - \frac{|\tilde{V}_{TH}|^2 R_L \cdot 2(R_{TH} + R_L)}{\left[(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2 \right]^2} = 0$$

$$= \frac{|\tilde{V}_{TH}|^2}{(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2} \left[1 - \frac{2R_L(R_{TH} + R_L)}{(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2} \right] = 0$$

MUST = 0 for MAX power xfer to R_L

so
$$\frac{2R_L(R_{TH} + R_L)}{(R_{TH} + R_L)^2 + (X_{TH} + X_L)^2} = 1$$

so (A) then (B)
$$2R_L R_{TH} + 2R_L^2 = R_{TH}^2 + 2R_L R_{TH} + R_L^2 + (X_{TH} + X_L)^2$$

(B) Note, if $X_L = -X_{TH}$, $R_L = R_{TH}$, so $Z_L = Z_{TH}^*$ yields MAX power to R_L

(A)
$$R_L^2 - R_{TH}^2 = (X_{TH} + X_L)^2 \Rightarrow R_L^2 = R_{TH}^2 + (X_{TH} + X_L)^2$$

FOR MAX POWER TO R_L