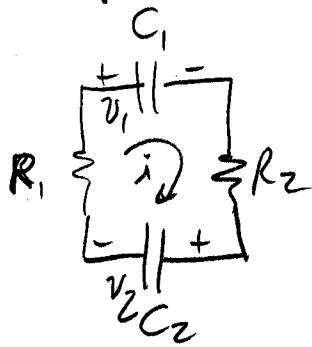


Multiple C's, L's



Series C's

KVL

$$R_1 i + \frac{1}{C_1} \int i dt + R_2 i + \frac{1}{C_2} \int i dt = 0$$


$$(R_1 + R_2) i + \left(\frac{1}{C_1} + \frac{1}{C_2}\right) \int i dt = 0$$

$$(R_1 + R_2) \frac{di}{dt} + \left(\frac{1}{C_1} + \frac{1}{C_2}\right) i = 0$$

$$\frac{di}{dt} = \frac{1}{(R_1 + R_2)} \cdot \left(\frac{1}{C_1} + \frac{1}{C_2}\right) i$$

$$\frac{di}{dt} = \frac{1}{R_{eq} C_{eq}} i \rightarrow R_{eq} = R_1 + R_2$$
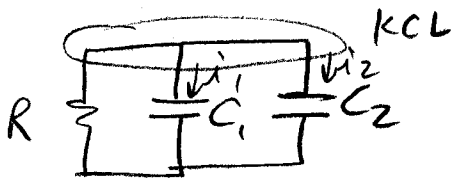
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$



Parallel C's


KCL

$$\frac{v}{R} + C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} = 0$$

$$(C_1 + C_2) \frac{dv}{dt} = -\frac{v}{R}$$

$$\frac{dv}{dt} = \frac{-1}{R(C_1 + C_2)} v, \quad R_{eq} = R$$

$$C_{eq} = C_1 + C_2$$

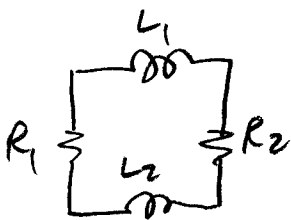

Series L's

KVL

$$R_1 i + L_1 \frac{di}{dt} + R_2 i + L_2 \frac{di}{dt} = 0$$

$$(L_1 + L_2) \frac{di}{dt} = -(R_1 + R_2) i$$

$$\frac{di}{dt} = \frac{-(R_1 + R_2)}{(L_1 + L_2)} i, \quad R_{eq} = R_1 + R_2$$

$$L_{eq} = L_1 + L_2$$



Parallel L's

KCL

$$\frac{v}{R} + \frac{1}{L_1} \int v dt + \frac{1}{L_2} \int v dt = 0$$

$$\frac{1}{R} \frac{dv}{dt} + \frac{v}{L_1} + \frac{v}{L_2} = 0, \quad \frac{dv}{dt} = \frac{-R \left(\frac{1}{L_1} + \frac{1}{L_2}\right)}{1} v$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$