

# Power Electronics as Efficient Interface in Dispersed Power Generation Systems

Frede Blaabjerg, *Fellow, IEEE*, Zhe Chen, *Senior Member, IEEE*, and Soeren Baekhoej Kjaer, *Member, IEEE*


Nice paper but doesn't include multiple-input converters (MILCs)

More about MILCs later

What are MILCs?

To answer the question let's see what is the purpose of MILCs

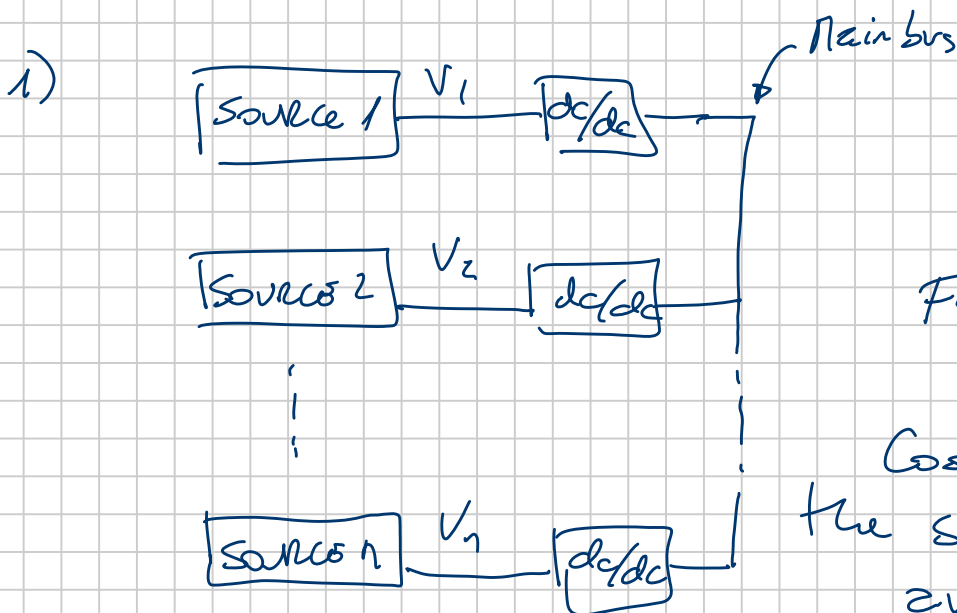There are several ways to connect multiple dc sources to a common bus:




Fully distributed system

Cost is higher but the system has higher availability


We assume that all voltages are different

$$\text{Availability (A)} = \frac{\text{Mean up time}}{\text{Mean time between failures}}$$

$$A = \frac{MTUP}{MTBF}$$

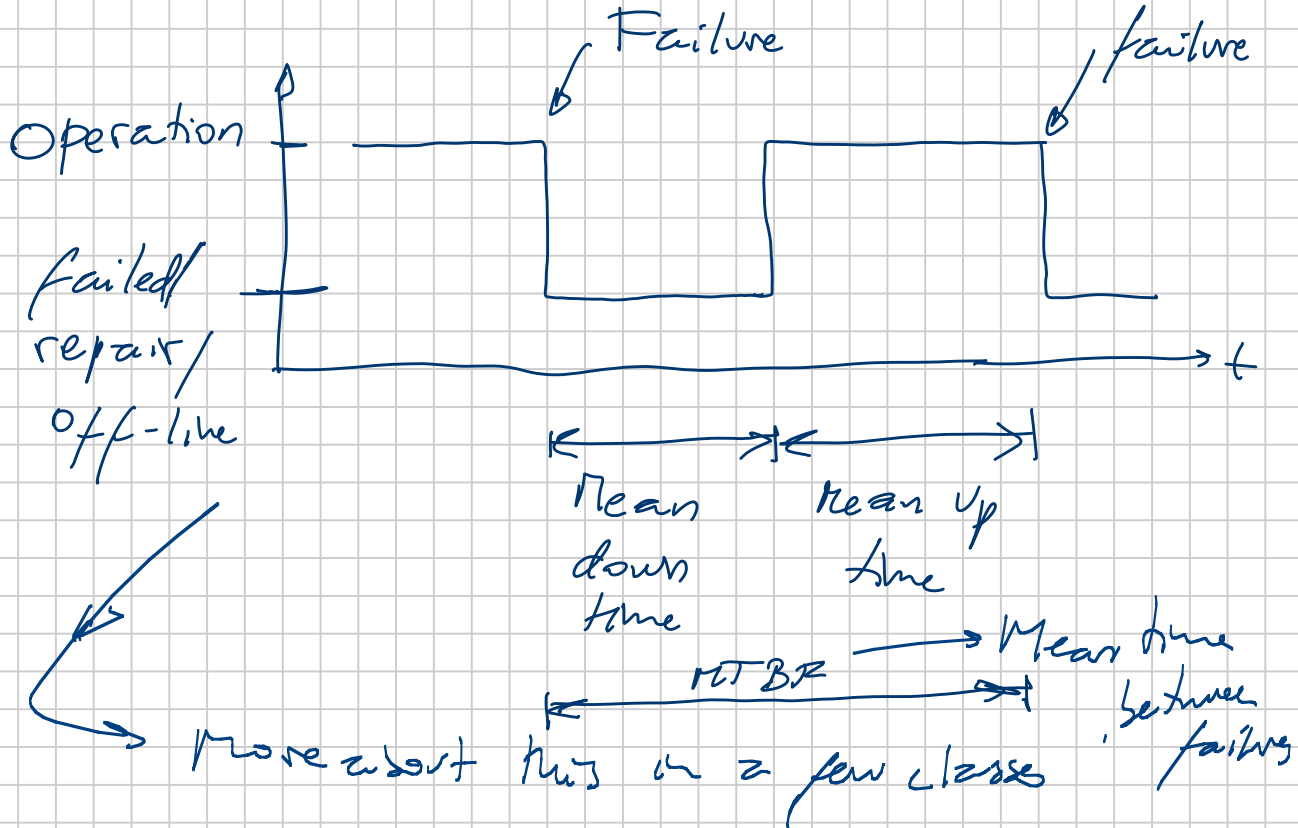


## 2) Centralized system

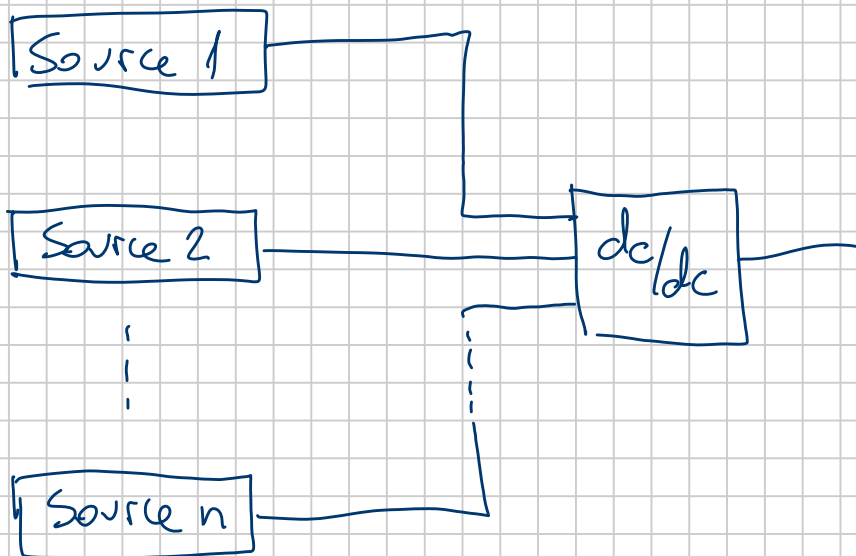


Lower cost  
but lower  
availability

- A MIZ is a topology derived from the above to avoid reducing the availability.

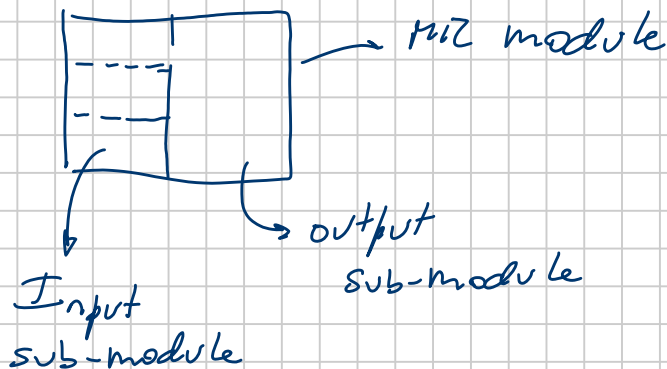
- The difference is to have a modular design



So we can build a modular system:

 

or

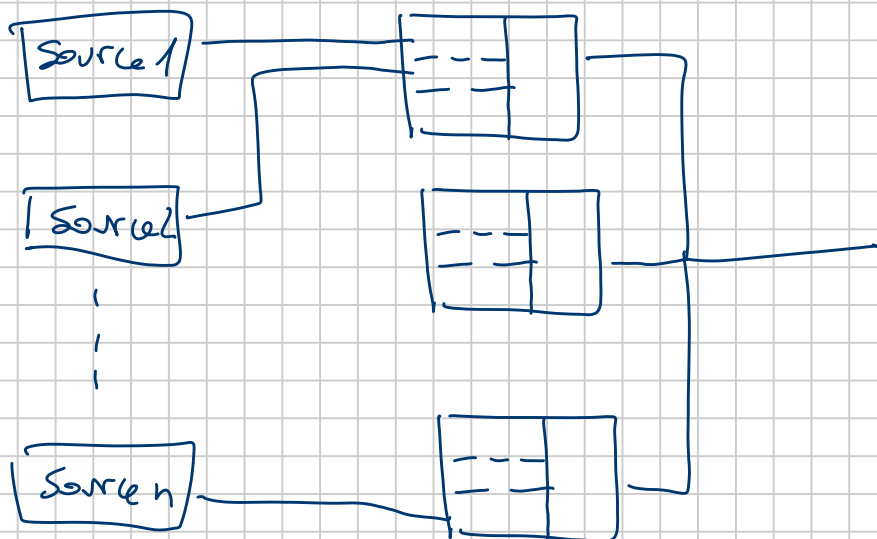

Advantages of modular design to avoid reducing the availability → when a module fails I can change it quickly (CRT)

→ I can implement  $n+1$  redundant configurations or other techniques to avoid single point of failures

→ I have greater flexibility by allowing integration of different sources.

Multis are made from the single-input versions.

There are 2 approaches:


- 1) Simultaneous input-to-output power transfer
- 2) No constraints on input-to-output power transfer

1) Simultaneous input-to-output power transfer


They allow for simultaneous power drawn from each source and injected into the output.

These configurations require more components than the unrestricted cases and often leads to trivial parallel connection of converters sharing only the output capacitor. e.g. MIL Boost converter:

Single input Boost:

 

Multiple input boost:

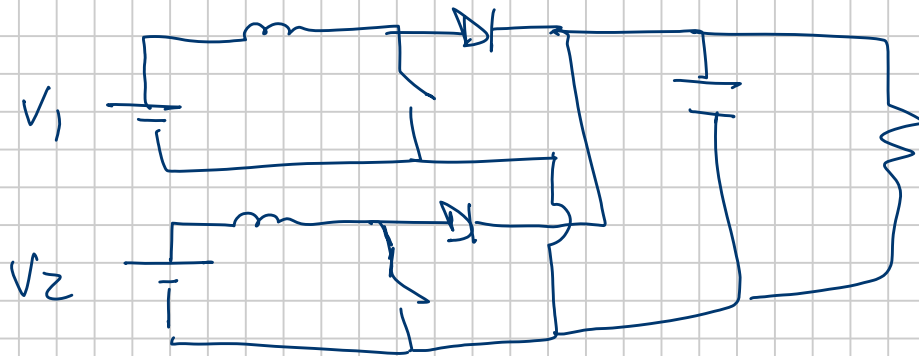

The switch has no restrictions here.

The problem with this approach is that cost savings are not significant.

Some more information can be found in

## A Systematic Approach to Synthesizing Multi-Input DC/DC Converters

Yuan-Chuan Liu and Yaow-Ming Chen



Look in here for additional references

Paper presented in PESC 2007

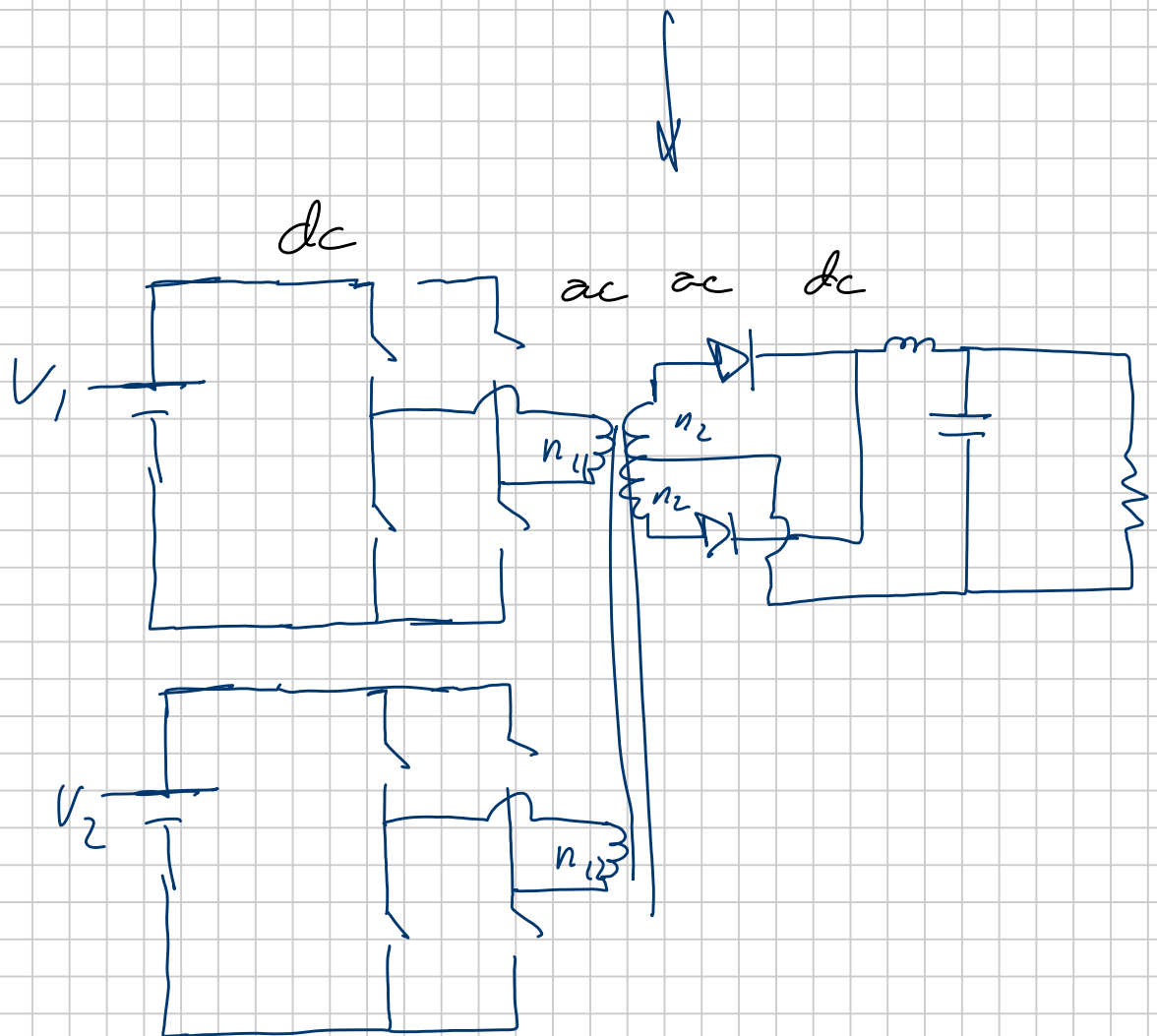 2) No constraints on input-to-output power transfer

With this approach it is possible to find both cases of non-simultaneous power input and cases allowing simultaneous power drawn from sources.

In these cases we can also find some trivial cases in which the inputs are all connected together at the ac intermediate stage of forward converters. e.g. full bridge converter.




These cases are not going to be discussed further because they are trivial.

Let's see how we synthesize pacs with this approach.

• Assumptions, restrictions and conditions:

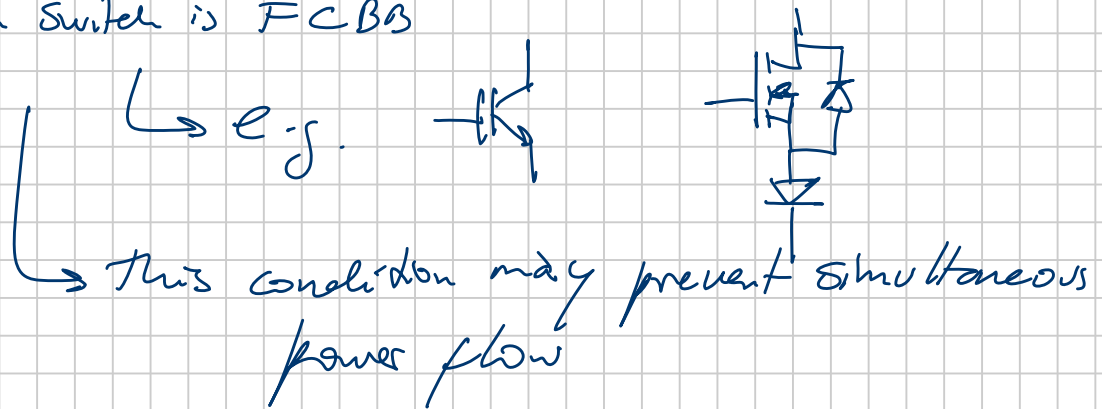- 1) Power flow is from source to load
- 2) Total number of components minimization
- 3) Main switch is FCBS



- 4) Each of the input voltages are different
- 5) it should be possible to control each input.

The previous 5 points lead to the following rules

rule #1 Each input cell must contain at least one FCBS switch

↳ this rule is derived from condition #5 above.


rule #2 The connectors of input cell should not lead to redundant switches. I.e., both switch terminals cannot be terminals for the input cell

rule #3 For topologies with center capacitor (e.g. buck and SEPIC) the voltage of this capacitor in the single-input configuration must not depend on the input voltage


rule #4

Both ends of the input source should not be terminals of the input cell (IC)

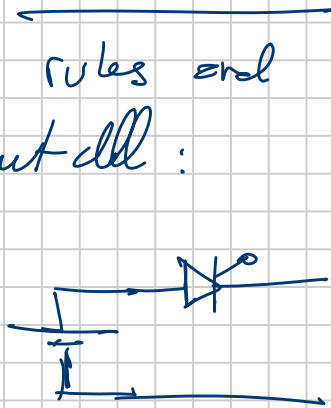
With the above rules and 5 points there is only one feasible input cell:



 This is the IC for the  $\pi$ i Buck and  $\pi$ i Buck Boost



 Assume always that  $V_1 > V_2$  and  $D_1 < D_2$ , then



When both  $Q_1$  &  $Q_2$  are closed only  $Q_1$  conducts current.



Hence, the switching period is divided in 3 phases:

1)  $D_1 T \rightarrow$  power is taken from source #1


2)  $D_{2eff} T \rightarrow$  power is taken from source #2

3)  $(1-D_2) T \rightarrow$  Diode conducts

So the power provided by source #2 is limited by the power provided by source #1

$$D_{2eff} = D_2 - D_1$$


$\pi$ i Buck-Boost:

 








$$V_{out} = - \frac{D_1 E_1 + D_{2eff} E_2}{(1-D_2)}$$

The problem with this FC is that, it is not suitable for sources, such as fuel cells, that require low current ripple.

One solution is adding filters:





 


Unfeasible ICS:

       

Boost, SEPIC and Cuk input cells

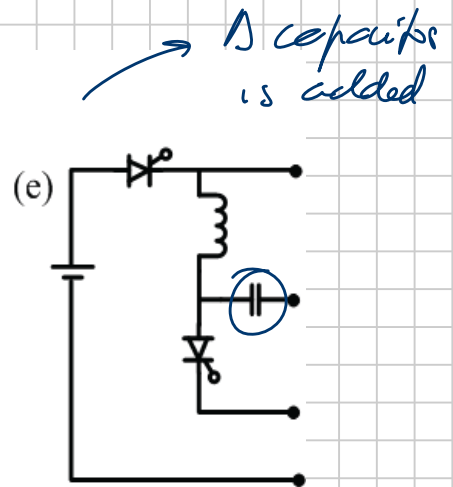    If the condition #2 is relaxed (total number of components minimization) then some new ICS can be realized:




risePIC & Cuk

Advantages

power is continuously drawn from all sources simultaneously

↳ current source input

 Disadvantages → Duty cycle in all but one switch depend on the duty cycle of the switch with the highest voltage



$$V_L = 0 = -D_1 \bar{E}_1 - D_{2eff} \bar{E}_2 + (1-D_2) V_{out}$$

$$V_{out} = \frac{D_1 \bar{E}_1 + D_{2eff} \bar{E}_2}{(1-D_2)}$$

$$D_D = 1 - D_2$$

Dynamic equations

$$L_1 \dot{x}_1 = E_1 - g_{2eff} (x_{C1} - x_{C2}) - g_D (x_C + x_{C1})$$

$$L_2 \dot{x}_2 = E_2 - g_{1eff} (x_{C2} - x_{C1}) - g_D (x_C + x_{C2})$$


$$L \dot{x}_L = g_1 E_1 + g_{2eff} \bar{E}_2 - g_D x_C$$

$$C_1 \dot{x}_{C1} = (1-g_1) x_{L1} - g_1 (x_C + x_{C2})$$



$$C_2 \dot{x}_{C2} = (1-g_{2eff}) x_{L2} - g_{2eff} (x_C + x_{C1})$$



$$C \dot{x}_C = g_D (x_L + x_{C1} + x_{C2}) - \frac{x_C}{R}$$

Cv h

 


Other topologies

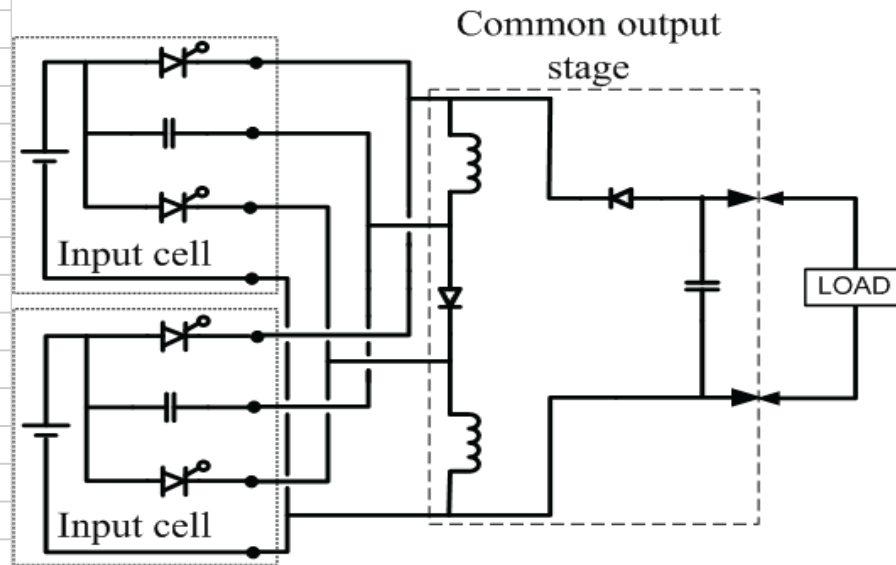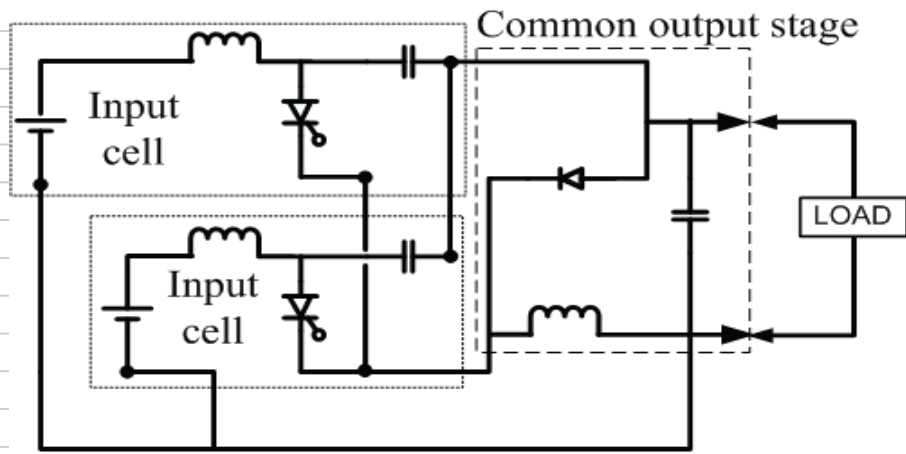

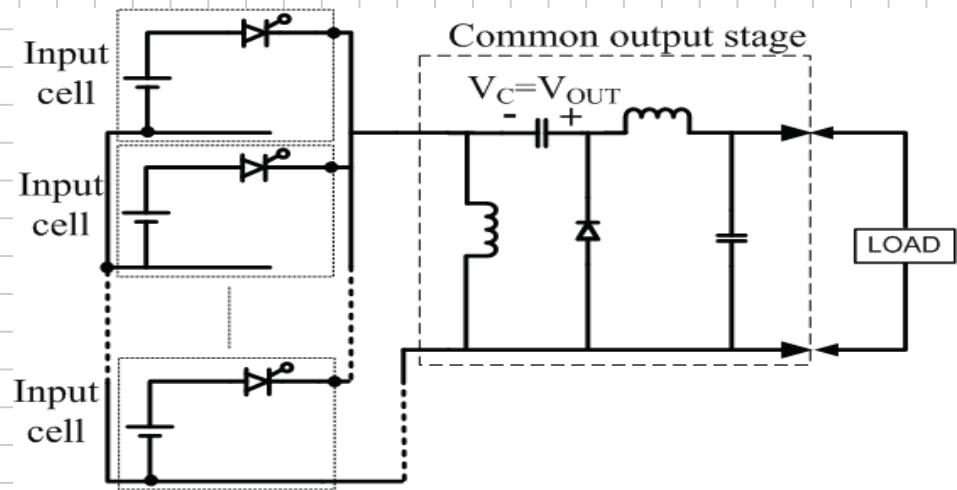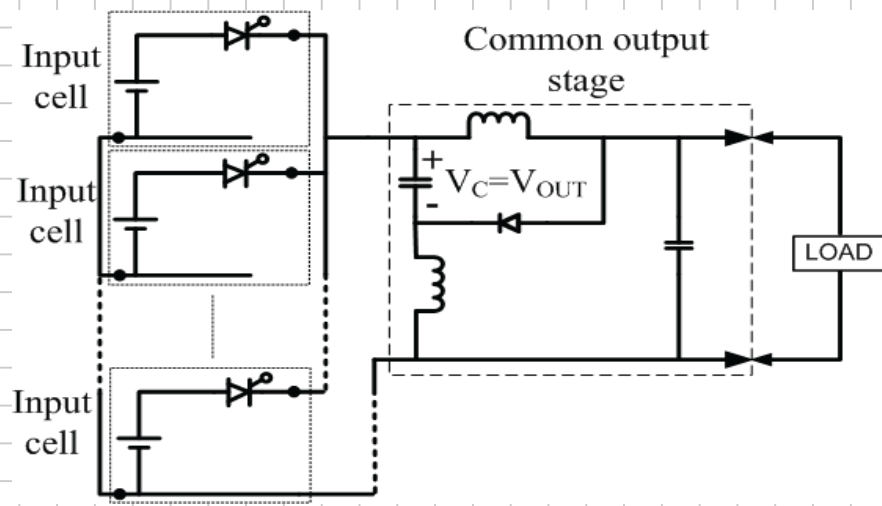

One problem with time shared rect is that there is so much time ( $T_s$ ) to split among input switches and the output diode which may lead to very small duty cycles for the output diode.


One solution is to add isolation:

 


$$\text{Now } V_{OUT} = \frac{N_2}{N_1} \left( \frac{D_1 E_1 + D_{\text{eff}} E_2}{1 - D_2} \right)$$

For  $E_1 > E_2$

 So same output voltages can be achieved with smaller duty cycles if  $N_2 > N_1$



Non isolated

 

Isolated

$D_{\text{eff}} > D_{\text{eff isolated}}$

But senses voltages

