EE394J-11 Homework Assignment #1

Due date: 9/30/2013

Consider a buck-boost converter with $L = 500 \mu$ H, C = 1 mF, $R = 10 \Omega$, E = 30 V. For all questions write some few conclusions or comments about the results.

- 1) Write the dynamic equations for the switched model, the fast average model, and the linear model. For the switched model and the fast average model simulate the converter for a duty cycle of 0.4 and switching frequencies of 100 Hz and 20 kHz. Plot the state variables in time domain and on a phase portrait.
- 2) Find the equilibrium points for the switched model and sketch the trajectories (i.e. on a phase portrait) for the two circuit configurations (when the switch is on and when it is off).
- 3) For the average model, find the relationship between input and output voltage in steady state. On a phase portrait, plot the curve representing the various equilibrium points for different duty ratios. Please do this plot on the same plot that you used to answer question #2.

Now consider the SEPIC converter in the next figure. Circuit parameters are E = 48 V, all inductors 400 µH, output capacitance equal to 1000 µF, $R = 10 \Omega$ and center capacitance equal to 50 µF.

- 4) Write the dynamic equations for the switched model, the fast average model, and the linear model. For the switched model and the fast average model simulate the converter for a duty cycle of 0.4 and switching frequencies of 100 Hz and 25 kHz. Plot these state variables in a time domain figure.
- 5) Find the equilibrium points for the switched model considering the two circuit configurations (when the switch is on and when it is off).
- 6) For the average model, find the relationship between input and output voltage (in steady state).
- 7) Finally, replace the output inductor for a pair of coupled inductors and write down the same equations than in question #4 but now for the new circuit configuration. Also repeat question #6.

