

# Power Conversion Issues with energy harvesting

Note Title

11/23/2011

Some typical applications of less conventional power generation through energy harvesting include

- wave energy
- ↳ human (or some other kind) movement

↳ e.g. piezoelectric generator using the energy exchange in each step.

Common problems → Need for small volume (high density)




vs:



power source → low frequency (pulses in the order of Hz)


↳ low voltage ( $\approx 1V$ )

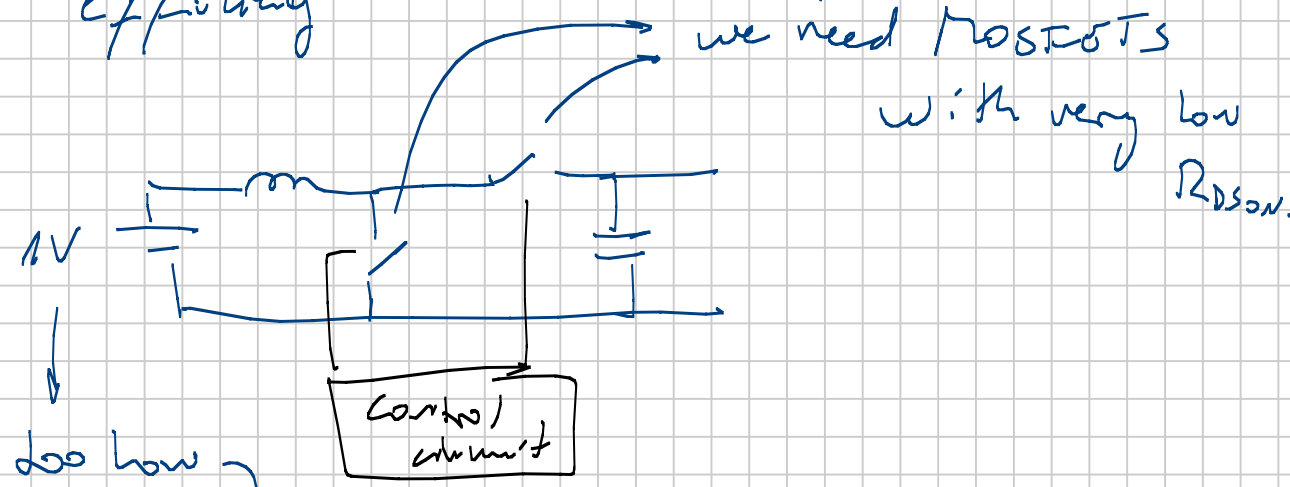Consider a synchronous boost for improved efficiency



The control circuit must be powered from the higher voltage output

Hence, we need a startup circuit.

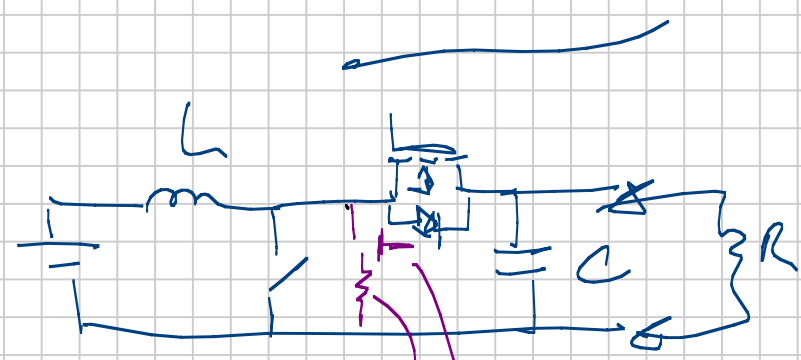

Resistor  
switch

Limits the current through the inductor during startup.


- Startup procedure →
- 1) Switch is closed and L is charged
  - 2) Switch is released
  - 3) Current from the inductor

flows to the output capacitor

the output voltage increases and the controller and gate driver can be powered.

Now consider a source like this:

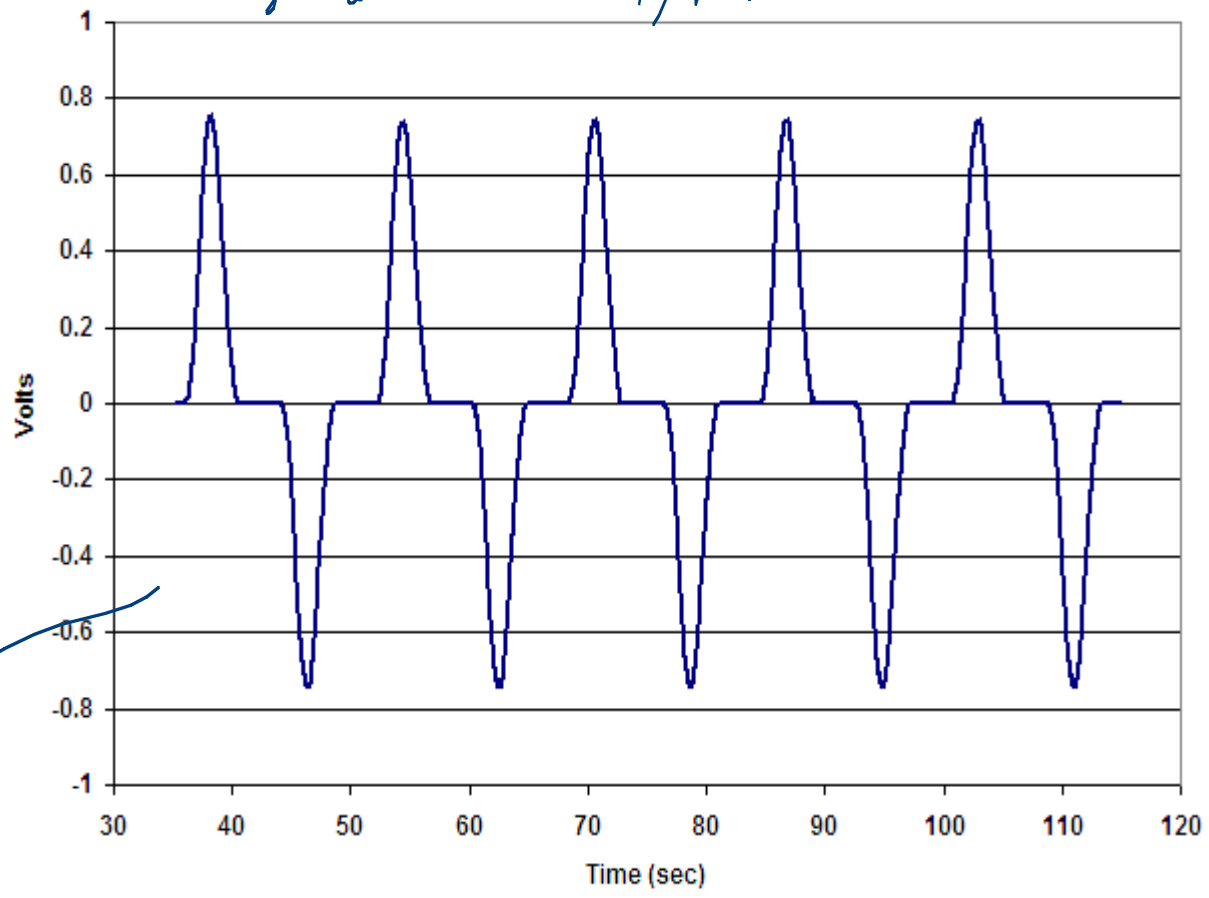e.g. a wave moving a generator back and forth




62.5 kHz

Power converter output  $\rightarrow$  14Vdc (to charge a battery)  
 $\rightarrow$  1000W

When the signal is rectified with 2 synchronous rectifiers with MOSFETs with  $R_{DS(on)} = 6.1 m\Omega$


↓ or parallel of MOSFETs

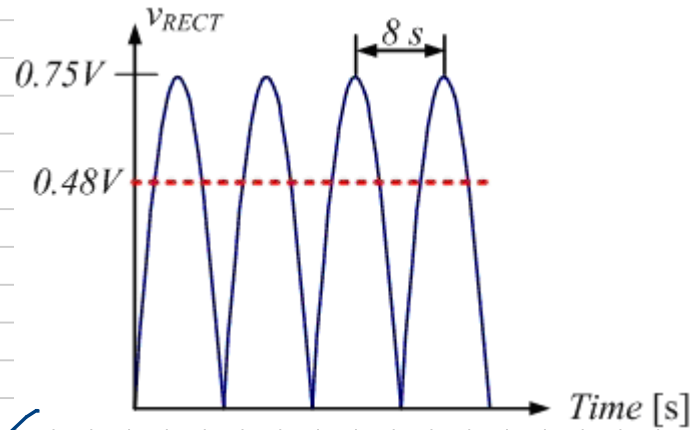

If  $P = 1000W$   
 $\Delta V = 0.2V$   
 $f = 0.125 Hz$

$C = 66 F$   
 ↓  
 too big.

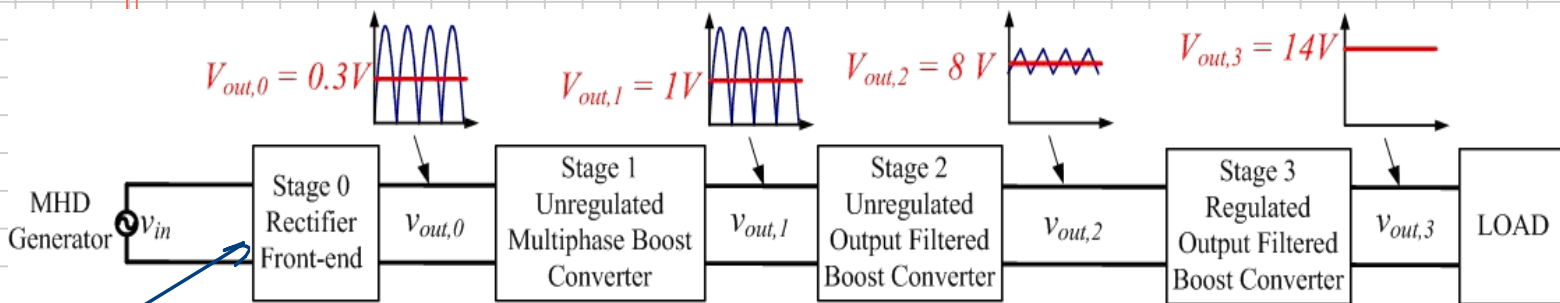
Solution: → Divide the rectifier in  $\left\{ \begin{array}{l} \text{rectifier} \\ \text{filter} \end{array} \right.$





Plain Rectifier



es-

Altracap.

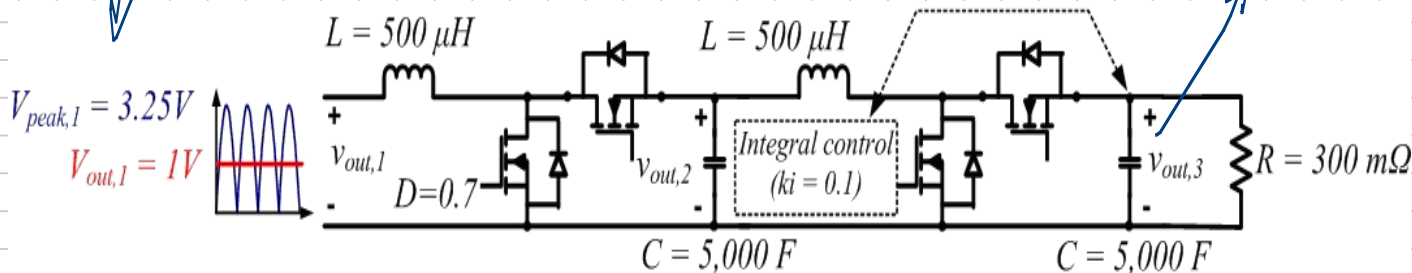

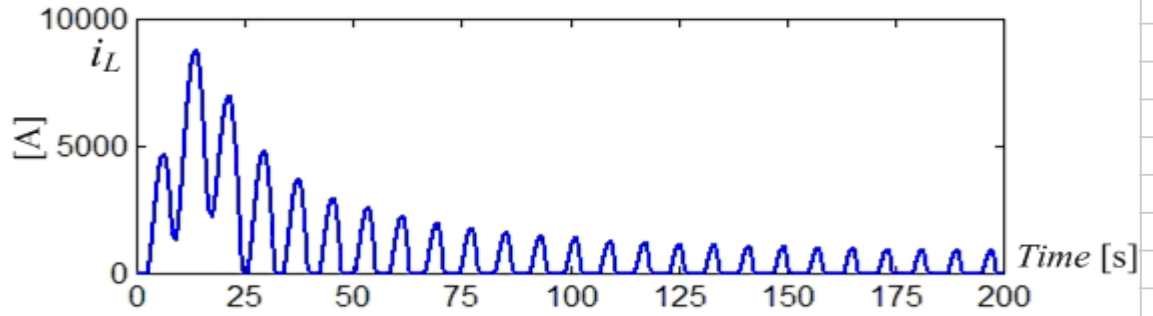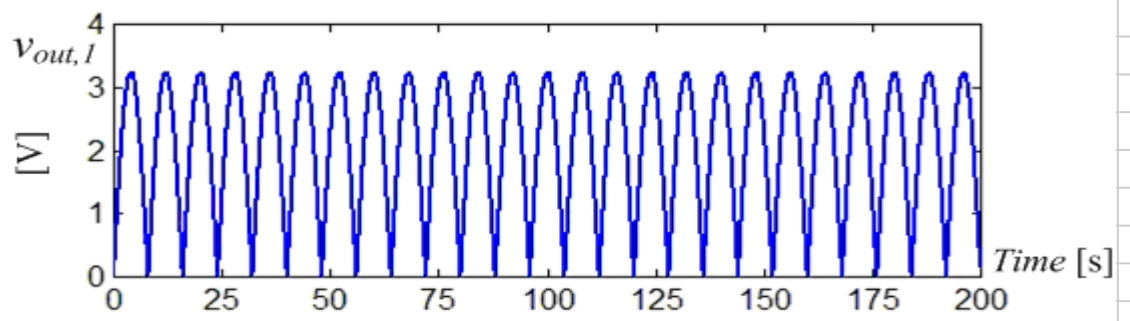

6 steps :

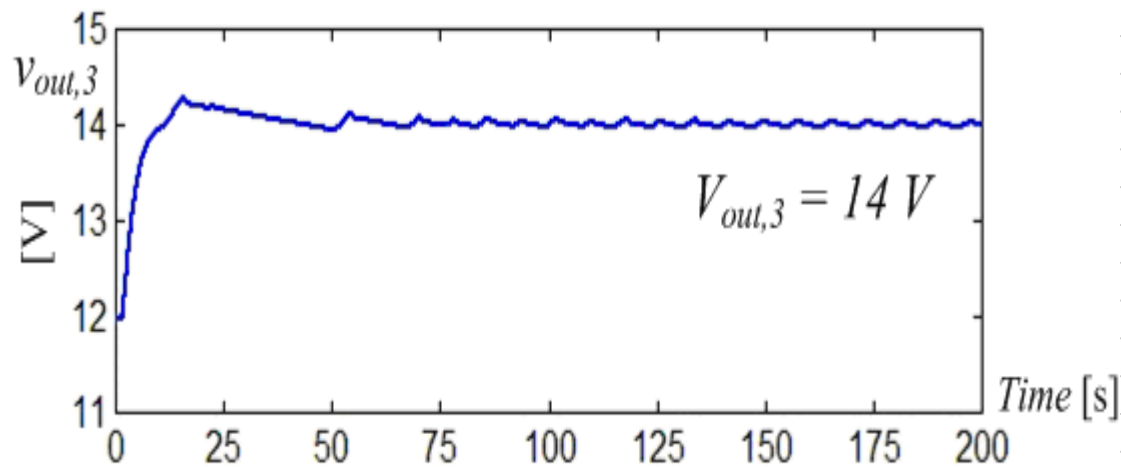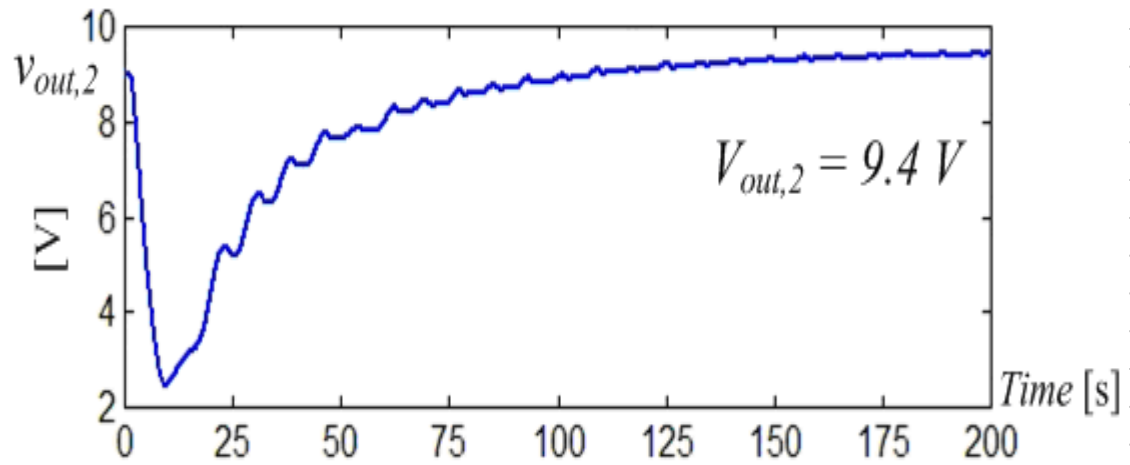

Additional problem  $\rightarrow$  efficiency of intermediate steps  
with 10W input  $\Rightarrow V_{in} < 1V$  an inductor with  
 $R = 0,1 m\Omega$  is too high  $\rightarrow$  Very low efficiency

$\swarrow$   
solution: multiplex boost

$\downarrow$   
like 2 multiple-input boost

$\swarrow$   
As a result overall efficiency is about 60%