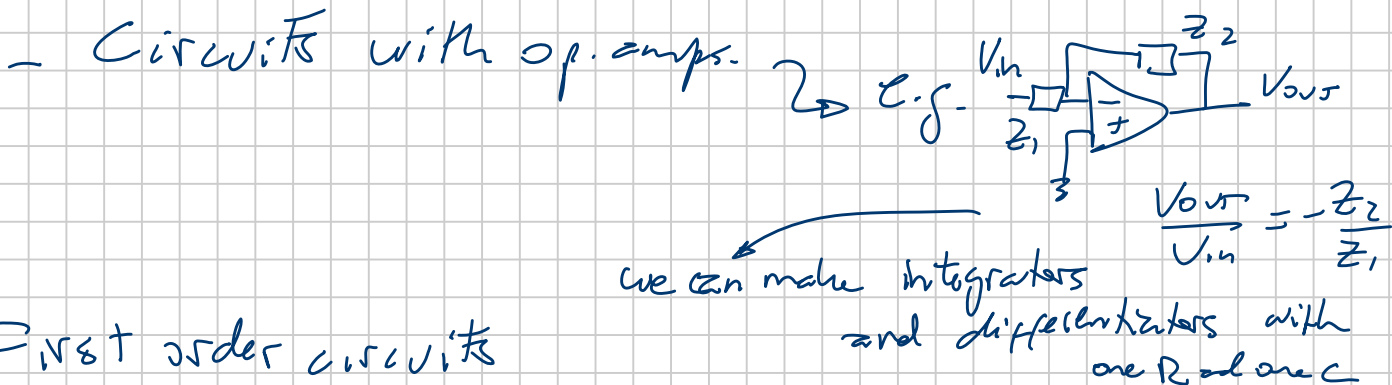


Some important concepts for test #2

- Operational amplifiers:
 - Analysis of circuits with ideal op. amp. $Z_{in} = \infty$
 - $V^+ = V^-$
 - $Z_{out} = 0$



First order circuits

$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$

$$g(t) = \frac{du}{dt} = \begin{cases} 0 & t < 0 \\ \text{undefined} & t = 0 \\ 0 & t > 0 \end{cases}$$

$$\int_{t=0^-}^{t=0^+} g(t) dt = 1$$

$$r(t) = \int_{-\infty}^t u(t) dt = \begin{cases} 0 & t \leq 0 \\ t & t > 0 \end{cases}$$

$$\int_a^b f(t) g(t-b) dt = f(b)$$

$\hookrightarrow a \leq t \leq b$


Complete response = natural response + forced response

\swarrow stored energy \searrow source

time constant \rightarrow depends on circuit parameters



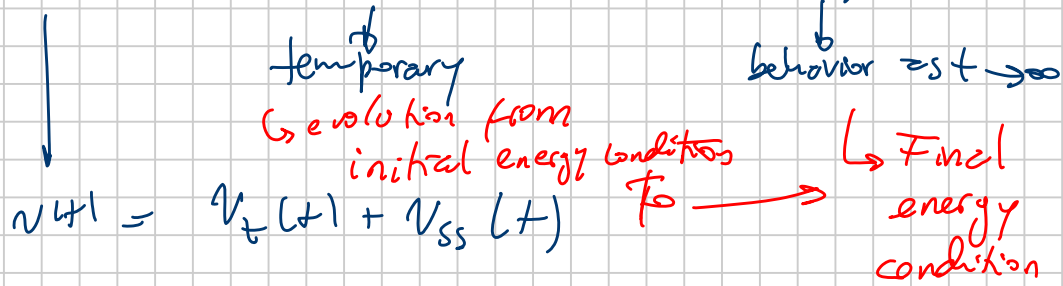Complete response = transient response + steady state response



$$f(t) = f(t \rightarrow \infty) + [f(0) - f(t \rightarrow \infty)] e^{-\frac{t}{\tau}}$$

some signal usually \rightarrow voltage for capacitors
 \rightarrow current for inductors

• Second order circuits

- No external source

\rightarrow First write down characteristic equation:

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

\downarrow Solution leads to 3 cases

- Case a) $\alpha > \omega_0$

$$f(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

\rightarrow solution

\rightarrow A_1 and A_2 are obtained from initial conditions

$$s_1 \neq s_2$$

\rightarrow Both s_1 & s_2 are real numbers

- Case b) $\alpha = \omega_0$

$$s_1 = s_2 = s$$

$$f(t) = (A_1 + A_2 t) e^{-s t}$$

\rightarrow From initial conditions

\downarrow Real number

Case d) $\alpha < \omega_0$

$$f(t) = e^{-\alpha t} (B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t))$$

From initial conditions

S_1 and S_2 are complex conjugates

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

With external source:

$$v(t) = v_n(t) + v_f(t)$$

\downarrow \downarrow
 Natural forced

where $v_f(t)$ depends on $v_s(t)$

$v_f(t)$ has the same form than $v_s(t)$

So if $v_s(t) = V_s$

$$\text{then } v_f(t) = V_{f_0}$$

or if $v_s(t) = V_s \cos \omega_s t$

$$\text{then } v_f(t) = V_{f_1} \cos(\omega_f t) + V_{f_2} \sin(\omega_f t)$$

In all these cases V_{f_i} is unknown.

(we'll see in a short while how to obtain it)

Also we know that $v_n(t)$ depends on circuit initial conditions

$$(*) \left\{ \begin{array}{l} \text{overdamped circuit} \rightarrow V_n(t) = A_1 e^{\alpha_1 t} + A_2 e^{\alpha_2 t} \\ \text{critically damped circuit} \rightarrow V_n(t) = (A_1 + A_2 t) e^{\alpha t} \\ \text{underdamped circuit} \rightarrow V_n(t) = e^{-\alpha t} (A_1 \cos \omega_0 t + A_2 \sin \omega_0 t) \end{array} \right.$$

So here it is the recipe:

1) Solve characteristic eq

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0$$

↓
obtain $(s_{1,2})$ or α or (α, ω_0)
depending which of the cases (*)
is present in this problem

2) Look at $V_s(t)$ and suggest $V_f(t) =$ "same form than $V_s(t)$ "
if $V_s(t) = V_s e^{kt} \rightarrow V_f(t) = V_f e^{kt}$

if $V_s(t) = V_s \rightarrow V_f(t) = V_f_0$

if $V_s(t) = M \cos(\omega_s t) \rightarrow V_f(t) = V_{f1} \cos(\omega_s t) + V_{f2} \sin(\omega_s t)$

Important: see special cases below

3) Calculate $\frac{dV_f}{dt}$ and $\frac{d^2 V_f}{dt^2}$ and replace

them in the circuit equation, i.e.

$$\frac{d^2 V_f}{dt^2} + \frac{R}{L} \frac{dV_f}{dt} + \frac{1}{LC} V_f = \frac{V_s}{LC}$$

↳ Solve the equation to obtain V_{f0} or (V_{f1}, V_{f2})

4) Now, the solution is

$$v_c(t) = v_n(t) + v_f(t)$$

5) $\left\{ \begin{array}{l} \text{Make } v_c(t \rightarrow \infty) = V_0 = v_n(t \rightarrow \infty) + v_f(t \rightarrow \infty) \\ \text{make } \frac{dv_c}{dt}(t \rightarrow \infty) = \frac{dv_n}{dt}(t \rightarrow \infty) + \frac{dv_f}{dt}(t \rightarrow \infty) \end{array} \right.$

→ Solve to obtain A_1 and A_2 .

So initial conditions are applied in the last step!!

Special case

• Suppose that from the characteristic equation:

$$s_{1,2} = \pm j\omega_0$$

And $v_s(t) = V_s \cos \omega_0 t$

then $v_n(t) = A_1 \cos \omega_0 t + A_2 \sin \omega_0 t$

If we do as above then


$$v_f(t) = V_{f1} \cos(\omega_0 t) + V_{f2} \sin(\omega_0 t)$$

Since they
are the same it
won't work


Instead, propose

$$v_f(t) = t (V_{f1} \cos(\omega_0 t) + V_{f2} \sin(\omega_0 t))$$

So instead of having 2 solutions like →

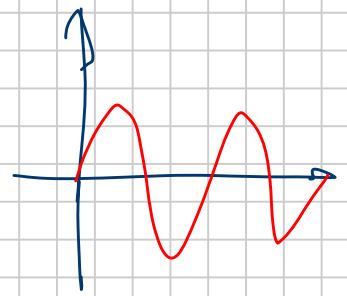

I have →

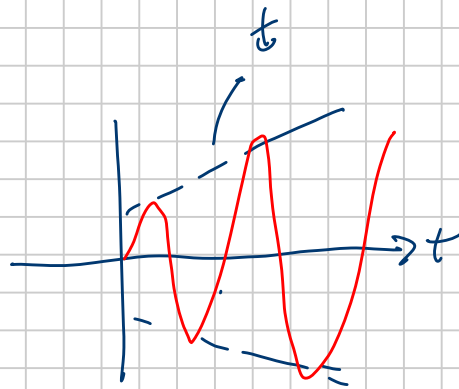

This is just a special case for when

$$N(s) = V_{s1} e^{s_1 t} + V_{s2} e^{s_2 t}$$

and $s_1 = -\sigma_1$ and/or $s_2 = -\sigma_2$

- Sinusoids and phasors / Sinusoidal steady state analysis

$$N(t) = V \cos(\omega t + \phi) = \text{Re}(V e^{j\phi} e^{j\omega t})$$

$$\begin{aligned} \underline{V} &= V \angle \phi = \\ &= V(\cos \phi + j \sin \phi) \end{aligned}$$

Complex number → requires 2 inputs

$$\underline{V}_1 \underline{V}_2 = V_1 V_2 \angle \phi_1 + \phi_2$$

$$\begin{aligned} \underline{V} & \searrow \\ & \phi \end{aligned}$$

time domain

frequency domain

$$\frac{dN(t)}{dt}$$



$$j\omega \underline{V}$$




$$\int N(t) dt$$



$$\frac{\underline{V}}{j\omega}$$

Ohm's law in phasor's domain

$$\hookrightarrow \underline{V} = \underline{I} \underline{Z}$$

Element	\underline{Z}	\underline{Z} (polar)	Resistance	Reactance
	R	$R \angle 0$	R	0
	$j\omega L$	$\omega L \angle 90$	0	ωL
	$\frac{1}{j\omega C}$	$\frac{1}{\omega C} \angle -90$	0	$-\frac{1}{\omega C}$

\downarrow
 $-X_C$

$$KVL \rightarrow \sum_{i=1}^n \underline{V}_i = 0$$

$$KCL \rightarrow \sum_{i=1}^n \underline{I}_i = 0$$

$$\underline{Z}_{eqs} = \sum_{i=1}^n \underline{Z}_i$$

$$\underline{Z}_{eq||} = \frac{1}{\sum_{i=1}^n \frac{1}{\underline{Z}_i}}$$

At resonance $|X_L| = |X_C|$

• AC Power

Instantaneous power

$$p(t) = v(t) i(t) = \frac{V_m I_m}{2} \left[\underbrace{\cos(\varphi_v - \varphi_i)}_{\text{constant}} + \underbrace{\cos(2\omega t + \varphi_v + \varphi_i)}_{\text{time varying}} \right]$$

$$\text{Average power} \rightarrow P(t) = \frac{1}{T} \int_0^T p(t) dt = \frac{V_m I_m}{2} \cos(\varphi_v - \varphi_i)$$

$$r_{rms} \text{ value} \rightarrow X_{rms} = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$$

Complex power $\rightarrow S = VI^* = P + jQ \rightarrow S = V_{rms} I_{rms}$

$$S = I_{rms}^2 Z$$

$$P = V_{rms} I_{rms} \cos(\varphi_V - \varphi_I)$$

$$Q = V_{rms} I_{rms} \sin(\varphi_V - \varphi_I)$$

power factor

$$p.f. = \frac{P}{S}$$

$$p.f. = \cos(\arg(Z))$$

Load	P	Q
R	$I_{rms}^2 R$	0
L	0	$I_{rms}^2 X_L = I_{rms}^2 \omega L$
C	0	$I_{rms}^2 X_C = -\frac{I_{rms}^2}{\omega C}$


Power factor correction

$$C = \frac{P (\tan \theta_1 - \tan \theta_2)}{\omega V_{rms}^2}$$

• 3-phase circuits


wye
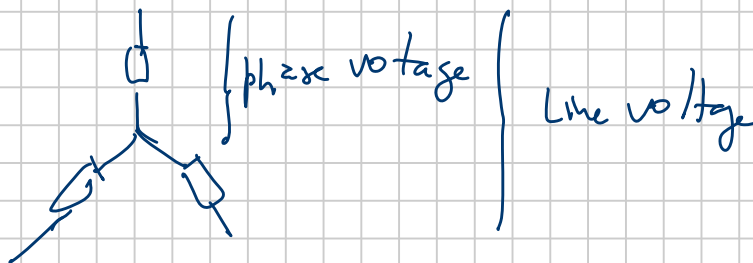
$$V_L = \sqrt{3} V_{ph} \angle 30^\circ$$



$$I_{ph} = I_{line}$$

Delta

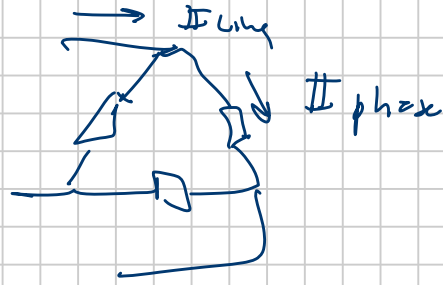

$$I_{Line} = \sqrt{3} I_{Phase} \angle -30^\circ$$

$$V_{ph} = V_{Line}$$

$$|G| = 3 V_{rms, ph} I_{rms, ph} \cos \varphi$$

$$P_{ph} = V_{rms, ph} I_{rms, ph}$$

$$P = \sqrt{3} V_{rms, L} I_{rms, L} \cos \varphi = 3 V_{rms, ph} I_{rms, ph} \cos \varphi$$

$$Q = \sqrt{3} V_{rms, L} I_{rms, L} \sin \varphi = 3 V_{rms, ph} I_{rms, ph} \sin \varphi$$

$$S = \sqrt{3} V_{rms, L} I_{rms, L}^*$$