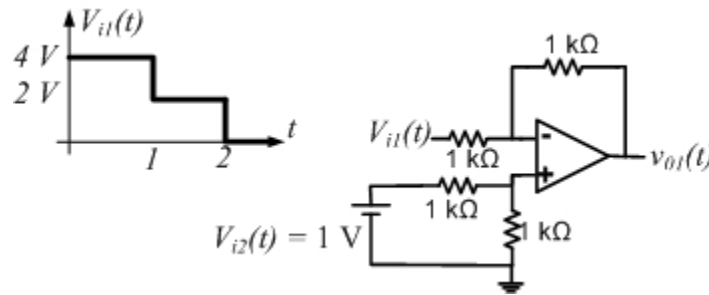


EE411 – Summer 2008, Test 1


Please, show all your work on the test sheets. A correct answer without supporting work gets no credit. One sheet of notes is permitted. Write your name in all pages. Do not un-staple. You have 60 minutes to complete the test.

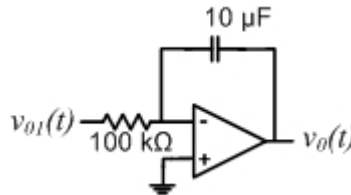**Problem 1 (35 points)**

For the circuit in the next figure, sketch  $v_{o1}(t)$ .





Using  $v_{o1}(t)$  as your input voltage for the next circuit, sketch the output voltage  $v_o(t)$  considering that at the initial time  $t=0, v_o(t=0) = 0$



Top circuit: Difference Amplifier

$$v_{o1} = \frac{R_2}{R_1} \frac{(1 + \frac{R_1}{R_2})}{(1 + \frac{R_3}{R_4})} v_{i2} - \frac{R_2}{R_1} v_{i1}$$

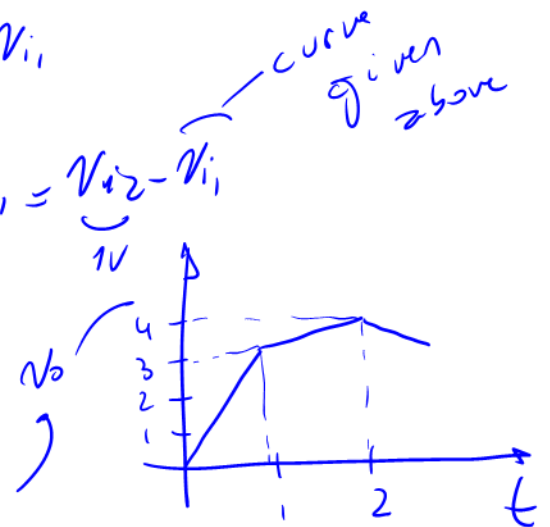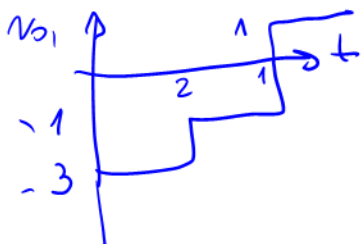Since all Resistances are equal then  $v_{o1} = v_{i2} - v_{i1}$




The second circuit is an integrator. So,

$$v_o = \begin{cases} -\frac{1}{R_c} \int_0^t (-3) dt = -(-3)t = 3t & \text{for } 0 \leq t < 1 \\ -\frac{1}{R_c} \int_1^t (-1) dt + v_o(t=1) = -\int_1^t (-1) dt + 3 = t - 1 + 3 = t + 2 & \text{for } 1 \leq t < 2 \\ -\frac{1}{R_c} \int_2^t (1) dt + v_o(t=2) = -t + 2 + 4 = -t + 6 & \text{for } 2 \leq t < \infty \end{cases}$$


## EE411 – Summer 2008, Test 1

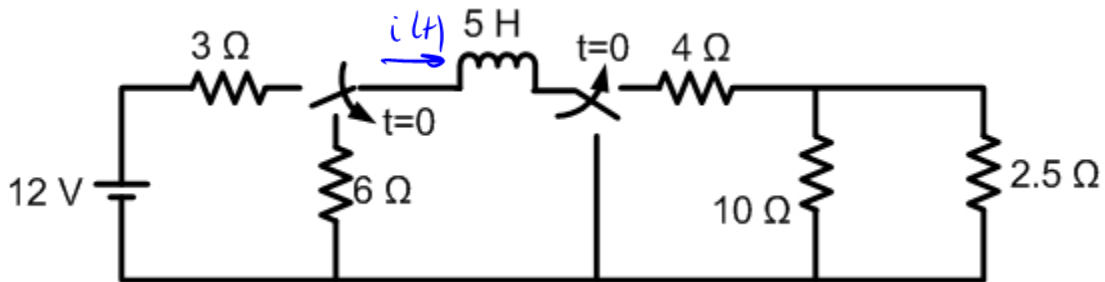**Problem 2 (30 points)**


Find out the equation for  $i(t)$  with  $t \geq 0$  for the circuit in the next figure. Notice that the two switches move at the same time.



For  $t=0^-$

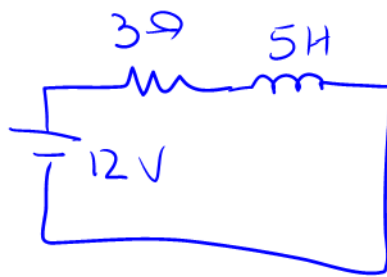


The inductor  
is a  
short  
circuit

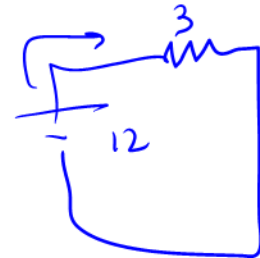

$$i_L(0^-) = \frac{12}{3} = 4A = I_0$$

For  $t=0^+$

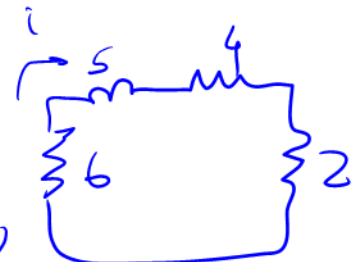


$$i(t) = I_0 e^{-t/\tau} = 4e^{-2.4t}$$

$$\tau = \frac{L}{R} = \frac{5}{12} = 2.4$$




EE411 – Summer 2008, Test 1

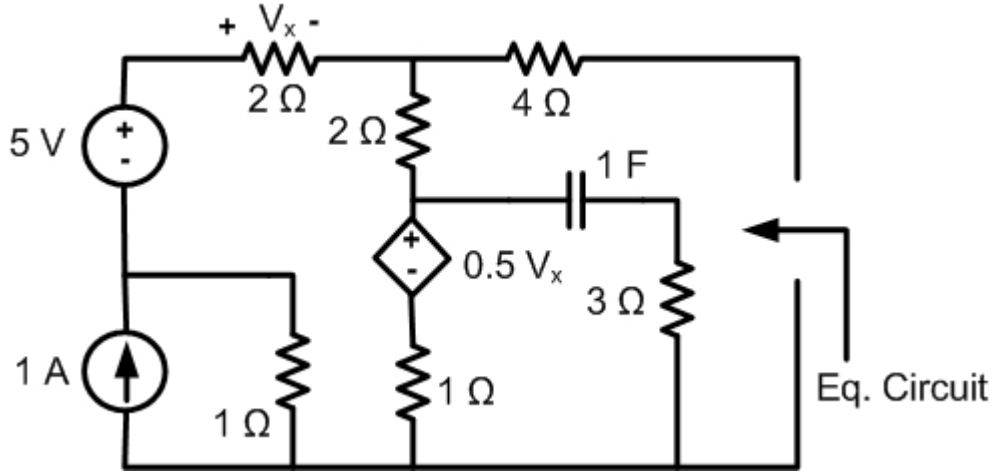**Problem 3 (35 points)**

Find the Thevenin and Norton equivalents for the dc circuit in the next figure.



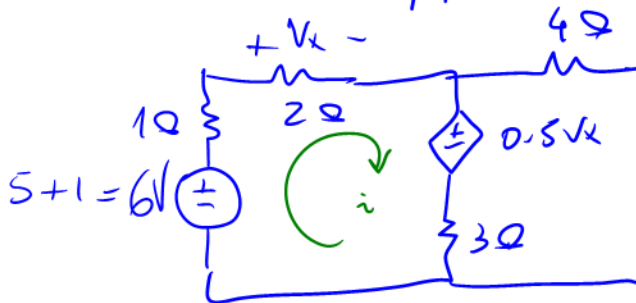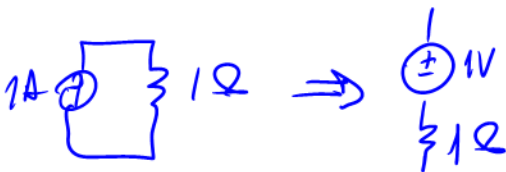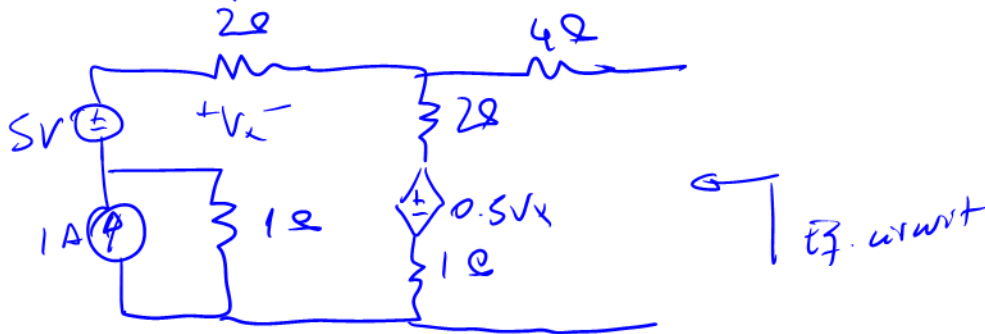with dc the capacitor is an open circuit. hence,




$$V_o = 0.5V_x + 3i$$

$$6 = 1 \cdot i + 2 \cdot i + 3 \cdot i + 0.5 \cdot 2i$$

$$6 = 7i \implies i = \frac{6}{7} = 0.857A$$
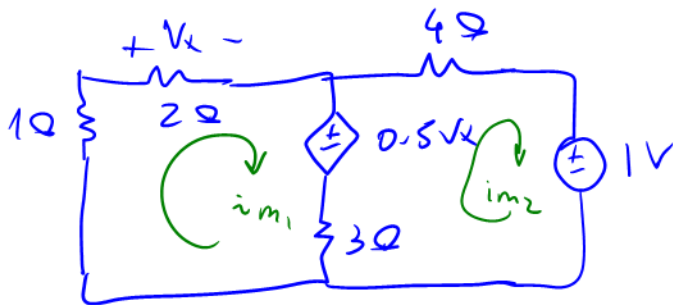
$$\text{hence } V_o = 0.5 \cdot 2 \cdot i + 3i = 4i \approx 3.43V$$



#1 
$$1i_{m1} - 2i_{m1} - \underbrace{0.5(2i_{m1})}_{V_x} - 3(i_{m1} - i_{m2}) = 0$$

$$7i_{m1} + 3i_{m2} = 0 \rightarrow 7i_{m1} - 3i_{m2} = 0$$

#2 
$$-3(i_{m2} - i_{m1}) + 0.5(2i_{m1}) - 4i_{m2} - 1 = 0$$

$$-7i_{m2} + 4i_{m1} - 1 = 0$$



$$\hookrightarrow -4i_{m1} + 7i_{m2} = -1$$

$$\begin{cases} 7i_{m1} - 3i_{m2} = 0 \\ -4i_{m1} + 7i_{m2} = -1 \end{cases}$$

$$i_{m2} = \frac{\begin{vmatrix} 7 & 0 \\ -4 & -1 \end{vmatrix}}{\begin{vmatrix} 7 & -3 \\ -4 & 7 \end{vmatrix}} = \frac{-7}{49 - 12} = \frac{-7}{37} = 0.189$$


$$i_o = -i_{m2} = 0.189$$
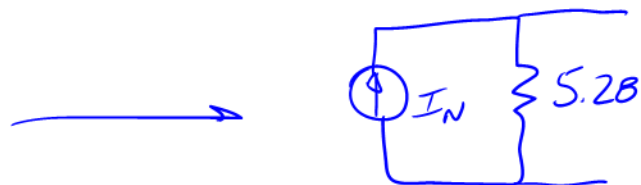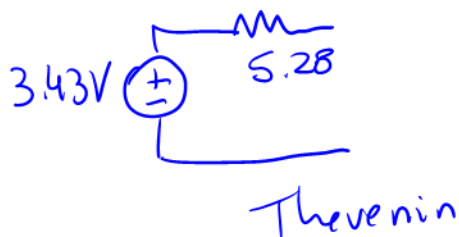
$$R_{TH} = R_N = \frac{V_o}{i_o} = \frac{1}{0.189} \approx 5.28$$



$$I_N = \frac{3.43}{5.28} = 0.648$$

Norton → Safety check

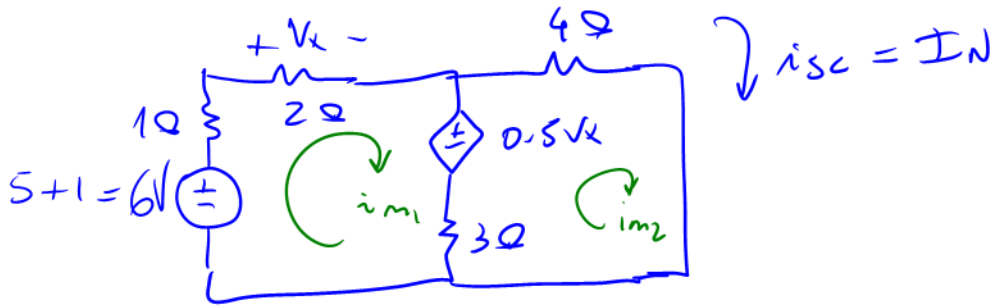

#1 →  $7i_{m1} - 3i_{m2} = 6$

#2 →  $-3(i_{m2} - i_{m1}) + 0.5(2i_{m1}) - 4i_{m2} = 0$

$-4i_{m1} + 7i_{m2} = 0$

→  $i_{m1} = \frac{7}{4}i_{m2}$

$\frac{49}{4}i_{m2} - 3i_{m2} = 6$

↓  
 $37i_{m2} = 24$

$i_{sc} = i_{m2} = \frac{24}{37} = 0.648 \text{ A}$

