

EE411 – Fall 2009, Test 2

Please, show all your work on the test sheets. A correct answer without supporting work gets no credit. One sheet of notes is permitted. Write your name in all pages. Do not un-staple. You have 60 minutes to complete the test.

Problem 1 (30 points)

Consider a series RLC circuit excited by a sinusoidal voltage source with an amplitude of 10 V. Consider also that $R = 5 \Omega$, $L = 2 \text{ mH}$, and $C = 8 \text{ mF}$. Please answer the following questions:

- Please write down the expression without numbers for the current phasor \mathbf{I} in terms of the input voltage phasor \mathbf{V}_s .
- What is the (resonant) frequency of the voltage source that yields the maximum magnitude for \mathbf{I} ? Write down the expression without numbers for \mathbf{I} at this specific condition.
- What is the maximum magnitude of \mathbf{I} ? (with numbers)

$$a) \quad \mathbf{I} = \frac{\mathbf{V}_s}{\mathbf{Z}} = \frac{\mathbf{V}_s}{R + j(\omega L - \frac{1}{\omega C})}$$

$$b) \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{16 \cdot 10^{-6}}} = 0.25 \cdot 10^3 = 250$$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{250}{2\pi} = 39.79 \text{ Hz}$$

$$\mathbf{I} = \frac{\mathbf{V}_s}{R}$$

$$c) \quad \mathbf{I} = \frac{10}{5} = 2 \text{ A}$$


EE411 – Fall 2009, Test 2

Problem 2 (30 points)

The figure shows the equivalent circuit of a typical industrial load with capacitors compensating the power factor. Unfortunately, the person that calculated the capacitors didn't take EE411 and the capacitance does not provide enough compensation.

- What is the active and reactive power measured at the grid tie?
- What is power factor?
- How much capacitance should be added to reach a power factor of at least 0.9?
- How much capacitance should be added to reach a power factor of at least 0.9 if you were in Europe where the line frequency is 50 Hz?

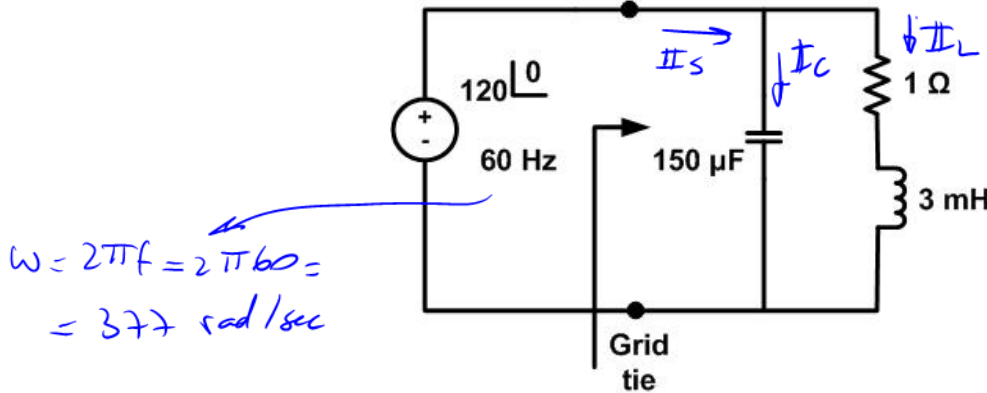Consider that all voltages and currents magnitudes are rms values.



$$a) P_L = I_L^2 R = \frac{120^2}{\left(\sqrt{1 + (3 \cdot 10^{-3} \cdot 377)^2}\right)^2} \approx 6.32 \text{ kW}$$

$$Z_L = 1 + j 377 \cdot 3 \cdot 10^{-3} = 1.51 \angle 48.52^\circ$$

$$Q_L = I_L^2 X_L = (79.47)^2 \cdot 3 \cdot 10^{-3} \cdot 377 \approx 7.14 \text{ kVAR}$$

$$\hookrightarrow I_L = \frac{120}{1.51} = 79.47$$

$$Q_C = \frac{V_S^2}{X_C} = 120^2 \cdot 377 \cdot 150 \cdot 10^{-6} = 814.32 \text{ VAR}$$

$$\Delta \text{ at the grid tie} \rightarrow P \approx 6.32 \text{ kW}$$

$$\hookrightarrow Q \approx 7.14 - 0.814 \approx 6.33 \text{ kVAR}$$

$$b) \text{ pf} = \frac{P}{S} = \frac{6.32}{\sqrt{6.32^2 + 6.33^2}} = 0.706 \rightarrow \varphi_0 = \cos^{-1} 0.706 \approx 45^\circ$$

c) For $\cos \varphi_n = 0.9 \rightarrow \varphi_n = 25.84^\circ$

$$\begin{aligned} \text{New } C &= \left| \frac{P (\tan \varphi_n - \tan \varphi_0)}{\omega V_s^2} \right| = \left| \frac{6320 (\tan 25.84 - \tan 45)}{377 \cdot 120^2} \right| \\ &= \left| \frac{6320 (0.4842 - 1)}{5428800} \right| \approx 600 \mu\text{F} \end{aligned}$$

d) In Europe

$$\omega = 2\pi f = 314.16$$

$$I_L = \frac{120}{\sqrt{1 + (3 \cdot 10^{-3} \cdot 314.16)^2}} = \frac{120}{1.374} = 87.32$$

$$P_L = I_L^2 R = (87.32)^2 \cdot 1 \approx 7.63 \text{ kW}$$

$$Q_L = I_L^2 X_L = (87.32)^2 \cdot 314.16 \cdot 3 \cdot 10^{-3} = 7.187 \text{ kVAR}$$

$$Q_C = \frac{V_s^2}{X_C} = \frac{120^2 \cdot 314.16 \cdot 150 \cdot 10^{-6}}{1} \approx 6.78 \text{ kVAR}$$

$$P_L = 7.63 \text{ kW}$$

$$Q = 7.187 - 0.678 = 6.508 \text{ kVAR}$$

$$\text{PF} = \frac{7.63}{\sqrt{7.63^2 + 6.51^2}} = 0.76 \rightarrow \varphi_0 = 40.47$$

$$\text{New } C = \left| \frac{7630 (\tan 25.84 - \tan 40.47)}{314.16 \cdot 120^2} \right| = 622 \mu\text{F}$$


EE411 – Fall 2009, Test 2

Problem 3 (40 points)

For the 3-phase circuit in the figure calculate:

- Load's phase and line voltage phasors (all 6 of them).
- Load's phase and line current phasors (all 6 of them).
- Load's total active and reactive power.
- Load's complex power.
- Source's total reactive power.

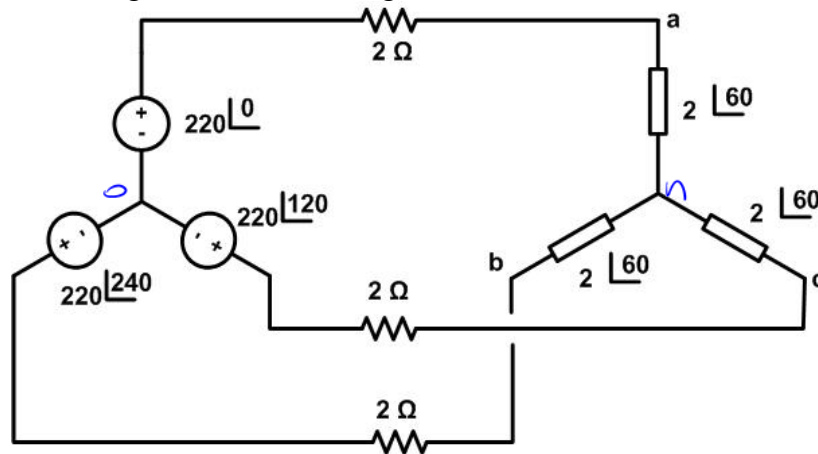Consider that all voltages and currents magnitudes are rms values.



b) Load's phase and line currents are the same

$$Z_T = 2 \angle 0 + 2 \angle 60 = 3.46 \angle 30$$

$$I_a = \frac{V_{ao}}{Z_T} = \frac{220 \angle 0}{3.46 \angle 30} = 63.51 \angle -30$$

$$I_b = I_a \angle -120 = 63.51 \angle -150$$

$$I_c = I_a \angle 120 = 63.51 \angle 90$$

$$a) V_{an} = I_a Z_L = 63.51 \angle -30 \cdot 2 \angle 60 = 127.02 \angle 30$$

$$V_{bn} = V_{an} \angle -120 = 127.02 \angle -90$$

$$V_{cn} = V_{an} \angle 120 = 127.02 \angle 150$$

Line voltages

$$V_{ab} = V_{an} \sqrt{3} \angle 30 = 220 \angle 0$$

$$V_{bc} = V_{ab} \angle -120 = 220 \angle -120$$

$$V_{ca} = V_{bc} \angle 120 = 220 \angle 120$$

$$c) P_L = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \cdot 63.51 \cdot 220 \cdot \cos(60) = 12.1 \text{ kW}$$

$$Q_L = \sqrt{3} V_L I_L \sin \phi = 21 \text{ kVAR}$$

$$d) S = P_L + jQ_L = 12.1 + j21$$

$$\hookrightarrow S_L = \sqrt{P_L^2 + Q_L^2} = 24.2 \text{ kVA}$$

$$e) \text{ From conservation of energy } Q_S = Q_L = 21 \text{ kVAR}$$