 


**Fall 2018**  
**EE 460R: Introduction to VLSI Design**  
**EE 382M-7: VLSI-1**  
**Homework #3**


**Assigned: September 25<sup>th</sup>, 2018**

**Due: October 4<sup>th</sup>, 2018**

1. Find the rising and falling propagation delays of an AND-OR-INVERT gate using the Elmore delay model. Estimate the diffusion capacitance based on a stick diagram of the layout.
2. Find the worst-case Elmore parasitic delay of an  $n$ -input NOR gate and an  $n$ -input NAND gate.
3. Consider the two designs of a 2-input AND gate shown in the following figure. Give an intuitive argument about which will be faster. Back up your argument with a calculation of the Elmore delay, and input capacitances  $x$  and  $y$  to achieve the delay.



 4. Size the following gates using a stage ratio of 3. Assume a unit inverter has a pMOS transistor of width 4 and an nMOS transistor of width 2.



5. Size the following gate so that it has the same drive strength as an inverter that has a pMOS transistor of width 3 and an nMOS transistor of width 1.

