

**Fall 2018**  
**EE 460R: Introduction to VLSI Design**  
**EE 382M-7: VLSI-1**  
**Homework #7**

**Assigned: November 13<sup>th</sup>, 2018**


**Due: November 27<sup>th</sup>, 2018**

**1. Problem 12.10 from the Exercises for Chapter 11**


12.10 Sketch a dot diagram for a 2-input XOR using a PLA.

**2. Derive the switching probabilities for the following circuits:**


a)

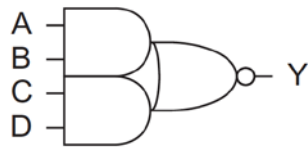

b)

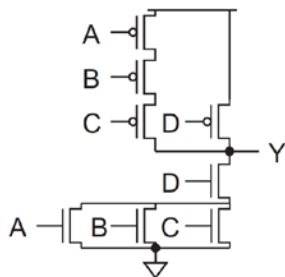


c)

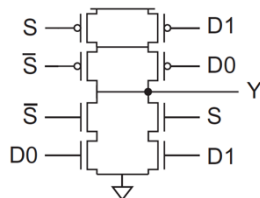

### 3. Problem 5.4 from the Exercises for Chapter 11

5.4 Determine the activity factor for the signal shown in Figure 5.34. The clock rate is 1 GHz.

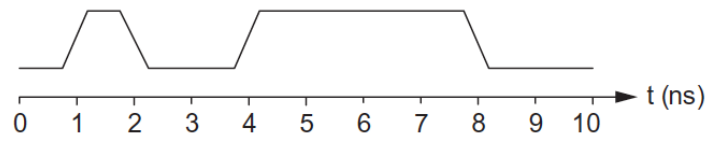

**FIGURE 5.34** Signal for Exercise 5.4

4) Derive the following dynamic power equation:

$$\text{Power}_{\text{dyn}} = \frac{1}{2} C_{\text{switch}} * V_{\text{dd}} * \Delta V_{\text{switch}} * \text{Freq}$$