


# Lecture 10: Sequential Elements (Latches and Flip Flops)

**Mark McDermott**


**Electrical and Computer Engineering  
The University of Texas at Austin**
 
# Sequencing

- **Combinational logic (CL)**
  - output depends on current inputs
- **Sequential logic**
  - output depends on current and previous inputs
  - Requires separating previous, current, future
  - Called *state* or *tokens*
  - Ex: FSM, pipeline



Finite State Machine

 

Pipeline


# Sequencing (cont)

---





- **If tokens moved through pipeline at constant speed, no sequencing elements would be necessary**
- **Ex: fiber-optic cable**
  - Light pulses (tokens) are sent down cable
  - Next pulse sent before first reaches end of cable
  - No need for hardware to separate pulses
  - But dispersion sets min time between pulses
- **This is called wave pipelining in circuits**
- **In most circuits, dispersion is high**
  - Delay fast tokens so they don't catch slow ones.
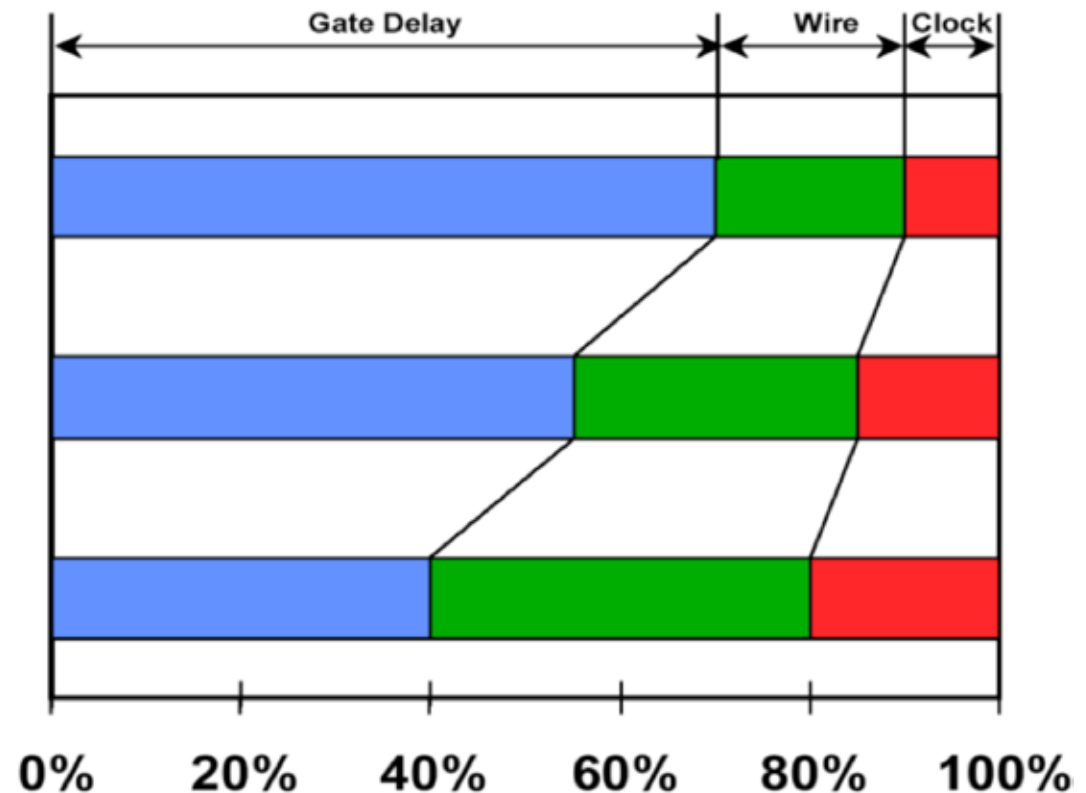
# Sequencing Overhead


- Use flip-flops to delay fast tokens so they move through exactly one stage each cycle
- Inevitably adds some delay to the slow tokens
- Makes circuit slower than just the logic delay
  - Called sequencing overhead
- Some people call this clocking overhead
  - But it applies to asynchronous circuits too
  - Inevitable side effect of maintaining sequence



# Basic LATCH Operation

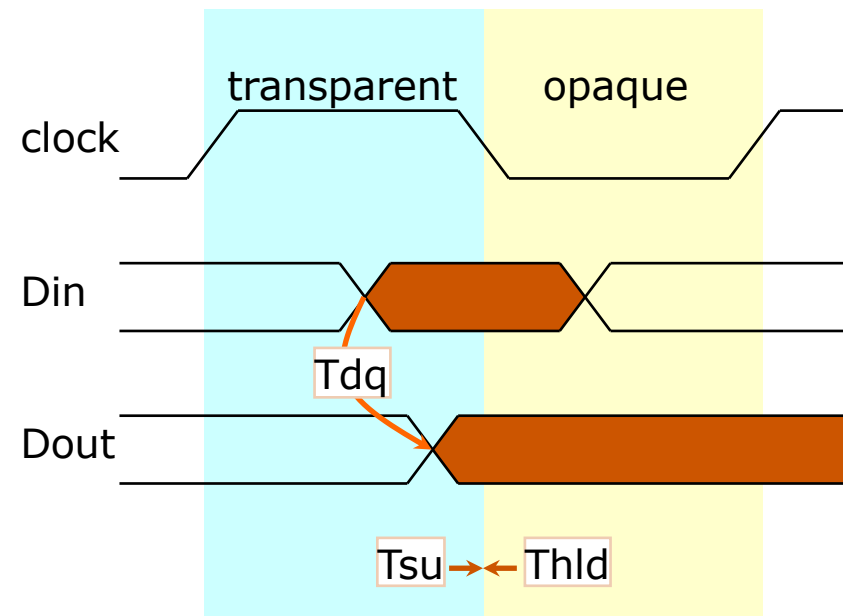 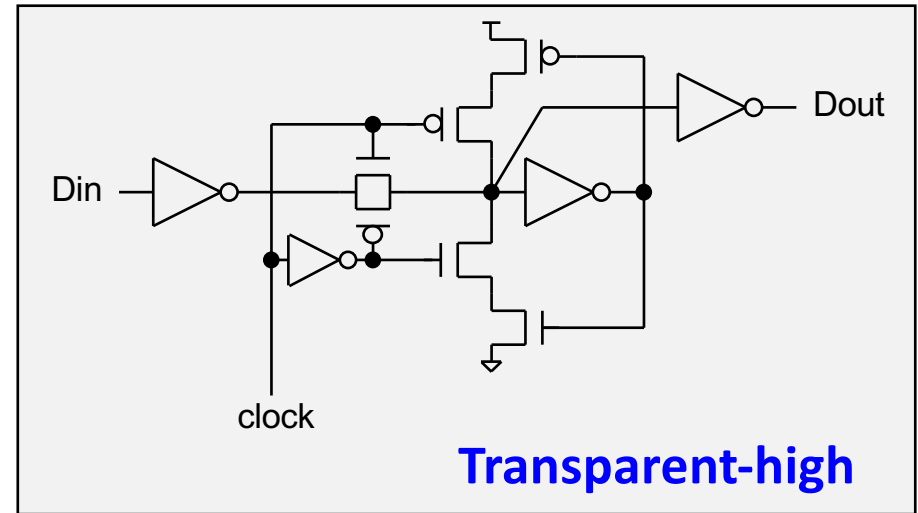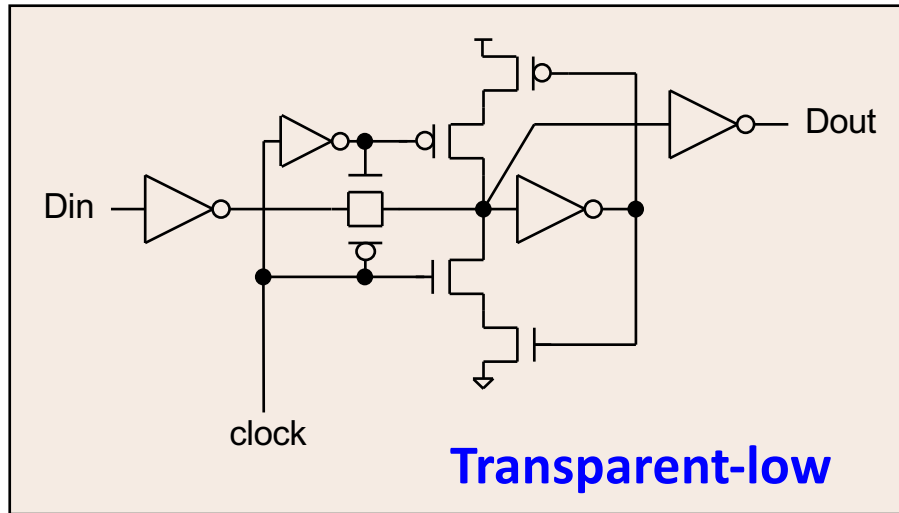

# Building a Flip-Flop with Two Latches

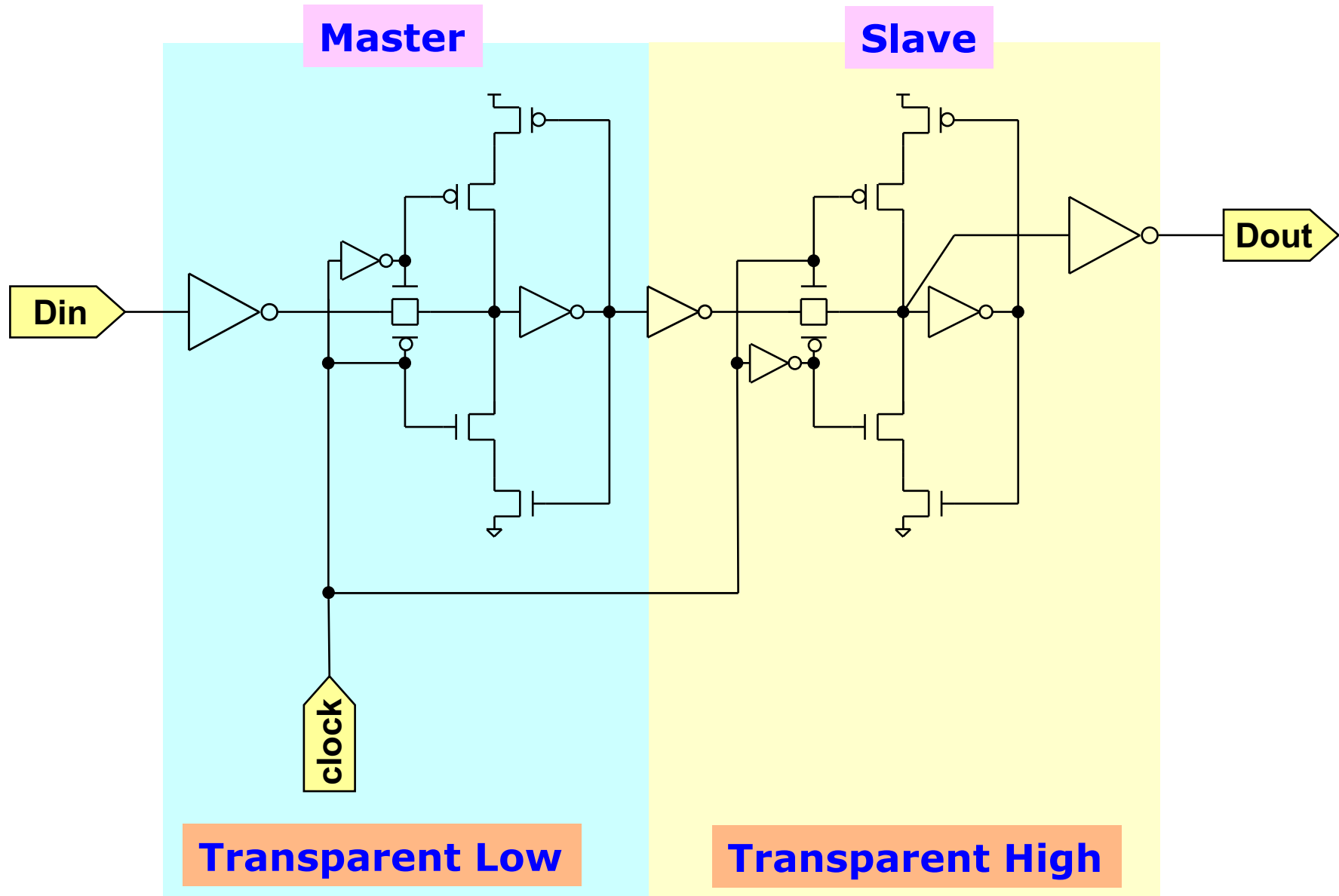




# Difference between a Latch and a Flip-Flop

## Latch: Level sensitive

a.k.a. transparent latch, D latch
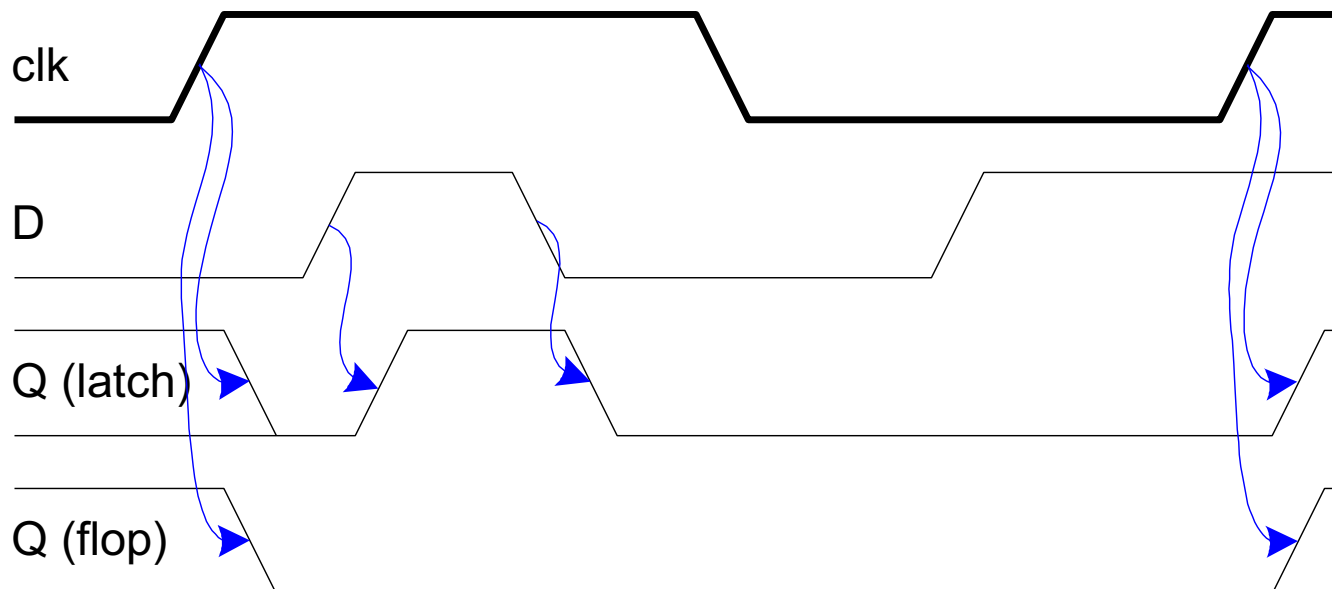  
## Flip-flop: Edge triggered

a.k.a. master-slave flip-flop, D flip-flop, D register, FLOP




# Static Latch Design

- Static latches are essential for DSM applications


- **Tristate feedback**

 - + Static
- Backdriving risk
- Susceptible to noise on D input



- **Buffered input**

 
- + Fixes diffusion input
- + Noninverting






 
# Static Latch Design (cont.)

- **Buffered output**
  - + No back driving
  
- **Widely used in standard cells**
  - + Very robust (most important)
    - Rather large
    - Rather slow (1.5 – 2 FO4 delays)
    - High clock loading



  
# Static Latch Design (cont.)

- **Datapath latch**
  - + Smaller, faster
  - un-buffered input -> okay for datapaths




# AMD K5: Datapath

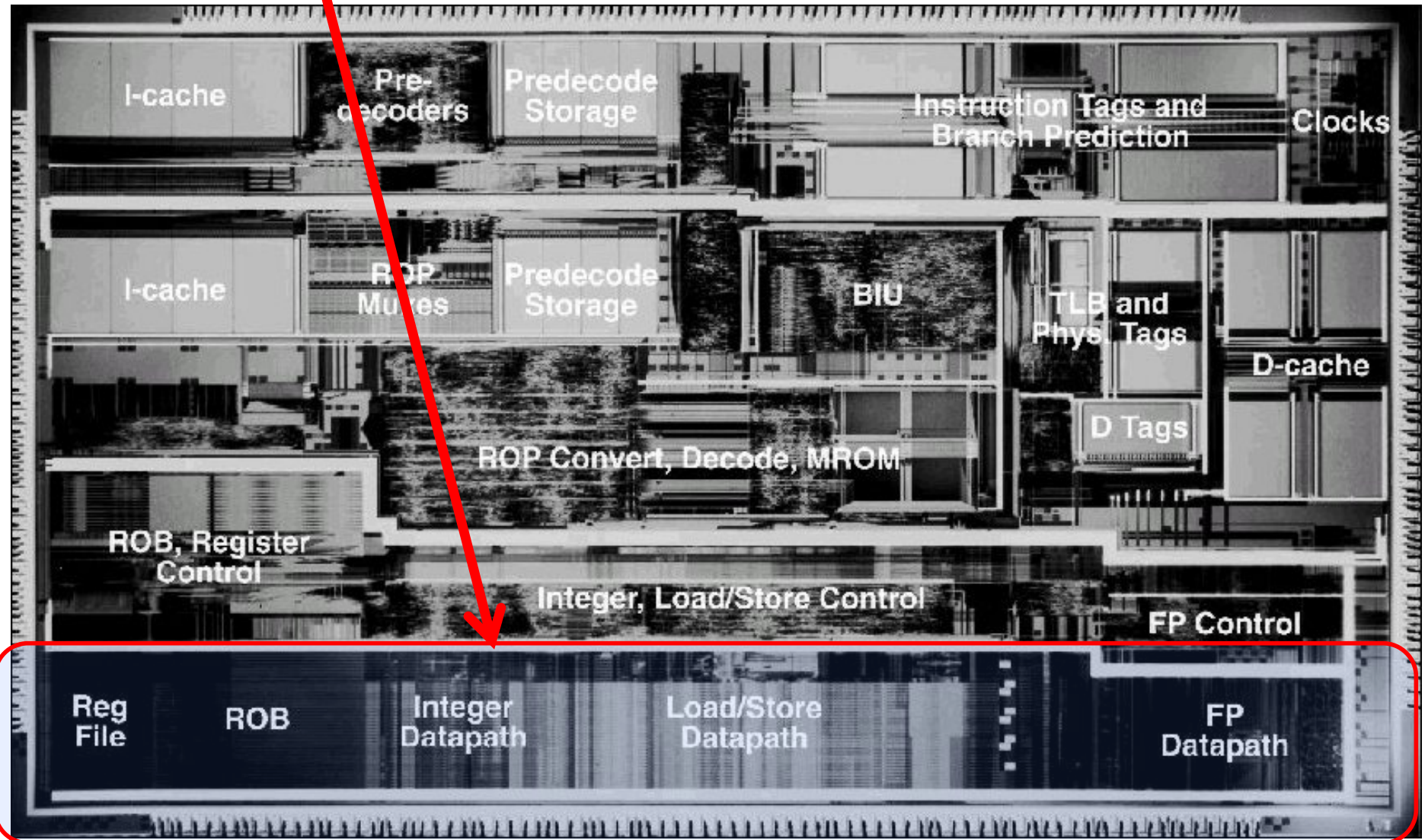
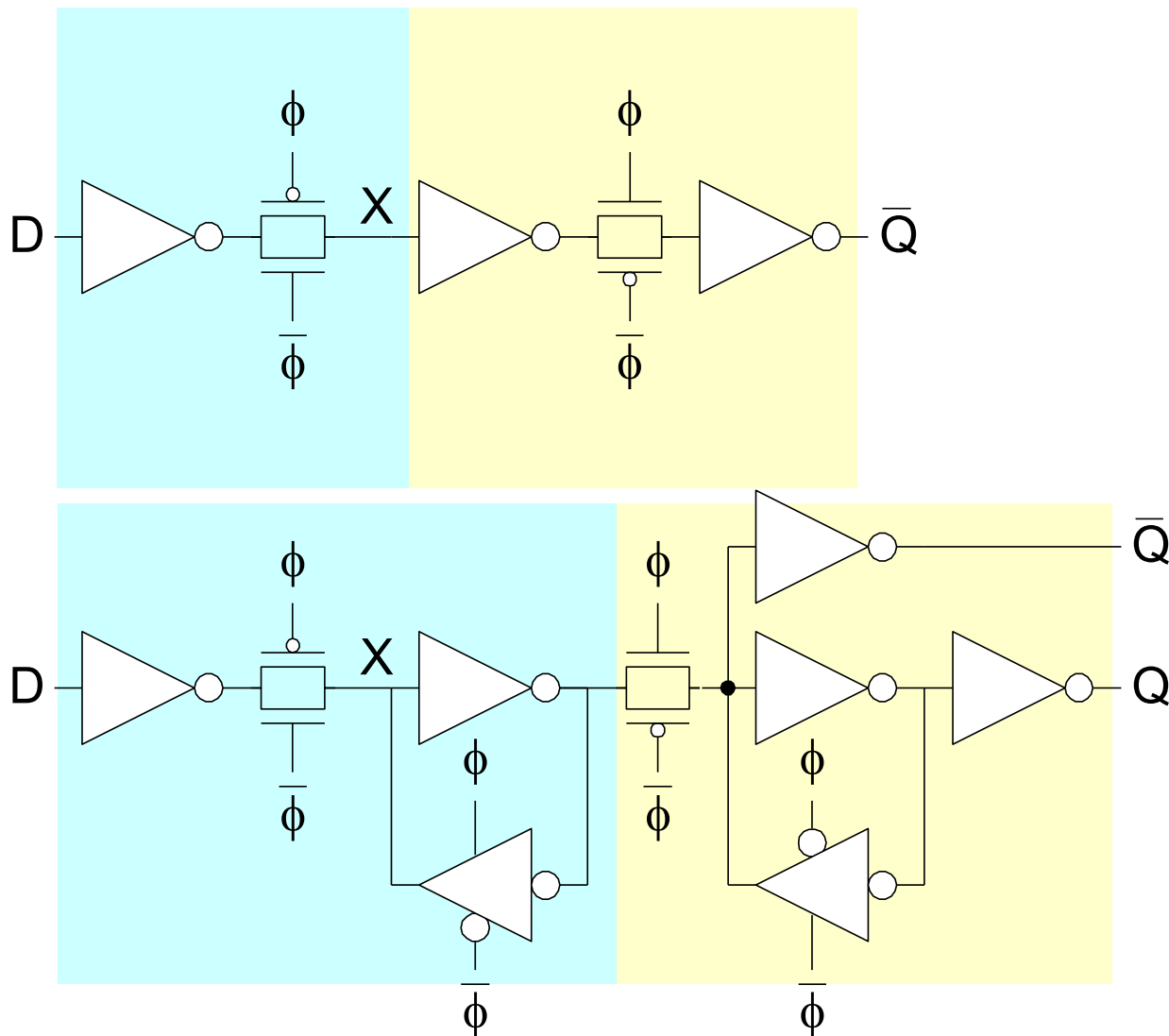
# Flip-Flop Designs


- Flip-flop is built as pair of back-to-back latches




# Clock Enable

- **Clock Enable: ignore clock when en = 0**
  - Mux: increases latch D-Q delay
  - Clock Gating: increase enable setup time, skew





Symbol

 

Multiplexer Design

 


Clock Gating Design

    

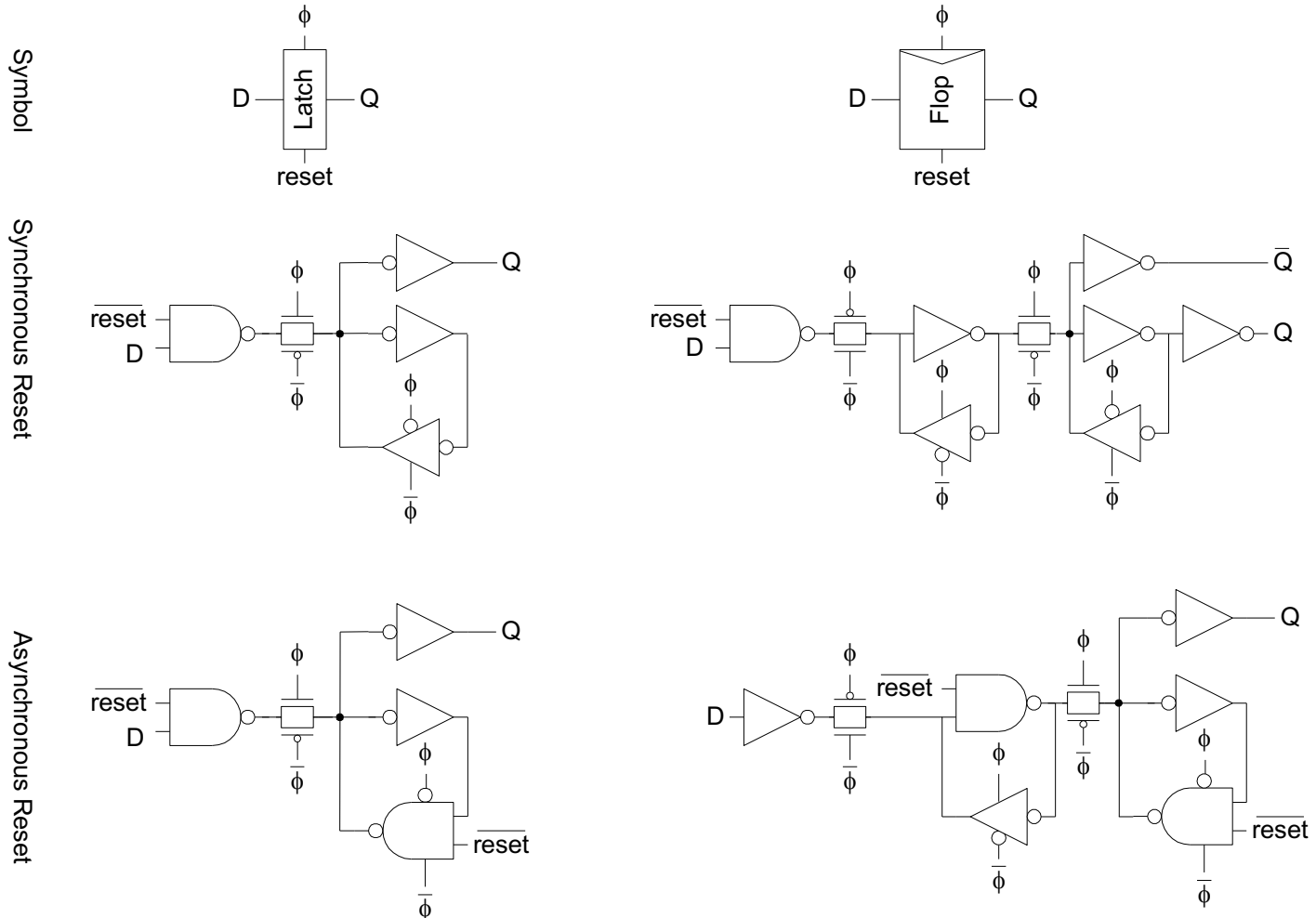
# Reset

- Force output low when reset asserted
- Synchronous vs. asynchronous



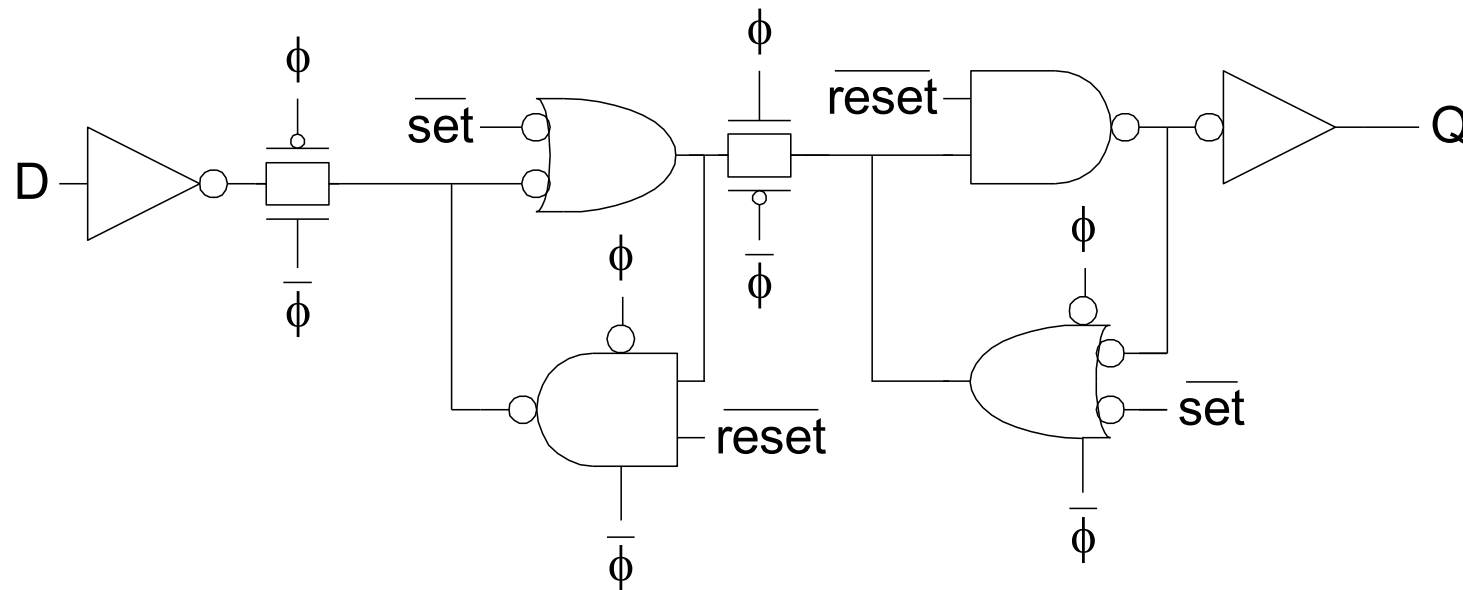
# Set / Reset

- Set forces output high when enabled
- Flip-flop with asynchronous set and reset


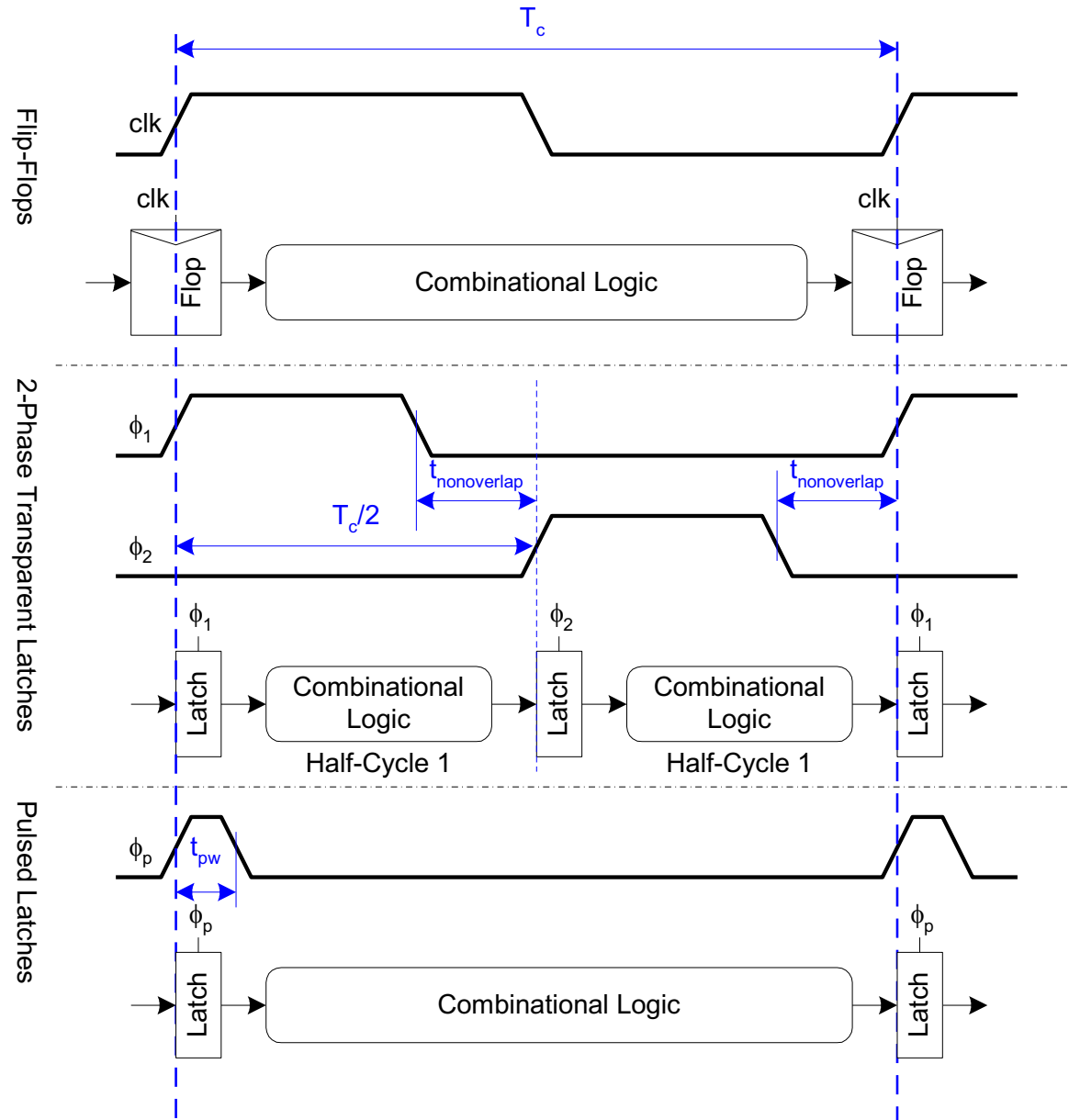
# Sequencing Methods

- Flip-flops
- 2-Phase Latches
- Pulsed Latches











# Timing Diagrams


## Contamination and Propagation Delays

|             |                              |
|-------------|------------------------------|
| $t_{pd}$    | Logic Propagation Delay      |
| $t_{cd}$    | Logic Contamination Delay    |
| $t_{pcq}$   | Latch/Flop Clk-Q Prop Delay  |
| $t_{ccq}$   | Latch/Flop Clk-Q Cont. Delay |
| $t_{pdq}$   | Latch D-Q Prop Delay         |
| $t_{cdq}$   | Latch D-Q Cont. Delay        |
| $t_{setup}$ | Latch/Flop Setup Time        |
| $t_{hold}$  | Latch/Flop Hold Time         |

      

# Master-Slave Flip-Flop

## Illustration of delays

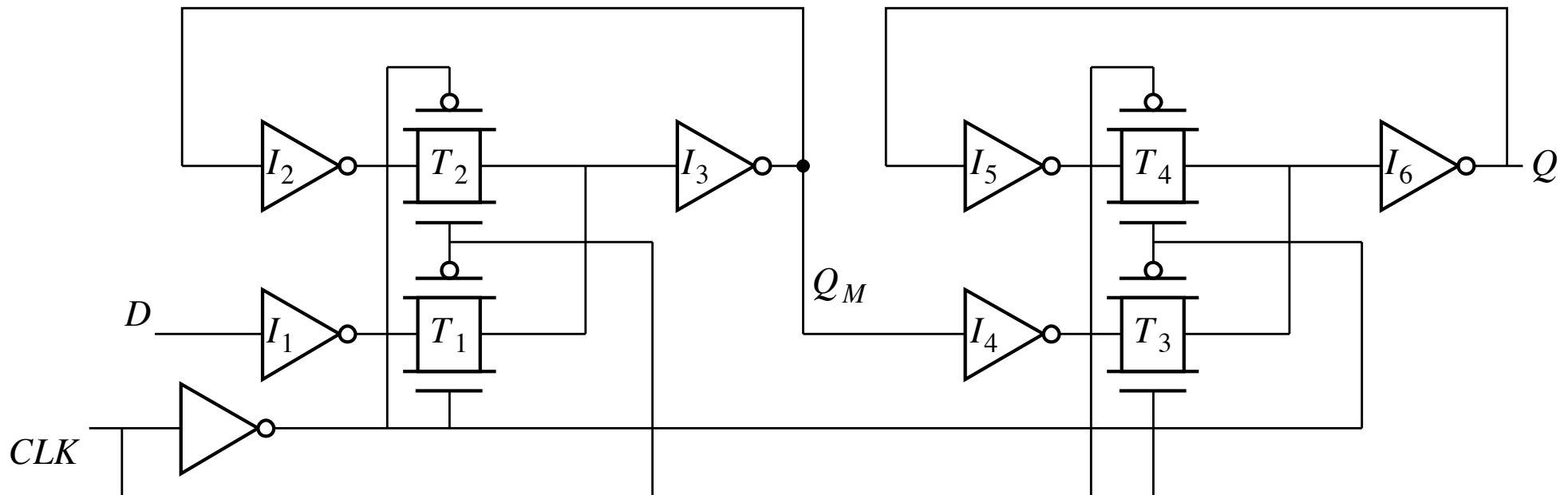


$t_{\text{setup}} =$

$t_{\text{pcq}} =$

$t_{\text{hold}} \geq$

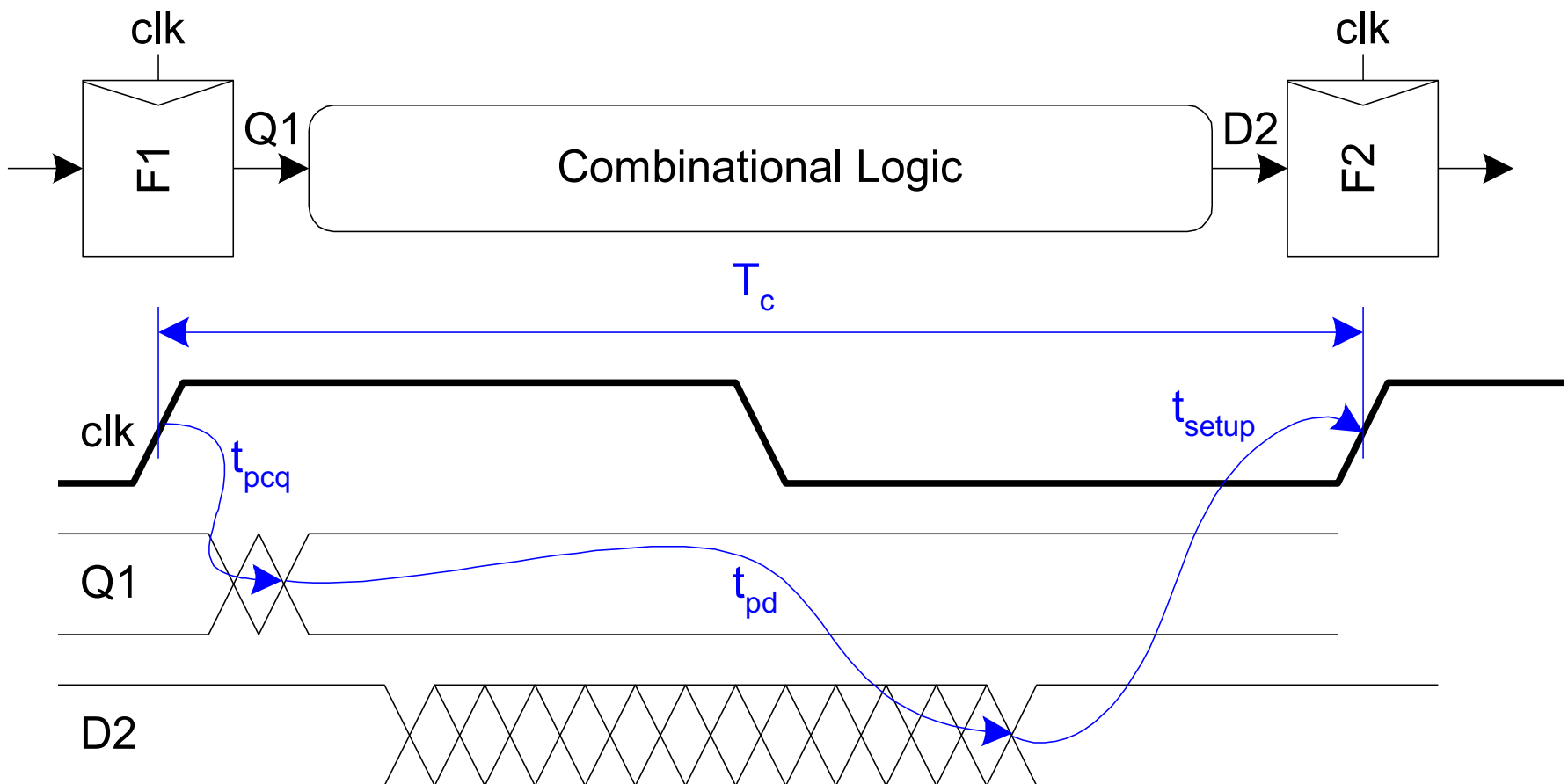
# Max-Delay: Flip-Flops

$$T_c \geq t_{pd} + \underbrace{(t_{setup} + t_{pcq})}_{\text{sequencing overhead}}$$




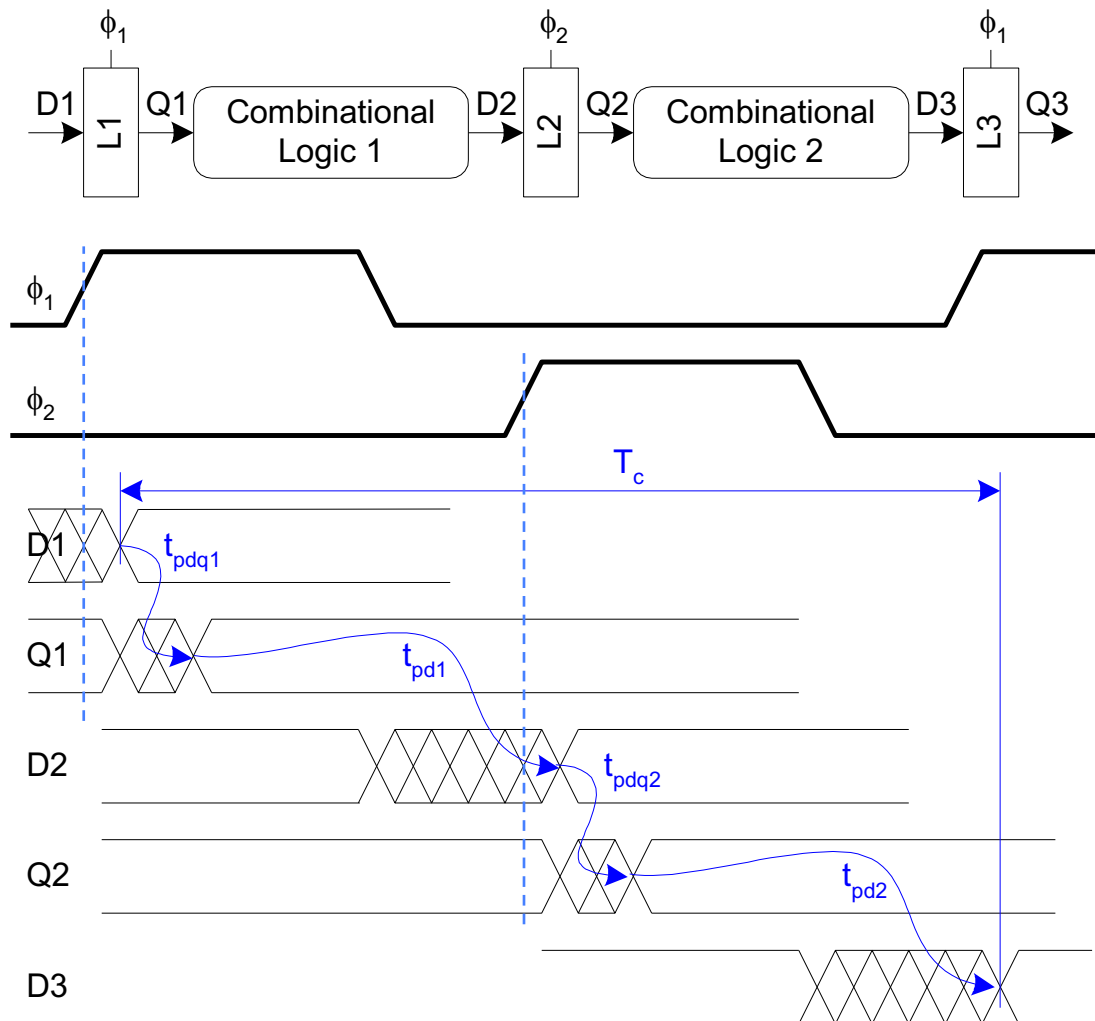
# Max Delay: 2-Phase Latches

$$T_c \geq t_{pd1} + t_{pd2} + \underbrace{t_{pdq1} + t_{pdq2}}_{\text{sequencing overhead}}$$



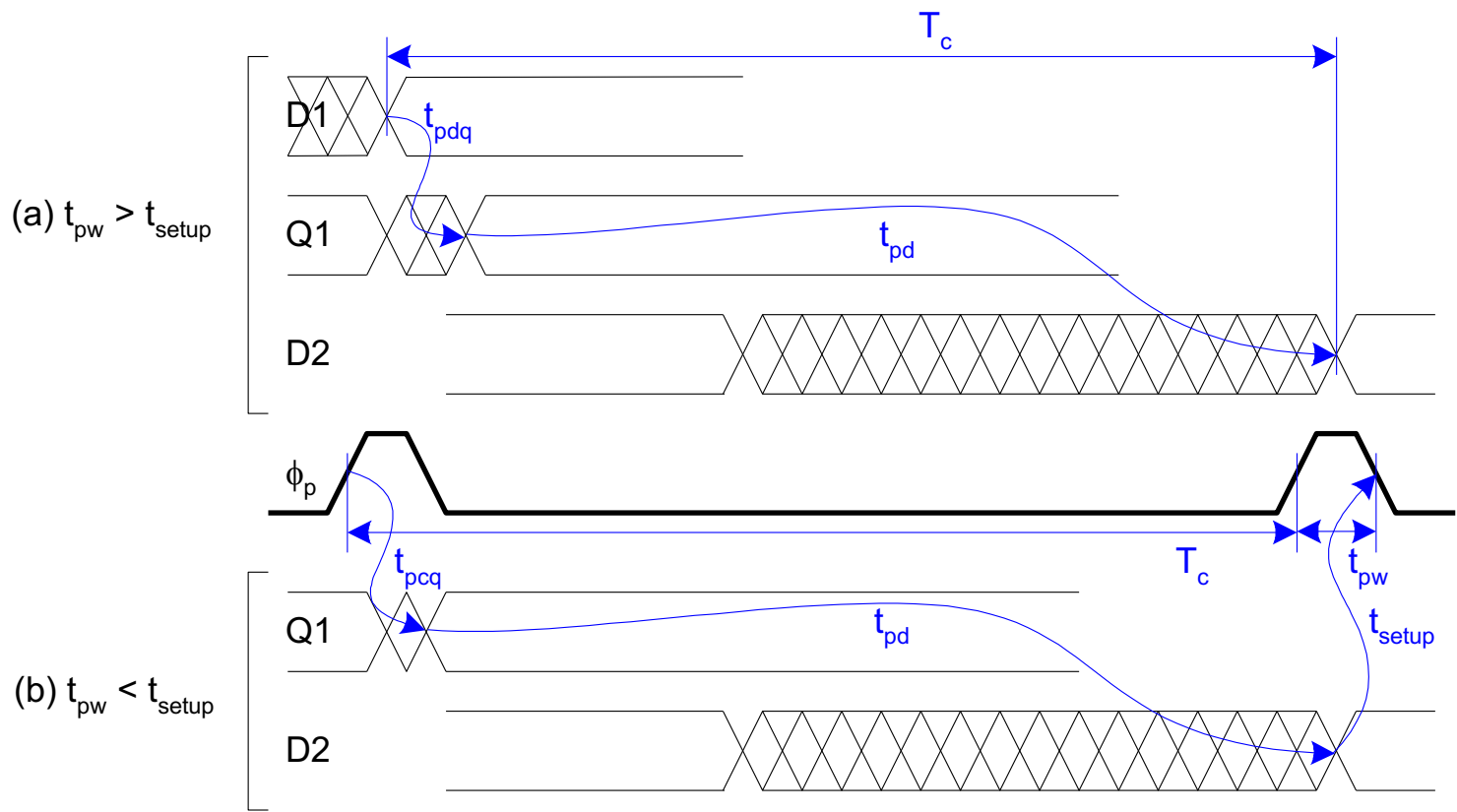 
# Max Delay: Pulsed Latches


$$t_{pd} + \underbrace{\max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw})}_{\text{sequencing overhead}} \leq T_c$$



# Min-Delay: Flip-Flops

 

 
$$t_{cd} \geq t_{\text{hold}} - t_{ccq}$$


 
# Min-Delay: 2-Phase Latches


$$t_{cd1}, t_{cd2} \geq t_{hold} - t_{ccq} - t_{nonoverlap}$$




Hold time reduced by non-overlap

Paradox: hold applies twice each cycle, vs. only once for flops.


But a flop is made of two latches!

 


# Min-Delay: Pulsed Latches

 
 
$$t_{cd} \geq t_{\text{hold}} - t_{ccq} + t_{pw}$$



Hold time increased by pulse width

 




# Time Borrowing

---

- **In a flop-based system:**
  - Data launches on one rising edge
  - Must setup before next rising edge
  - If it arrives late, system fails
  - If it arrives early, time is wasted
  - Flops have hard edges
  
- **In a latch-based system**
  - Data can pass through latch while transparent
  - Long cycle of logic can borrow time into next
  - As long as each loop completes in one cycle


# Time Borrowing Example

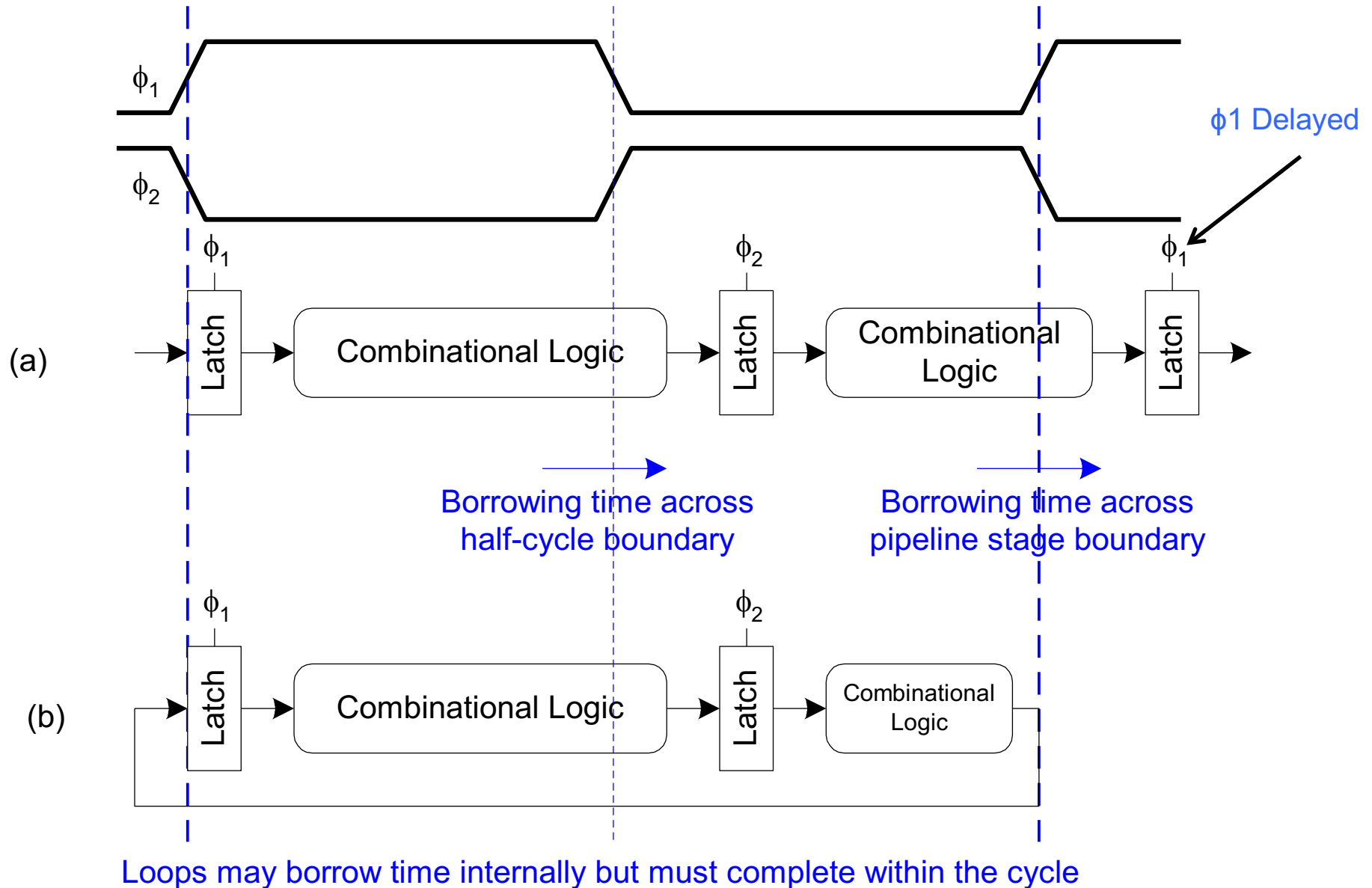

# How Much Borrowing?


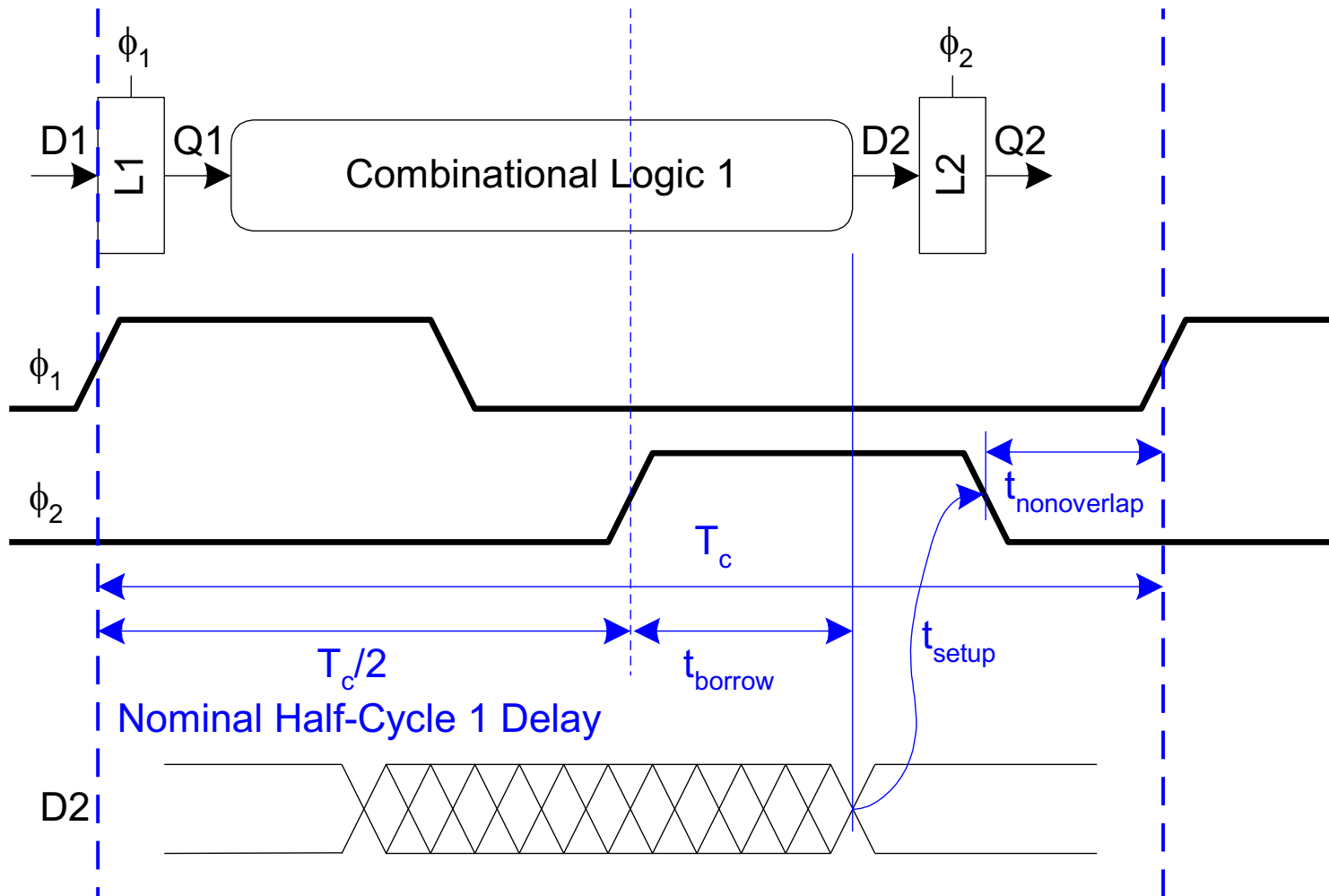
## 2-Phase Latches

$$t_{\text{borrow}} \leq \frac{T_c}{2} - (t_{\text{setup}} + t_{\text{nonoverlap}})$$



  
# Clock Skew

- We have assumed zero clock skew
- Clocks really have uncertainty in arrival time
  - Decreases maximum propagation delay
  - Increases minimum contamination delay
  - Decreases time borrowing



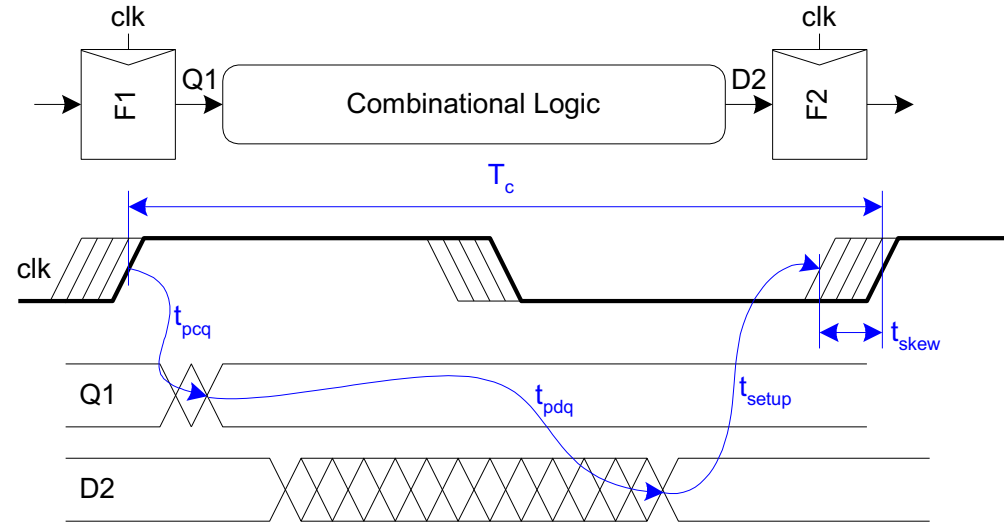
# Clock Skew: Flip-Flops

$$T_c \geq t_{pd} + \underbrace{(t_{pcq} + t_{setup} + t_{skew})}_{\text{sequencing overhead}}$$


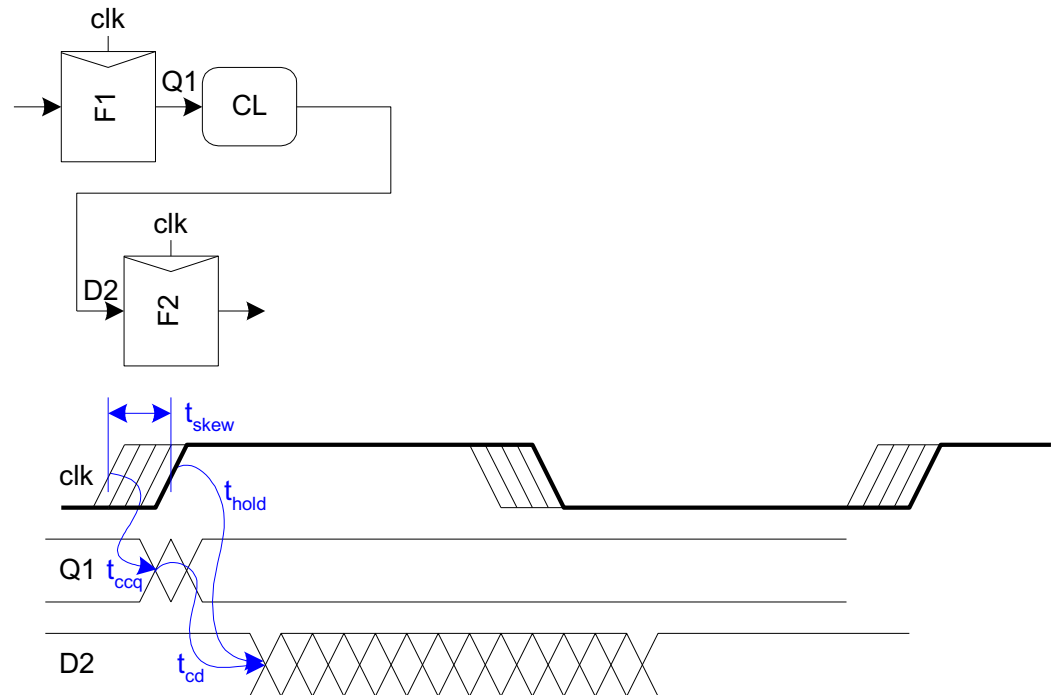
$$t_{cd} \geq t_{hold} - t_{ccq} + t_{skew}$$




# Clock Skew: Latches

## 2-Phase Latches

$$t_{pd} \leq T_c - \underbrace{(2t_{pdq})}_{\text{sequencing overhead}}$$

$$t_{cd1}, t_{cd2} \geq t_{hold} - t_{ccq} - t_{nonoverlap} + t_{skew}$$
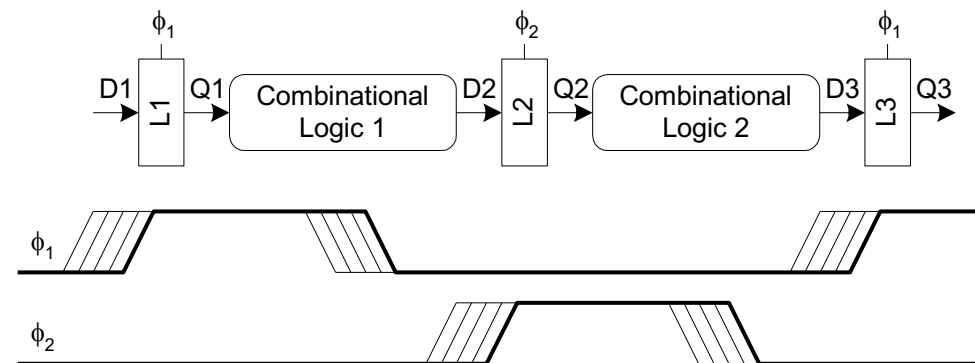
$$t_{borrow} \leq T_c/2 - (t_{setup} + t_{nonoverlap} + t_{skew})$$



## Pulsed Latches

$$t_{pd} \leq T_c - \underbrace{\max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw} + t_{skew})}_{\text{sequencing overhead}}$$

$$t_{cd} \geq t_{hold} + t_{pw} - t_{ccq} + t_{skew}$$



$$t_{borrow} \leq T_{pw} - (t_{setup} + t_{skew})$$

# Clocking realities

---

- **If setup times are violated, reduce clock speed**
- **Useful clock skew can be your friend**
- **Jitter is NEVER your friend**
- **Pulse latches do not scale well from generation to generation**
  - Use them if you want lot's of debugging experience 😊
- **Metastability is very real (and deadly)**
- **Lastly, if hold times are violated, chip fails at any speed and PVT**
  - You have a “brick” for a chip
  - You may be out of business if you are a startup

# Metastability

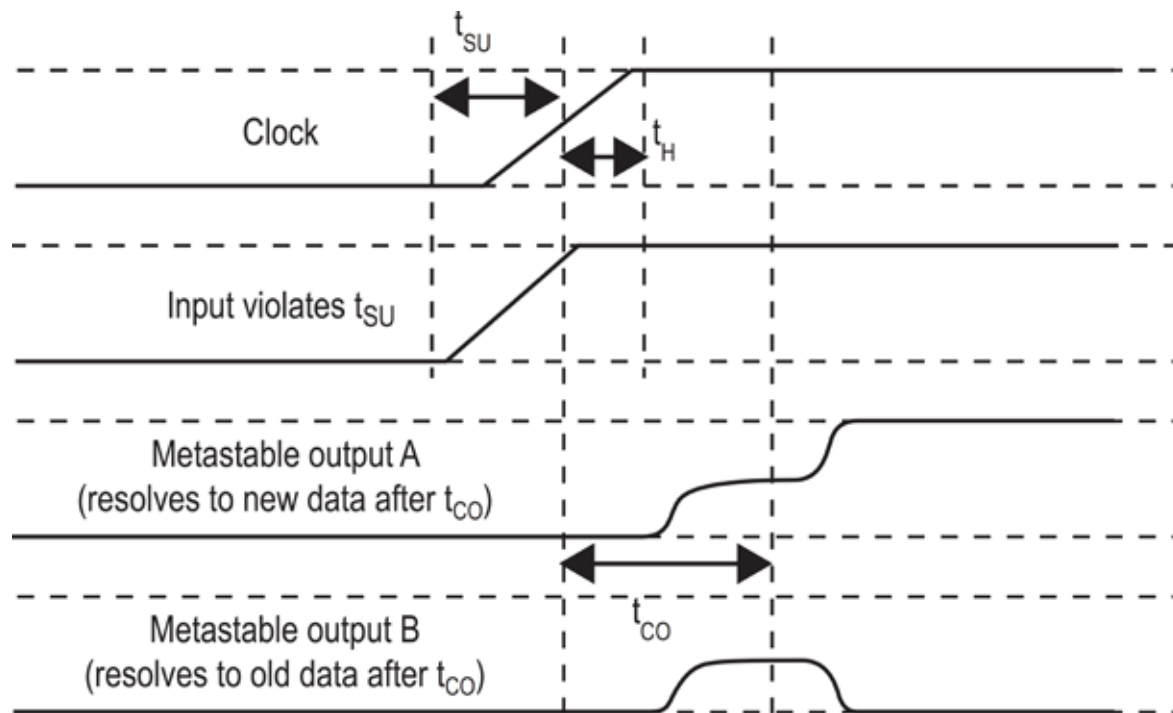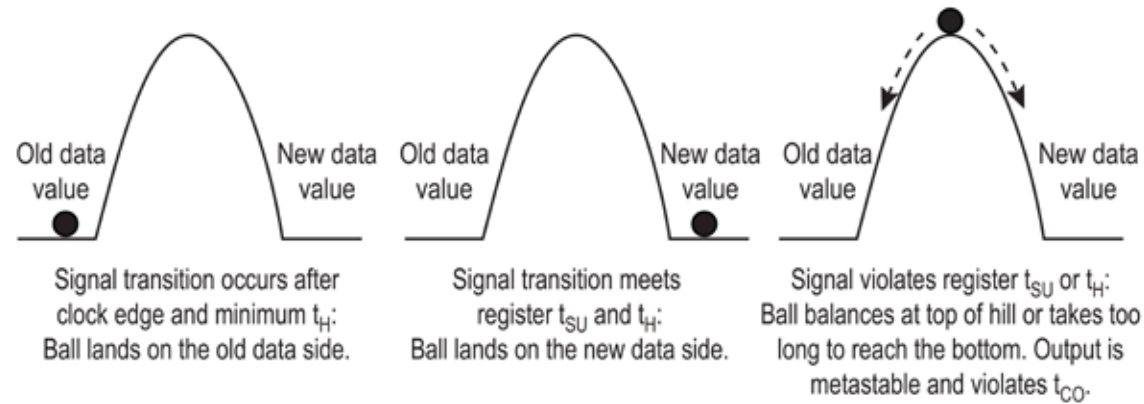

Courtesy Altera




# Metastability - MTBF

- The  $C_1$  and  $C_2$  constants depend on the device process and operating conditions. Determined empirically.
- $f_{CLK}$  is the clock frequency of the clock domain receiving the asynchronous signal
- $f_{DATA}$  is the toggling frequency of the asynchronous input data signal. Faster clock frequencies and faster-toggling data reduce (or worsen) the MTBF.
- The  $t_{MET}$  parameter is the available metastability settling time, or the timing slack available beyond the register's  $t_{CO}$ , for a potentially metastable signal to resolve to a known value.

$$MTBF = \frac{e^{t_{MET}/C_2}}{C_1 \cdot f_{CLK} \cdot f_{DATA}}$$

# MTBF vs. $T_{MET}$

 

$$C_2 = \frac{\Delta \ln(MTBF)}{\Delta t_{MET}}$$

$$C_1 = \frac{e^{(C_2 \times t_{MET})}}{MTBF \times f_{CLOCK} \times f_{DATA}}$$

Courtesy Altera

# MTBF: Alternate definition

To avoid synchronizer failure wait long enough before using a synchronizer's output. Where "long enough", is the mean time between synchronizer failures and is several orders of magnitude longer than the designer's expected length of employment!

*John Wakerly*




# Preventing Metastability

- The  $t_{MET}$  for a synchronization chain is the sum of the output timing slacks for each register in the chain.


$$MTBF = \frac{e^{t_{MET}/C_2}}{C_1 \cdot f_{CLK} \cdot f_{DATA}}$$
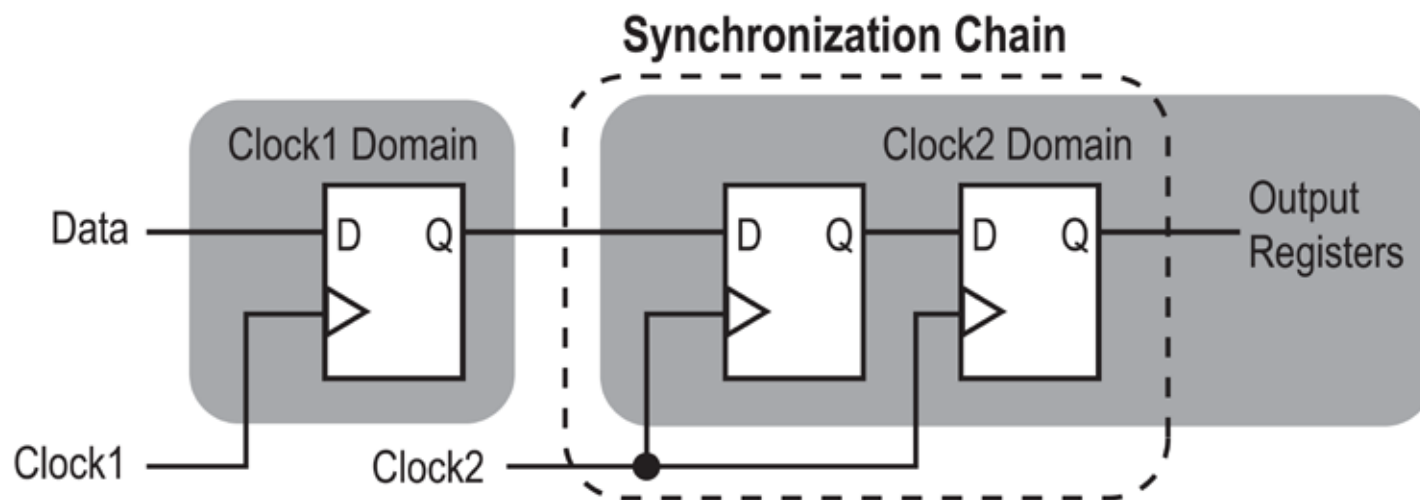
$$failure\_rate_{design} = \frac{1}{MTBF_{design}} = \sum_{i=1}^{number\ of\ chains} \frac{1}{MTBF_i}$$




Courtesy Altera


# Simulating Metastability

 


# Simulating Metastability (cont.)

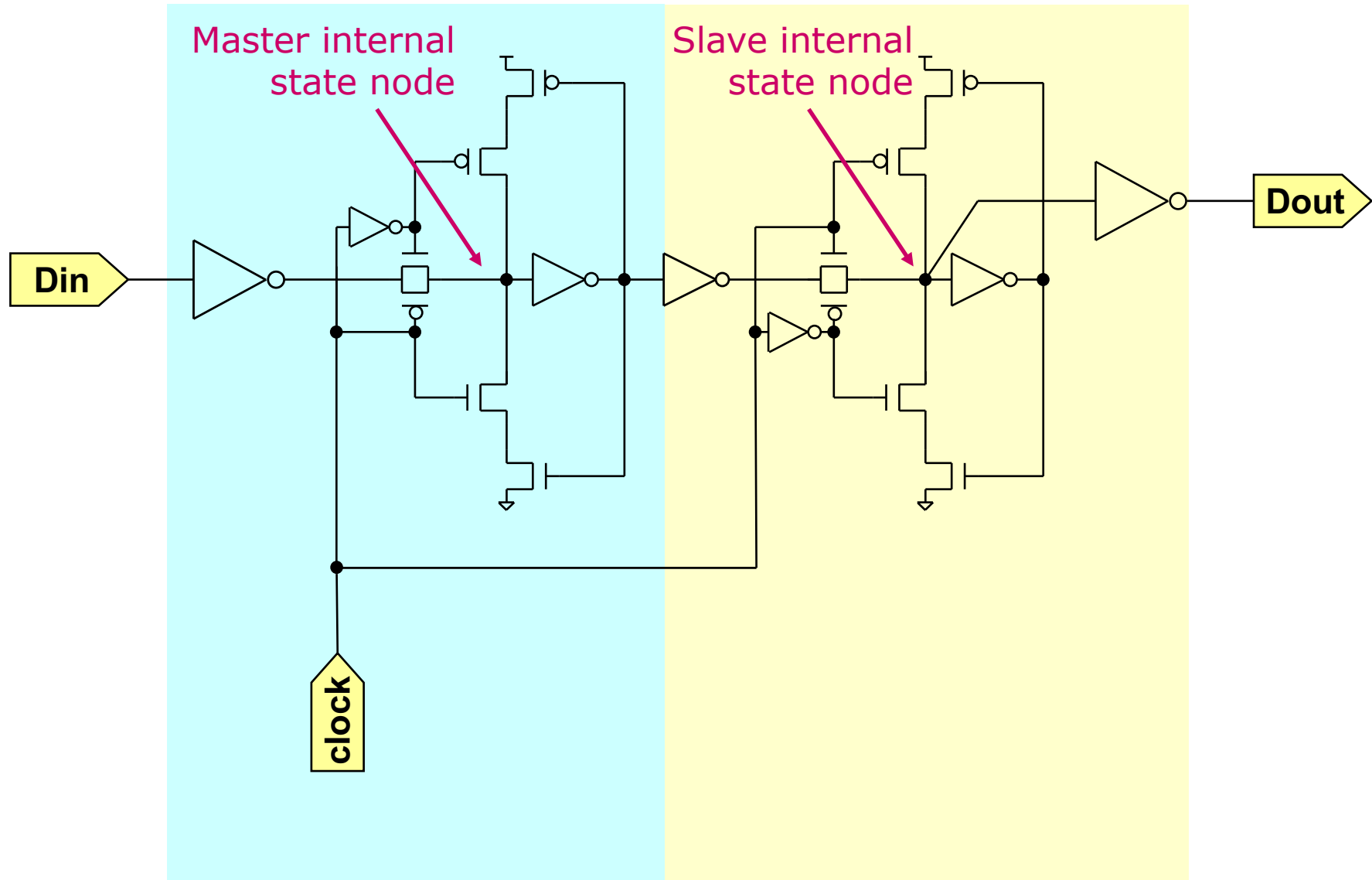

# Functional Pass/Failure vs. Tsu and Th

 


Input setup time

 

Condition FLOP 1st


Input hold time
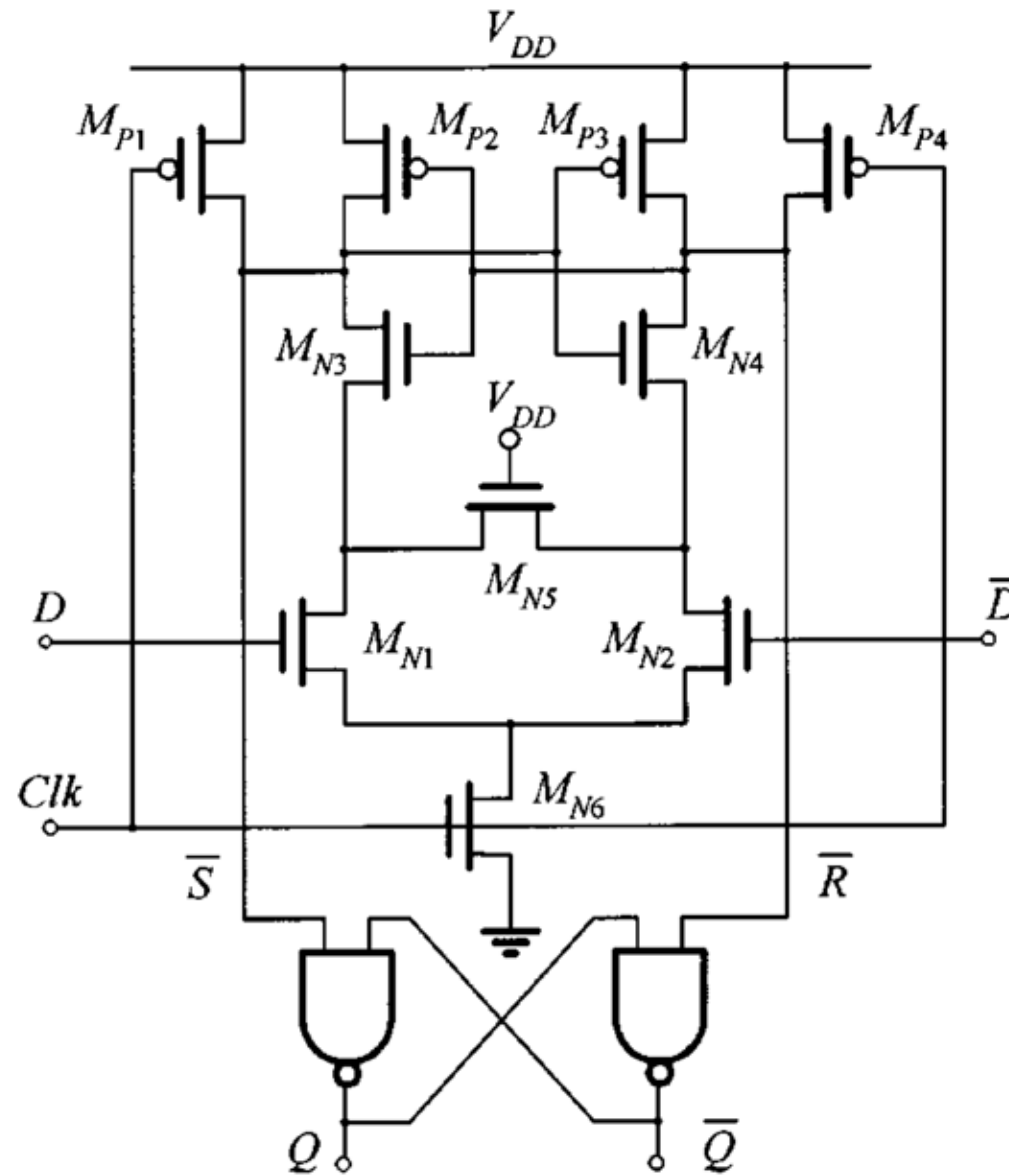
# High Speed Flip-Flop for Synchronization





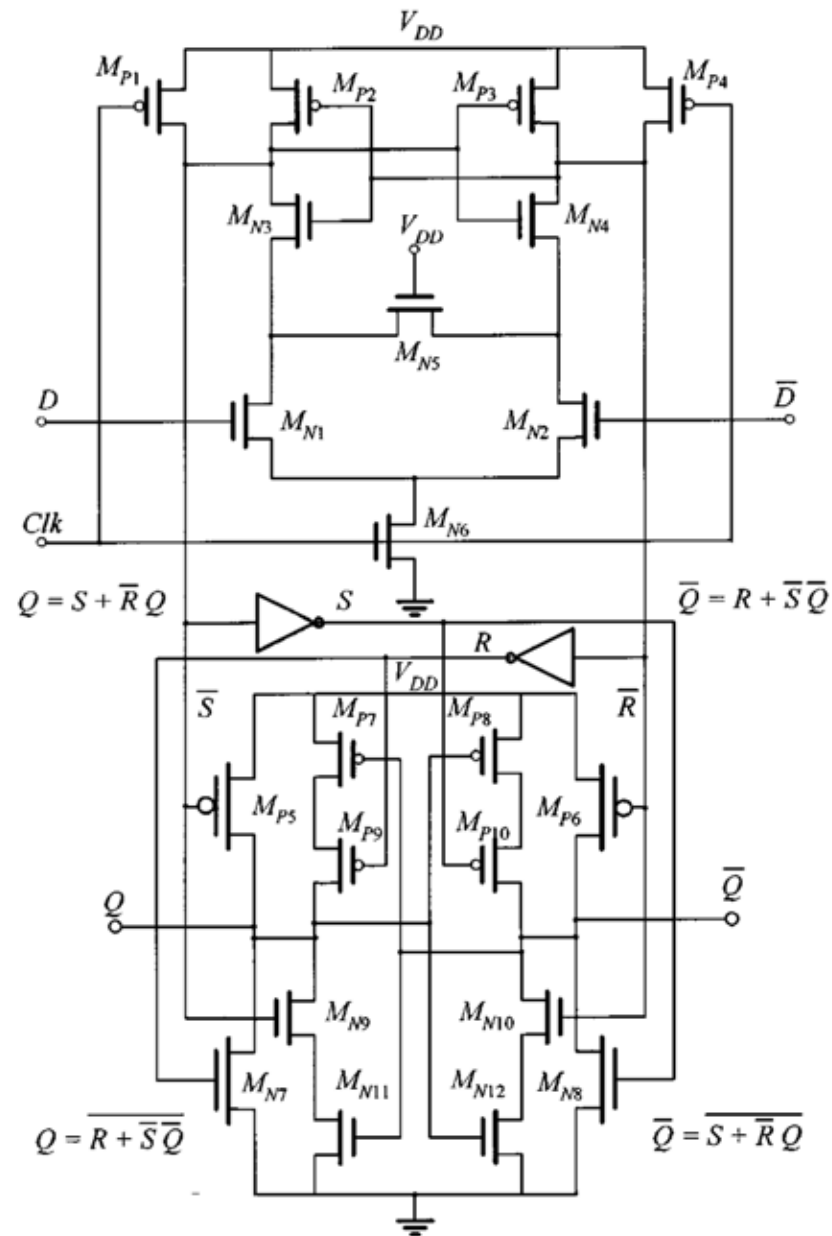
# High Speed Flip-Flop for Synchronization (cont.)




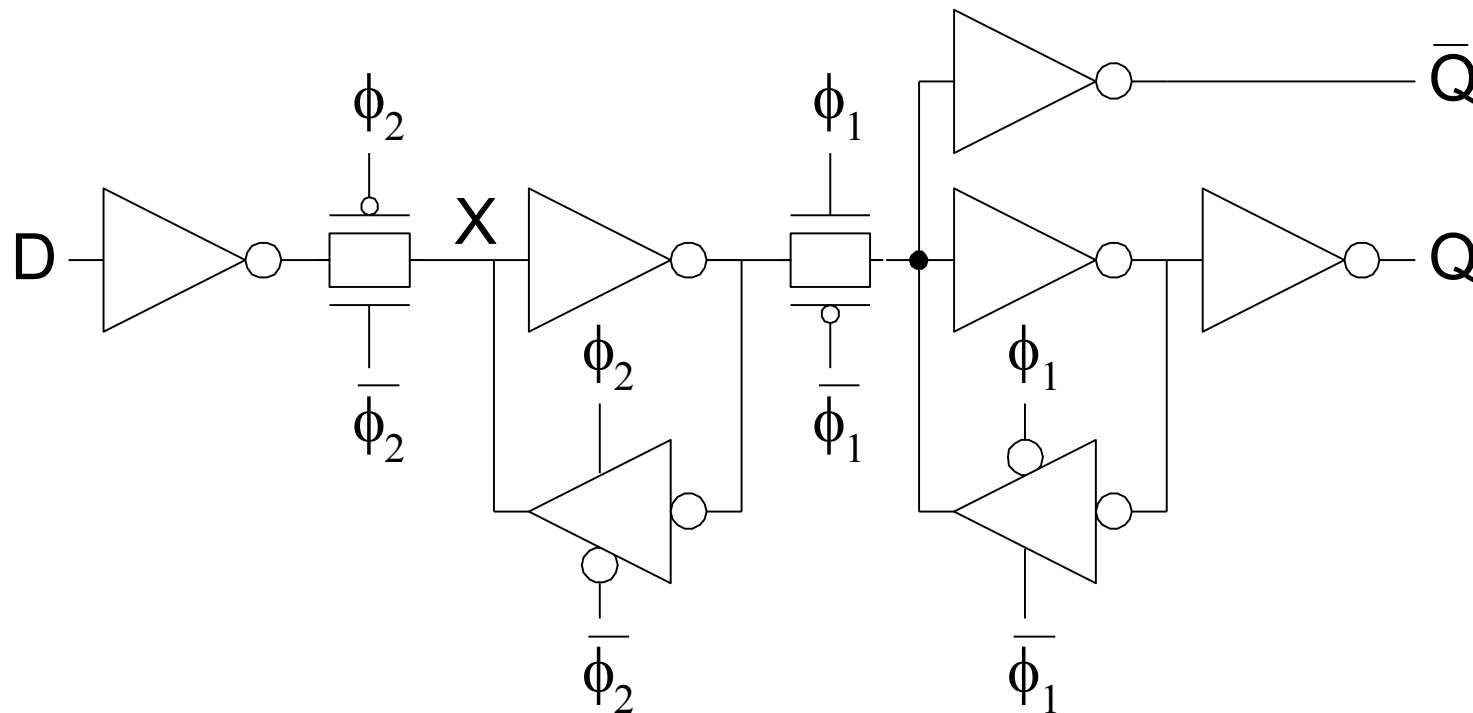
# Safe Flip-Flop

- **Use flip-flop with non-overlapping clocks**
  - Very slow – non-overlap adds to setup time
  - But no hold times
- **In industry, use a better timing analyzer**
  - Add buffers to slow signals if hold time is at risk




# C<sup>2</sup>MOS FLOPS

 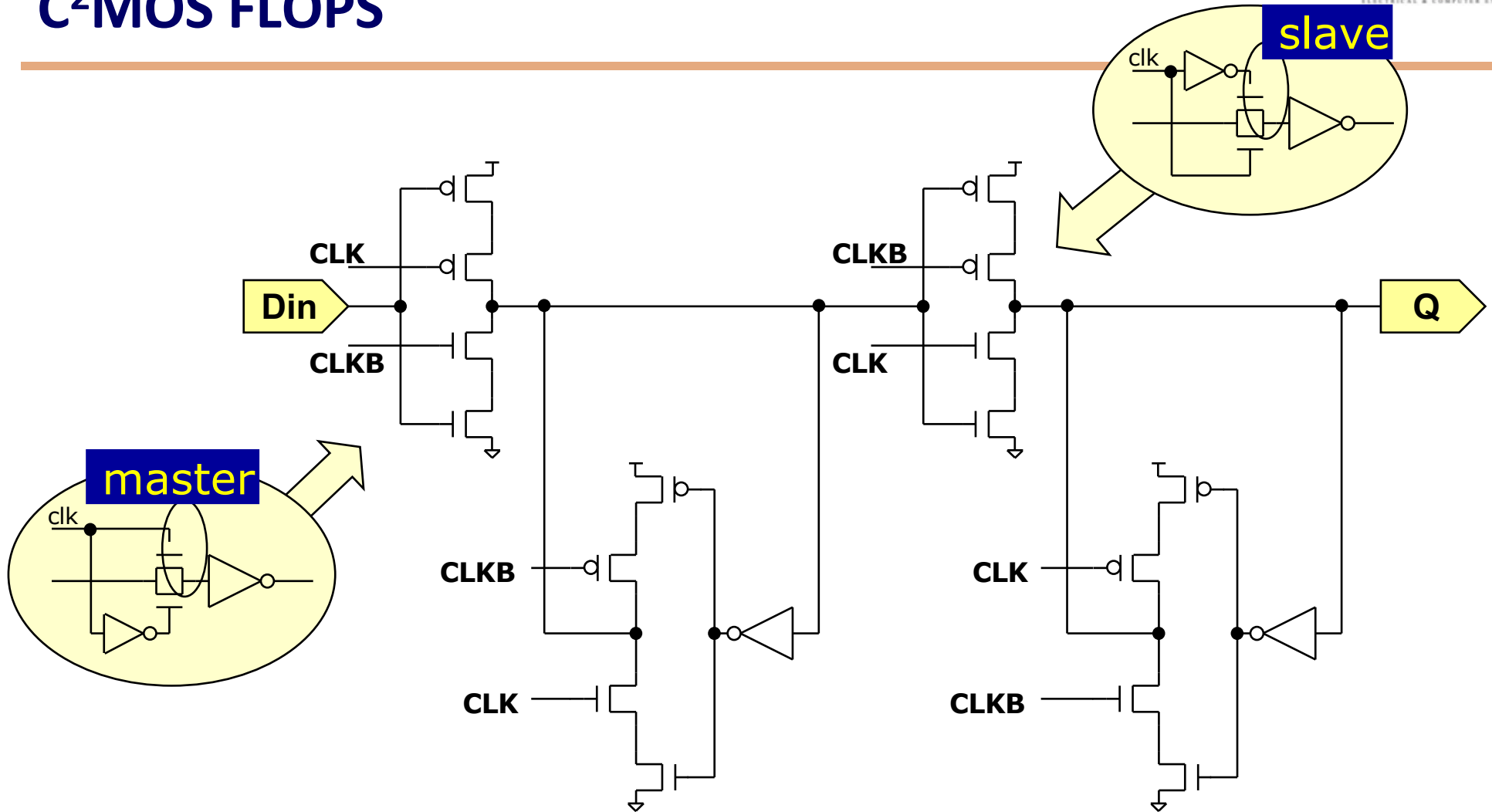


**Clock slope becomes critical**  
**Low power feedback**  
**Poor driving capability**

# Hybrid Latch Flip-Flop (HLFF)

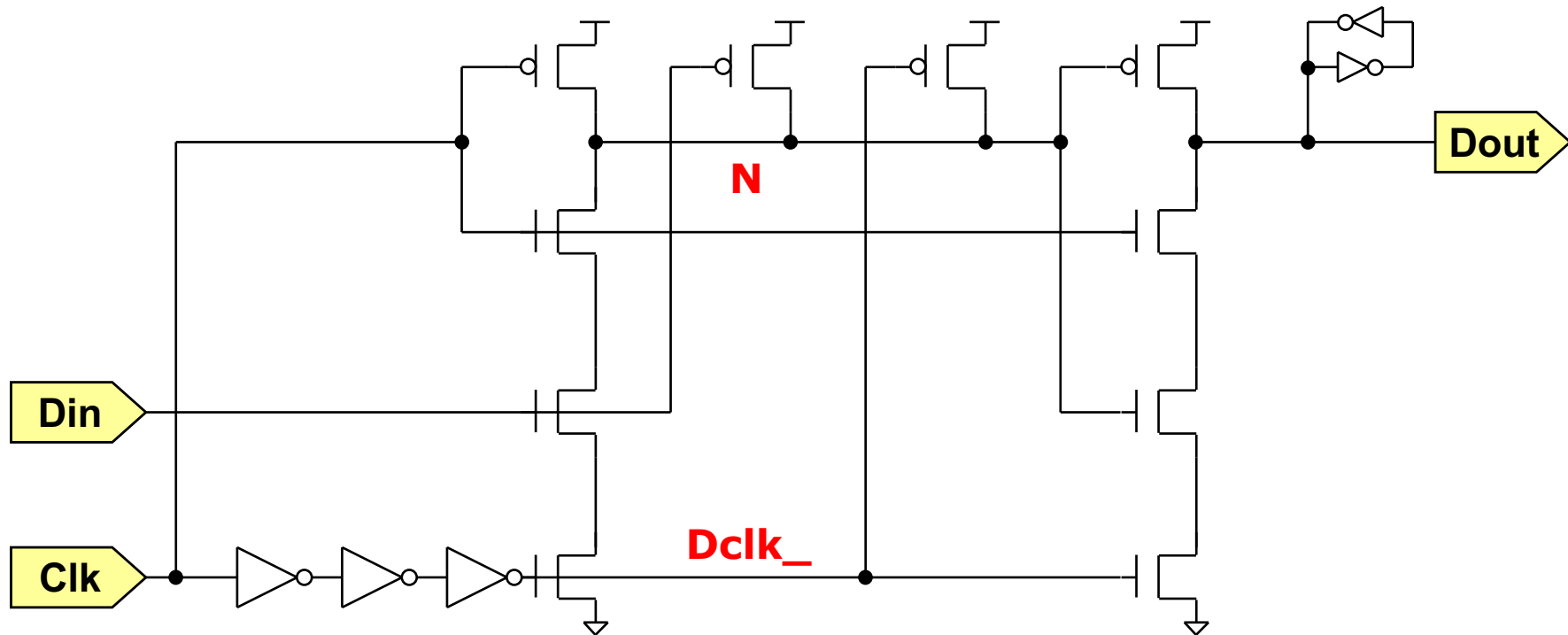


(AMD K-6, Partovi, ISSCC 1996)


# Hybrid Latch Flip-Flop Timing

 

# Pulse Latch

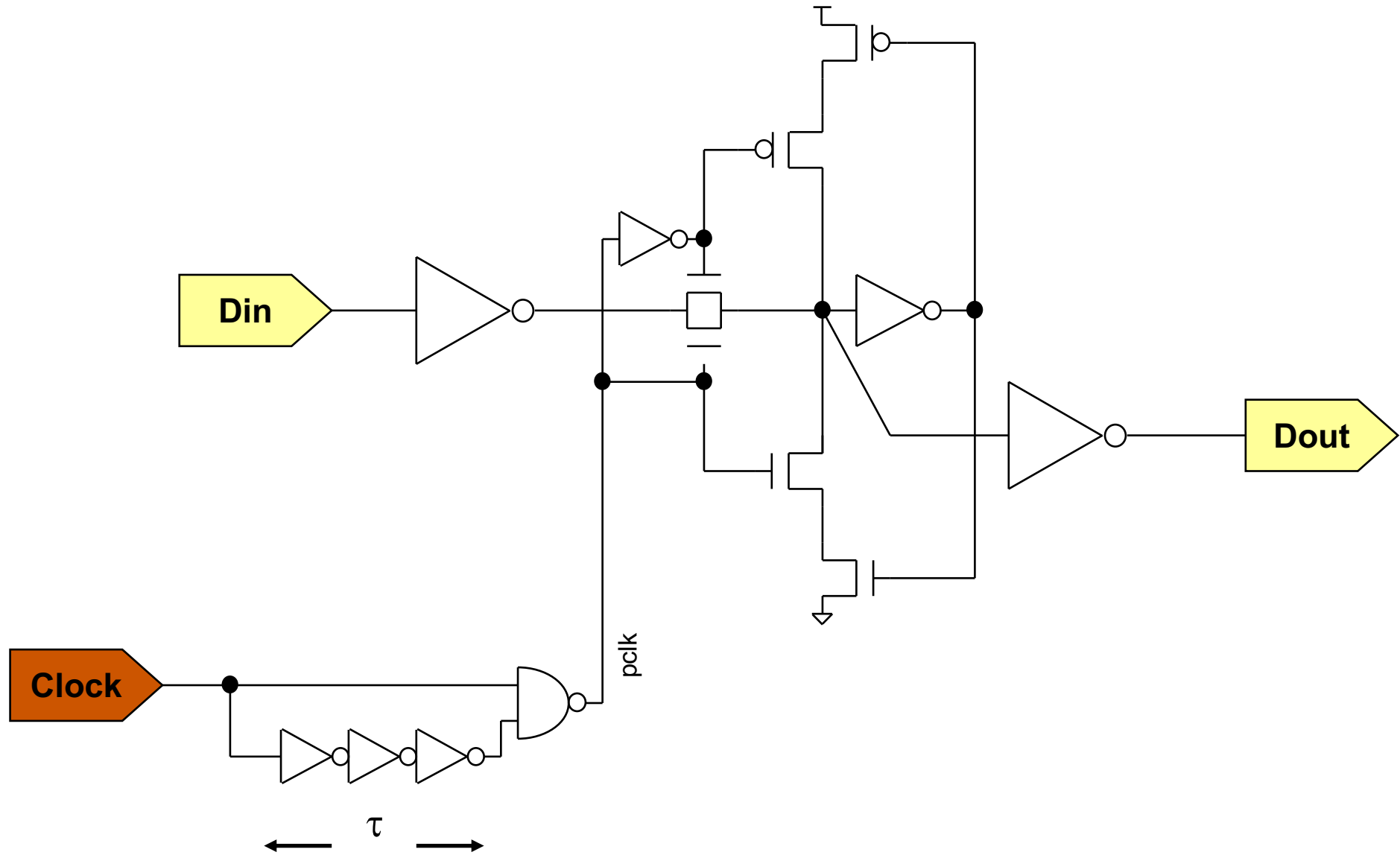


# Pulse Latch Waveforms

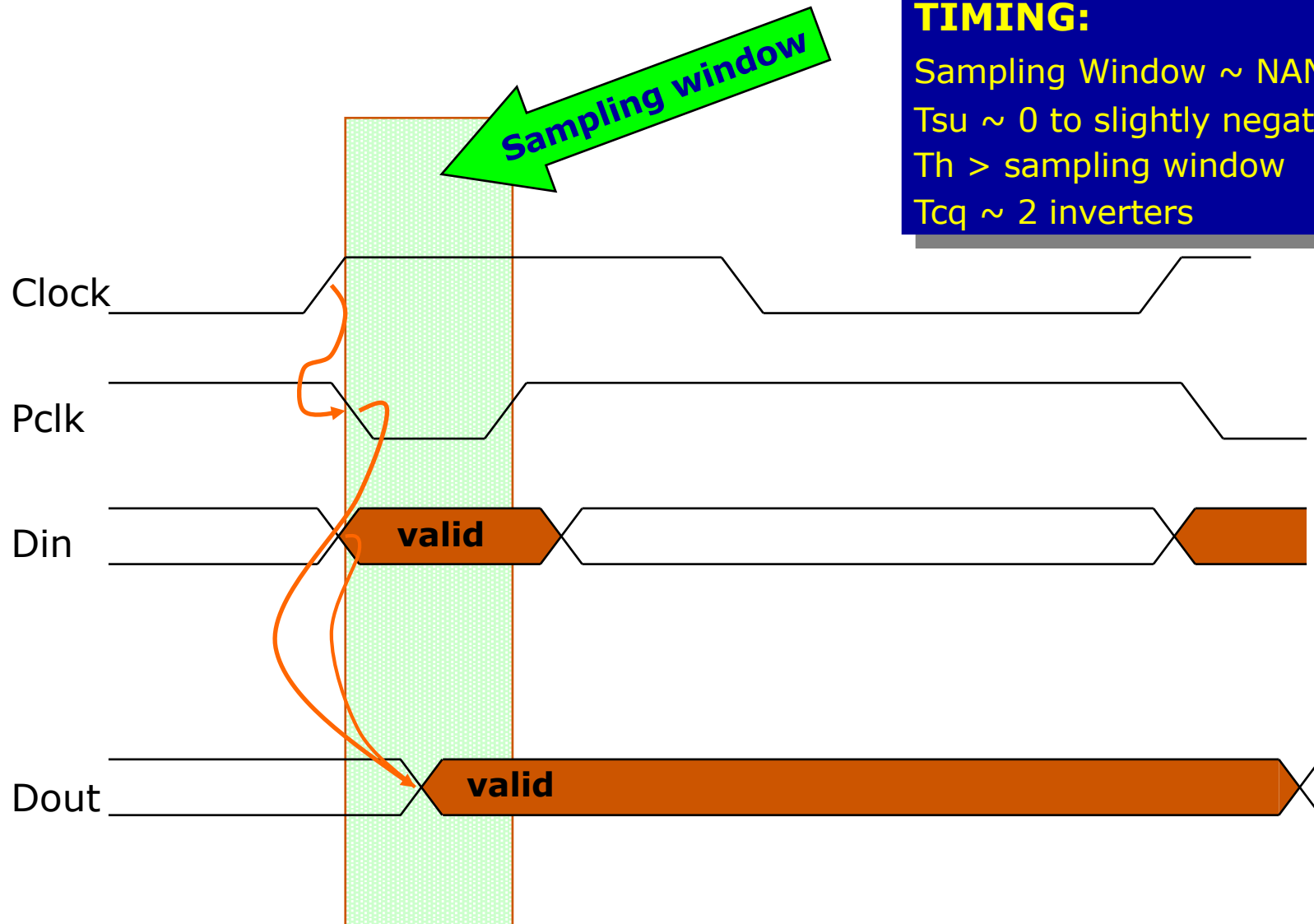

**TIMING:**  
 Sampling Window  $\sim$  NAND +  $\tau$   
 $T_{su} \sim 0$  to slightly negative  
 $T_h >$  sampling window  
 $T_{cq} \sim 2$  inverters

# Merged Function inverting FLOP

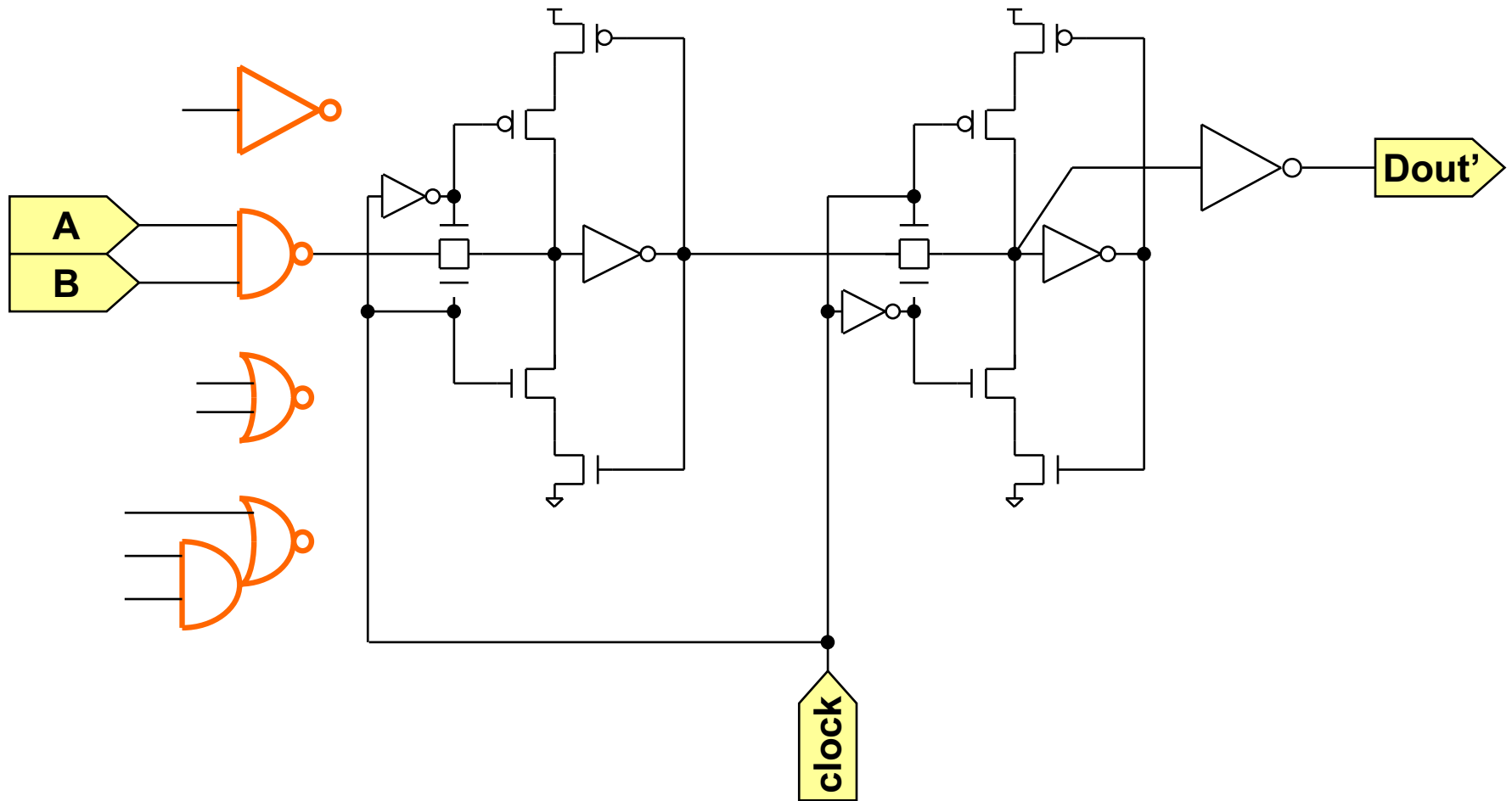



# Flip-Flop Summary

- **Flip-Flops:**
  - Very easy to use, supported by all tools
- **2-Phase Transparent Latches:**
  - Lots of skew tolerance and time borrowing
  - Supported by most tools. Can cause timing loops.
- **Pulsed Latches:**
  - Fast, some skew tol. & borrow, hold time risk

|                                     | Sequencing overhead<br>( $T_c - t_{pd}$ )                     | Minimum logic delay<br>$t_{cd}$  | Time borrowing<br>$t_{borrow}$                            |
|-------------------------------------|---|--|---|
| Flip-Flops                          | $t_{pcq} + t_{setup} + t_{skew}$                              | $t_{hold} - t_{ccq} + t_{skew}$  | 0   |
| Two-Phase<br>Transparent<br>Latches | $2t_{pdq}$  | $t_{hold} - t_{ccq} - t_{nonoverlap} + t_{skew}$<br>in each half-cycle | $\frac{T_c}{2} - (t_{setup} + t_{nonoverlap} + t_{skew})$ |
| Pulsed<br>Latches                   | $\max(t_{pdq}, t_{pcq} + t_{setup} - t_{p\tau w} + t_{skew})$ | $t_{hold} - t_{ccq} + t_{p\tau w} + t_{skew}$                          | $t_{p\tau w} - (t_{setup} + t_{skew})$                    |

# Backup

# Dynamic Latch Design


## ■ Pass Transistor Latch

### ■ Pros

- Tiny
- Low clock load
 
### ■ Cons

- $V_t$  drop
- Non-restoring
- Back driving
- Output noise sensitivity
- Dynamic
- Diffusion input
- Requires capacitance on output to store state.



Used in the 1970s

# Dynamic Latch Design (cont.)

- **Transmission gate**
  - + No  $V_t$  drop
  - Requires inverted clock
  
- **Inverting buffer**
  - + Restoring
  - + No back driving
  - + Fixes either
    - **Output noise sensitivity**
    - **Or diffusion input**
  - **Inverted output**

