

Lecture 11: Adder Design

Mark McDermott


**Electrical and Computer Engineering
The University of Texas at Austin**

Single-Bit Addition

Half Adder

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

 


A	B	C _{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Full Adder

$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$

 


A	B	C	G	P	K	C _{out}	S
0	0	0	0	0	1	0	0
0	0	1	0	0	1	0	1
0	1	0	0	1	0	0	1
0	1	1	0	1	0	1	0
1	0	0	0	1	0	0	1
1	0	1	0	1	0	1	0
1	1	0	1	0	0	1	0
1	1	1	1	0	0	1	1

Full Adder Design I

- Brute force implementation from equations


$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$

 


Full Adder Design II

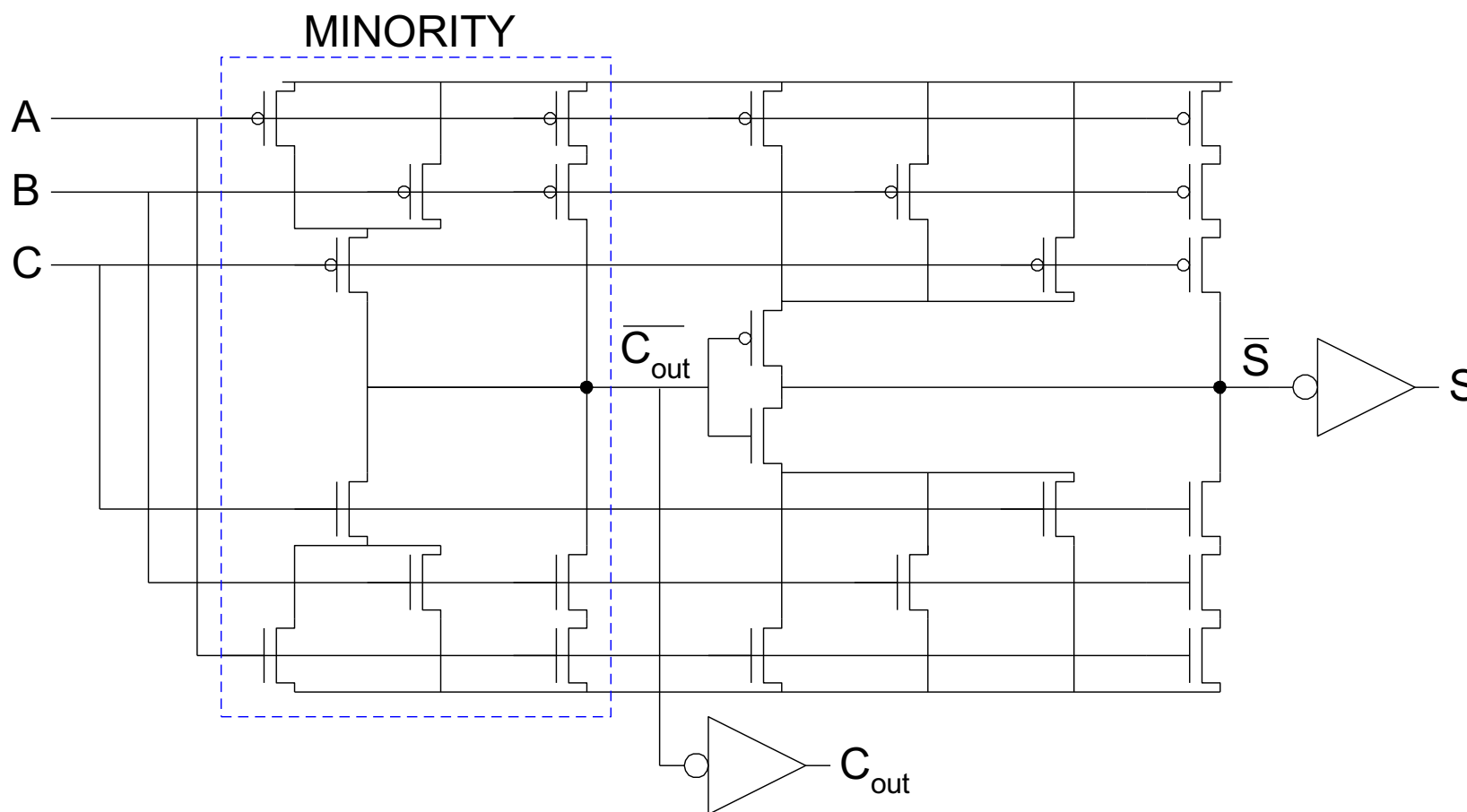- **Factor S in terms of Cout**
 - $S = ABC + (A + B + C)(\sim C_{out})$
- **Critical path is usually C to Cout in ripple adder**



Layout

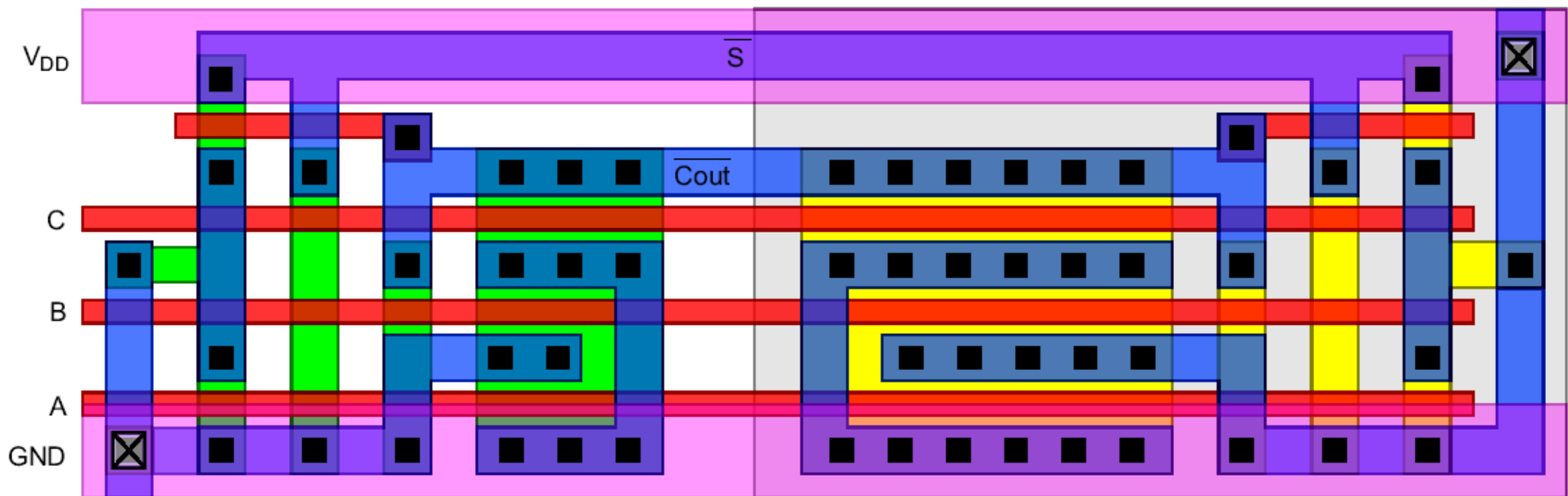
- **Clever layout circumvents usual line of diffusion**
 - Use wide transistors on critical path
 - Eliminate output inverters



Full Adder Design III


■ Complementary Pass Transistor Logic (CPL)

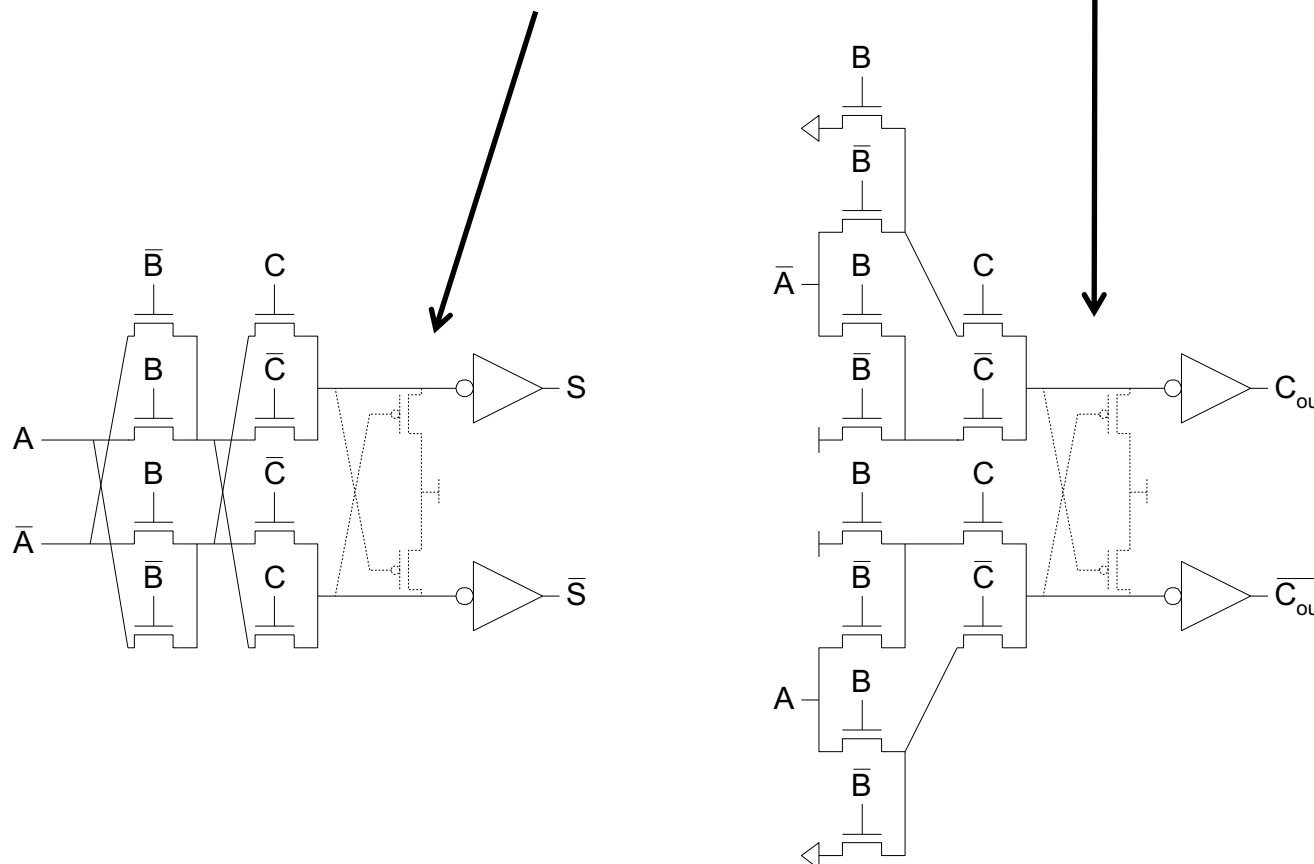- Slightly faster, but more area
- Requires true and complement signals
- There is some signal degradation through the pass transistors.
 - Cross coupled PMOS devices are used to restore logic levels.




Ripple Carry Adder

 - **Simplest design: cascade full adders**
 - Critical path goes from C_{in} to C_{out}
 - Design full adder to have fast carry delay



Use Inversions to speed up Carry Path



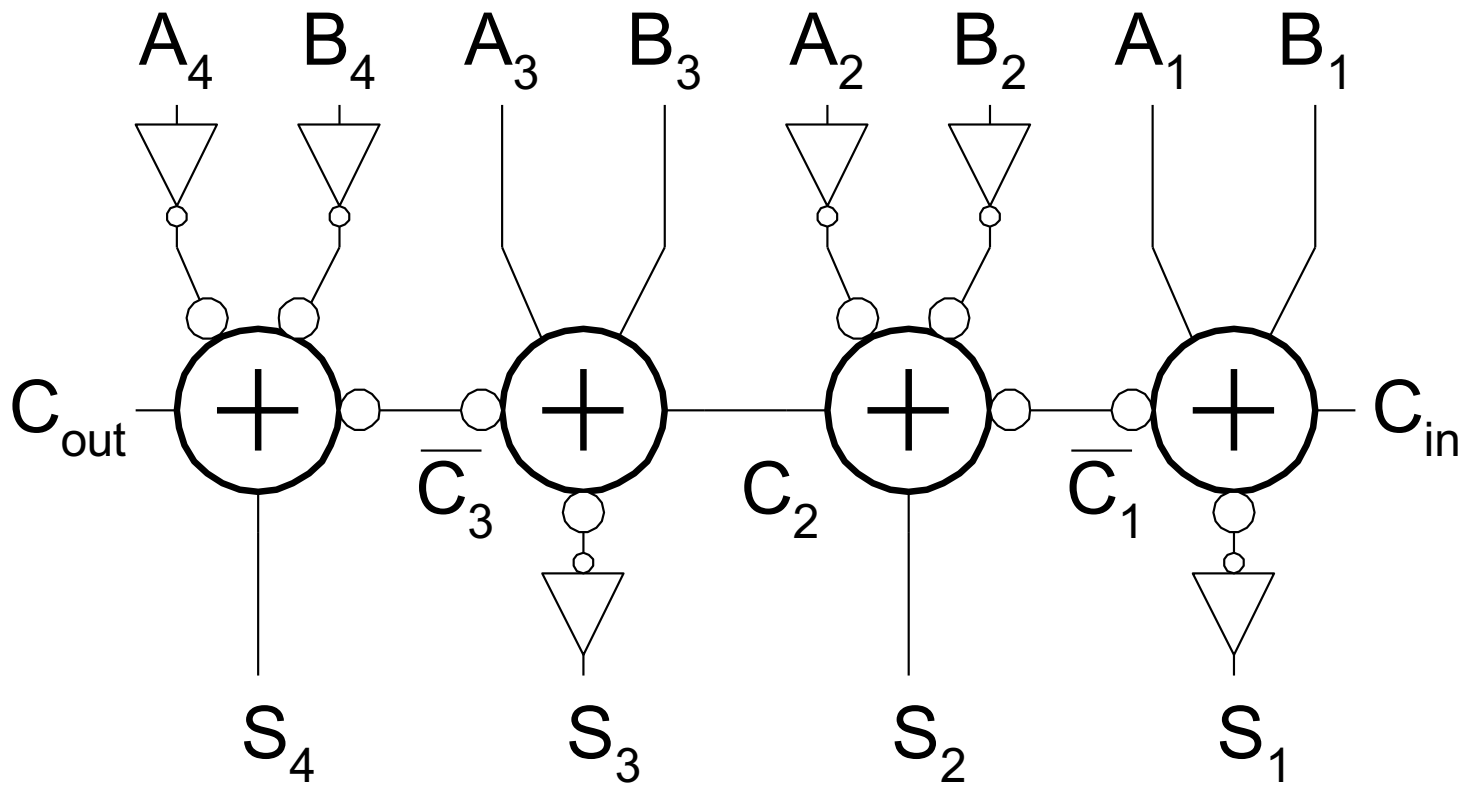
- **Critical path passes through majority gate**
 - Built from minority + inverter
 - Eliminate inverter and use inverting full adder



Carry Propagate Adders

- **N-bit adder called CPA**

   - Each sum bit depends on all previous carries
- How do we compute all these carries quickly?



Carry Propagate, Generate, Kill (PGK)

- For a full adder, define what happens to carries

Generate: $C_{out} = 1$ independent of C

$$G = A \bullet B$$

Propagate: $C_{out} = C$

$$P = A \oplus B$$

Kill: $C_{out} = 0$ independent of C

$$K = \sim A \bullet \sim B \text{ (i.e., } \sim K = A + B)$$

A	B	C	G	P	K	C_{out}	S
0	0	0	0	0	1	0	0
0	0	1	0	0	1	0	1
0	1	0	0	1	0	0	1
0	1	1	0	1	0	1	0
1	0	0	0	1	0	0	1
1	0	1	0	1	0	1	0
1	1	0	1	0	0	1	0
1	1	1	1	0	0	1	1

Propagate / Generate (PG)

- Equations often factored into P and G
- Propagate and generate for groups spanning $i:j$

$$G_{i:j} = G_{i:k} + P_{i:k} \cdot G_{k-1:j}$$

$$P_{i:j} = P_{i:k} \cdot P_{k-1:j}$$

- Base case


$$G_{i:i} \equiv G_i = A_i \cdot B_i$$

$$G_{0:0} \equiv G_0 = C_{in}$$

$$P_{i:i} \equiv P_i = A_i \oplus B_i$$


$$P_{0:0} \equiv P_0 = 0$$

- Sum: $S_i = P_i \oplus G_{i-1:0}$

 


Ripple Carry Revisited in PG Framework

$$G_{i:0} = G_i + P_i \cdot G_{i-1:0}$$

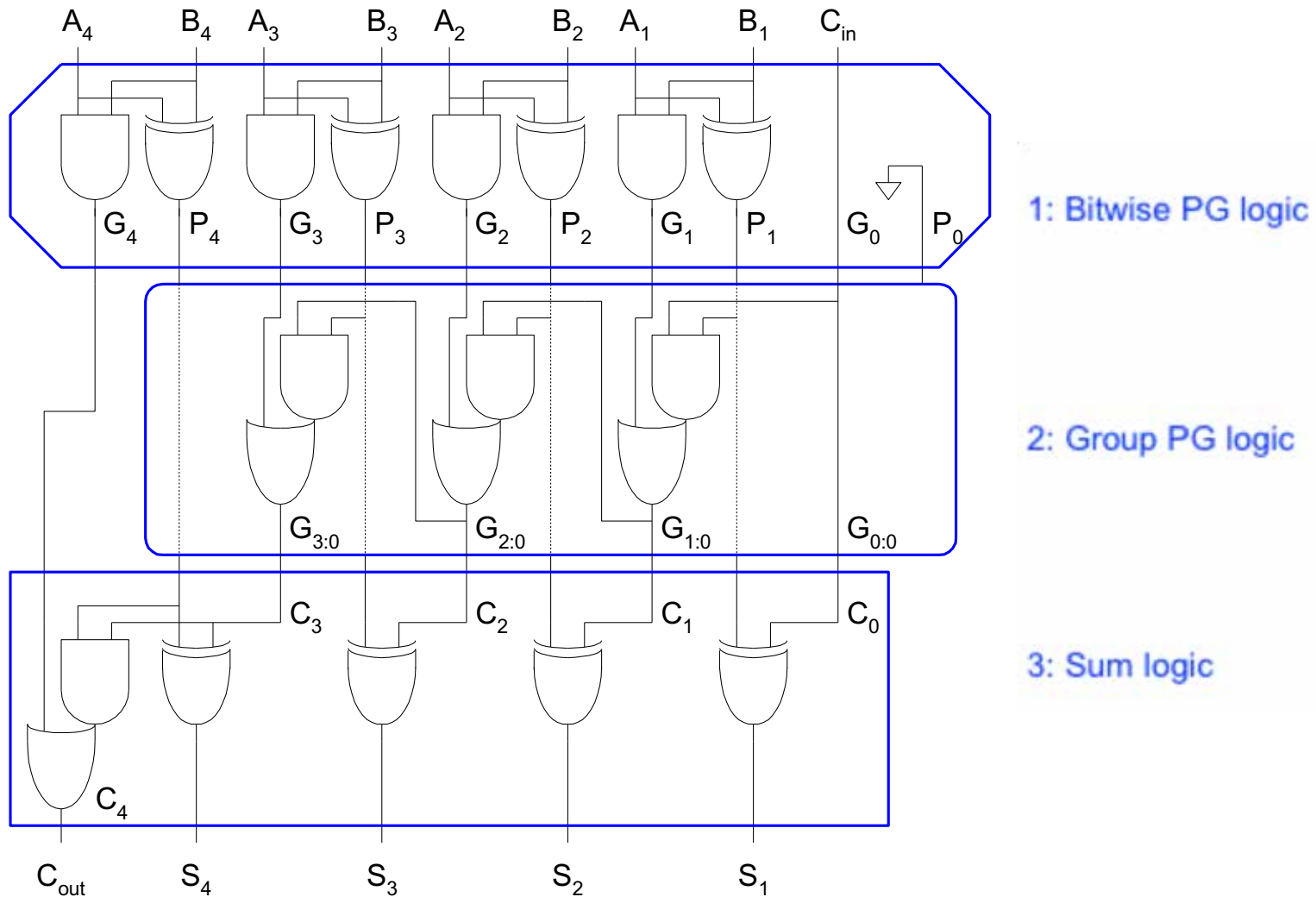


PG Diagram Notation





Black cell

 

Gray cell


 


Buffer

    


Ripple Carry PG Diagram
 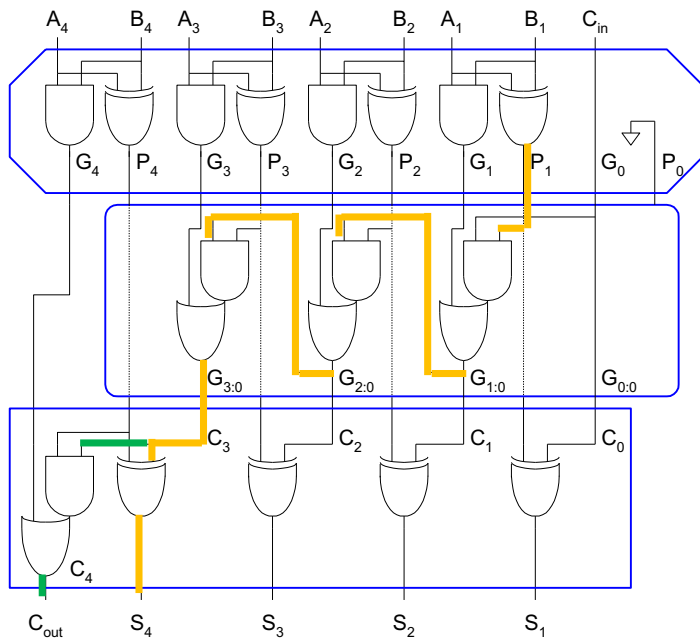
$$t_{\text{ripple}} = t_{pg} + (N - 1)t_{AO} + t_{\text{xor}}$$




Carry-Skip Adder

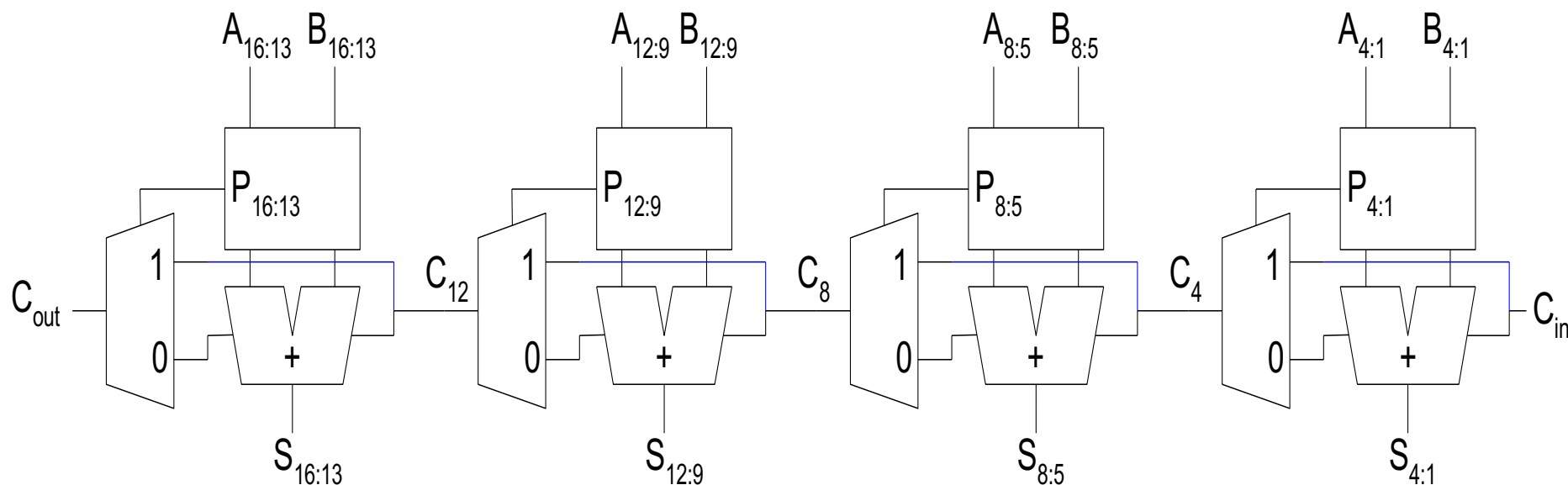- Ripple carry is slow through all N stages
- Carry-skip allows carry to skip over groups of n bits
 - Decision based on n-bit propagate signal




Manchester Carry-Skip Adder

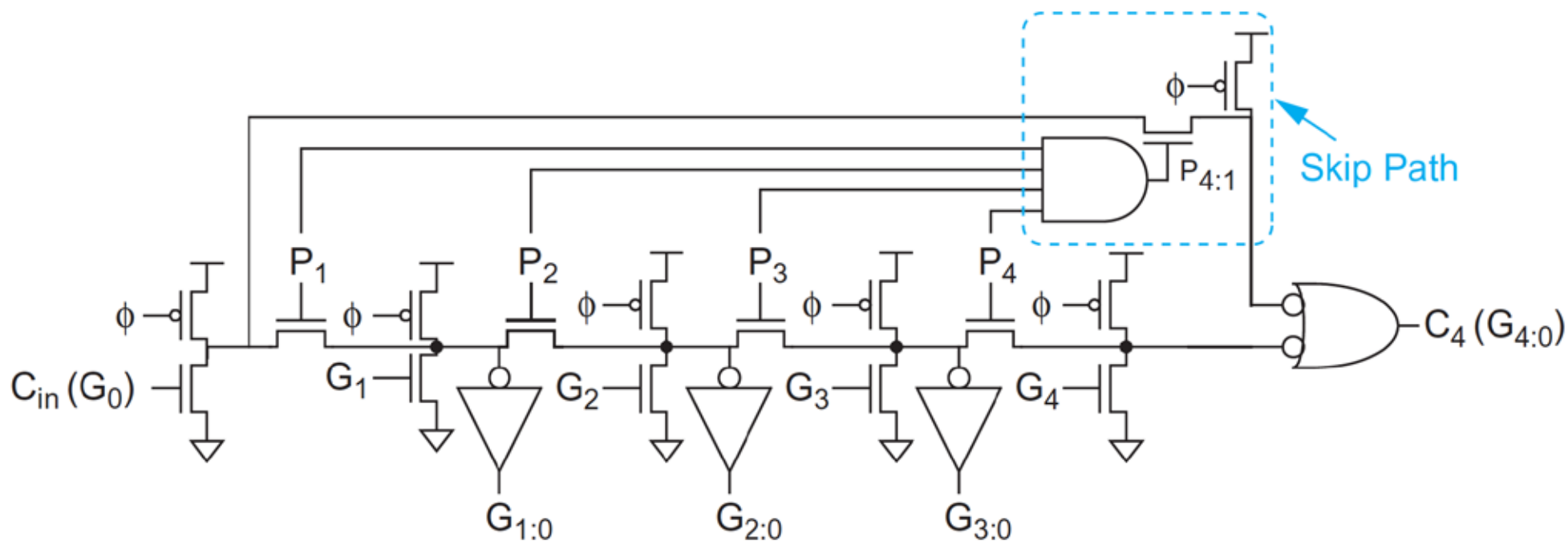- Uses dynamic logic and n-channel pass gates
- Can skip across 4 bits




Carry-Skip PG Diagram

- For k n -bit groups ($N = nk$)

 

$$t_{\text{skip}} = t_{pg} + \left[2(n-1) + (k-1) \right] t_{AO} + t_{\text{xor}}$$


Variable Group Size

 



Delay grows as $O(\sqrt{N})$

Carry-Lookahead Adder

 
- Carry-lookahead adder computes $G_{i:0}$ for many bits in parallel
- Uses higher-valency cells with more than two inputs



Higher-Valency Cells

 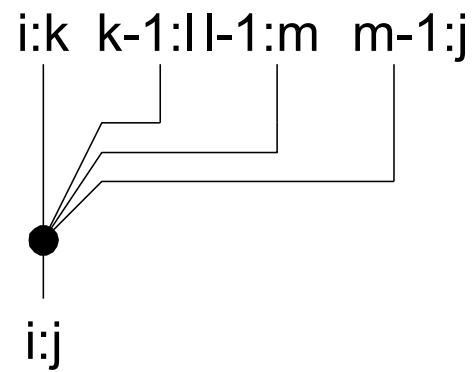


 CLA PG diagram using higher valency cells




Carry-Select Adder

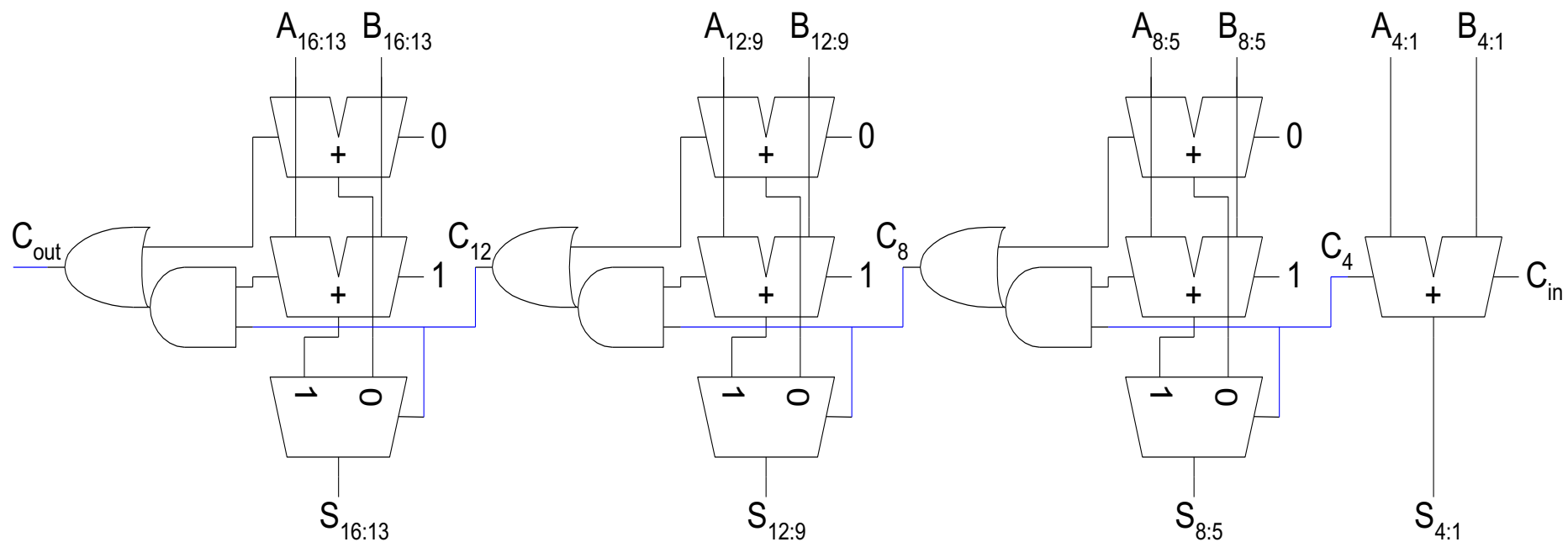- **Trick for critical paths dependent on late input X**
 - Precompute two possible outputs for $X = 0, 1$
 - Select proper output when X arrives
- **Carry-select adder precomputes n-bit sums**
 - For both possible carries into n-bit group



Carry-Increment Adder

 
- Factor initial PG and final XOR out of carry-select



$$t_{\text{increment}} = t_{pg} + \left[(n-1) + (k-1) \right] t_{AO} + t_{xor}$$

Variable Group Size

- **Buffer noncritical signals**

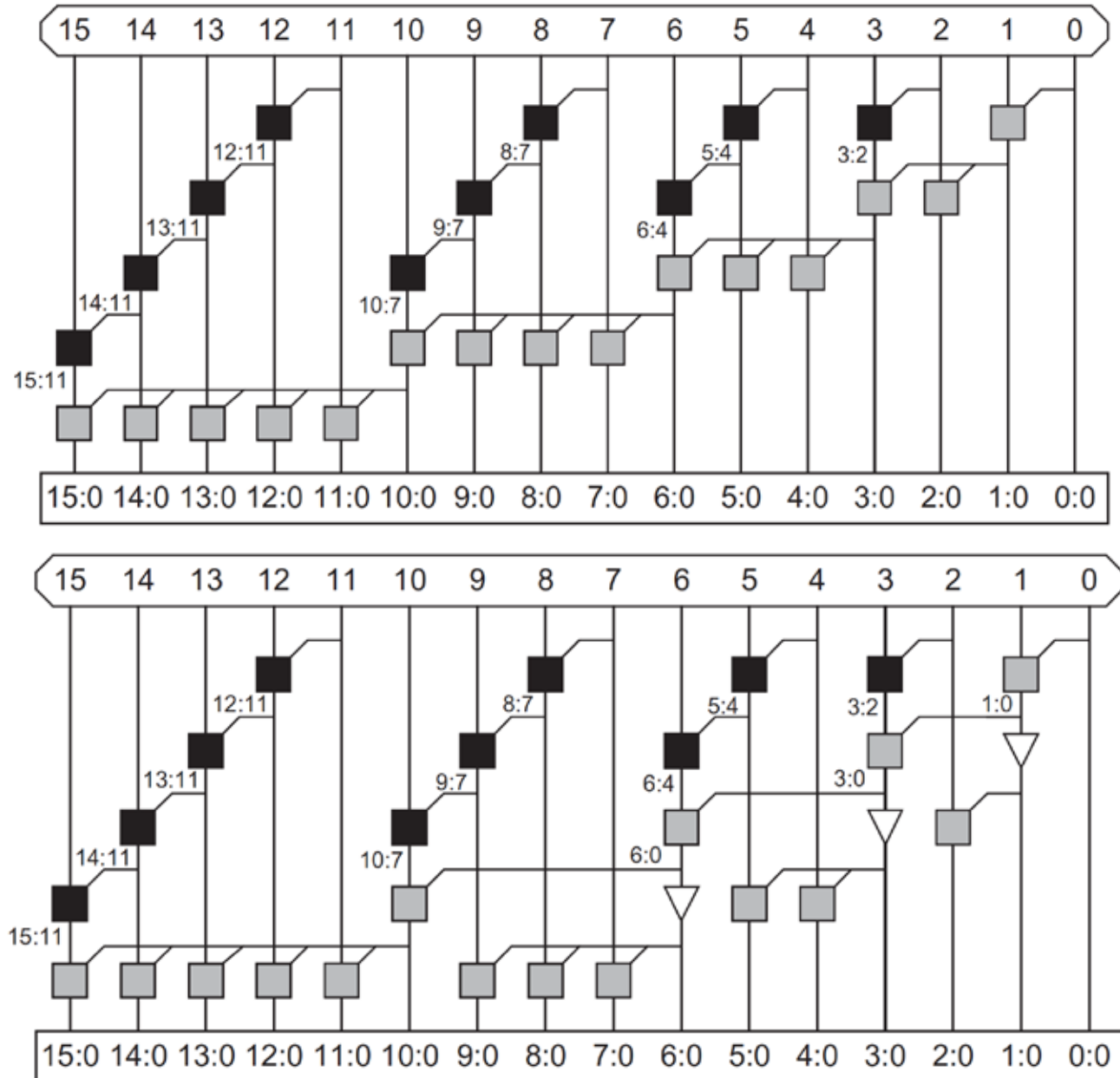



Tree Adder

- **If look-ahead is good, look-ahead across lookahead!**
 - Recursive lookahead gives $O(\log N)$ delay


- **Many variations on tree adders**

 - **Three metrics to worry about:**
 - Wiring tracks
 - Levels of logic
 - Fanout



 

Kogge-Stone

 

Tree Adder Taxonomy


- **Ideal N-bit tree adder would have**
 - $L = \log N$ logic levels
 - Fanout never exceeds 2
 - No more than one wiring track between levels


- **We describe adders with 3-D taxonomy (l, f, t)**
 - Logic levels: $L + l$
 - Fanout: $2^f + 1$
 - Wiring tracks: 2^t

- **Known tree adders sit on plane defined by**


$$l + f + t = L - 1$$

Basic Tree Adder Taxonomy

 


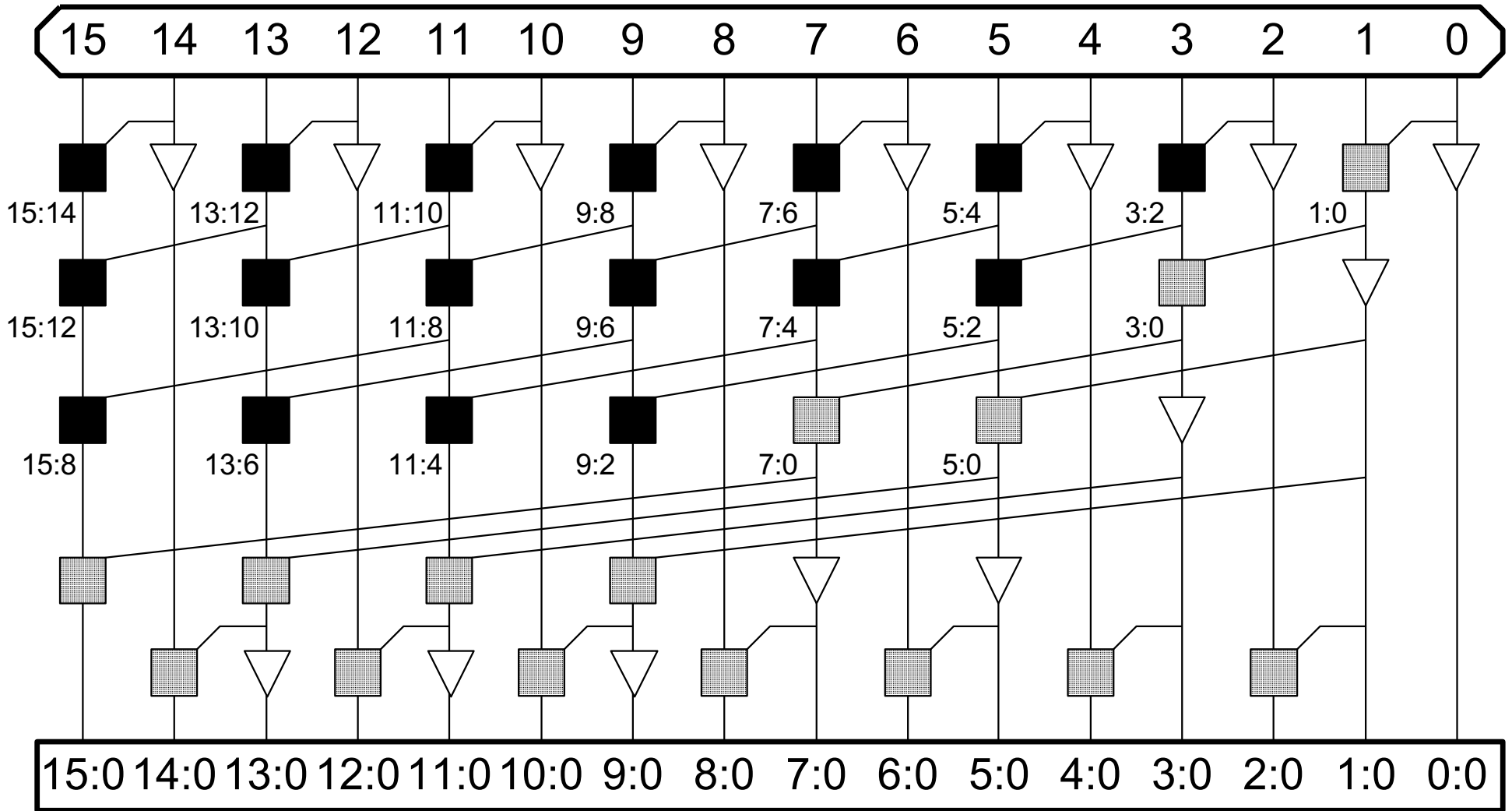


Knowles

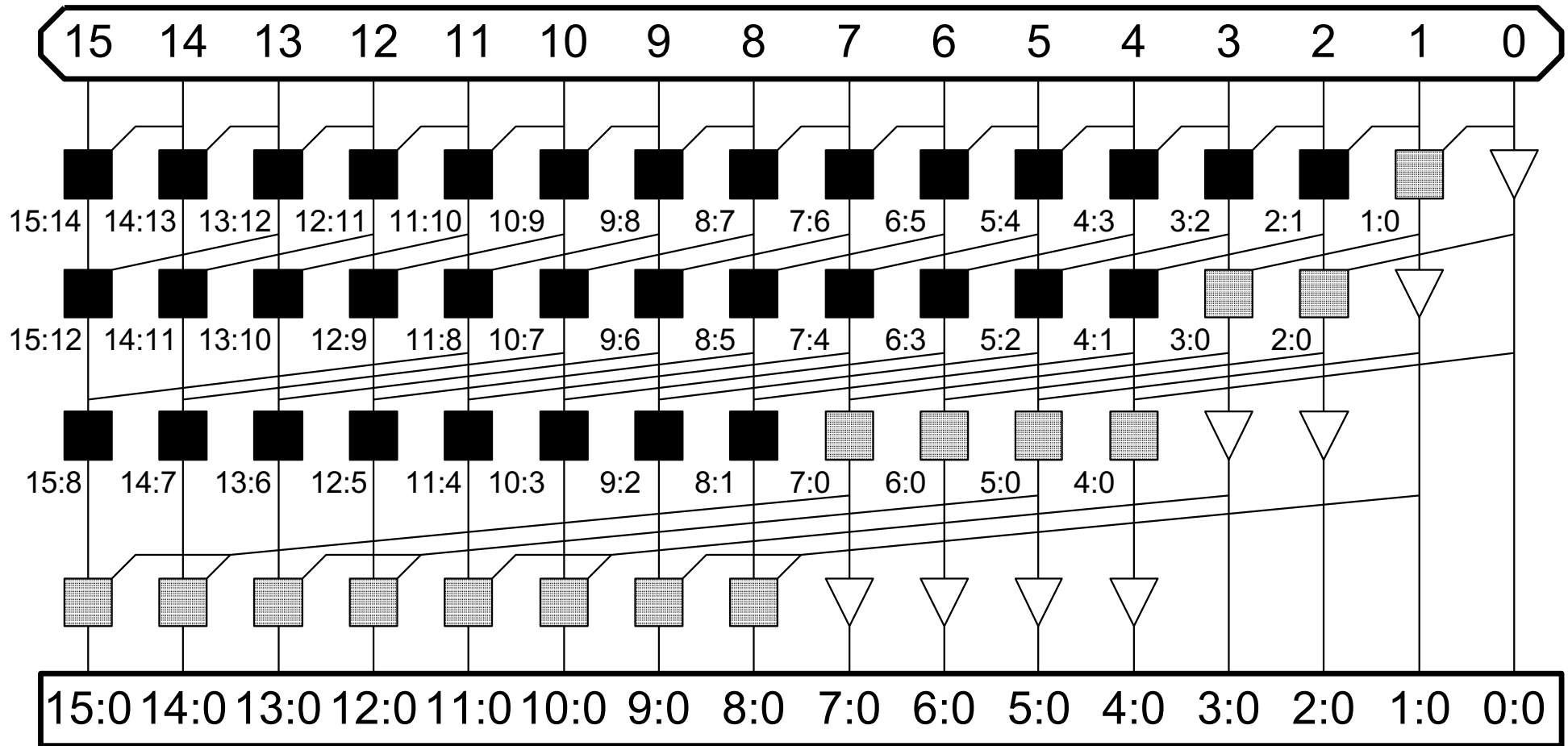


Revised Tree Adder Taxonomy

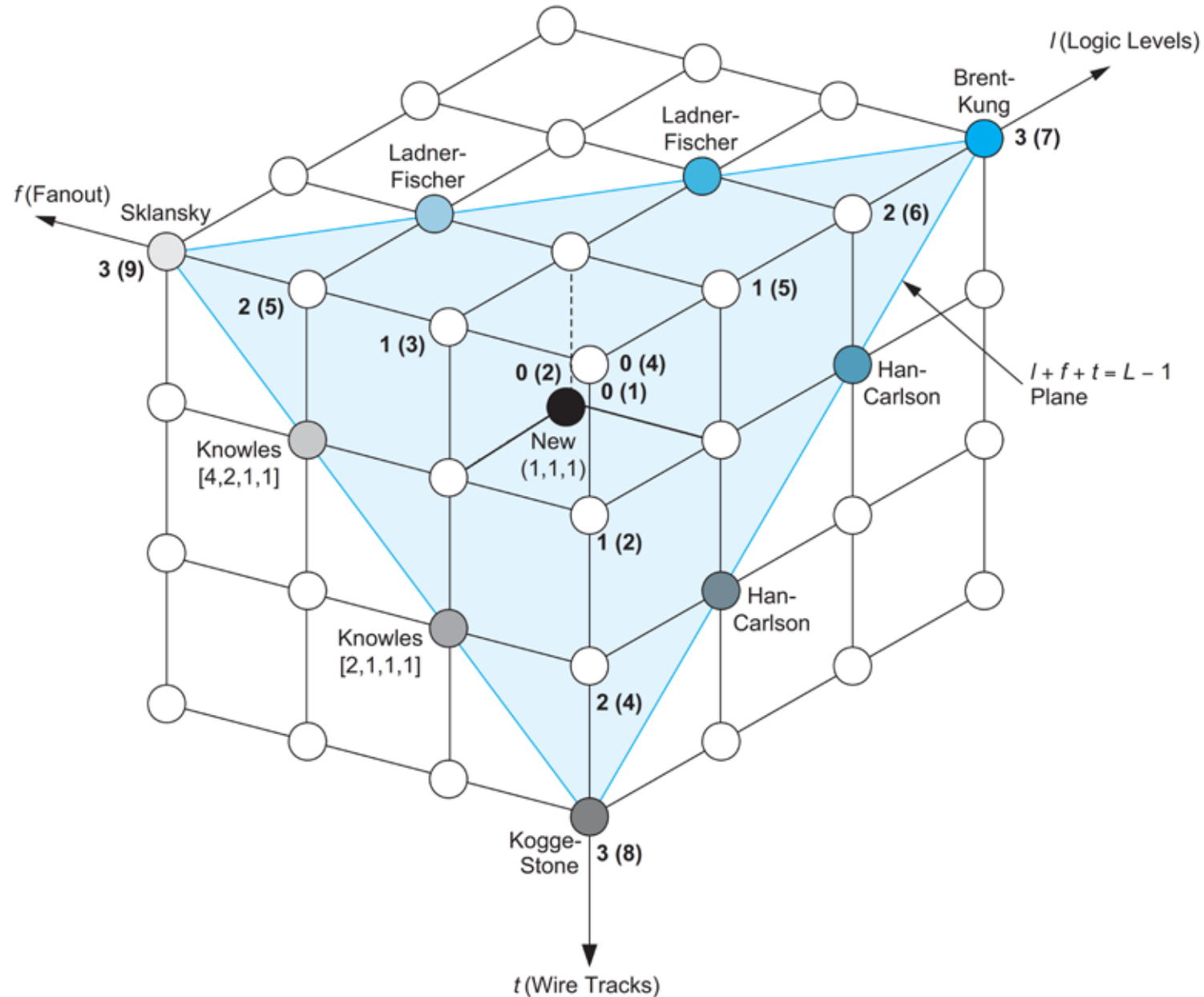

Tree Adder Taxonomy Overview

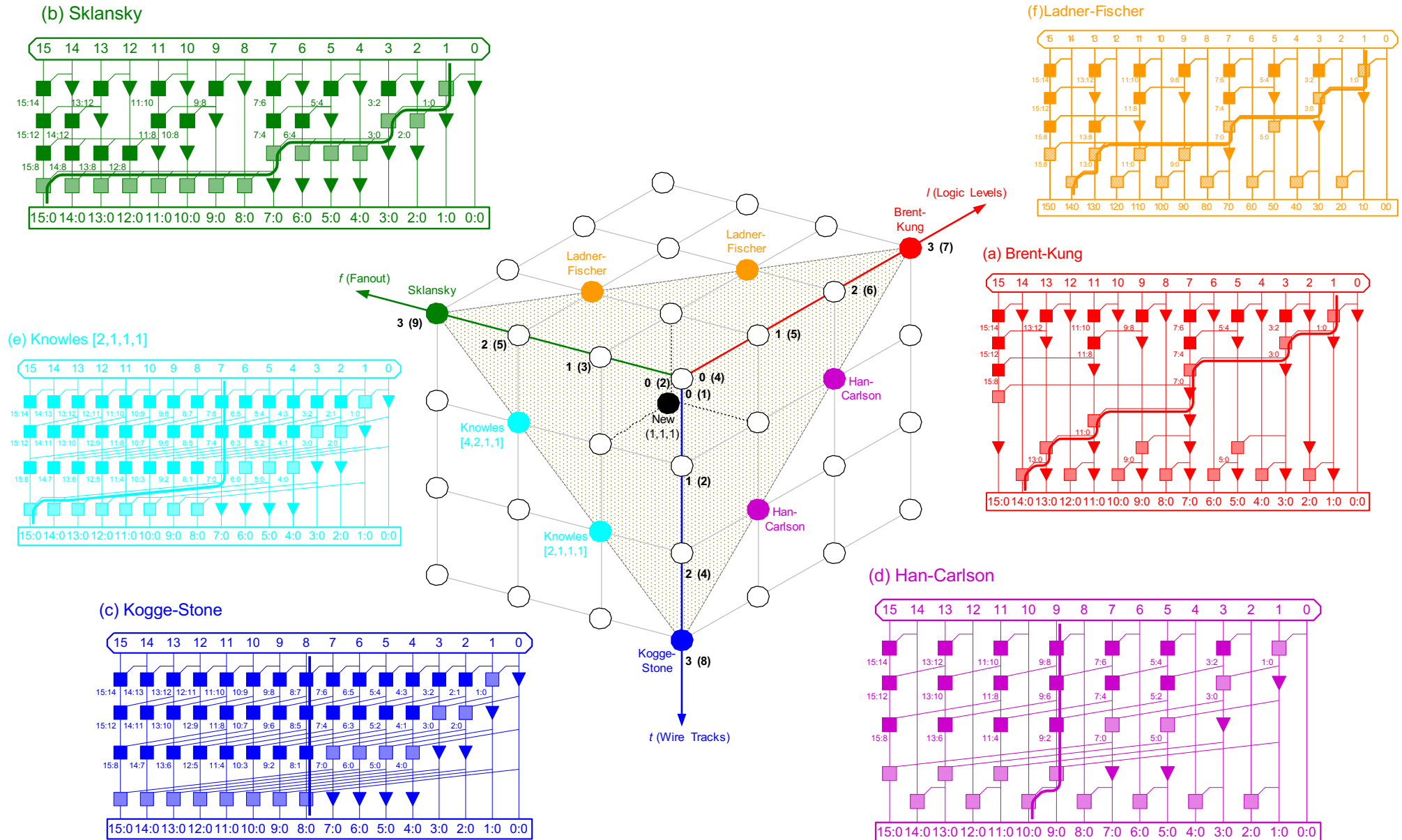

Area vs. delay of synthesized adders

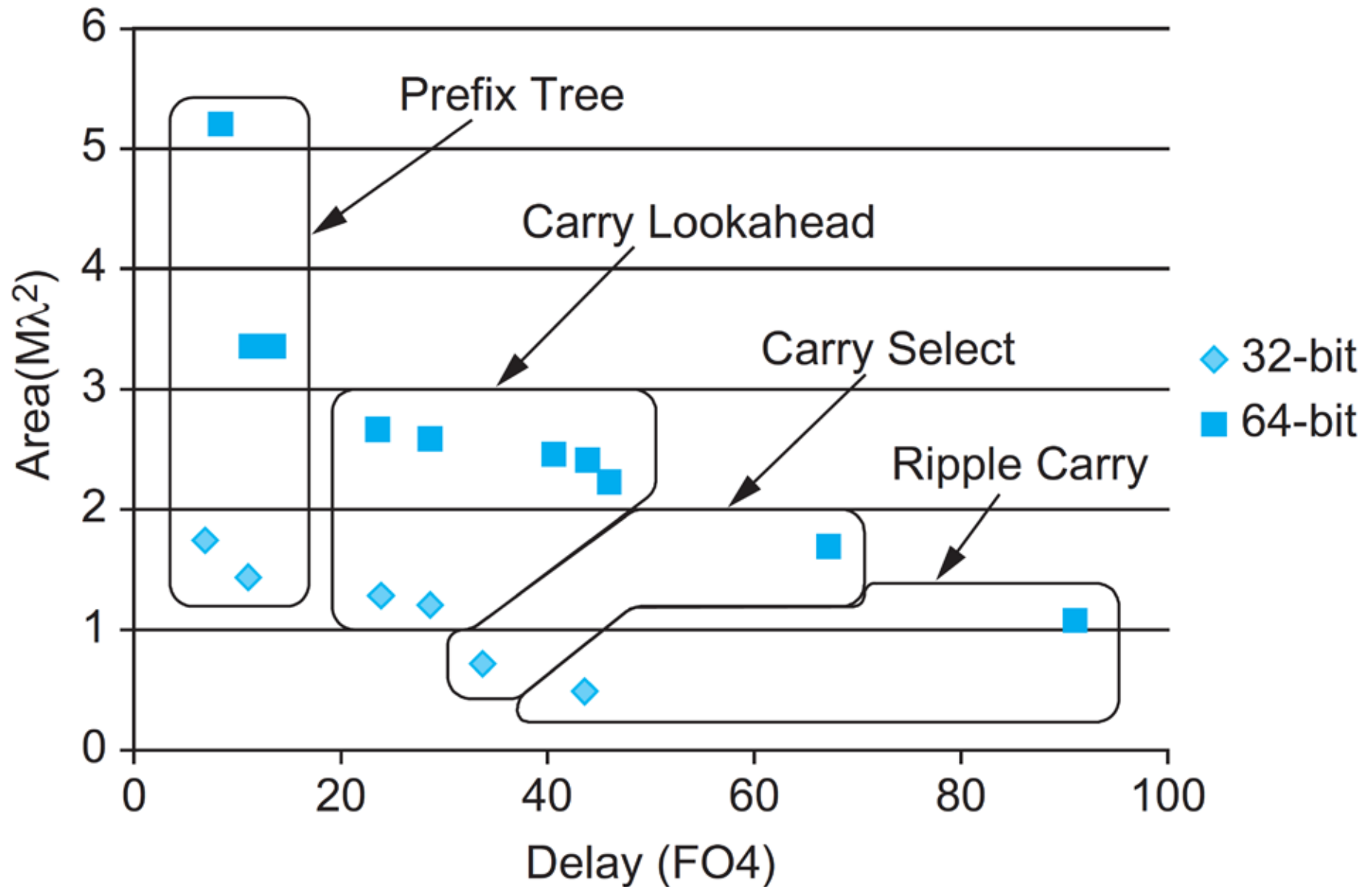

Summary

Adder architectures offer area / power / delay tradeoffs.

Choose the best one for your application.

Architecture	Classification	Logic Levels	Max Fanout	Tracks	Cells
Carry-Ripple		$N - 1$	1	1	N
Carry-Skip ($n = 4$)		$N/4 + 5$	2	1	$1.25N$
Carry-Increment ($n = 4$)		$N/4 + 2$	4	1	$2N$
Carry-Increment (variable group)		$\sqrt{2N}$	$\sqrt{2N}$	1	$2N$
Brent-Kung	$(L-1, 0, 0)$	$2\log_2 N - 1$	2	1	$2N$
Sklansky	$(0, L-1, 0)$	$\log_2 N$	$N/2 + 1$	1	$0.5 N \log_2 N$
Kogge-Stone	$(0, 0, L - 1)$	$\log_2 N$	2	$N/2$	$N \log_2 N$
Han-Carlson	$(1, 0, L - 2)$	$\log_2 N + 1$	2	$N/4$	$0.5 N \log_2 N$
Ladner Fischer ($l = 1$)	$(1, L - 2, 0)$	$\log_2 N + 1$	$N/4 + 1$	1	$0.25 N \log_2 N$
Knowles [2,1,...,1]	$(0, 1, L - 2)$	$\log_2 N$	3	$N/4$	$N \log_2 N$