


Lecture 12: Datapath Design

Mark McDermott


**Electrical and Computer Engineering
The University of Texas at Austin**

Datapath Design

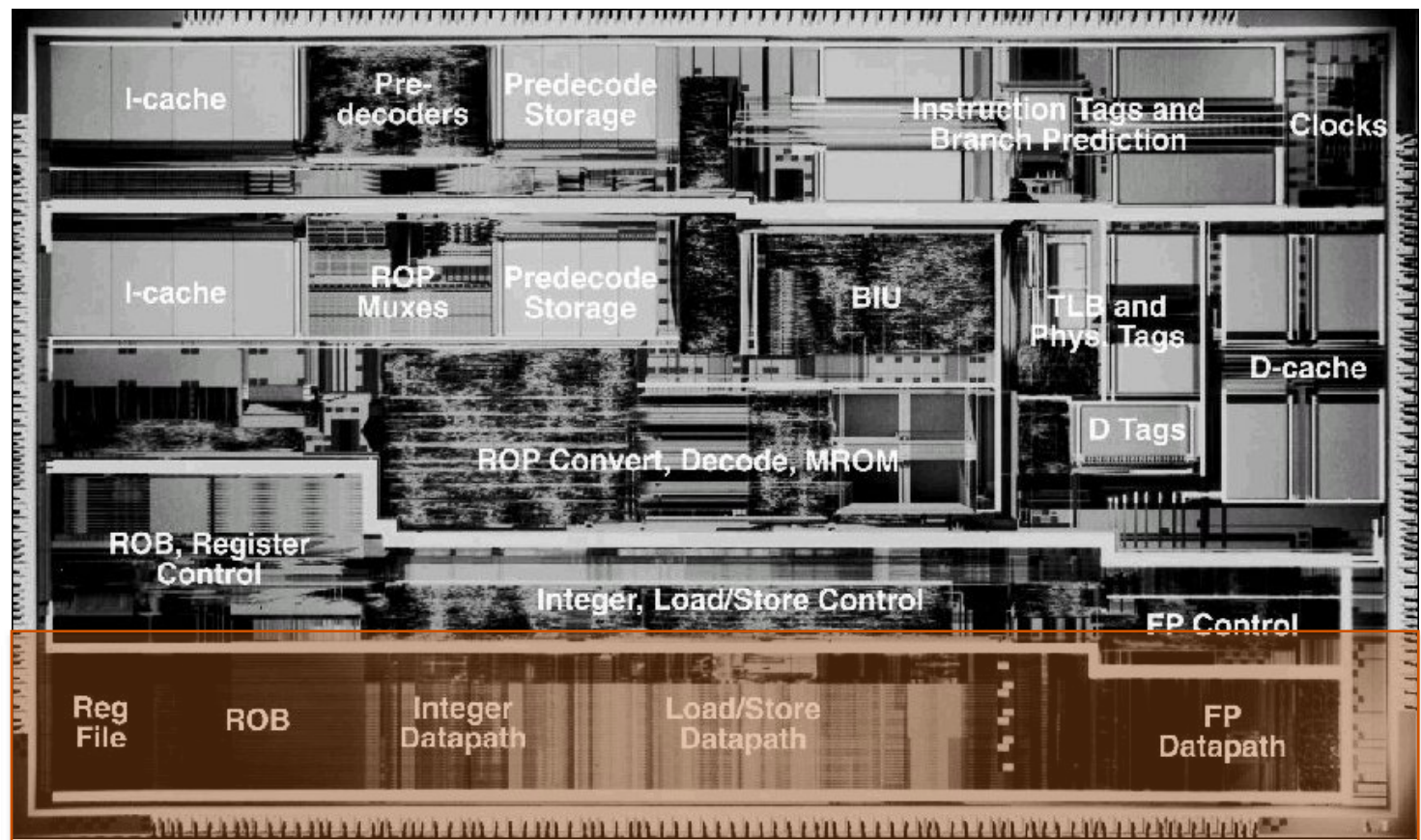- Comparators
- Shifters
- Adders
- Multipliers
- Registers



ARM Datapath



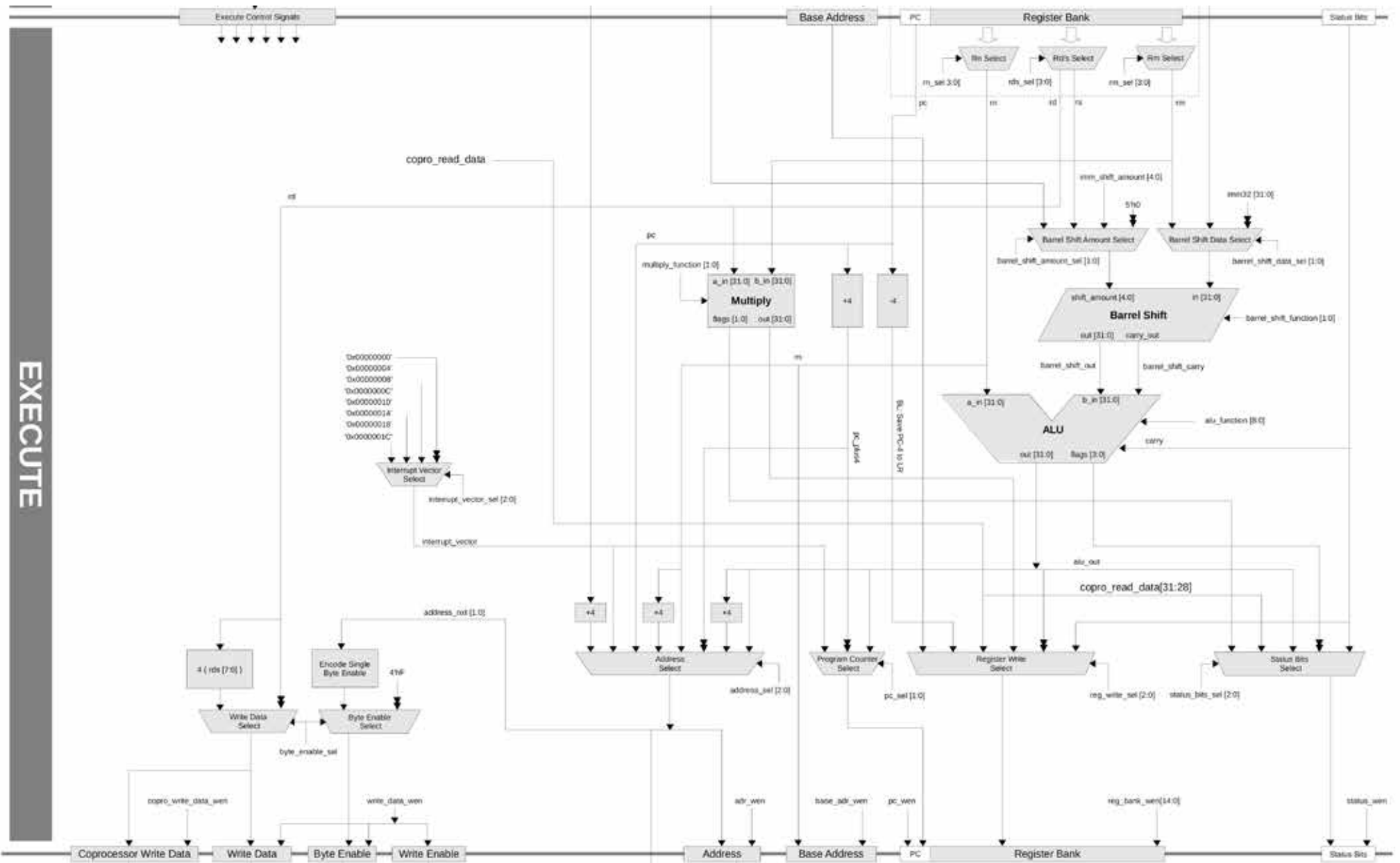


Comparators

- **0' s detector:** **$A = 00\dots000$**
- **1' s detector:** **$A = 11\dots111$**
- **Equality comparator:** **$A = B$**
- **Magnitude comparator:** **$A < B$**


1's & 0's Detectors

   - **1's detector: N-input AND gate**
- **0's detector: NOTs + 1's detector (N-input NOR)**




Equality Comparator

 - Check if each bit is equal (XNOR, or “equality gate”)
- 1’s detect on bitwise equality



Magnitude Comparator

 - Compute $B-A$ and look at sign
- $B-A = B + \sim A + 1$
- For unsigned numbers, carry out is sign bit



Signed vs. Unsigned

- **For signed numbers, comparison is harder**
 - **C: carry out**
 - **Z: zero (all bits of A-B are 0)**
 - **N: negative (MSB of result)**
 - **V: overflow (inputs had different signs, output sign \neq B)**


Table 10.4 Magnitude comparison		
Relation	Unsigned Comparison	Signed Comparison
$A = B$	Z	Z
$A \neq B$	\bar{Z}	\bar{Z}
$A < B$	$\overline{C + Z}$	$\overline{(N \oplus V) + Z}$
$A > B$	\bar{C}	$(N \oplus V)$
$A \leq B$	C	$\overline{(N \oplus V)}$
$A \geq B$	$\bar{C} + Z$	$(N \oplus V) + Z$

Shifters

■ Logical Shift:

– Shifts number left or right and fills with 0's

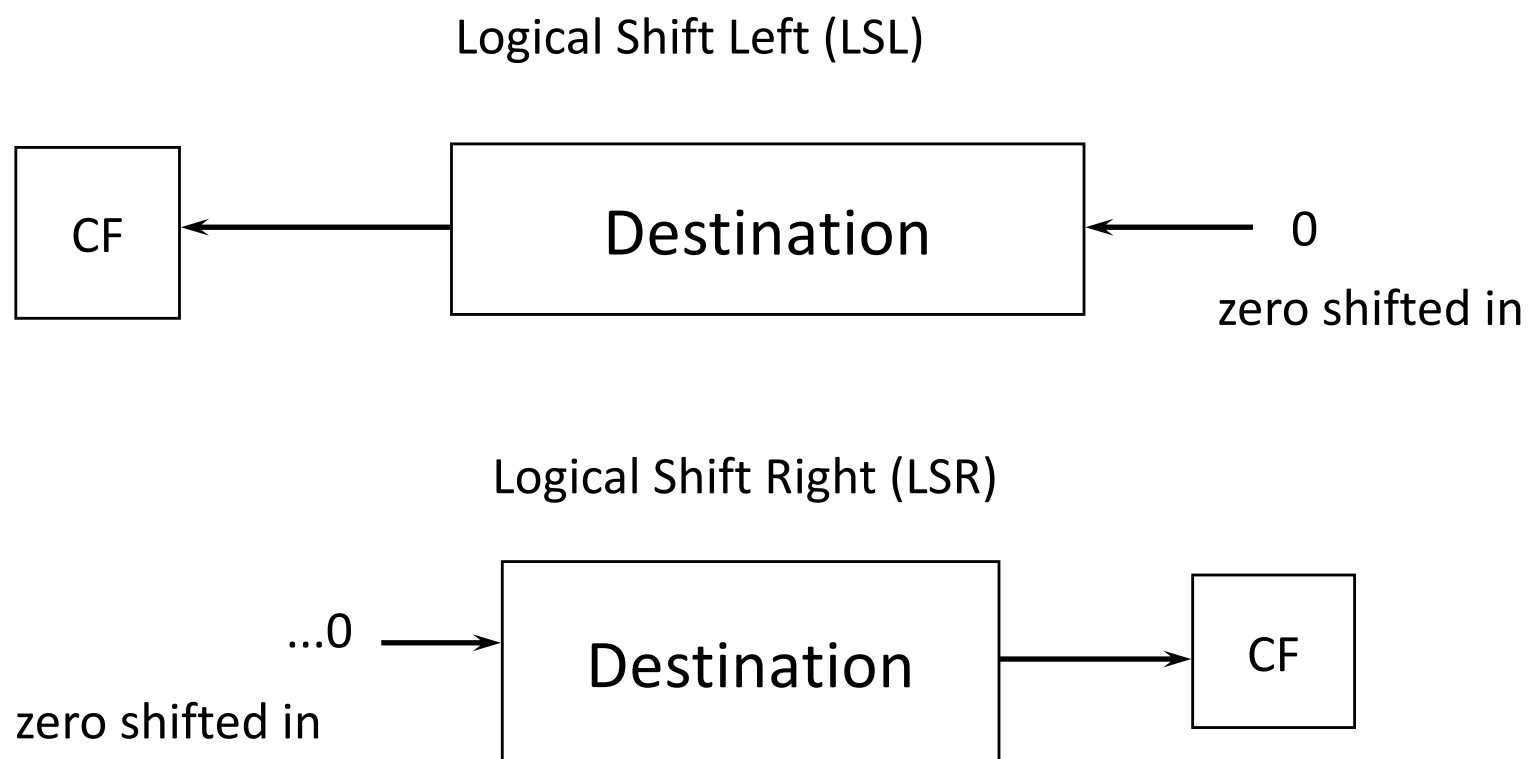- **1011 LSR 1 = 0101** **1011 LSL1 = 0110**



Shifters

- **Arithmetic Shift:**

- Shifts number left or right. Right shift sign extends

1011 ASR1 = 1101 1011 ASL1 = 0110

Arithmetic Shift Right (ASR)

Shifts right (divides by powers of two) and preserves the sign bit, for 2's complement operations.
 e.g.

ASR #5 = divide by 32

Arithmetic Shift Right



Sign bit shifted in

Shifters

- **Barrel Shift (Rotate):**

- Shifts number left or right and fills with lost bits


1011 ROR1 = 1101 1011 ROL1 = 0111

Rotate Right (ROR)

Similar to an ASR but the bits wrap around as they leave the LSB and appear as the MSB.

e.g. **ROR #5**

 
Note the last bit rotated is also used as the Carry Out.




Rotate Right Extended (RRX)

This operation uses the CPSR C flag as a 33rd bit.

 Rotates right by 1 bit. Encoded as **ROR #0**



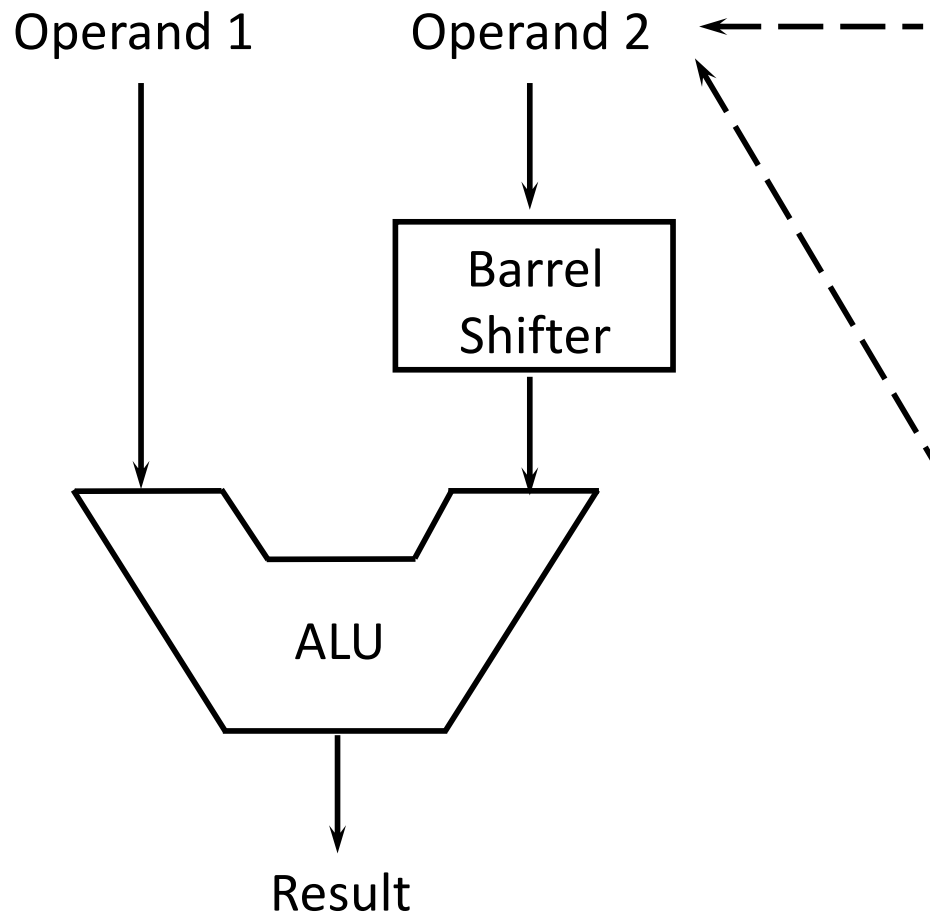ARM: Using the Barrel Shifter: The Second Operand



Register, optionally with shift operation applied.

Shift value can be either be:

5 bit unsigned integer

Specified in bottom byte of another register.

Immediate value

8 bit number

Can be rotated right through an even number of positions.

Assembler will calculate rotate for you from constant.

Second Operand: Using a Shifted Register


- Using a multiplication instruction to multiply by a constant means first loading the constant into a register and then waiting a number of internal cycles for the instruction to complete.
- A more optimum solution can often be found by using some combination of MOVs, ADDs, SUBs and RSBs with shifts.
 - Multiplications by a constant equal to a $(\text{power of } 2) \pm 1$ can be done in one cycle.

```

MOV R2, R0, LSL #2      ; Shift R0 left by 2, write to R2, (R2=R0x4)
ADD R9, R5, R5, LSL #3  ; R9 = R5 + R5 x 8 or R9 = R5 x 9
RSB R9, R5, R5, LSL #3  ; R9 = R5 x 8 - R5 or R9 = R5 x 7
SUB R10, R9, R8, LSR #4 ; R10 = R9 - R8 / 16
MOV R12, R4, ROR R3     ; R12 = R4 rotated right by value of R3
  
```

Funnel Shifter

 - A funnel shifter can do all six types of shifts
- Selects N-bit field Y from 2N-bit input
 - Shift by k bits ($0 \leq k < N$)



Funnel Shifter Operation

Table 10.10 Funnel shifter operation

Shift Type	B	C	Offset
Logical Right	$0\dots 0$	$A_{N-1}\dots A_0$	k
Logical Left	$A_{N-1}\dots A_0$	$0\dots 0$	$N-k$
Arithmetic Right	$A_{N-1}\dots A_{N-1}$ (sign extension)	$A_{N-1}\dots A_0$	k
Arithmetic Left	$A_{N-1}\dots A_0$	0	$N-k$
Rotate Right	$A_{N-1}\dots A_0$	$A_{N-1}\dots A_0$	k
Rotate Left	$A_{N-1}\dots A_0$	$A_{N-1}\dots A_0$	$N-k$

Simplified Funnel Shifter

- Optimize down to $2N-1$ bit input



Table 10.11 Simplified funnel shifter

Shift Type	Z	Offset
Logical Right	$0..0, A_{N-1}...A_0$	k
Logical Left	$A_{N-1}...A_0, 0..0$	\bar{k}
Arithmetic Right	$A_{N-1}...A_{N-1}, A_{N-1}...A_0$	k
Arithmetic Left	$A_{N-1}...A_0, 0..0$	\bar{k}
Rotate Right	$A_{N-2}...A_0, A_{N-1}...A_0$	k
Rotate Left	$A_{N-1}...A_0, A_{N-1}..A_1$	\bar{k}

Funnel Shifter Design 1


- **N N-input multiplexers**

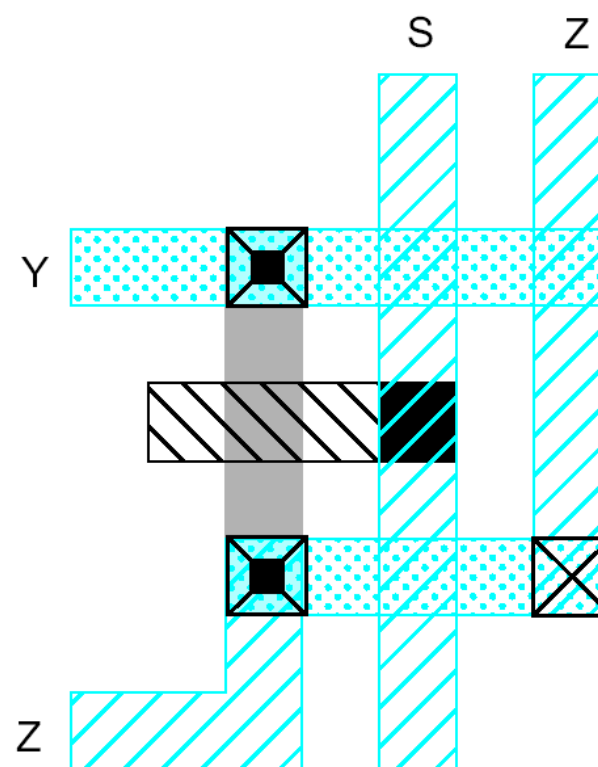 - Use 1-of-N hot select signals for shift amount
- nMOS pass transistor design (Vt drops!)




Funnel Shifter Design 2

 
- **Log N stages of 2-input MUXes**
 - No select decoding needed




Logarithmic Barrel Shifter

 

Right shift only

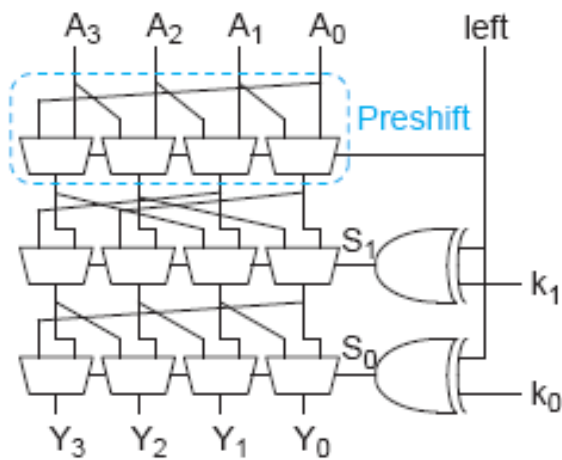


Right/Left shift

 

Right/Left Shift & Rotate


32-bit Logarithmic Barrel

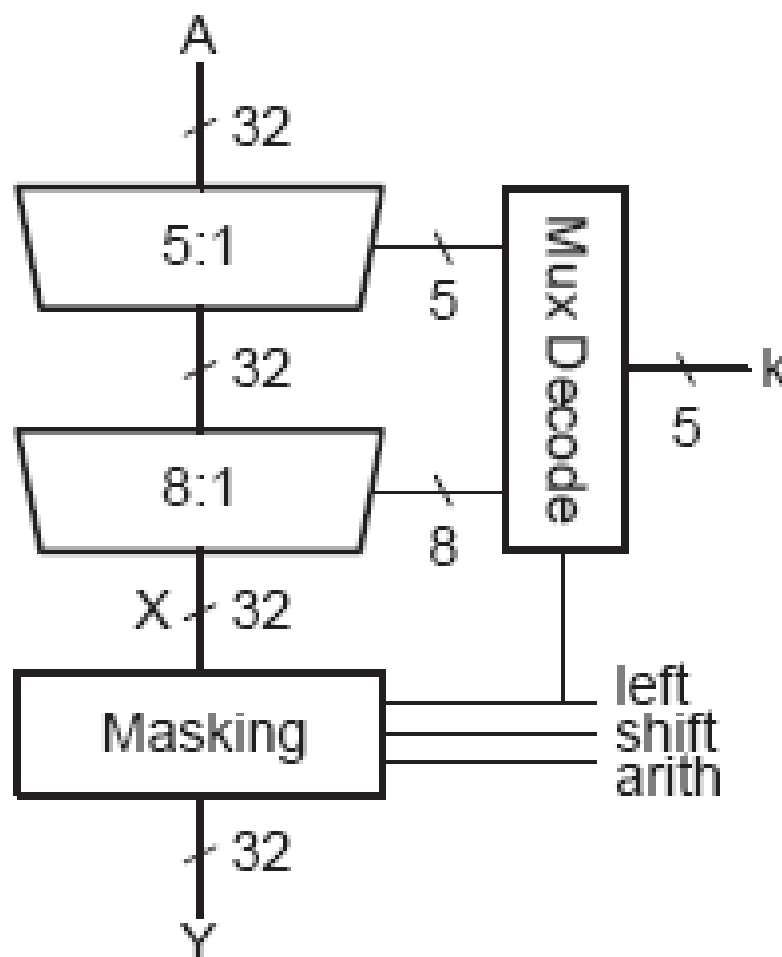- Datapath never wider than 32 bits
- First stage preshifts by 1 to handle left shifts




Multi-input Adders

 - **Suppose we want to add k N-bit words**
 - Ex: $0001 + 0111 + 1101 + 0010 = 10111$
- **Straightforward solution: k-1 N-input CPAs**
 - Large and slow




Carry Save Addition

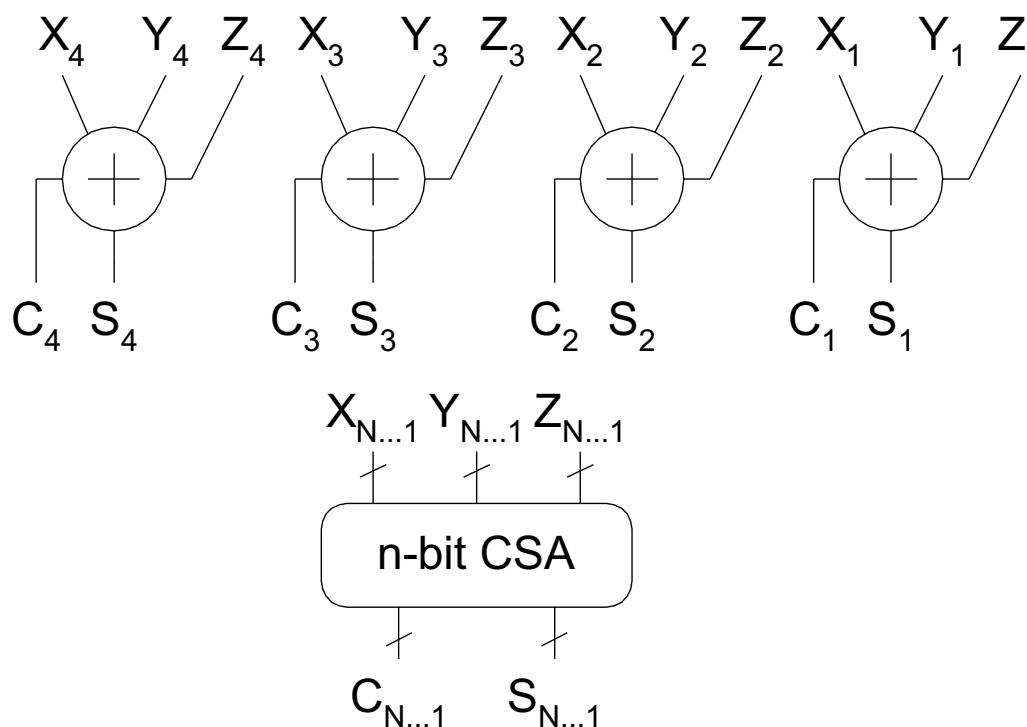- **Full adder sums 3 inputs, produces 2 outputs**
 - Carry output has twice *weight* of sum output
- **N full adders in parallel: *carry save adder***
 - Produce N sums and N carry outs



CSA Application

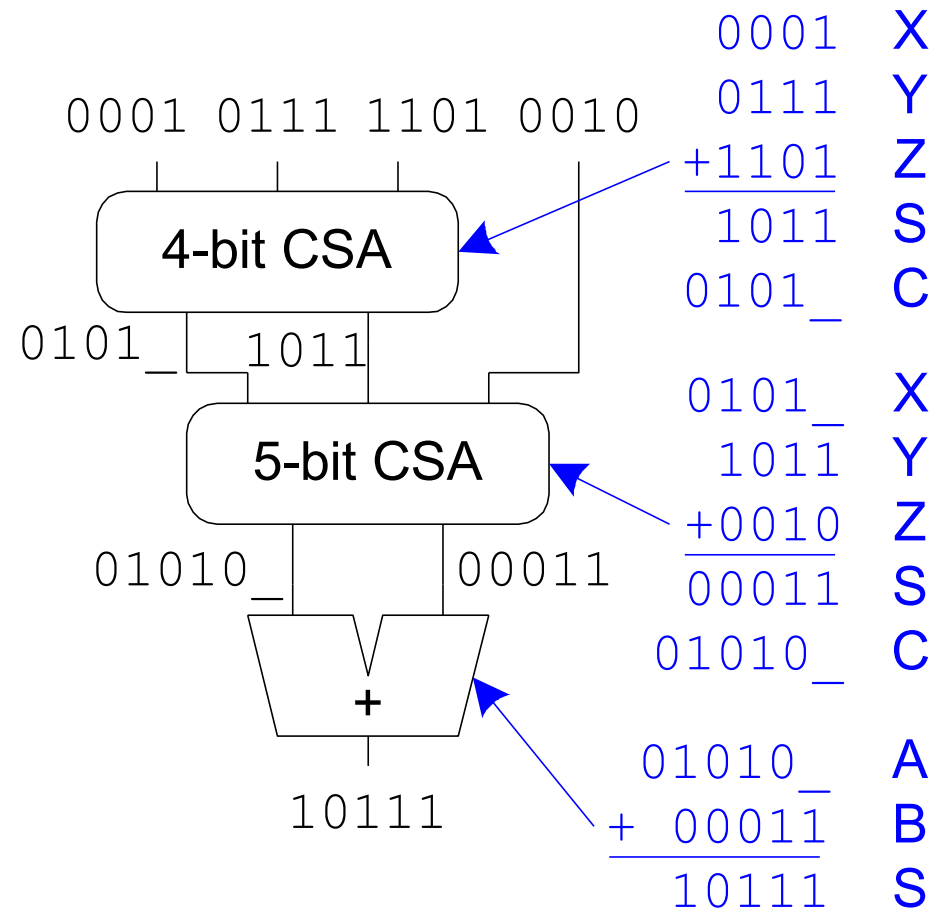- **Use k-2 stages of CSAs**
 - Keep result in carry-save redundant form
- **Final CPA computes actual result**



Multiplication

■ **Example:**

1100	:	12 ₁₀	<div style="display: flex; align-items: center;"> <div style="font-size: 4em; margin-right: 10px;">}</div> <div> <p style="margin: 0;">multiplicand</p> <p style="margin: 0;">multiplier</p> <p style="margin: 0;">partial products</p> <p style="margin: 0;">product</p> </div> </div>
0101	:	5 ₁₀	
<u>1100</u>			
0000			
1100			
<u>0000</u>			
00111100	:	60 ₁₀	

■ **M x N-bit multiplication**

- Produce N M-bit partial products
- Sum these to produce M+N-bit product

General Form


- **Multiplicand:** $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$
- **Multiplier:** $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$

- **Product:**
$$P = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$



						y_5	y_4	y_3	y_2	y_1	y_0	multiplicand multiplier
						x_5	x_4	x_3	x_2	x_1	x_0	
						$x_0 y_5$	$x_0 y_4$	$x_0 y_3$	$x_0 y_2$	$x_0 y_1$	$x_0 y_0$	
					$x_1 y_5$	$x_1 y_4$	$x_1 y_3$	$x_1 y_2$	$x_1 y_1$	$x_1 y_0$		
				$x_2 y_5$	$x_2 y_4$	$x_2 y_3$	$x_2 y_2$	$x_2 y_1$	$x_2 y_0$			
			$x_3 y_5$	$x_3 y_4$	$x_3 y_3$	$x_3 y_2$	$x_3 y_1$	$x_3 y_0$				
		$x_4 y_5$	$x_4 y_4$	$x_4 y_3$	$x_4 y_2$	$x_4 y_1$	$x_4 y_0$					
	$x_5 y_5$	$x_5 y_4$	$x_5 y_3$	$x_5 y_2$	$x_5 y_1$	$x_5 y_0$						
p_{11}	p_{10}	p_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0	partial products

Dot Diagram

- Each dot represents a bit

 


Array Multiplier

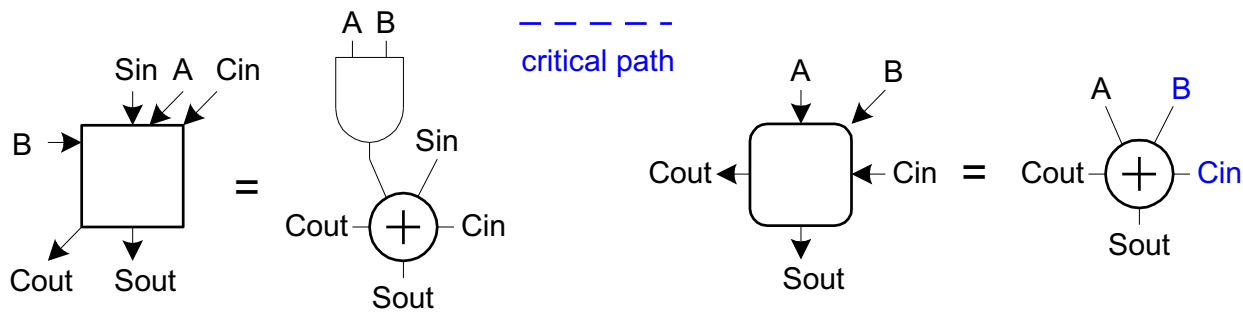 

Rectangular Array

 - Squash array to fit rectangular floorplan



Fewer Partial Products

- **Array multiplier requires N partial products**
- **If we looked at groups of r bits, we could form N/r partial products.**
 - Faster and smaller?
 - Called radix- 2^r encoding
- **Ex: $r = 2$: look at pairs of bits**
 - Form partial products of $0, Y, 2Y, 3Y$
 - First three are easy, but $3Y$ requires adder 😞


Booth Encoding

- Instead of $3Y$, try $-Y$, then increment next partial product to add $4Y$
- Similarly, for $2Y$, try $-2Y + 4Y$ in next partial product


Inputs			Partial Product	Booth Selects		
x_{2i+1}	x_{2i}	x_{2i-1}	PP_i	X_i	$2X_i$	M_i
0	0	0	0	0	0	0
0	0	1	Y	1	0	0
0	1	0	Y	1	0	0
0	1	1	$2Y$	0	1	0
1	0	0	$-2Y$	0	1	1
1	0	1	$-Y$	1	0	1
1	1	0	$-Y$	1	0	1
1	1	1	$-0 (= 0)$	0	0	1

Booth Hardware

 - **Booth encoder generates control lines for each PP**
 - Booth selectors choose PP bits




Booth hardware

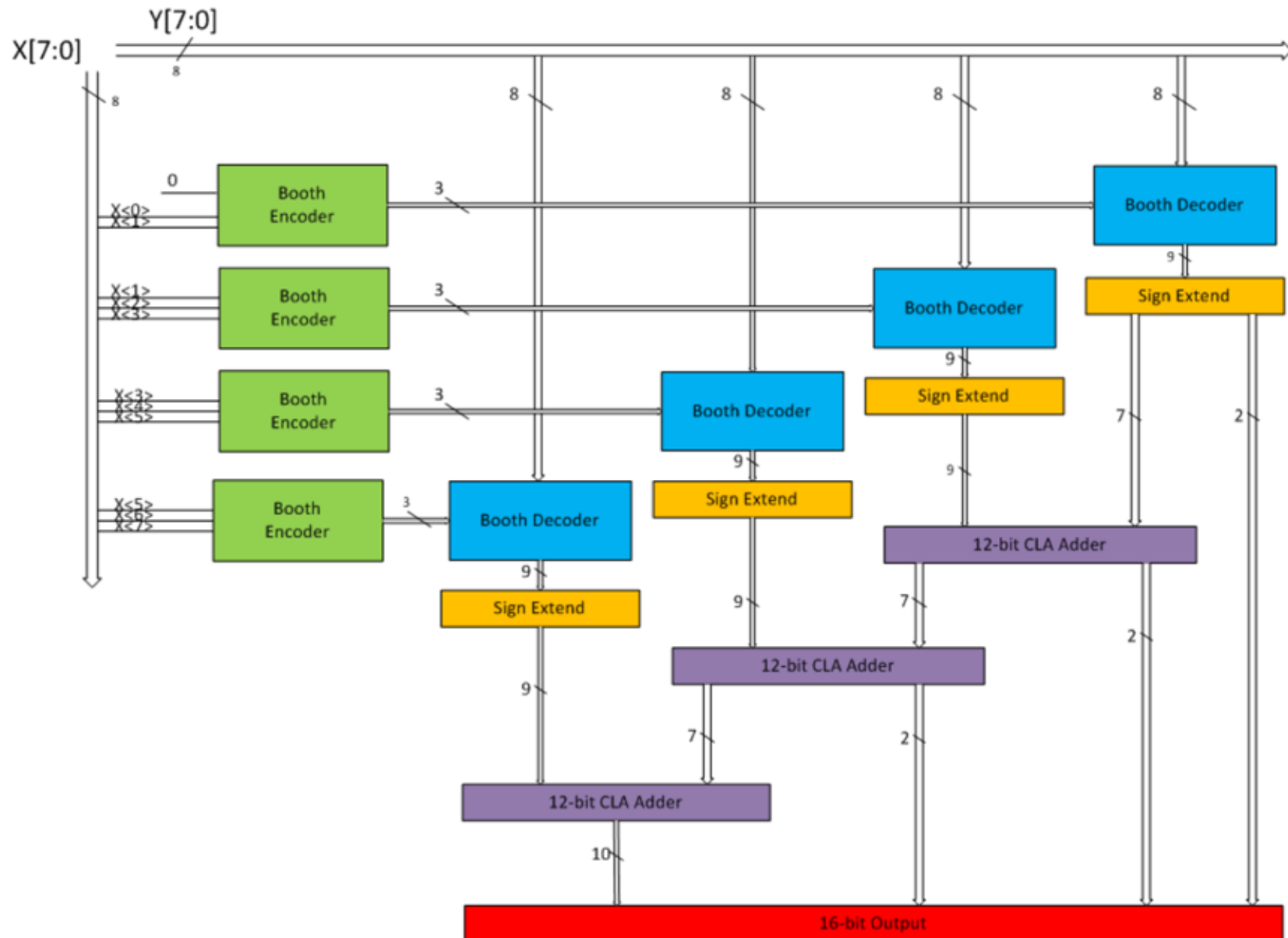


Sign Extension

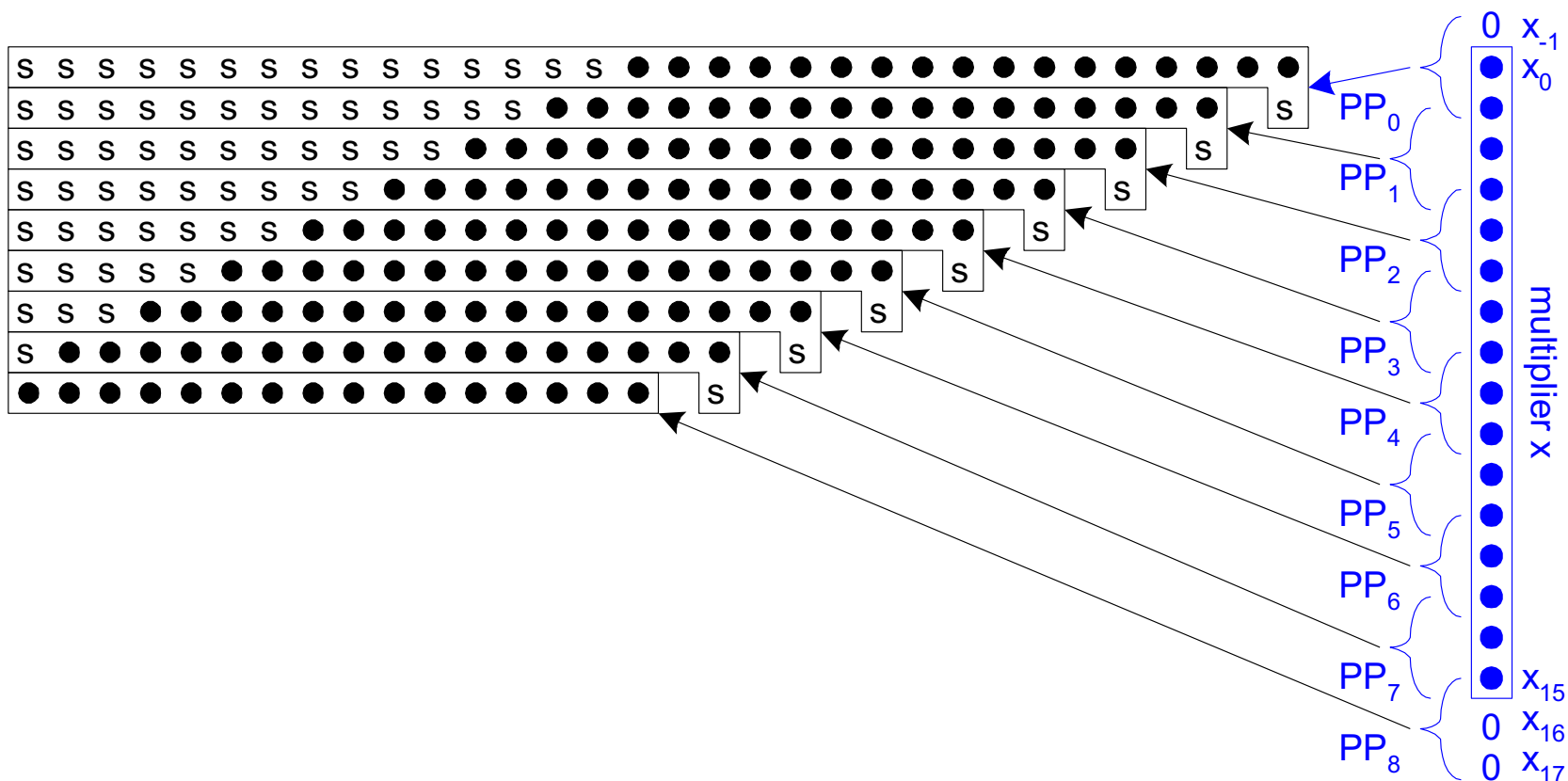- **Partial products can be negative**
 - Require sign extension, which is cumbersome
 - High fanout on most significant bit




Simplified Sign Extension

 - **Sign bits are either all 0's or all 1's**
 - Note that all 0's is all 1's + 1 in proper column
 - Use this to reduce loading on MSB



Even Simpler Sign Extension

 - **No need to add all the 1's in hardware**
 - Precompute the answer!



Advanced Multiplication

- **Signed vs. unsigned inputs**
- **Higher radix Booth encoding**
- **Array vs. tree CSA networks**