

---

# Lecture 13: Interconnects in CMOS Technology

**Mark McDermott**

**Electrical and Computer Engineering  
The University of Texas at Austin**

# Introduction

---

- **Chips are mostly made of wires called interconnect**
  - In stick diagram, wires set size
  - Transistors are little things under the wires
  - Many layers of wires
- **Wires are as important as transistors**
  - Speed
  - Power
  - Noise
- **Alternating layers run orthogonally**

## **HVH**

**M1: Horizontal**

**M2: Vertical**

**M3: Horizontal**

**M4: Vertical**

**:**

## **VHV**

**M1: Vertical**

**M2: Horizontal**

**M3: Vertical**

**M4: Horizontal**


**:**

# Choice of Metals


- **Until 180 nm generation, most wires were aluminum**
- **Modern processes often use copper**
  - Cu atoms diffuse into silicon and damage FETs
  - Must be surrounded by a diffusion barrier

<b>Metal</b>	<b>Bulk resistivity (<math>\mu\Omega\cdot\text{cm}</math>)</b>
Silver (Ag)	1.6
Copper (Cu)	1.7
Gold (Au)	2.2
Aluminum (Al)	2.8
Tungsten (W)	5.3
Molybdenum (Mo)	5.3

35%-40%  
improvement

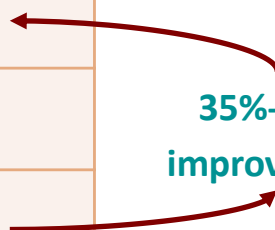

# Metal Layer Cross Section 65nM

 

# 45nm Interconnect


## Loose pitch + thick metal on upper layers:

High speed global wires

Low resistance power grid


## Tight pitch on lower layers:

Maximum density for local interconnects

 

Source: Mark Bohr, Intel Corporation
 
# SEM MICRO-GRAPH (ILM DIELECTRIC REMOVED)




Courtesy: IBM




# Advanced Metallization

## Dual damascene IC process


- Oxide deposition

 


- Stud lithography and reactive ion etch

 


- Wire lithography and reactive ion etch

 



- Stud and wire metal deposition

 


- Metal chemical-mechanical polish

 

Source: IBM Corp.

  

# Interconnect Process Dual Damascene

 


•C.-K. Hu and J.M.E. Harper, *Mater. Chem. Phys.*, 52 (1998), p. 5.


 
# WIRE GEOMETRY

- **PITCH = width + space**
- **Height (h) = distance to top/bottom routes**
- **ASPECT RATIO (AR) = thickness / width**
  - Deep submicron processes have  $AR < 2$  to maintain sheet resistances at a reasonable level
  - Coupling to neighboring routes dominates



$$R = \rho L / tw$$

# Wire Resistance

- $\rho = \text{resistivity } (\Omega \cdot \text{m})$

$$R = \frac{\rho}{t} \frac{l}{w} = R_{\square} \frac{l}{w}$$


where  $\rho = \text{resistivity}$

- $R_{\square} = \text{sheet resistance } (\Omega/\square)$

—  $\square$  is a dimensionless unit(!)

- **Count number of squares**

 —  $R = R_{\square} * (\# \text{ of squares})$



1 Rectangular Block  
 $R = R_{\square} (L/W) \Omega$

4 Rectangular Blocks  
 $R = R_{\square} (2L/2W) \Omega$   
 $= R_{\square} (L/W) \Omega$

# Sheet Resistance

---

- **Typical sheet resistances in 180 nm process**

Layer	Sheet Resistance ( $\Omega/\square$ )
Diffusion (silicided)	3-10
Diffusion (no silicide)	50-200
Polysilicon (silicided)	3-10
Polysilicon (no silicide)	50-400
Metal1	0.08
Metal2	0.05
Metal3	0.05
Metal4	0.03
Metal5	0.02
Metal6	0.02

# CONTRIBUTION OF WIRES (they are not free)

---

## ■ DELAY

- Function of R, L and C, VIA resistance, local .vs. global

## ■ POWER

- Charging/discharging of C is a function of  $CV^2F$

## ■ NOISE

- Attackers/victims impact on functionality and delay

## ■ POWER SUPPLY IR DROPS and GROUND BOUNCE

- Affects delay leading to timing failures

## ■ RELIABILITY

- Electro-migration, self heat, maximum current


## ■ COST

- Number of layers .vs. area/performance targets, yield
 
# Contact/VIA Resistance


---

- **Contacts and vias also have 2-20  $\Omega$  resistance**
- **Use many contacts for lower R**
  - Many small contacts for current crowding around periphery


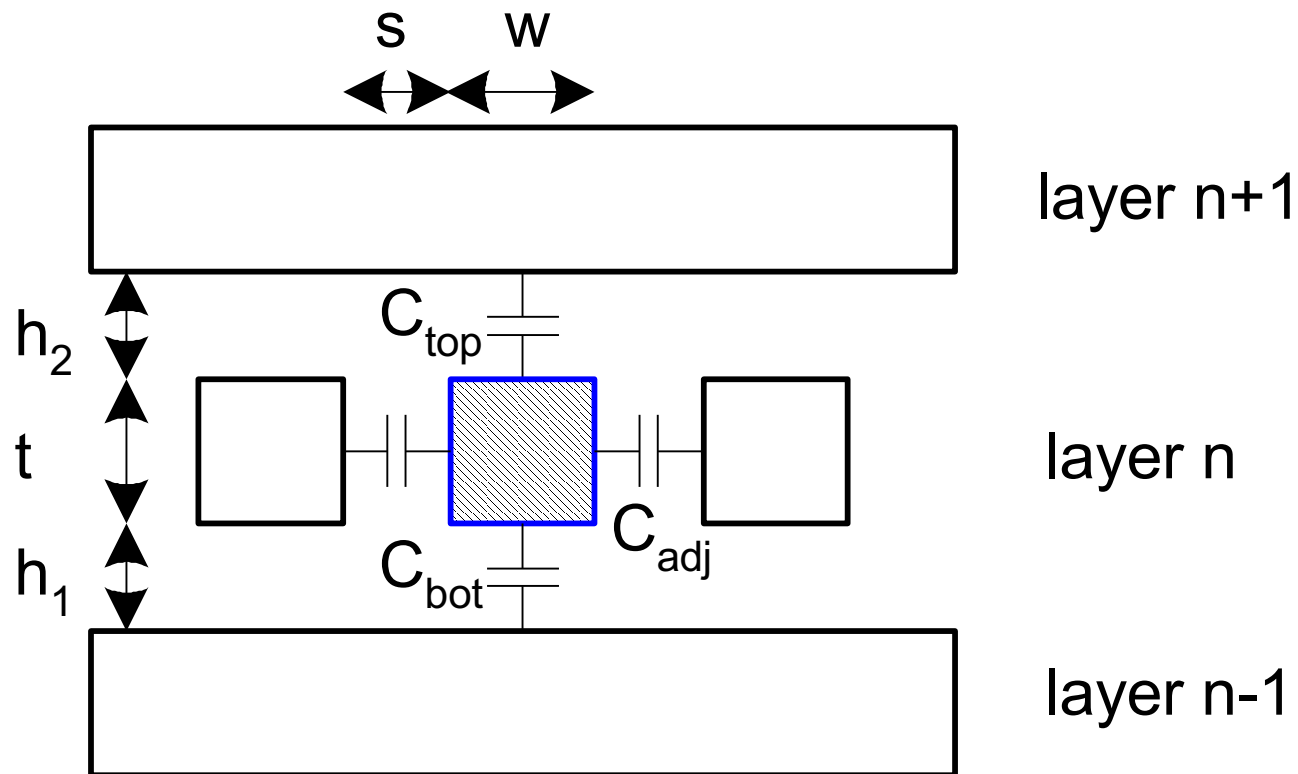
# Wire Capacitance

- **Wire has capacitance per unit length**
  - To neighbors
  - To layers above and below
- $C_{\text{total}} = C_{\text{top}} + C_{\text{bot}} + 2C_{\text{adj}}$






# Capacitance Trends

---

- **Parallel plate equation:  $C = \epsilon A/d$** 
  - Wires are not parallel plates, but obey trends
  - Increasing area ( $W, t$ ) increases capacitance
  - Increasing distance ( $s, h$ ) decreases capacitance
- **Dielectric constant**
  - $\epsilon = k\epsilon_0$
- **$\epsilon_0 = 8.85 \times 10^{-14}$  F/cm**
- **$k = 3.9$  for  $\text{SiO}_2$**
- **Processes are starting to use low-k dielectrics**
  - $k \approx 3$  (or less) as dielectrics use air pockets
 
# M2 Capacitance Data

- Typical wires have  $\sim 0.2 \text{ fF}/\mu\text{m}$ 
  - Compare to  $2 \text{ fF}/\mu\text{m}$  for gate capacitance




# Diffusion & Polysilicon

---

- **Diffusion capacitance is very high (about 2 fF/ $\mu\text{m}$ )**
  - Comparable to gate capacitance
  - Diffusion also has high resistance
  - Avoid using diffusion *runners* for wires!
- **Polysilicon has lower C but high R**
  - Use for transistor gates
  - Occasionally for very short wires between gates
 
# Lumped Element Models

- **Wires are a distributed system**
  - Approximate with lumped element models




- **3-segment  $\pi$ -model is accurate to 3% in simulation**
- **L-model needs 100 segments for same accuracy!**
- **Use single segment  $\pi$ -model for Elmore delay**
 
# Example

---

- **Metal2 wire in 180 nm process**
  - 5 mm long
  - 0.32  $\mu\text{m}$  wide
- **Construct a 3-segment  $\pi$ -model**
  - $R_{\square} = 0.05 \Omega/\square \Rightarrow R = 781 \Omega$
  - $C_{\text{permicron}} = 0.2 \text{ fF}/\mu\text{m} \Rightarrow C = 1 \text{ pF}$




# Wire RC Delay

- Estimate the delay of a 10x inverter driving a 2x inverter at the end of the 5mm wire from the previous example.

- $R = 2.5 \text{ k}\Omega \cdot \mu\text{m}$  for gates

- Unit inverter:  $0.36 \mu\text{m}$  nMOS,  $0.72 \mu\text{m}$  pMOS

- $t_{pd} = 1.1 \text{ ns}$

 




# Crosstalk

---

- **A capacitor does not like to change its voltage instantaneously.**
- **A wire has high capacitance to its neighbor.**
  - When the neighbor switches from 1- $\rightarrow$  0 or 0- $\rightarrow$ 1, the wire tends to switch too.
  - Called capacitive *coupling* or *crosstalk*.
- **Crosstalk effects**
  - Noise on non-switching wires
  - Increased delay on switching wires
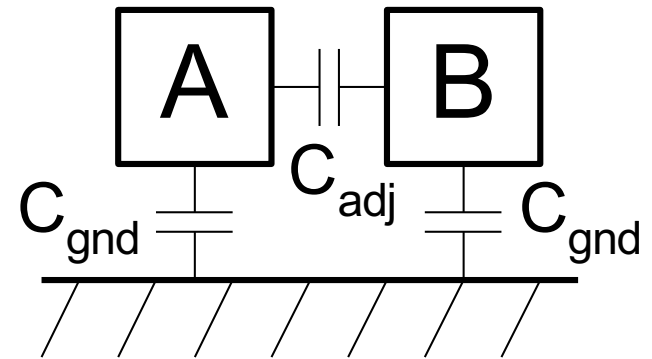
# Crosstalk Delay

- Assume layers above and below on average are quiet
  - Second terminal of capacitor can be ignored
  - Model as  $C_{\text{gnd}} = C_{\text{top}} + C_{\text{bot}}$
- Effective  $C_{\text{adj}}$  depends on behavior of neighbors
  - Miller Coupling Factor (MCF)




B	DV	$C_{\text{eff(A)}}$	MCF
Constant	$V_{\text{DD}}$	$C_{\text{gnd}} + C_{\text{adj}}$	1
Switching with A	0	$C_{\text{gnd}}$	0
Switching opposite A	$2V_{\text{DD}}$	$C_{\text{gnd}} + 2C_{\text{adj}}$	2
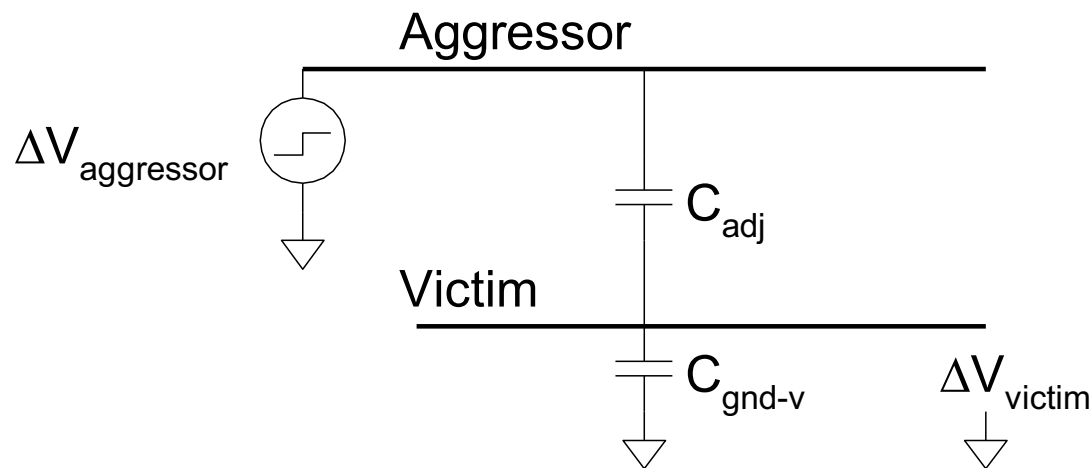
# Crosstalk Noise

- Crosstalk causes [functional/voltage] noise on nonswitching wires
- If victim is floating:
  - model as capacitive voltage divider


$$\Delta V_{victim} = \frac{C_{adj}}{C_{gnd-v} + C_{adj}} \Delta V_{aggressor}$$


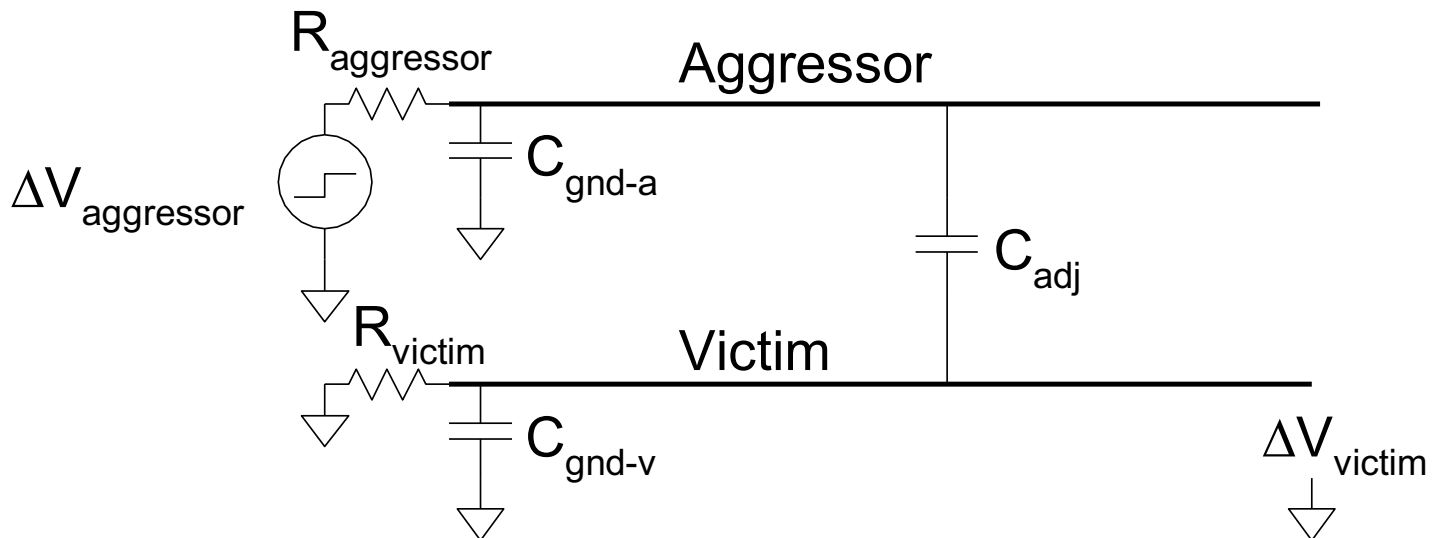
# Driven Victims


- Usually victim is driven by a gate that fights noise
  - Noise depends on relative resistances
  - Victim driver is in linear region, aggressor in saturation
  - If sizes are same,  $R_{aggressor} = 2-4 \times R_{victim}$

$$\Delta V_{victim} = \frac{C_{adj}}{C_{gnd-v} + C_{adj}} \frac{1}{1+k} \Delta V_{aggressor} \quad k = \frac{\tau_{aggressor}}{\tau_{victim}} = \frac{R_{aggressor} (C_{gnd-a} + C_{adj})}{R_{victim} (C_{gnd-v} + C_{adj})}$$


 
# Coupling Waveforms

- Simulated coupling for  $C_{adj} = C_{victim}$



# Noise Implications

---

- **Do we care if we have noise?**
- **If the noise is less than the noise margin, nothing happens**
- **Static CMOS logic will eventually settle to correct output even if disturbed by large noise spikes**
  - **But glitches cause extra delay**
  - **Also cause extra power from false transitions**
- **Dynamic logic never recovers from glitches**
- **Memories and other sensitive circuits also can produce the wrong answer**






# Wire Engineering

- Goal: achieve delay, area, power goals with acceptable noise



- Degrees of freedom:

- Width
- Spacing
- Layer
- Shielding

  
 

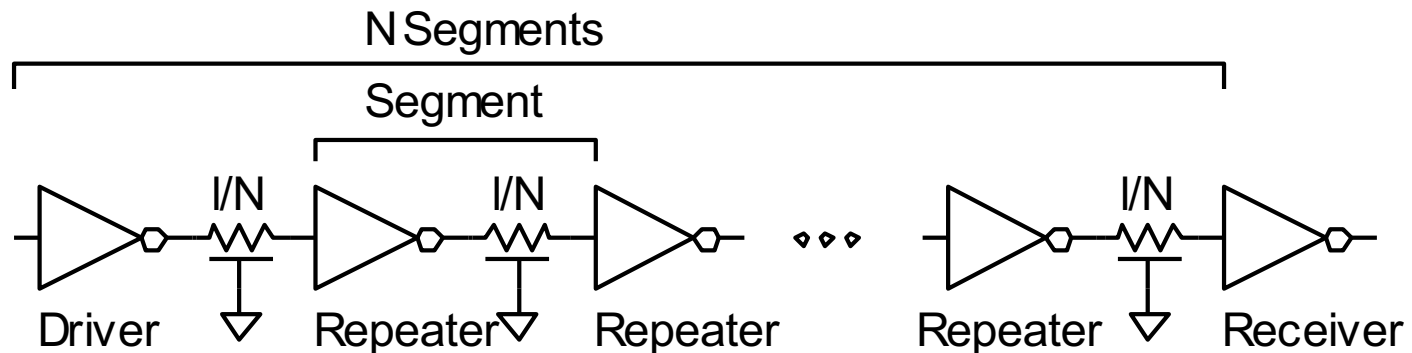 
# Repeaters

- **R and C are proportional to  $L$**
- **RC delay is proportional to  $L^2$** 
  - Unacceptably great for long wires
- **Break long wires into  $N$  shorter segments**
  - Drive each one with an inverter or buffer




# Repeated Interconnect

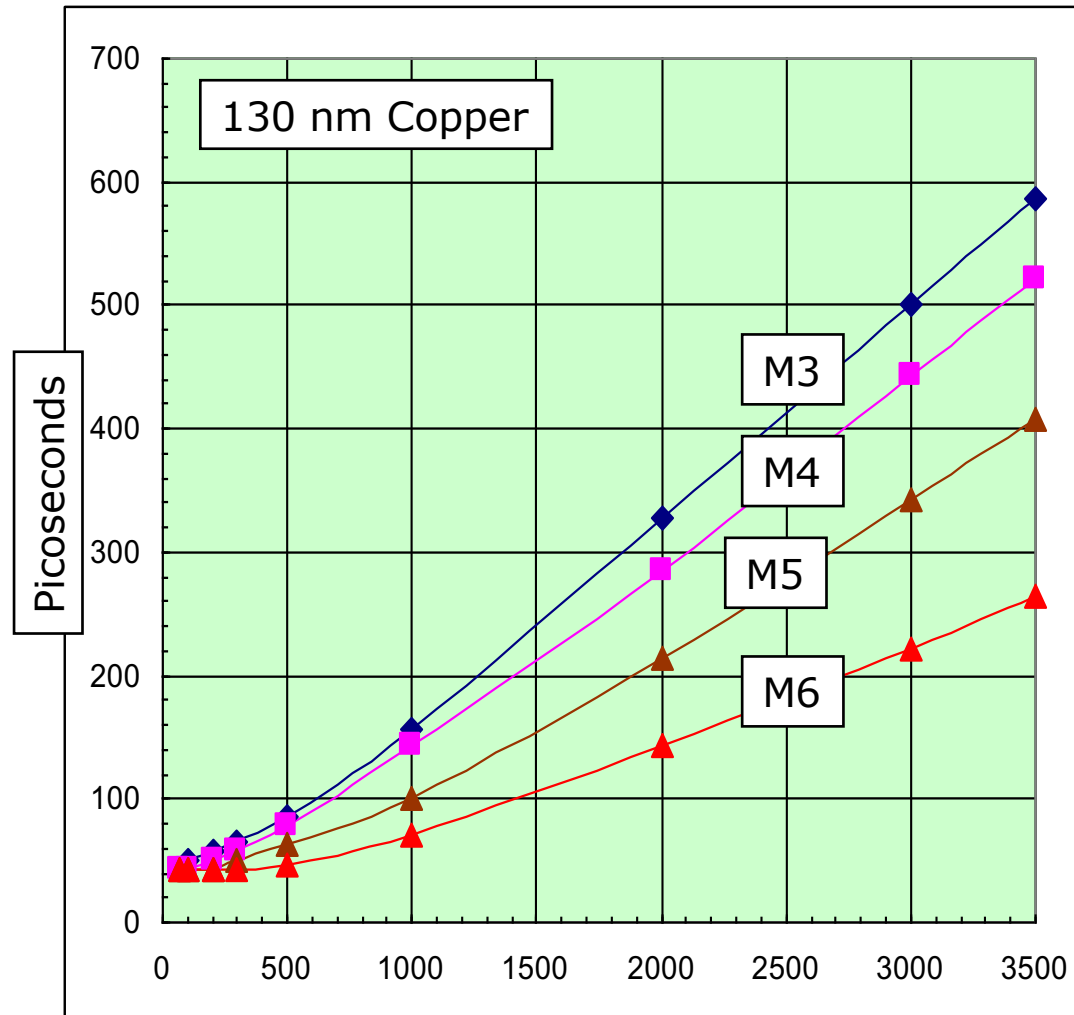 
 
# Repeater Design

- How many repeaters should we use?
- How large should each one be?
- Equivalent Circuit
  - Wire length  $l$ 
    - Wire Capacitance  $C_w * l$  & Resistance  $R_w * l$
  - Inverter width  $W$  (nMOS =  $W$ , pMOS =  $2W$ )
    - Gate Capacitance  $C' * W$  & Resistance  $R/W$



# Repeater Results

- **Write equation for Elmore Delay**
  - Differentiate with respect to  $W$  and  $N$
  - Set equal to 0, solve

$$t_{pd-seg} = \frac{R}{W} \left( \frac{C_w l}{N} + C'W \right) + \left( \frac{R_w l}{N} \right) \left( \frac{C_w l}{2N} + C'W \right)$$

The total delay is  $N$  times greater:

$$t_{pd} = NRC' + L \left( R_w C'W + \frac{RC_w}{W} \right) + L^2 \frac{R_w C_w}{2N}$$

Take the partial derivatives with respect to  $N$  and  $W$  and set them to 0 to minimize delay:

$$\frac{\partial t_{pd}}{\partial N} = RC' - l^2 \frac{R_w C_w}{2N^2} = 0 \Rightarrow N = l \sqrt{\frac{R_w C_w}{2RC'}}$$


~60-80 ps/mm

$$\frac{\partial t_{pd}}{\partial W} = l \left( R_w C' - \frac{RC_w}{W^2} \right) = 0 \Rightarrow W = \sqrt{\frac{RC_w}{R_w C'}}$$


in 180 nm process

# Repeater Placements

---

 

Staggering the inverters

 

Avoiding the Miller cap by opposite going signals

---

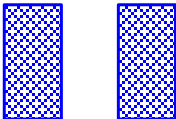
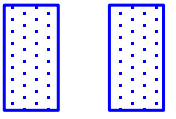
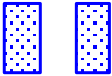
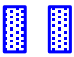
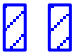

# BACKUP


# Layer Stack

- AMI 0.6  $\mu\text{m}$  process has 3 metal layers
- Modern processes use 6-10+ metal layers
- Example:

Intel 180 nm process

- **M1: thin, narrow ( $< 3\lambda$ )**
  - High density cells
- **M2-M4: thicker**
  - For longer wires
- **M5-M6: thickest**
  - For  $V_{DD}$ , GND, clk

Layer	T (nm)	W (nm)	S (nm)	AR	
6	1720	860	860	2.0	
	1000				
5	1600	800	800	2.0	
	1000				
4	1080	540	540	2.0	
	700				
3	700	320	320	2.2	
	700				
2	700	320	320	2.2	
	700				
1	480	250	250	1.9	
	800				

  
 Substrate