

---


# Lecture 14: Memory Elements

**Mark McDermott**

**Electrical and Computer Engineering  
The University of Texas at Austin**
 
# Memory Elements


- Memory arrays
- SRAMs
- Serial Memories
- Dynamic memories




Pentium-4 (Willamette)

Yellow boxes are memory arrays


# Memory Arrays

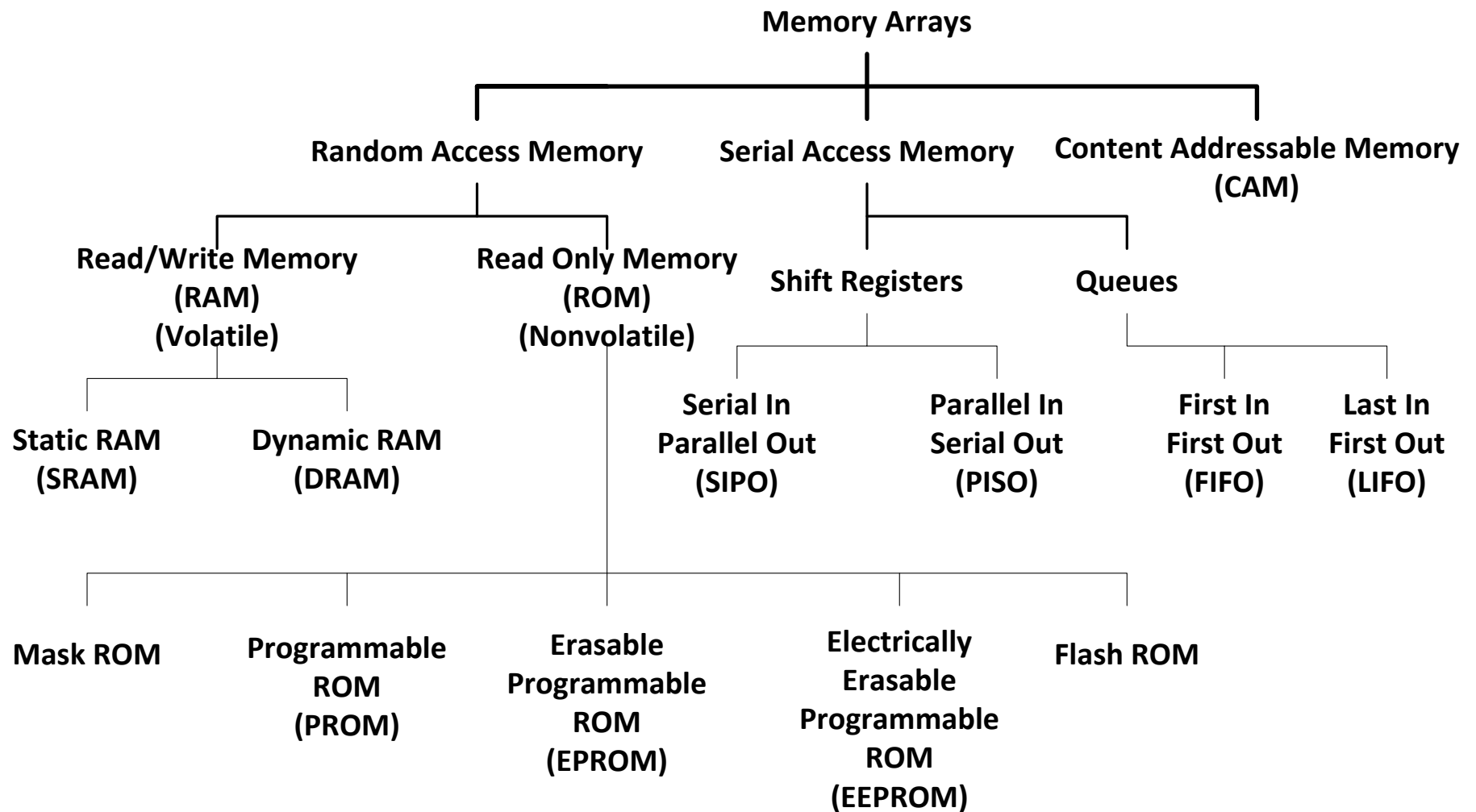

# 1D Memory Architecture

 

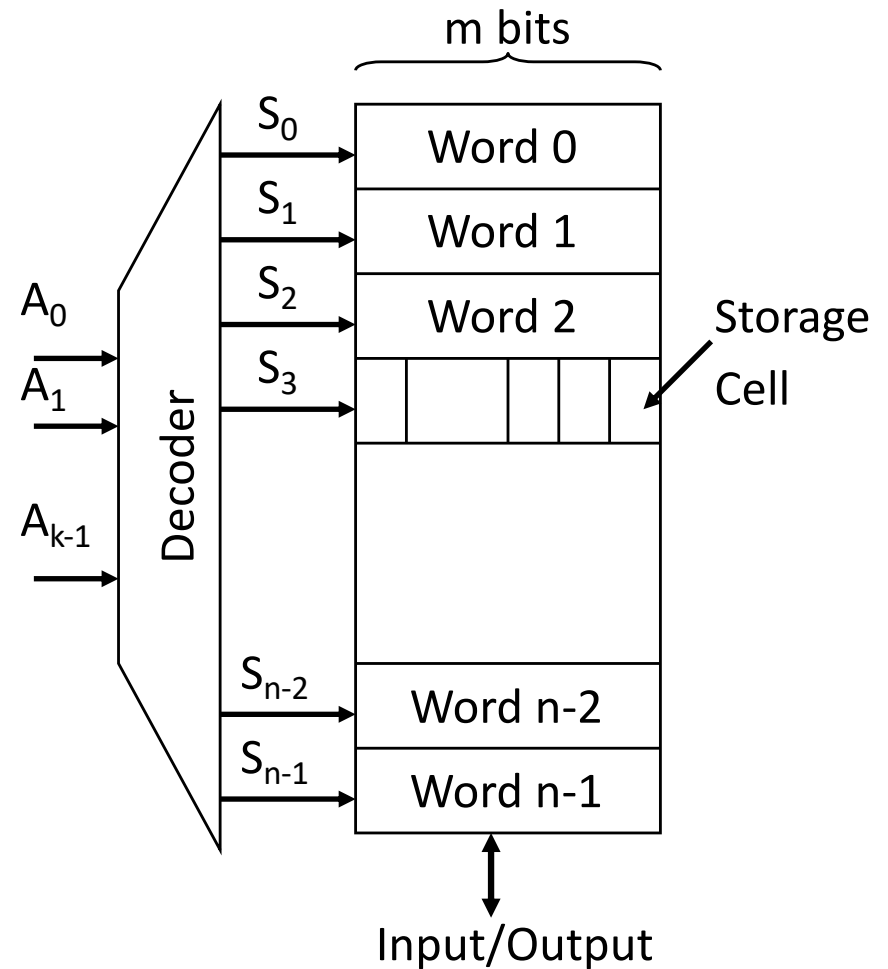
$n$  words  $\rightarrow$   $n$  select signals



Decoder reduces # of inputs


$$k = \log_2 n$$

# 2D Memory Architecture

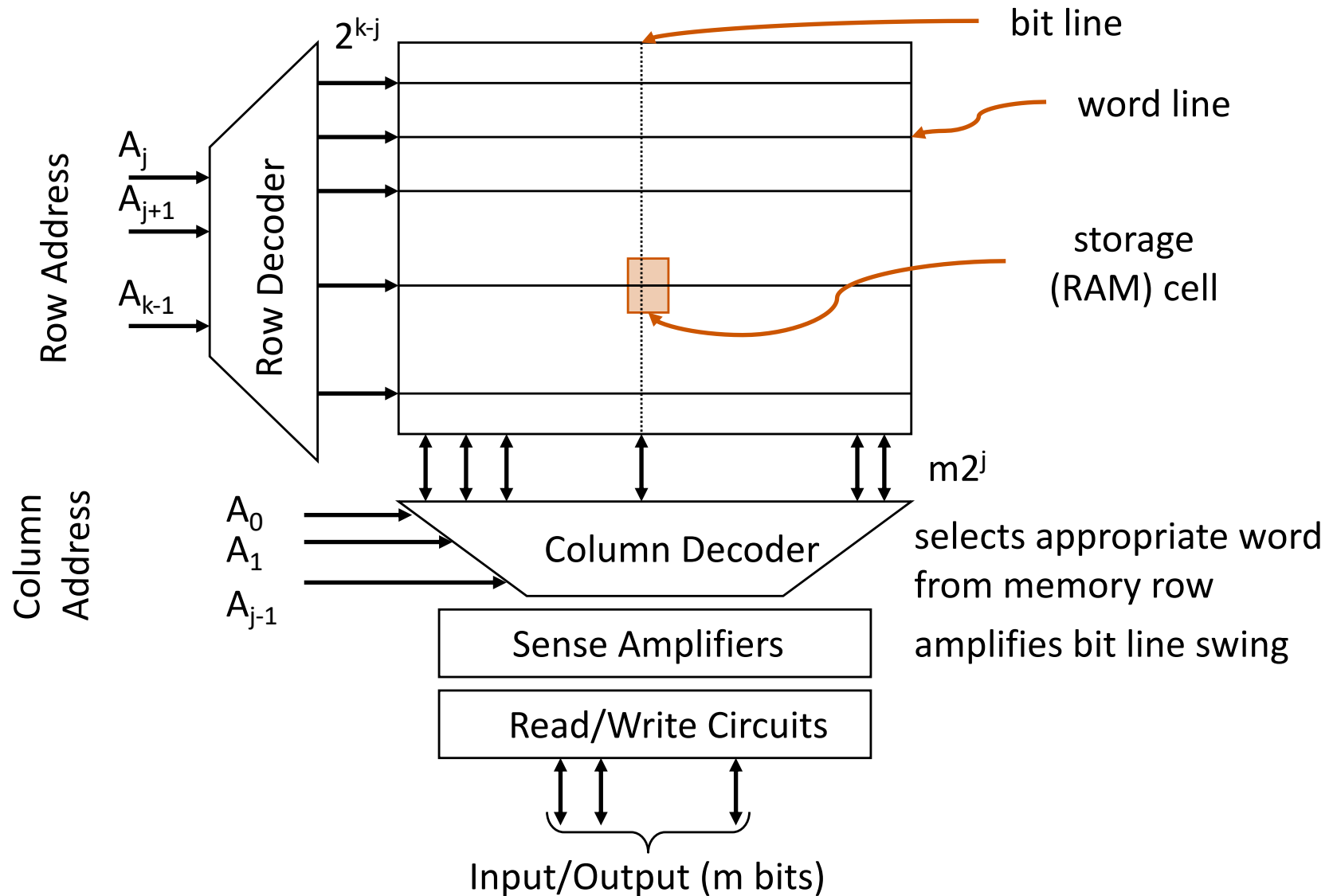

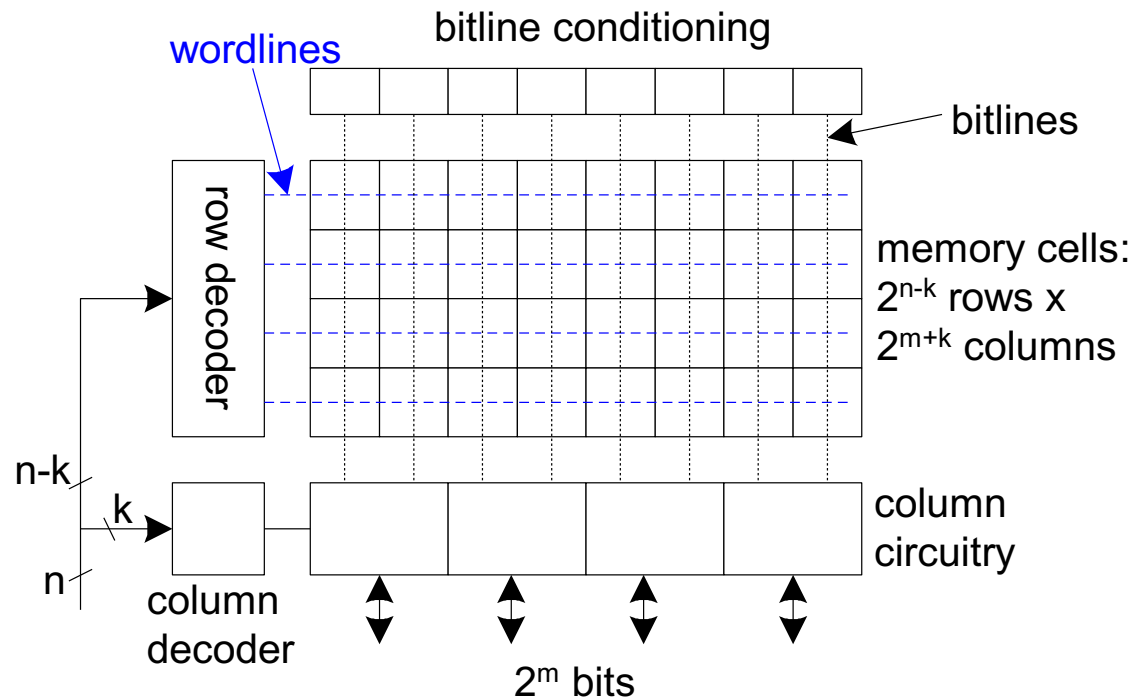
# Array Architecture

- $2^n$  words of  $2^m$  bits each
- If  $n \gg m$ , fold by  $2^k$  into fewer rows of more columns




- Good regularity – easy to design
- Very high density if good cells are used

# SRAM Block Diagram

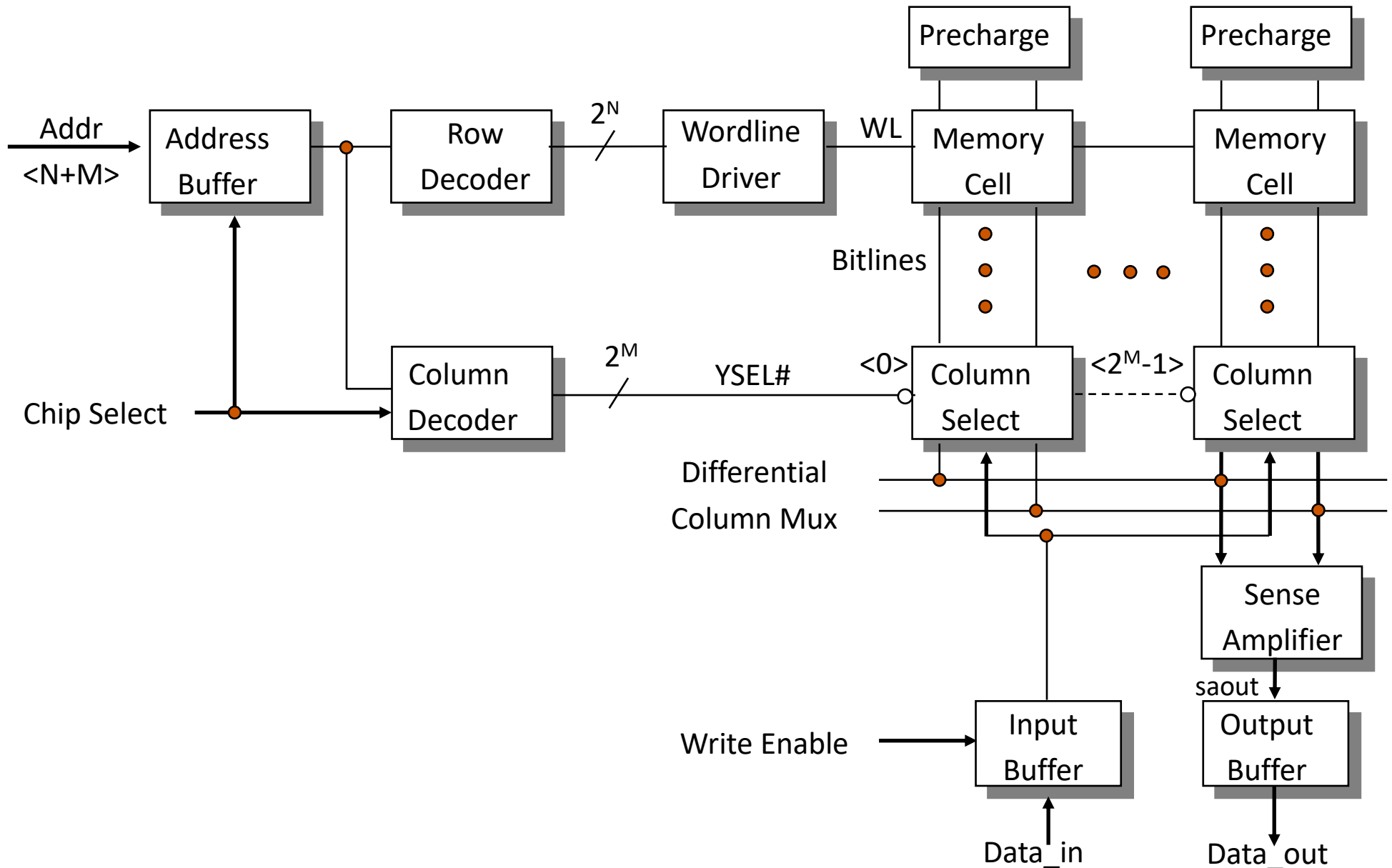


# SRAM Simulation Cross Section

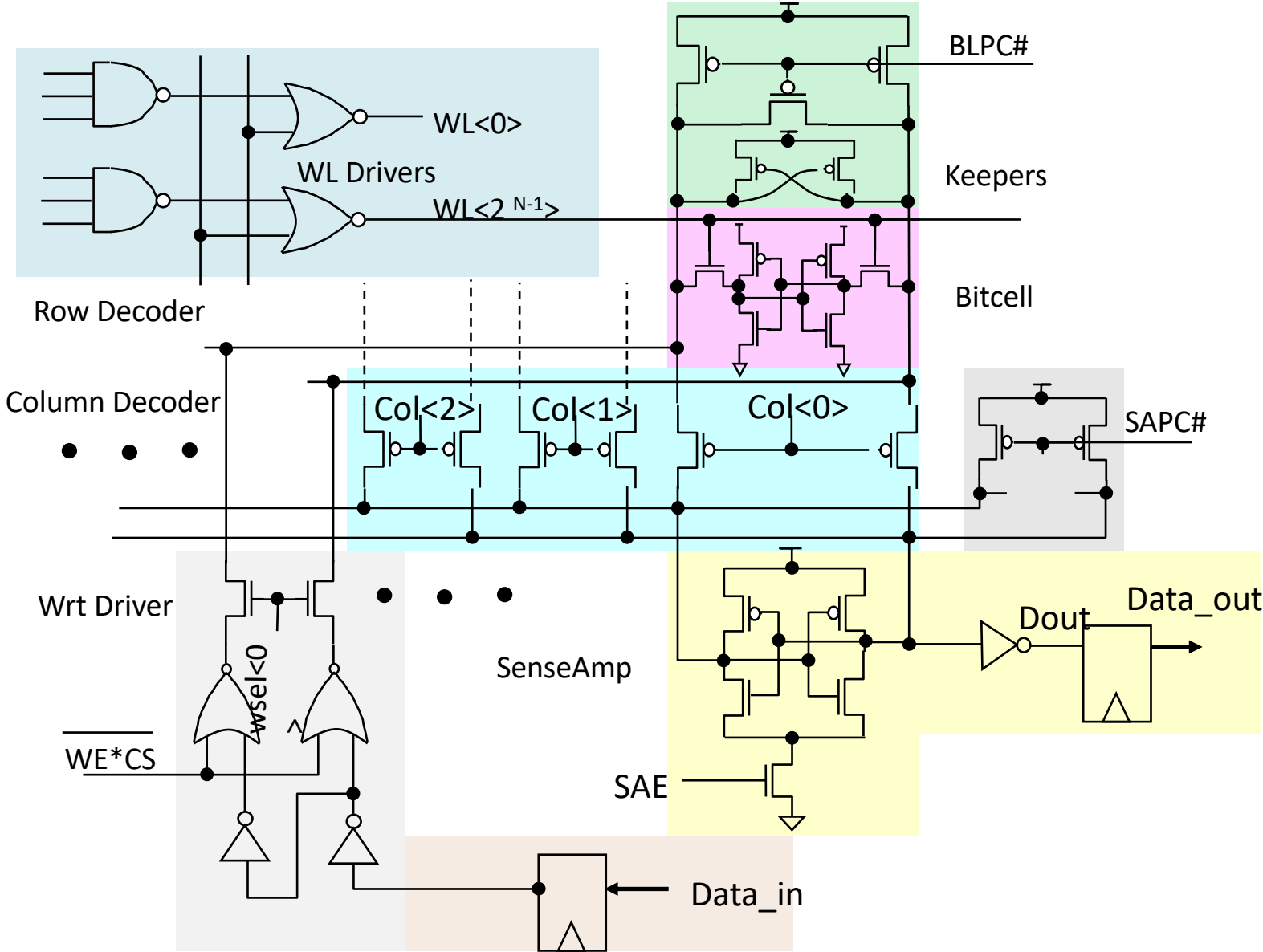



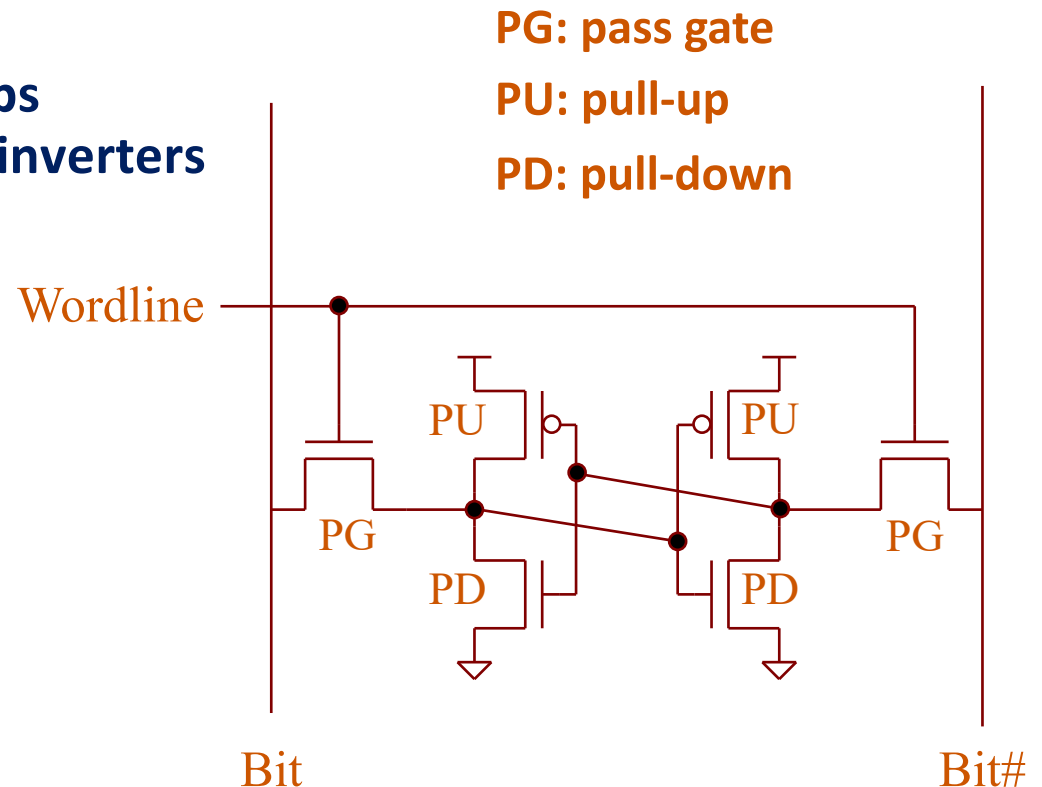
# 6T SRAM Cell

- **Cell size accounts for most of array size**
  - Reduce cell size at expense of complexity
- **6T SRAM Cell**
  - Used in most commercial chips
  - Data stored in cross-coupled inverters
- **Read:**
  - Precharge bit, bit\_b
  - Raise wordline
- **Write:**
  - Drive data onto bit, bit\_b
  - Raise wordline



# Moore's Law Scaling for Memory

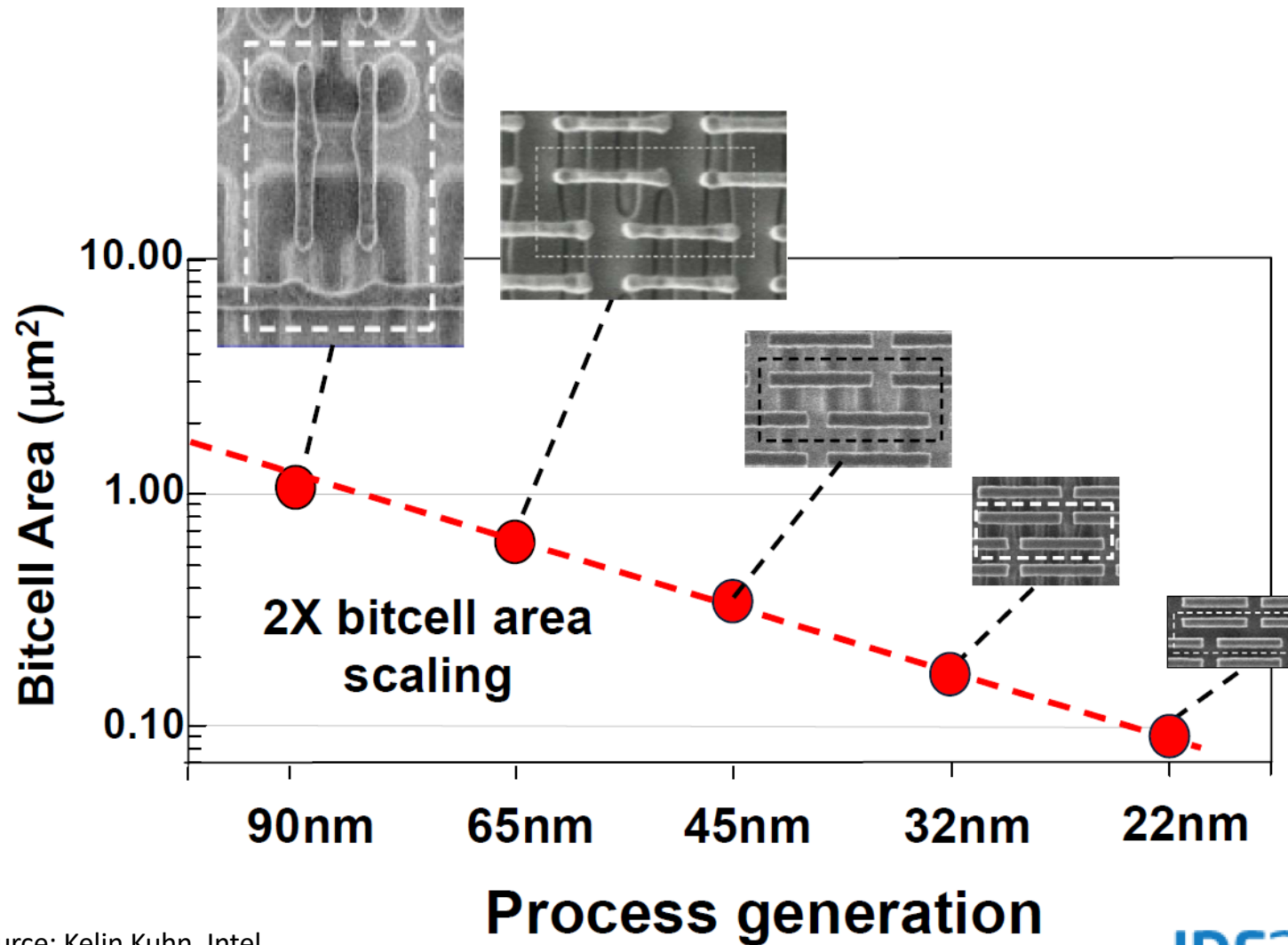


Source: Kelin Kuhn, Intel

IDF2011

# SRAM Memory Cell Improvements

---


22 nm Process

 

$.108 \text{ } \mu\text{m}^2$

(Used on CPU products)

14 nm Process


 


$.0588 \text{ } \mu\text{m}^2$

(0.54x area scaling)

 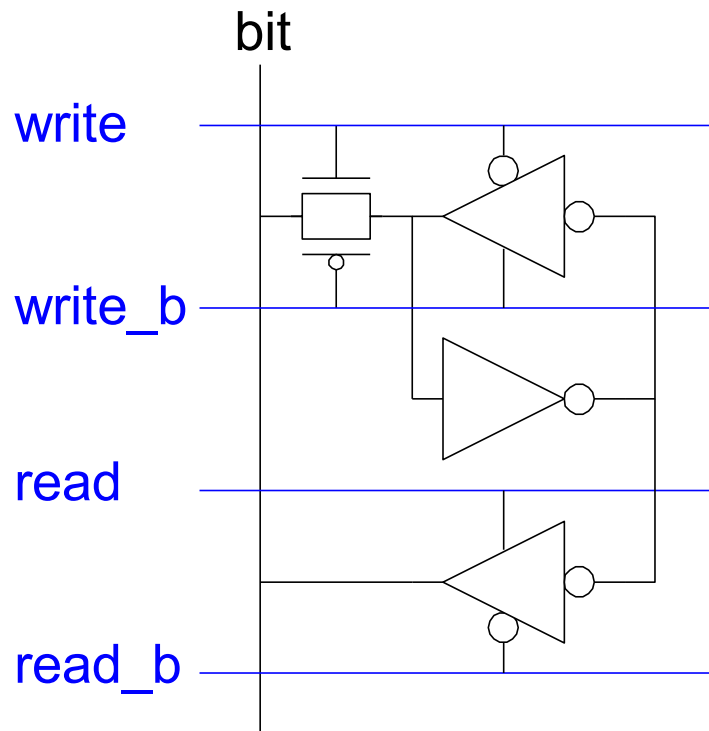
# 12T SRAM Cell

- **Basic building block: SRAM Cell**
  - Holds one bit of information, like a latch
  - Must be read and written
- **12-transistor (12T) SRAM cell**
  - Use a simple latch connected to bitline
  - $46 \times 75 \lambda$  unit cell



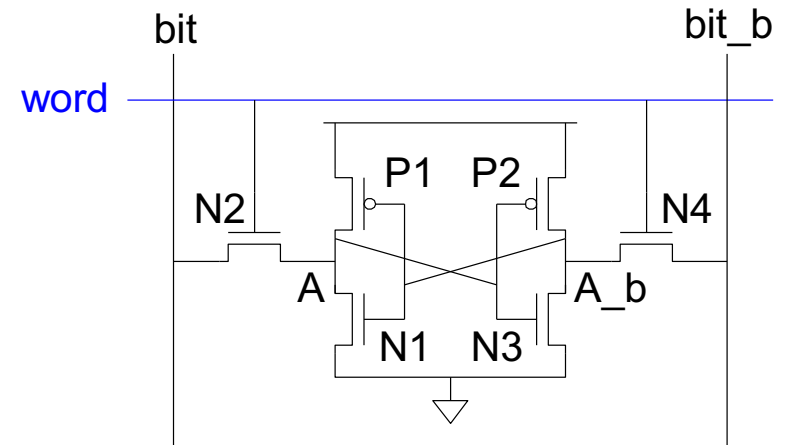
# SRAM Read

- Improve performance when bit-line capacitance is high
- Precharge both bitlines high
- Then turn on wordline
- One of the two bitlines will be pulled down by the cell




- Ex:  $A = 0, A_b = 1$ 
  - bit discharges, bit\_b stays high
  - But A bumps up slightly

 - **Read stability**
  - A must not flip
  - $N1 \gg N2$




# Read Timing

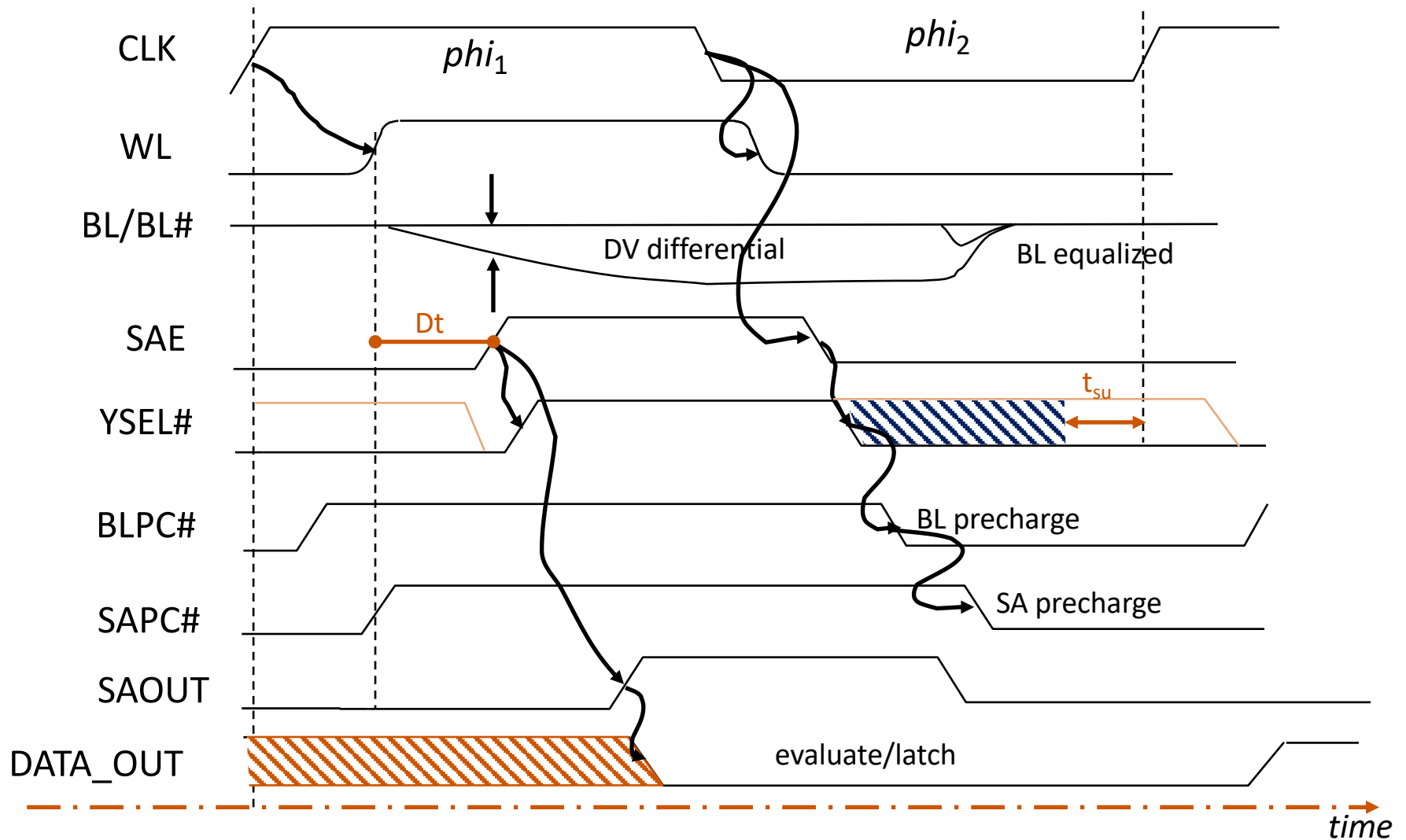
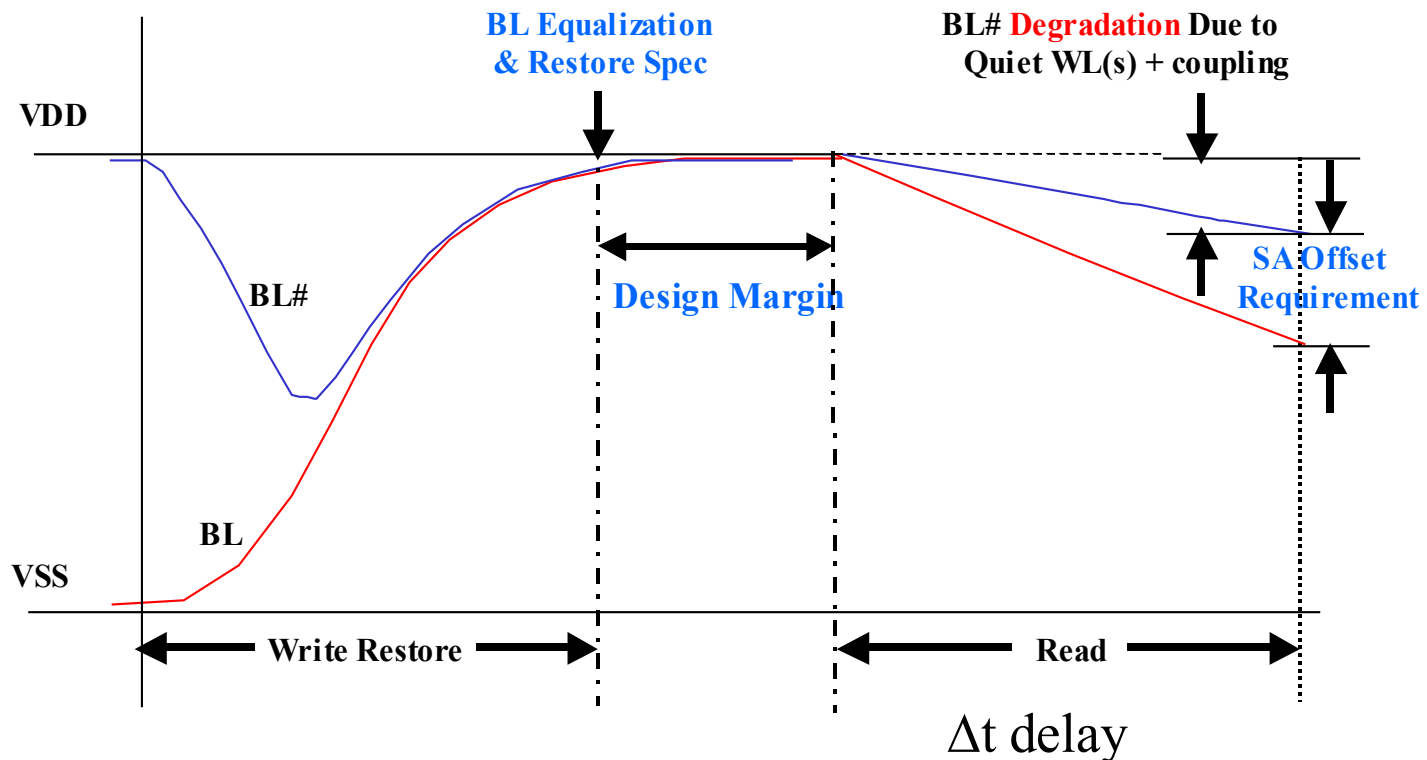
# Read Requirements

- Pre-charge & equalize bit-lines from previous cycle
- Minimum “Design Margin” before next READ begins
- Delay requirement to allow sufficient bit-line voltage development





- NOTE: The  $\Delta t$  delay can be generated by a chain of inverter delays or by replica “dummy” row and column composed of bitcells.

# SRAM Write

- Drive one bitline high, the other low
- Then turn on wordline
- Bitlines overpower cell with new value


- Ex:  $A = 0$ ,  $A_b = 1$ ,  
 $bit = 1$ ,  $bit_b = 0$ 
  - Force  $A_b$  low,  
then  $A$  rises high

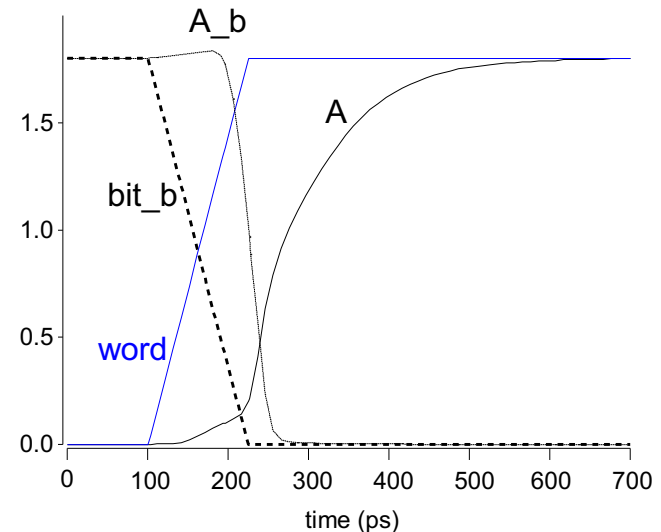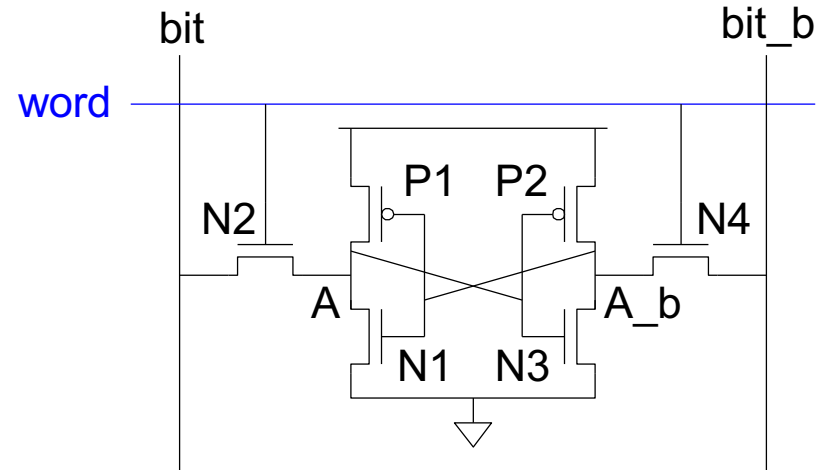- **Writability**
  - Must overpower feedback inverter
  - $N4 \gg P2$
  - $N2 \gg P1$  (symmetry)






# Write Timing

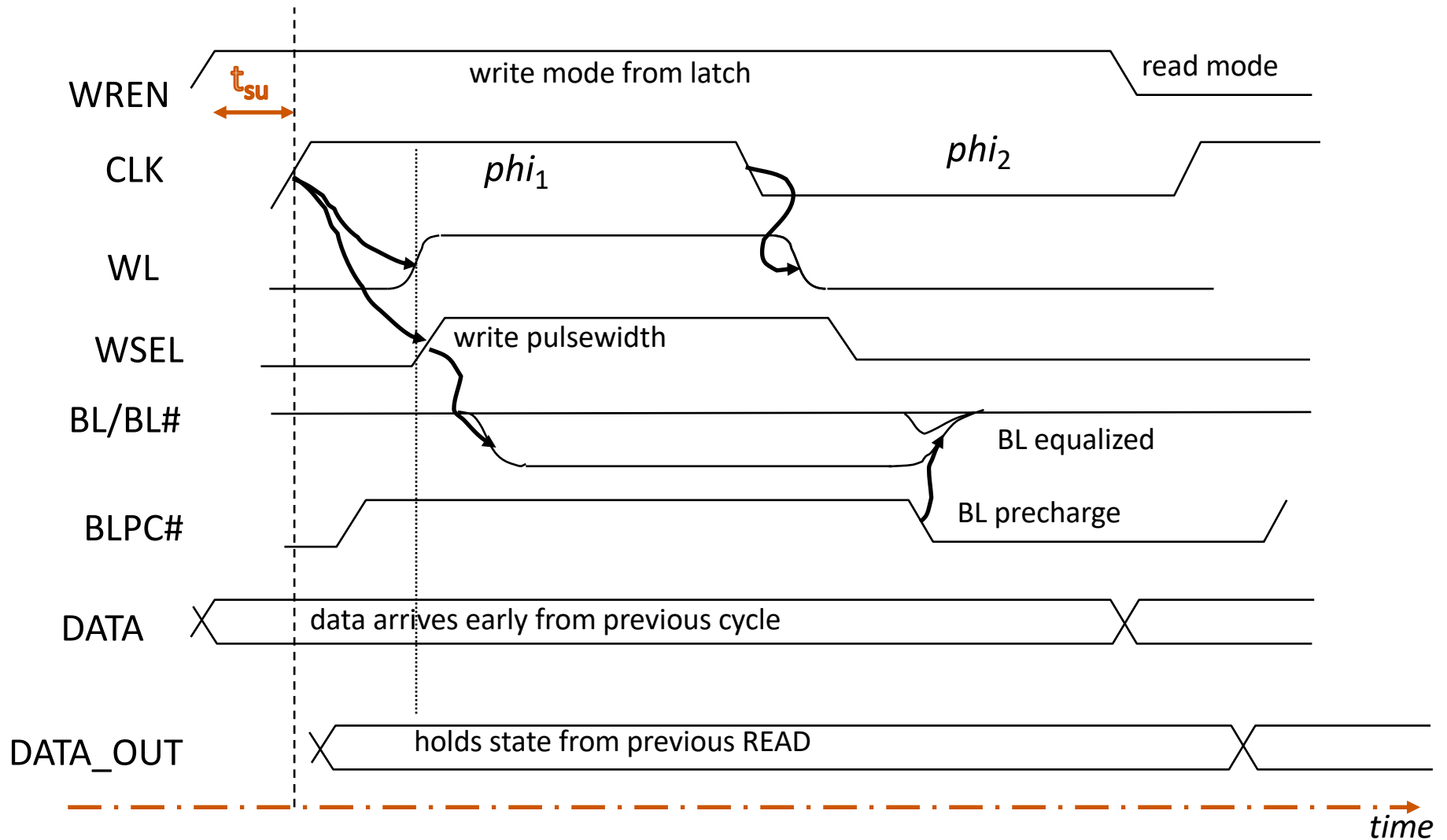
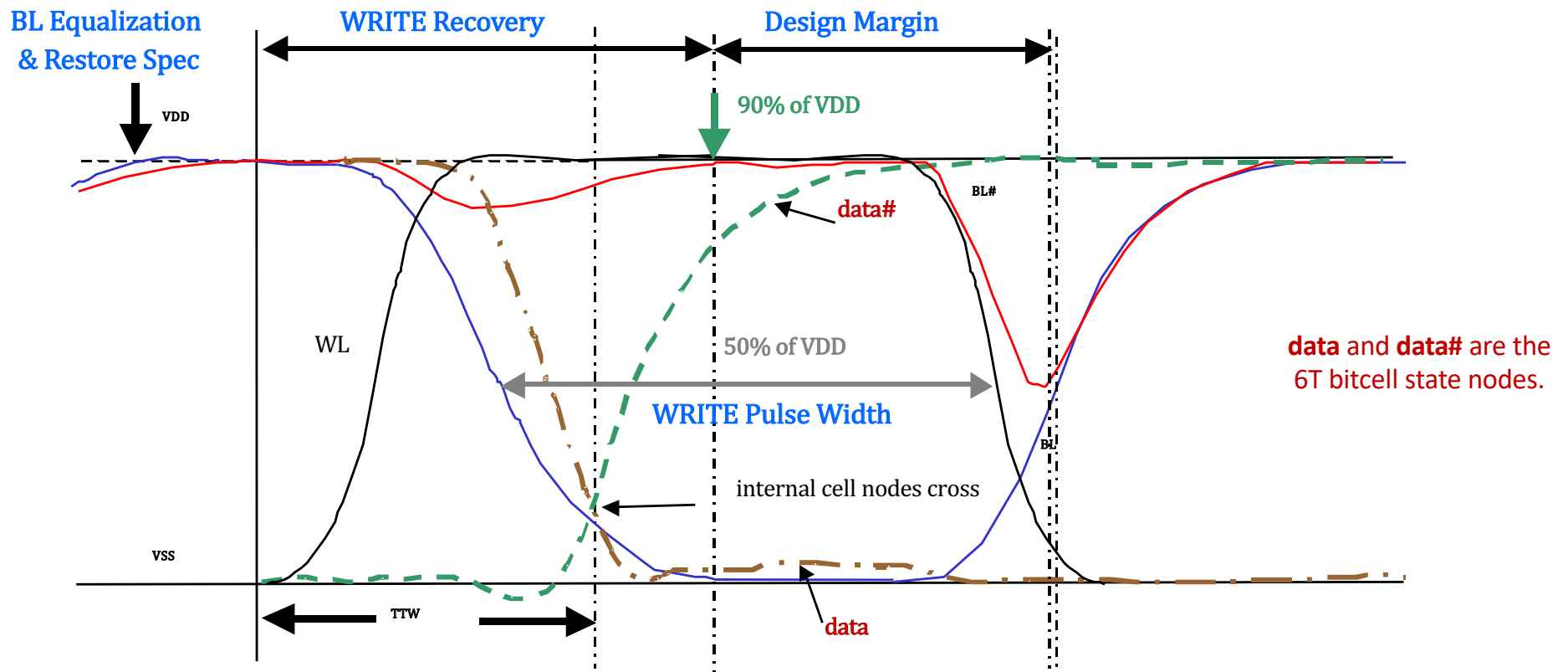
# Write Requirements


- Pre-charge & equalize bit-lines from previous cycle
- WRITE can begin as soon as word-line is available
- Must guarantee minimum write pulse-width, data valid time and write recovery; internal “high node” reaches say 90% of VDD



- **NOTE: Write pulse-width margin increases with lower frequency**
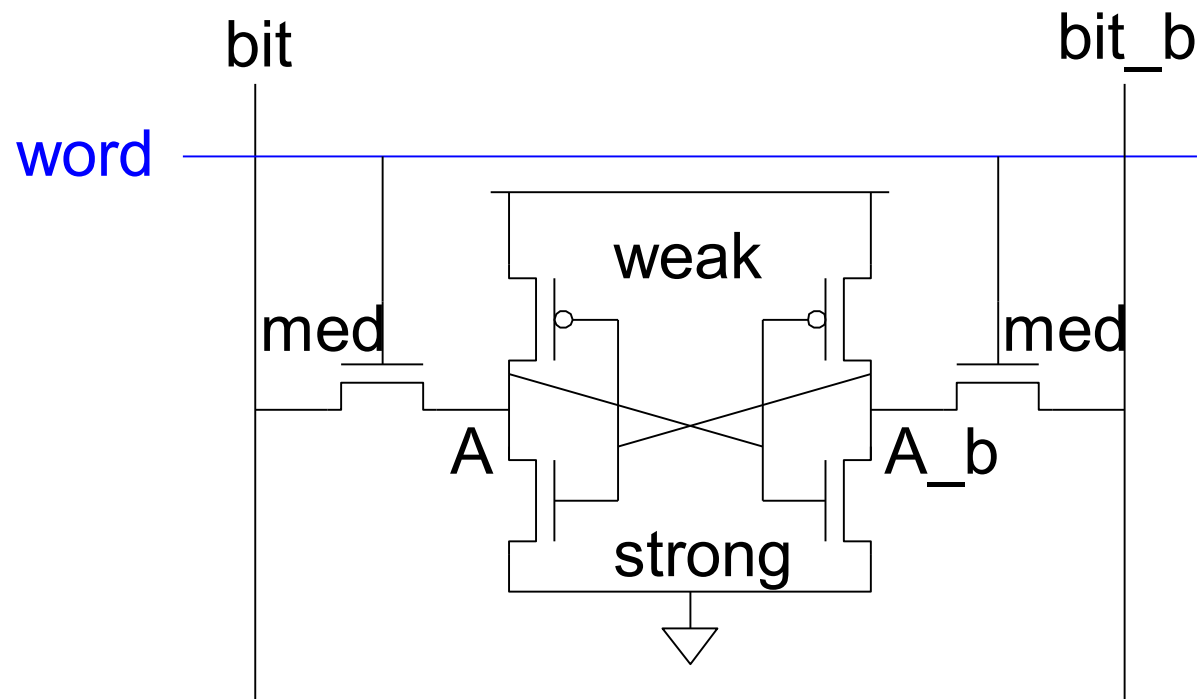
# SRAM Sizing

- High bitlines must not overpower inverters during reads
- But low bitlines must write new value into cell




**$W_{dn} > W_{pass}$  for read stability**

**$W_{pass} > W_{up}$  to enable writes**

# 6-Transistor SRAM Cell Layout

transistor	LEFT	RIGHT
PG	1.00	1.00
PD	1.38	1.38
PU	0.44	0.44

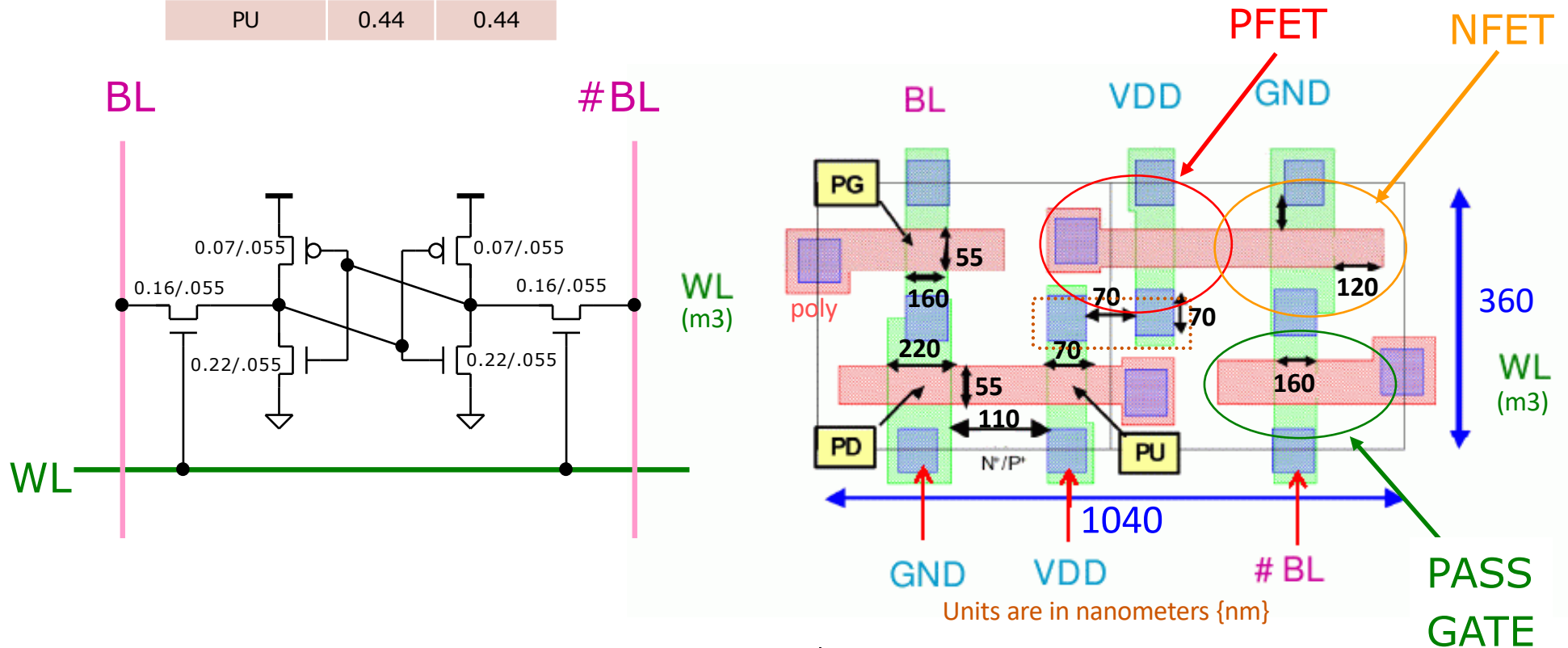



In 45nm CMOS, a typical 6T bit-cell area =  $0.38 \mu\text{m}^2$





# Decoders

- **$n:2^n$  decoder consists of  $2^n$  n-input AND gates**
  - One needed for each row of memory
  - Build AND from NAND or NOR gates

## Static CMOS

  


## Pseudo-nMOS

  

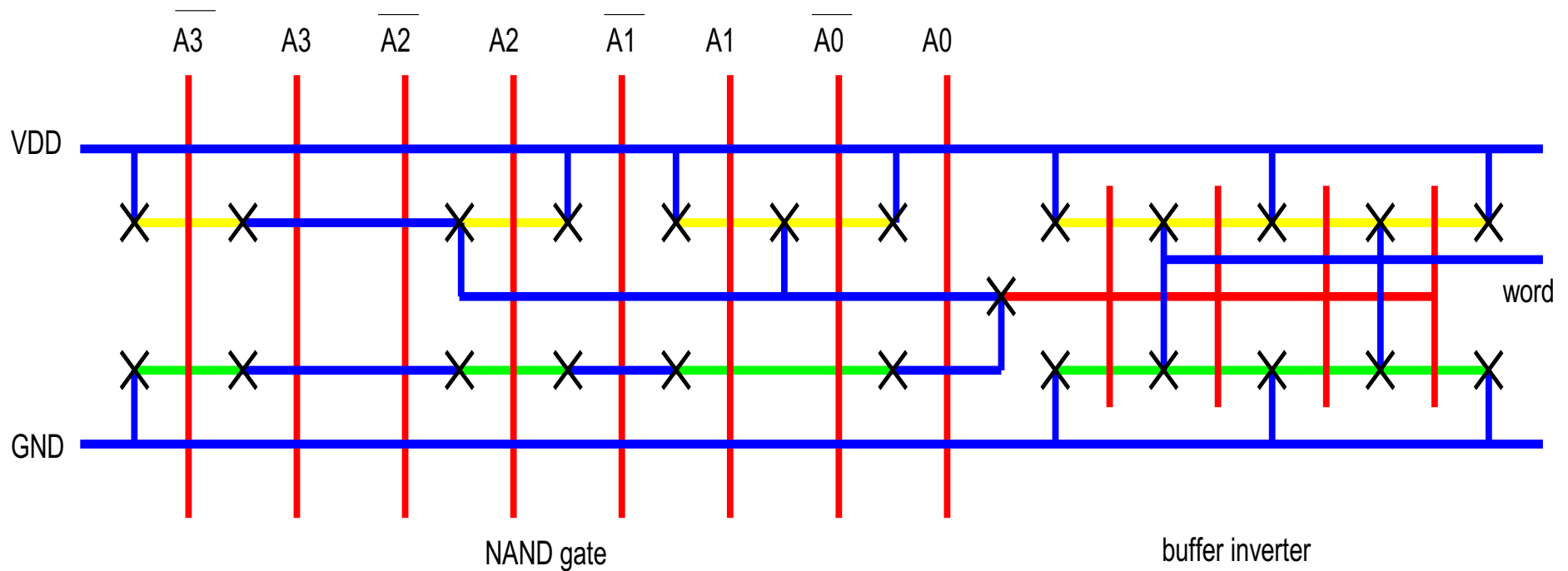
# Decoder Layout

- Decoders must be pitch-matched to SRAM cell
  - Requires very skinny gates


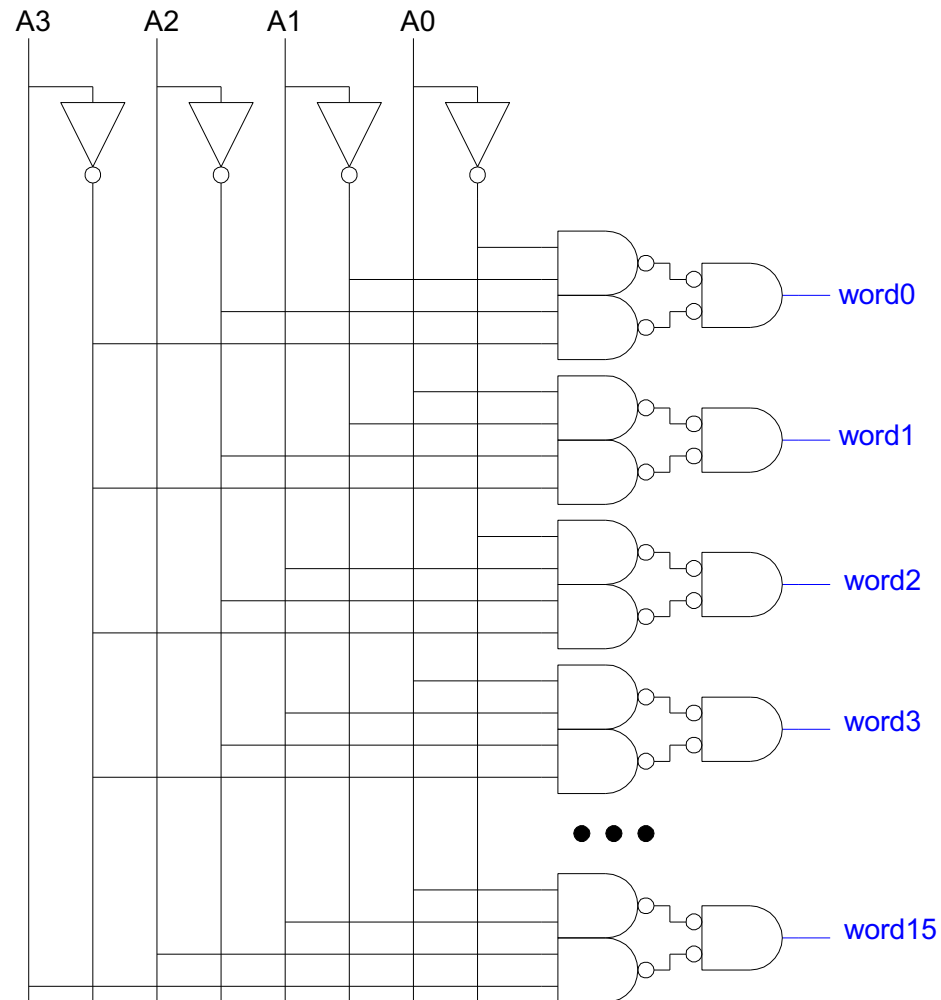
# Large Decoders


- For  $n > 4$ , NAND gates become slow
  - Break large gates into multiple smaller gates


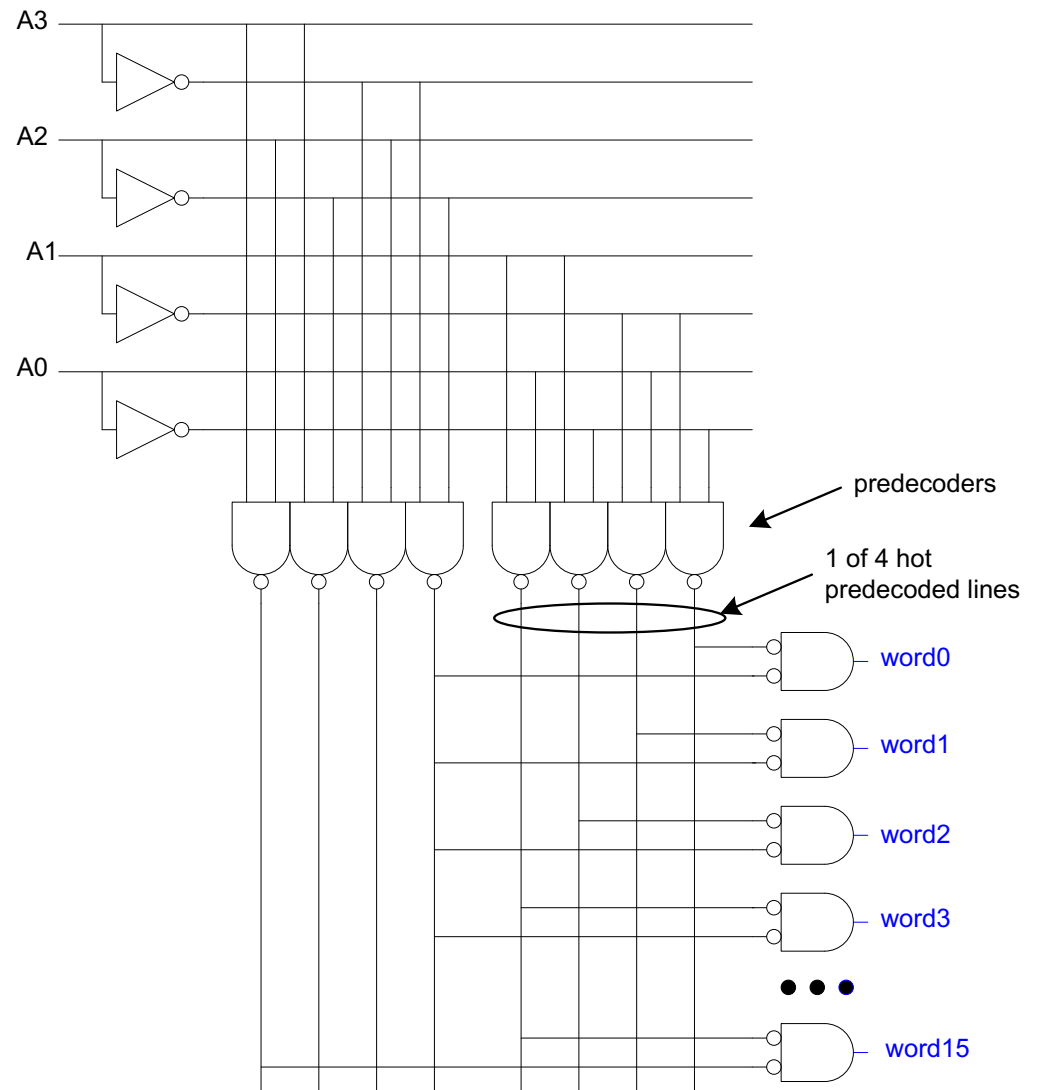
# Predecoding

- **Many of these gates are redundant**


- Factor out common gates into pre-decoder
- Saves area
- Same path effort






 
# Column Circuitry

- **Some circuitry is required for each column**
  - Bitline conditioning
  - Sense amplifiers
  - Column multiplexing



  
# Bitline Conditioning

- Precharge bitlines high before reads
- Equalize bitlines to minimize voltage difference when using sense amplifiers


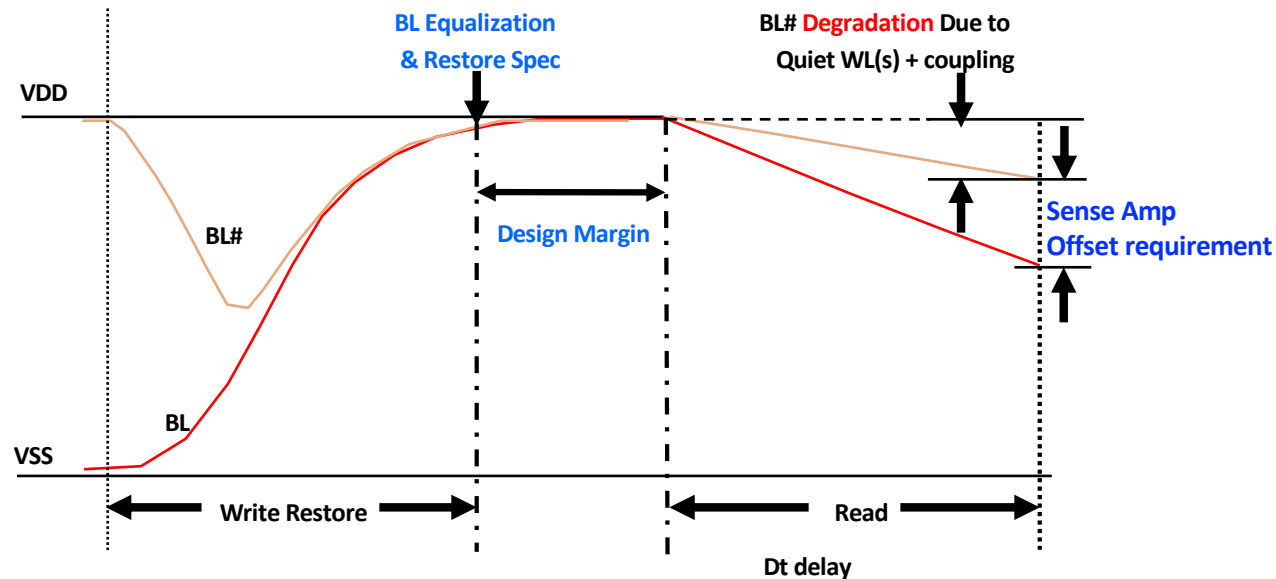
# Sense Amplifiers


- **Bitlines have many cells attached**
  - Ex: 32-kbit SRAM has 256 rows x 128 cols
  - 128 cells on each bitline
- **$t_{pd} \propto (C/I) \Delta V$** 
  - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
  - Discharged slowly through small transistors (small I)
- **Sense amplifiers are triggered on small voltage swing (reduce  $\Delta V$ )**


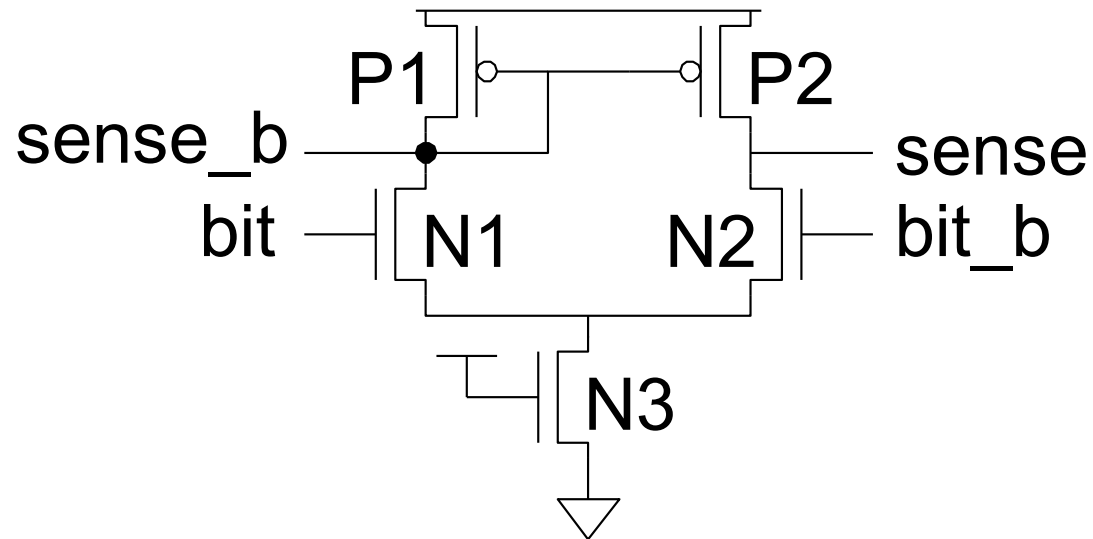
# Differential Pair Amp


---

- Differential pair requires no clock
- But always dissipates static power



 
# Clocked Sense Amp

- Clocked sense amp saves power
- Requires timing the sense\_clk signal to arrive after enough bitline swing
- Isolation transistors cut off large bitline capacitance


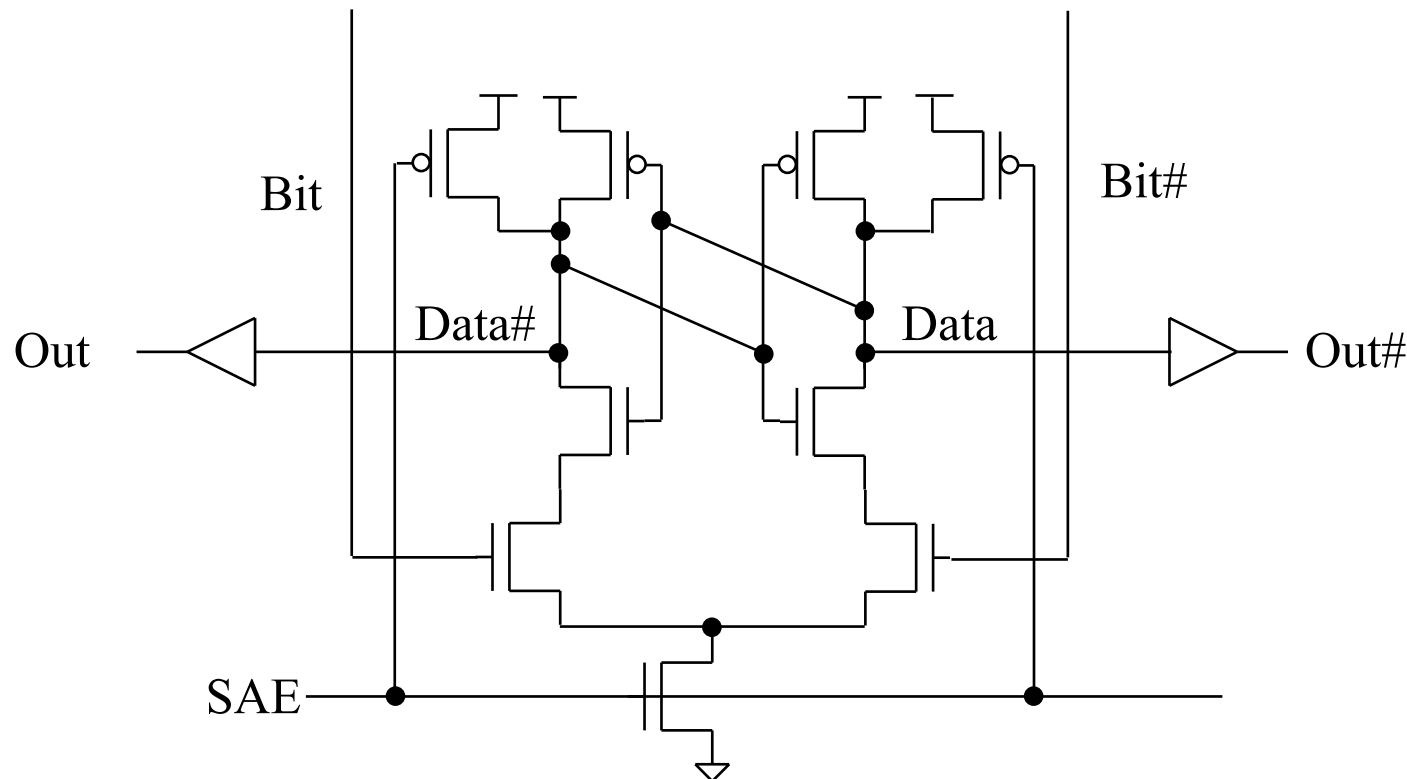
# De-coupled Sense Amplifier


- With SAE low; Data and Data# are pre-charge high
- When SAE goes high; source-coupled pair acts as differential amplifier
- Cross coupled inverters amplify and latch any voltage difference


 
# Twisted Bitlines


---

- **Sense amplifiers also amplify noise**
  - Coupling noise is severe in modern processes
  - Try to couple equally onto bit and bit\_b (common mode)
  - Done by twisting bitlines


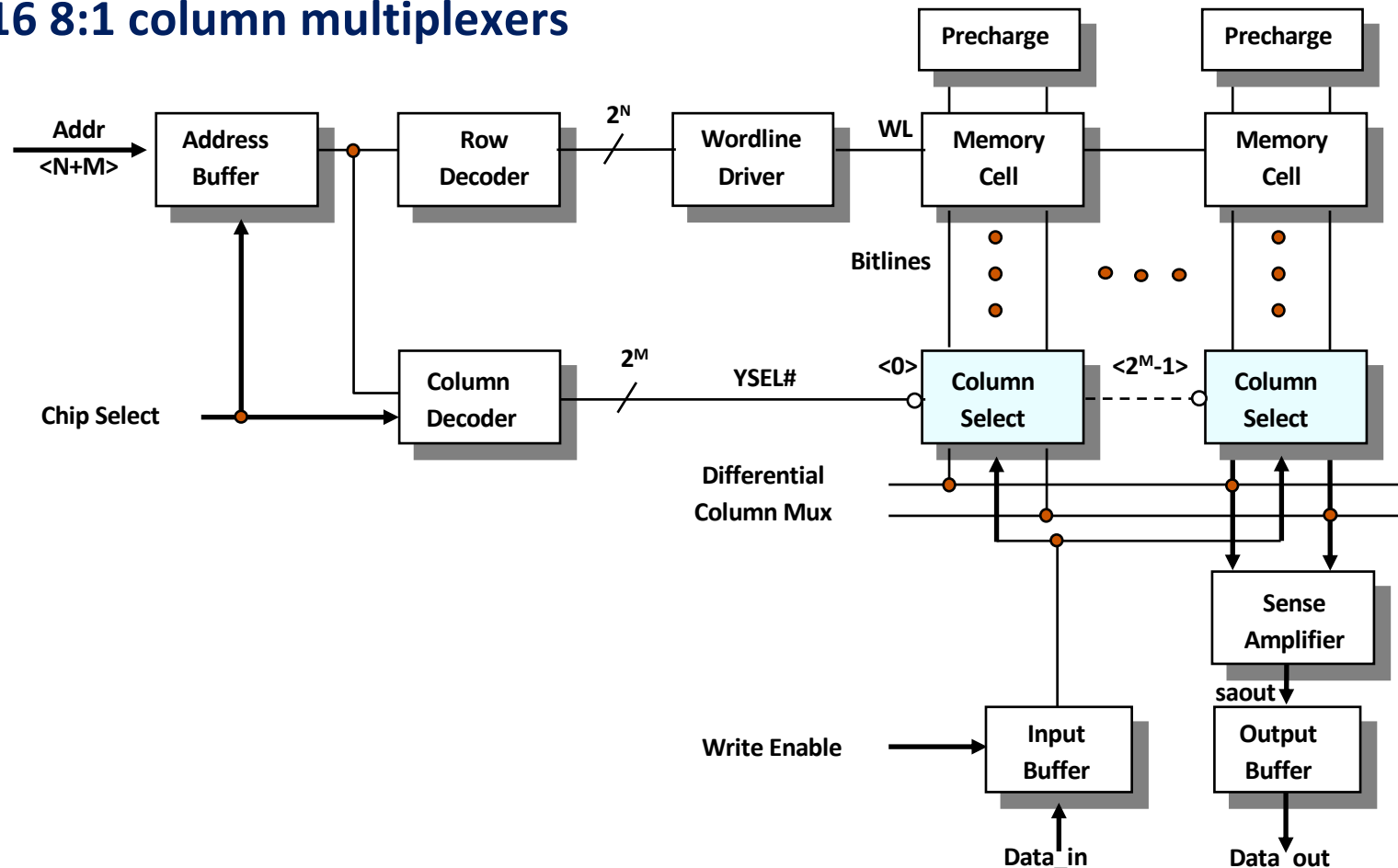
# Column Multiplexing


- Recall that array may be folded for good aspect ratio
- Ex: 2 kword x 16 folded into 256 rows x 128 columns
  - Must select 16 output bits from the 128 columns
  - Requires 16 8:1 column multiplexers





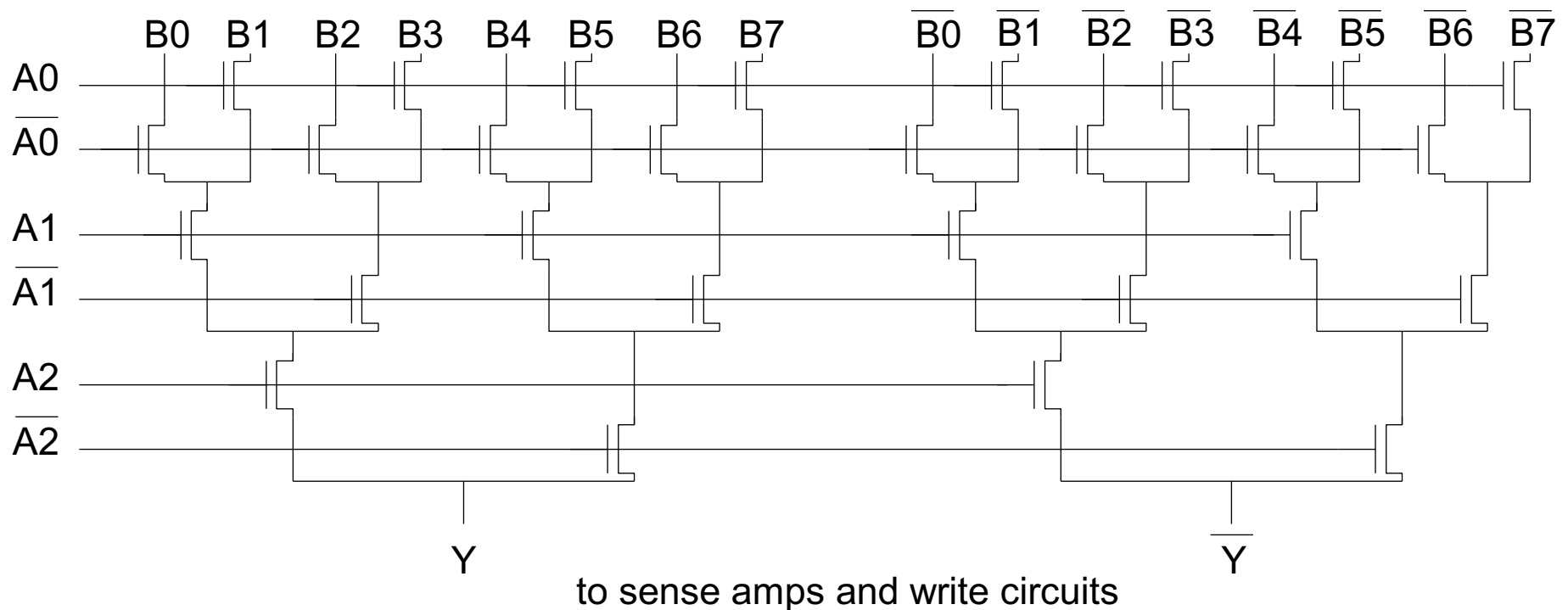
# Tree Decoder Mux

- **Column mux can use pass transistors**
  - Use nMOS only, precharge outputs
- **One design is to use k series transistors for 2k:1 mux**
  - No external decoder logic needed



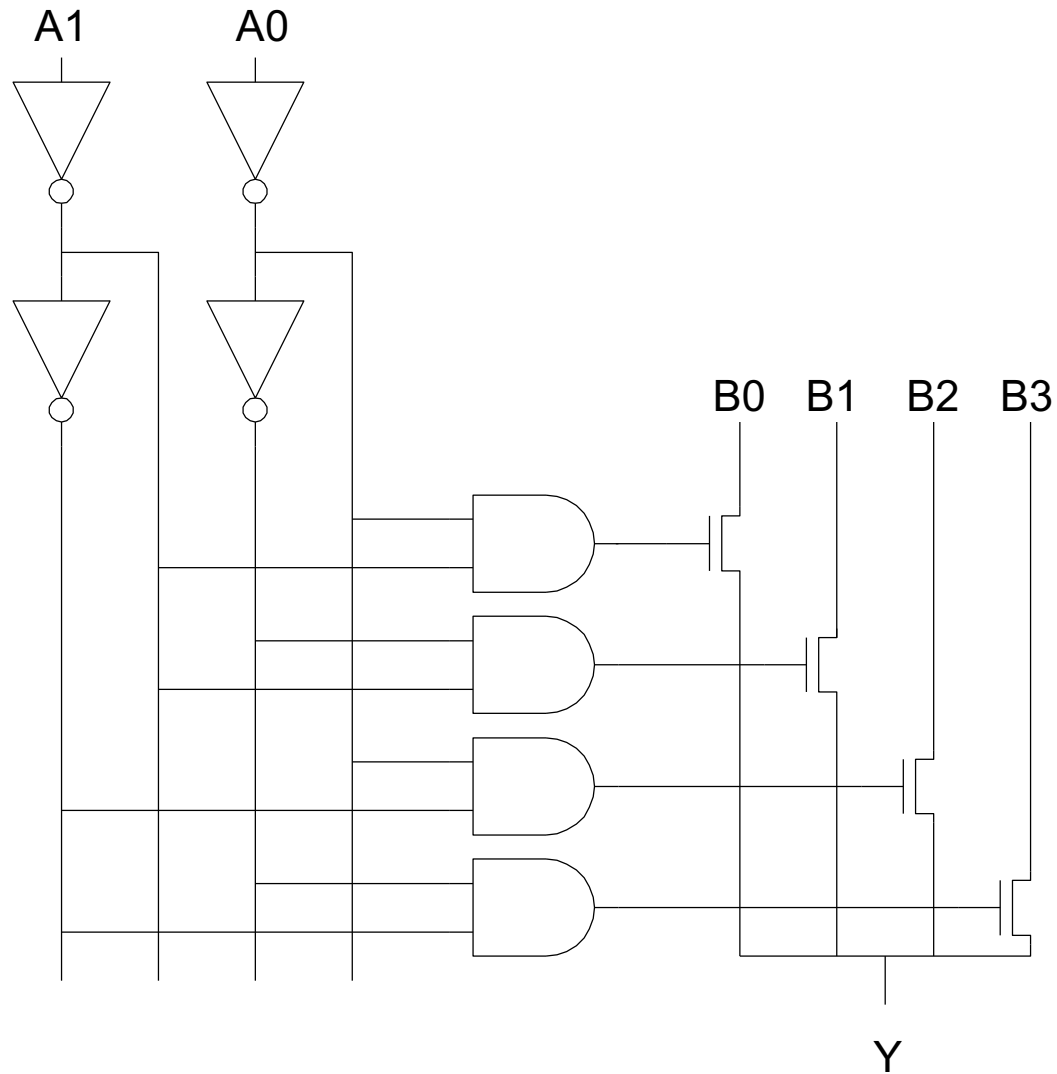
# Single Pass-Gate Mux

- Or eliminate series transistors with separate decoder



# Ex: 2-way Muxed SRAM

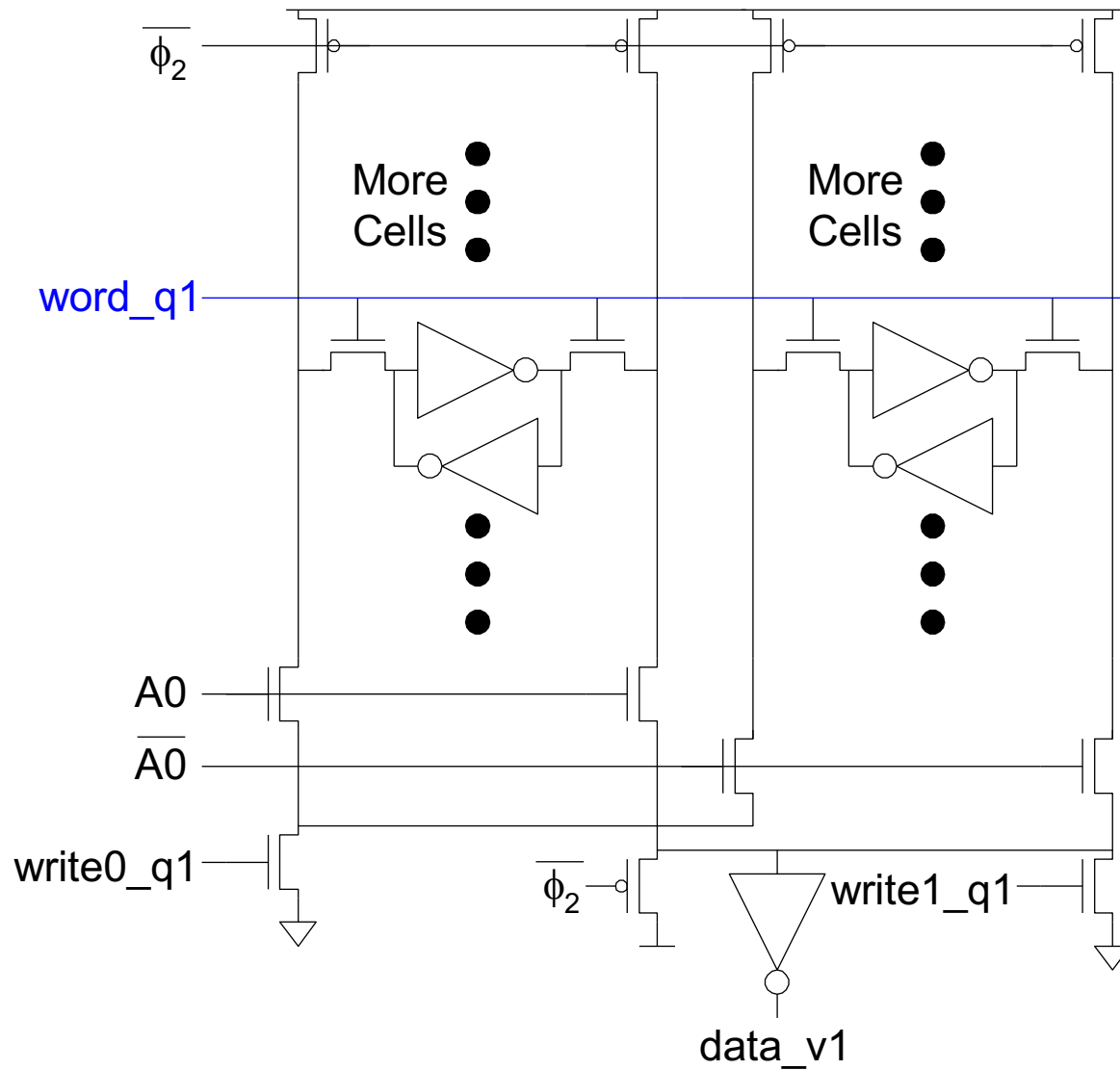


# Multiple Ports

---

- **We have considered single-ported SRAM**
  - One read or one write on each cycle
- ***Multiported* SRAM are needed for register files**
- **Examples:**
  - Multicycle MIPS must read two sources or write a result on some cycles
  - Pipelined MIPS must read two sources and write a third result each cycle
  - Superscalar MIPS must read and write many sources and results each cycle
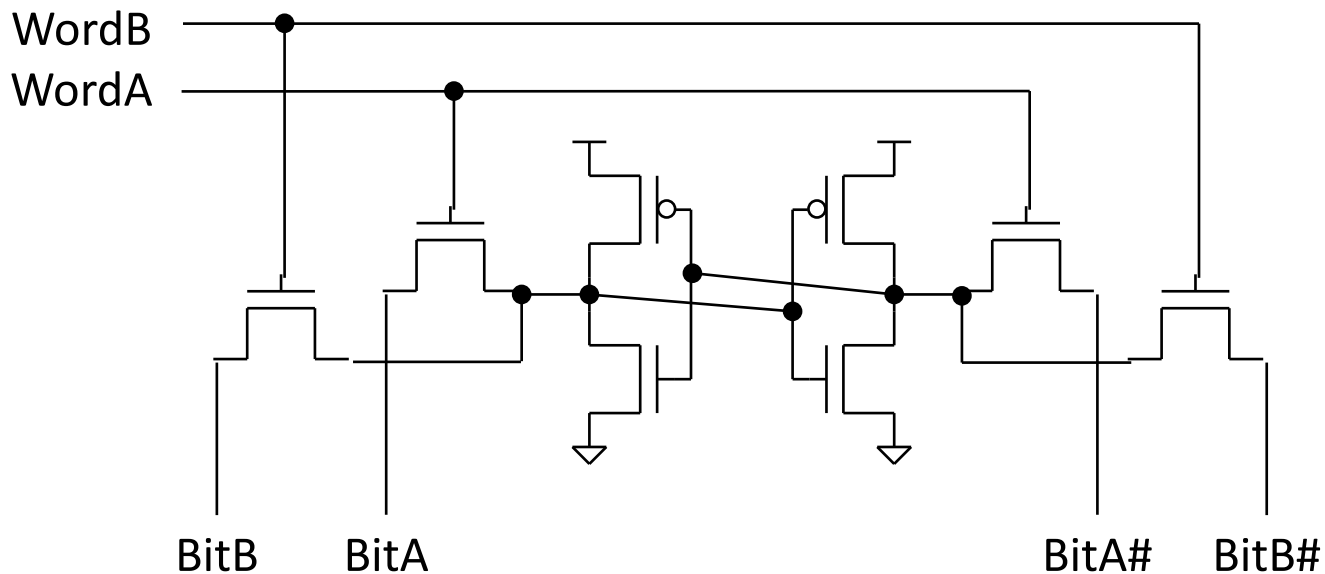
# Dual-Ported SRAM


- **Simple dual-ported SRAM**
  - Two independent single-ended reads
  - Or one differential write




- **Do two reads and one write by time multiplexing**
  - Read during ph1, write during ph2
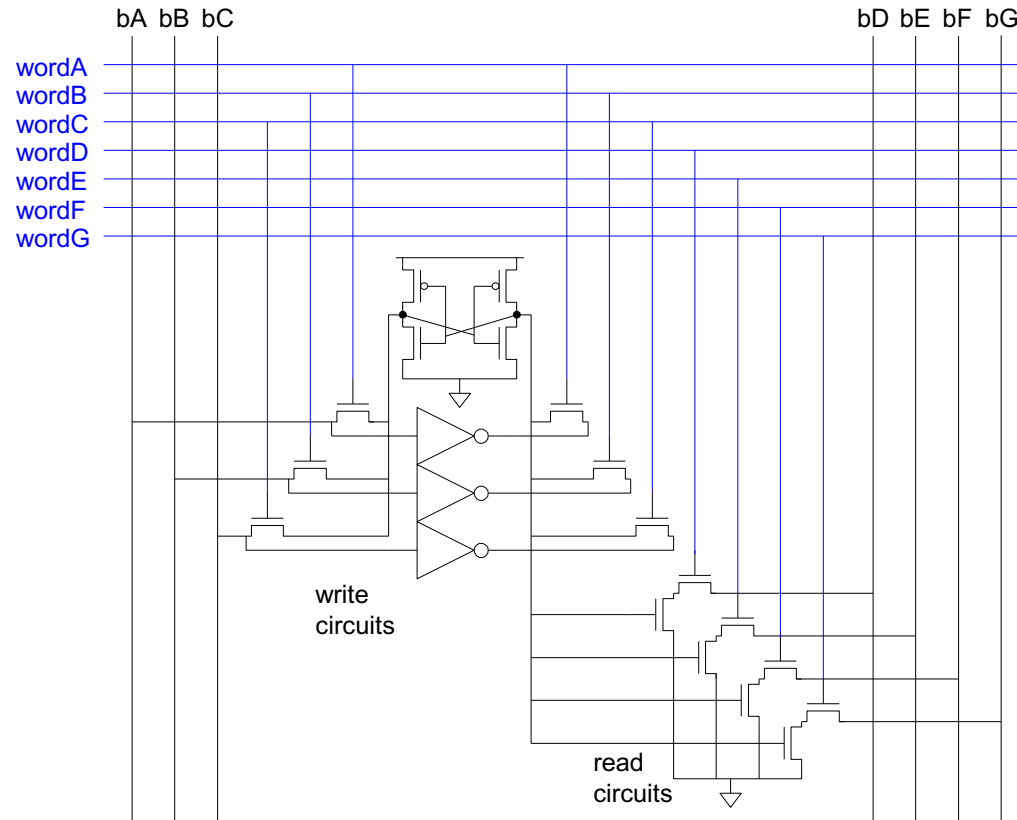
# Multi-Ported SRAM

- Adding more access transistors hurts read stability
- Multi-ported SRAM isolates reads from state node
- Single-ended design minimizes number of bitlines



# BASIC ARRAY LAYOUT

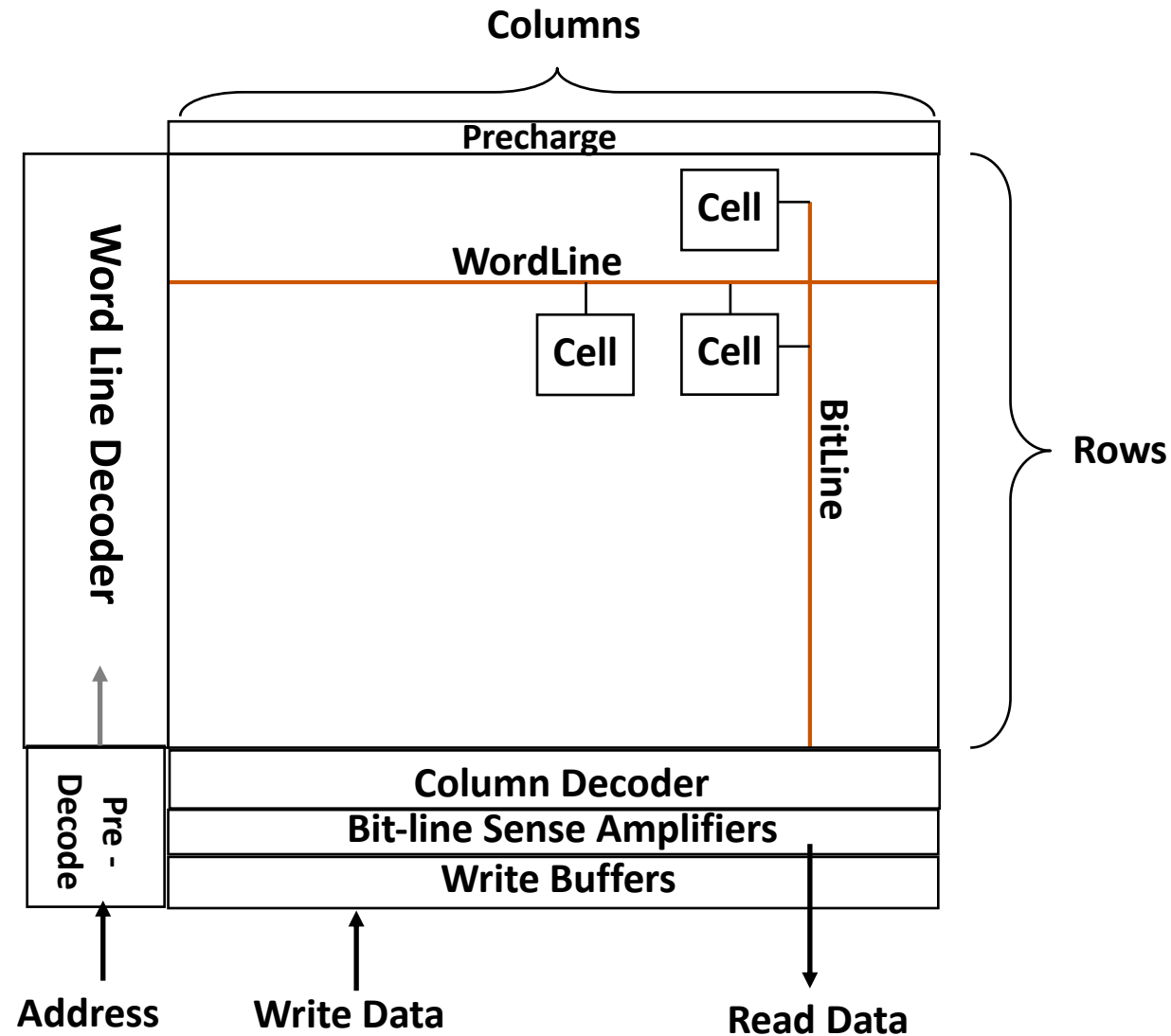

# SRAM Layout Using a Memory Compiler


---






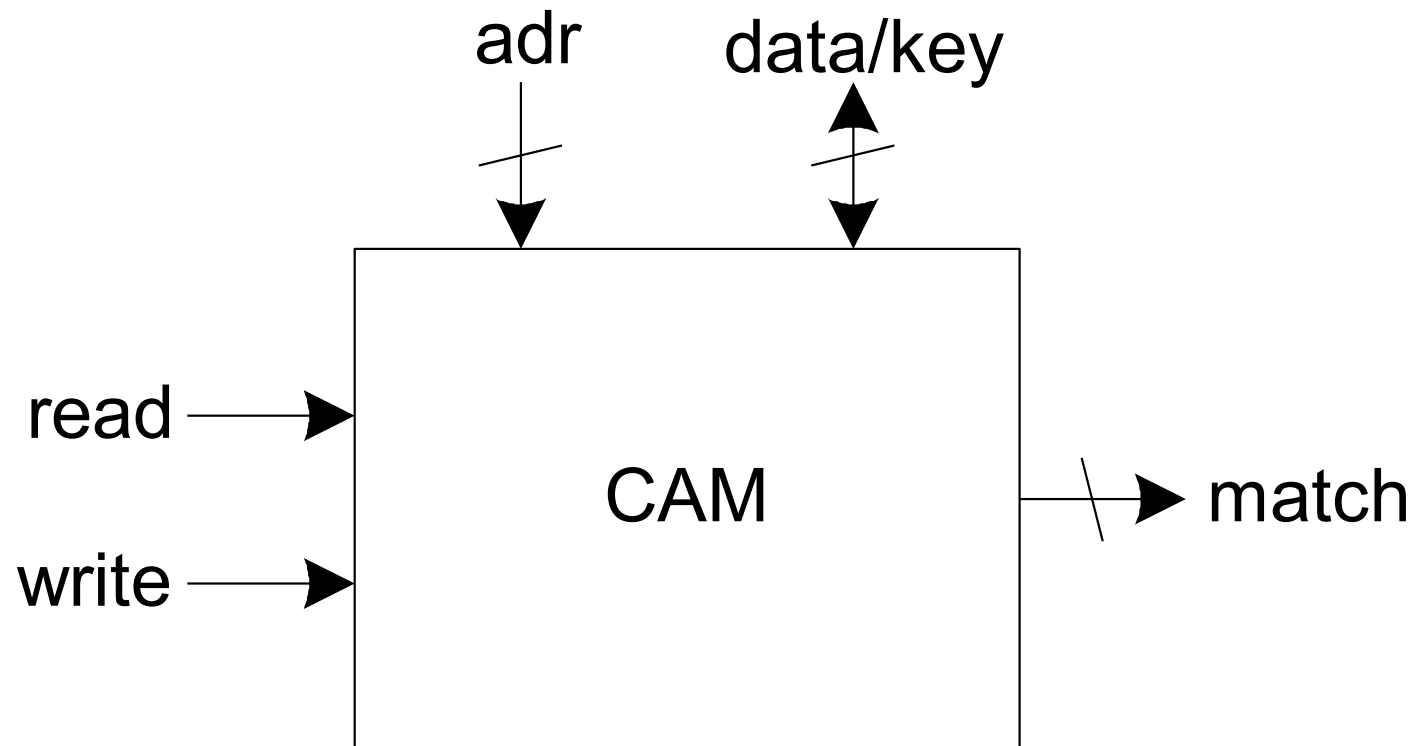
# CAMs

- **Extension of ordinary memory (e.g. SRAM)**
  - Read and write memory as usual
  - Also *match* to see which words contain a *key*



  
# 10T CAM Cell

- **Add four match transistors to 6T SRAM**
  - 56 x 43  $\lambda$  unit cell



 
# CAM Cell Operation



- **Read and write like ordinary SRAM**
- **For matching:**
  - Leave wordline low
  - Precharge matchlines
  - Place key on bitlines
  - Matchlines evaluate
- **Miss line**
  - Pseudo-nMOS NOR of match lines
  - Goes high if no words match



# 4x4 DRAM Memory

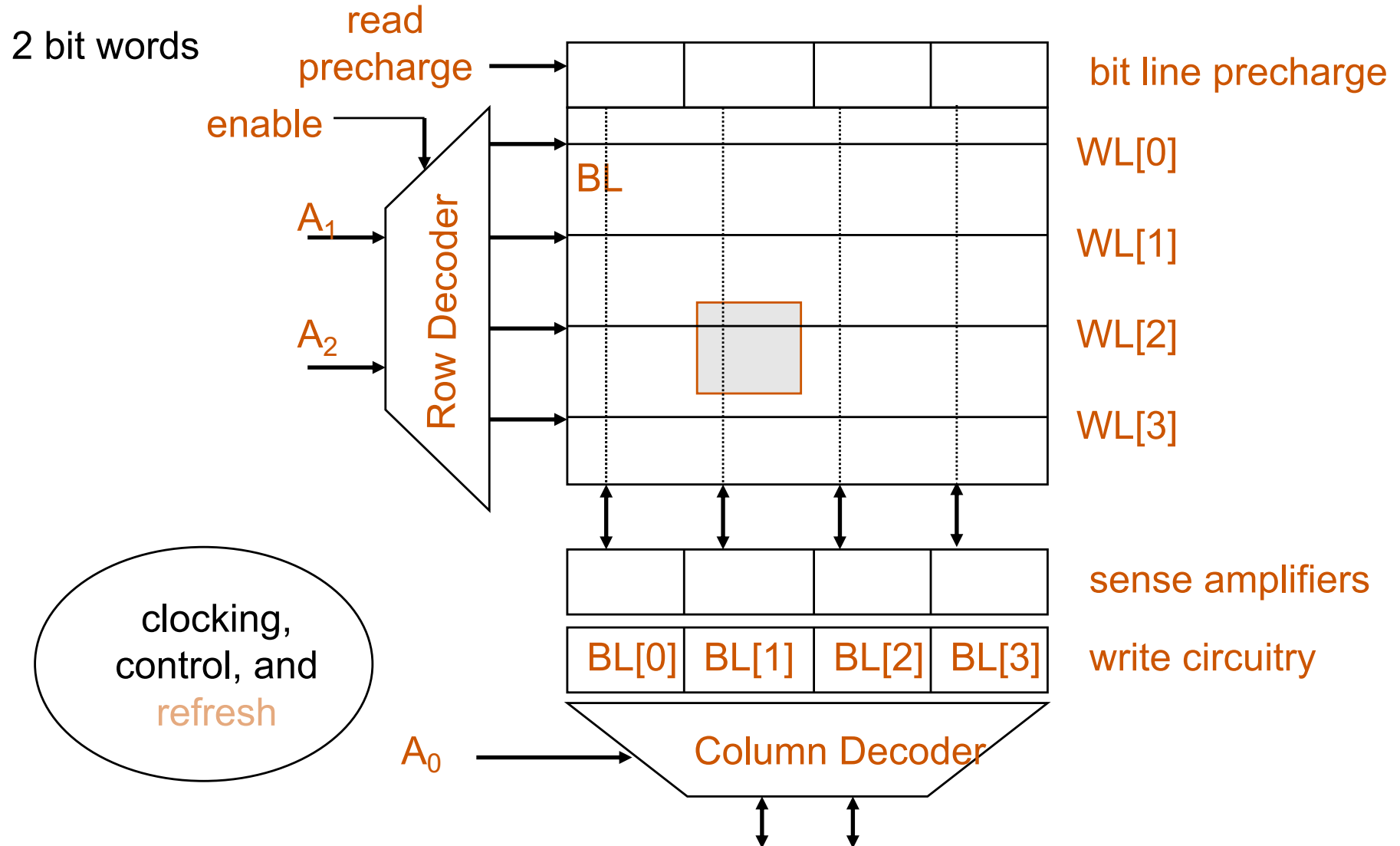

# 3-Transistor DRAM Cell

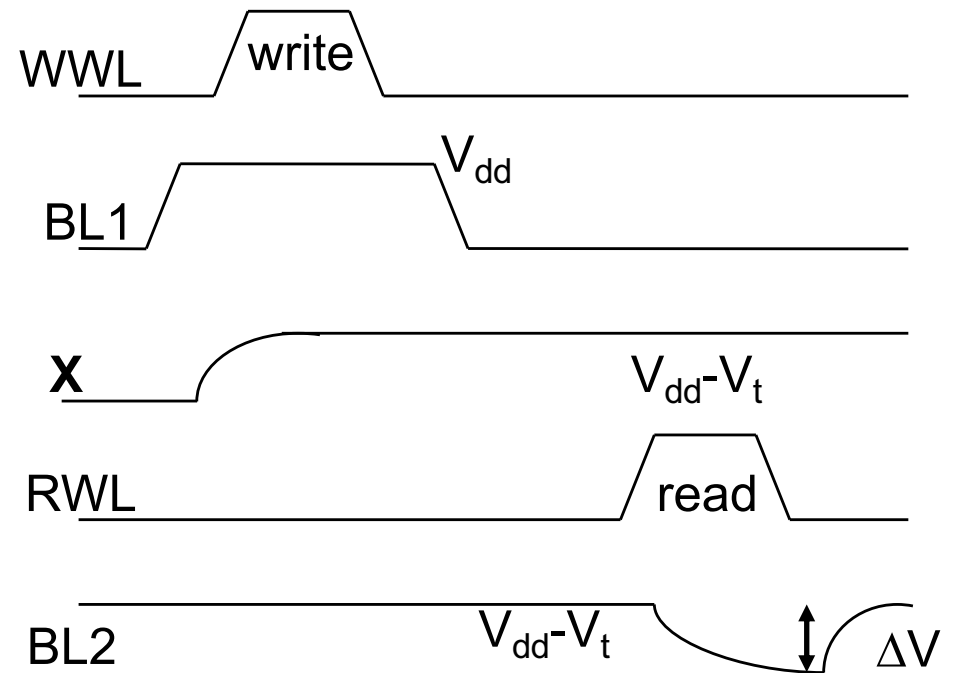 


No constraints on device sizes (ratioless)

Reads are non-destructive

Value stored at node X when writing a "1" is  $V_{WWL} - V_{tn}$

# 1-Transistor DRAM Cell

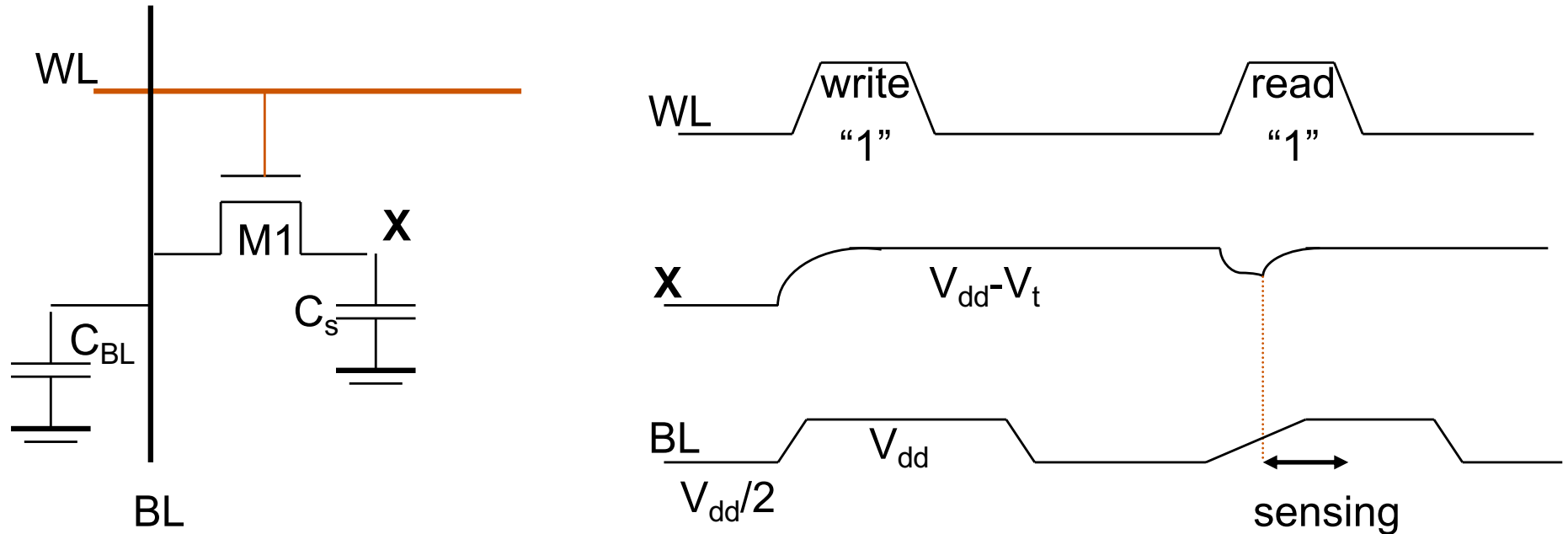


Write:  $C_s$  is charged (or discharged) by asserting WL and BL

Read: Charge redistribution occurs between  $C_{BL}$  and  $C_s$

Read is destructive, so must refresh after read

# 1-T DRAM Cell

 


**Used Polysilicon-Diffusion Capacitance**

**Expensive in Area**

# Dense 1T DRAM Cell

---

 

Trench Cell



# DRAM Cell Observations

---

- **DRAM memory cells are single ended (complicates the design of the sense amp)**
- **1T cell requires a sense amp for each bit line due to charge redistribution read**
- **1T cell read is destructive; refresh must follow to restore data**
- **1T cell requires an extra capacitor that must be explicitly included in the design**
- **A threshold voltage is lost when writing a 1 (can be circumvented by bootstrapping the word lines to a higher value than V<sub>dd</sub>)**

# Serial Access Memories


---

- **Serial access memories do not use an address**
  - Shift Registers
  - Tapped Delay Lines
  - Serial In Parallel Out (SIPO)
  - Parallel In Serial Out (PISO)
 
# Shift Register


---

- Shift registers store and delay data
- Simple design: cascade of registers
  - Watch your hold times!



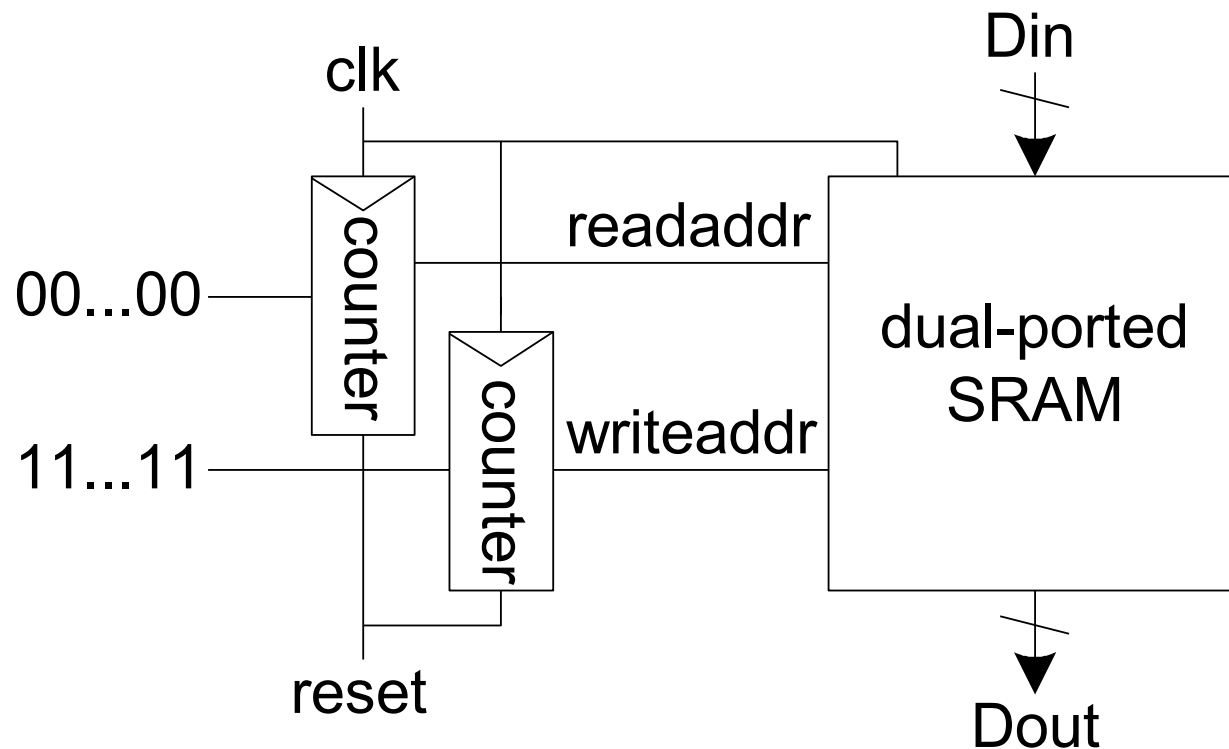
# Denser Shift Registers

- Flip-flops aren't very area-efficient
- For large shift registers, keep data in SRAM instead
- Move R/W pointers to RAM rather than data
  - Initialize read address to first entry, write to last
  - Increment address on each cycle


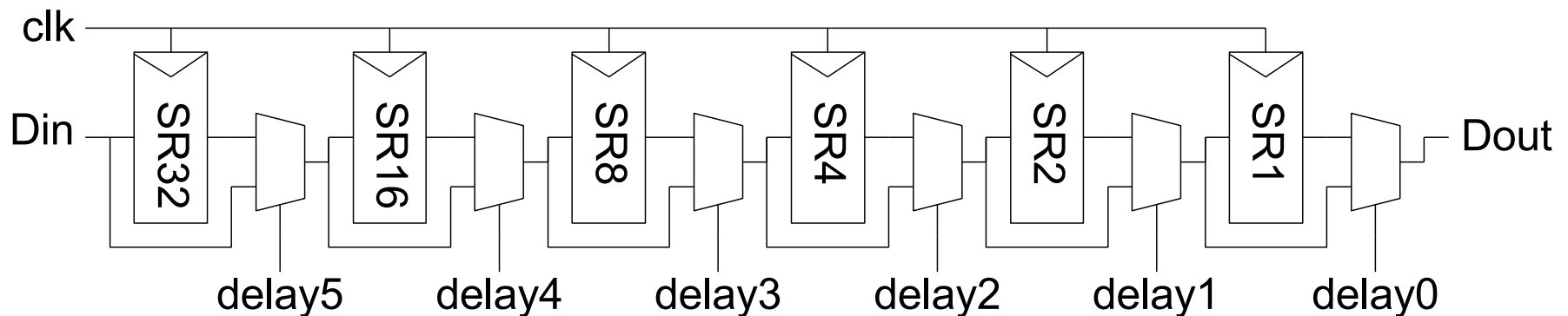
# Tapped Delay Line


- **A *tapped delay line* is a shift register with a programmable number of stages**
- **Set number of stages with delay controls to mux**
  - **Ex: 0 – 63 stages of delay**


 
# Serial In Parallel Out


---

- **1-bit shift register reads in serial data**
  - After N steps, presents N-bit parallel output


 
# Parallel In Serial Out

- **Load all N bits in parallel when shift = 0**
  - Then shift one bit out per cycle



---

# SOFT ERROR RATE (SER)



# BACKGROUND

---

- **There are 2 categories of system failure:**
  - hard failure (permanent failures that require replacement)
  - soft failure (non-permanent random system failures)
- **Cause of failures could be noise, power glitches, design margins, etc**
- **In large memory systems, soft errors are mostly due to radiation**
- **In 1978, May & Woods[5] (Intel) found radioactive materials in memory packages emitting alpha particles which can generate sufficient charge to switch the state of stored charge in DRAMs**
- **Minute traces of radioactive elements can be found in alumina-based ceramics, zirconia & silica fillers used in packaging**
- **Another potential source of alpha particles is from cosmic radiation**
  - High energy particles from cosmic rays can have energies greater than 1GeV
  - Alpha particle energies typically range from 0.1 to 10 MeV


# ALPHA PARTICLES

---

- **An alpha-particle is a doubly charged helium nucleus (2 protons, 2 neutrons) that is generated during radioactive decay of high-Z atoms**
- **More than 300 known alpha-emitting nuclides:**
  - Uranium(238), Thorium(232) can be found in package materials for semiconductors
  - Radioactive decay of U238  $\rightarrow$  Th234 + He4 until it decays to a stable Pb206 (8 alphas are generated)
  - Thorium generates 6 alphas as it decays from Th232 to stable Pb208
- **Alpha particles interact with silicon to generate an ionization trail of electron-hole pairs**
- **The amount of electron-hole pairs generated depends on the particle's initial energy ( $\sim 3.6\text{eV}$  per e-h pair)**

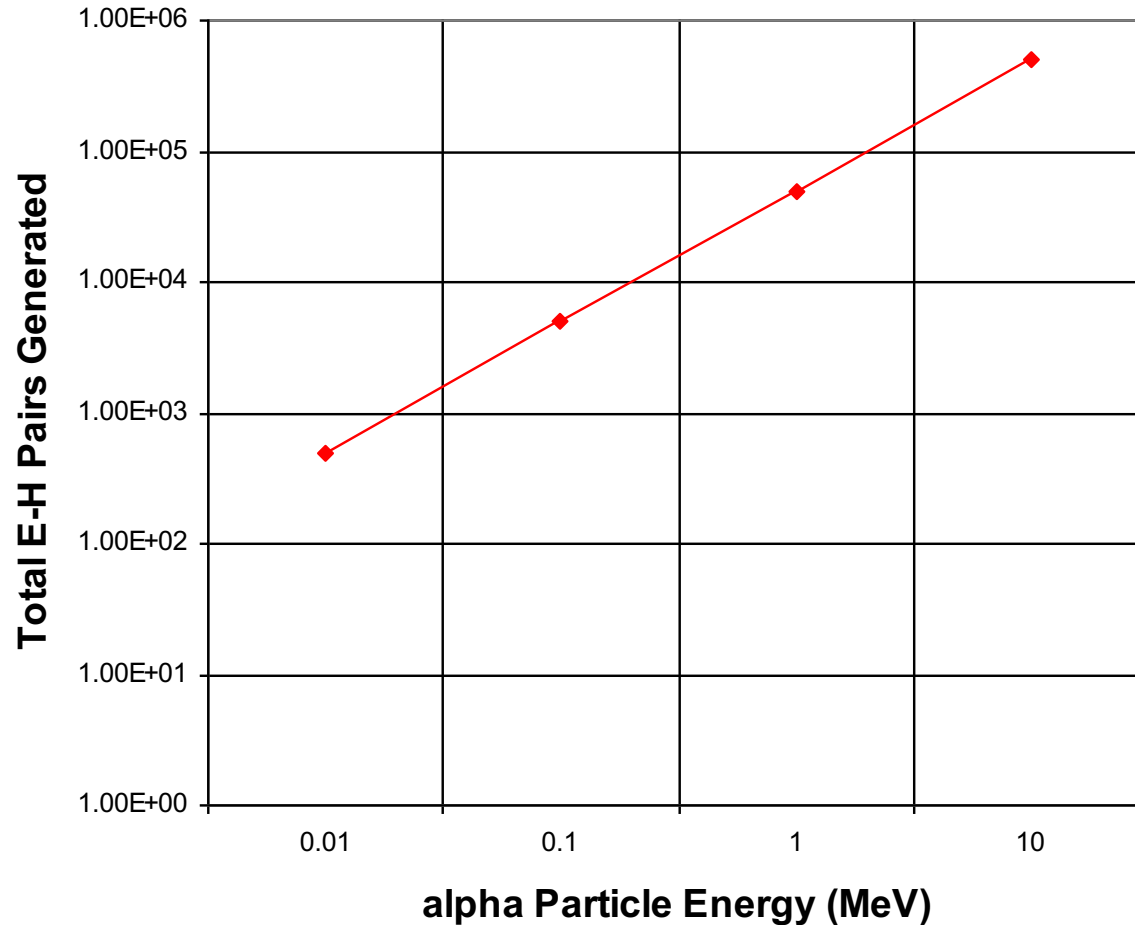
# $\alpha$ Particle Energy for Silicon

Electron-Hole Pair Generation versus alpha energy for Silicon



Alpha particles generated from  $\text{Th}^{232}$  and  $\text{U}^{238}$  will have energies ranging from 3.95MeV to 8.78MeV


# FUNNEL EFFECT

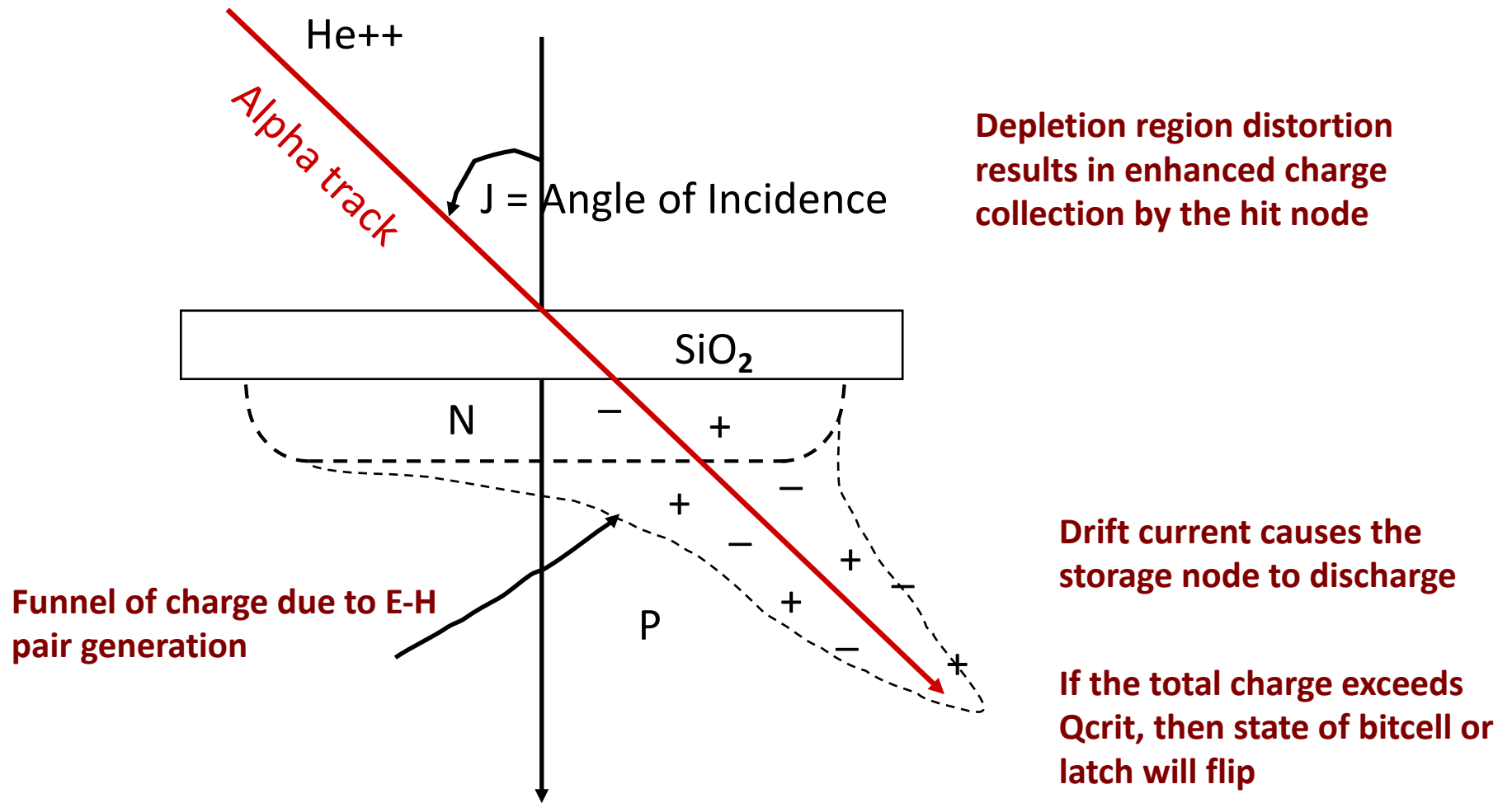

$Q_{crit}$  = number of electrons which differentiates between a "1" and "0"  
(May & Woods) <sup>[1]</sup>

# SOFT ERROR RATE

6-transistor SRAM cell

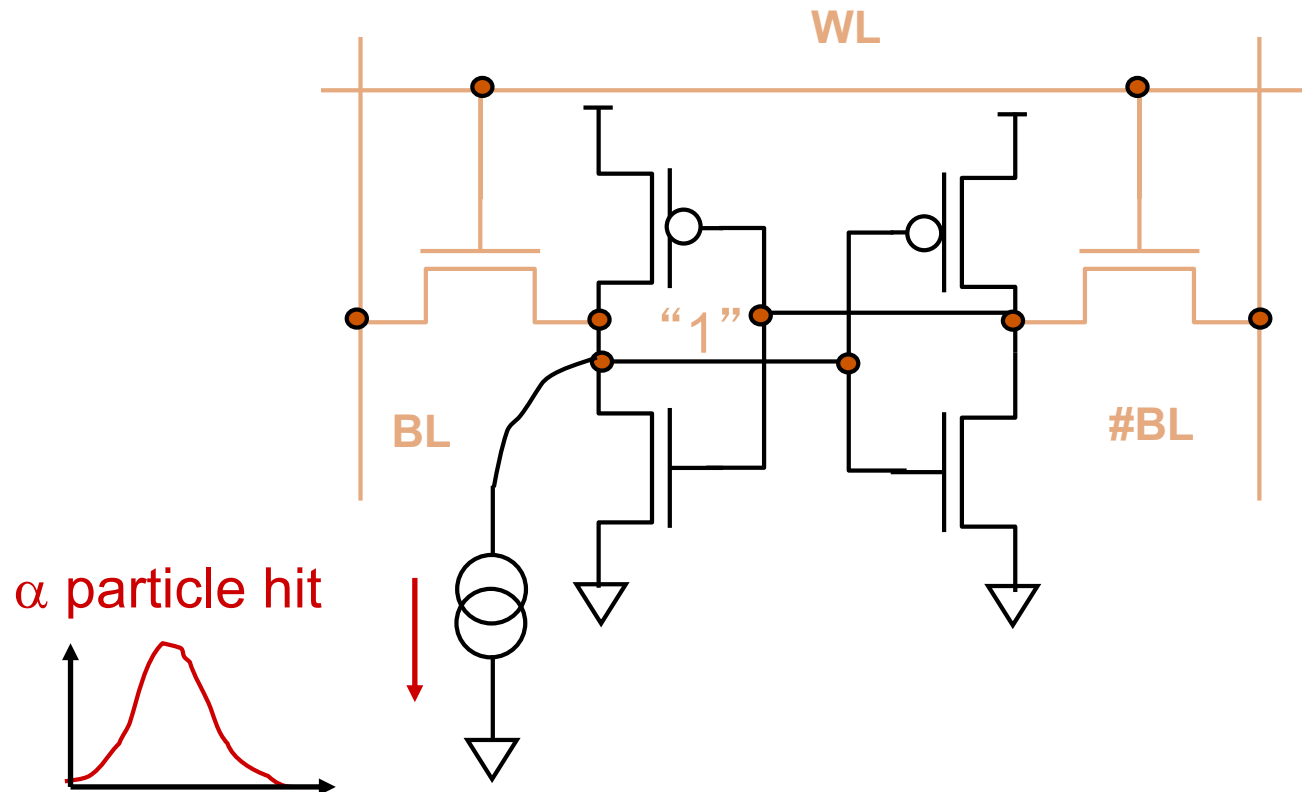


**a-particle "hit" can be modeled as a sub-nanosecond current pulse as described by Chenming Hu**


---

# Memory Array Redundancy

# BASIC ARRAY LAYOUT

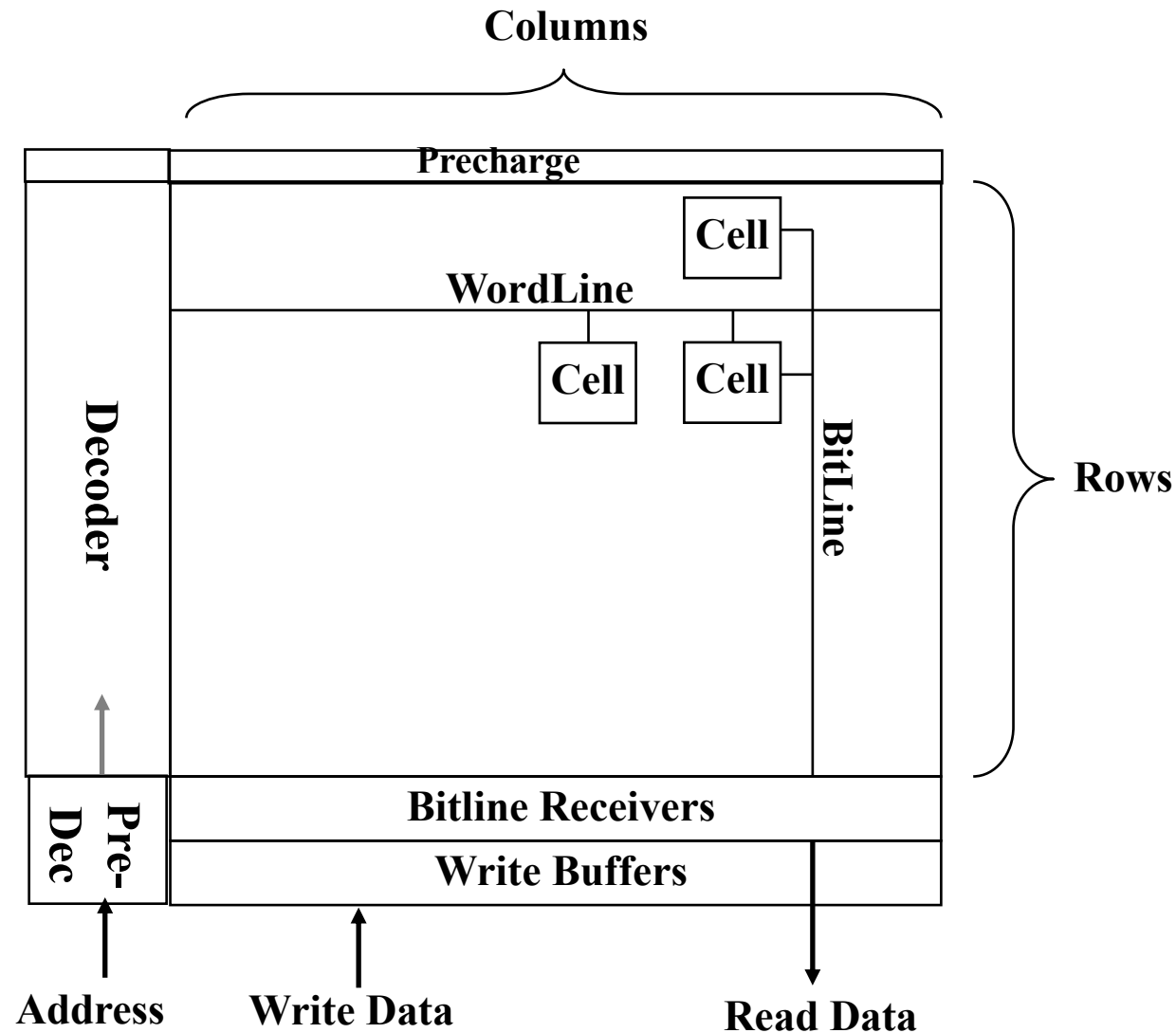

# ARRAY REDUNDANT ELEMENTS

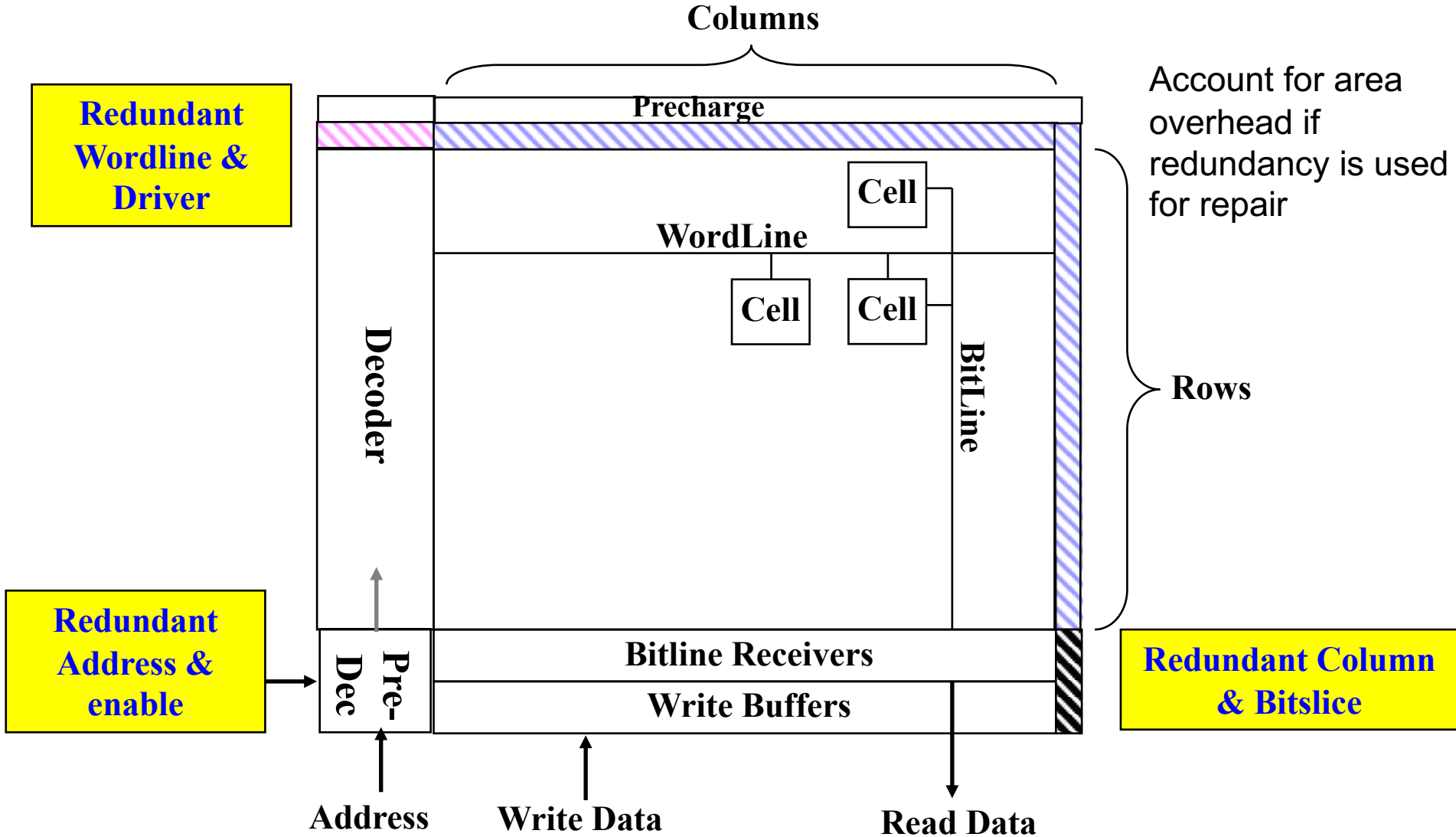




---

# SRAM Cell Stability Analysis
 
# SRAM Cell Stability Analysis


---

- Bitlines are precharged to  $V_{CC}$  → this is the critical situation because the nmos access device “shunts” the pmos load device; thereby reducing the gain of the inverters
- Static noise voltage sources are inserted into cross-couple path between inverters




- SNM is defined by the maximum value of  $V_n$  that can be tolerated before changing state; sweep noise voltage from 0V to the point where differential collapses to zero
- Include temperature, voltage and process variation using a Monte Carlo simulator

# SRAM Cell Stability Analysis

 


Large diagonal due to access devices being “OFF”

 Standby or “Data Retention” state when wordline is not selected → Cell is stable




The “maximum square” is approximately  $V_{CC}/2$

# SRAM Cell Stability Analysis

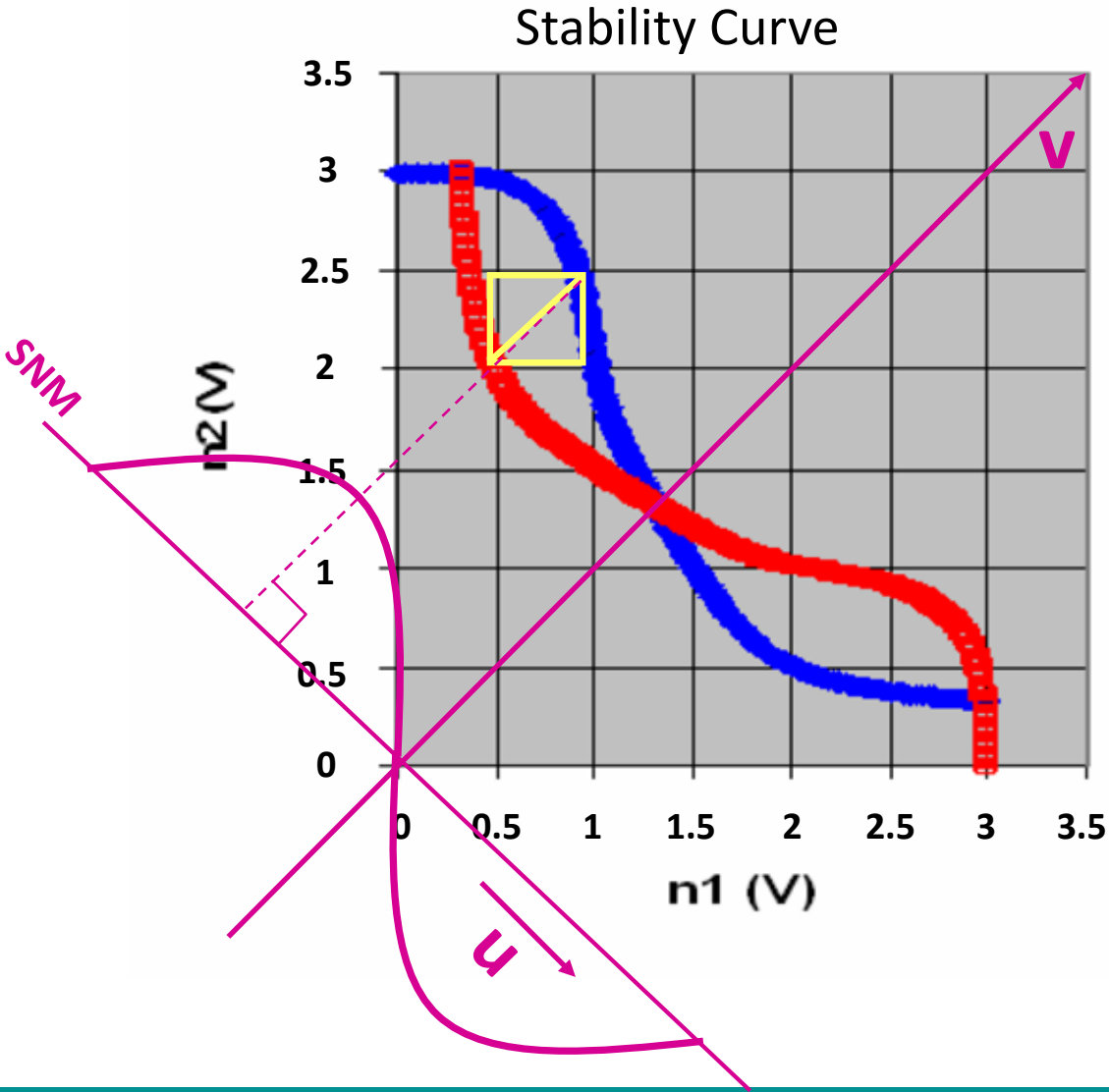

Diagonal is reduced since access device is "ON"

 The "maximum square" represents SNM of the bitcell



Transform coordinates 45°

$$x = \frac{1}{\sqrt{2}} u + \frac{1}{\sqrt{2}} v$$


$$y = \frac{1}{\sqrt{2}} u - \frac{1}{\sqrt{2}} v$$

---

# Backup
 
# 4-Transistor Dynamic RAM Cell

Remove the two p-channel transistors from static RAM cell, to get a four-transistor dynamic RAM cell




Data stored as charge on gate capacitors  
(complementary nodes)

Data must be refreshed regularly

Dynamic cells must be designed very carefully


## 3-Transistor Dynamic RAM Cell

 

**Data stored on the gate of a transistor**

**Need two additional transistors, one for write and the other for read control**

# 1-Transistor Dynamic RAM Cell

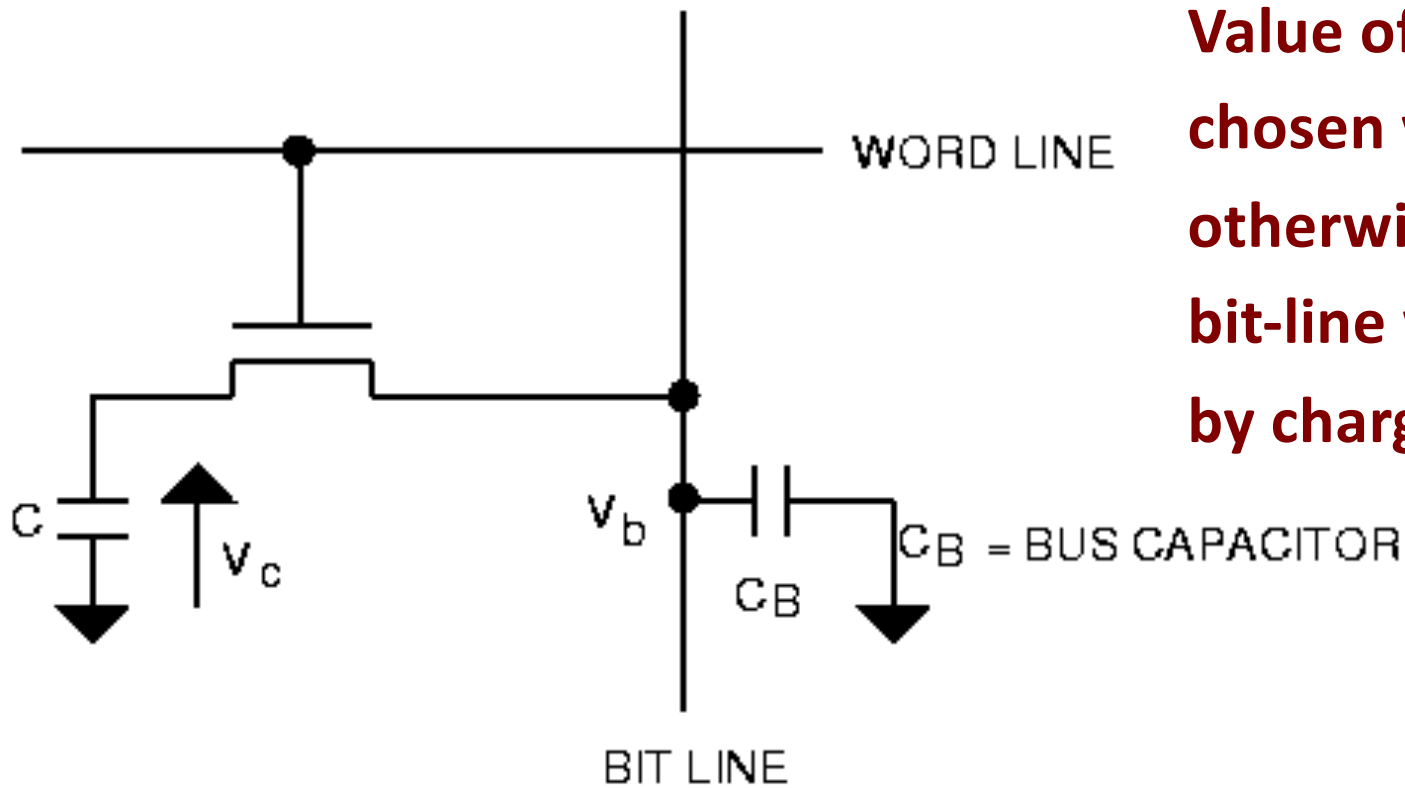

**Value of  $C_B$  must be chosen very carefully; otherwise, voltage on bit-line will be affected by charge sharing**

**Cannot get any smaller than this: data stored on a (trench) capacitor  $C$ , need a transistor to control data  
Bit line normally precharged to  $\frac{1}{2} V_{DD}$  (need a sense amplifier)**



# SRAM Layout

- Cell size is critical:  $26 \times 45 \lambda$  (even smaller in industry)
- Tile cells sharing  $V_{DD}$ , GND, bitline contacts

