

Lecture 18: VLSI Building Blocks


Mark McDermott

**Electrical and Computer Engineering
The University of Texas at Austin**


Agenda

- **System overview**
 - Dataflow programming paradigm
- **Dataflow Processing Element (DPE)**
 - Queues (FIFO), Stacks (LIFO), Queued-Stacks
 - Datapaths
 - Lookup Tables
 - Microcode Control
 - Finite State Machines (FSM)
- **On-chip Networks**
 - Serializers & Deserializers (SERDES)
 - Cross bar switches
 - Arbiters



Synchronous Dataflow (SDF) Tutorial

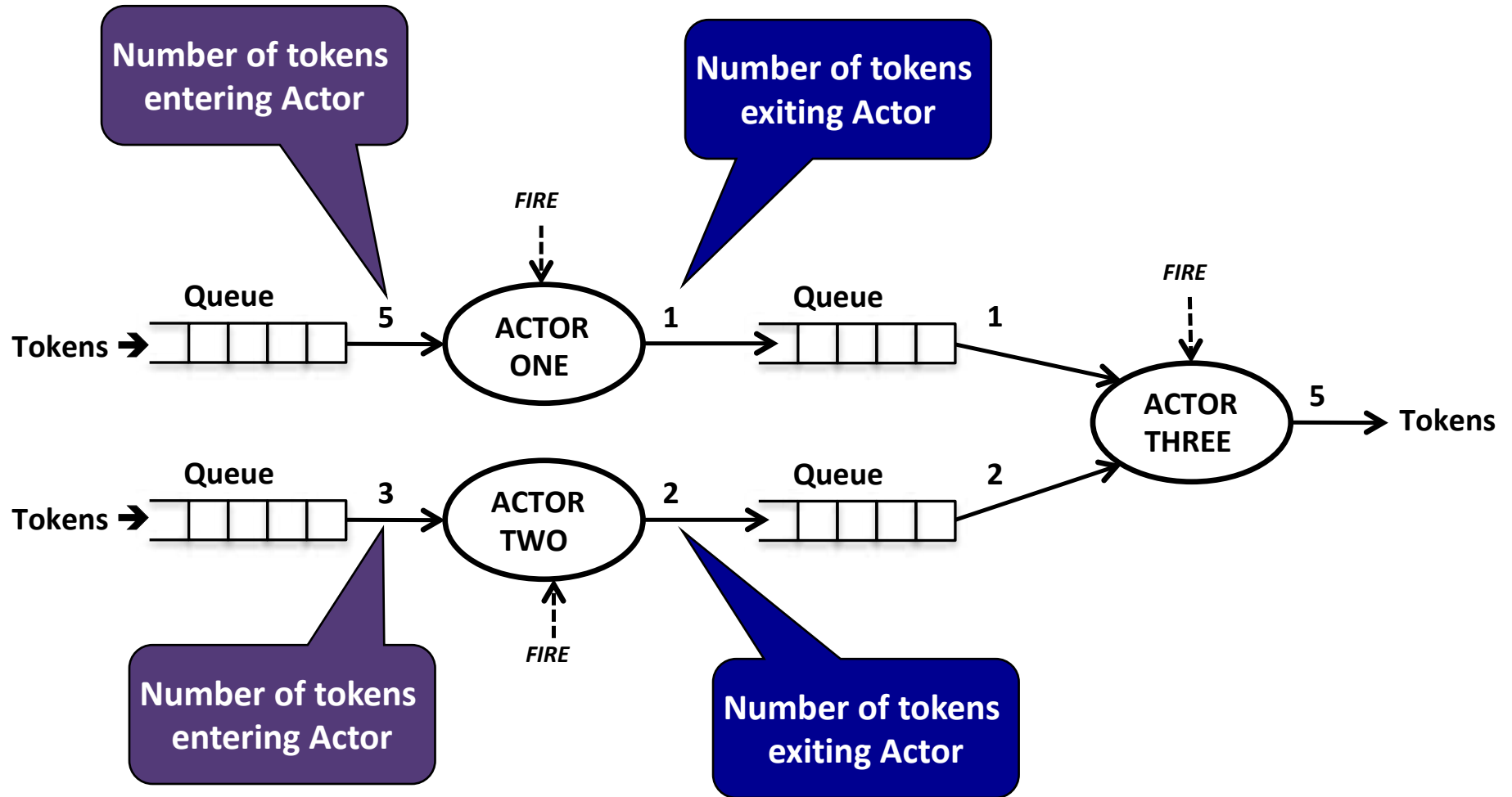


Synchronous Dataflow (SDF) Tutorial

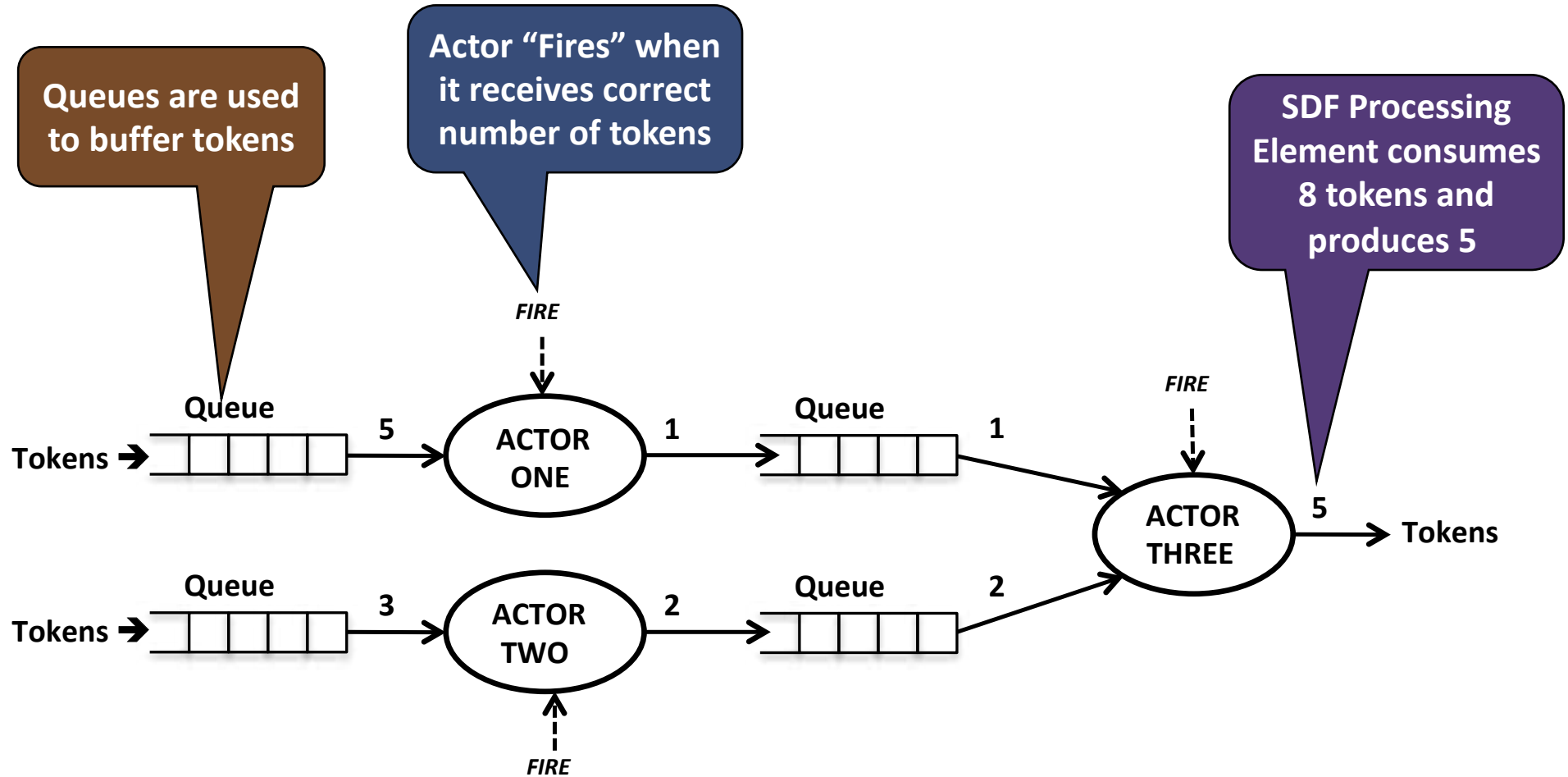


Programming a Dataflow Engine

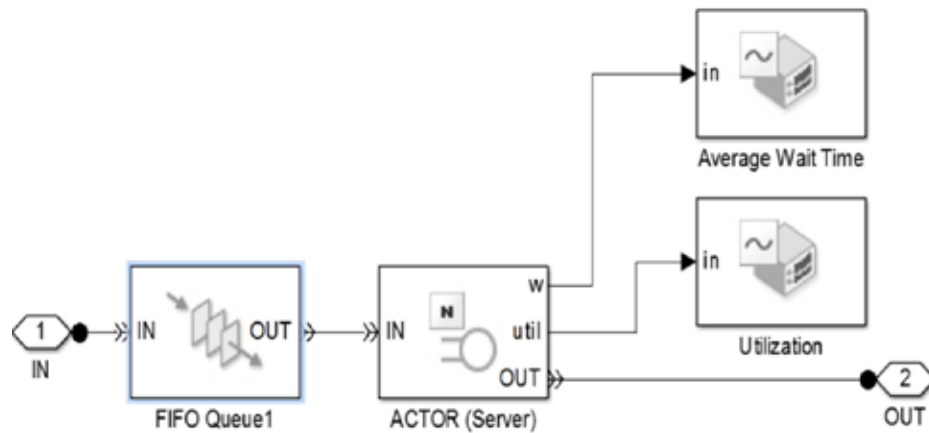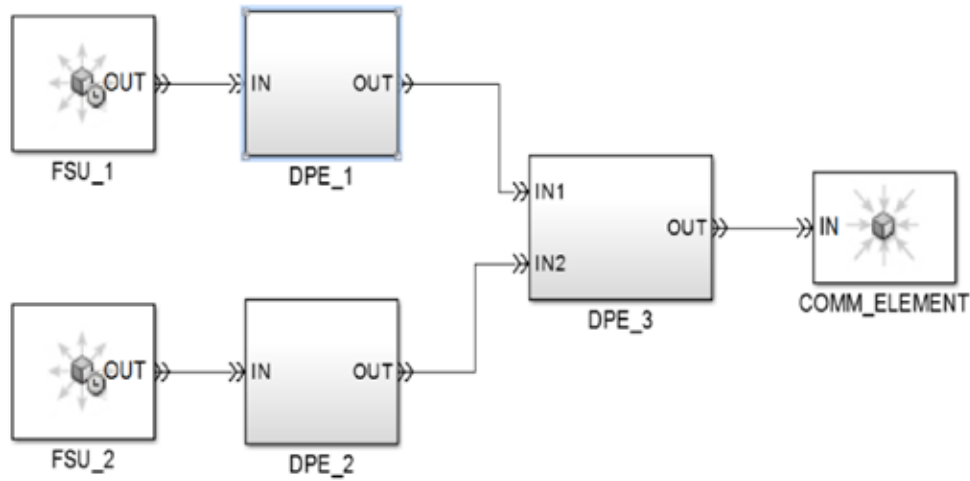



Programming a Dataflow Engine

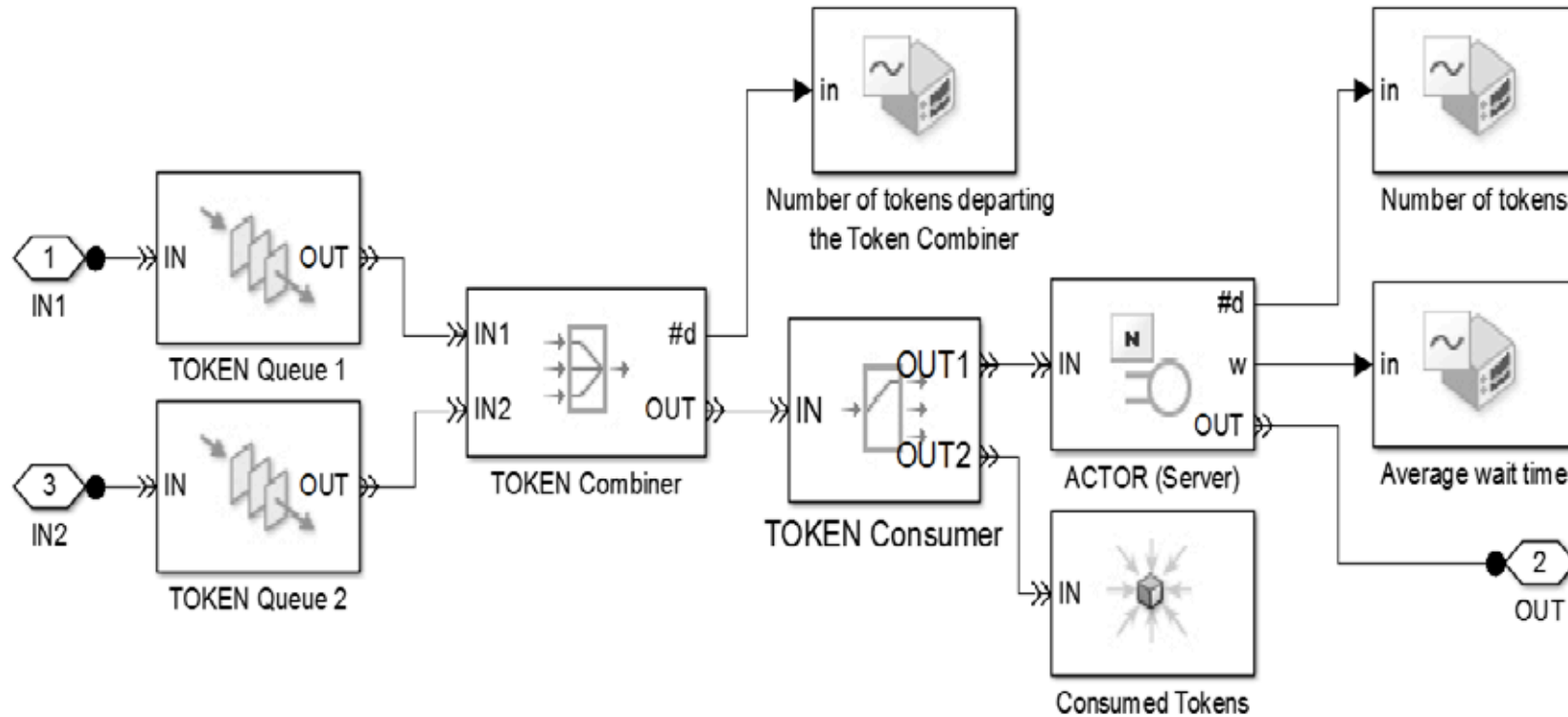



Dataflow Processing Element (DPE)

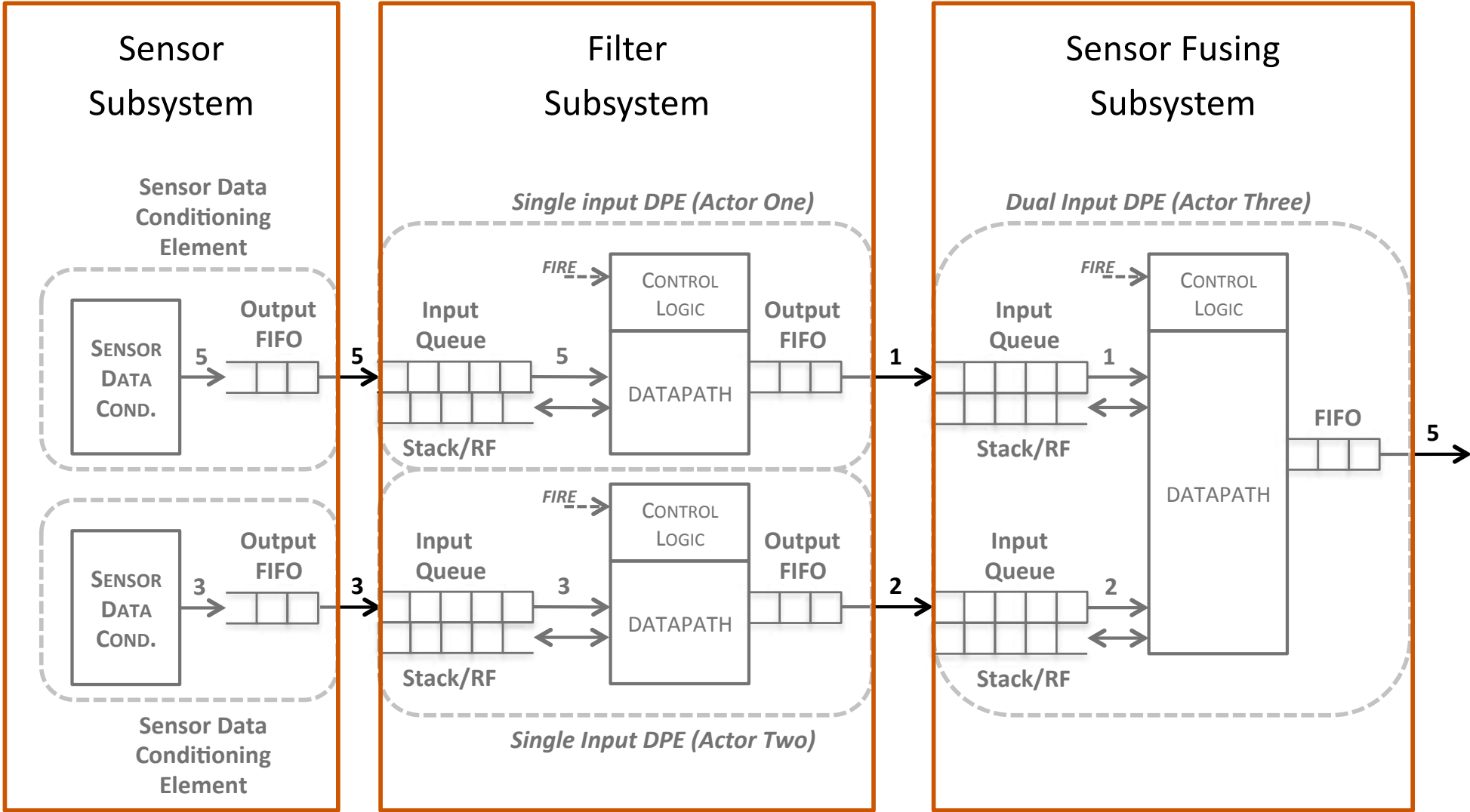


Filter Subsystem: FIR Filter

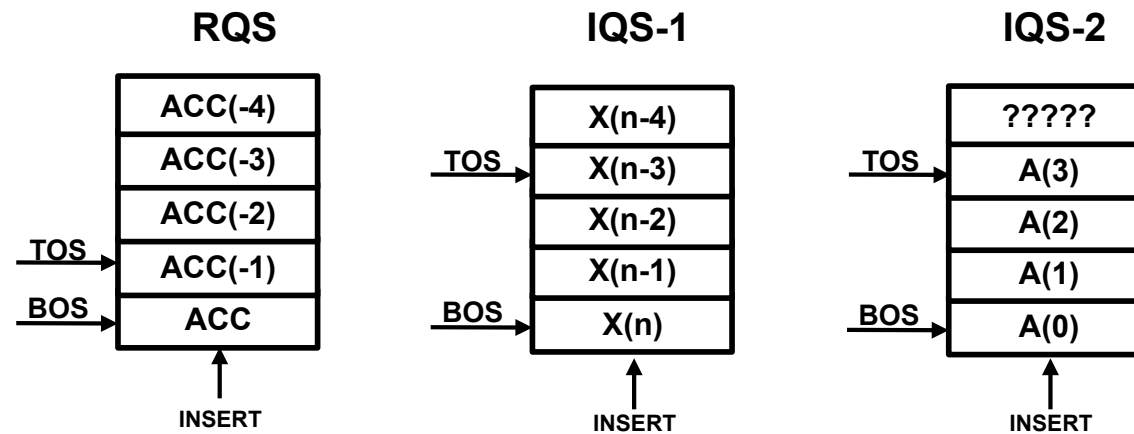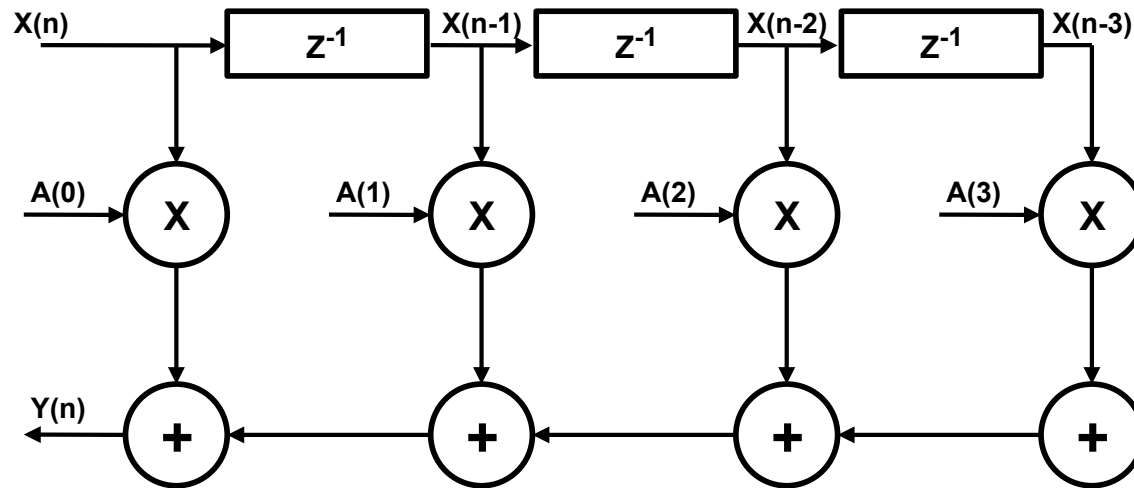


Filter Subsystem: IIR Filter

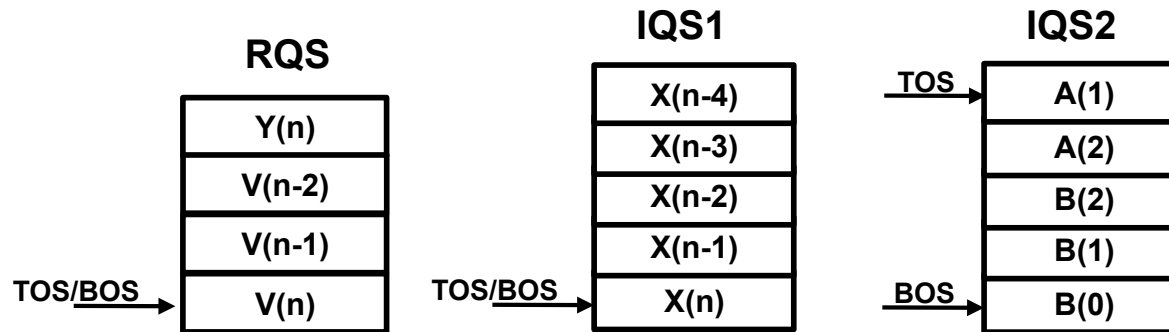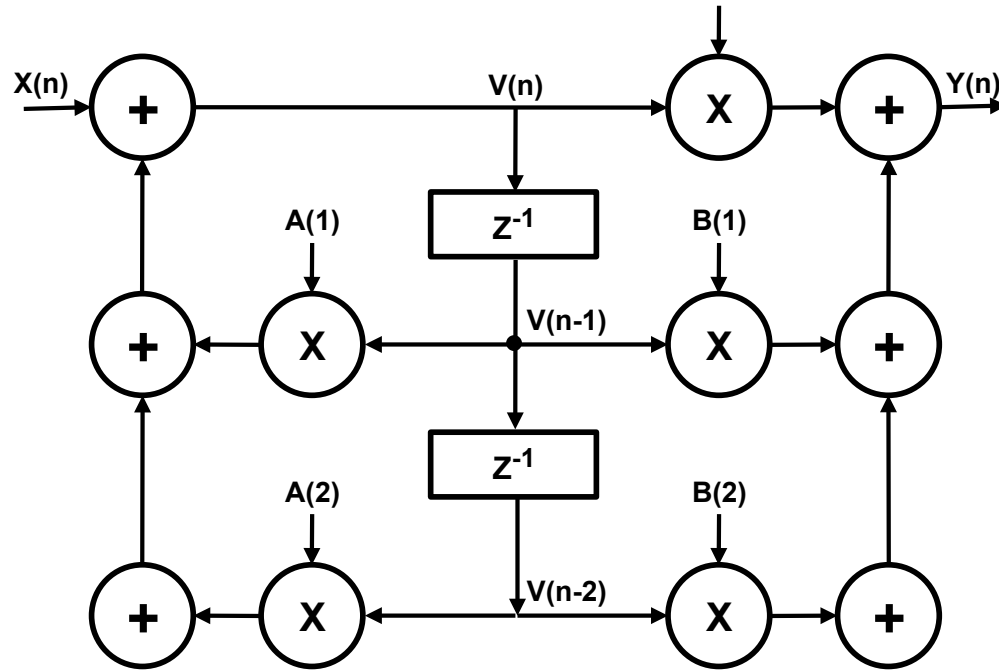

Fuzzy Logic Based Sensor Fusing DPE

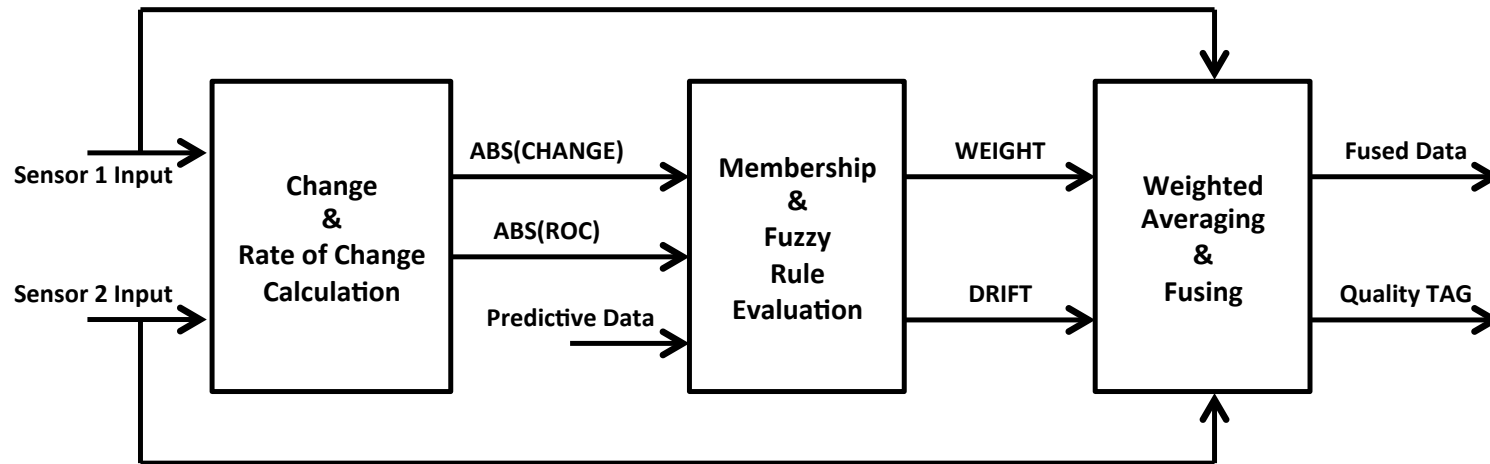

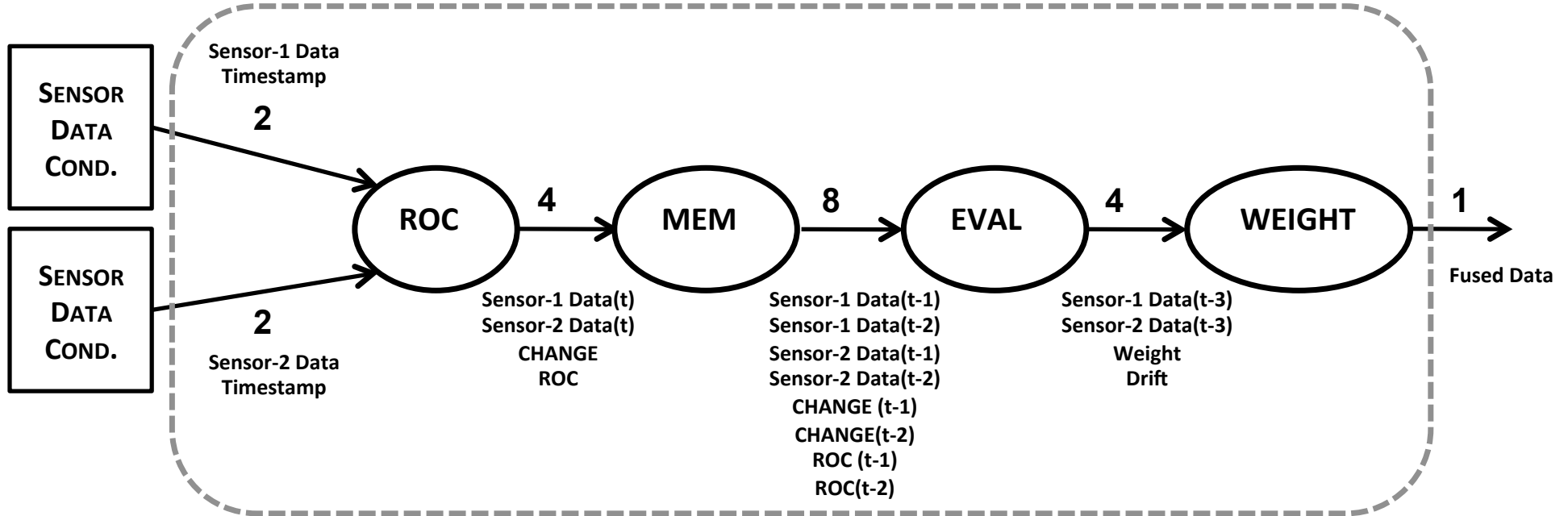Dual Input DPE (Four Actors: ROC, MEM, EVAL, WEIGHT)



Agenda

- System overview
- **Dataflow Processing Element (DPE)**
 - Queues (FIFO), Stacks (LIFO), Queued-Stacks
 - Datapaths
 - Lookup Tables
 - Microcode Control
 - Finite State Machines (FSM)
- On-chip Networks
 - Serializers & Deserializers (SERDES)
 - Cross bar switches
 - Arbiters


FIFO/Queue & LIFO/Stack

- **First In First Out (FIFO)**
 - Initialize read and write pointers to first element
 - Queue is EMPTY
 - On write, increment write pointer
 - If write almost catches read, Queue is FULL
 - On read, increment read pointer

- **Last In First Out (LIFO)**
 - Also called a stack
 - Use a single stack pointer for read and write


FIFO/Queues

 - Queues allow data to be read and written at different rates.
- Read, Write each use their own clock, data
- Queue indicates whether it is full or empty
- Build with multi-ported SRAM and read/write counters (pointers)




LIFO/Stack

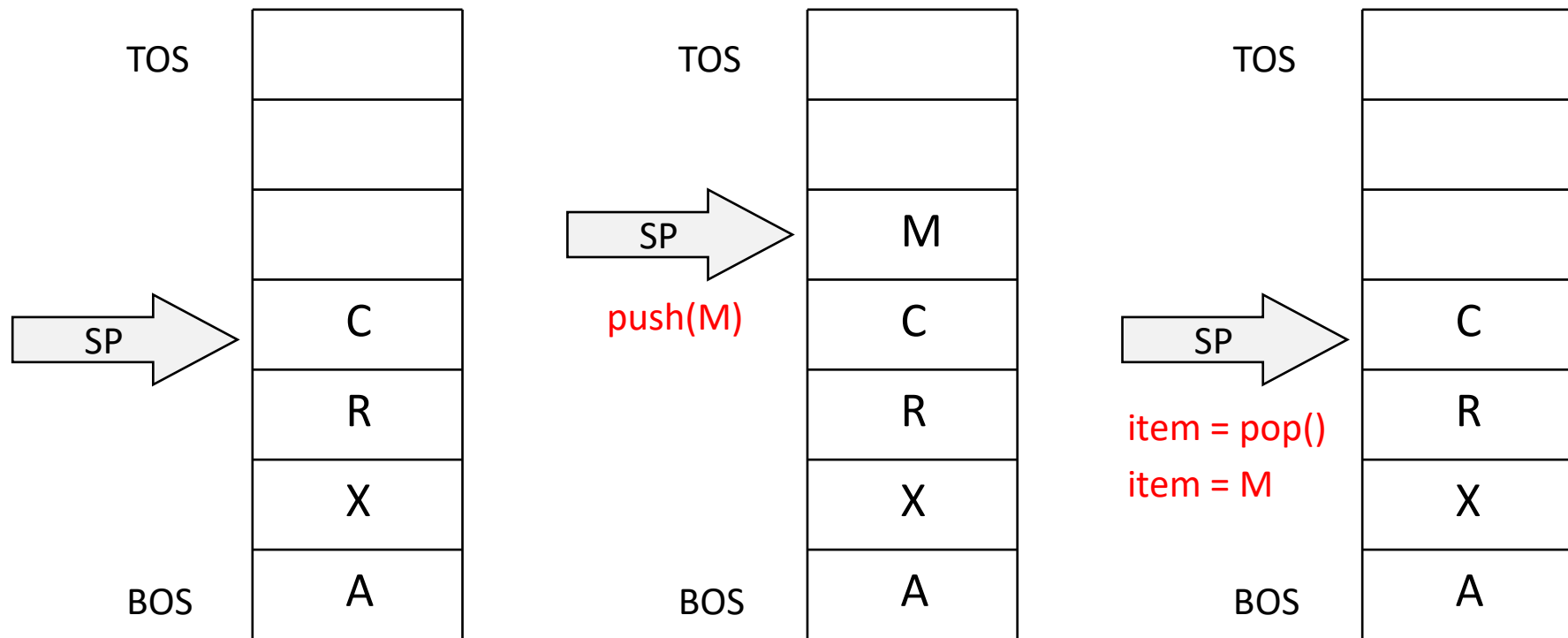- Stack uses a single pointer that points to last valid data entry.
- Pointer is pre-incremented before write during a push op
- Pointer is post-decremented after read during a pop op



Queued-Stack (QS)

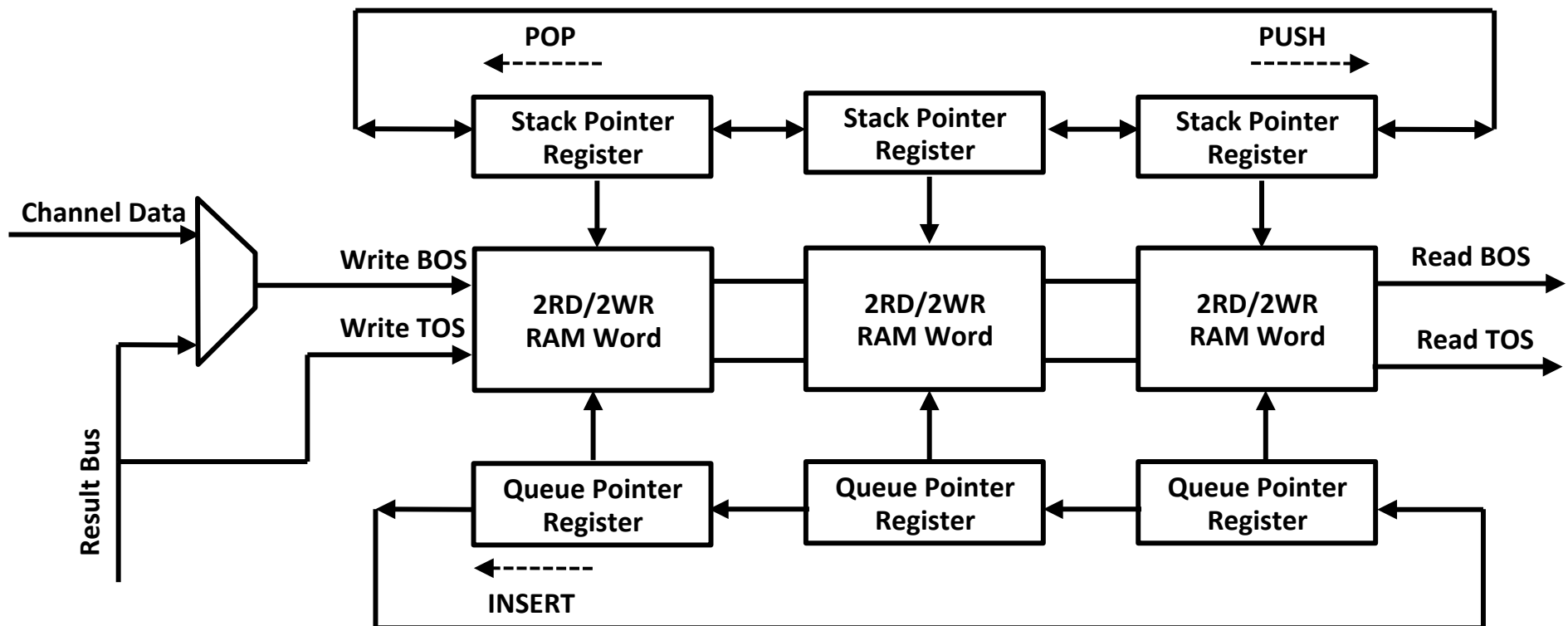
- Merges function of a Queue and a Stack into single element
- Uses two circular pointers and 2 port R/W memory
- Depth of the QS is determined by the algorithm executed by the DPE



QS Operations

Operation	Description
PUSH	ROTATE TOS POINTER RIGHT AND WRITE RESULT-BUS VALUE TO NEW TOS
POP	ROTATE TOS POINTER LEFT (W/O WRITE)
POP_WR	ROTATE TOS POINTER LEFT AND WRITE RESULT-BUS VALUE TO NEW TOS
INS	ROTATE BOS POINTER LEFT AND WRITE RESULT-BUS VALUE TO BOS
INS_NW	ROTATE BOS POINTER LEFT (W/O WRITE)
PUSH_NW	ROTATE TOS POINTER RIGHT (W/O WRITE)
TOP	WRITE RESULT BUS VALUE TO TOS W/O ROTATING POINTER
BOT	WRITE RESULT BUS VALUE TO BOS W/O ROTATING POINTER
TOP_BOT	WRITE RESULT BUS VALUE TO TOS/BOS W/O ROTATING POINTERS
PUSH_INS	ROTATE BOTH POINTERS AND WRITE RESULT-BUS VALUE TO TOS/BOS
POP_BOT	ROTATE TOS POINTER LEFT AND WRITE RESULT-BUS TO BOS
POP_INS	ROTATE TOS POINTER LEFT, ROTATE BOS LEFT AND WRITE RESULT-BUS TO NEW BOS
POP_WR_BOT	ROTATE TOS POINTER LEFT AND WRITE RESULT-BUS TO BOS AND TO NEW TOS
PUSH_NW_BOT	ROTATE TOS POINTER RIGHT AND WRITE RESULT-BUS TO BOS
TOP_INS	ROTATE BOS POINTER LEFT AND WRITE RESULT-BUS TO TOS AND TO NEW BOS
NOP	NO OPERATION


DPE using multiple Queued-Stacks

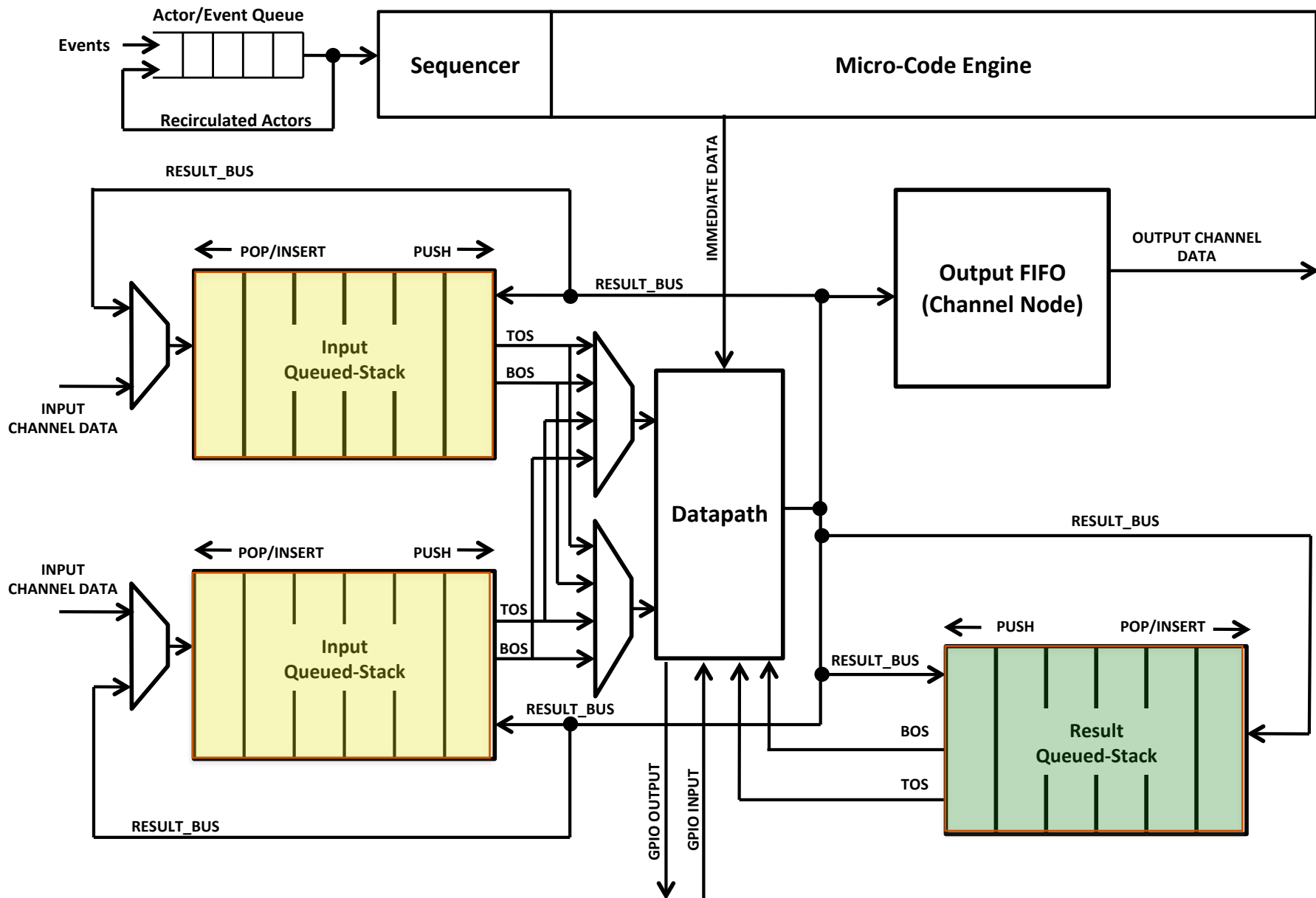

Agenda

- System overview
- Dataflow Processing Element (DPE)
 - Queues (FIFO), Stacks (LIFO), Queued-Stacks
 - **Datapaths**
 - Lookup Tables
 - Microcode Control
 - Finite State Machines (FSM)
- On-chip Networks
 - Serializers & Deserializers (SERDES)
 - Cross bar switches
 - Arbiters

DPE Datapath

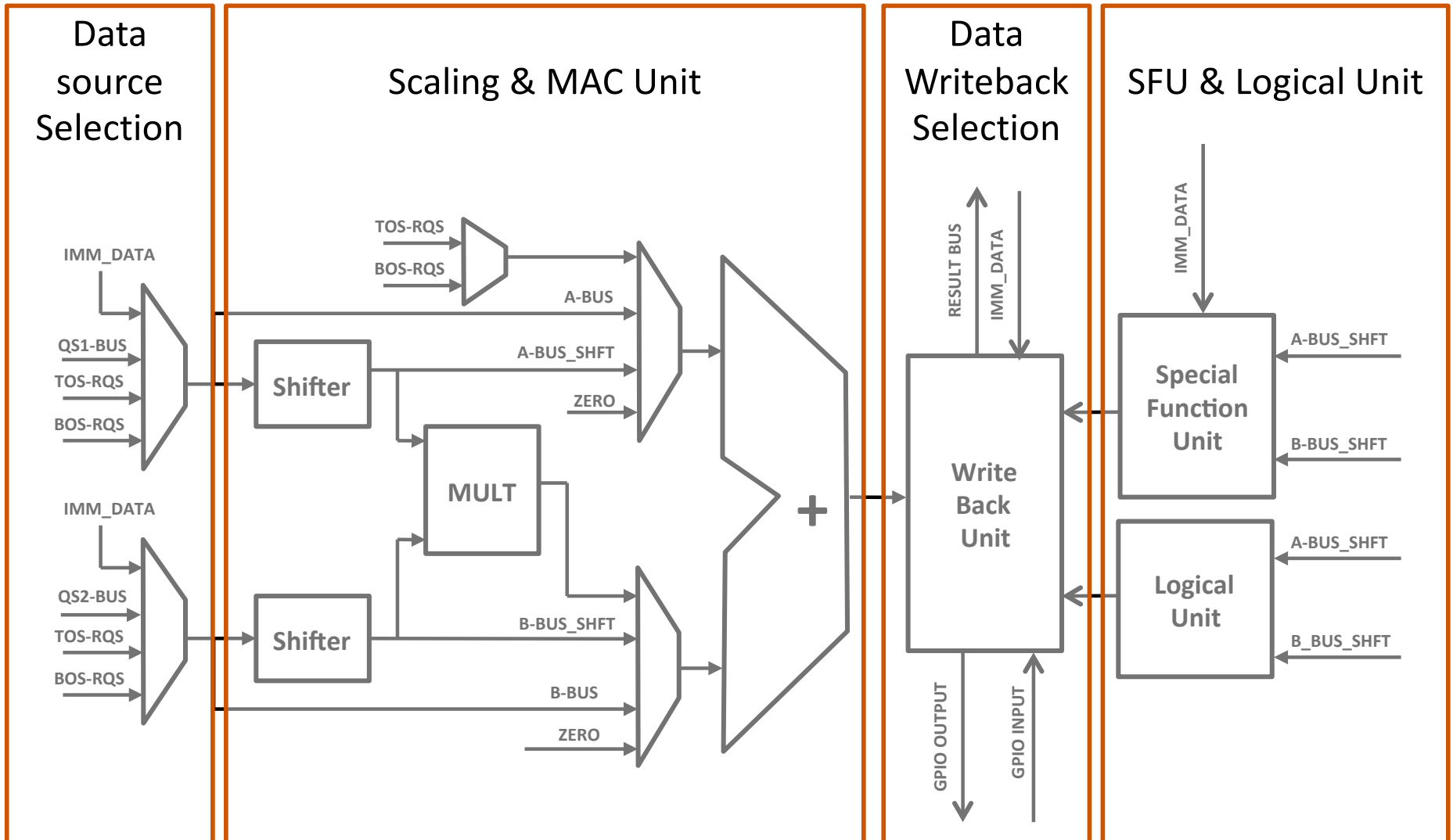

Datapath Operations

SHIFT MODE A <44>	SHIFT A <38:34>	SHIFT TC A <32>	DATA TC <19>	MSB OP	OPERATION
1	0-31	0	-	-	LEFT ARITHMETIC SHIFT, LOGIC 0 PADDING
1	0-31	1	-	0	LEFT ARITHMETIC SHIFT, LOGIC 0 PADDING
1	0-31	1	0	0	RIGHT ARITHMETIC SHIFT, LOGIC 0 PADDING
1	0-31	1	1	1	RIGHT ARITHMETIC SHIFT, SIGN EXT. PADDING
0	0-31	0	-	0	LEFT BARREL SHIFT
0	0-31	1	-	1	RIGHT BARREL SHIFT

MULT MODE <31>	DATA TC <19>	OPERATION
0	-	NO OPERATION
1	0	UNSIGNED MULTIPLY
1	1	SIGNED MULTIPLY



ADD/SUB <28>	SAT <30>	DATA TC <19>	OPERATION
0	0	0	UNSIGNED ADD
0	0	1	SIGNED ADD
0	1	0	SATURATED UNSIGNED ADD
0	1	1	SATURATED SIGNED ADD
1	0	0	UNSIGNED SUBTRACT
1	0	1	SIGNED SUBTRACT
1	1	0	SATURATED UNSIGNED SUBTRACT
1	1	1	SATURATED SIGNED SUBTRACT

Agenda

- System overview
- Dataflow Processing Element (DPE)
 - Queues (FIFO), Stacks (LIFO), Queued-Stacks
 - Datapaths
 - **Lookup Tables**
 - Microcode Control
 - Finite State Machines (FSM)
- On-chip Networks
 - Serializers & Deserializers (SERDES)
 - Cross bar switches
 - Arbiters

Lookup Table (LUT)

  - Combinatorial logic is stored in Look-Up Tables (LUTs)
 - Also called Function Generators (FGs)
 - Capacity is limited by the number of inputs, not by the complexity




Truth table

S	A	B	Z
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

SRAM Based Lookup Table

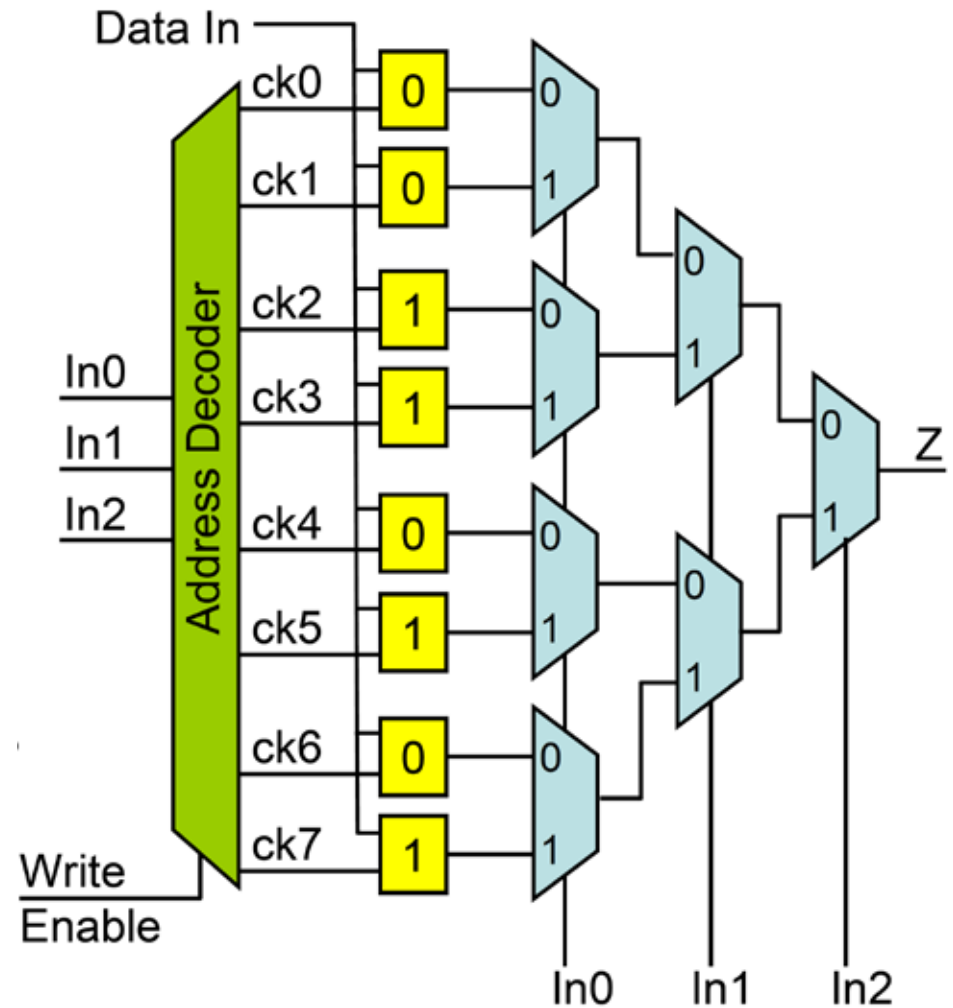- Normal LUT mode performs read operations
- Address decoder with write enable generates clock signals to latches for write operations




Agenda

- System overview
- Dataflow Processing Element (DPE)
 - Queues (FIFO), Stacks (LIFO), Queued-Stacks
 - Datapaths
 - Lookup Tables
 - **Microcode Control**
 - Finite State Machines (FSM)
- On-chip Networks
 - Serializers & Deserializers (SERDES)
 - Cross bar switches
 - Arbiters


Microcode controller

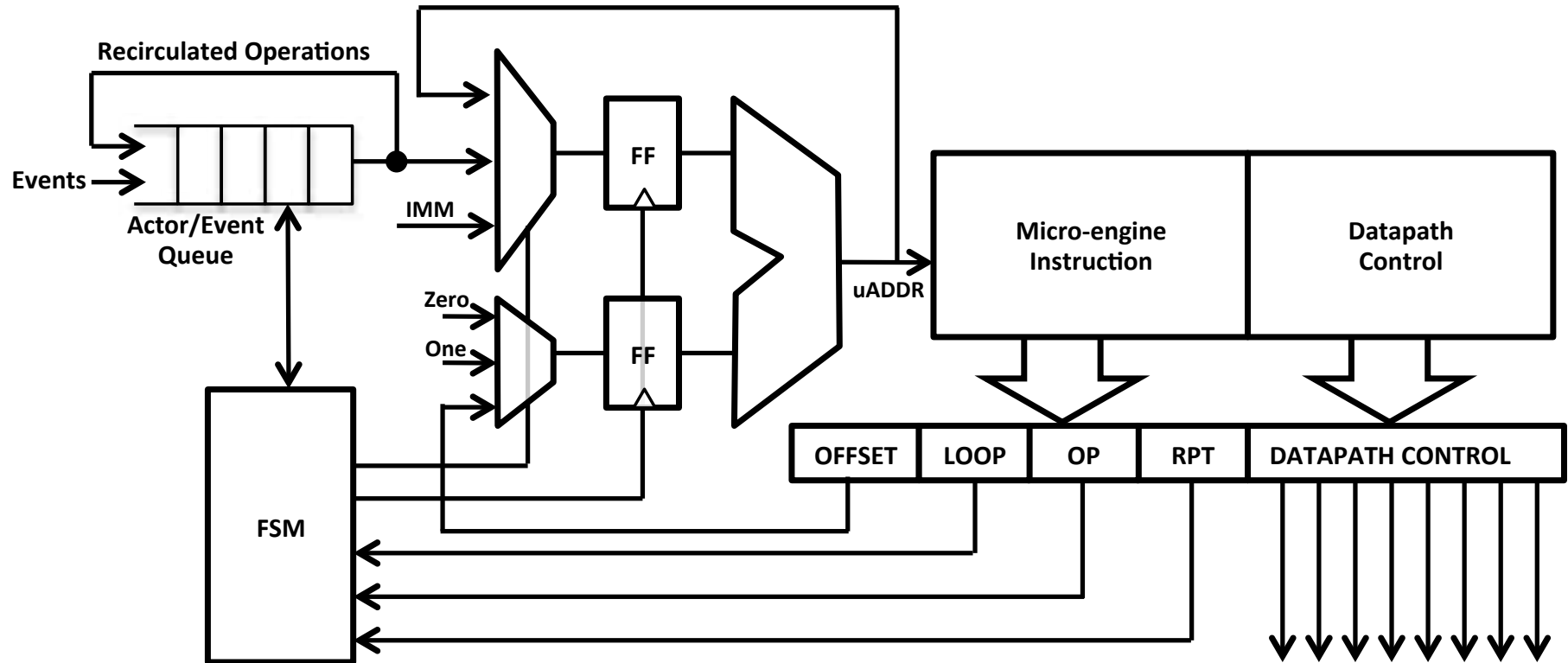- **Microcode word is 96 bits wide**
 - 32 bits is used for the micro-engine control
 - Remainder is used for datapath control
 - **Combination of one-hot control bits and encoded bit fields**



Next Micro Address Detail

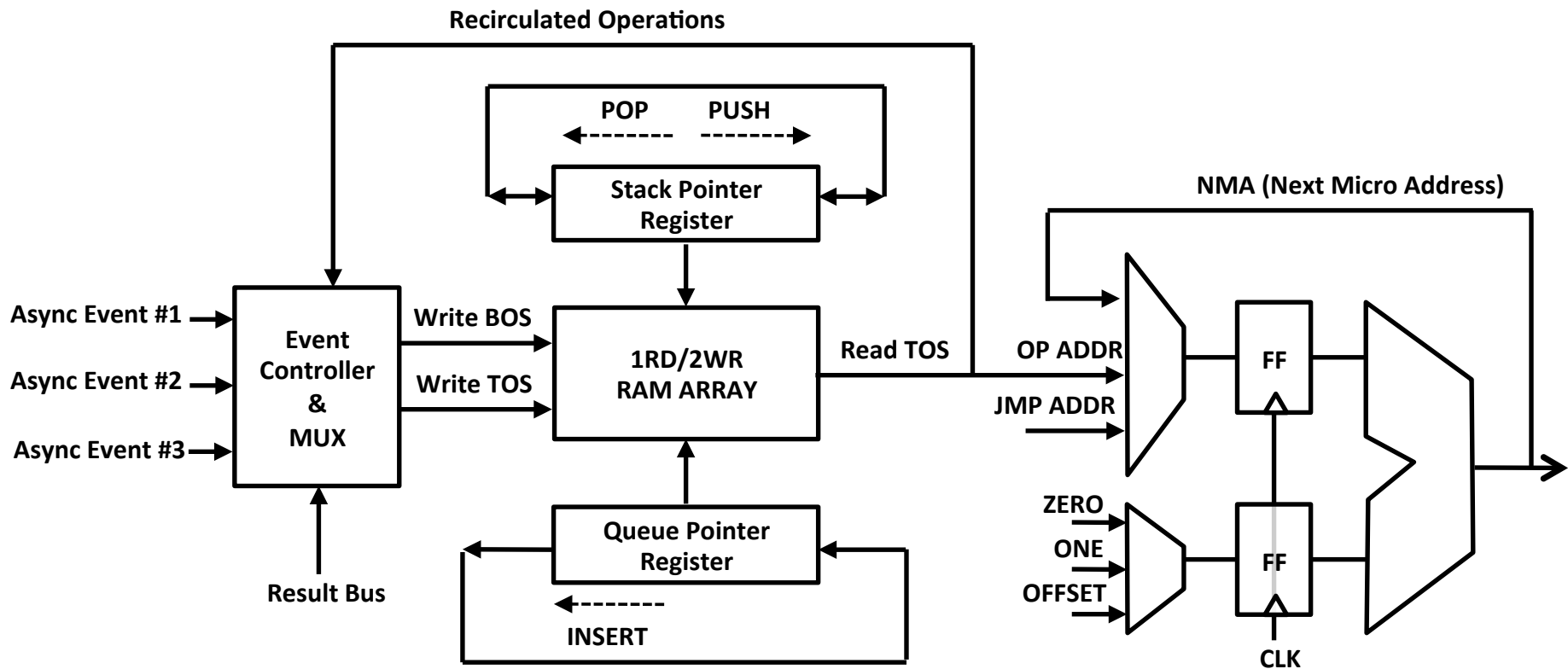- Sequences through a set of microcoded Actors to perform DPE functions.
- Asynchronous events inject special Actors into the sequence
 - Event Actors are squashed when completed



Microcode fields

Micro-engine control:

IMMED DATA <95:80>	BRANCH OFFSET <79:73>	LOOP COUNTER NUM <72:71>	REPEAT COUNT <70:68>	UCODE OP <67:64>
--------------------------	-----------------------------	-----------------------------------	----------------------------	------------------------

Datapath control:

SHFT MODE B <45>	SHFT MODE A <44>	SHFT B <43:39>	SHFT A <38:34>	SHFT TC B <33>	SHFT TC A <32>	MULT <31>	SAT <30>	DP EN <29>	ADD/SUB <28>
---------------------------	---------------------------	----------------------	----------------------	-------------------------	-------------------------	--------------	-------------	------------------	-----------------

Queued-Stack control for next operand selection:

READ TOS QS2 <63>	READ TOS QS1 <62>	READ BOS QS2 <61>	READ BOS QS1 <60>	QS2 CTL <59:56>	QS1 CTL <55:52>	B_BUS MUX <51:50>	A_BUS MUX <49:48>	CHAN MUX QS2 <47>	CHAN MUX QS1 <46>
----------------------------	----------------------------	----------------------------	----------------------------	-----------------------	-----------------------	-------------------------	-------------------------	----------------------------	----------------------------

Queued-Stack control for write-back operations:

QS2 BUS SEL <23:22>	QS1 BUS SEL <21:20>	WB MUX SEL <18:17>	RQS CTL <9:6>	RD RQS <4>	RQS BUS MUX <3>
------------------------------	------------------------------	-----------------------------	---------------------	------------------	--------------------------


SFU & I/O control:

LOGIC OP <16:14>	SFU OP <13:11>	WR SFU LAT <10>	WR EQ LAT <5>	FIFO WE <2>	GPIO WE <0>
------------------------	----------------------	--------------------------	------------------------	-------------------	-------------------

Agenda

- System overview
- Dataflow Processing Element (DPE)
 - Queues (FIFO), Stacks (LIFO), Queued-Stacks
 - Datapaths
 - Lookup Tables
 - Microcode Control
 - **Finite State Machines (FSM)**
- On-chip Networks
 - Serializers & Deserializers (SERDES)
 - Cross bar switches
 - Arbiters

Communicating FSM Control Flow

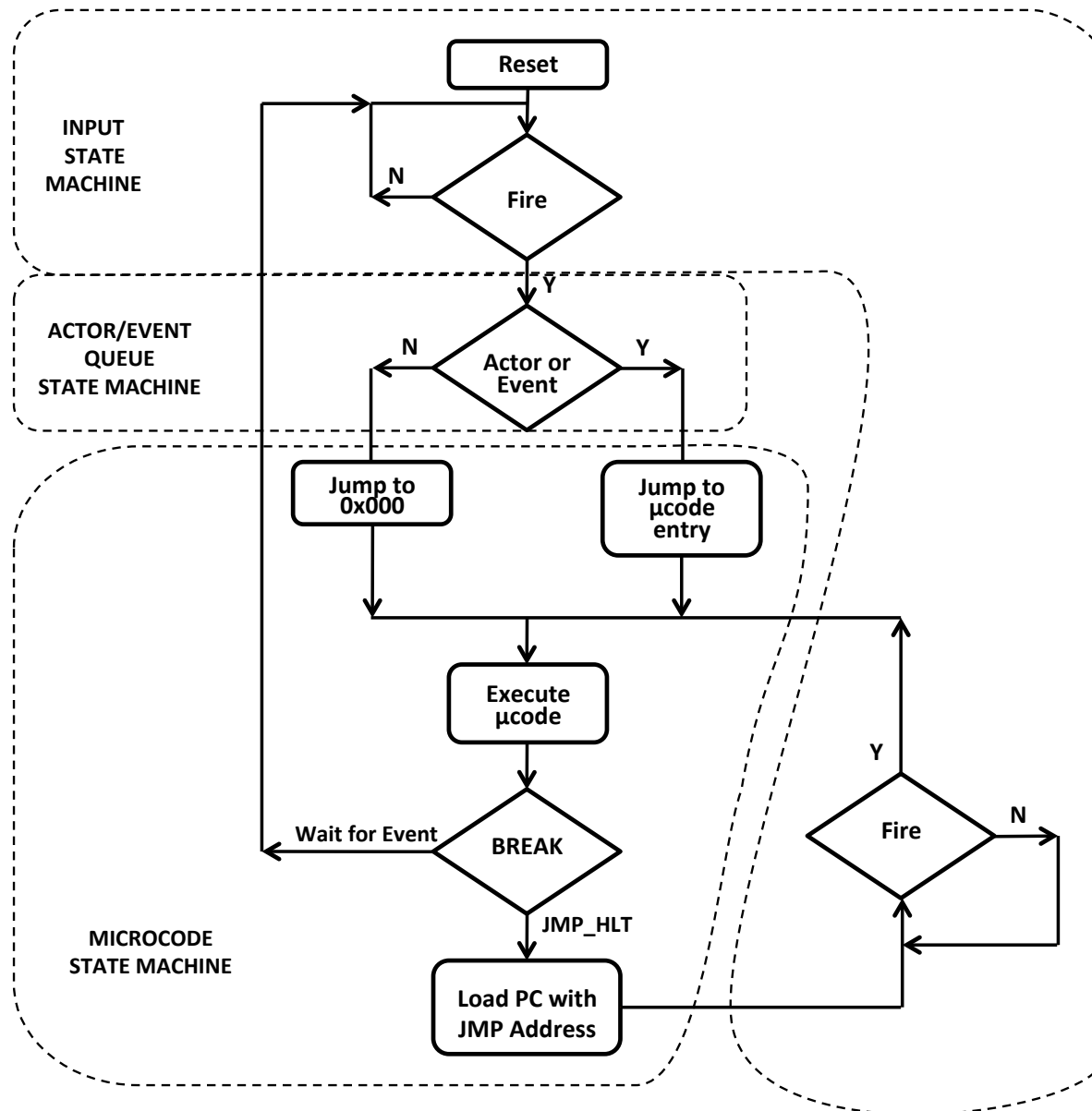

Master FSM Verilog Code

```

// -----
//          MASTER STATE MACHINE
// -----

always @(posedge clk or negedge reset_b) begin
    if (!reset_b) begin          // In RESET
        state      <= 2'b0;      // Start in State 0
        sm_error   <= 1'b0;
        cpe_hold_out <= 1'b1;    // Disable channel data to CPE
        chan_insert <= 1'b0;
        fire_early <= 1'b0;    // Negate signal
    end

// -----
// MAIN CONTROL LOOP
// -----

    else if (reset_b) begin

        // -----
        //          STATE 0
        // -----

        if ((!cpe_ready_in) && (state_0)) begin
            state      <= 2'b00;    // Stay in STATE 0
            cpe_hold_out <= 1'b0;    // Negate hold
        end

        else if ((cpe_ready_in) && (state_0)) begin
            state      <= 2'b01;    // GOTO STATE 1
        end

// -----
//          STATE 1
// -----

        else if (state_1) begin
            state      <= 2'b10;    // GOTO STATE 2
            chan_insert <= 1'b1;
        end

        else if ((!dwn_ctr_zd) && (state_2)) begin
            state      <=2'b10;    // Stay in STATE 2
        end

        else if ((dwn_ctr_zd) && (state_2)) begin
            state      <= 2'b11;    // GOTO STATE 3
            fire_early <= 1'b1;    // Start ucode engine
            cpe_hold_out <= 1'b1;
            chan_insert <= 1'b0;
        end

// -----
//          STATE 3: Wait for ucode engine to complete processing
// -----

        else if ((!ucode_idle) && (state_3)) begin
            state      <= 2'b11;    // Stay in STATE 3
            fire_early <= 1'b0;    // Negate fire -
            // ucode engine is running
        end

        else if ((ucode_idle) && (state_3)) begin
            state      <= 2'b00;    // GOTO STATE 0
            cpe_hold_out <= 1'b0;    // Negate hold
            fire_early <= 1'b0;
        end

    end // END of: else if (reset_b) begin

end // END of: always @(posedge clk or negedge reset_b) begin

```


Agenda

- System overview
- Dataflow Processing Element (DPE)
 - Queues (FIFO), Stacks (LIFO), Queued-Stacks
 - Datapaths
 - Lookup Tables
 - Microcode Control
 - Finite State Machines (FSM)
- **On-chip Networks**
 - **Serializers & Deserializers (SERDES)**
 - **Cross bar switches**
 - **Arbiters**


NOC Topologies

- **Heritage of networks with new constraints**
 - Need to accommodate interconnects in a 2D layout
 - Cannot route long wires (clock frequency bound)

 
- a) SPIN,
- b) CLICHE' & Mesh
- c) Torus
- d) Folded torus
- e) Octagon
- f) BFT



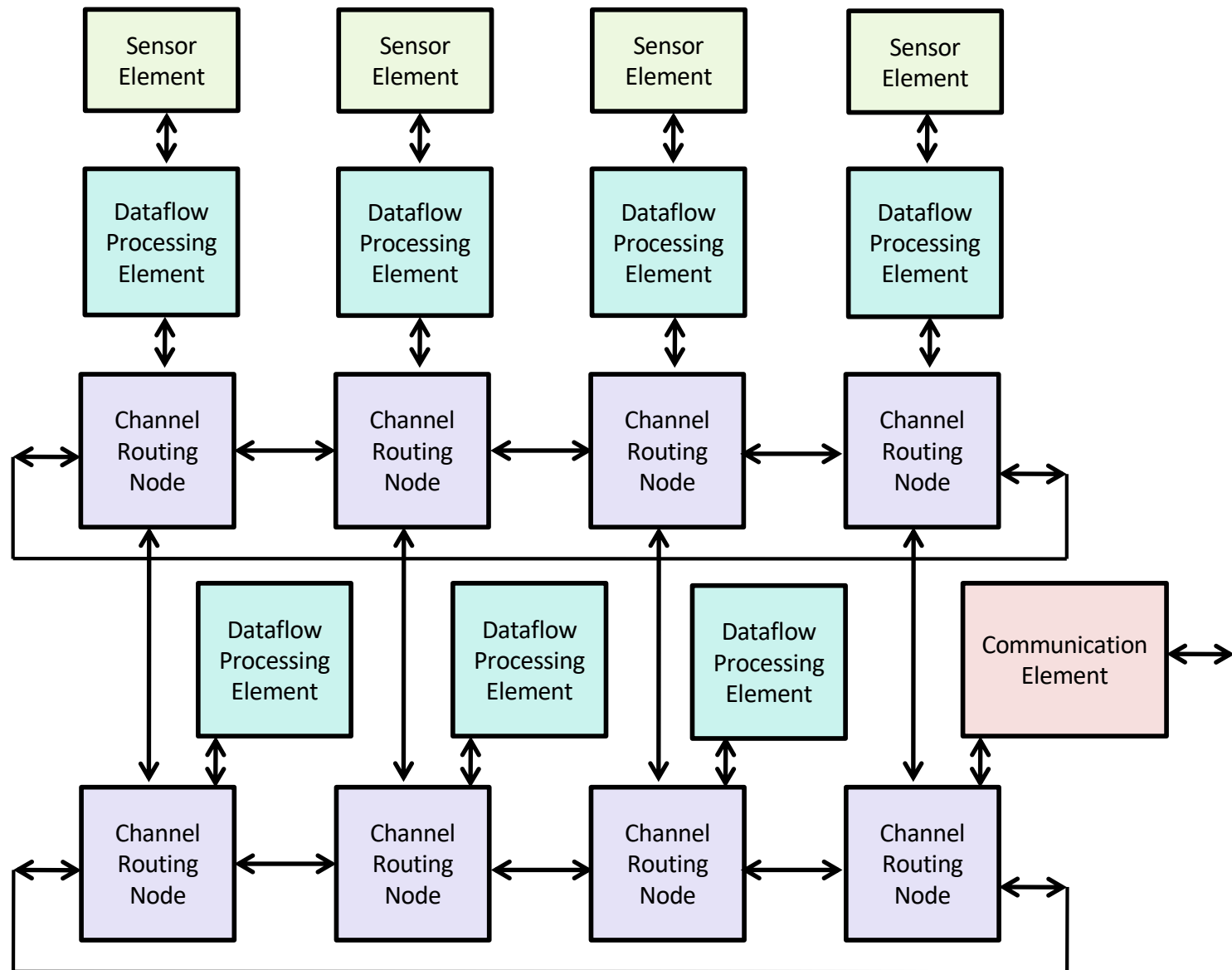Multiple DPEs connected via Channel Routers




Typical NoC Router

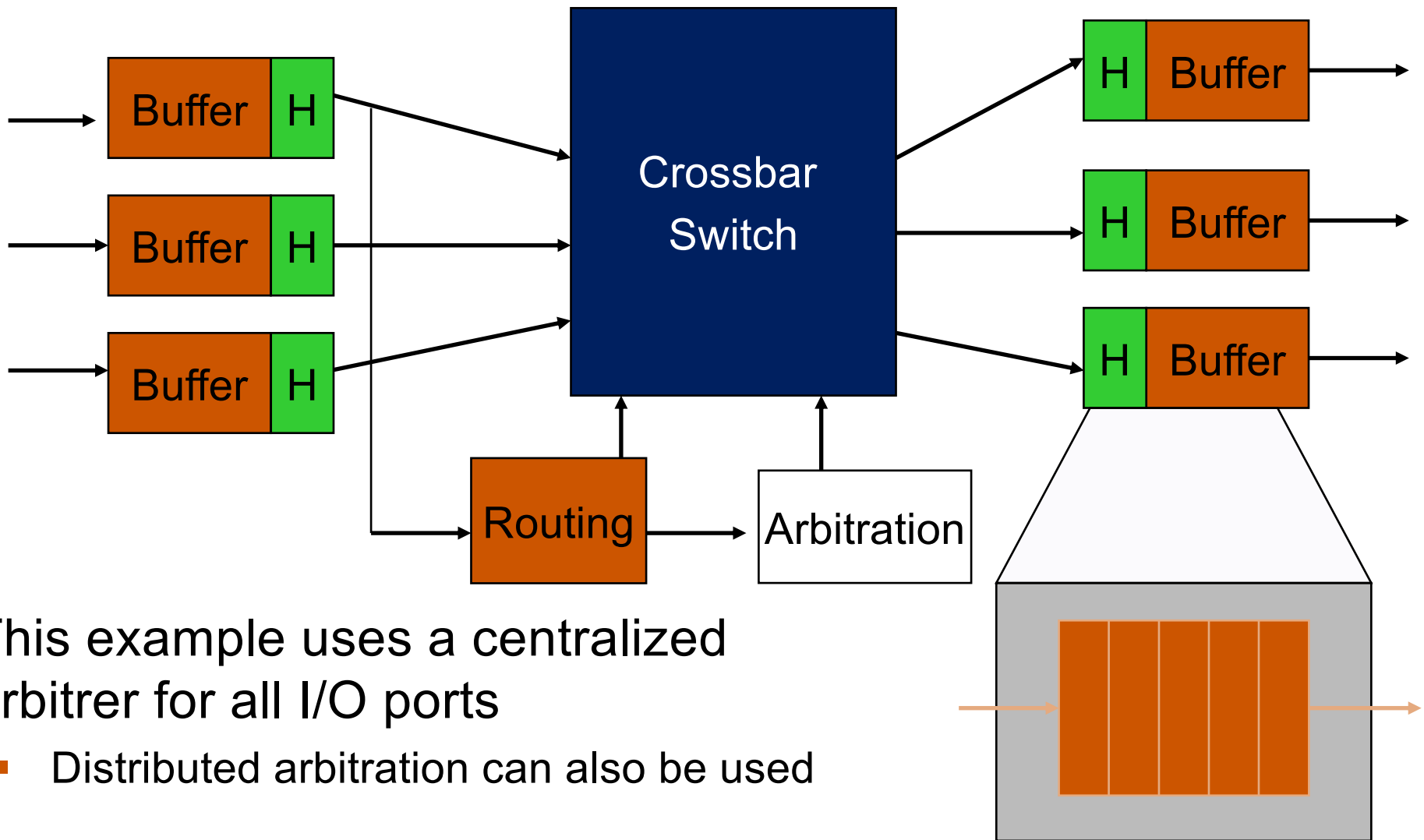

- This example uses a centralized arbiter for all I/O ports
 - Distributed arbitration can also be used

Channel Router Node

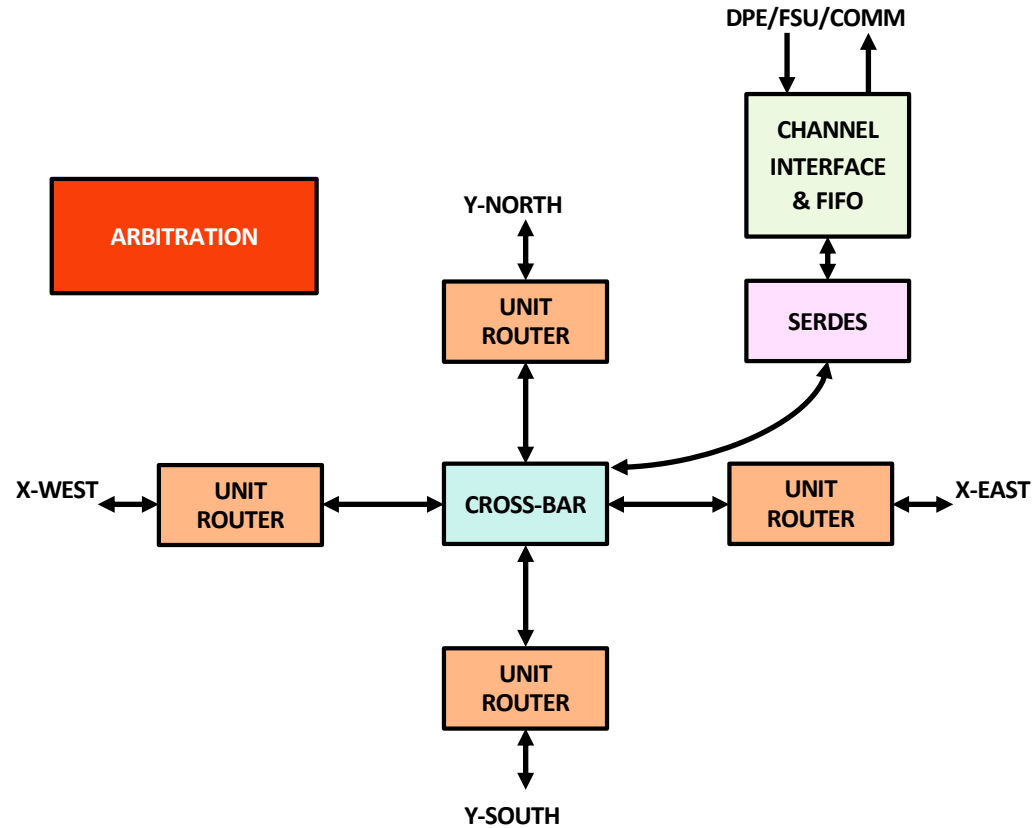


Agenda


- System overview
- Dataflow Processing Element (DPE)
 - Queues (FIFO), Stacks (LIFO), Queued-Stacks
 - Datapaths
 - Lookup Tables
 - Microcode Control
 - Finite State Machines (FSM)
- On-chip Networks
 - **Serializers & Deserializers (SERDES)**
 - Cross bar switches
 - Arbiters

Serializers & Deserializers (SERDES)

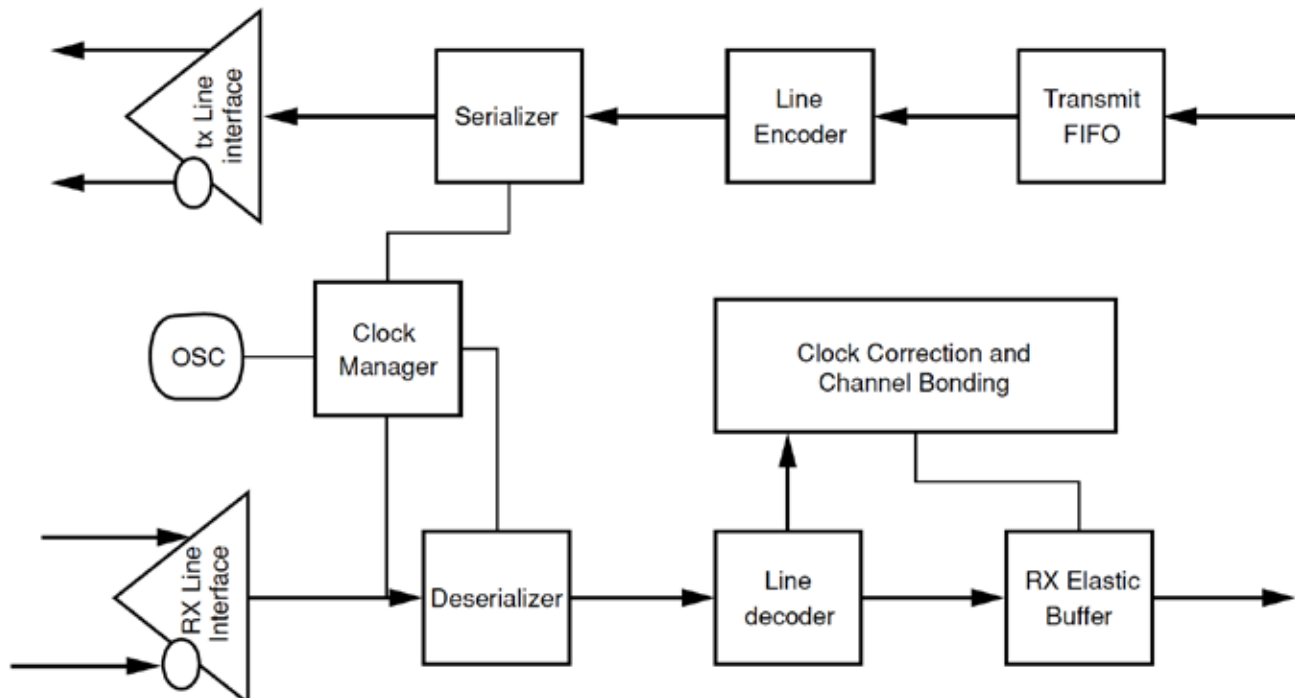- **SERializer**
 - Takes n bits of parallel data changing at rate y and transforms them into a serial stream at a rate of n times y .
- **DESerializer:**
 - Takes serial stream at a rate of n times y and changes it into parallel data of width n changing at rate y .




LFSR Based Scrambler/Descrambler

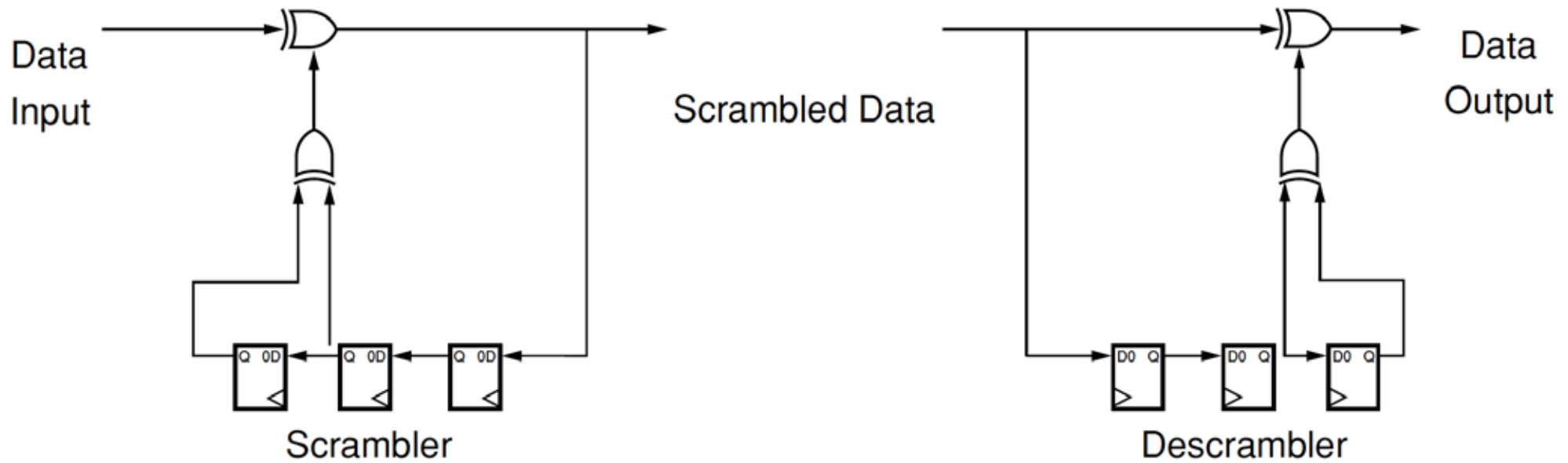

Agenda


- System overview
- Dataflow Processing Element (DPE)
 - Queues (FIFO), Stacks (LIFO), Queued-Stacks
 - Datapaths
 - Lookup Tables
 - Microcode Control
 - Finite State Machines (FSM)
- On-chip Networks
 - Serializers & Deserializers (SERDES)
 - **Cross bar switches**
 - Arbiters

Crossbar Switching System

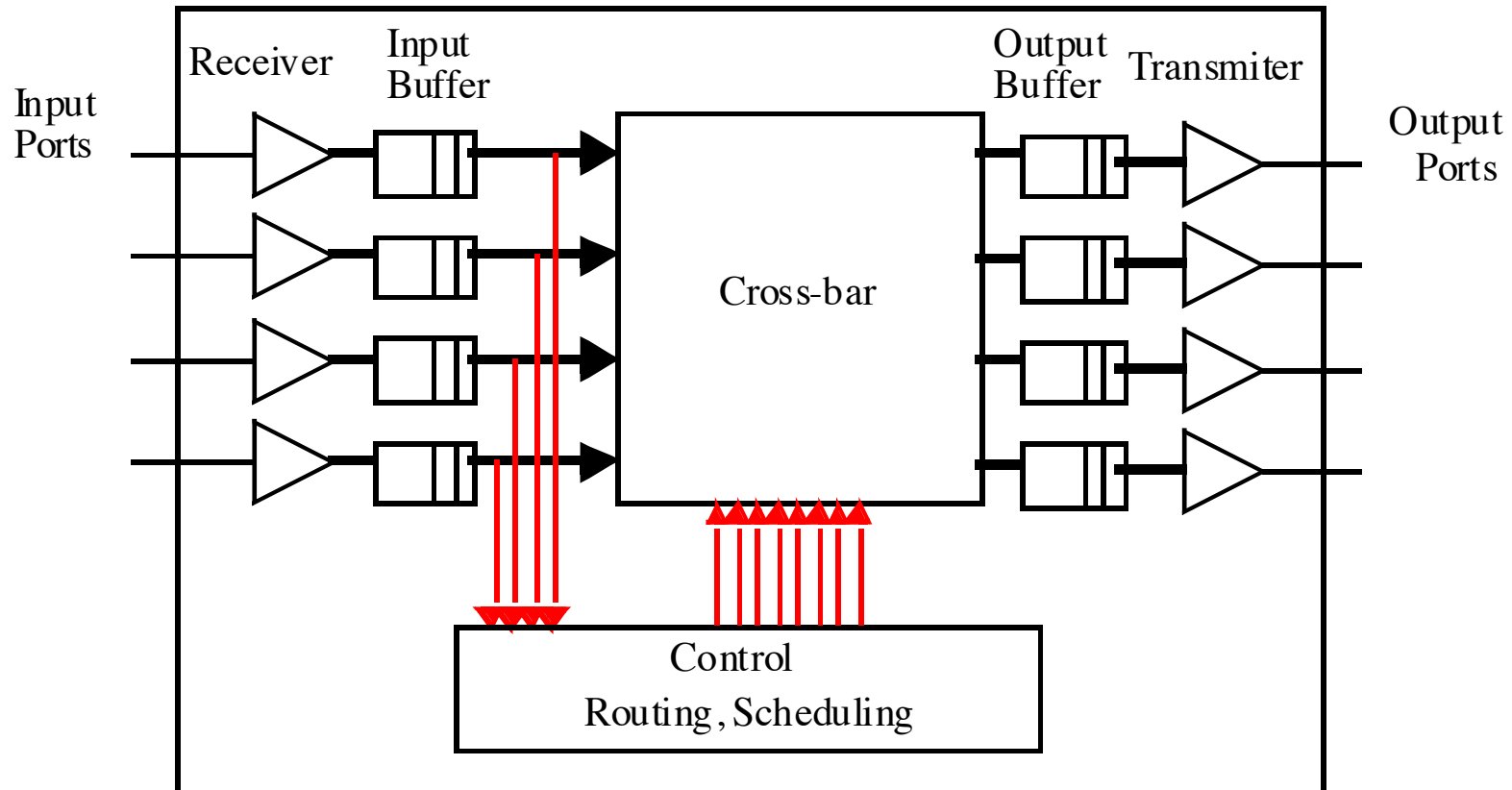


Complexity $O(N^2)$ for an $N \times N$ Crossbar

Crossbar Switch Design

 

 Multiplexors are controlled from the arbiter/controller/scheduler





N^2 switches \Rightarrow Cost $O(N^2)$

Time taken by the arbiter = $O(N^2)$

Agenda


- System overview
- Dataflow Processing Element (DPE)
 - Queues (FIFO), Stacks (LIFO), Queued-Stacks
 - Datapaths
 - Lookup Tables
 - Microcode Control
 - Finite State Machines (FSM)
- On-chip Networks
 - Serializers & Deserializers (SERDES)
 - Cross bar switches
 - **Arbiters**

Tree Arbiter Element

 
 


Tree-Arbiter Element

Multiway Arbiters

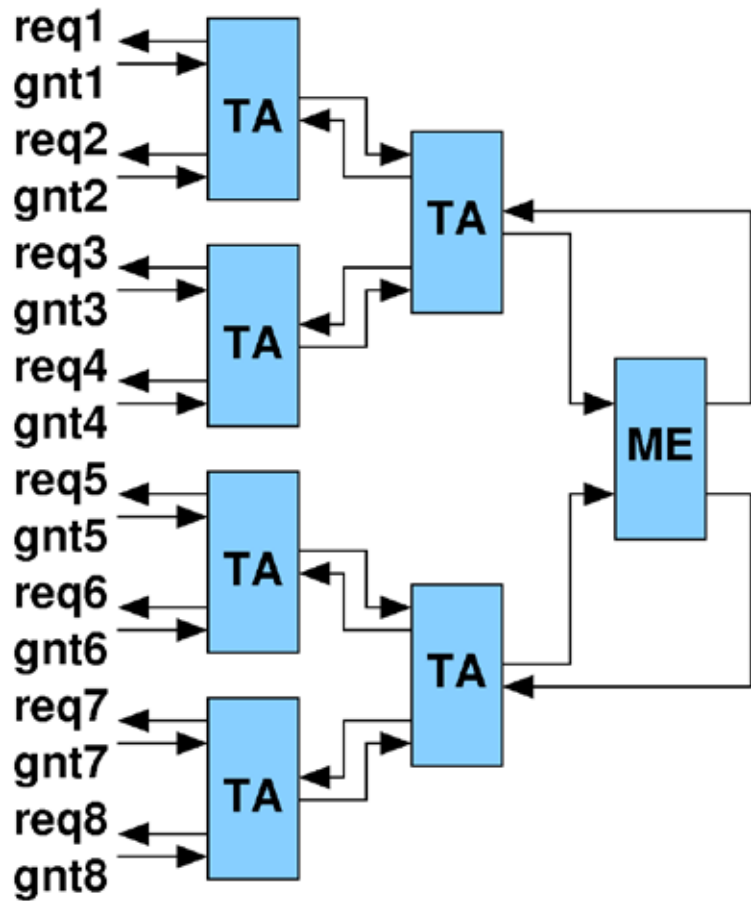


Tree Arbitrer

  

Cascaded MUTEXes

Static Priority Arbiters

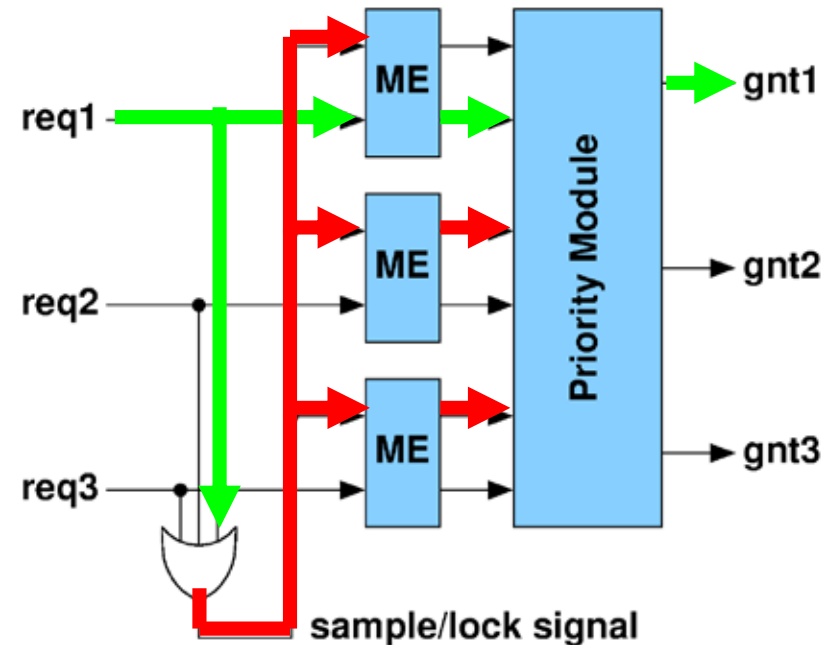- **“Priority Arbiters”**
Bystrov/Kinniment/Yakovlev (ASYNC’00)
- **First stage samples/locks current request vector**
- **Static or dynamic priority**
- **Original design updated to tackle performance and QoS issues**
Felicijan/Bainbridge/Furber (ICM’03)



Basis for sample/lock and prioritise arbiter

Mullins, Cambridge