

---

# **Lecture 19: Circuit Pitfalls, Tip & Tricks**

**Mark McDermott**  
**Electrical and Computer Engineering**  
**The University of Texas at Austin**

# Agenda

---


- **Circuit Pitfalls**
- **Circuit Tips & Tricks**
- **Circuit Robustness**
  - **Noise**
  - **Reliability**

# Bad Circuit 1

---

## ■ Circuit

- 2:1 multiplexer

 

## ■ Symptom

- Mux works when selected D is 0 but not 1
- Or fails at low VDD
- Or fails in SFSF corner


## ■ Principle: Threshold drop

- X never rises above  $VDD - V_t$
- $V_t$  is raised by the body effect
- The threshold drop is most serious as  $V_t$  becomes a greater fraction of VDD

## ■ Solution: Use transmission gates, not pass transistors

# Bad Circuit 2

- **Circuit**
  - Latch

 


- **Symptom**
  - Load a 0 into Q
  - Set  $f = 0$
  - Eventually Q spontaneously flips to 1

- **Principle: Leakage**

- X is a dynamic node holding value as charge on the node
- Eventually subthreshold leakage may disturb charge

- **Solution: Refresh node with feedback**

 
- Or periodically refresh node (requires fast clock, not practical processes with big leakage)



# Bad Circuit 3

- **Circuit**

- Domino AND gate

 


- **Principle: Leakage**

- X is a dynamic node holding value as charge on the node
- Eventually subthreshold leakage may disturb charge

- **Solution: Keeper**

- **Symptom**

 - Precharge gate (Y=0)
- Then evaluate
- Eventually Y spontaneously flips to 1




# Bad Circuit 4

---

- **Circuit**

- Pseudo-nMOS OR

 

- **Symptom**

- When only one input is true,  $Y = 0$
- Perhaps only happens in SF corner


- **Principle: Ratio Failure**

- nMOS and pMOS fight each other.
- If the pMOS is too strong, nMOS cannot pull X low enough.

- **Solution: Check that ratio is satisfied in all corners**


# Bad Circuit 5

- **Circuit**
  - Latch

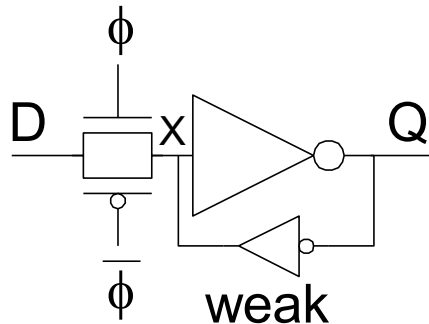

- **Symptom**
  - Q stuck at 1.
  - May only happen for certain latches where input is driven by a small gate located far away.

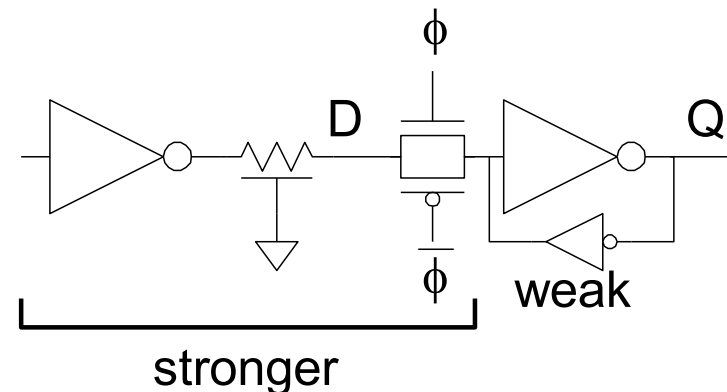
- **Principle: Ratio Failure (again)**
  - Series resistance of D driver, wire resistance, and pass-gate must be much less than weak feedback inverter.
- **Solutions: Check relative strengths**
  - Avoid un-buffered diffusion inputs where driver is unknown



# Bad Circuit 6

## ■ Circuit

- Domino AND gate

 

## ■ Symptom

- Precharge gate while
- $A = B = 0$ , so  $Z = 0$
- Set  $f = 1$
- A rises
- Z is observed to sometimes rise

## ■ Principle: Charge Sharing


- If X was low, it shares charge with Y

## ■ Solutions: Limit charge sharing

- Safe if  $C_Y \gg C_X$

$$V_x = V_Y = \frac{C_Y}{C_x + C_Y} V_{DD}$$

- Or precharge node X too

 




# Bad Circuit 7

---

## ■ Circuit

- Dynamic gate + latch

 

## ■ Principle: Charge Sharing

- If Y was low, it shares charge with X

## ■ Solution: Buffer dynamic nodes before before

- driving transmission gate


## ■ Symptom

- Precharge gate while transmission gate latch is opaque
- Evaluate
- When latch becomes transparent, X falls

# Bad Circuit 8

## ■ Circuit

- Latch

 


## ■ Principle: Diffusion Input Noise Sensitivity

- If  $D < -V_t$ , transmission gate turns on
- Most likely because of power supply noise or coupling on  $D$

## ■ Solution: Buffer $D$ locally
 
## ■ Symptom



- $Q$  changes while latch is opaque
- Especially if  $D$  comes from a far-away driver


  
# Bad Circuit 9


- **Circuit**
  - Anything
- **Symptom**
  - Some gates are slower than expected

Principle: Hot Spots and Power Supply Noise




# Bad Circuit 10: Extremely Large Gate Delays

---

 

Node with very large gate delays are susceptible to noise.

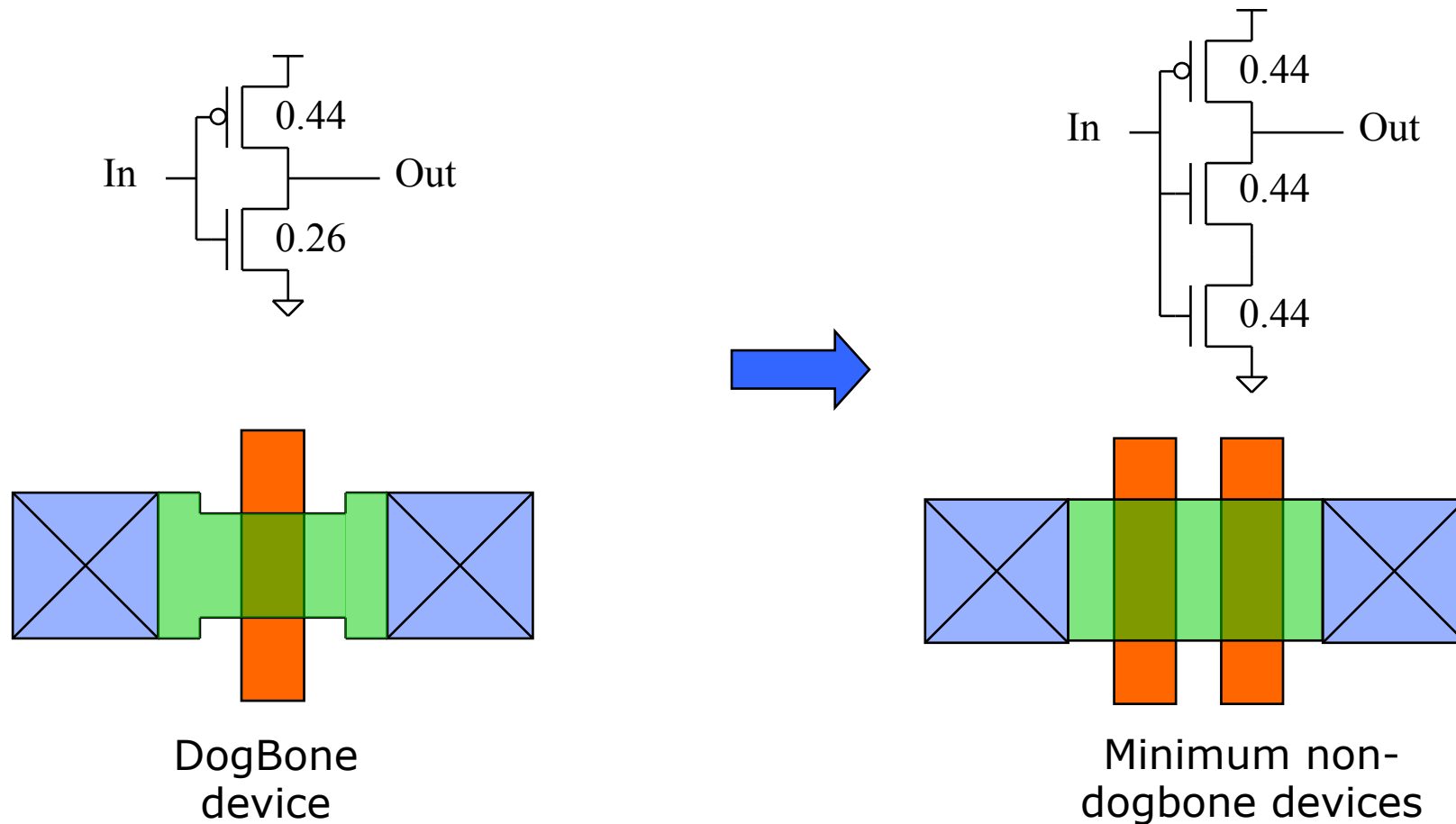
# Bad Circuit 11: DogBone Devices in Forward Path



Dog-Bone devices and non-minimum length devices have very large variations in their delay and should only be used for keepers.

# Bad Circuit 12: Charge Sharing Tristates


---

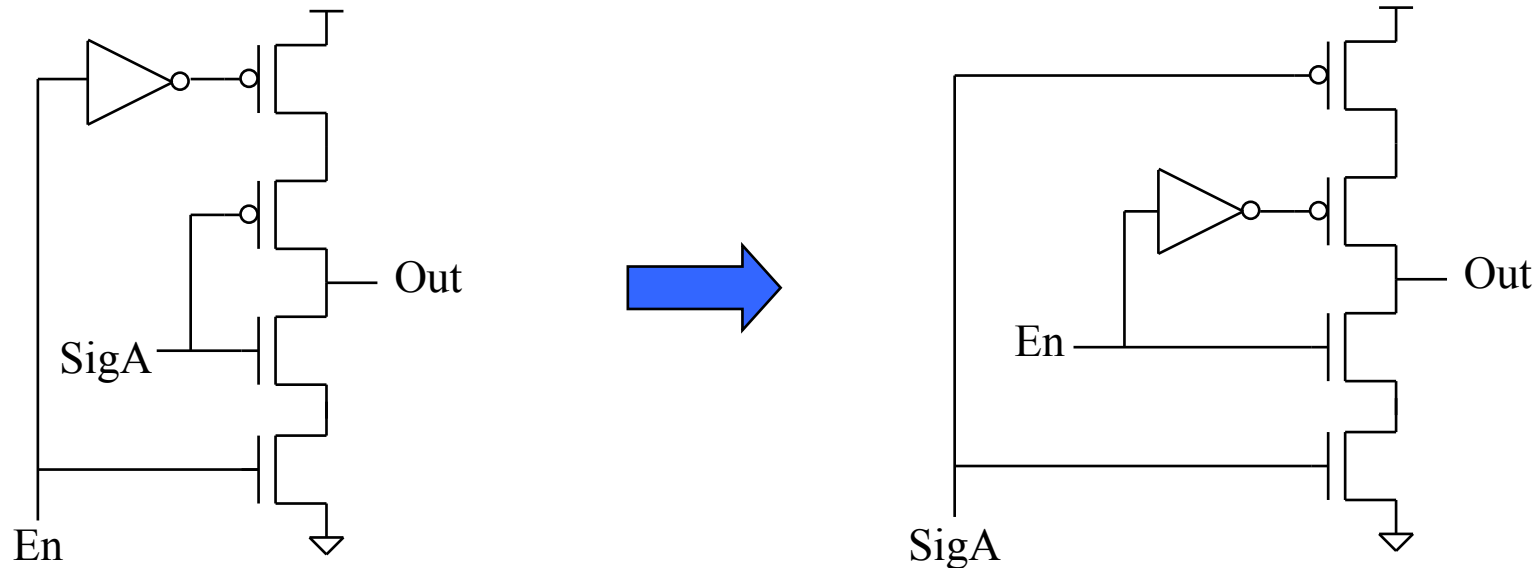

Placing data on the inside of a tristate allows charge sharing as well as extra capacitance on the output.



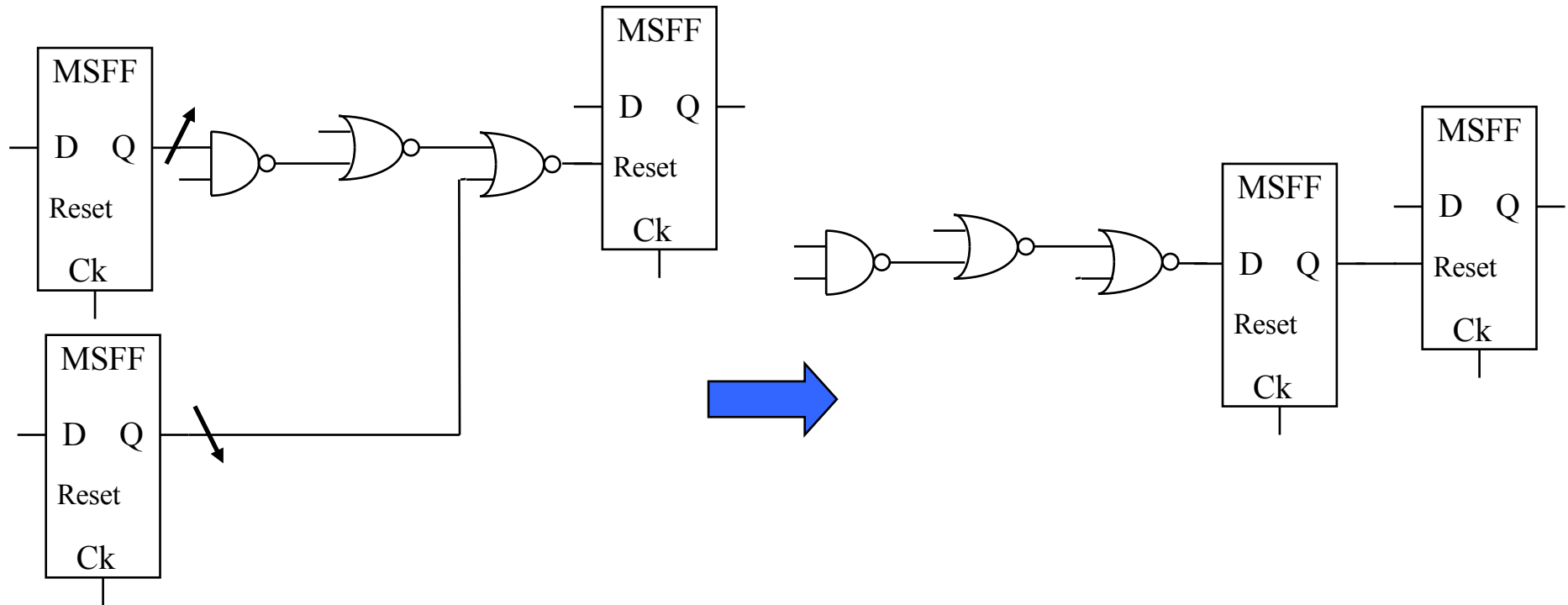
# Bad Circuit 14: Asynchronous Signals Driven from Logic



Logic glitches can trigger asynchronous resets improperly.




# Bad Circuit 15: Back-writing

 

Weakly held nodes driving directly into pass gates can have their data accidentally overwritten.

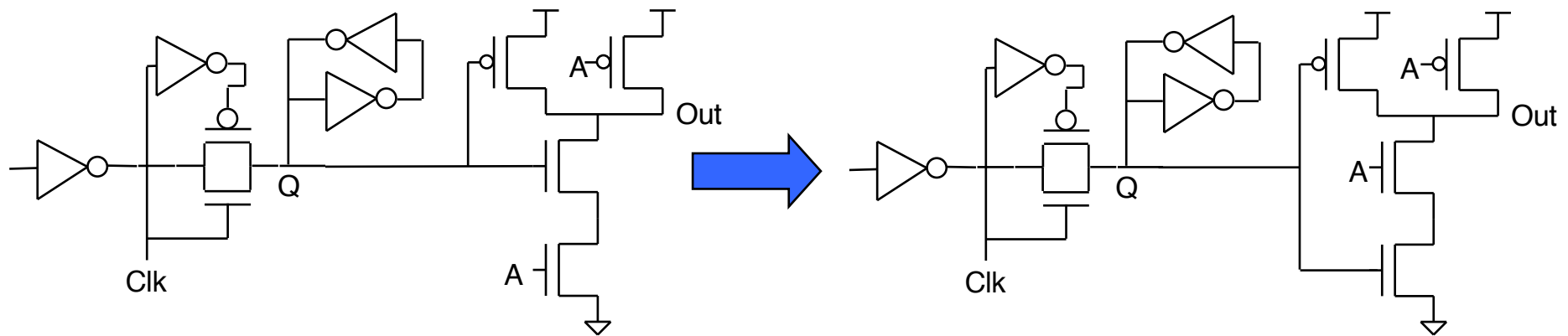
## Bad Circuit 16: Gate-to-Drain Coupling into Weakly Held Node



Weakly held nodes can be disturbed by gate to drain capacitance dramatically increasing gate delay.

## Bad Circuit 17: Oversized Keeper in Distributed Domino Gate

---

 

Significant RC between the pulldowns can prevent the keeper from being easily overcome.

Distributing multiple keepers with the pulldowns can allow for better noise immunity and delay.

---

# Circuit Tips & Tricks

# Outline

---

## ■ **MaxDelay Solutions**

- Every path has a maximum delay to be captured properly when running at frequency
- Most MaxDelay solutions make MinDelay worse


## ■ **MinDelay Solutions**

- Every path has a minimum delay to avoid false capture.
- Most MinDelay solutions make MaxDelay worse

## ■ **Circuit Pitfalls**

- Circuits topologies which can cause unexpected failures

# Review: Max-Delay & Min-Delay

 

**MAXDELAY:**  $T_{max} < T_{cycle} - T_{setup} - T_{maxskew}$


**MINDELAY:**  $T_{min} > T_{hold} + T_{minskew}$

---

# Max-Delay Solutions

# Use Late Signals Last

Assume the SigA is the critical path

 



Latest signals should be used in the last stages of logic.

**Con:** Slows down other paths


  
# Use Late Signals Last (II)

**Shannon's Theorem:**  $F(a,b,c) = (a\# \& F(0,b,c)) \mid (a \& F(1,b,c))$




Shannon's theorem allows any logic function to be rewritten to favor a late arriving input.

**Con:** Slows down other paths  
Can dramatically increase area

# Size Up Gates

---

 




Best gates to size up are those in the critical path having the largest delays and those after long wires.

**Con:** Increases area  
Increases power

# Combine Gates

---

Assume the SigA is the critical path

   


AOI gates are slow but faster than multiple gates.

**Con:** Slows down other paths

# Embed Logic in Latches

---

 


Logic gates can be used to drive or receive state nodes.

**Con:** Increases clock load  
Library characterization difficult

# Use Low Vt Devices

---


 


Low threshold devices turn on at lower voltages and provide more current when on.

**Con:** Increased power due to leakage

# Skew P/N Ratio

Assume rise of SigA is the critical path

  


Gate delay can be reduced by 15-25% by skewing P/N ratio

**Con:** Slows down opposite transition  
Reduces noise margins

# Late Signals Closest to Output

Assume the SigA is the critical path

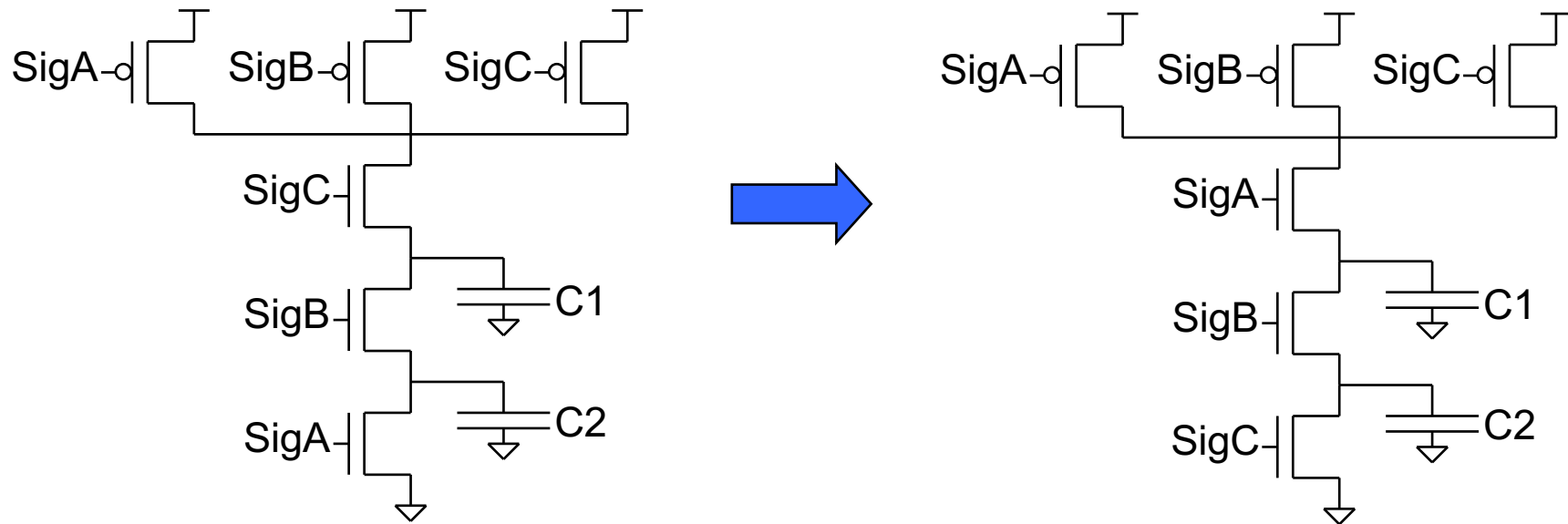


Placing critical path signal at the top of a series stack allows intermediate capacitances to switch early.

**Con:** Slows down other paths

# Taper Series Stacks

Assume rise of SigA is the critical path

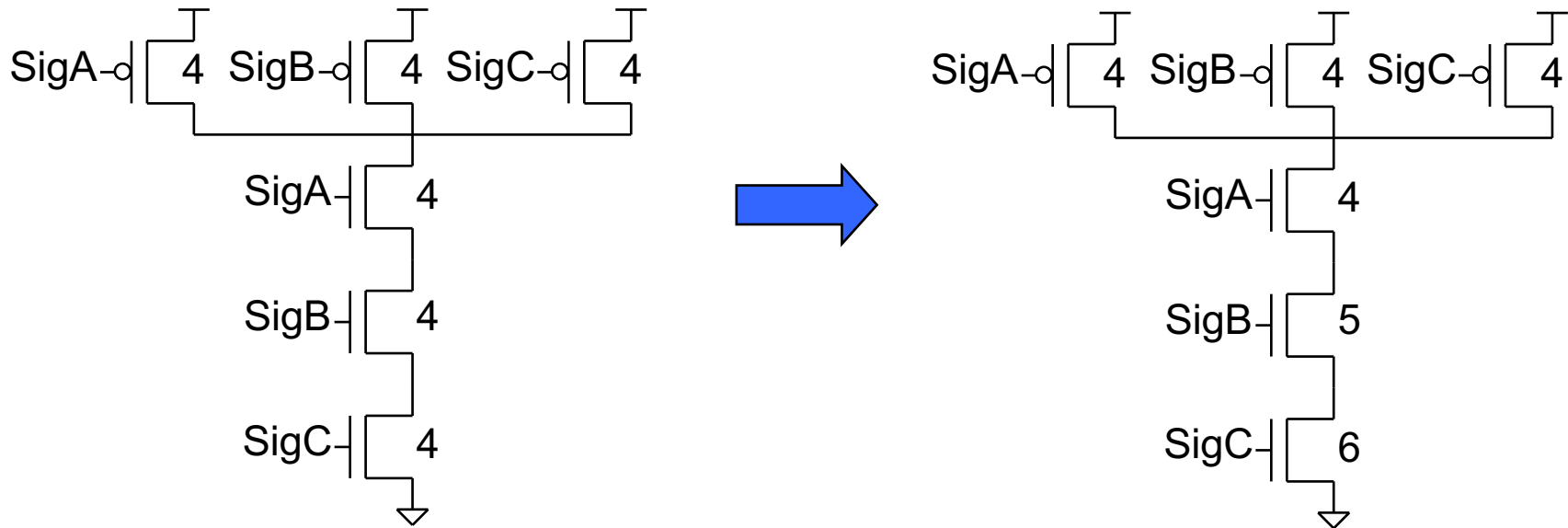


Larger devices at bottom of stack allow more current through top device.

**Con:** Slows down other paths  
Less regular layout



# Size Down Parallel Devices

Assume fall of SigA is the critical path

 


Larger devices at bottom of stack allow more current through top device.

**Con:** Slows down other paths  
Less regular layout

# Shield Critical Signals

Assume the SigA is the critical path

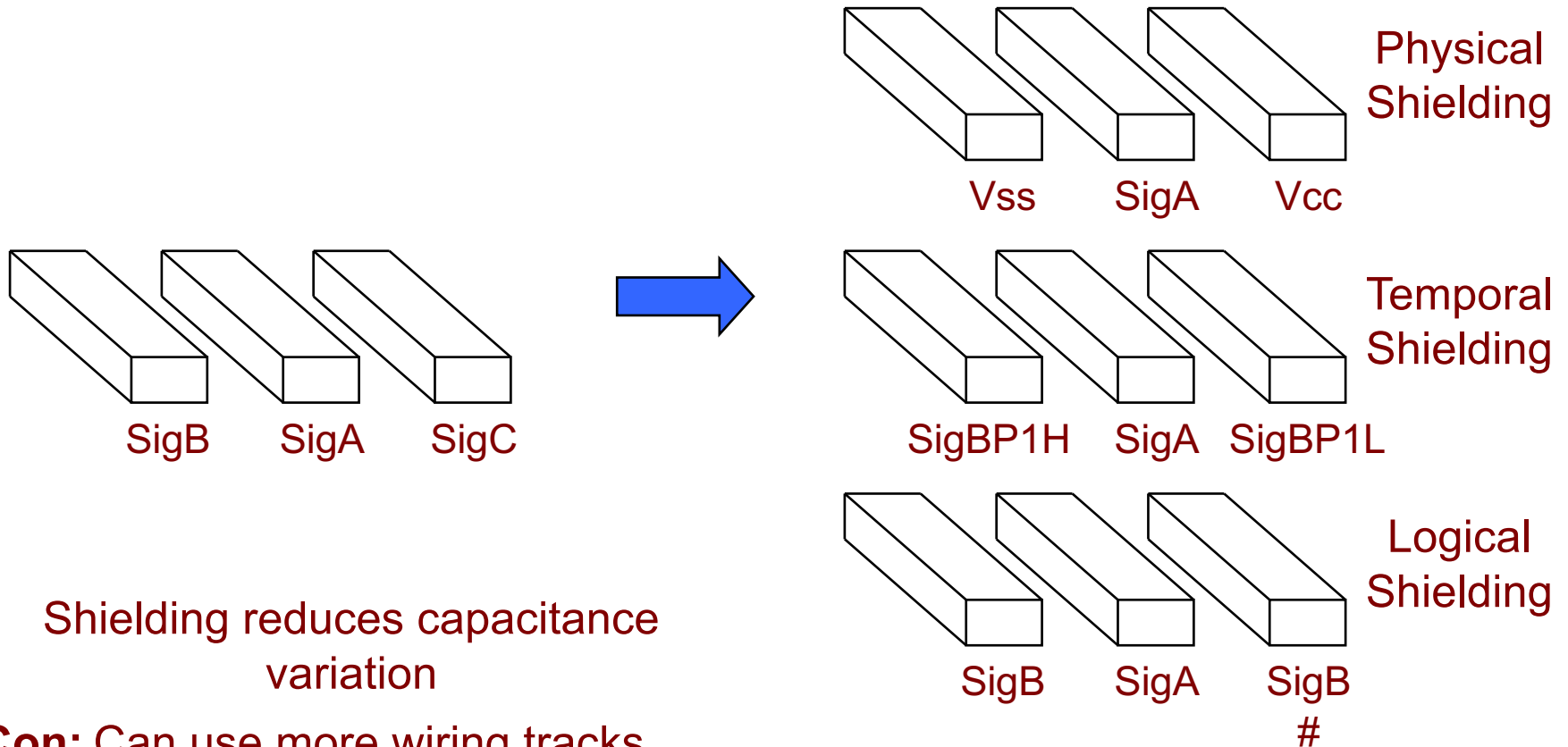

Shielding reduces capacitance variation


**Con:** Can use more wiring tracks

Shielding simultaneously improves maxdelay and mindelay.

# Increase Wire Spacing

---

Assume the SigA is the critical path

 


Increased wire spacing reduces total wire capacitance.

**Con:** Uses more wiring tracks

# Increase Wire Width

---

Assume the SigA is the critical path

 

When wire RC is significant, increasing wire width can reduce delay.


**Con:** Uses more wiring tracks  
Increases wire capacitance

A tapered wire may give the best delay but is a nuisance to layout.

# Use Higher Metal Layer

---

Assume the SigA is the critical path

 


Because higher level metals are thicker they have less resistance even at the same width.

**Con:** Takes tracks from global routes

# Buffer Side Loads

Assume OutB is not on critical path

 


Prevent the critical path from being slowed by large loads not on the critical path.

**Con:** Slows down other paths  
Increases area

# Add Repeaters

---

 


For routes longer than 1mm a repeater can reduce the total delay.

**Con:** Increases area

# Move Logic Across Sequentials

---

 


Cycles with maxdelay margin can be used to improve help other cycles

**Con:** Increases delay in other cycle  
May increase clock load




# Delay Receiver Clock

 

Delayed clocks allow logic to be divided into unequal pipestages.

**Con:** Mindelay significantly worse  
Reduces time in next pipestage  
Increases clock skew

# Closer Common Point for Clocks

 


A closer common point reduces clock skew.

**Con:** Reduces opportunities for clock gating  
May increase global clock load

Reduced clock skew improves maxdelay and mindelay.

# Speed Up Latch Feedback

 


Faster inverter in feedback loop can reduce latch setup time.

**Con:** Very small improvement  
Eventually start to slow latch node

# Design for Time Borrowing


---

 

Transparent sequentials can allow skew penalties to be avoided by allowing time borrowing.

**Con:** May increase clock load  
More difficult timing analysis

# Convert Static Logic to Domino

 


Domino speeds one transition by skewing the P/N ratio and adds precharge devices to keep the other transition from becoming the critical path.

**Con:** More design time  
More clock load  
More power  
More sensitive to noise

# Add Pipestages

---

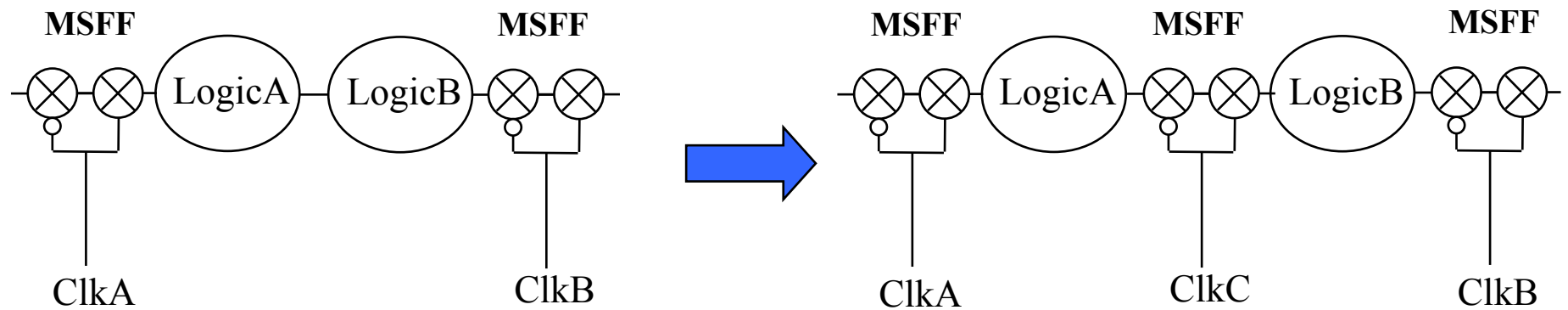

Any path can have its frequency increased by adding pipestages.


**Con:** Reduces IPC  
Increases clock load  
Increases area

---

# Min-Delay Solutions

# Add Buffers

---

 


Shortest paths between  
sequentials can be made  
longer by adding buffers.

**Con:** Increases area



# Size Down Gates

---



 


Best gates to size down are those in having the smallest delays and those driving long wires.

**Con:** Long routes more susceptible to coupling

# Skew P/N Ratio

Assume fall of SigA is critical race


 
 
 


Allows races to be improved for one particular transition.

**Con:** Reduces noise margin  
Speeds up other transition

# Shield Critical Signals

Assume the SigA is the critical race

    


Shielding reduces capacitance variation

**Con:** Can use more wiring tracks

Shielding simultaneously improves maxdelay and mindelay.

# Move Logic Across Sequential


---

 

Careful partitioning of logic between cycles can fix maxdelay and mindelay failures.

**Con:** May increase clock load


# Delay Driver Clock

 

Delayed clocks allow logic to be divided into unequal pipestages.

**Con:** Reduces time in this pipestage  
Increases clock skew

# Closer Common Point for Clocks

 


A closer common point reduces clock skew.

**Con:** Reduces opportunities for clock gating  
May increase global clock load

Reduced clock skew improves maxdelay and mindelay.


# Change Phase-based to Cycle-based

 

Using only flip-flops allows a full cycle of logic between sequentials.

**Con:** Eliminates time borrowing

# Pulsed Latches

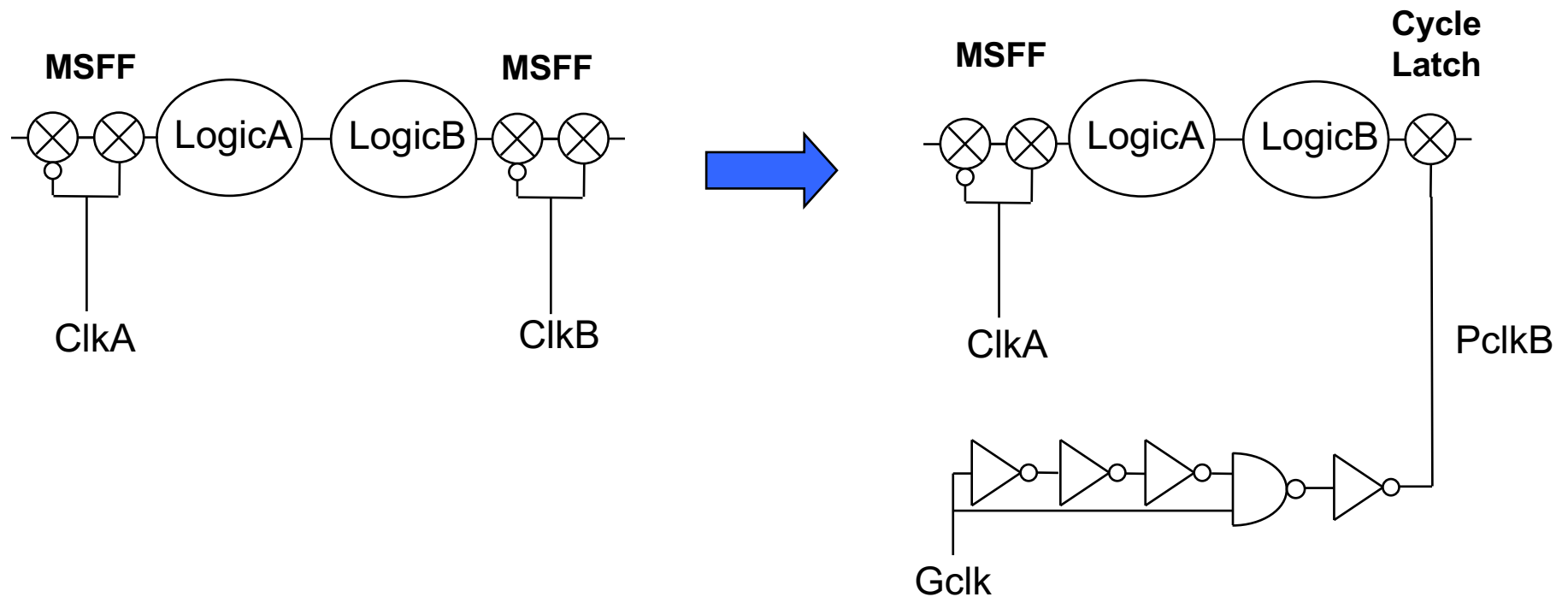


Reduce sequential overhead by replacing MSFF with latch driven by pulsed clock.

**Con:** Increased mindelay requirement  
More difficult timing analysis  
PulseWidth-to-Delay race created




# Speed Up Latch's Clock Inverter

 

Faster clock inverter closes pass gate sooner and reduces hold time.

**Con:** Very small improvement  
Increased clock load

# Change Jam Latch to Interrupted Keeper

 


State node can be made to switch faster by eliminating contention with the keeper.

**Con:** Very small improvement  
Increased clock load

# Timer Circuit

---

Assume fall of OutA is the critical race

 


Timing signal prevents switching before a well controlled delay.

**Con:** Increases clock load  
Increases area  
May not track with process variation

# Current Limiting Device

Assume fall of OutA is the critical race

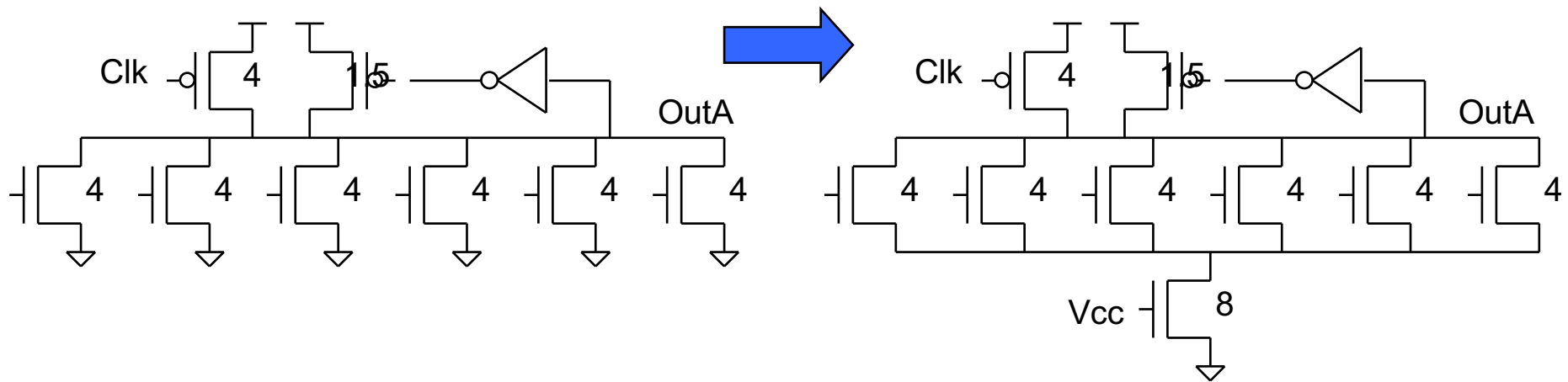

Added series device limits current when multiple parallel devices are on.

**Con:** Also slows single input switching

# Review

---

- **MaxDelay Solutions**
  - Many methods available most make mindelay worse
- **MinDelay Solutions**
  - Many methods available, most make maxdelay worse
- **Pitfalls**
  - Be careful with contention, floating, and weakly held nodes

---

# Circuit Robustness

# Noise

---

## ■ Sources

- Power supply noise / ground bounce
- Capacitive coupling
- Charge sharing
- Leakage
- Noise feedthrough


## ■ Consequences

- Increased delay (for noise to settle out)
- Or incorrect computations

# Reliability

---

- **Hard Errors**
- **Soft Errors**

 



# Electromigration

---

- “Electron wind” causes movement of metal atoms along wires
- Excessive electromigration leads to open circuits
- Most significant for unidirectional (DC) current
  - Depends on current density  $J_{dc}$  (current / area)
  - Exponential dependence on temperature

- Black’ s Equation: 
$$MTTF \propto \frac{e^{\frac{E_a}{kT}}}{J_{dc}^n}$$

- Typical limits:  $J_{dc} < 1 - 2 \text{ mA} / \mu\text{m}^2$

# Self-Heating

---

- **Current through wire resistance generates heat**
  - Oxide surrounding wires is a thermal insulator
  - Heat tends to build up in wires
  - Hotter wires are more resistive, slower
- **Self-heating limits AC current densities for reliability**

$$I_{rms} = \sqrt{\frac{\int_0^T I(t)^2 dt}{T}}$$

- Typical limits:  $J_{rms} < 15 \text{ mA} / \mu\text{m}^2$


# Hot Carriers

---

- **Electric fields across channel impart high energies to some carriers**
  - These “hot” carriers may be blasted into the gate oxide where they become trapped
  - Accumulation of charge in oxide causes shift in  $V_t$  over time
  - Eventually  $V_t$  shifts too far for devices to operate correctly
- **Choose  $V_{DD}$  to achieve reasonable product lifetime**
  - Worst problems for inverters and NORs with slow input rise time and long propagation delays

 
# Latchup

- **Latchup: positive feedback leading to  $V_{DD}$  – GND short**
  - Major problem for 1970s CMOS processes before it was well understood
- **Avoid by minimizing resistance of body to GND /  $V_{DD}$** 
  - Use plenty of substrate and well taps


 
# Guard Rings

- Latchup risk greatest when diffusion-to-substrate diodes could become forward-biased
- Surround sensitive region with guard ring to collect injected charge



# Overvoltage

---

- **High voltages can damage transistors**
  - Electrostatic discharge (ESD)
  - Oxide arcing
  - Punchthrough
  - Time-dependent dielectric breakdown (TDDB)
    - Accumulated wear from tunneling currents
- **Requires low  $V_{DD}$  for thin oxides and short channels**
- **Use ESD protection structures where chip meets real world**

# Soft Errors

---

- **In 1970s, DRAMs were observed to occasionally flip bits for no apparent reason**
  - **Ultimately linked to alpha particles and cosmic rays**
- **Collisions with particles create electron-hole pairs in substrate**
  - **These carriers are collected on dynamic nodes, disturbing the voltage**
- **Minimize soft errors by having plenty of charge on dynamic nodes**
- **Tolerate errors through ECC, redundancy**

# Summary

---

- **Static CMOS gates are very robust**
  - Will settle to correct value if you wait long enough
- **Other circuits suffer from a variety of pitfalls**
  - Tradeoff between performance & robustness
- **Very important to check circuits for pitfalls**
  - For large chips, you need an automatic checker
  - Design rules aren't worth the paper they are printed on unless you back them up with a tool