
VLSI-1 Course Review

Mark McDermott
Electrical and Computer Engineering
The University of Texas at Austin

Final Exam


- **December 15th, RLP 0.126, 9:00AM - 11:59AM**
- **Topics may include (but are not limited to):**
 - D Flip-Flop timing analysis
 - Combinational logic timing analysis
 - Combination logic transistor sizing
 - Circuit optimization and analysis
 - Fault testing
 - State machines, state diagrams, state tables, PLAs
 - Memory design
 - General knowledge questions about transistors, wires, capacitors, power, energy, etc.

Overview

- **Combinational logic**
- **Sequential logic**
- **Datapath**
- **Memories**
- **Scaling**

Simplified Design Rules


- Conservative rules to get you started

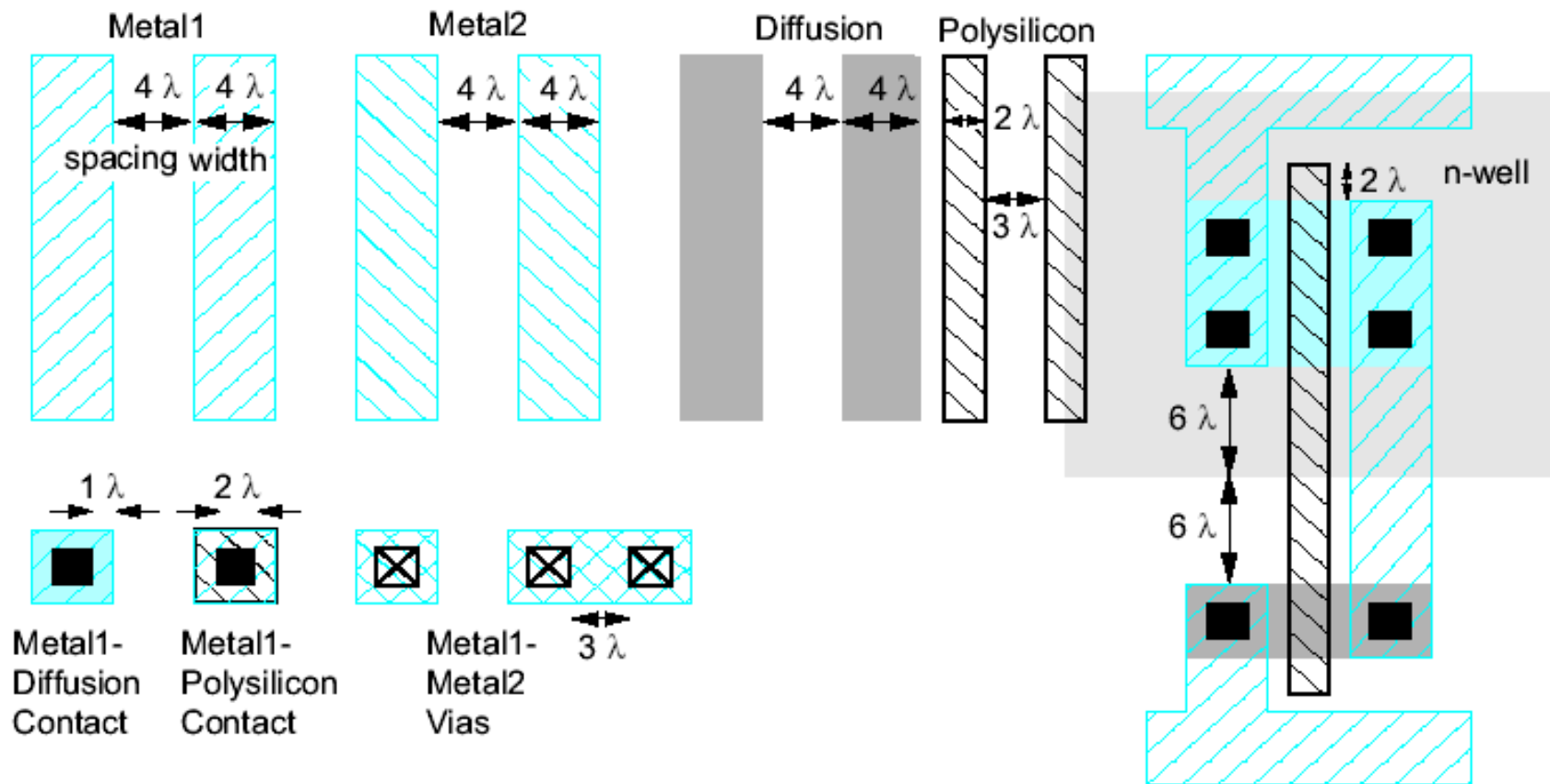

Complementary CMOS

- **Complementary CMOS logic gates**
 - nMOS *pull-down network*
 - pMOS *pull-up network*
 - a.k.a. static CMOS

	Pull-up OFF	Pull-up ON
Pull-down OFF	Z (float)	1
Pull-down ON	0	X (crowbar)

 



I-V Characteristics

- **In Linear region, I_{ds} depends on**
 - How much charge is in the channel?
 - How fast is the charge moving?

Channel Charge

- MOS structure looks like parallel plate capacitor while operating in inversion
 - Gate – oxide – channel
- $Q_{\text{channel}} = CV$
- $C = C_g = \epsilon_{\text{ox}} WL/t_{\text{ox}} = C_{\text{ox}} WL$
- $V = V_{\text{gc}} - V_t = (V_{\text{gs}} - V_{\text{ds}}/2) - V_t$
  
$$C_{\text{ox}} = \epsilon_{\text{ox}} / t_{\text{ox}}$$



Carrier velocity

- Charge is carried by e-
- Carrier velocity v proportional to lateral E-field between source and drain
- $v = \mu E$ μ called mobility
- $E = V_{ds}/L$
- Time for carrier to cross channel:
 - $t = L / v$

nMOS Linear I-V

■ Now we know

- How much charge Q_{channel} is in the channel
- How much time t each carrier takes to cross

$$I_{ds} = \frac{Q_{\text{channel}}}{t}$$

$$= \mu C_{\text{ox}} \frac{W}{L} \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

$$= \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds}$$

$$\beta = \mu C_{\text{ox}} \frac{W}{L}$$


Example

■ Example: a 0.6 μm process from AMI semiconductor

- $t_{\text{ox}} = 100 \text{ \AA}$
- $\mu = 350 \text{ cm}^2/\text{V}\cdot\text{s}$
- $V_t = 0.7 \text{ V}$

■ Plot I_{ds} vs. V_{ds}

 
- $V_{\text{gs}} = 0, 1, 2, 3, 4, 5$
- Use $W/L = 4/2 \lambda$



$$\beta = \mu C_{\text{ox}} \frac{W}{L} = (350) \left(\frac{3.9 \cdot 8.85 \cdot 10^{-14}}{100 \cdot 10^{-8}} \right) \left(\frac{W}{L} \right) = 120 \frac{W}{L} \mu\text{A}/\text{V}^2$$


Ideal nMOS I-V Plot

 - 180 nm TSMC process
- Ideal Models
 - $\beta = 155(W/L) \mu\text{A}/\text{V}^2$
 - $V_t = 0.4 \text{ V}$
 - $V_{DD} = 1.8 \text{ V}$



Simulated nMOS I-V Plot

 
- 180 nm TSMC process
- BSIM 3v3 SPICE models
- What differs?
 - Less ON current
 - No square law
 - Current increases in saturation



Velocity Saturation


- **We assumed carrier velocity is proportional to E-field**
 - $v = \mu E_{\text{lat}} = \mu V_{\text{ds}}/L$
- **At high fields, this ceases to be true**
 - Carriers scatter off atoms
 - Velocity reaches v_{sat}
 - Electrons: $6\text{-}10 \times 10^6$ cm/s
 - Holes: $4\text{-}8 \times 10^6$ cm/s
 - Better model
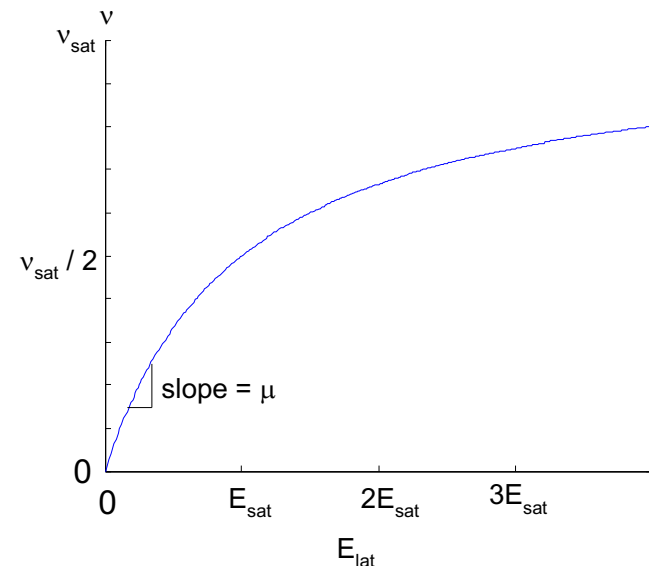
$$v = \frac{\mu E_{\text{lat}}}{1 + \frac{E_{\text{lat}}}{E_{\text{sat}}}} \Rightarrow v_{\text{sat}} = \mu E_{\text{sat}}$$



Channel Length Modulation

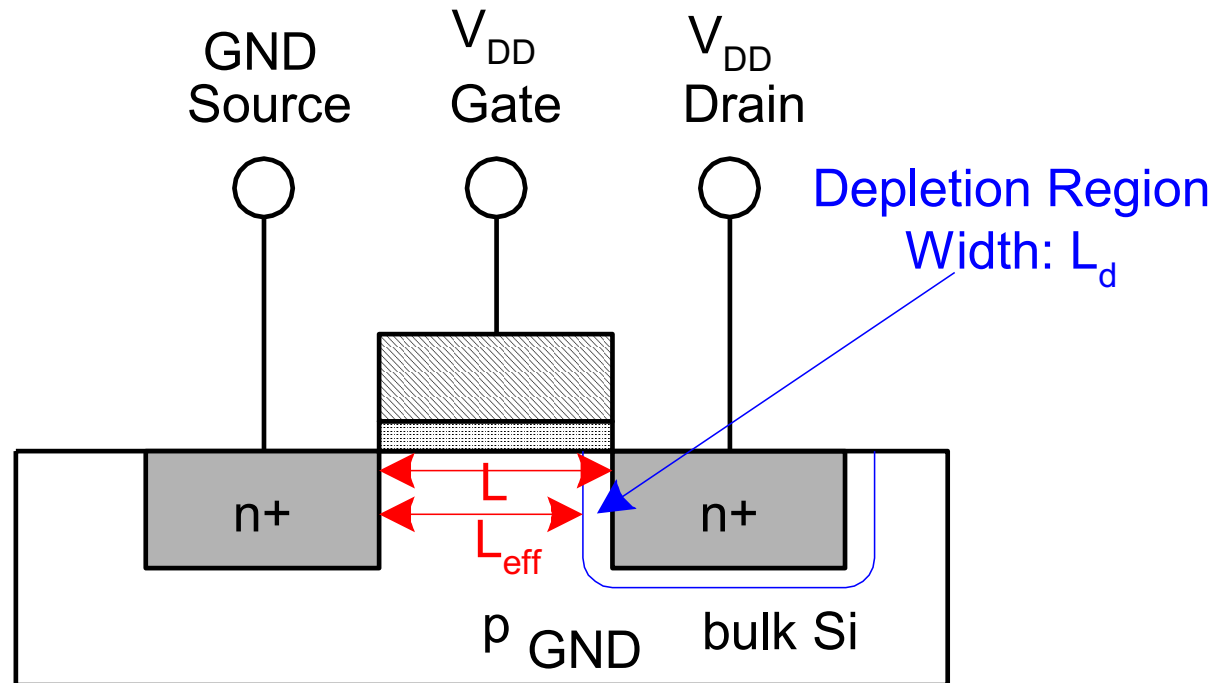- **Reverse-biased p-n junctions form a *depletion region***
 - Region between n and p with no carriers
 - Width of depletion L_d region grows with reverse bias
 - $L_{\text{eff}} = L - L_d$
- **Shorter L_{eff} gives more current**
 - I_{ds} increases with V_{ds}
 - Even in saturation




Body Effect

- V_t : gate voltage necessary to invert channel
- Increases if source voltage increases because source is connected to the channel
- Increase in V_t with V_s is called the *body effect*

OFF Transistor Behavior

 - What about current in cutoff?
- Simulated results
- What differs?
 - Current doesn't go to 0 in cutoff



Leakage Sources

- **Subthreshold conduction**
 - Transistors can't abruptly turn ON or OFF
- **Junction leakage**
 - Reverse-biased PN junction diode current
- **Gate leakage**
 - Tunneling through ultra-thin gate dielectric


- **Subthreshold leakage is the biggest source in modern transistors**

Capacitance

- **Any two conductors separated by an insulator have capacitance**
- **Gate to channel capacitor is very important**
 - **Creates channel charge necessary for operation**
- **Source and drain have capacitance to body**
 - **Across reverse-biased diodes**
 - **Called diffusion capacitance because it is associated with source/drain diffusion**


Gate Capacitance

 - Approximate channel as connected to source
- $C_{gs} = \epsilon_{ox} WL/t_{ox} = C_{ox} WL = C_{permicron} W$
- $C_{permicron}$ is typically about 2 fF/ μm





Diffusion Capacitance

 - C_{sb} , C_{db}
- Undesirable, called *parasitic capacitance*
- Capacitance depends on area and perimeter
 - Use small diffusion nodes
 - Comparable to C_g for contacted diff
 - $\frac{1}{2} C_g$ for uncontacted
 - Varies with process



RC Delay Model

  - **Use equivalent circuits for MOS transistors**
 - Ideal switch + capacitance and ON resistance
 - Unit nMOS has resistance R , capacitance C
 - Unit pMOS has resistance $2R$, capacitance C
- **Capacitance proportional to width**
- **Resistance inversely proportional to width**




Interconnects

- **Chips are mostly made of wires called *interconnect***
 - In stick diagram, wires set size
 - Transistors are little things under the wires
 - Many layers of wires
- **Wires are as important as transistors**
 - Speed
 - Power
 - Noise
- **Alternating layers run orthogonally**


Wire Capacitance

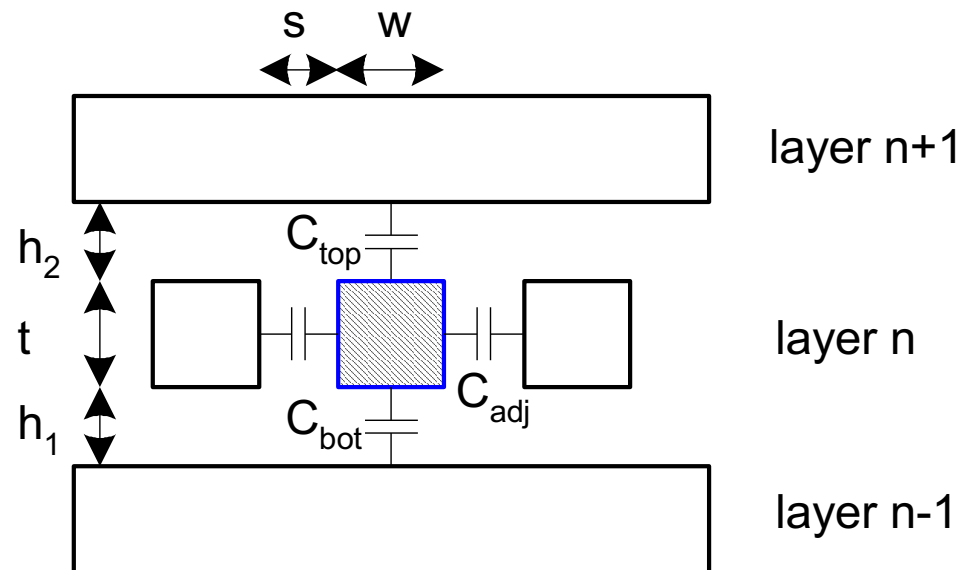- **Wire has capacitance per unit length**
 - To neighbors
 - To layers above and below
- $C_{\text{total}} = C_{\text{top}} + C_{\text{bot}} + 2C_{\text{adj}}$



Lumped Element Models

 - **Wires are a distributed system**
 - Approximate with lumped element models




- **3-segment π -model is accurate to 3% in simulation**
- **L-model needs 100 segments for same accuracy!**
- **Use single segment π -model for Elmore delay**

Crosstalk

- **A capacitor does not like to change its voltage instantaneously.**
- **A wire has high capacitance to its neighbor.**
 - When the neighbor switches from 1- \rightarrow 0 or 0- \rightarrow 1, the wire tends to switch too.
 - Called capacitive *coupling* or *crosstalk*.
- **Crosstalk effects**
 - Noise on nonswitching wires
 - Increased delay on switching wires

Coupling Waveforms


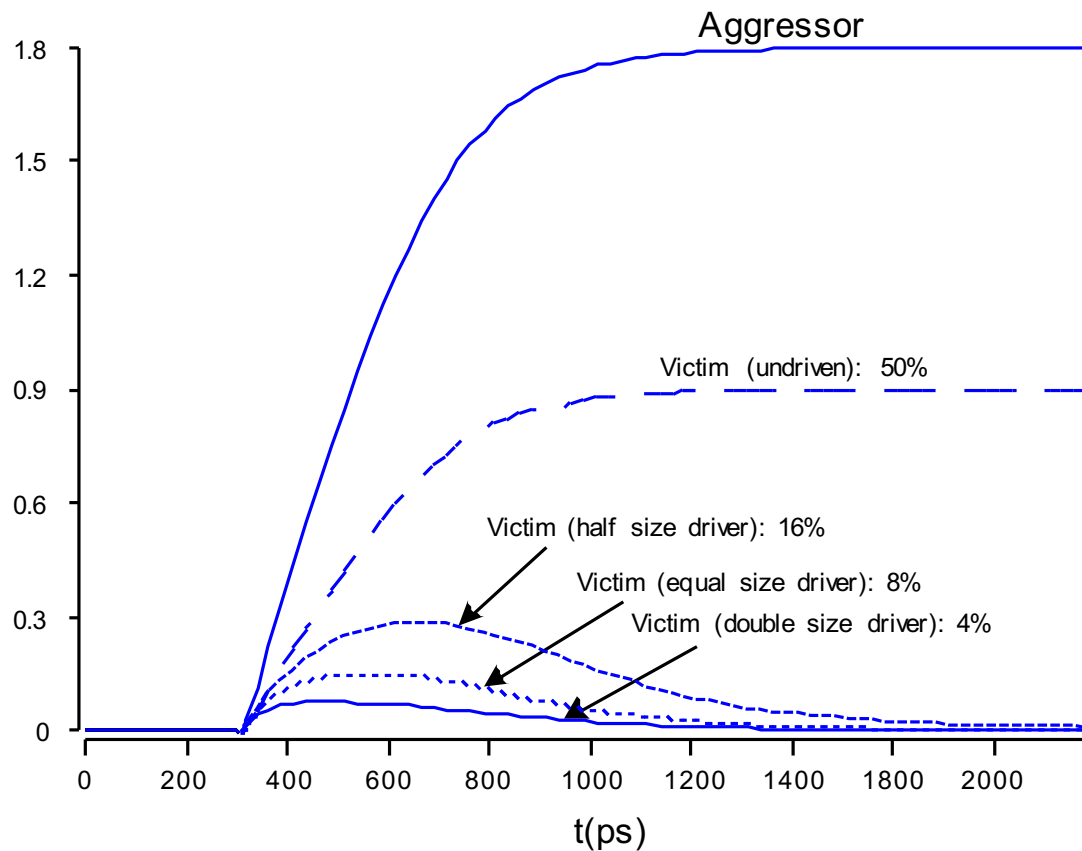
- Simulated coupling for $C_{adj} = C_{victim}$



Pass Transistor Circuits


- Use pass transistors like switches to do logic
- Inputs drive diffusion terminals as well as gates

  - **CMOS + Transmission Gates:**
 - 2-input multiplexer
 - Gates should be restoring




Sequencing

 - **Combinational logic**
 - output depends on current inputs
- **Sequential logic**
 - output depends on current and previous inputs
 - Requires separating previous, current, future
 - Called *state* or *tokens*
 - Ex: FSM, pipeline



Finite State Machine

 


Pipeline

Sequencing Overhead

- **Use flip-flops to delay fast tokens so they move through exactly one stage each cycle.**
- **Inevitably adds some delay to the slow tokens**
- **Makes circuit slower than just the logic delay**
 - **Called sequencing overhead**
- **Some people call this clocking overhead**
 - **But it applies to asynchronous circuits too**
 - **Inevitable side effect of maintaining sequence**


Sequencing Elements

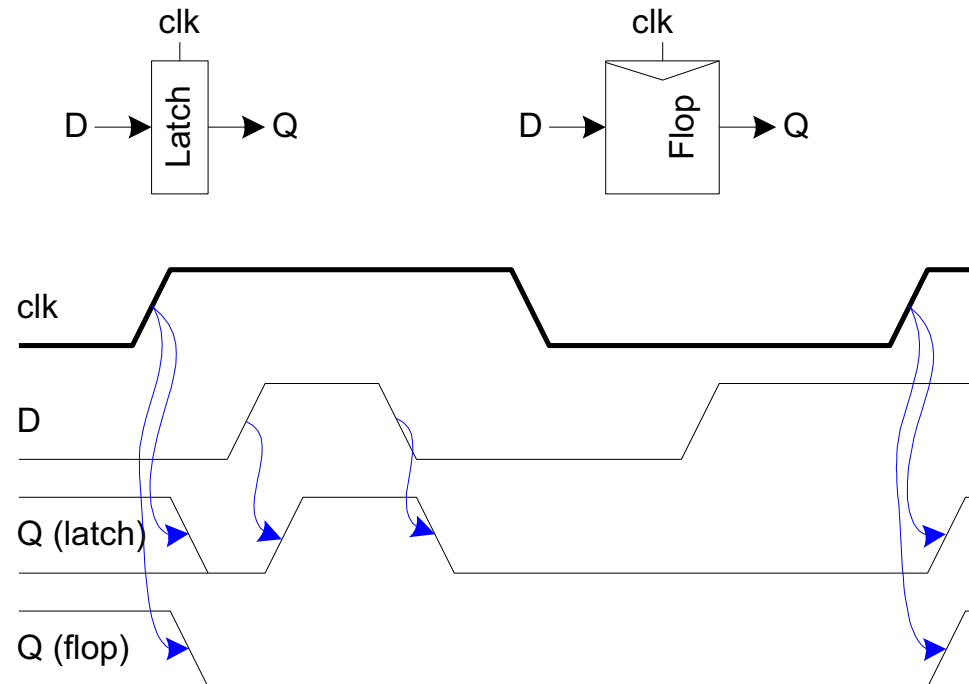- **Latch: Level sensitive**
 - a.k.a. transparent latch, D latch
- **Flip-flop: edge triggered**
 - A.k.a. master-slave flip-flop, D flip-flop, D register
- **Timing Diagrams**
 - Transparent
 - Opaque
 - Edge-trigger




Latch Design

 - **Buffered output**
 - + No backdriving
- **Widely used in standard cells**
 - + Very robust (most important)
 - Rather large
 - Rather slow (1.5 – 2 FO4 delays)
 - High clock loading




Sequencing Methods


Flip-flops

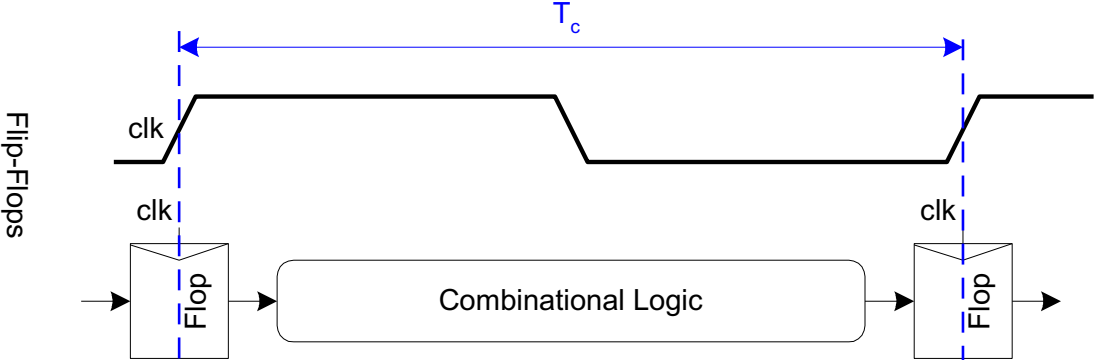

2-Phase Latches

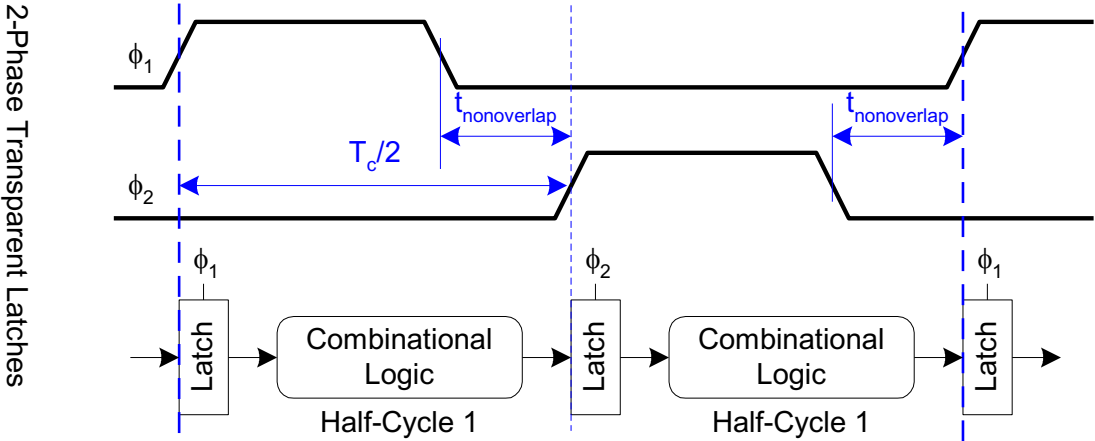







Pulsed Latches

 

Timing Diagrams


Contamination and Propagation Delays

t_{pd}	Logic Propagation Delay
t_{cd}	Logic Contamination Delay
t_{pcq}	Latch/Flop Clk-Q Prop Delay
t_{ccq}	Latch/Flop Clk-Q Cont. Delay
t_{pdq}	Latch D-Q Prop Delay
t_{cdq}	Latch D-Q Cont. Delay
t_{setup}	Latch/Flop Setup Time
t_{hold}	Latch/Flop Hold Time

      


Max-Delay: Flip-Flops
 
$$T_c \geq t_{pd} + \underbrace{(t_{setup} + t_{pcq})}_{\text{sequencing overhead}}$$





Max Delay: 2-Phase Latches
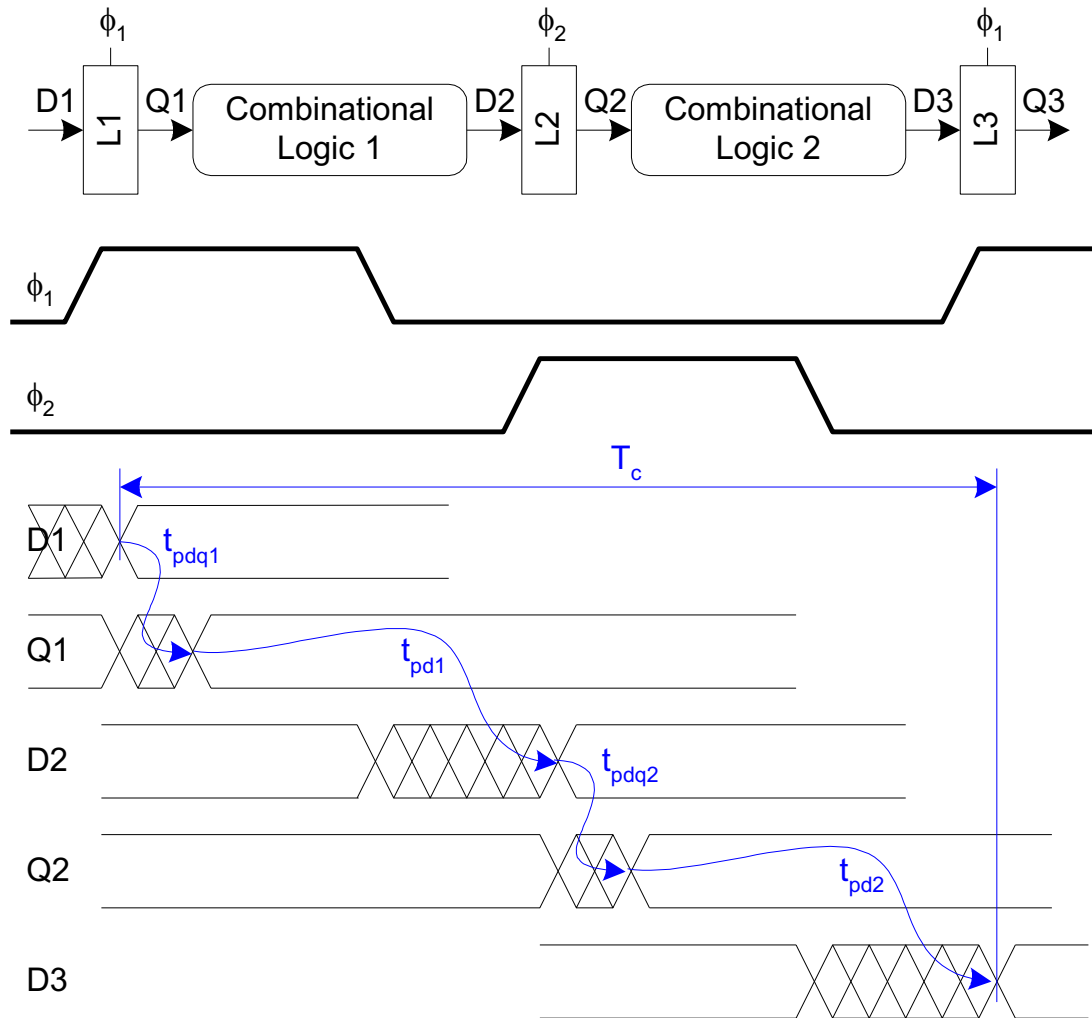
$$T_c \geq t_{pd1} + t_{pd2} + \underbrace{t_{pdq1} + t_{pdq2}}_{\text{sequencing overhead}}$$




Max Delay: Pulsed Latches

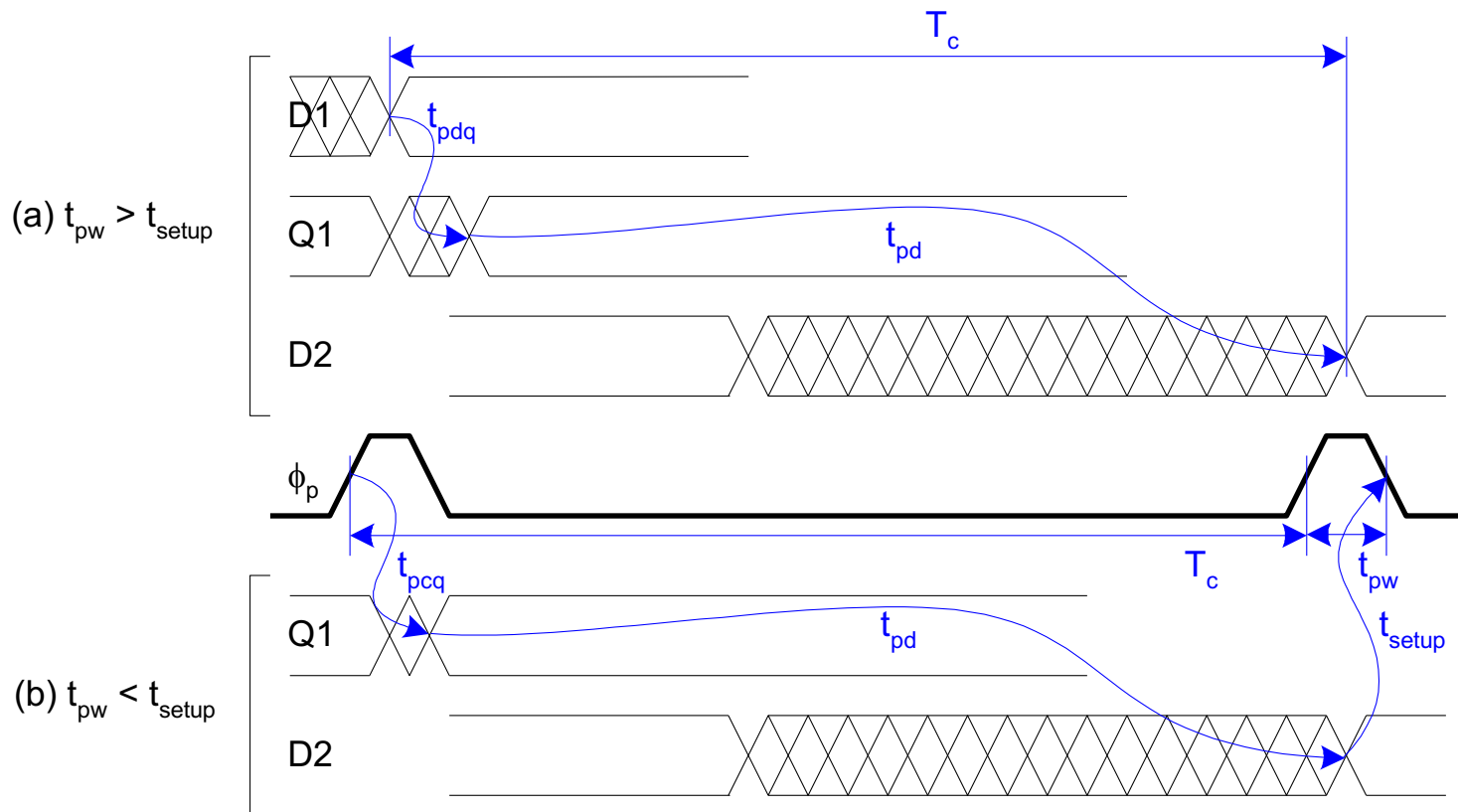 
$$t_{pd} + \underbrace{\max(t_{pdq}, t_{pcq} + t_{setup} - t_{pw})}_{\text{sequencing overhead}} \leq T_c$$



Min-Delay: Flip-Flops

 

 
$$t_{cd} \geq t_{\text{hold}} - t_{ccq}$$



Sequencing Methods

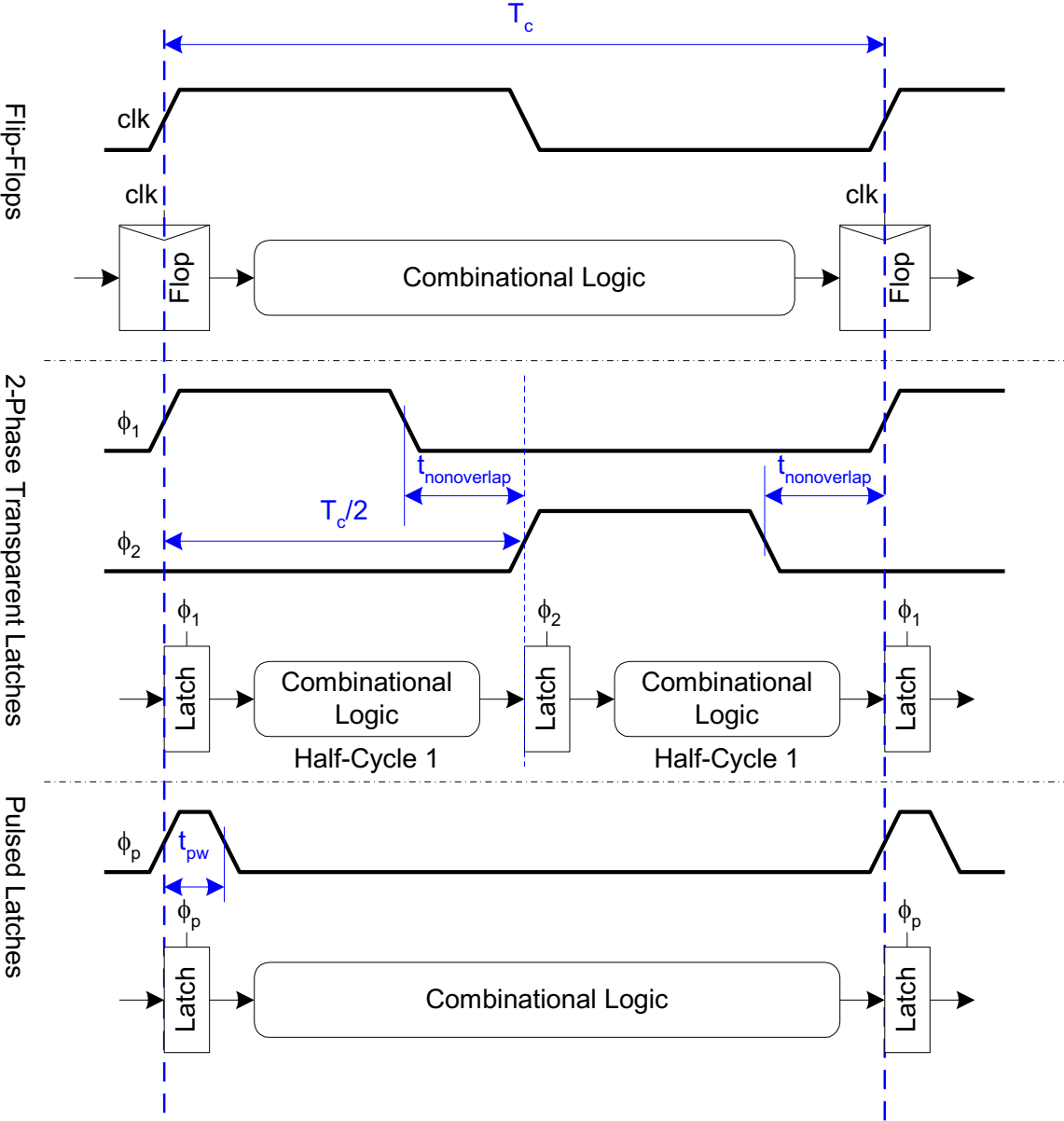- Flip-flops
- 2-Phase Latches
- Pulsed Latches



Flip-Flop Summary

- **Flip-Flops:**
 - Very easy to use, supported by all tools
- **2-Phase Transparent Latches:**
 - Lots of skew tolerance and time borrowing
- **Pulsed Latches:**
 - Fast, some skew tol & borrow, hold time risk


	Sequencing overhead ($T_c - t_{pd}$)	Minimum logic delay t_{cd}	Time borrowing t_{borrow}
Flip-Flops	$t_{pcq} + t_{setup} + t_{skew}$	$t_{hold} - t_{ccq} + t_{skew}$	0
Two-Phase Transparent Latches	$2t_{pdq}$	$t_{hold} - t_{ccq} - t_{nonoverlap} + t_{skew}$ in each half-cycle	$\frac{T_c}{2} - (t_{setup} + t_{nonoverlap} + t_{skew})$
Pulsed Latches	$\max(t_{pdq}, t_{pcq} + t_{setup} - t_{prw} + t_{skew})$	$t_{hold} - t_{ccq} + t_{prw} + t_{skew}$	$t_{prw} - (t_{setup} + t_{skew})$

Full Adder Design I

- Brute force implementation from eqns

$$S = A \oplus B \oplus C$$


$$C_{\text{out}} = \text{MAJ}(A, B, C)$$

 

Tree Adder


- **If lookahead is good, lookahead across lookahead!**
 - Recursive lookahead gives $O(\log N)$ delay
- **Many variations on tree adders**

Memory Arrays

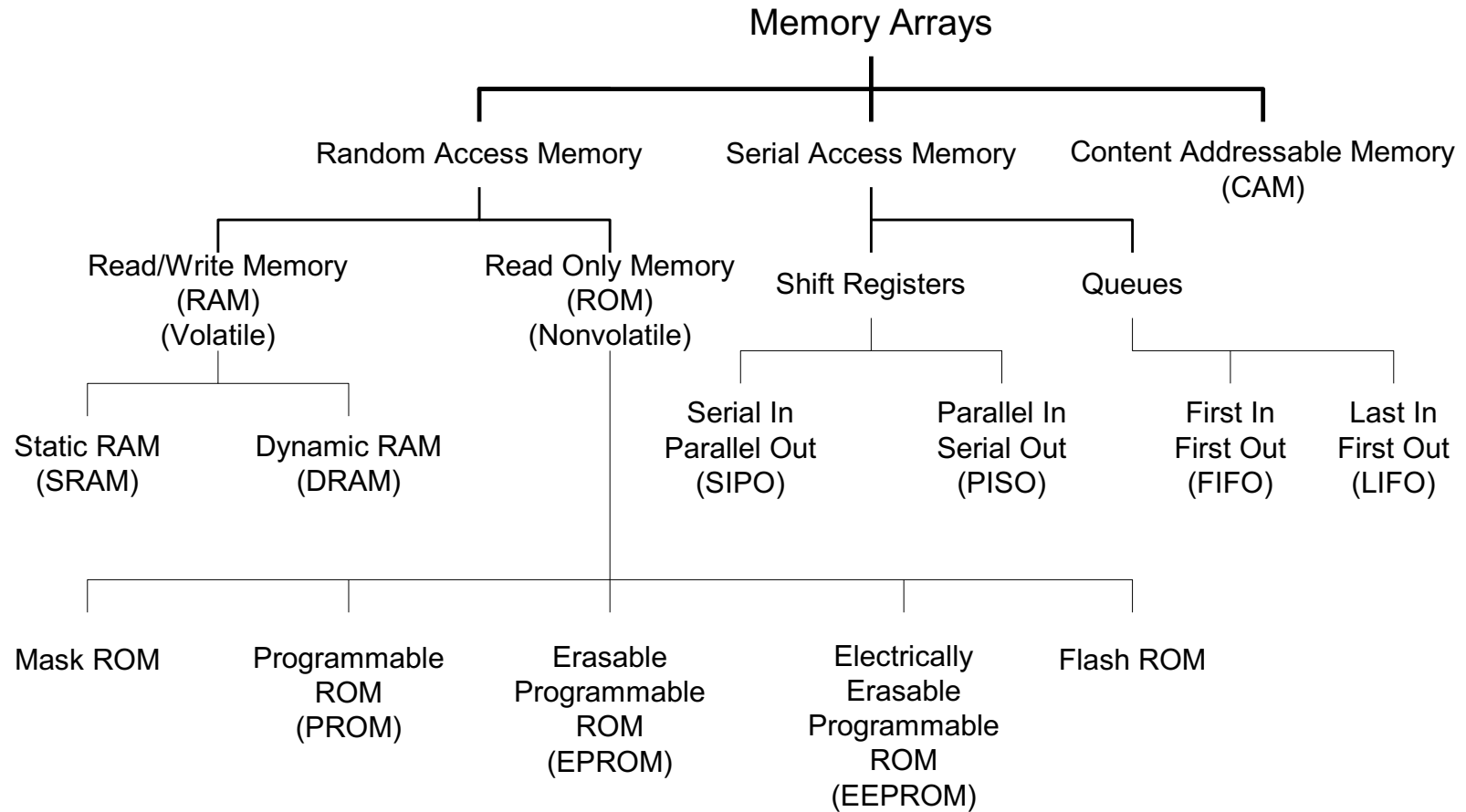

Array Architecture

 
- 2^n words of 2^m bits each
- If $n \gg m$, fold by 2^k into fewer rows of more columns



- **Good regularity – easy to design**
- **Very high density if good cells are used**


6T SRAM Cell

 - **Cell size accounts for most of array size**
 - Reduce cell size at expense of complexity
- **6T SRAM Cell**
 - Used in most commercial chips
 - Data stored in cross-coupled inverters
- **Read:**
 - Precharge bit, bit_b
 - Raise wordline
- **Write:**
 - Drive data onto bit, bit_b
 - Raise wordline



SRAM Sizing


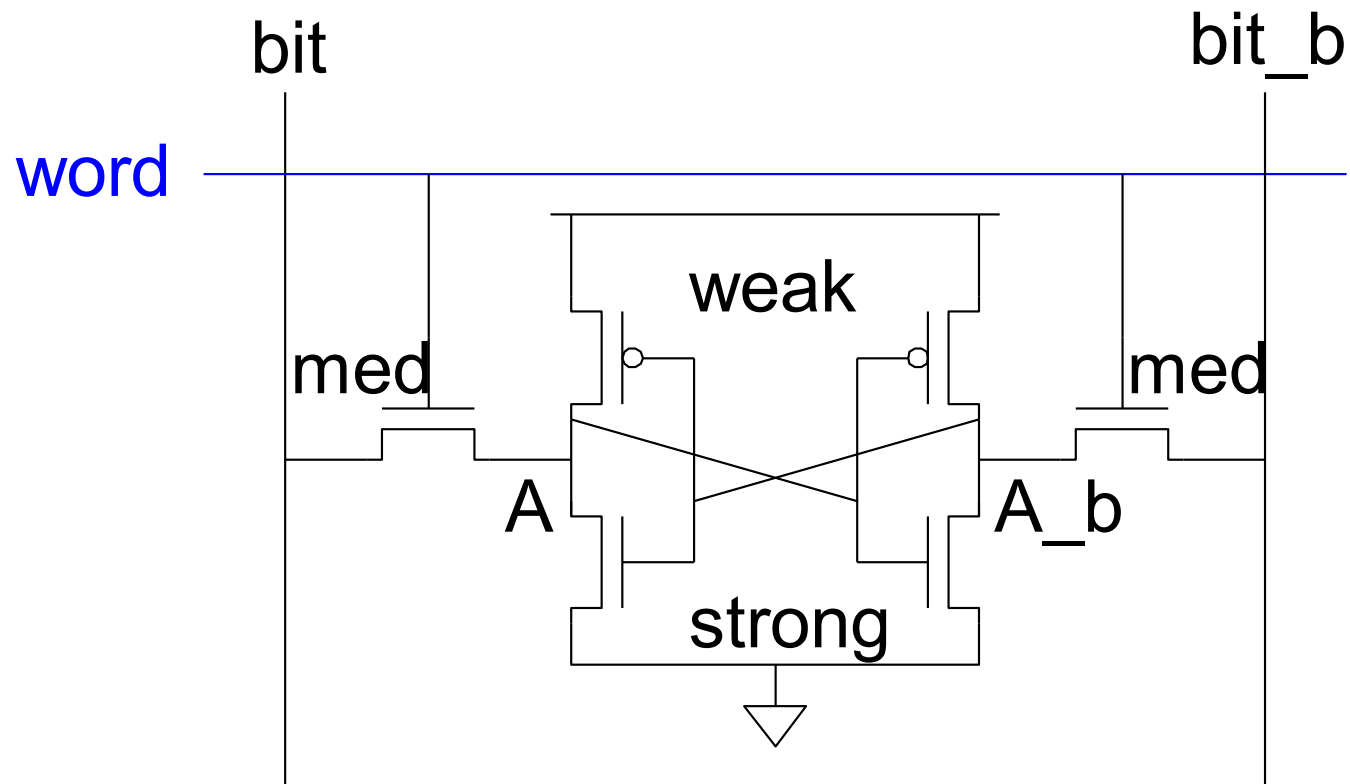
- High bitlines must not overpower inverters during reads
- But low bitlines must write new value into cell



Decoders


- **$n:2^n$ decoder consists of 2^n n-input AND gates**
 - One needed for each row of memory
 - Build AND from NAND or NOR gates
- **Static CMOS**

Pseudo-nMOS

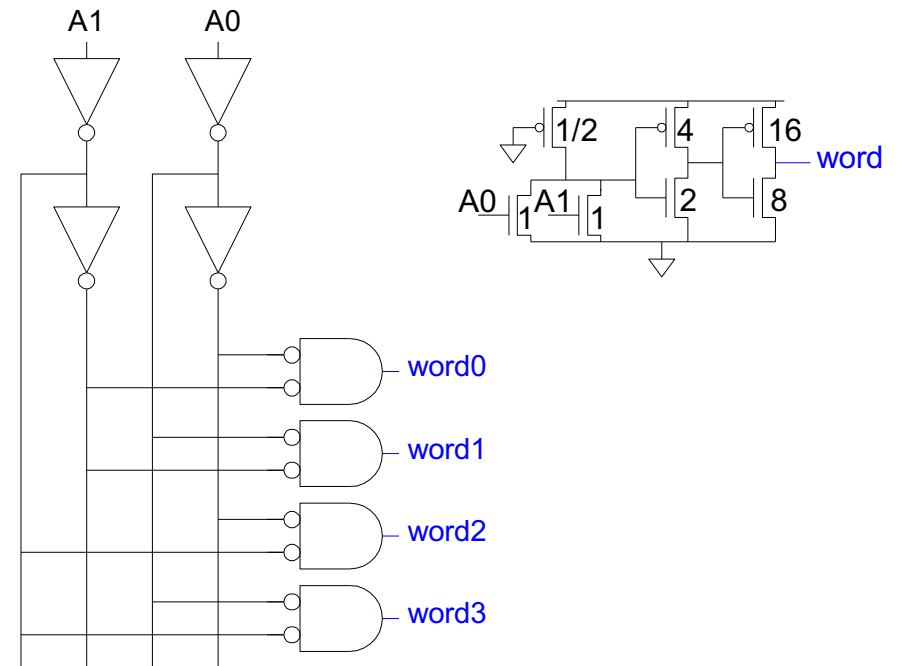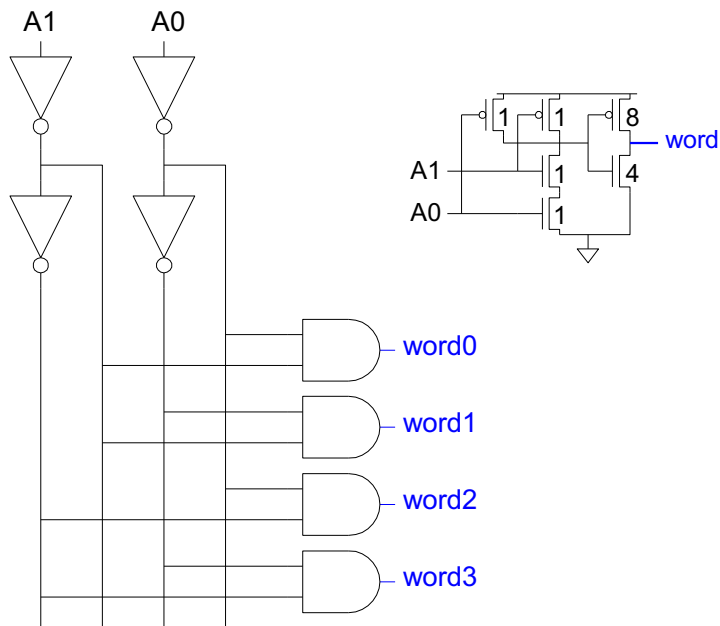

Decoder Layout

 - Decoders must be pitch-matched to SRAM cell
 - Requires very skinny gates




Sense Amplifiers

- **Bitlines have many cells attached**
 - Ex: 32-kbit SRAM has 256 rows x 128 cols
 - 128 cells on each bitline
- **$t_{pd} \propto (C/I) \Delta V$**
 - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
 - Discharged slowly through small transistors (small I)
- ***Sense amplifiers* are triggered on small voltage swing (reduce ΔV)**



CAMs

 - **Extension of ordinary memory (e.g. SRAM)**
 - Read and write memory as usual
 - Also *match* to see which words contain a *key*




10T CAM Cell

  - Add four match transistors to 6T SRAM
 - 56 x 43 λ unit cell



CAM Cell Operation

 - **Read and write like ordinary SRAM**
- **For matching:**
 - Leave wordline low
 - Precharge matchlines
 - Place key on bitlines
 - Matchlines evaluate
- **Miss line**
 - Pseudo-nMOS NOR of match lines
 - Goes high if no words match



ROM Example

■ 4-word x 6-bit ROM



- Represented with dot diagram
- Dots indicate 1's in ROM

Word 0: **010101**

Word 1: **011001**

Word 2: **100101**

Word 3: **101010**

 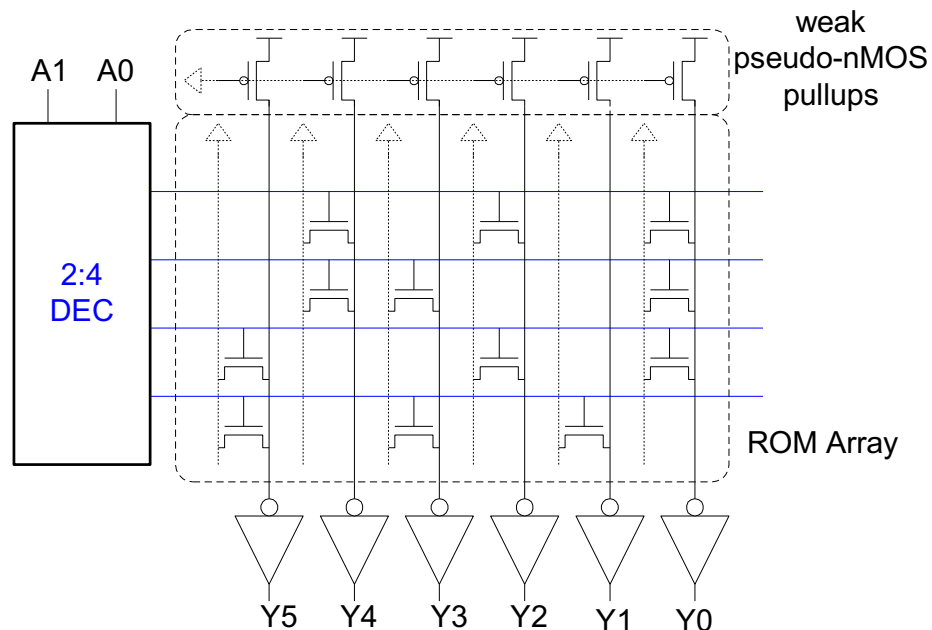

Looks like 6 4-input pseudo-nMOS NORs


PLAs

- A *Programmable Logic Array* performs any function in sum-of-products form.
- *Literals*: inputs & complements
- *Products / Minterms*: AND of literals
- *Outputs*: OR of Minterms



- **Example: Full Adder**

$$s = a\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}\bar{b}c + abc$$

$$c_{out} = ab + bc + ac$$

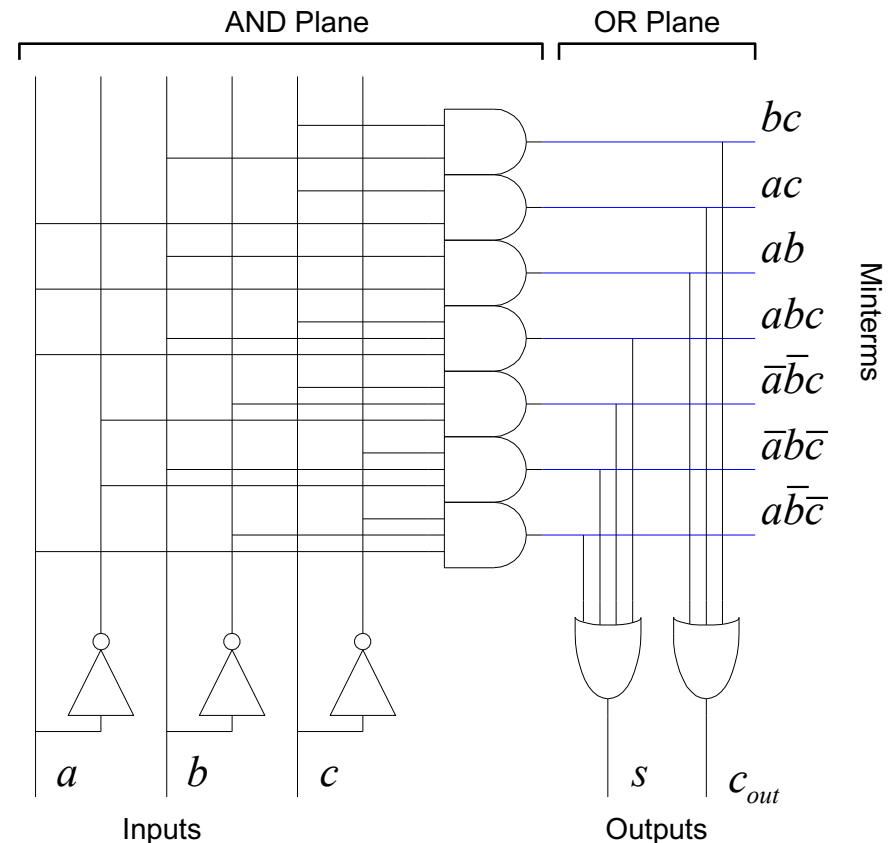

PLA Schematic & Layout

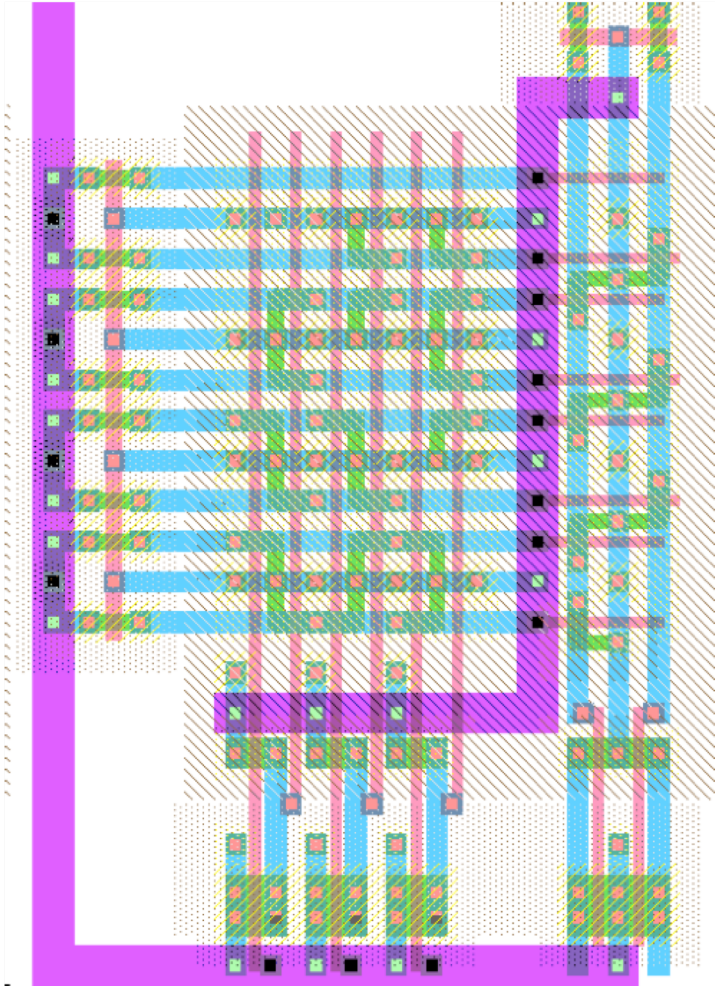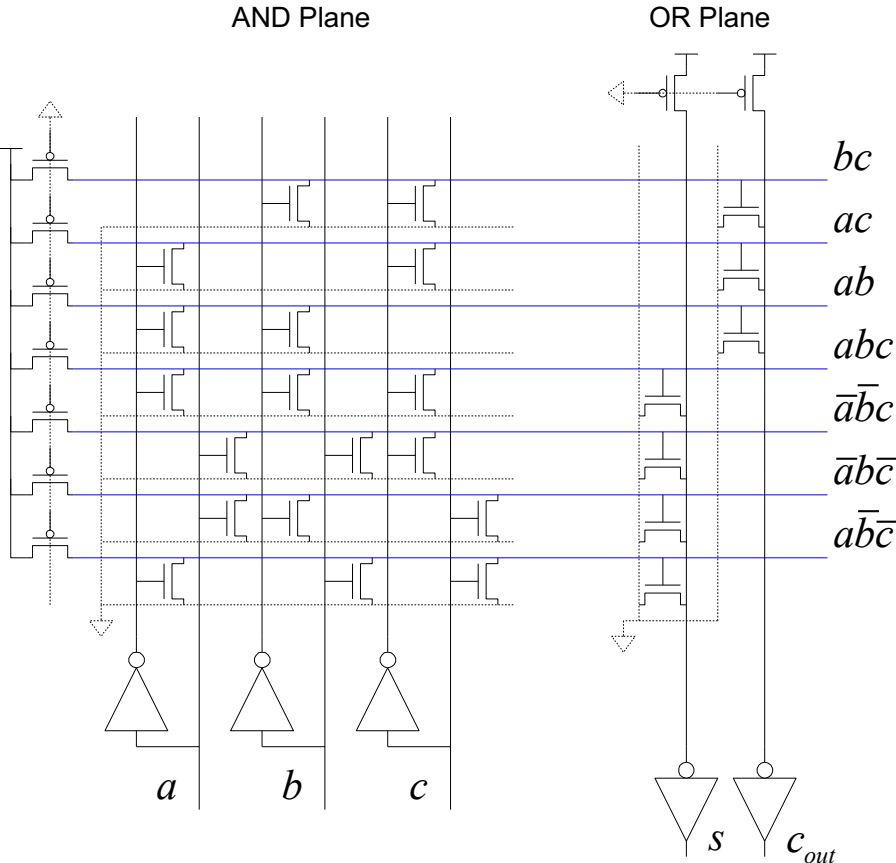

Low Power Design

- **Reduce dynamic power**


- α : clock gating, sleep mode
- C: small transistors (esp. on clock), short wires
- V_{DD} : lowest suitable voltage
- f: lowest suitable frequency

- **Reduce static power**

- Selectively use ratioed circuits
- Selectively use low V_t devices
- Leakage reduction:
stacked devices, body bias, low temperature


Chip-to-Package Bonding

 - **Traditionally, chip is surrounded by *pad frame***
 - Metal pads on 100 – 200 μm pitch
 - Gold *bond wires* attach pads to package
 - *Lead frame* distributes signals in package
 - Metal *heat spreader* helps with cooling



Bidirectional Pads

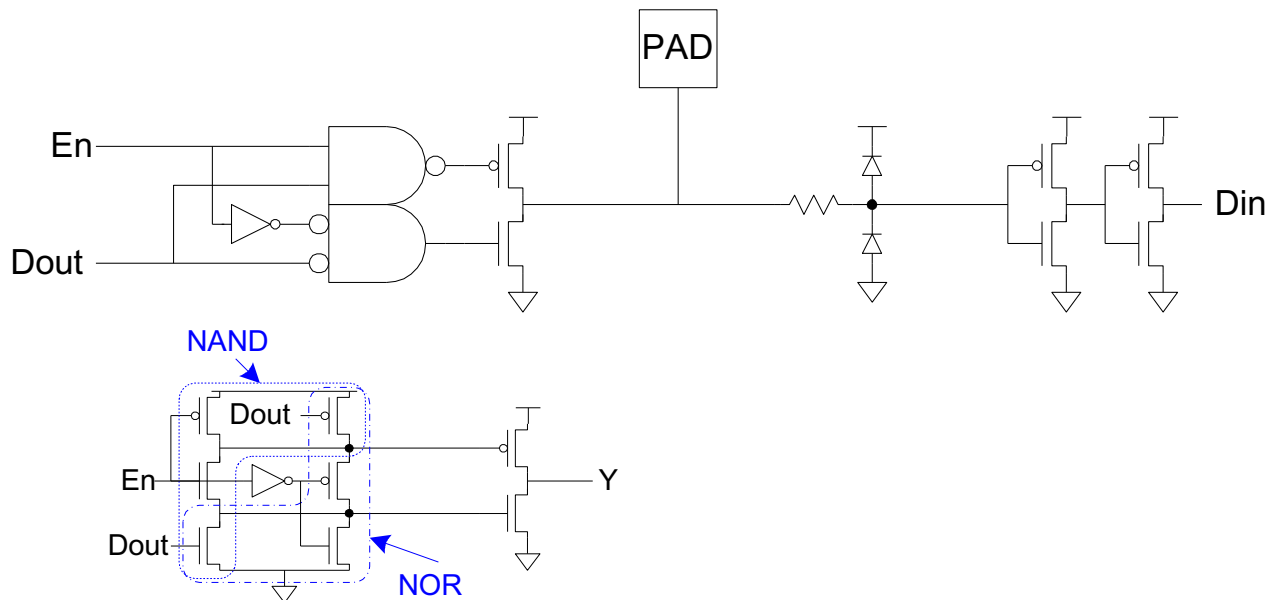- **Combine input and output pad**
- **Need tristate driver on output**
 - Use enable signal to set direction
 - Optimized tristate avoids huge series transistors



Device Scaling

Table 4.15 Influence of scaling on MOS device characteristics

Parameter	Sensitivity	Constant Field	Lateral
Scaling Parameters			
Length: L		$1/S$	$1/S$
Width: W		$1/S$	1
Gate oxide thickness: t_{ox}		$1/S$	1
Supply voltage: V_{DD}		$1/S$	1
Threshold voltage: V_{tn}, V_{tp}		$1/S$	1
Substrate doping: N_A		S	1
Device Characteristics			
β	$\frac{W}{L} \frac{1}{t_{ox}}$	S	S
Current: I_{ds}	$\beta(V_{DD} - V_t)^2$	$1/S$	S
Resistance: R	$\frac{V_{DD}}{I_{ds}}$	1	$1/S$
Gate capacitance: C	$\frac{WL}{t_{ox}}$	$1/S$	$1/S$
Gate delay: τ	RC	$1/S$	$1/S^2$
Clock frequency: f	$1/\tau$	S	S^2
Dynamic power dissipation (per gate): P	CV^2f	$1/S^2$	S
Chip area: A		$1/S^2$	1
Power density	P/A	1	S
Current density	I_{ds}/A	S	S

Interconnect Delay

Table 4.16 Influence of scaling on interconnect characteristics

Parameter	Sensitivity	Reduced Thickness	Constant Thickness
Scaling Parameters			
Width: w		$1/S$	
Spacing: s		$1/S$	
Thickness: t		$1/S$	1
Interlayer oxide height: h		$1/S$	
Local/Scaled Interconnect Characteristics			
Length: l		$1/S$	
Unrepeated wire RC delay	$l^2 t_{wu}$	1	between $1/S, 1$
Repeated wire delay	$l t_{wr}$	$\sqrt{1/S}$	between $1/S, \sqrt{1/S}$
Global Interconnect Characteristics			
Length: l		D_c	
Unrepeated wire RC delay	$l^2 t_{wu}$	$S^2 D_c^2$	between $SD_c^2, S^2 D_c^2$
Repeated wire delay	$l t_{wr}$	$D_c \sqrt{S}$	between $D_c, D_c \sqrt{S}$

Energy and Power

- **Energy is drawn from a voltage source**


- **Instantaneous Power:** $P(t) = i_{DD}(t)V_{DD}$

- **Energy:** $E = \int_0^T P(t)dt = \int_0^T i_{DD}(t)V_{DD}dt$

- **Average Power:** $P_{\text{avg}} = \frac{E}{T} = \frac{1}{T} \int_0^T i_{DD}(t)V_{DD}dt$


Dynamic Power

 - Dynamic power required to charge and discharge load capacitances when transistors switch
- One cycle involves a rising and falling output
- On rising output, charge $Q = CV_{DD}$ is required
- On falling output, charge is dumped to GND
- This repeats $T \cdot f_{sw}$ times over an interval of T



Dynamic Power (Cont.)
 
$$\begin{aligned} P_{\text{dynamic}} &= \frac{1}{T} \int_0^T i_{DD}(t) V_{DD} dt \\ &= \frac{V_{DD}}{T} \int_0^T i_{DD}(t) dt \\ &= \frac{V_{DD}}{T} [T f_{\text{sw}} C V_{DD}] \\ &= C V_{DD}^2 f_{\text{sw}} \end{aligned}$$



Activity Factor

- Suppose the system clock frequency = f
- Let $f_{sw} = \alpha f$, where α = activity factor
 - If the signal is a clock, $\alpha = 1$
 - If the signal switches once per cycle, $\alpha = \frac{1}{2}$
 - Dynamic gates:
 - Switch either 0 or 2 times per cycle, $\alpha = 1$
 - Static gates:
 - Depends on the type of gate and logic network, but typically $\alpha = 0.1 - 0.2$
- Dynamic power: $P_{dyn} = \alpha * C * V_{dd} * \Delta V * freq$

Activity Factor Estimation


- Let $P_i = \text{Prob}(\text{node } i = 1)$
 - $\overline{P}_i = 1 - P_i$
- $\alpha_i = \overline{P}_i * P_i$
- Completely random data has $P = 0.5$ and $\alpha = 0.25$
- Data is often not completely random
 - e.g. upper bits of 64-bit words representing bank account balances are usually 0
- Data propagating through ANDs and ORs has lower activity factor
 - Depends on design, but typically $\alpha \approx 0.1$

Switching Probability

Gate	P_Y
AND2	$P_A P_B$
AND3	$P_A P_B P_C$
OR2	$1 - \bar{P}_A \bar{P}_B$
NAND2	$1 - P_A P_B$
NOR2	$\bar{P}_A \bar{P}_B$
XOR2	$P_A \bar{P}_B + \bar{P}_A P_B$

Switching Probability Example

 - A 4-input AND is built out of two levels of gates
- Estimate the activity factor at each node if the inputs have $P = 0.5$




Stuck-At Faults

- **How does a chip fail?**
 - Need “fault model”
 - Usually failures are shorts between two conductors or opens in a conductor
 - This can cause very complicated behavior

- **A simpler model: *Stuck-At***
 - Assume all failures cause nodes to be “stuck-at” 0 or 1, i.e. shorted to GND or V_{DD}
 - Not quite true, but works well in practice

Examples

 

Observability & Controllability


- **Observability:** ease of observing a node by watching external output pins of the chip
- **Controllability:** ease of forcing a node to 0 or 1 by driving input pins of the chip
- **Combinational logic is usually easy to observe and control**
- **Finite state machines can be very difficult, requiring many cycles to enter desired state**
 - Especially if state transition diagram is not known to the test engineer

Test Pattern Generation

- **Manufacturing test ideally would check every node in the circuit to prove it is not stuck.**
- **Apply the smallest sequence of test vectors necessary to prove each node is not stuck.**
- **Good observability and controllability reduces number of test vectors required for manufacturing test.**
 - **Reduces the cost of testing**
 - **Motivates design-for-test**

Test Example

	SA1	SA0
■ A_3	{0110}	{1110}
■ A_2	{1010}	{1110}
■ A_1	{0100}	{0110}
■ A_0	{0110}	{0111}
■ n1	{1110}	{0110}
■ n2	{0110}	{0100}
■ n3	{0101}	{0110}
■ Y	{0110}	{1110}

 

- Minimum set: {0100, 0101, 0110, 0111, 1010, 1110}