
Lecture 3: CMOS Layout, Floorplanning & other implementation styles

Mark McDermott

Electrical and Computer Engineering
The University of Texas at Austin


Layout

- **Describes actual layers and geometry on the silicon substrate to implement a function**
- **Need to define transistors, interconnection**
 - Transistor widths (for performance)
 - Spacing, interconnect widths, to reduce defects, satisfy power requirements
 - Contacts (between poly or active and metal), and vias (between metal layers)
 - Wells and their contacts (to power or ground)
- **Layout of lower-level cells constrained by higher-level requirements: “floorplanning”**
 -


Layout (Cont.)

- Chips are specified with set of masks
- Minimum dimensions of masks determine transistor size (and hence speed, cost, and power)
- Feature size f = distance between source and drain
 - Set by minimum width of polysilicon
- Feature size improves 30% every 3 years or so
- Normalize for feature size when describing design rules
- Express rules in terms of $\lambda = f/2$
 - E.g. $\lambda = 0.3 \mu\text{m}$ in $0.6 \mu\text{m}$ process


CMOS Inverter Layout

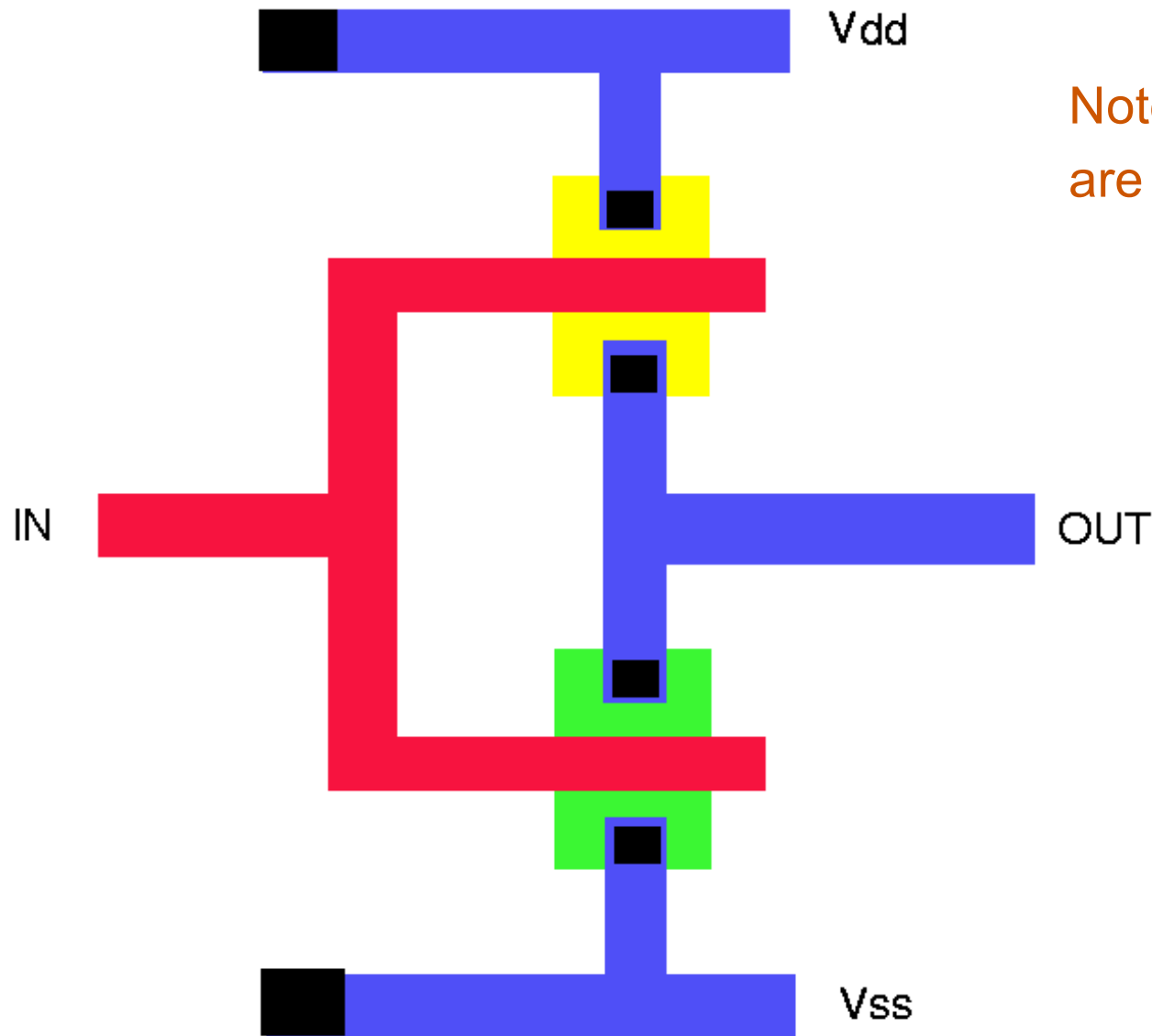

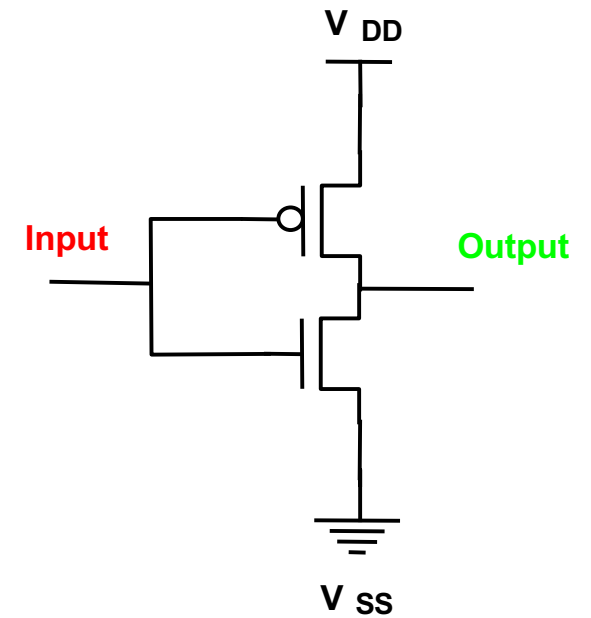
Note: the N- and P- wells are not shown here




Another CMOS Inverter Layout

 


CMOS Inverter with Wider Transistors

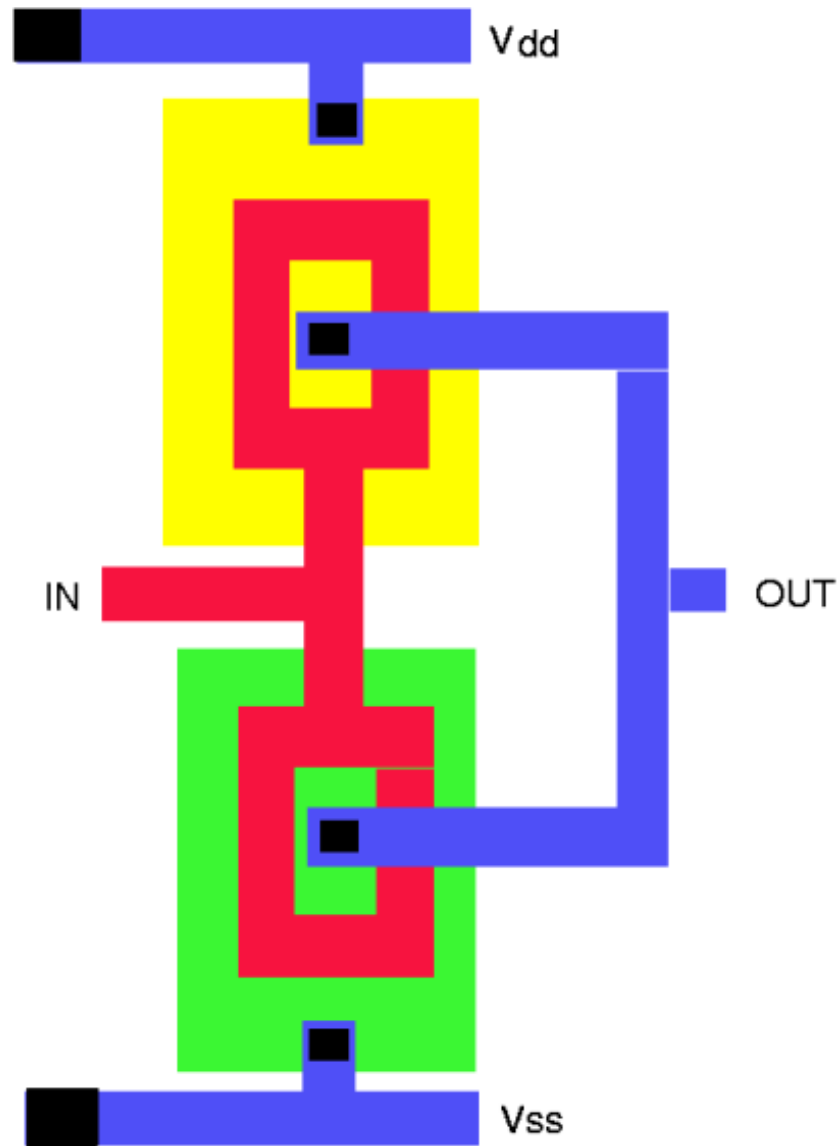


Buffer with Two Inverters

 


Buffer with Stacked Inverters

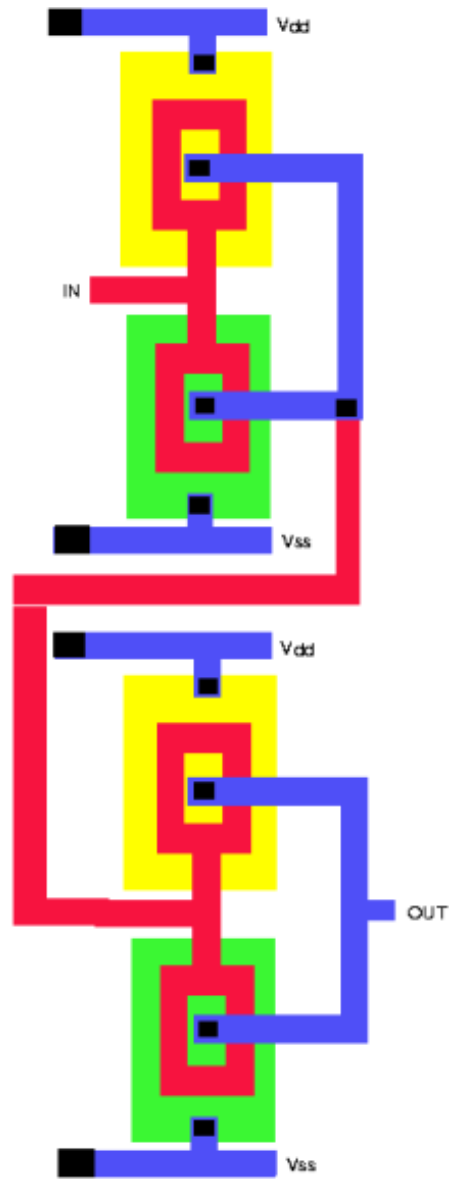

Efficient Buffer with Stacked Inverters

 


Simplified Layout of NAND Gate

 


“Stick” Diagram for NAND Gate

 - Identifies actual layers, can be annotated with transistor sizes





Simplified Design Rules

- Conservative rules to get you started

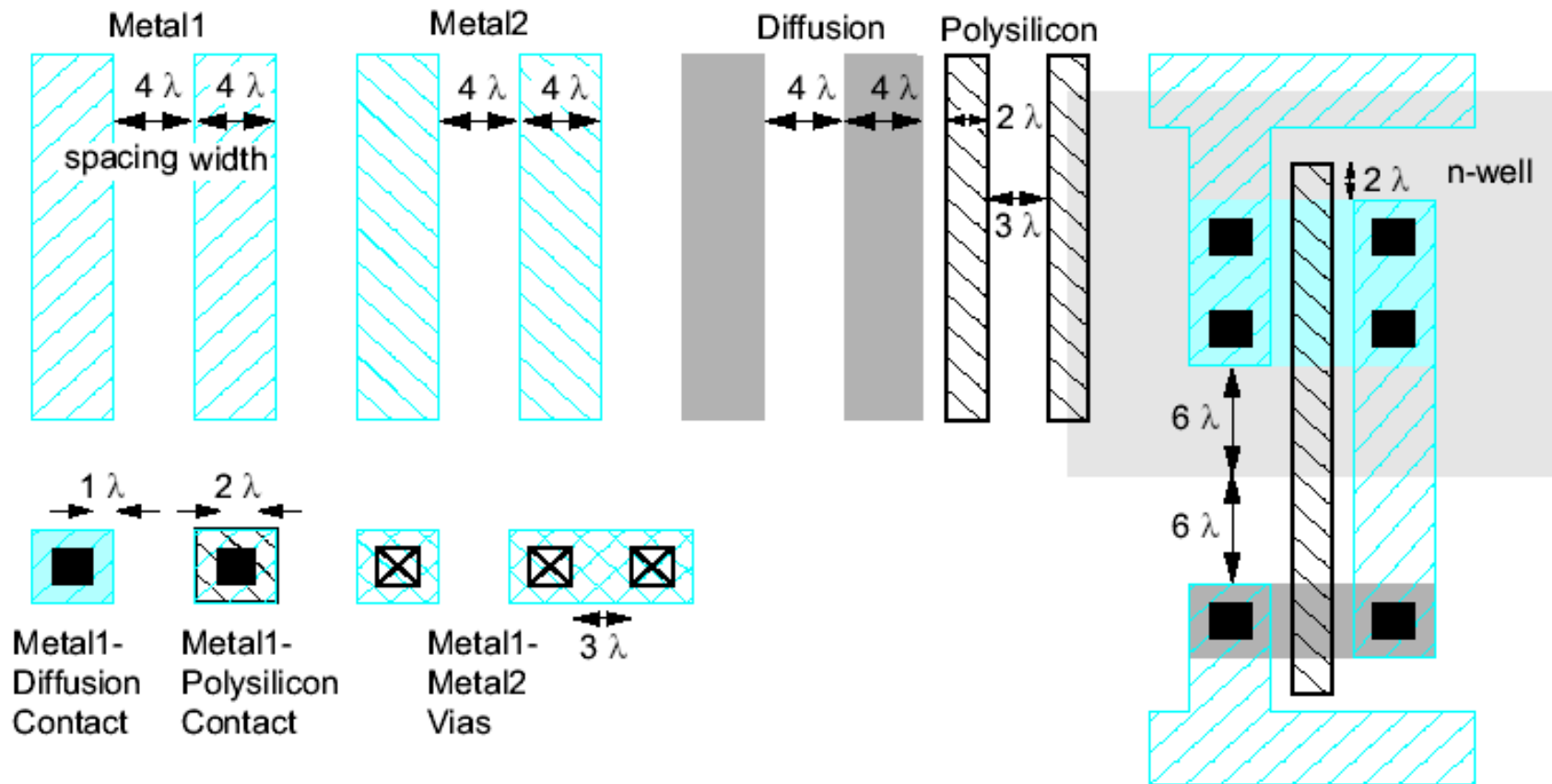

Inverter Layout

  - **Transistor dimensions specified as Width / Length**
 - Minimum size $4\lambda / 2\lambda$, sometimes called 1 unit or standard pitch
 - In $f = 0.6 \mu\text{m}$ process, this is $1.2 \mu\text{m}$ wide, $0.6 \mu\text{m}$ long




Typical Layout Densities

- **Typical numbers of high-quality layout**
- **Derate by 2 for class projects to allow routing and some sloppy layout.**
- **Allocate space for big wiring channels**

Element	Area
Random logic (2 metal layers)	1000-1500 λ^2 / transistor
Datapath	250 – 750 λ^2 / transistor Or 6 WL + 360 λ^2 / transistor
SRAM	1000 λ^2 / bit
DRAM	100 λ^2 / bit
ROM	100 λ^2 / bit


Area Calculation Example: NAND3

 - Horizontal N-diffusion and p-diffusion strips
- Vertical polysilicon gates
- Metal1 V_{DD} rail at top
- Metal1 GND rail at bottom
- 32λ by 40λ




Cell Flipping

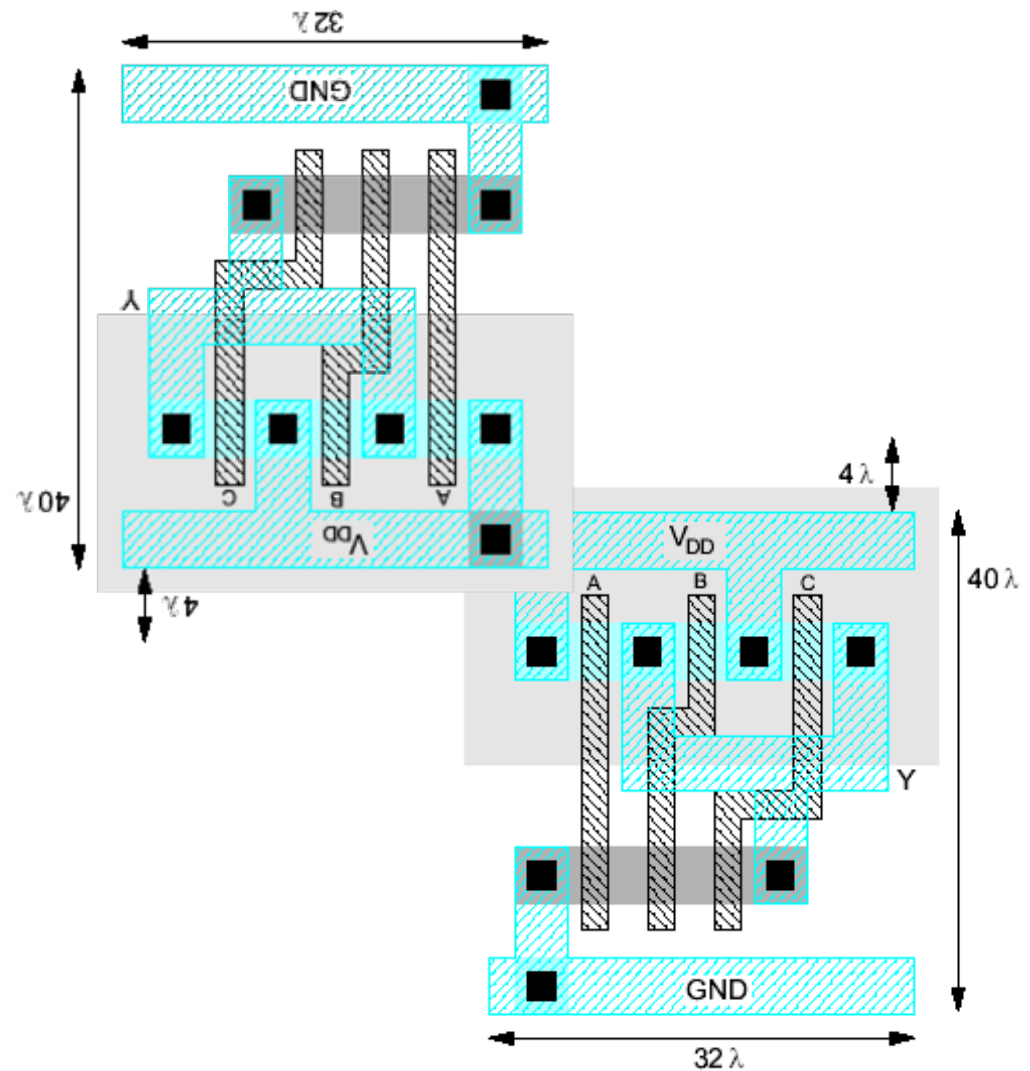- Flip every other cell
- Cells share VDD & GND
- Cells share N-WELL and substrate connections
- Reduces cell height
 - Measure contact center to contact center




Wiring Tracks

 - A *wiring track* is the space required for a wire
 - 4λ width, 4λ spacing from neighbor = 8λ pitch
- Transistors also consume one wiring track




Well spacing

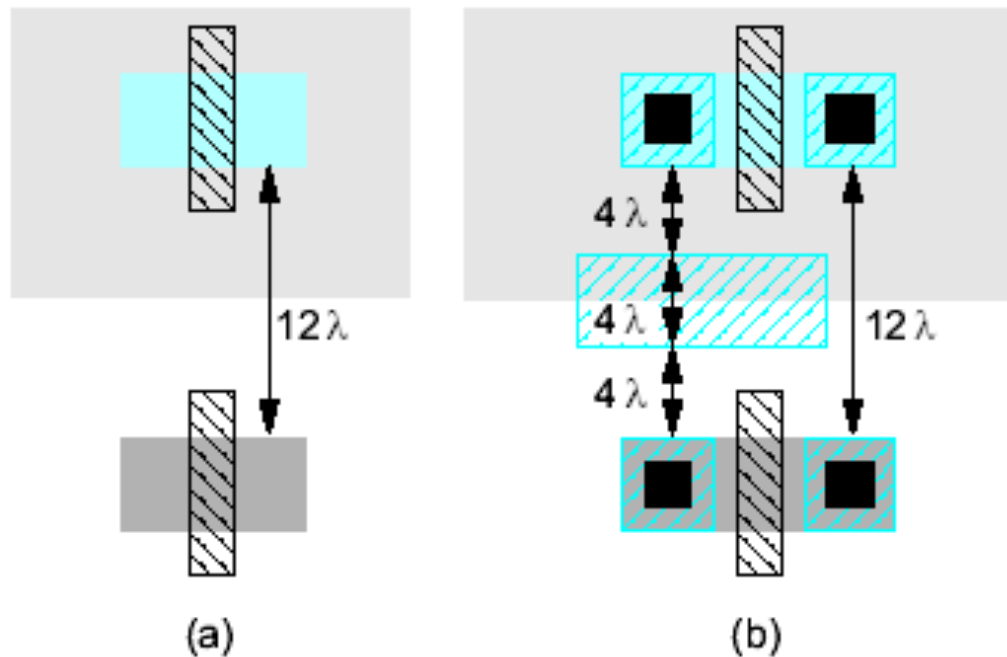- **Wells must surround transistors by 6λ**
 - Implies 12λ between opposite transistor flavors
 - Leaves room for one wire track



Area Estimation

 - **Estimate area by counting wiring tracks**
 - Multiply by 8 to express in λ



Example: O3AI


- Sketch a stick diagram for O3AI and estimate area

$$Y = \overline{(A + B + C)} \text{ } \& D$$

Example: O3AI

- Sketch a stick diagram for O3AI and estimate area


$$Y = \overline{(A + B + C)} * D$$

 

Example: O3AI

- Sketch a stick diagram for O3AI and estimate area

$$Y = \overline{(A + B + C)} * D$$

 


The MOSIS Scalable CMOS Rules

- λ -based rules
- Designs using these rules are fabricated by a variety of companies
- Multiple designs are put on a single die
 - Each chip wired to a particular design
- Support for submicron digital CMOS, analog (buried poly layer for capacitor), micromachines, etc.
- www.mosis.org/Technical/Designrules/scmos/

Floorplanning


Floorplanning 101

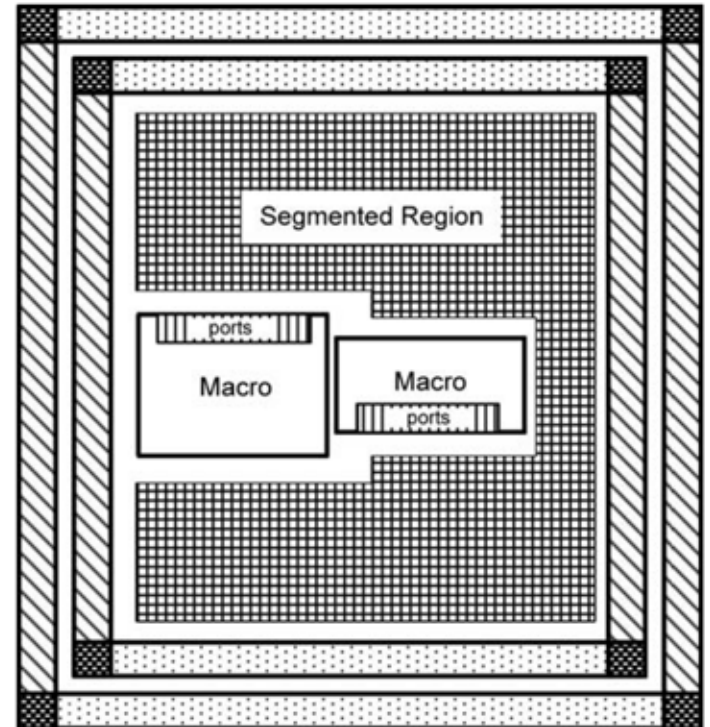- **Determine block sizes**
 - Function of SC pitch, Cell Placement, RLM, SC/SDP, Custom/Memory Block Sizing and Block Routing Overhead (Signals, Clocking, Power)



Floorplanning 101

 - **Determine block sizes**
 - Function of SC pitch, Cell Placement, RLM, SC/SDP, Custom/Memory Block Sizing and Block Routing Overhead (Signals, Clocking, Power)
- **Determine core size**
 - Function of #Blocks, Block sizes, Block Aspect Ratios, Global Routing Overhead (Signals, Clocking, Power)
- **Determine I/O ring size**
 - Function of the number of I/O, Number



Floorplanning

- **How do you estimate block areas?**
 - Begin with block diagram
 - Each block has
 - Inputs
 - Outputs
 - Function (draw schematic)
 - Type: array, datapath, random logic
- **Estimation depends on type of logic**
 - RLM: Random Logic Macro
 - Datapath
 - Array

Area Estimation

■ Arrays:

- Layout basic cell
- Calculate core area from # of cells
- Allow area for decoders, column circuitry

■ Datapaths

- Sketch slice plan
- Count area of cells from cell library
- Ensure wiring is possible

■ Random logic



- Compare complexity do a design you have done

Metal Planning

- **Metal layer, width, spacing and shielding are negotiable**
 - “Negotiable” means you have to plead your case to the integration leader
 - All of these impose a physical constraint for layout
- **Typical 8 layer metal layer allocation**
 - M1,M2 : Local routing (standard cell)
 - M3,M4, M5, M6 : Data and control
 - M7,M8 : Power, Ground, Clock, Reset, etc
 - Assume HVH routing:
 - Metal-1: Horizontal
 - Metal-2: Vertical
 - Metal-3: Horizontal
 - Metal-4: Vertical
 -
- **Use standard 'HALO' cells to make the resulting 'floor-plannable' objects 'snap' to the desired power and routing grids.**
 - Added to the boundary of all custom layouts (as well as synthesized blocks).

Chip & Block Level Clock Routing

 
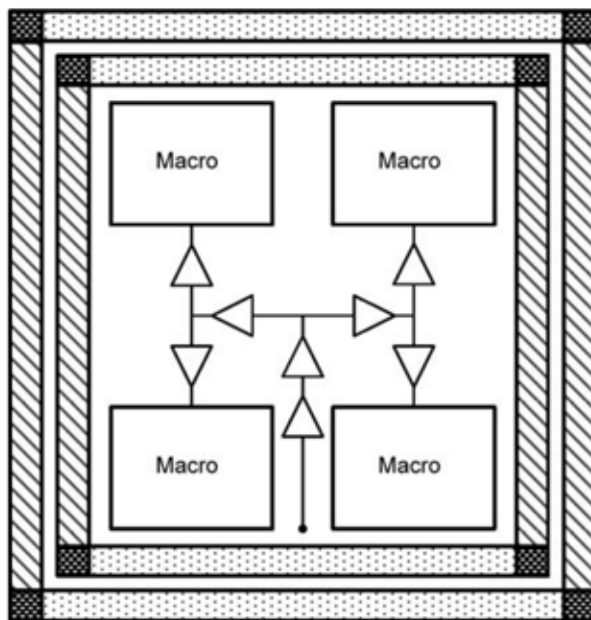
- Watch out for the clock, it's your most critical net
- Make sure the physical design treats it accordingly
- Help reduce clock power by eliminating unnecessary load
- Make sure the clock net has enough via coverage
- Use a combination of Global (Chip) and Block Level Clock distribution



Chip level power routing


- **Power busses are a combination of rings and/or grids.**
 - Rings are generally in the I/O ring.
 - Grids are used at the chip and block level
 - Grid pitch is set by horizontal and vertical routing resource requirements

  - **Special consideration needs to be taken for multiple power domains.**
 - There can be any number of power domains depending on the system architecture
 - Analog blocks require isolation rings
 - Interfaces between blocks require level shifters




Eye candy: Floorplan examples


Apple A8 SOC (for iPhone)

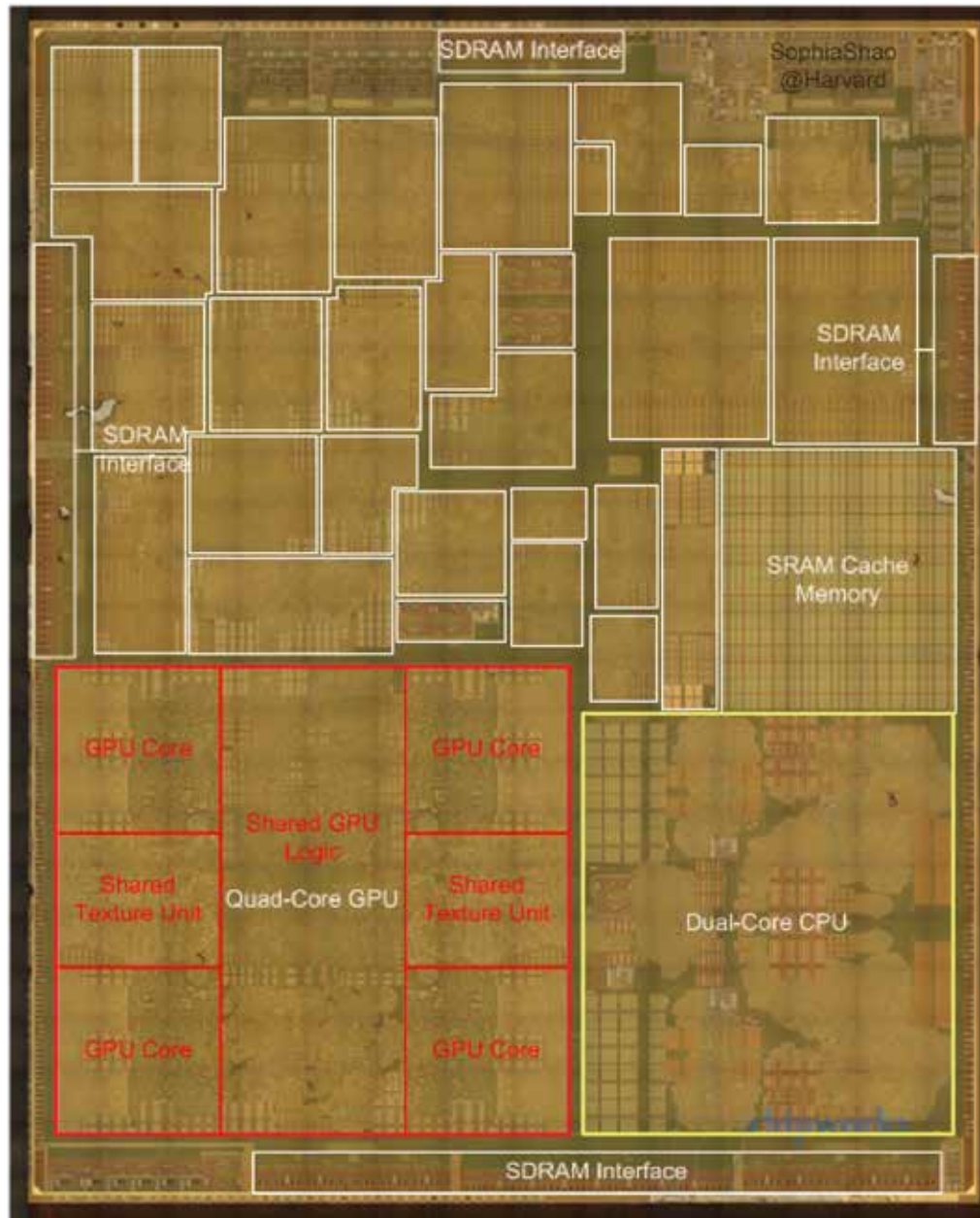

Apple A8X SOC (for iPad)

 


Flip chip power mesh for AMD Jaguar

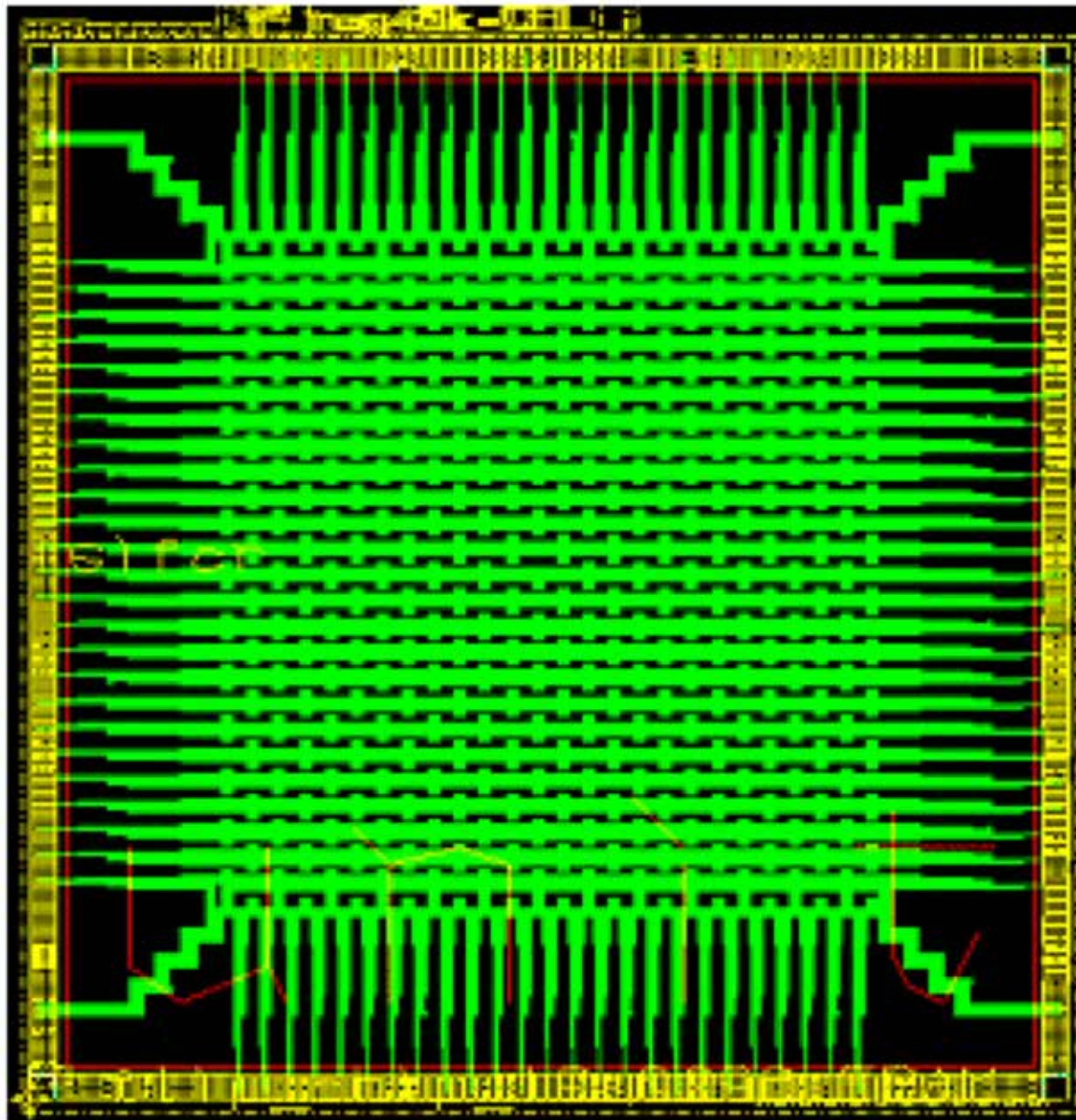


Flip-Chip
Power Mesh
(Top Layer)


SPARC Multicore Processor

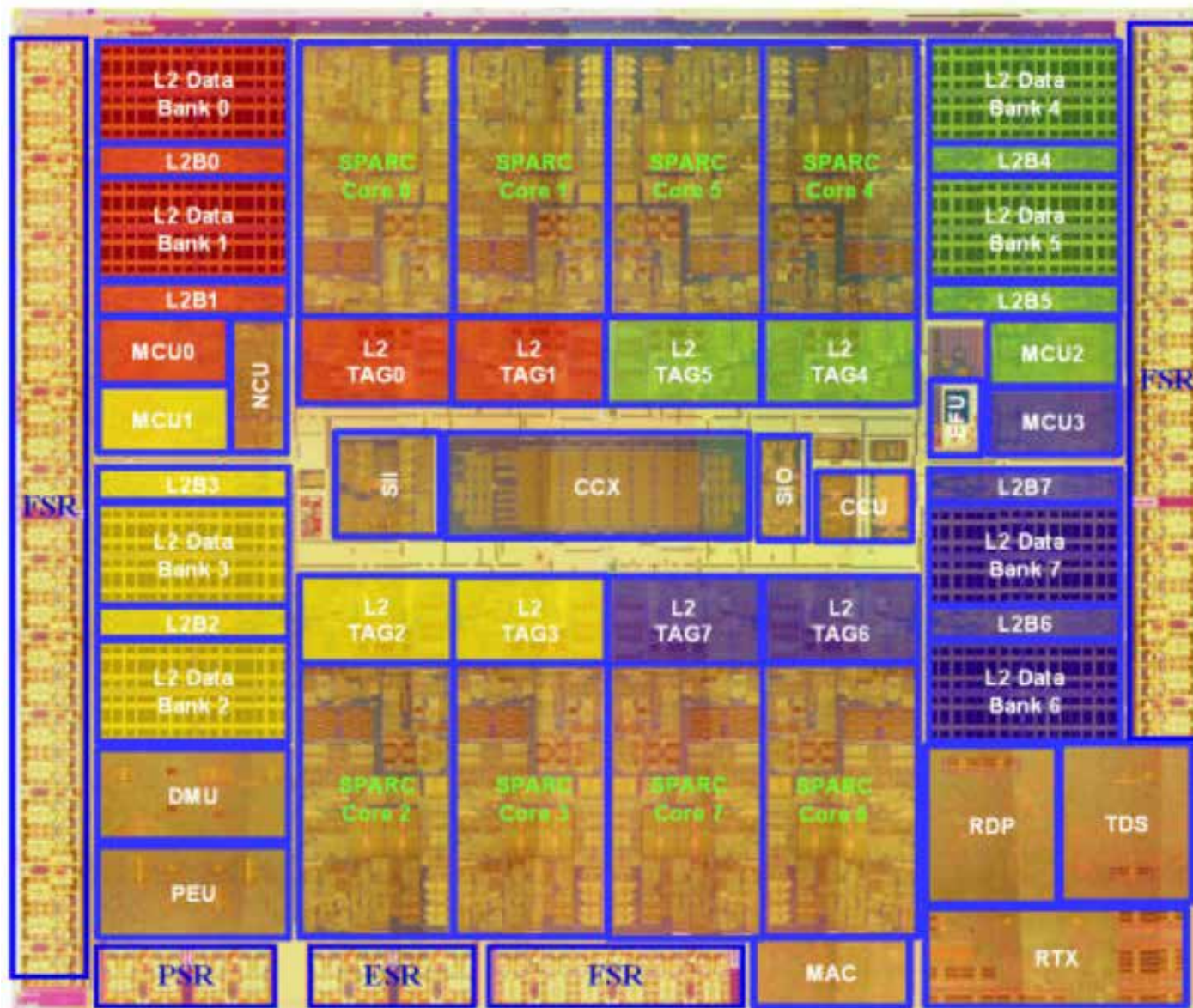

Xilinx XC2C32A CPLD

 


Analog Devices LNA

 


Implementation Techniques


Implementation Choices

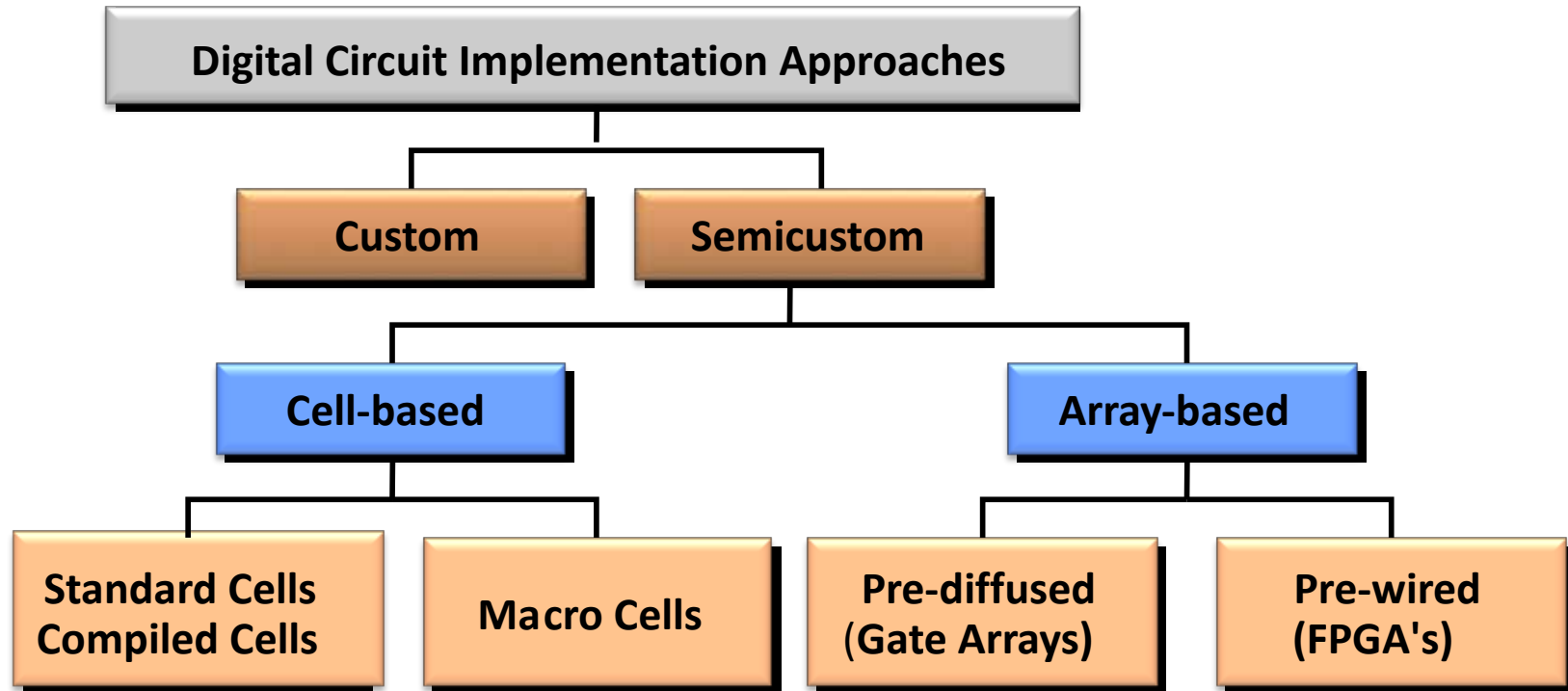

Path from RTL to structural netlist

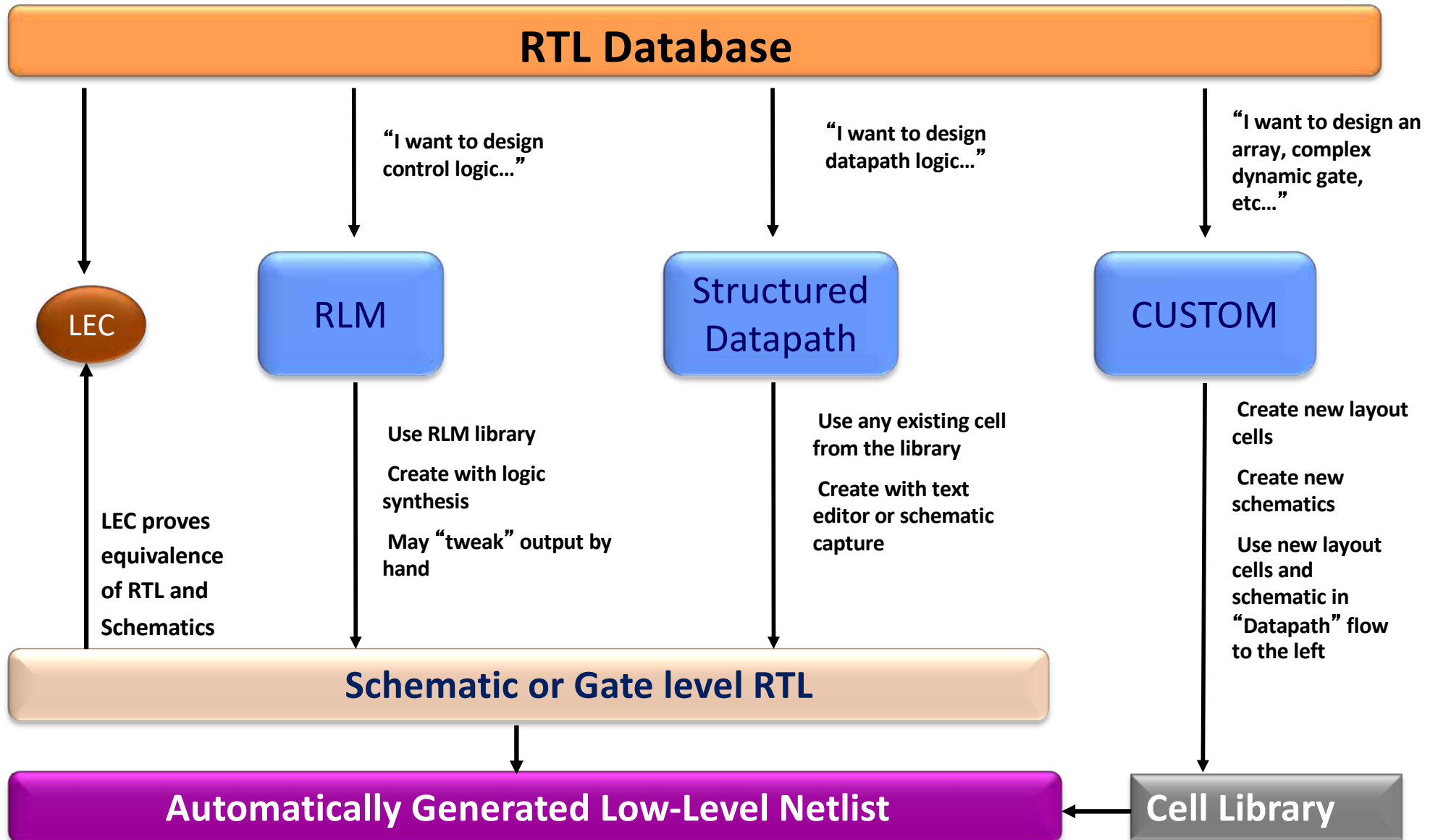

The Custom Approach

 


Intel 4004


© Digital Integrated Circuits^{2nd}

Courtesy Intel

 
Transition to Automation and Regular Structures




Intel 4004 ('71)

 


Intel 8080

 

Intel 8085

 

Intel 8286

 


Intel 8486


© Digital Integrated Circuits^{2nd}

Courtesy Intel

Cell-based Design (or standard cells)

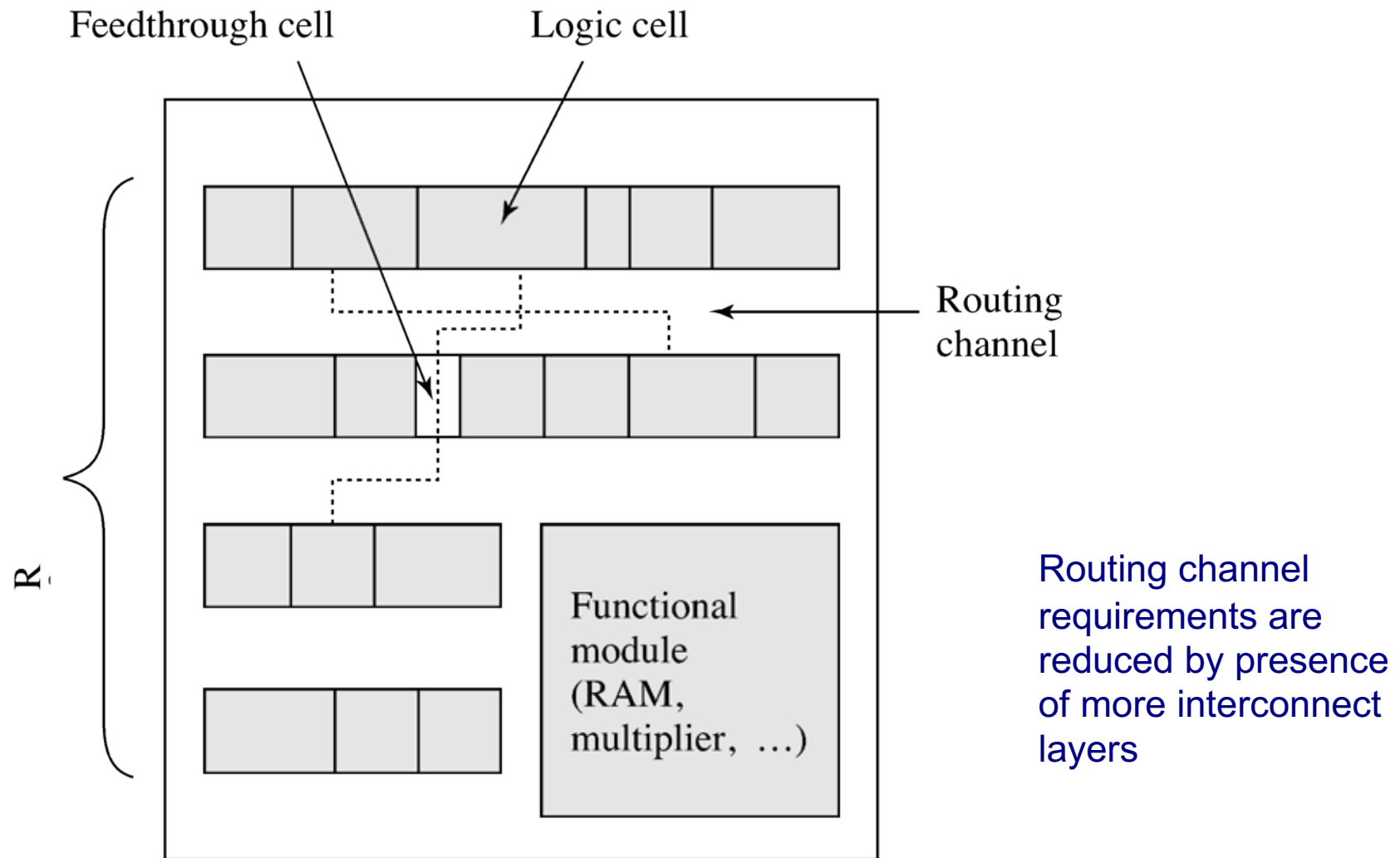


Standard Cell — Example

 

[Brodersen92]

© Digital Integrated Circuits^{2nd}


Standard Cell – The New Generation

 

*Cell-structure
hidden under
interconnect layers*

© Digital Integrated Circuits^{2nd}


Standard Cell - Example

 

Path	1.2V - 125°C	1.6V - 40°C
$In1-t_{pLH}$	$0.073+7.98C+0.317T$	$0.020+2.73C+0.253T$
$In1-t_{pHL}$	$0.069+8.43C+0.364T$	$0.018+2.14C+0.292T$
$In2-t_{pLH}$	$0.101+7.97C+0.318T$	$0.026+2.38C+0.255T$
$In2-t_{pHL}$	$0.097+8.42C+0.325T$	$0.023+2.14C+0.269T$
$In3-t_{pLH}$	$0.120+8.00C+0.318T$	$0.031+2.37C+0.258T$
$In3-t_{pHL}$	$0.110+8.41C+0.280T$	$0.027+2.15C+0.223T$

3-input NAND cell
(from ST Microelectronics):
C = Load capacitance
T = input rise/fall time

Automatic Cell Generation

 

Initial transistor geometries


Placed transistors

Routed cell

Compacted cell

Finished cell


MacroModules

 


256×32 (or 8192 bit) SRAM
Generated by hard-macro module generator

© Digital Integrated Circuits^{2nd}



“Soft” MacroModules

 
 
```
string mat = "booth";  
directive (multtype = mat);  
output signed [16] Z = A * B;
```




“Intellectual Property” (IP) Cores

 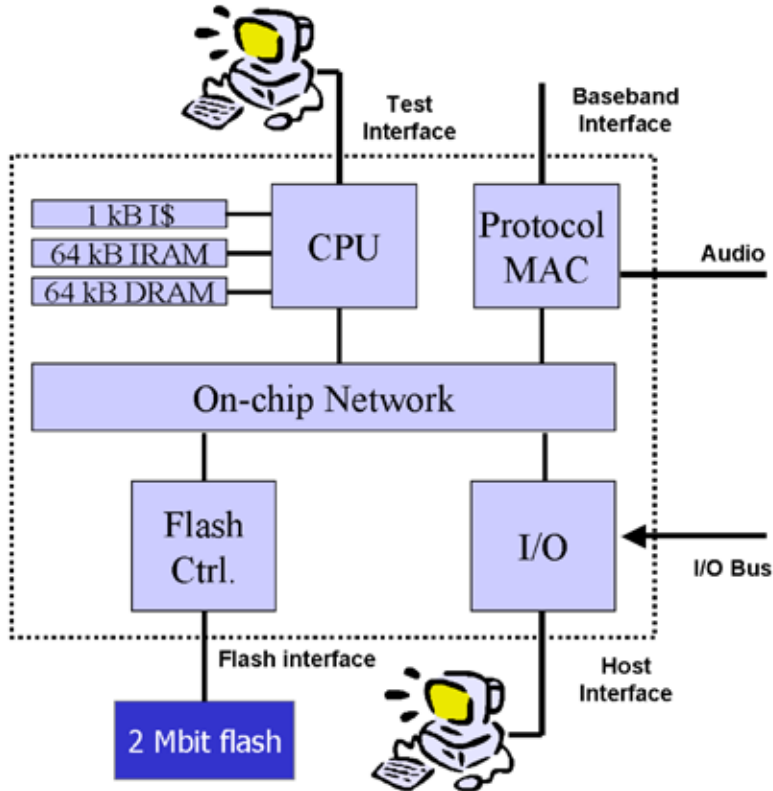


A Protocol Processor for Wireless

© Digital Integrated Circuits^{2nd}

Semicustom Design Flow

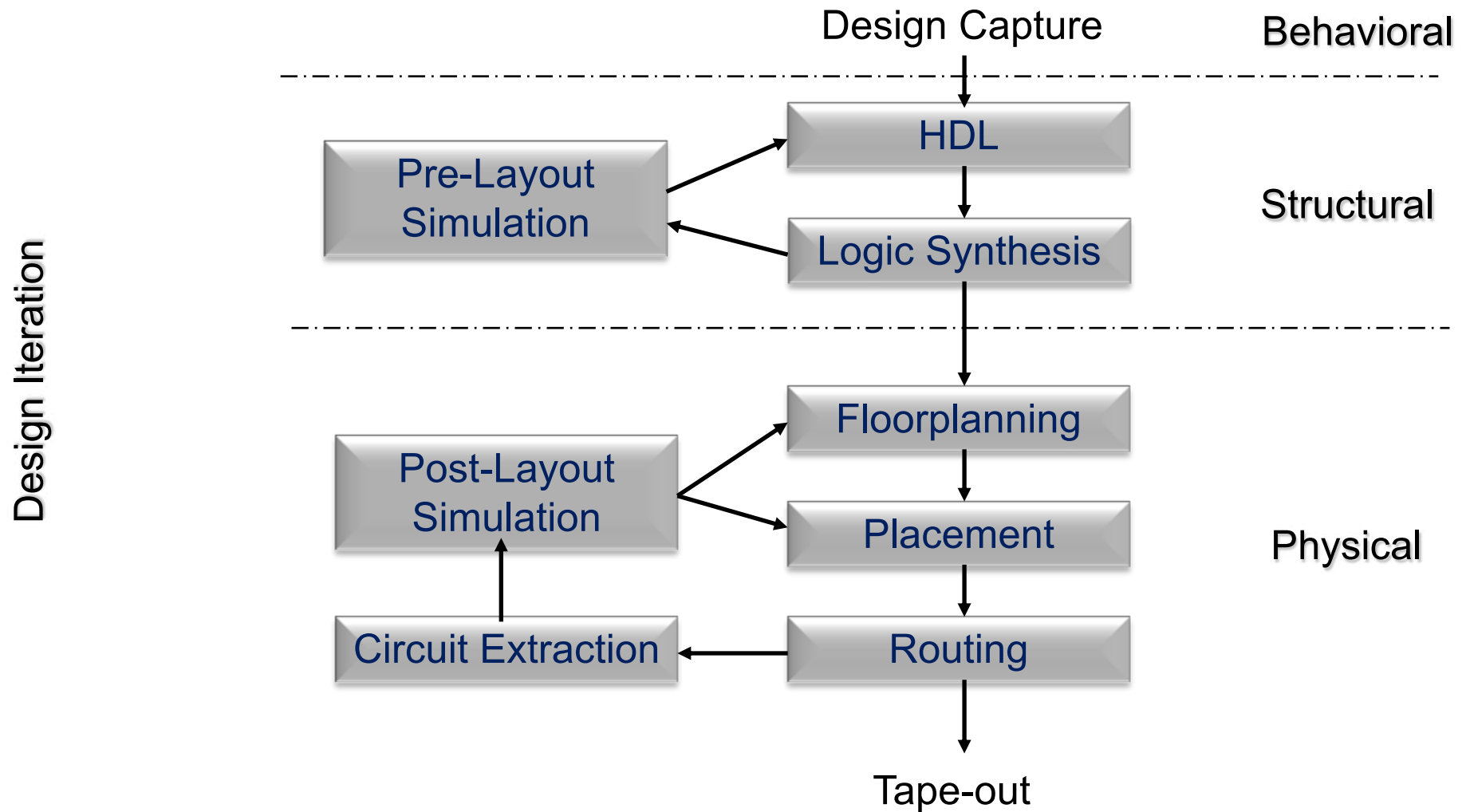


The “Design Closure” Problem

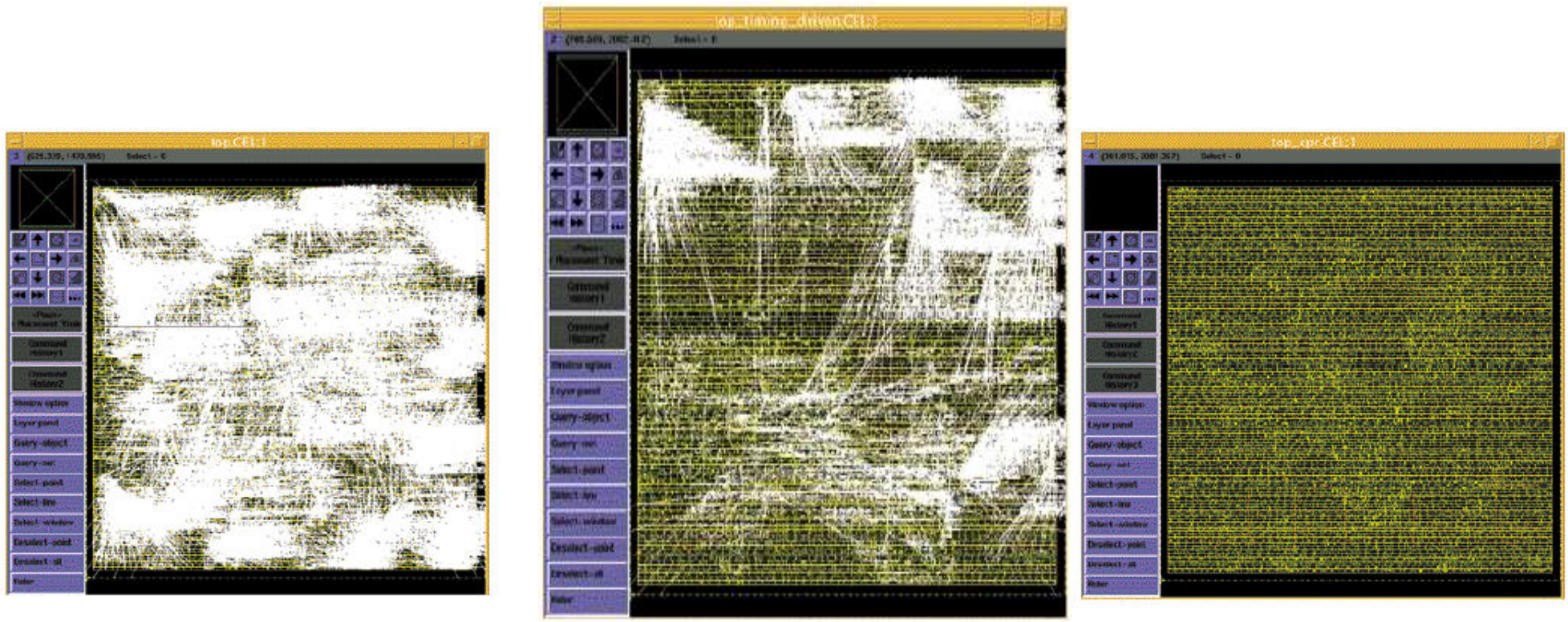


Iterative Removal of Timing Violations (white lines)

Courtesy Synopsys


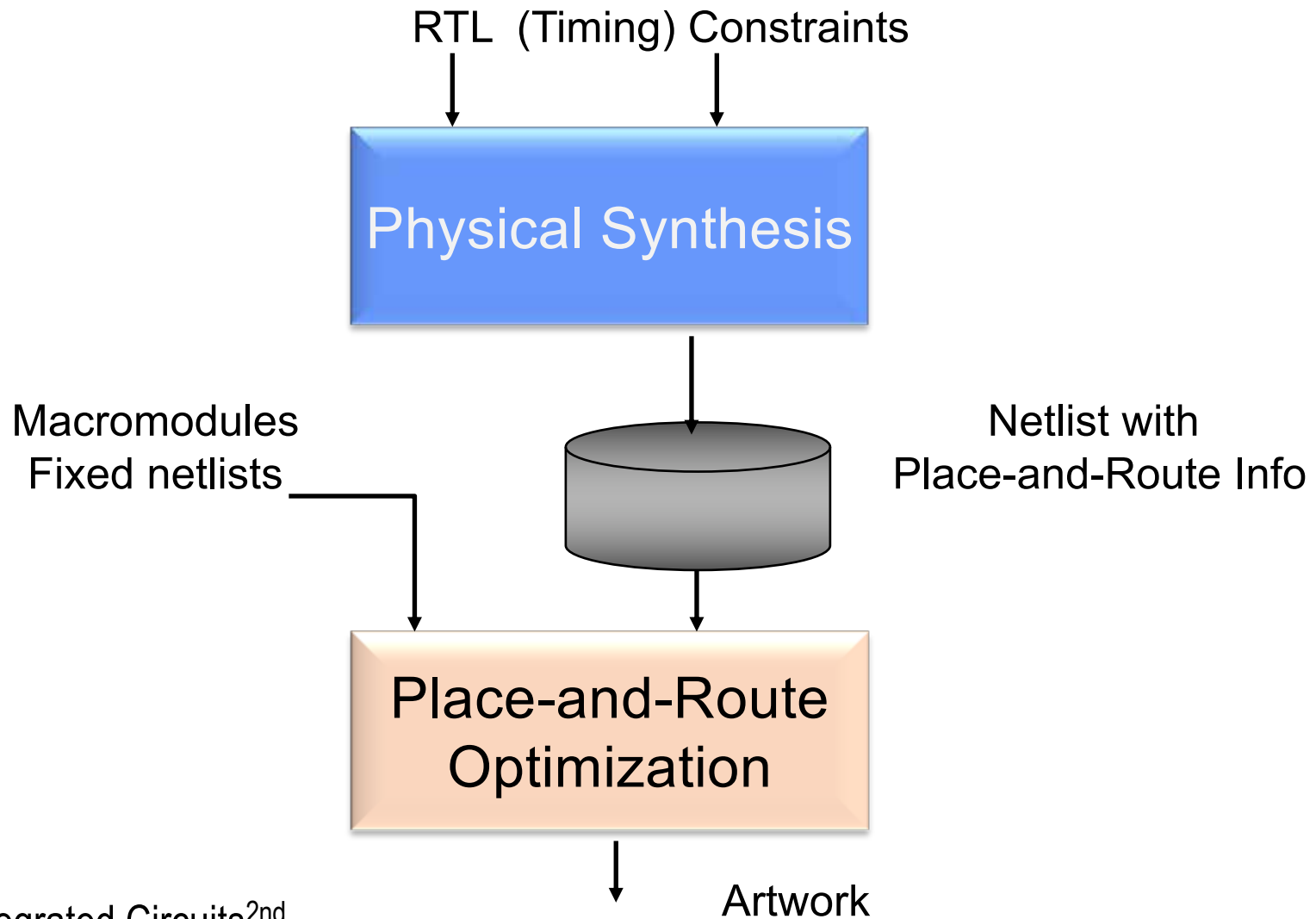
Integrating Synthesis with Physical Design




Late-Binding Implementation

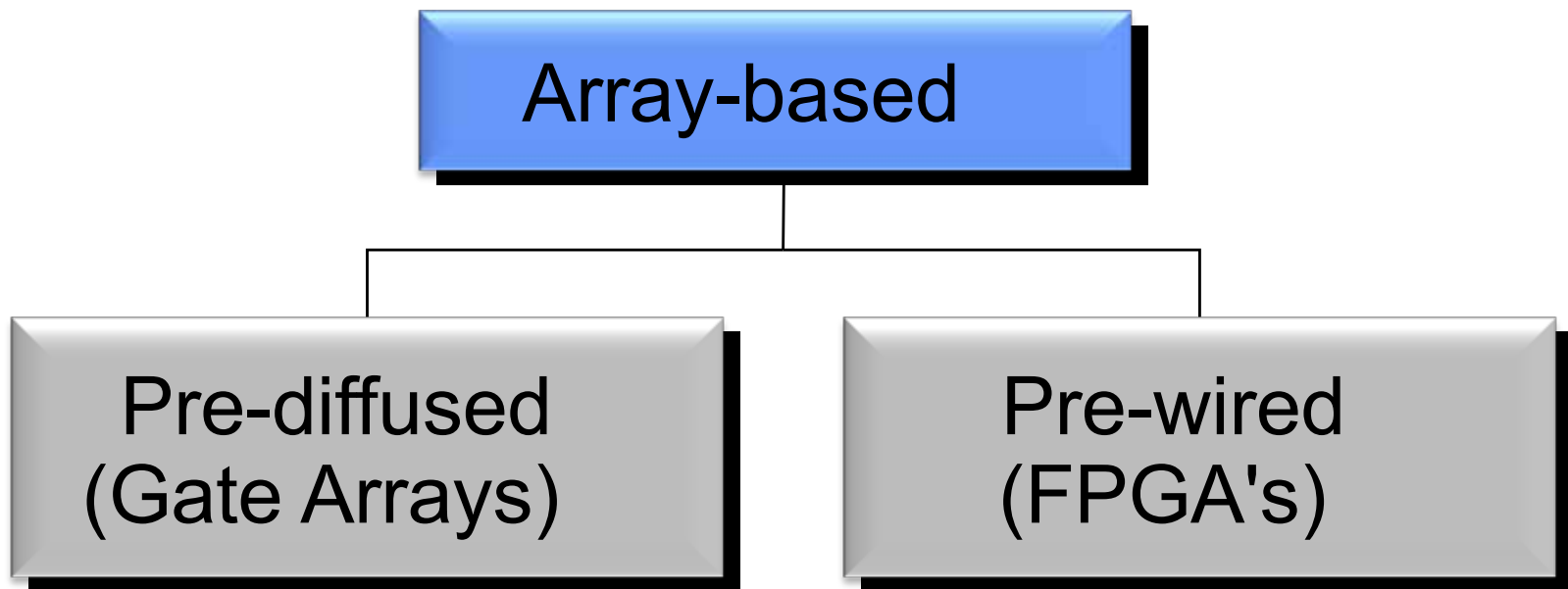

Gate Array — Sea-of-gates

 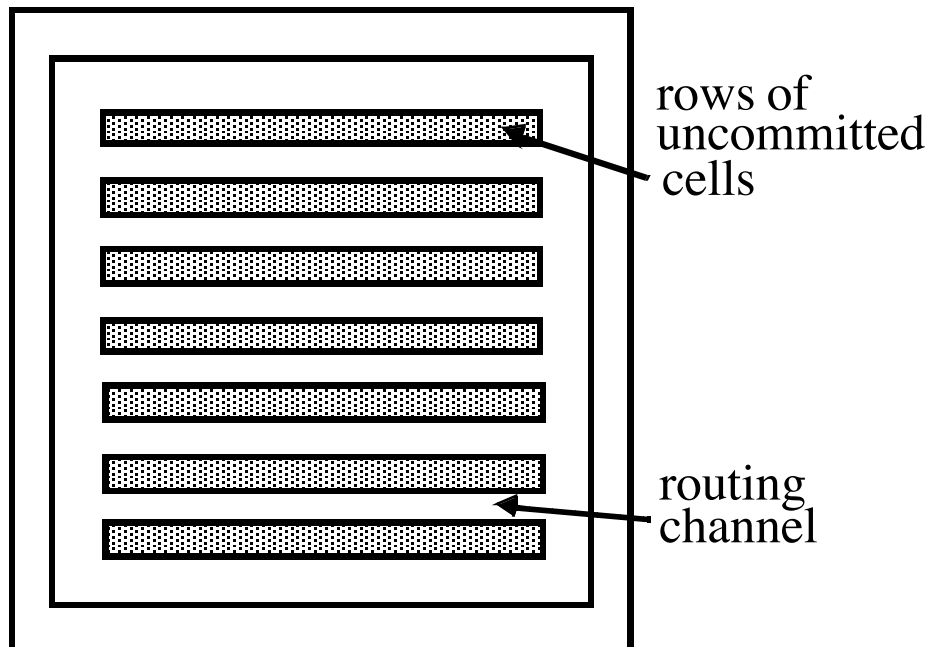


Uncommitted Cell

 


Committed Cell
(4-input NOR)

Sea-of-gate Primitive Cells

 


Using oxide-isolation

 


Using gate-isolation

Example: Base Cell of Gate-Isolated GA

 


Example: Flip-Flop in Gate-Isolated GA

 

© Digital Integrated Circuits^{2nd}

From Smith97

Sea-of-gates

 

© Digital Integrated Circuits^{2nd}

LSI Logic LEA300K
(0.6 μm CMOS)

Courtesy LSI Logic

Prewired Arrays

- **Classification of prewired arrays (or field-programmable devices):**
 - **Based on Programming Technique**
 - Fuse-based (program-once)
 - Non-volatile EPROM based
 - RAM based
 - **Programmable Logic Style**
 - Array-Based
 - Look-up Table
 - **Programmable Interconnect Style**
 - Channel-routing
 - Mesh networks