
Lecture 4: Implementing Logic in CMOS

Mark McDermott


**Electrical and Computer Engineering
The University of Texas at Austin**

Review of DeMorgan's Theorem

Recall that:







$$(AB)' = A' + B' \quad \text{and} \quad AB = (A' + B')'$$
 
$$(A+B)' = A'B' \quad \text{and} \quad A+B = (A'B)'$$




Bubble Pushing

      - Start with network of AND / OR gates
- Convert to NAND / NOR + inverters
- Push bubbles around to simplify logic




Static CMOS Circuits

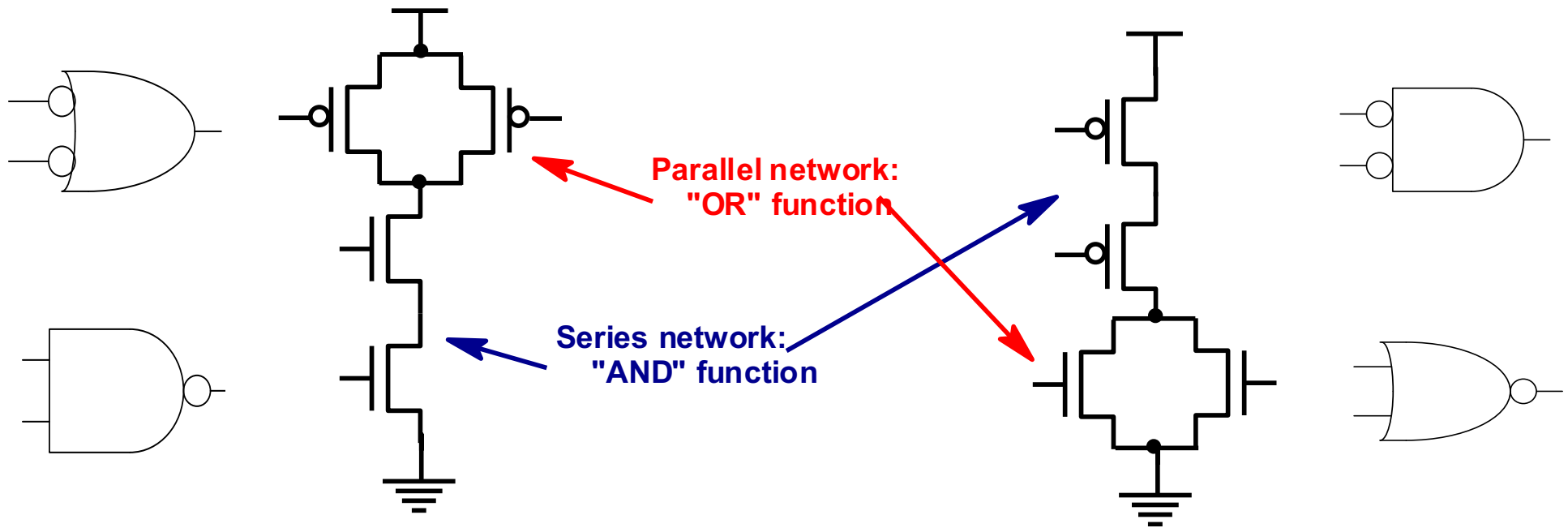- **N and P channel networks implement logic functions**
 - Each network connected between Output and VDD or VSS



Duality in CMOS Circuits

 - N and P networks must implement complementary functions
- Duality is sufficient for correct operation




What are the values of A, B and C which will produce a connection between P and Q

$$A + B * C$$


Constructing Complex Gates

 - **Example: $F = \overline{(A * B) + (C * D)}$**
 - Take un-inverted function $F = (AB + CD)$ and derive N-network
 - Identify AND, OR components; F is OR of AB,CD
 - Make connections of transistors
 - **AND , Series connection, OR , Parallel**




Example of Compound Gate

$$F = \overline{(A + B + C)} * D$$



 


Example of More Complex Gate

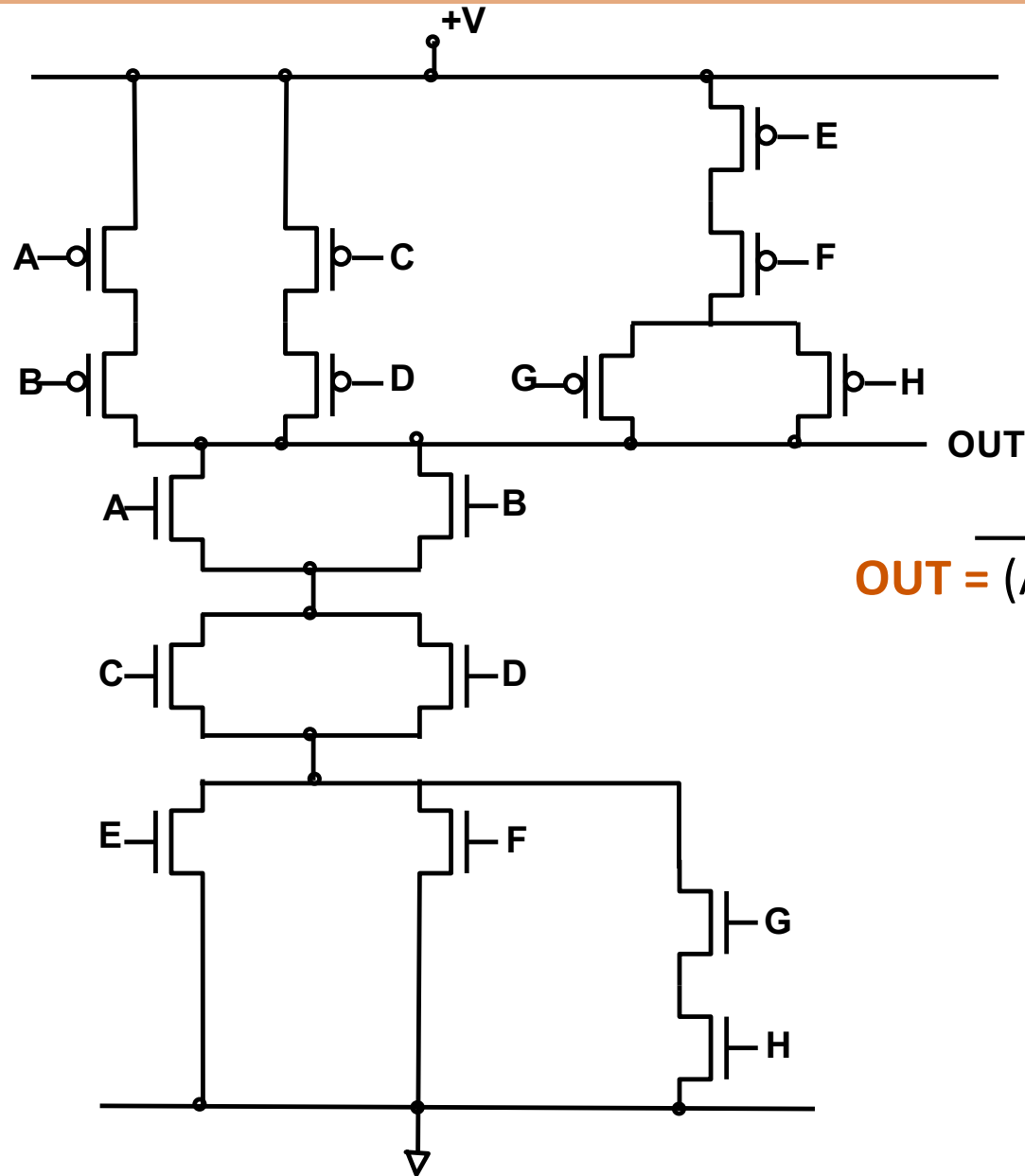


$$\text{OUT} = (A+B) * (C+D) * (E+F+GH)$$

Exclusive-NOR Gate in CMOS

   


Pseudo nMOS Logic

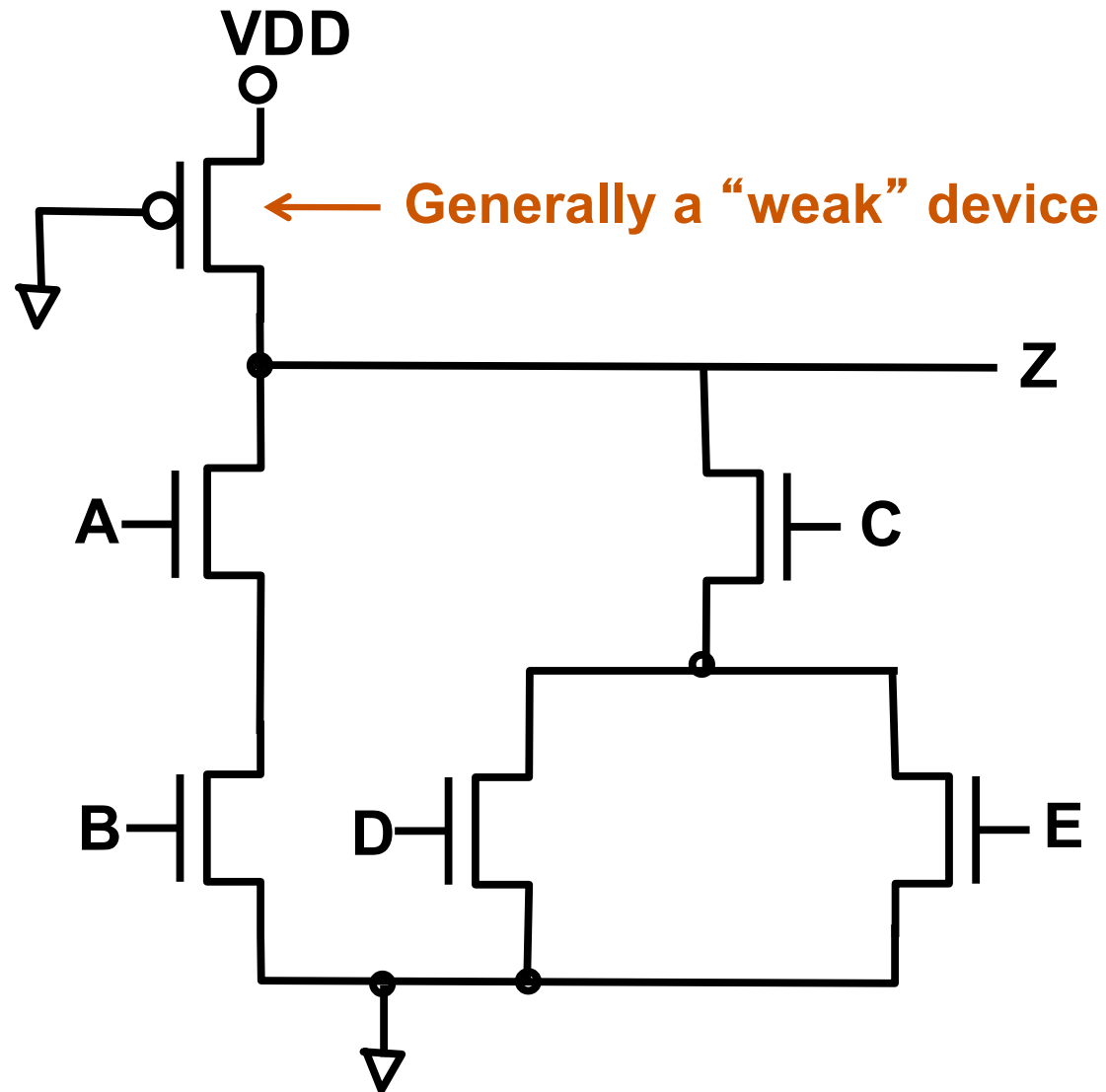

Duality is not Necessary

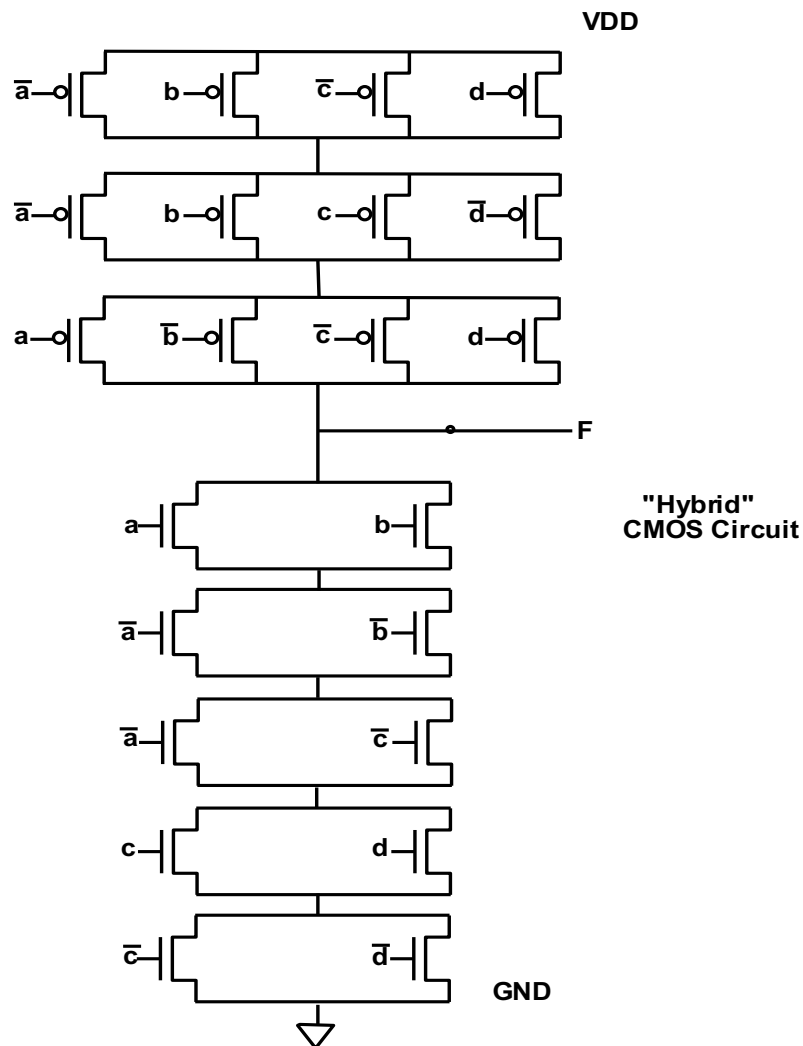
- Functions realized by N and P networks must be complementary, and one of them must conduct for every input combination



$$F = ab + a' b' + a' c' + cd + c' d'$$

The N and P networks are NOT duals, but the switching functions they implement are **complementary**

Example of "Dual Rail" Complex CMOS Gate

 

F =










G =

Signal Strength

- **Strength of signal**
 - How close it approximates ideal voltage source
- **V_{DD} and GND rails are strongest 1 and 0**
- **nMOS pass strong 0**
 - But degraded or weak 1
- **pMOS pass strong 1**
 - But degraded or weak 0
- **Thus nMOS are best for pull-down network**


Pass Transistors

- Transistors can be used as switches

         


Transmission Gates

 
- Pass transistors produce degraded outputs
- *Transmission gates* pass both 0 and 1 well




$g = 0, gb = 1$

 





$g = 1, gb = 0$

 

$g = 1, gb = 0$

 


$g = 1, gb = 0$

    


Pass Transistor Logic -- Better Layout

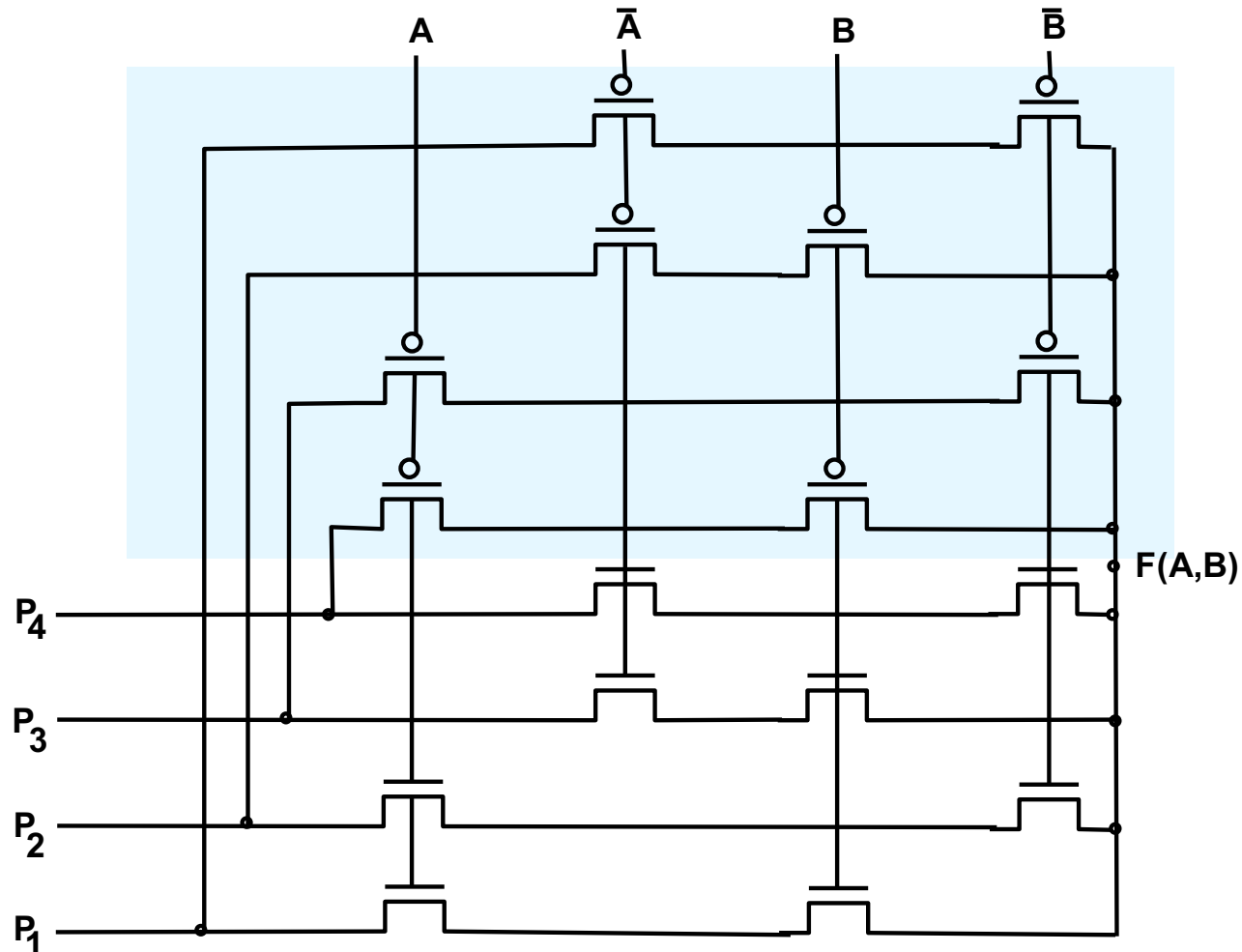- Group similar transistors, so they can be in the same well



Pass Transistor Logic Pull-Up Version

 
- How do voltage levels at the output of this gate differ from that of the pass-transistor multiplexer in the previous foil?



Tristates


- *Tristate buffer produces Z when not enabled*

EN	A	Y
0	0	
0	1	
1	0	
1	1	

 


Non-restoring Tri-state[®]

 - **Transmission gate acts as Tri-state[®] buffer**
 - Only two transistors
 - But nonrestoring
 - Noise on A is passed on to Y



Tri-state[®] Inverter

 
- **Tri-state[®] inverter produces restored output**
 - Violates conduction complement rule
 - Because we want a Z output



Multiplexers (mux)

- **2:1 multiplexer chooses between two inputs**



S	D1	D0	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

 

Gate-Level Mux Design


- How many transistors are needed?
  
$$Y = SD_1 + \bar{S}D_0 \text{ (too many transistors)} \quad 20$$




Transmission Gate Mux

 - **Nonrestoring mux uses two transmission gates**
 - Only 4 transistors if both of the select signals are available
 - If not then it takes 6 transistors...




Inverting Mux

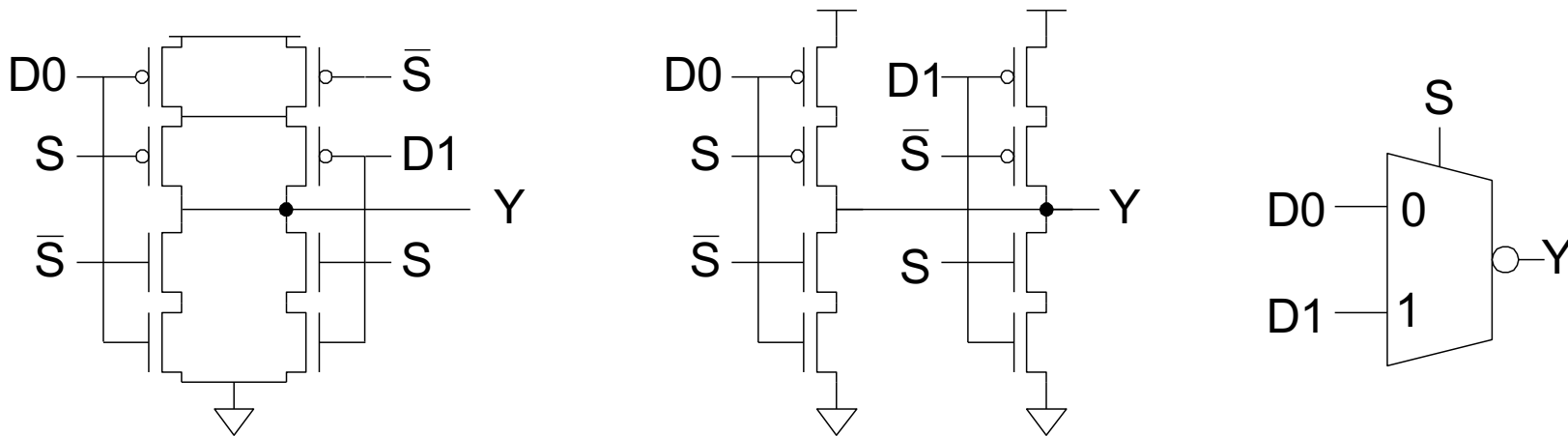- **Inverting multiplexer**
 - Use compound AOI22
 - Or pair of tristate inverters
 - Essentially the same thing
- **Non-inverting multiplexer requires adding an inverter**




4:1 Multiplexer

 - **4:1 mux chooses one of 4 inputs using two selects**
 - Two levels of 2:1 muxes
 - Or four tristates




Requires pre-decoded signals

 

D Latch**


 
- When $CLK = 1$, latch is *transparent*
 - D flows through to Q like a buffer
- When $CLK = 0$, the latch is *opaque*
 - Q holds its old value independent of D



** *transparent latch or level-sensitive latch*



D Latch Design

- Multiplexer chooses D or old Q

  

D Flip-flop Design

- Built from master and slave D latches

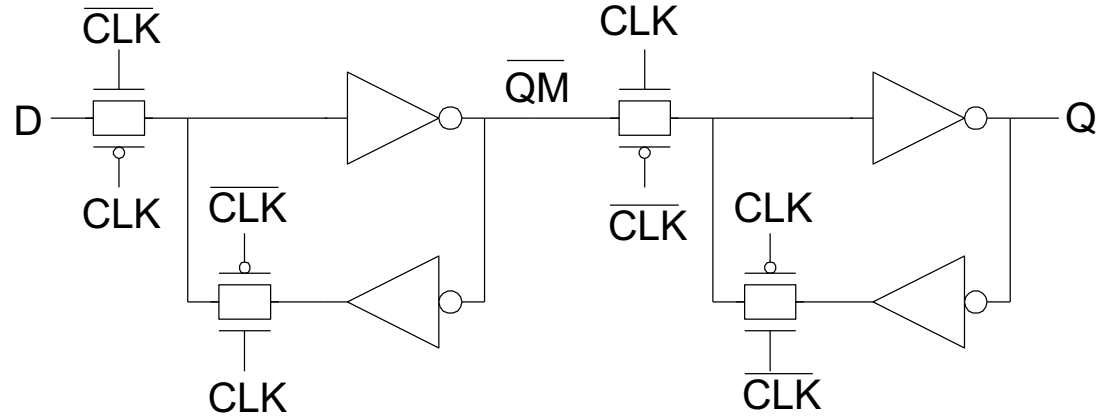 

Questions?