

Lecture 7: CMOS DC & Transient Response

Mark McDermott

Electrical and Computer Engineering
The University of Texas at Austin

Agenda

- **DC Response**
- **Logic Levels and Noise Margins**
- **Transient Response**
- **Delay Estimation**

DC Response


- **DC Response: V_{out} vs. V_{in} for a gate**

- **Ex: Inverter**

- When $V_{in} = 0 \rightarrow V_{out} = V_{DD}$
- When $V_{in} = V_{DD} \rightarrow V_{out} = 0$
- In between, V_{out} depends on transistor size and current
- By KCL, we know that


$$I_{dsn} = |I_{dsp}|$$

 - We could solve equations
- But graphical solution gives more insight



Transistor Operation Review

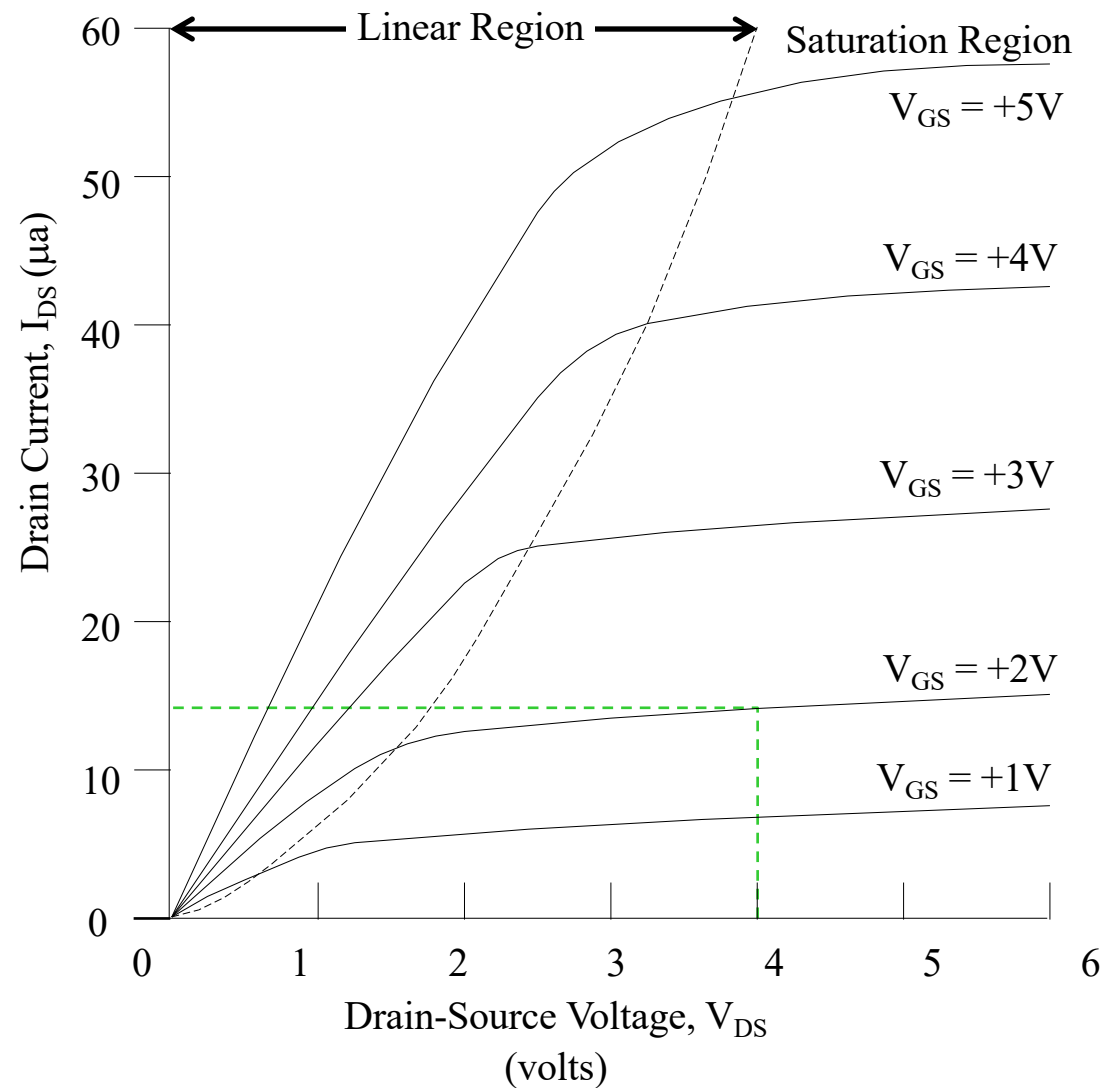- **Current depends on region of transistor behavior**
- **For what V_{in} and V_{out} are nMOS and pMOS in**
 - Cutoff?
 - Linear?
 - Saturation?




nMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} < V_{tn}$ $V_{in} < V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} < V_{gsn} - V_{tn}$ $V_{out} < V_{in} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} > V_{gsn} - V_{tn}$ $V_{out} > V_{in} - V_{tn}$

$$V_{gsn} = V_{in}$$

$$V_{dsn} = V_{out}$$

 


pMOS Operation

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$ $V_{in} > V_{DD} + V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$

$$V_{gsp} = V_{in} - V_{DD}$$


$$V_{dsp} = V_{out} - V_{DD}$$

$$V_{tp} < 0$$

 


I-V Characteristics

 - Make pMOS wider than nMOS such that $\beta_n = \beta_p$




Current vs. V_{out} , V_{in}

 


Load Line Analysis

- For a given V_{in} :
 - Plot I_{dsn}, I_{dsp} vs. V_{out}
 - V_{out} must be where |currents| are equal

 


Load Line Analysis

- $V_{in} = 0$

 


Load Line Analysis

- $V_{in} = 0.2V_{DD}$

 


Load Line Analysis

- $V_{in} = 0.4V_{DD}$

 


Load Line Analysis

- $V_{in} = 0.6V_{DD}$

 


Load Line Analysis

- $V_{in} = 0.8V_{DD}$

 


Load Line Analysis

- $V_{in} = V_{DD}$


 


Load Line Summary

 

DC Transfer Curve

  
- Transcribe points onto V_{in} vs. V_{out} plot



Operating Regions



- Revisit transistor operating regions

Region	nMOS	pMOS
A	Cutoff	Linear
B	Saturation	Linear
C	Saturation	Saturation
D	Linear	Saturation
E	Linear	Cutoff

 


Beta Ratio

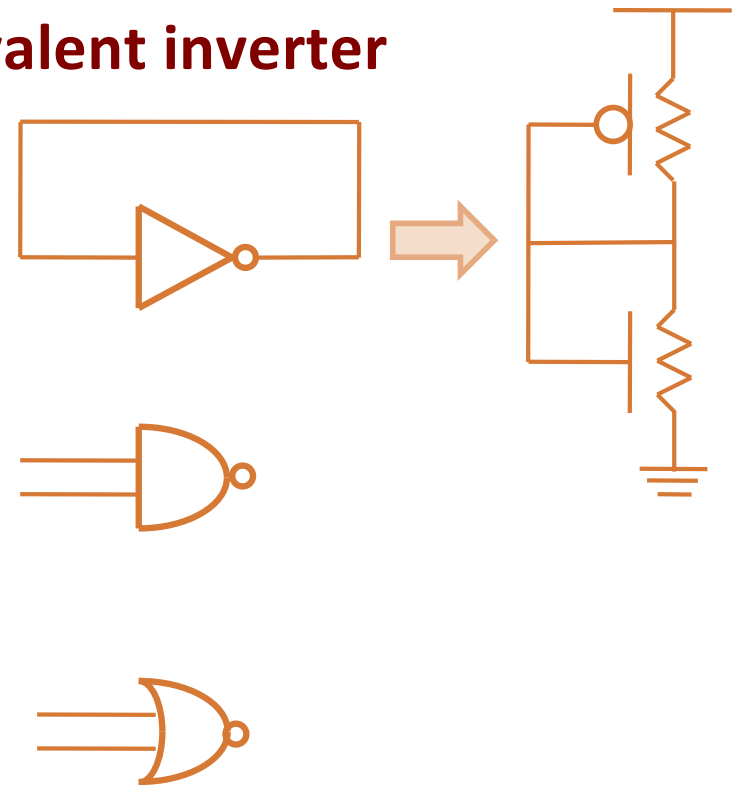 - If $\beta_p / \beta_n \neq 1$, switch point will move from $V_{DD}/2$
- Called a *skewed gate*
- Other gates: decompose into an equivalent inverter




Noise Margins

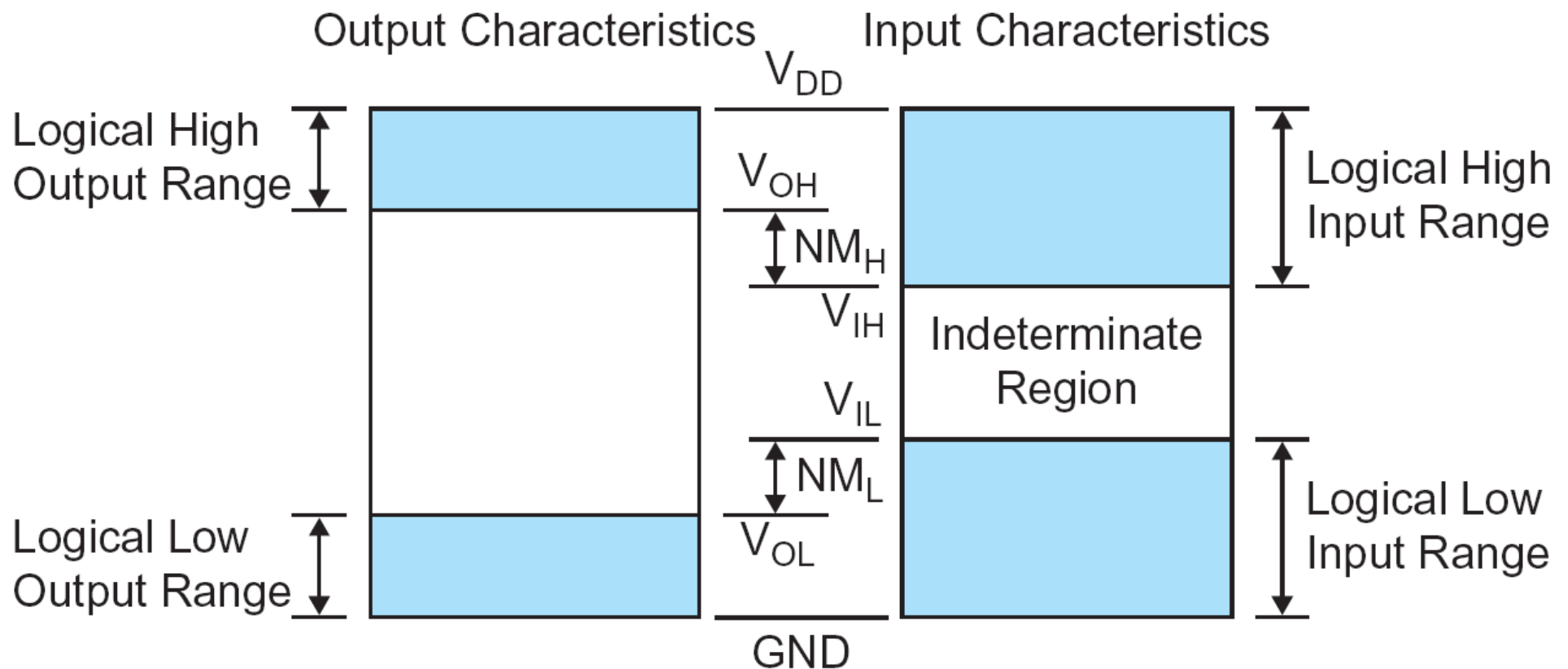- How much noise can a gate input see before it does not recognize the input?



Logic Levels

 - To maximize noise margins, select logic levels at the unity gain point of DC transfer characteristic



Transient Response

- ***DC analysis*** tells us V_{out} if V_{in} is constant

- ***Transient analysis*** tells us $V_{out}(t)$ if $V_{in}(t)$ changes
 - Requires solving differential equations

- **Input is usually considered to be a step or ramp**
 - From 0 to V_{DD} or vice versa

Inverter Step Response



- Ex: find step response of inverter driving load cap

$$V_{in}(t) = u(t - t_0)V_{DD}$$

$$V_{out}(t < t_0) = V_{DD}$$


$$\frac{dV_{out}(t)}{dt} = -\frac{I_{dsn}(t)}{C_{load}}$$
 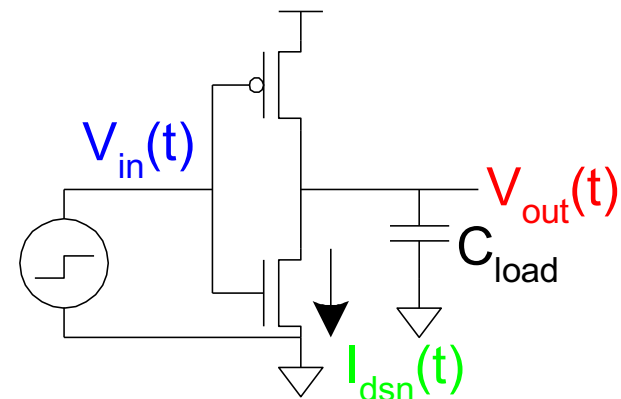
$$I_{dsn}(t) = \begin{cases} 0 & t \leq t_0 \\ \frac{\beta}{2}(V_{DD} - V)^2 & V_{out} > V_{DD} - V_t \\ \beta\left(V_{DD} - V_t - \frac{V_{out}(t)}{2}\right)V_{out}(t) & V_{out} < V_{DD} - V_t \end{cases}$$




Delay Definitions

- **t_{pdr} : rising propagation delay**
 - Max time from input to rising output crossing $V_{DD}/2$
- **t_{pdf} : falling propagation delay**
 - Max time from input to falling output crossing $V_{DD}/2$
- **t_{pd} : average propagation delay**
 - $t_{pd} = (t_{pdr} + t_{pdf})/2$
- **t_r : rise time**
 - From output crossing $0.2 V_{DD}$ to $0.8 V_{DD}$
- **t_f : fall time**
 - From output crossing $0.8 V_{DD}$ to $0.2 V_{DD}$

 

Delay Definitions

 - **t_{cdr} : rising contamination delay**
 - Minimum time from input to rising output crossing $V_{DD}/2$
- **t_{cdf} : falling contamination delay**
 - Minimum time from input to falling output crossing $V_{DD}/2$
- **t_{cd} : average contamination delay**
 - $t_{pd} = (t_{cdr} + t_{cdf})/2$




NOTE:

Contamination delay is not the same thing as **minimum delay**. It is the minimum amount of time from an input signal change to an output signal change

Minimum delay - is the minimum amount of time from an input signal change (to its correct value) to an output signal taking on its correct value (t_{pd})


Simulated Inverter Delay

 - Solving differential equations by hand too hard
- SPICE simulator solves equations numerically
 - Uses more accurate I-V models too!
 - But simulations can take a long time to run




Delay Estimation

 - **We would like to be able to easily estimate delay**
 - Not as accurate as simulation
 - But easier to ask “What if?”
- **The step response usually looks like a 1st order RC response with a decaying exponential.**
- **Use RC delay models to estimate delay**
 - C = total capacitance on output node
 - Use effective resistance R
 - So that $t_{pd} = R_{eff}C$





Effective Resistance

- **Shockley models have limited value**
 - Not accurate enough for modern transistors
 - Too complicated for much hand analysis
- **Simplification: treat transistor as resistor**
 - Replace $I_{ds}(V_{ds}, V_{gs})$ with effective resistance R
 - $I_{ds} = V_{ds}/R$
 - R averaged across switching of digital gate
- **Too inaccurate to predict current at any given time**
 - But good enough to predict RC delay

 

RC Delay Models

  - **Use equivalent circuits for MOS transistors**
 - Ideal switch + capacitance and ON resistance
 - Unit nMOS has resistance R , capacitance C
 - Unit pMOS has resistance $2R$, capacitance C
- **Capacitance proportional to width**
- **Resistance inversely proportional to width**



RC Values

■ Capacitance

- $C = C_g = C_s = C_d = 2 \text{ fF}/\mu\text{m}$ of gate width for technology scaled devices

■ Resistance


- $R \approx 10 \text{ K}\Omega \cdot \mu\text{m}$ in $0.6 \mu\text{m}$ process
- Improves with shorter channel lengths
- $1.25 \text{ K}\Omega \cdot \mu\text{m}$ in 65 nm process

■ Unit transistors


- May refer to minimum contacted device ($4/2 \lambda$)
- Or maybe $1 \mu\text{m}$ wide device
- Doesn't matter as long as you are consistent

Inverter Delay Estimate

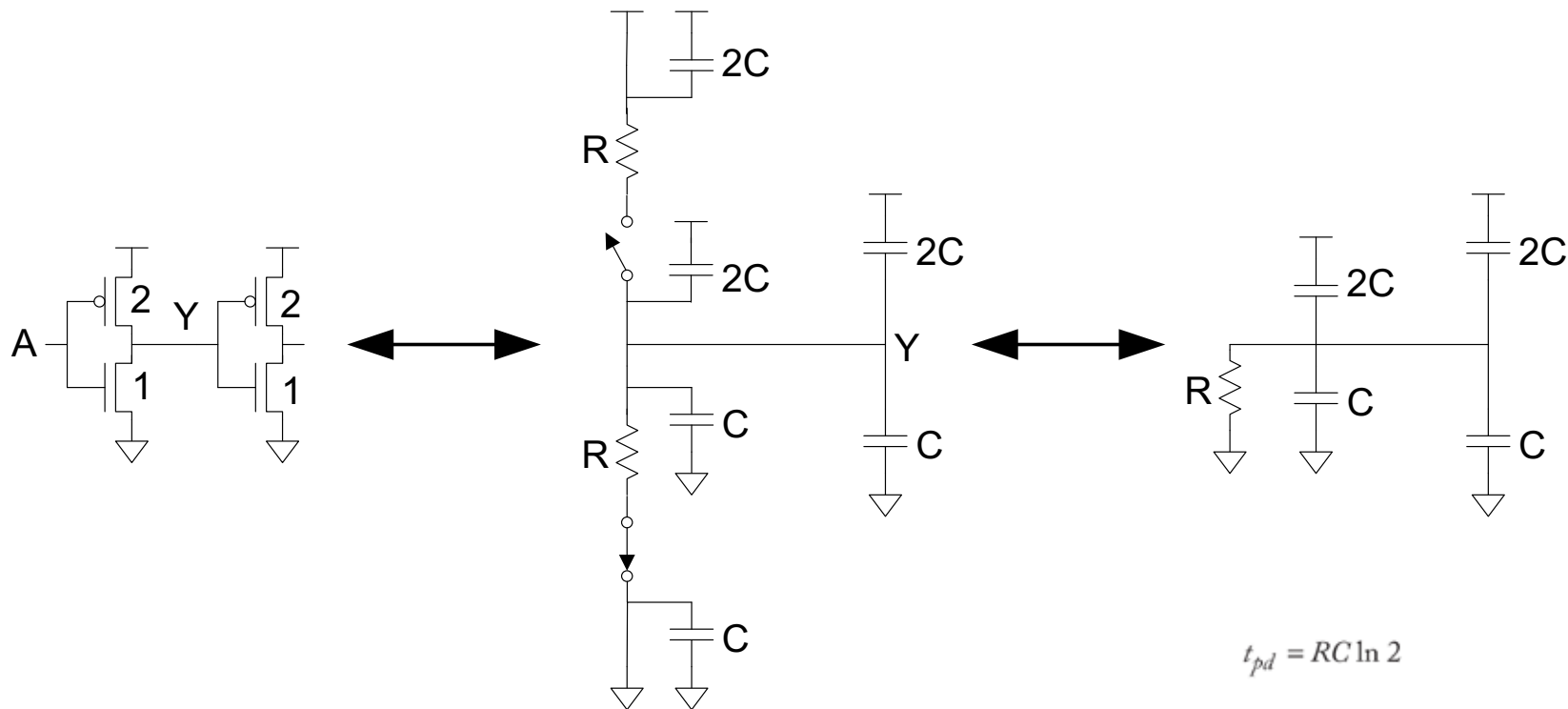
- Estimate the delay of a fanout-of-1 inverter



$$d = R_{\text{eff}} * 6C$$

 


Delay Model Comparison

 

 
Example: 3-input NAND

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).
 - Assume $\beta_p = \frac{1}{2}\beta_n$



3-input NAND Caps

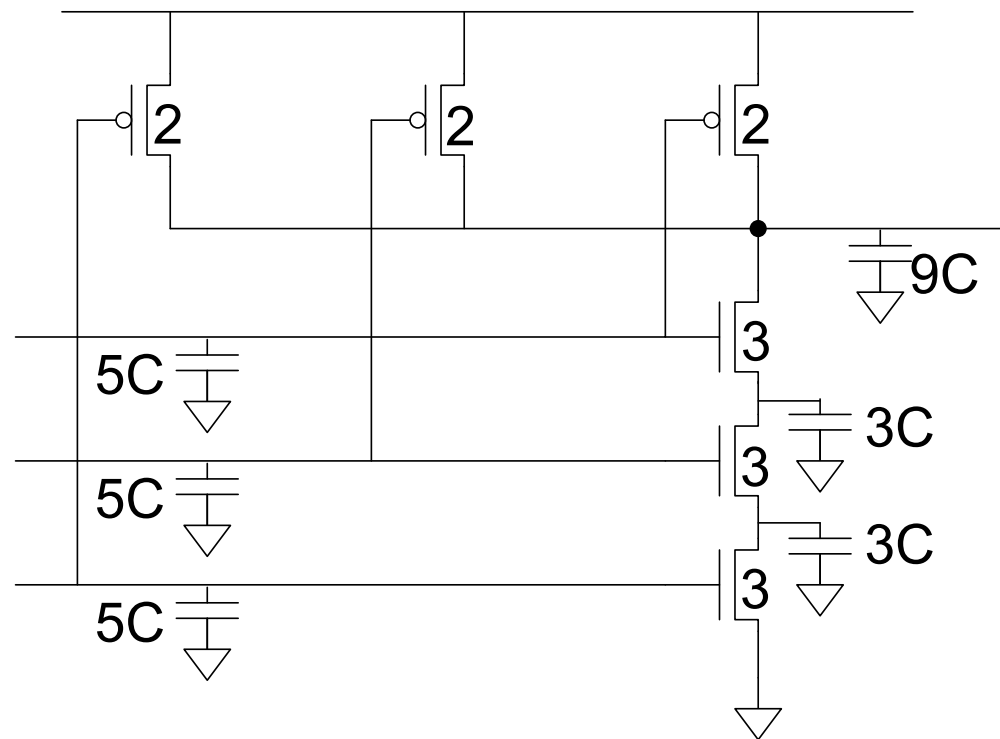- Annotate the 3-input NAND gate with gate and diffusion capacitance.




Elmore Delay

- ON transistors look like resistors
- Pullup or pulldown network modeled as *RC ladder*
- Elmore delay of RC ladder





$$t_{pd} \approx \sum_{\text{nodes } i} R_{i\text{-to-source}} C_i$$
 
$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$



Fanout Example: 3-input NAND

  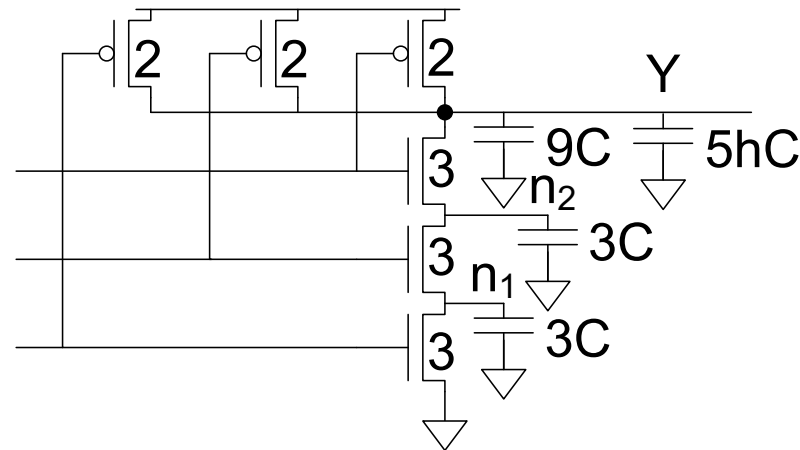 - Estimate worst-case rising and falling delay of 3-input NAND driving h identical gates.




$$t_{pdr} = (9 + 5h)RC$$

$$t_{pdf} = (3C)\left(\frac{R}{3}\right) + (3C)\left(\frac{R}{3} + \frac{R}{3}\right) + [(9 + 5h)C]\left(\frac{R}{3} + \frac{R}{3} + \frac{R}{3}\right)$$


$$= (12 + 5h)RC$$

Delay Components

 - **Delay has two parts**
 - **Parasitic delay**
 - **9 or 12 RC**
 - **Independent of load**
 - **Effort delay**
 - **5h RC**
 - **Proportional to load capacitance**



$$t_{pdr} = (9 + 5h) RC$$


 


$$t_{pdf} = (3C)\left(\frac{R}{3}\right) + (3C)\left(\frac{R}{3} + \frac{R}{3}\right) + [(9 + 5h)C]\left(\frac{R}{3} + \frac{R}{3} + \frac{R}{3}\right)$$

$$= (12 + 5h) RC$$

Contamination Delay

 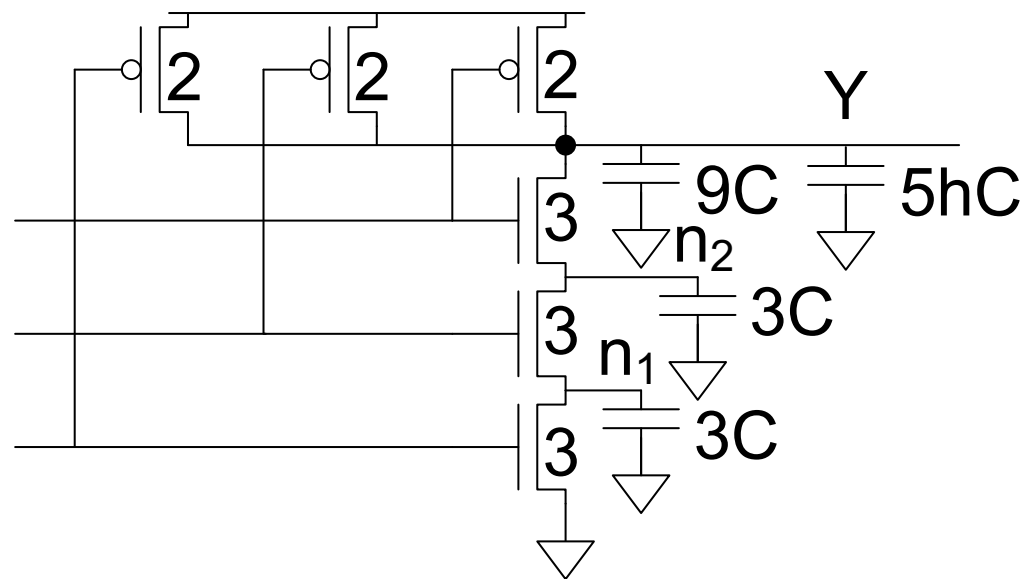
- Best-case (contamination) delay can be substantially less than propagation delay.
- Ex: If all three inputs fall simultaneously



$$t_{cdr} = [(9 + 5h)C] \left(\frac{R}{3} \right) = \left(3 + \frac{5}{3}h \right) RC$$

Diffusion Capacitance

 - We assumed contacted diffusion on every source / drain.
- Good layout minimizes diffusion area
- Ex: NAND3 layout shares one diffusion contact
 - Reduces output capacitance by $2C$
 - Merged uncontacted diffusion might help too



Layout Comparison

- Which layout is better?

