

EEE DEPT
THE UNIVERSITY OF TEXAS

EE 306


SHT 1 OF 7

Supplemental Note
Sept. 27, 2006


On Monday, I designed for you a combinational (or, rather sequential) lock, complete with Master-Slave flip-flops. This is a tough concept, one worth repeating. So, in these notes, I will try to carefully take you through the design of another sequential circuit, again complete with Master-Slave Flip-flops.

First, a statement of the problem: Design a controller for a warning sign that operates as follows when the input switch is in the ON position.

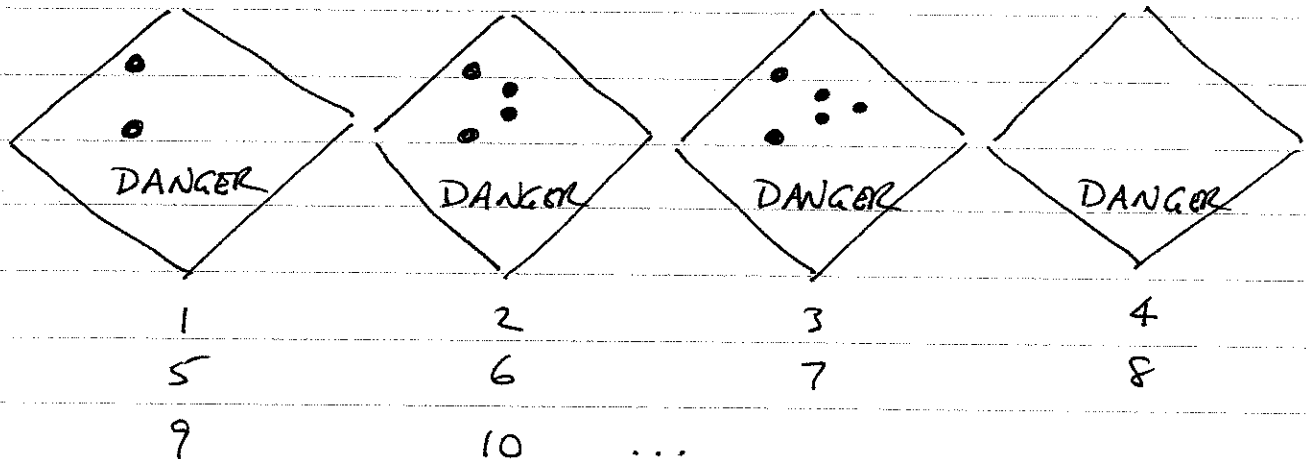That is, with the Switch ON, the goal is to have the lights flash as shown below: 1st two ON, then four, then all five (completing the "arrow"), then all off, then two, etc. With the Switch OFF, all lights remain OFF.



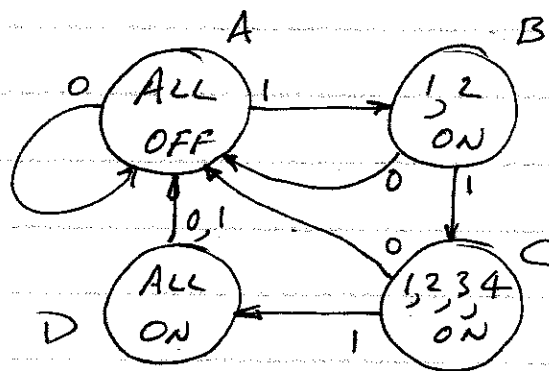We can represent the behavior of our controller with a finite state machine, thus:



Note there are four states, which we label for convenience A, B, C, D.


Note there is one input (the Switch). When ON, we cycle through the states. When OFF, we ^{go to and} remain in State A.

Note that we associate the outputs with the States ONLY

We can also represent the finite state machine as a State Table, and assign a unique code to each state:

$s_1 s_0$		SW OFF	SW ON	1, 2	3, 4	5
(00) A	A	A	B	0	0	0
(01) B	A	A	C	1	0	0
(10) C	A	A	D	1	1	0
(11) D	A	A	A	1	1	1

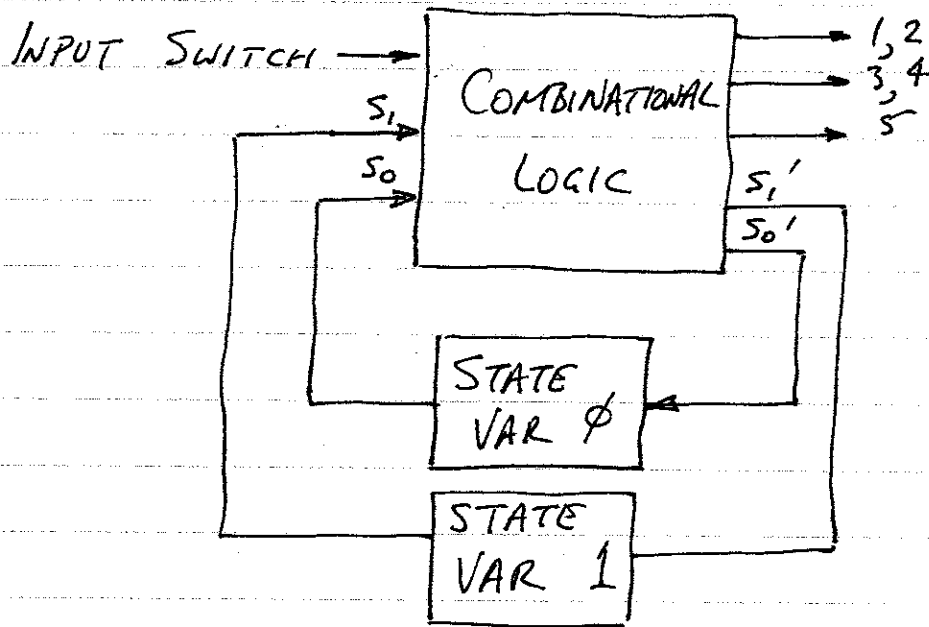Our job is to design the logic to implement this state table. First an overall block diagram




WE HAVE THREE TASKS:

- COMBINATIONAL LOGIC FOR THE LIGHTS
- COMBINATIONAL LOGIC FOR THE "NEXT STATE"
- DESIGN OF THE FLIP-FLOPS

THE OUTPUT LIGHTS:


	STATE	1,2	3,4	5
A	00	0	0	0
B	01	1	0	0
C	10	1	1	0
D	11	1	1	1

 





NEXT STATE
FUNCTION:

S_w	s_1, s_0 STATE	s_1', s_0' NEXT STATE
0	00	00
0	01	00
0	10	00
0	11	00
1	00	01
1	01	10
1	10	11
1	11	00

COMBINATIONAL
LOGIC

 

THE MASTER-SLAVE FLIP-FLOP

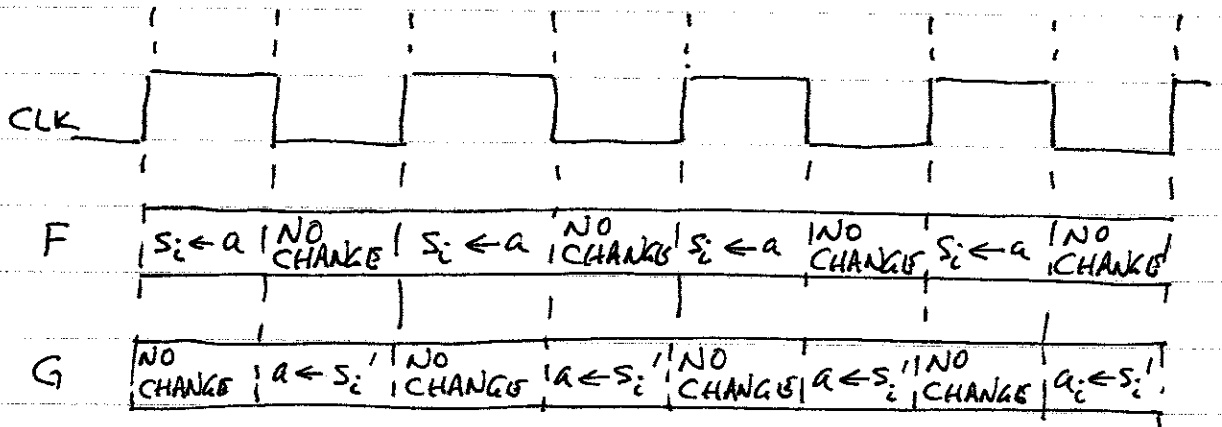   

EXAMPLE: WE START IN CYCLE 1 IN STATE A (0,0) WITH THE SWITCH ON.

CYCLE 1

F_{s1}	0	
G_{s1}		
$F_{s\phi}$	0	
$G_{s\phi}$		

IN THE FIRST HALF OF CYCLE 1, CLK PREVENTS G_i FROM LATCHING $S_i\'$

IN THE SECOND HALF OF CYCLE 1, $\overline{CLK} = 1$, SO S_i' CAN BE LATCHED IN G_i . BUT, SINCE $CLK = \phi$, THE OUTPUT OF G_i (WHICH IS a_i) CAN NOT BE LATCHED IN F_i . THE RESULT:

	CYCLE 1	
F_{s1}	0	0
G_{s1}		0
F_{s0}	0	0
G_{s0}		1


AT THE START OF CYCLE 2, $CLK = 1$, SO F_i CAN LATCH a_i (THE OUTPUT OF G_i). SINCE $\overline{CLK} = 0$, THE SUBSEQUENT GENERATION OF THE NEW S_i' CAN NOT BE LATCHED IN G_i . THE RESULT

	CYCLE 1		CYCLE 2	
F_{s1}	0	0	0	0
G_{s1}		0	0	0
F_{s0}	0	0	1	1
G_{s0}		1	1	1

IN THE SECOND HALF OF CYCLE 2, $\overline{CLK} = 1$, SO THE NEXT S_i' CAN BE LATCHED IN G_i . BUT SINCE $CLK = \phi$, THE OUTPUT OF G_i CAN NOT BE LATCHED IN F_i .

	CYCLE 1		CYCLE 2	
F_{s1}	0	0	0	0
G_{s1}		0	0	1
F_{s0}	0	0	1	1
G_{s0}		1	1	0

 WE CAN CONTINUE ON, TO CYCLE 3, THEN CYCLE 4, ETC. THE RESULT



STATE: 00 01 10 11 00

F_{S1}, F_{S0} SPECIFY THE STATE

G_{S1}, G_{S0} LATCH THE NEXT STATE IN THE SECOND HALF OF EACH CYCLE.