

Physical Memory

1. Overview

- A type of Storage (locations contain data)
- Access methods (Sequential, DASD, RAM, CAM)
- Address Space (How many locations)
- Addressability (How many bits at each location)
 - A datum may require multiple locations (Endianness)

2. DRAM vs SRAM cells

3. ~~The DRAM Chip~~ A ^{Simplified} ~~Single~~ DRAM chip

4. Alignment (Who gets the cushy job) - Hardware or Software

5. Interleaving (old days: latency, ^(PAGE MODE) today: multiple concurrent)

6. Error ^{Detect} Correction (Parity, ECC, ~~Bit~~ ~~error~~ checksum)

7. Memory Controller - What it is, how it works

8. A ~~Memory Controller~~ DRAM ~~chip~~ system


Channel / Rank / Row / Column / Bank / Bus

The chip


9. Other

- SDRAM
- RAMBUS
- Flash

DRAM cell

 


SRAM cell

 

| <u>Tradeoffs</u> | <u>SRAM</u> | <u>DRAM</u> |
|------------------|-------------|-------------|
| Speed | fast | slow |
| Density | low | high |
| Static | Yes | No |
| Refresh | No | Yes |
| Volatil | Yes | Yes. |

Simplified DRAM chip

 


A SIMPLE EXAMPLE
TO ILLUSTRATE
UNALIGNED ACCESS

UN-ALIGNED ACCESS ①
(NON-INTERLEAVED)

Mem 3

- * EIGHT CHIPS
 - * EACH CHIP STORES 8 BYTES
- THAT IS 64 BYTES OF MEMORY

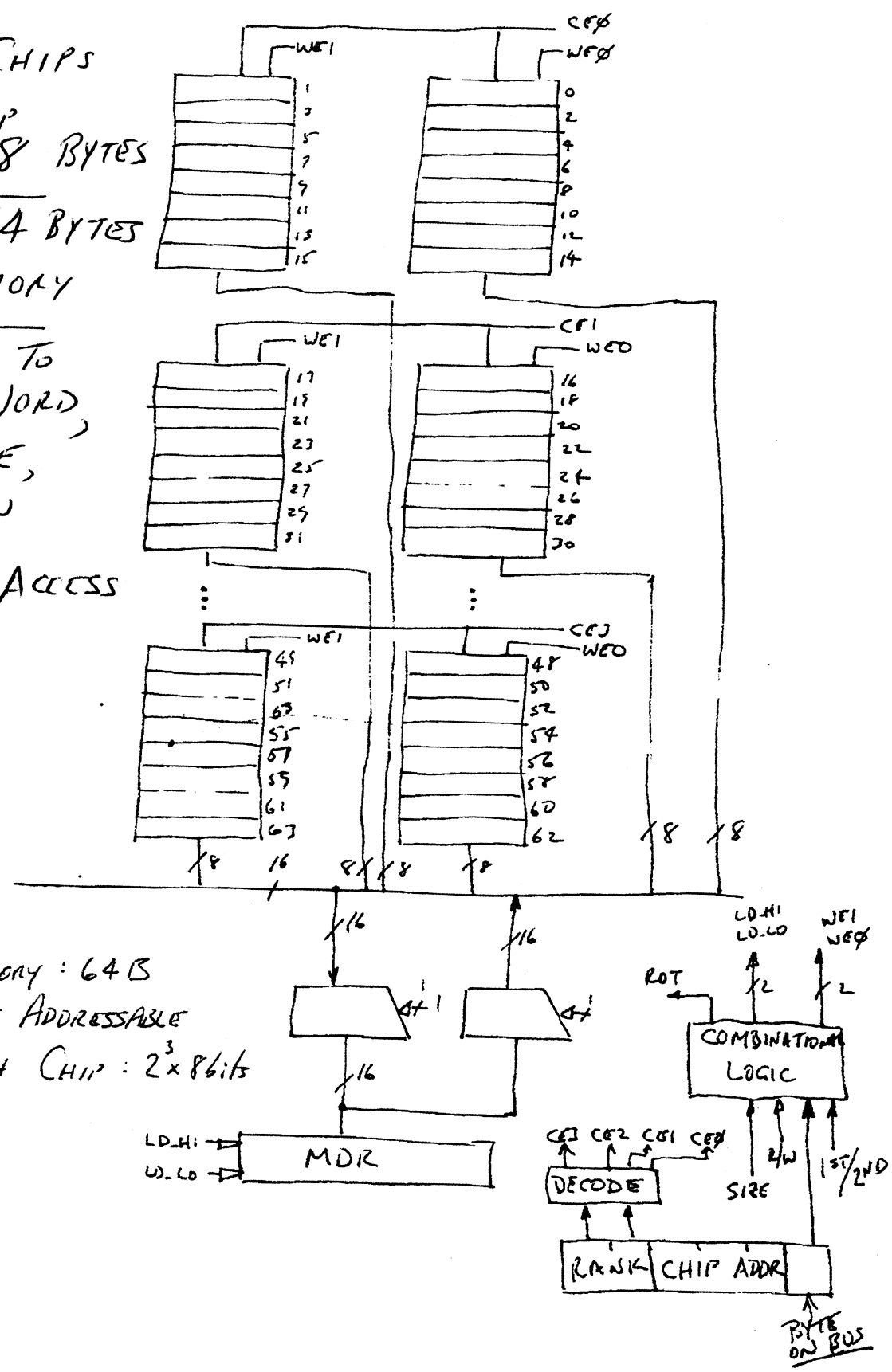WE WANT TO DO BYTE/WORD, LOAD/STORE, AND ALLOW UNALIGNED ACCESS




Memory : 64 B
 BYTES ADDRESSABLE
 EACH CHIP : $2^3 \times 8 \text{ bits}$

UN-ALIGNED ACCESS (2)

Min/4


| R/W | SIZE | MAR[0] | 1 st / ₂ nd | SEN | LDH | LDL | ROT | WE1 | WE0 |
|-----|------|--------|--|-----|-----|-----|-----|-----|-----|
| R | B | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| R | B | 0 | 2 | X | 0 | 0 | X | 0 | 0 |
| R | B | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 |
| R | B | 1 | 2 | X | 0 | 0 | X | 0 | 0 |
| R | W | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 |
| R | W | 0 | 2 | X | 0 | 0 | X | 0 | 0 |
| R | W | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |
| R | W | 1 | 2 | 0 | 1 | 0 | 1 | 0 | 0 |
| W | B | 0 | 1 | X | 0 | 0 | 0 | 0 | 1 |
| W | B | 0 | 2 | X | 0 | 0 | X | 0 | 0 |
| W | B | 1 | 1 | X | 0 | 0 | 1 | 1 | 0 |
| W | B | 1 | 2 | X | 0 | 0 | X | 0 | 0 |
| W | W | 0 | 1 | X | 0 | 0 | 0 | 1 | 1 |
| W | W | 0 | 2 | X | 0 | 0 | X | 0 | 0 |
| W | W | 1 | 1 | X | 0 | 0 | 1 | 1 | 0 |
| W | W | 1 | 2 | X | 0 | 0 | 1 | 0 | 1 |

 

CONTROL SIGNALS
NEED TO IMPLEMENT
UNALIGNED LD/ST
BYTE/WORD

SEN: SIGN-EXTEND
WE1, WE0: WRITE
ENABLE

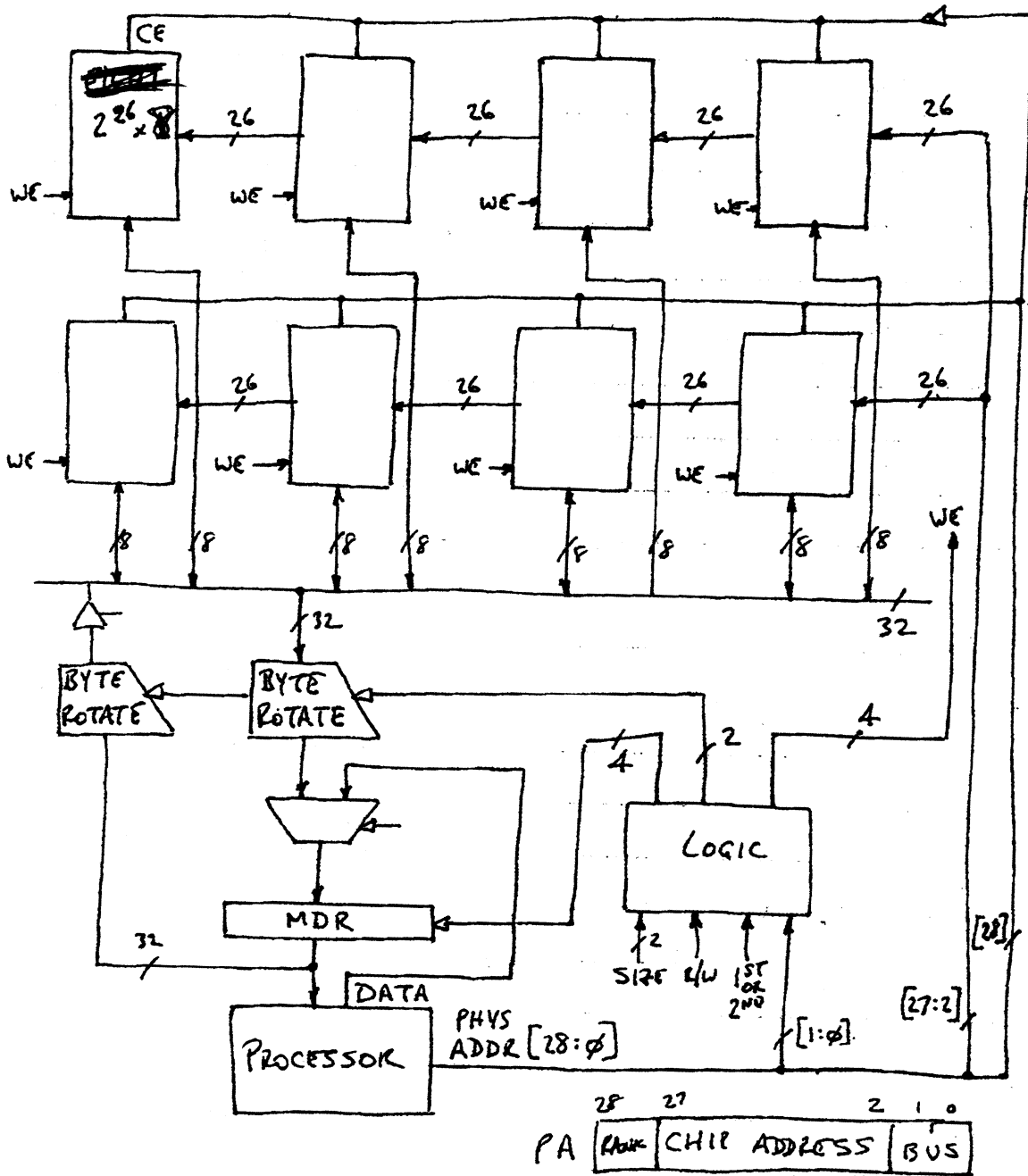EXTEND UNALIGNED TO 2^{27} BYTE-ADDRESSABLE MEMORY
 STILL NO INTERLEAVED
 BUS WIDTH: 32 bits Mem/5




UNALIGNED ACCESSES
 (SIMPLIFIED BLOCK DIAGRAM)


A SIMPLE ILLUSTRATION OF INTERLEAVING

INTERLEAVING (SHT 1)




Mem/6

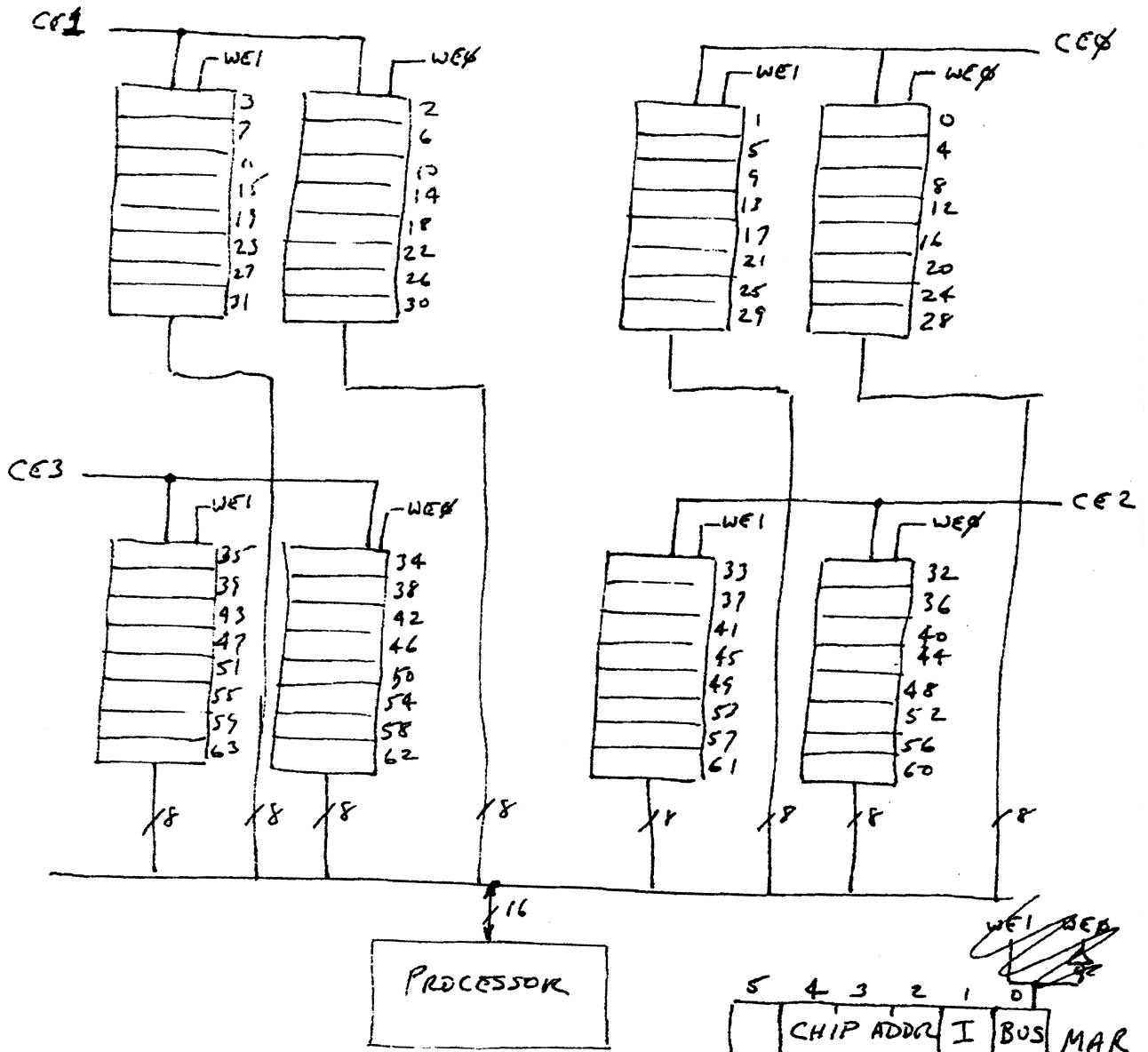

 64 BYTES OF MEMORY
 EACH CHIP: $2^3 \times 8$ bits
 BYTE-ADDRESSABLE MEMORY
 16 BIT BUS
 TWO-WAY INTERLEAVED




INTERLEAVING (SHT 2)

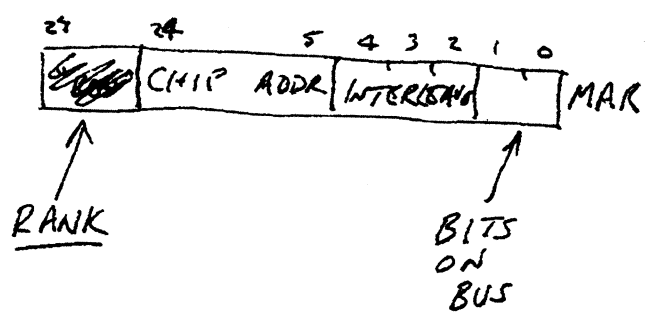  

A 1 GB DRAM SYSTEM

* FIRST, THE DRAM STRUCTURE

 

- THE DRAM ARRAY STORES 2^{24} BYTES OF INFORMATION
i.e. A 16 MB ARRAY

- IF THE "NEXT" ACCESS IS TO THE SAME ROW
AS THE PREVIOUS ACCESS, WE GET A ROW BUFFER
HIT

ERGO, NO NEED TO TRANSFER ROW ADDR AGAIN.
FASTER. CALLED PAGE MODE

* THE DRAM CHIP

- THE DRAM CHIP CONSISTS OF 8 OF THESE
DRAM STRUCTURES, EACH WITH ITS OWN
ROW ADDR REG., COL. ADDR REG., ROW BUFFER.


Mon/9

1 GB DRAM (CONTINUED)

* THE DRAM CHIP (CONTINUED)


- THIS ALLOWS INTERLEAVING THE 8 ARRAYS ON THE CHIP INTO 8-WAY INTERLEAVED MEMORY
- TOTAL STORAGE ON THE CHIP: $8 \times 16 \text{ MB}$
(SILLY MARKETING CALLS IT 1 Gbit)
I PREFER 128 MB SINCE WE HAVE 2^{27} ADDRESSES, EACH OF WHICH STORES ONE BYTE

 * A TYPICAL SYSTEM CONTAINS A MODULE CONSISTING OF 8 DRAM CHIPS, AS FOLLOWS



- THIS PROVIDES FOR A 64-bit ~~MEM~~ WIDE TRANSFER BETWEEN THE PROCESSOR AND MEMORY
- ADDRESSES TO THE SAME BANK IN ALL CHIPS ARE IDENTICAL

ONE EXAMPLE OF

 

To Deal with Errors in Transmission

I also got email asking if I would include in the handout "Check Sum" or "CRC." So, sure.

① Simplest form. A single parity bit.


$$P = D_n \oplus D_{n-1} \oplus D_{n-2} \oplus \dots \oplus D_1$$

- * We transmit $n+1$ bits - n Data + 1 Parity.
- * We can detect if exactly one bit transmitted in error. (What happens if two errors).
- * Assumes: Each bit is statistically independent with respect to all the others, i.e. transmitting in error.

② ECC. Hamming Code. When detecting is not enough. We want to be able correct, so we need a code that allows us to identify the "bad bit." (The next two pages provide the detail I promised,

③ Check sum or CRC. - Cyclic Redundancy Check.

 - * When the probability of error of the bits are not independent.
- * When you may get a short sequence clobbered.
- * Original scheme was to use a Shift register, thus:



* Large no. of bits would come in and leave bit serial. BUT, they would be XOR'ed with selected older bits in the bit stream. After the last bit comes in you still have k bits as output to the shift register. These last bits referred to as CHECK SUM

ECC

Men/11

A little research uncovered a still better scheme, still due to Richard Hamming, and still based on XOR (or, parity functions).

Suppose we wish to transmit n bits. We can correct single errors by adding $\log_2 n + 1$ bits as follows:

Simplest way to show is by means of an example.

Let $n=8$. Then we need $\log_2 8 + 1 = 4$ parity bits.

12 bits altogether. We lay out the bits as follows

| | | | | | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 12 | 11 | 10 | 9 | 8 | 7 | 6 | 5 | 4 | 3 | 2 | 1 |
| D_7 | D_6 | D_5 | D_4 | P_8 | D_3 | D_2 | D_1 | P_4 | D_0 | P_2 | P_1 |

Note the "bit number" of each bit

| | |
|-----------------|-------|
| 1100 | D_7 |
| 1011 | D_6 |
| 1010 | D_5 |
| 1001 | D_4 |
| 1000 | P_8 |
| 0110 | D_3 |
| 0110 | D_2 |
| 0101 | D_1 |
| 0100 | P_4 |
| 0011 | D_0 |
| 0010 | P_2 |
| 0001 | P_1 |
| 0000 | |

We form a parity function of all bits having a 1 in the corresponding position of ~~each~~ the bit numbers.

$$\therefore P_8 = D_7 \oplus D_6 \oplus D_5 \oplus D_4$$

$$P_4 = D_7 \oplus D_3 \oplus D_2 \oplus D_1$$

$$P_2 = D_6 \oplus D_5 \oplus D_3 \oplus D_2 \oplus D_0$$

$$P_1 = D_6 \oplus D_4 \oplus D_3 \oplus D_1 \oplus D_0$$

ECC (Sheet 2)

If we lay out with x the bits provide even parity, we have





| | D_7 | D_6 | D_5 | D_4 | P_8 | D_3 | D_2 | D_1 | P_4 | D_0 | P_2 | P_1 |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| Row 4 | x | x | x | x | x | | | | | | | |
| Row 3 | x | | | | | x | x | x | x | | | |
| Row 2 | | | x | x | | x | x | | | x | x | |
| Row 1 | | x | | x | | x | | x | | x | | x |

When we receive the 12-bit value, we check the four even-parity functions. If ~~any~~ ^(exactly one) bit was received incorrectly, all rows having an x in that column will give an even-parity error message. Since each of the 12 columns provides a unique set of parity errors, we know immediately which bit was transmitted in error.

For example, suppose D_2 is the culprit. We would get odd-parity for row 2 and row 3. D_2 is the only bit that ~~bits~~ would give odd parity for only rows 2, 3 if it were transmitted in error.

A nice by-product is that if you examine parity for the four rows (0 = even, 1 = odd), the results tell you if no error occurred 0000, or gives you the "bit number" of the error bit. In the case of D_2 : 0110 which is the "bit number" of D_2 in the 12 bit transmission

8. DRAM Syst

 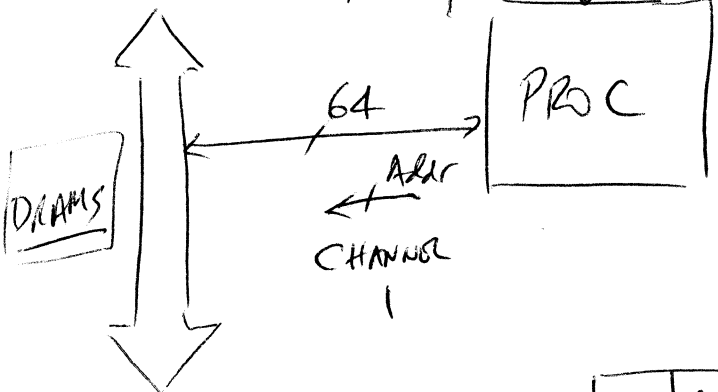  

DDR-4 Chip
 40 bits = 512 MB
 16 BANKS → 32 MB/BANK
 ↑
 25 bits of Addr
 15 Row
 10 Col.
 Row buffer (1 KB)