

VHDL = VHSIC Hardware Description Language

VHSIC = Very High Speed Integrated Circuit


Hardware description, simulation, and synthesis

**Describes hardware at different levels:
behavioral, logic equation, structural**

Top-down design methodology

Technology Independent

Figure 2-1 Gate Network

 

Concurrent Statements

```
C <= A and B after 5 ns;  
E <= C or D after 5 ns;
```

If delay is not specified, “delta” delay is assumed

```
C <= A and B;  
E <= C or D;
```

Order of concurrent statements is not important

```
E <= C or D;  
C <= A and B;
```


This statement executes repeatedly

```
CLK <= not CLK after 10 ns;
```

This statement causes a simulation error

```
CLK <= not CLK;
```

From Page 45-46

 

entity FullAdder **is**

port (X, Y, Cin: **in** bit; -- Inputs
Cout, Sum: **out** bit); -- Outputs

end FullAdder;

architecture Equations **of** FullAdder **is**


begin -- Concurrent Assignments

Sum <= X **xor** Y **xor** Cin **after** 10 ns;

Cout <= (X **and** Y) **or** (X **and** Cin) **or** (Y **and** Cin) **after** 10 ns;

end Equations;

Figure 2-2 VHDL Program Structure

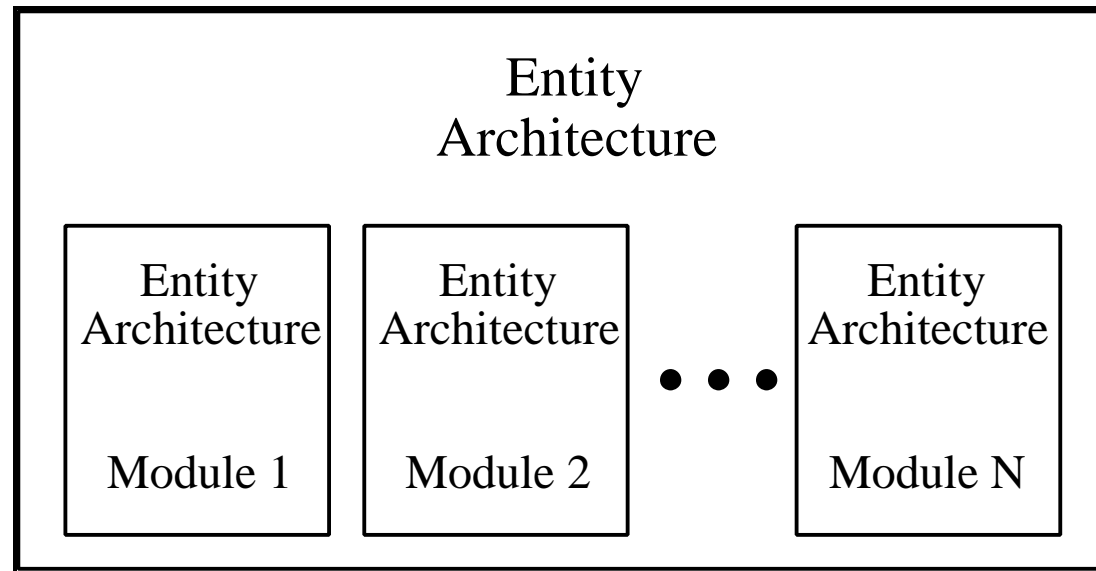

```
entity entity-name is  
  [port(interface-signal-declaration);]  
end [entity] [entity-name];
```

```
architecture architecture-name of entity-name is  
  [declarations]  
begin  
  architecture body  
end [architecture] [architecture-name];
```

Figure 2-3 4-bit Binary Adder

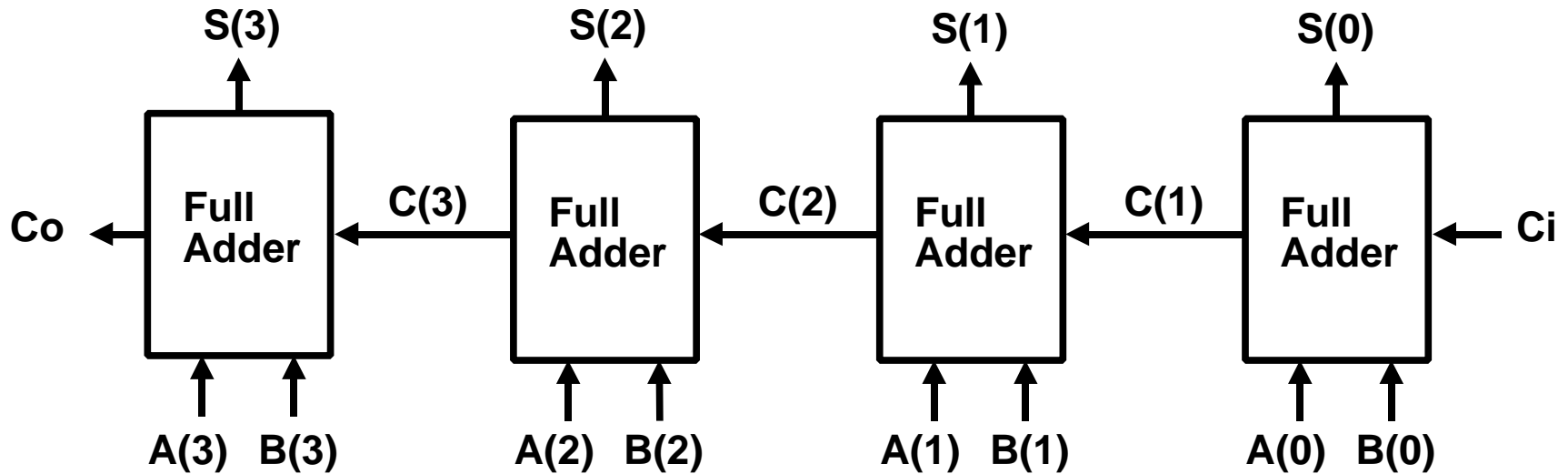


Figure 2-4(i) Structural Description of 4-bit Adder

entity Adder4 is

```
port (A, B: in bit_vector(3 downto 0); Ci: in bit;           -- Inputs  
      S: out bit_vector(3 downto 0); Co: out bit);          -- Outputs
```

Figure 2-3 4-bit Binary Adder

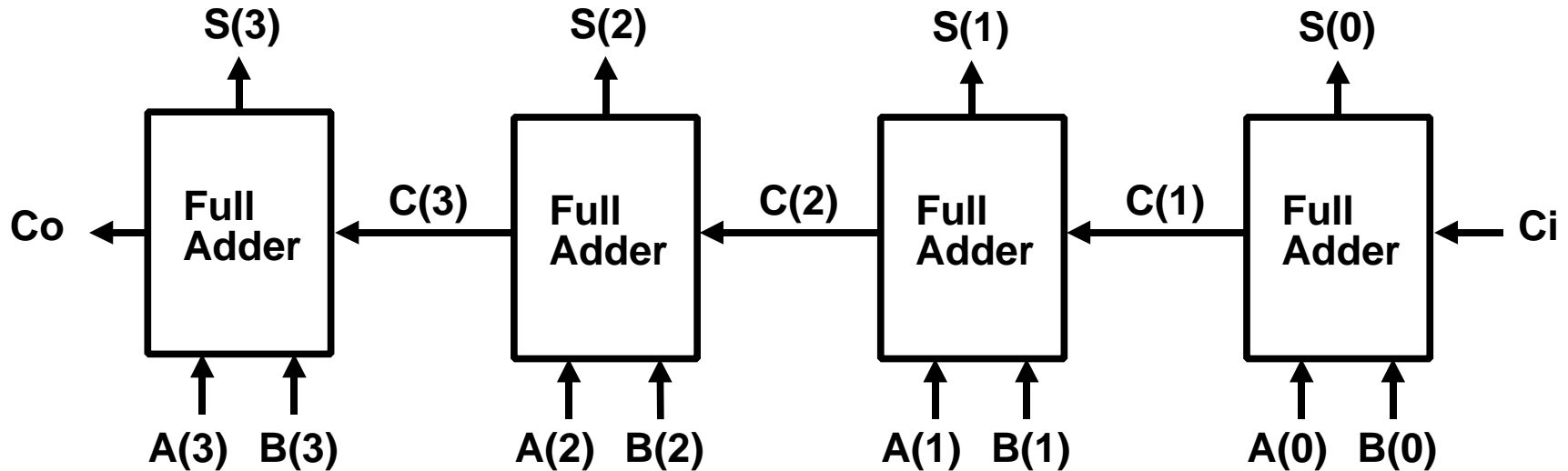


Figure 2-4(ii) Structural Description of 4-bit Adder

architecture Structure of Adder4 is

component FullAdder

port (X, Y, Cin: **in** bit; -- Inputs
 Cout, Sum: **out** bit); -- Outputs

end component;

signal C: bit_vector(3 **downto** 1);

begin --instantiate four copies of the FullAdder

FA0: FullAdder **port map** (A(0), B(0), Ci, C(1), S(0));

FA1: FullAdder **port map** (A(1), B(1), C(1), C(2), S(1));

FA2: FullAdder **port map** (A(2), B(2), C(2), C(3), S(2));

FA3: FullAdder **port map** (A(3), B(3), C(3), Co, S(3));

end Structure;

From Page 49

```
list A B Co C Ci S  -- put these signals on the output list
force A 1111        -- set the A inputs to 1111
force B 0001        -- set the B inputs to 0001
force Ci 1          -- set the Ci to 1
run 50              -- run the simulation for 50 ns
force Ci 0
force A 0101
force B 1110
run 50
```

ns	delta	a	b	co	c	ci	s
0	+0	0000	0000	0	000	0	0000
0	+1	1111	0001	0	000	1	0000
10	+0	1111	0001	0	001	1	1111
20	+0	1111	0001	0	011	1	1101
30	+0	1111	0001	0	111	1	1001
40	+0	1111	0001	1	111	1	0001
50	+0	0101	1110	1	111	0	0001
60	+0	0101	1110	1	110	0	0101
70	+0	0101	1110	1	100	0	0111
80	+0	0101	1110	1	100	0	0011

VHDL Processes

General form of Process

```
process(sensitivity-list)
begin
    sequential-statements
end process;
```

Process example

```
process (B, C, D)
begin
    A <= B; -- statement 1
    B <= C; -- statement 2
    C <= D; -- statement 3
end process;
```

Simulation results

time	delta	A	B	C	D	
0	+0	1	2	3	0	
10	+0	1	2	3	4	(statements 1,2,3 execute; then update A,B,C)
10	+1	2	3	4	4	(statements 1,2,3 execute; then update A,B,C)
10	+2	3	4	4	4	(statements 1,2,3 execute; then update A,B,C)
10	+3	4	4	4	4	(no further execution occurs)


Concurrent Statements

```
A <= B; -- statement 1
B <= C; -- statement 2
C <= D; -- statement 3
```

Simulation Results

time	Δ	A	B	C	D	
0	+0	1	2	3	0	
10	+0	1	2	3	4	(statement 3 executes first)
10	+1	1	2	4	4	(then statement 2 executes)
10	+2	1	4	4	4	(then statement 1 executes)
10	+3	4	4	4	4	(no further execution occurs)

Figure 2-5 D Flip-flop Model

 

```
entity DFF is  
  port (D, CLK: in bit;  
         Q: out bit; QN: out bit := '1');  
  -- initialize QN to '1' since bit signals are initialized to '0' by default  
end DFF;
```

```
architecture SIMPLE of DFF is  
begin  
  process (CLK)                -- process is executed when CLK changes  
  begin  
    if CLK = '1' then          -- rising edge of clock  
      Q <= D after 10 ns;  
      QN <= not D after 10 ns;  
    end if;  
  end process;  
end SIMPLE;
```

Figure 2-7 J-K Flip-flop Model


```
entity JKFF is
  port (SN, RN, J, K, CLK: in bit;
        Q: inout bit; QN: out bit := '1');
end JKFF;
```

-- inputs
-- see Note 1

```
architecture JKFF1 of JKFF is
begin
```

```
  process (SN, RN, CLK)
  begin
    if RN = '0' then Q <= '0' after 10 ns;
    elsif SN = '0' then Q <= '1' after 10 ns;
    elsif CLK = '0' and CLK'event then
      Q <= (J and not Q) or (not K and Q) after 10 ns;
    end if;
  end process;
  QN <= not Q;
end JKFF1;
```

-- see Note 2
-- see Note 3
-- see Note 4
-- see Note 5

 

Note 1: Q is declared as inout (rather than out) because it appears on both the left and right sides of an assignment within the architecture.


Note 2: The flip-flop can change state in response to changes in SN, RN, and CLK, so these 3 signals are in the sensitivity list.

Note 3: The condition (CLK = '0' and CLK'event) is TRUE only if CLK has just changed from '1' to '0'.

Note 4: Characteristic equation which describes behavior of J-K flip-flop.

Note 5: Every time Q changes, QN will be updated. If this statement were placed within the process, the old value of Q would be used instead of the new value.


Figure 2-8 Equivalent Representations of a Flowchart Using Nested Ifs and Elsifs

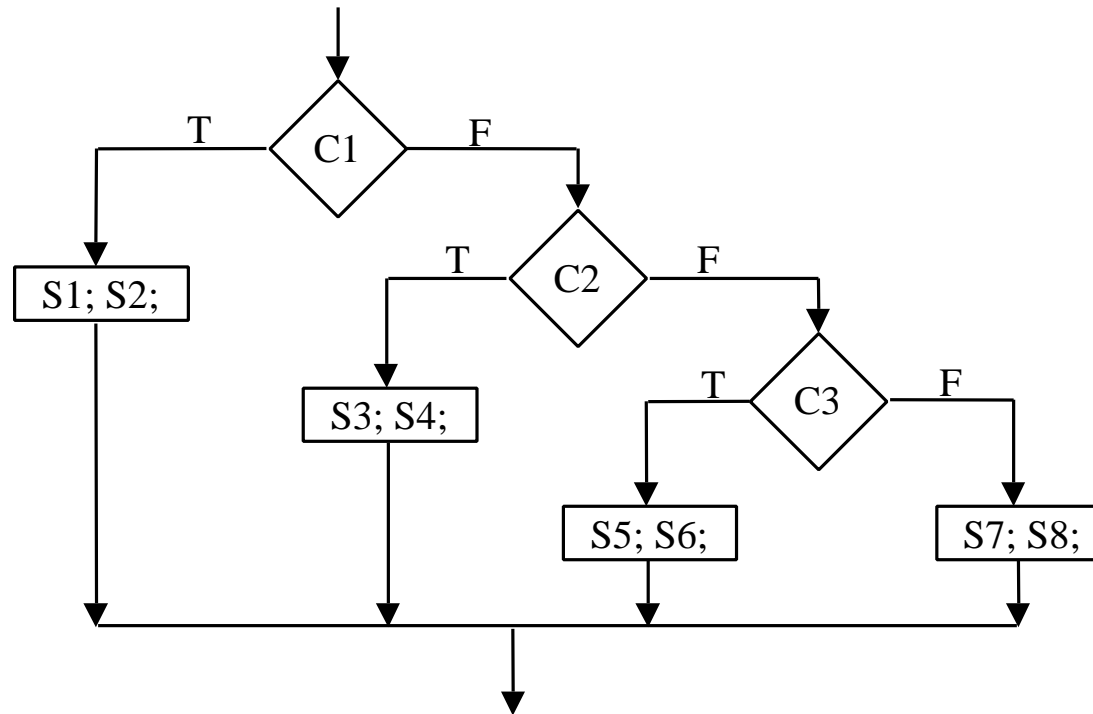

```
if (C1) then S1; S2;  
  else if (C2) then S3; S4;  
    else if (C3) then S5; S6;  
      else S7; S8;  
    end if;  
  end if;  
end if;
```

```
if (C1) then S1; S2;  
  elsif (C2) then S3; S4;  
  elsif (C3) then S5; S6;  
  else S7; S8;  
end if;
```

Figure 2-9 4-to-1 Multiplexer

 

$$F \leq (\text{not } A \text{ and not } B \text{ and } I_0) \text{ or} \\ (\text{not } A \text{ and } B \text{ and } I_1) \text{ or} \\ (A \text{ and not } B \text{ and } I_2) \text{ or} \\ (A \text{ and } B \text{ and } I_3);$$

MUX model using a *conditional signal assignment statement*:

```
F <= I0 when Sel = 0
     else I1 when Sel = 1
     else I2 when Sel = 2
     else I3;
```

In the above concurrent statement, Sel represents the integer equivalent of a 2-bit binary number with bits A and B.

General form of conditional signal assignment statement:

```
signal_name <= expression1 when condition1
             else expression2 when condition2
             ...
             [else expressionN];
```

Multiplexer Example From Page 55

If a MUX model is used inside a process, a concurrent statement cannot be used. As an alternative, the MUX can be modeled using a **case statement**:

```
case Sel is  
    when 0 => F <= I0;  
    when 1 => F <= I1;  
    when 2 => F <= I2;  
    when 3 => F <= I3;  
end case;
```

The case statement has the general form:

```
case expression is  
    when choice1 => sequential statements1  
    when choice2 => sequential statements2  
    . . .  
    [when others => sequential statements]  
end case;
```

Figure 2-10 Compilation, Elaboration, and Simulation of VHDL Code

 


Figure 2-11 VHDL Code for Simulation Example

```
entity simulation_example is  
end simulation_example;  
  
architecture test1 of simulation_example is  
    signal A,B: bit;  
begin  
    P1: process(B)  
        begin  
            A <= '1';  
            A <= transport '0' after 5 ns;  
        end process P1;  
  
    P2: process(A)  
        begin  
            if A = '1' then B <= not B after 10 ns; end if;  
        end process P2;  
end test1;
```

Figure 2-12 Signal Drivers for Simulation Example

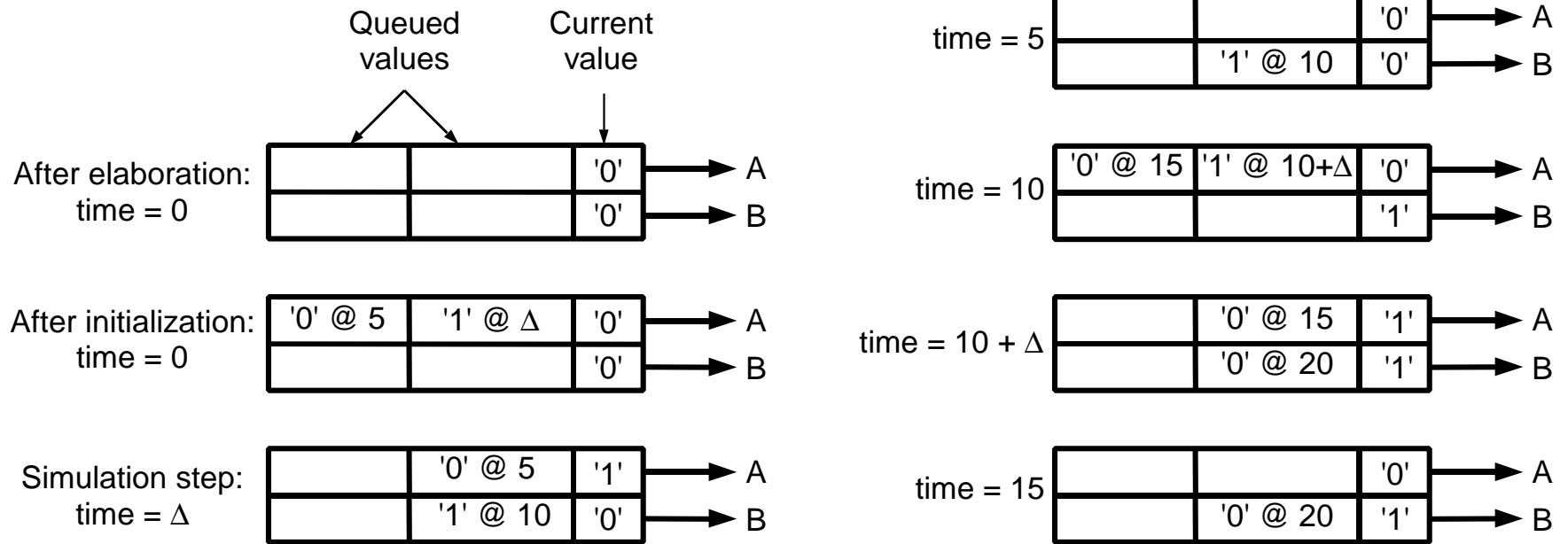


Figure 2-13(a) Behavioral Model for Figure 1-17

```

entity SM1_2 is
  port(X, CLK: in bit; Z: out bit);
end SM1_2;

architecture Table of SM1_2 is
  signal State, Nextstate: integer := 0;
begin
  process(State,X)                                --Combinational Network
  begin
  case State is
    when 0 =>
      if X='0' then Z<='1'; Nextstate<=1; end if;
      if X='1' then Z<='0'; Nextstate<=2; end if;
    when 1 =>
      if X='0' then Z<='1'; Nextstate<=3; end if;
      if X='1' then Z<='0'; Nextstate<=4; end if;
    when 2 =>
      if X='0' then Z<='0'; Nextstate<=4; end if;
      if X='1' then Z<='1'; Nextstate<=4; end if;
    when 3 =>
      if X='0' then Z<='0'; Nextstate<=5; end if;
      if X='1' then Z<='1'; Nextstate<=5; end if;
    when 4 =>
      if X='0' then Z<='1'; Nextstate<=5; end if;
      if X='1' then Z<='0'; Nextstate<=6; end if;
  
```

PS	NS		Z	
	X = 0	X = 1	X = 0	X = 1
S0	S1	S2	1	0
S1	S3	S4	1	0
S2	S4	S4	0	1
S3	S5	S5	0	1
S4	S5	S6	1	0
S5	S0	S0	0	1
S6	S0	—	1	—

Figure 2-13(b) Behavioral model for Figure 1-17

```
when 5 =>
  if X='0' then Z<='0'; Nextstate<=0; end if;
  if X='1' then Z<='1'; Nextstate<=0; end if;
when 6 =>
  if X='0' then Z<='1'; Nextstate<=0; end if;
  when others => null;           -- should not occur
end case;
end process;

process(CLK)                    -- State Register
  begin
    if CLK='1' then           -- rising edge of clock
      State <= Nextstate;
    end if;
  end process;
end Table;
```

A simulator command file that can be used to test Figure 2-13 is as follows:

```
wave CLK X State NextState Z
force CLK 0 0, 1 100 -repeat 200
force X 0 0, 1 350, 0 550, 1 750, 0 950, 1 1350
run 1600
```

Execution of the preceding command file produces the waveforms shown in Figure 2-14.

Figure 2-14 Waveforms for Figure 2-13

 


Figure 2-15 Sequential Machine Model Using Equations

-- The following is a description of the sequential machine of
-- Figure 1-17 in terms of its next state equations.
-- The following state assignment was used:
-- S0-->0; S1-->4; S2-->5; S3-->7; S4-->6; S5-->3; S6-->2

```
entity SM1_2 is  
  port(X,CLK: in bit;  
        Z: out bit);  
end SM1_2;
```

```
architecture Equations1_4 of SM1_2 is  
  signal Q1,Q2,Q3: bit;  
begin  
  process(CLK)  
  begin  
    if CLK='1' then           -- rising edge of clock  
      Q1<=not Q2 after 10 ns;  
      Q2<=Q1 after 10 ns;  
      Q3<=(Q1 and Q2 and Q3) or (not X and Q1 and not Q3) or  
        (X and not Q1 and not Q2) after 10 ns;  
    end if;  
  end process;  
  Z<=(not X and not Q3) or (X and Q3) after 20 ns;  
end Equations1_4;
```

Figure 2-16 Structural Model of Sequential Machine

-- The following is a STRUCTURAL VHDL description of the network of Figure 1-20.

```
library BITLIB;
use BITLIB.bit_pack.all;

entity SM1_2 is
  port(X,CLK: in bit;
        Z: out bit);
end SM1_2;

architecture Structure of SM1_2 is
  signal A1,A2,A3,A5,A6,D3: bit:= '0';
  signal Q1,Q2,Q3: bit:= '0';
  signal Q1N,Q2N,Q3N, XN: bit:= '1';
begin
  I1: Inverter port map (X,XN);
  G1: Nand3 port map (Q1,Q2,Q3,A1);
  G2: Nand3 port map (Q1,Q3N,XN,A2);
  G3: Nand3 port map (X,Q1N,Q2N,A3);
  G4: Nand3 port map (A1,A2,A3,D3);
  FF1: DFF port map (Q2N,CLK,Q1,Q1N);
  FF2: DFF port map (Q1,CLK,Q2,Q2N);
  FF3: DFF port map (D3,CLK,Q3,Q3N);
  G5: Nand2 port map (X,Q3,A5);
  G6: Nand2 port map (XN,Q3N,A6);
  G7: Nand2 port map (A5,A6,Z);
end Structure
```

Executing the simulator command file given below produces the waveforms of Figure 2-17.

```
wave CLK X Q1 Q2 Q3 Z
force CLK 0 0, 1 100 -repeat 200
force X 0 0, 1 350, 0 550, 1 750, 0 950, 1 1350
run 1600
```

Figure 2-17 Waveforms for Figure 2-16

 


Figure 2-18(a) Behavioral Model for Figure 1-17 Using a Single Process

```
library BITLIB;
use BITLIB.Bit_pack.all;
entity SM1_2 is port(X, CLK: in bit; Z: out bit); end SM1_2;
architecture Table of SM1_2 is signal State, Nextstate: integer := 0;
begin
    process
    begin
    case State is
        when 0 =>
            if X='0' then Z<='1'; Nextstate<=1; end if;
            if X='1' then Z<='0'; Nextstate<=2; end if;
        when 1 =>
            if X='0' then Z<='1'; Nextstate<=3; end if;
            if X='1' then Z<='0'; Nextstate<=4; end if;
        when 2 =>
            if X='0' then Z<='0'; Nextstate<=4; end if;
            if X='1' then Z<='1'; Nextstate<=4; end if;
        when 3 =>
            if X='0' then Z<='0'; Nextstate<=5; end if;
            if X='1' then Z<='1'; Nextstate<=5; end if;
        when 4 =>
            if X='0' then Z<='1'; Nextstate<=5; end if;
            if X='1' then Z<='0'; Nextstate<=6; end if;
        when 5 =>
            if X='0' then Z<='0'; Nextstate<=0; end if;
            if X='1' then Z<='1'; Nextstate<=0; end if;
    
```

Figure 2-18(b) Behavioral Model for Figure 1-17 Using a Single Process

```
    when 6 =>
        if X='0' then Z<='1'; Nextstate<=0; end if;
        when others => null;          -- should not occur
    end case;

    wait on CLK, X;
    if rising_edge(CLK) then          -- rising_edge function is in BITLIB *
        State <= Nextstate;
        wait for 0 ns;                -- wait for State to be updated
    end if;
    end process;
end table;
```

* Alternative:

```
if CLK'event and CLK = '1' then
```


Figure 2-19 Process Using Variables

```
entity dummy is  
end dummy;
```

```
architecture var of dummy is
```

```
    signal trigger, sum: integer:=0;
```

```
begin
```

```
    process
```

```
        variable var1: integer:=1;
```

```
        variable var2: integer:=2;
```

```
        variable var3: integer:=3;
```

```
    begin
```

```
        wait on trigger;
```

```
        var1 := var2 + var3;
```

```
        var2 := var1;
```

```
        var3 := var2;
```

```
        sum <= var1 + var2 + var3;
```

```
    end process;
```

```
end var;
```

var1 = 2 + 3 = 5

var2 = 5

var3 = 5

sum = 5 + 5 + 5 = 15 (after D)

Figure 2-20 Process Using Signals

```
entity dummy is  
end dummy;
```

```
architecture sig of dummy is
```

```
    signal trigger, sum: integer:=0;
```

```
    signal sig1: integer:=1;
```

```
    signal sig2: integer:=2;
```

```
    signal sig3: integer:=3;
```

```
begin
```

```
    process
```

```
    begin
```

```
        wait on trigger;
```

```
        sig1 <= sig2 + sig3;
```

```
        sig2 <= sig1;
```

```
        sig3 <= sig2;
```

```
        sum <= sig1 + sig2 + sig3;
```

```
    end process;
```

```
end sig;
```

sig1 = 2 + 3 = 5 ***(after D)***

sig2 = 1 ***(after D)***

sig3 = 2 ***(after D)***

sum = 1 + 2 + 3 = 6 ***(after D)***

From Page 67

Predefined VHDL types include:

bit	'0' or '1'
boolean	FALSE or TRUE
integer	an integer in the range $-(2^{31}-1)$ to $+(2^{31}-1)$ (some implementations support a wider range)
real	floating-point number in the range $-1.0E38$ to $+1.0E38$
character	any legal VHDL character including upper- and lower-case letters, digits, and special characters; each printable character must be enclosed in single quotes; e.g., 'd','7','+'
time	an integer with units fs, ps, ns, us, ms, sec, min, or hr

Note that the integer range for VHDL is symmetrical even though the range for a 32-bit 2's complement integer is -2^{31} to $+(2^{31} - 1)$.

Example of enumeration type (user-defined):

```
type state_type is (S0, S1, S2, S3, S4, S5);  
signal state : state_type := S1;
```

From Page 68

Example of array type:

```
type SHORT_WORD is array (15 downto 0) of bit;
```

Examples of array objects of type SHORT_WORD

```
signal DATA_WORD: SHORT_WORD;  
variable ALT_WORD: SHORT_WORD := "0101010101010101";  
constant ONE_WORD: SHORT_WORD := (others => '1');
```

General forms of the array type and array object declarations:

```
type array_type_name is array index_range of element_type;  
signal array_name: array_type_name [ := initial_values ];
```

*(signal may be replaced with **variable** or **constant**)*

Two-dimensional array example:

```
type matrix4x3 is array (1 to 4, 1 to 3) of integer;  
variable matrixA: matrix4x3 := ((1, 2, 3), (4, 5, 6), (7, 8, 9), (10, 11, 12));
```

The variable matrixA, will be initialized to:

```
1  2  3  
4  5  6  
7  8  9  
10 11 12
```

From Page 69 – 70

Example of an unconstrained array type:

```
type intvec is array (natural range <>) of integer;  
signal intvec5: intvec(1 to 5) := (3,2,6,8,1);
```

Two-dimensional array type with unconstrained row and column index ranges:

```
type matrix is array (natural range <>, natural range <>) of integer;
```

Predefined unconstrained array types in VHDL include bit-vector and string:

```
type bit_vector is array (natural range <>) of bit;  
type string is array (positive range <>) of character;
```

The following example declares a constant string1 of type string:

```
constant string1: string(1 to 29) := "This string is 29 characters."
```

A bit_vector literal may be written either as a list of bits separated by commas or as a string. For example, ('1','0','1','1','0') and "10110" are equivalent forms.

```
constant A : bit_vector(0 to 5) := "101011";
```

A subtype specifies a subset of the values specified by a type. Example:

```
subtype SHORT_WORD is bit_vector (15 downto 0);
```

Predefined subtypes of type integer: POSITIVE (all positive integers)
NATURAL (all positive integers and 0)

Figure 2-21 Sequential Machine Model Using State Table

```
entity SM1_2 is
  port (X, CLK: in bit;
        Z: out bit);
end SM1_2;

architecture Table of SM1_2 is
  type StateTable is array (integer range <>, bit range <>) of integer;
  type OutTable is array (integer range <>, bit range <>) of bit;
  signal State, NextState: integer := 0;
  constant ST: StateTable (0 to 6, '0' to '1') :=
    ((1,2), (3,4), (4,4), (5,5), (5,6), (0,0), (0,0));
  constant OT: OutTable (0 to 6, '0' to '1') :=
    (('1','0'), ('1','0'), ('0','1'), ('0','1'), ('1','0'), ('0','1'), ('1','0'));
begin
  NextState <= ST(State,X);      -- concurrent statements
  Z <= OT(State, X);            -- read next state from state table
  process(CLK)
  begin
    if CLK = '1' then        -- rising edge of CLK
      State <= NextState;
    end if;
  end process;
end Table;
```

2.8 VHDL Operators

Predefined VHDL operators can be grouped into seven classes:

1. binary logical operators: **and or nand nor xor xnor**
(*lowest* precedence -- applied last)
2. relational operators: = /= < <= > >=
3. shift operators: **sll srl sla sra rol ror**
4. adding operators: + - & (concatenation)
5. unary sign operators: + -
6. multiplying operators: * / **mod rem**
7. miscellaneous operators: **not abs ****
(*highest* precedence -- applied first)

Example of VHDL Operators

In the following expression, A, B, C, and D are bit_vectors:

$(A \ \& \ \mathbf{not} \ B \ \mathbf{or} \ C \ \mathbf{ror} \ 2 \ \mathbf{and} \ D) = "110010"$

The operators would be applied in the order:

not, **&**, **ror**, **or**, **and**, **=**

If A = "110", B = "111", C = "011000", and D = "111011", the computation would proceed as follows:

not B = "000" (bit-by-bit complement)

A & **not** B = "110000" (concatenation)

C **ror** 2 = "000110" (rotate right 2 places)

(A & **not** B) **or** (C **ror** 2) = "110110" (bit-by-bit or)

(A & **not** B **or** C **ror** 2) **and** D = "110010" (bit-by-bit and)

[(A & **not** B **or** C **ror** 2 **and** D) = "110010"] = TRUE

(the parentheses force the equality test to be done last and the result is TRUE)

Example of Shift Operators

The shift operators can be applied to any `bit_vector` or `boolean_vector`. In the following examples, `A` is a `bit_vector` equal to "10010101":

A **sll** 2 is "01010100" (shift left logical, filled with '0')

A **srl** 3 is "00010010" (shift right logical, filled with '0')

A **sla** 3 is "10101111" (shift left arithmetic, filled with right bit)

A **sra** 2 is "11100101" (shift right arithmetic, filled with left bit)

A **rol** 3 is "10101100" (rotate left)

A **ror** 5 is "10101100" (rotate right)

2.9 VHDL Functions

A function executes a sequential algorithm and returns a single value to the calling program. When the following function is called, it returns a bit vector equal to the input bit vector (reg) rotated one position to the right:

```
function rotate_right (reg: bit_vector)
    return bit_vector is
begin
    return reg ror 1;
end rotate_right;
```

A function call can be used anywhere that an expression can be used. For example, if A = "10010101", the statement

```
B <= rotate_right(A);
```

sets B equal to "11001010", and leaves A unchanged.

General form of function declaration:

```
function function-name (formal-parameter-list)
    return return-type is
    [declarations]
begin
    sequential statements -- must include return return-value;
end function-name;
```

General form of function call:

```
function_name (actual-parameter-list)
```

From Page 72

General form of a for loop:

```
[loop-label:] for loop-index in range loop  
    sequential statements  
end loop [loop-label];
```

Exit statement has the form:

```
exit;                -- or  
exit when condition;
```

For Loop Example:

```
-- compare two 8-character strings and return TRUE if equal  
function comp_string(string1, string2: string(1 to 8))  
    return boolean is
```

```
variable B: boolean;  
begin
```

```
    loopex: for j in 1 to 8 loop  
        B := string1(j) = string2(j);  
        exit when B=FALSE;  
    end loop loopex;  
    return B;  
end comp_string;
```

Note: The loop index (j) is automatically declared; it must not be declared in the program.

Figure 2-22 Add Function

-- This function adds 2 4-bit vectors and a carry.
-- It returns a 5-bit sum

```
function add4 (A,B: bit_vector(3 downto 0); carry: bit)
  return bit_vector is

variable cout: bit;
variable cin: bit := carry;
variable Sum: bit_vector(4 downto 0):="00000";
begin
loop1: for i in 0 to 3 loop
  cout := (A(i) and B(i)) or (A(i) and cin) or (B(i) and cin);
  Sum(i) := A(i) xor B(i) xor cin;
  cin := cout;
end loop loop1;
Sum(4):= cout;
return Sum;
end add4;
```

Example function call:

```
Sum1 <= add4(A1, B1, cin);
```

Figure 2-23 Procedure for Adding Bit_vectors

-- This procedure adds two n-bit bit_vectors and a carry and
-- returns an n-bit sum and a carry. Add1 and Add2 are assumed
-- to be of the same length and dimensioned n-1 downto 0.

```
procedure Addvec  
  (Add1,Add2: in bit_vector;  
   Cin: in bit;  
   signal Sum: out bit_vector;  
   signal Cout: out bit;  
   n:in positive) is  
   variable C: bit;  
begin  
  C := Cin;  
  for i in 0 to n-1 loop  
    Sum(i) <= Add1(i) xor Add2(i) xor C;  
    C := (Add1(i) and Add2(i)) or (Add1(i) and C) or (Add2(i) and C);  
  end loop;  
  Cout <= C;  
end Addvec;
```

Example procedure call:

```
Addvec(A1, B1, Cin, Sum1, Cout, 4);
```

Table 2-1 Parameters for Subprogram Calls

Mode	Class	Actual Parameter	
		Procedure Call	Function Call
in ¹	constant ²	expression	expression
	signal	signal	signal
	variable	variable	n/a
out/inout	signal	signal	n/a
	variable ³	variable	n/a

¹ default mode for functions ² default for in mode ³ default for out/inout mode

From Page 76

General form of Package declaration:

```
package package-name is  
    package declarations  
end [package][package-name];
```

General form of Package body:

```
package body package-name is  
    package body declarations  
end [package body][package name];
```

Packages and associated components can be placed in a library to allow easy access.

Library BITLIB (see Appendix B) contains functions and components that use signals of type bit.

To access components and functions within BITLIB, use the following statements:

```
library BITLIB;  
use BITLIB.bit_pack.all;
```

Appendix B Bit Package (i)

-- Bit package for Digital Systems Design Using VHDL

```
package bit_pack is
  function add4 (reg1,reg2: bit_vector(3 downto 0);carry: bit)
    return bit_vector;
  function falling_edge(signal clock:bit)
    return Boolean ;
  function rising_edge(signal clock:bit)
    return Boolean ;
  function vec2int(vec1: bit_vector)
    return integer;
  function int2vec(int1,NBits: integer)
    return bit_vector;
  procedure Addvec
    (Add1,Add2: in bit_vector;
     Cin: in bit;
     signal Sum: out bit_vector;
     signal Cout: out bit;
     n: in natural);

  component jkff
    generic(DELAY:time := 10 ns);
    port(SN, RN, J,K,CLK: in bit; Q, QN: inout bit);
  end component;

  component dff
    generic(DELAY:time := 10 ns);
    port (D, CLK: in bit; Q: out bit; QN: out bit := '1');
  end component;
```


Appendix B Bit Package (ii)

```
component and2  
  generic(DELAY:time := 10 ns);  
  port(A1, A2: in bit; Z: out bit);  
end component;
```

```
component and3  
  generic(DELAY:time := 10 ns);  
  port(A1, A2, A3: in bit; Z: out bit);  
end component;
```

```
component and4  
  generic(DELAY:time := 10 ns);  
  port(A1, A2, A3, A4: in bit; Z: out bit);  
end component;
```

```
component or2  
  generic(DELAY:time := 10 ns);  
  port(A1, A2: in bit; Z: out bit);  
end component;
```

```
component or3  
  generic(DELAY:time := 10 ns);  
  port(A1, A2, A3: in bit; Z: out bit);  
end component;
```

```
...  
(other component declarations go here)
```

```
...
```

```
end bit_pack;
```

Appendix B Bit Package (iii)

```
package body bit_pack is
-- This function adds 2 4-bit numbers, returns a 5-bit sum
function add4 (reg1,reg2: bit_vector(3 downto 0);carry: bit)
    return bit_vector is
variable cout: bit:='0';
variable cin: bit:=carry;
variable retval: bit_vector(4 downto 0):="00000";
begin
lp1: for i in 0 to 3 loop
    cout :=(reg1(i) and reg2(i)) or ( reg1(i) and cin) or
        (reg2(i) and cin );
    retval(i) := reg1(i) xor reg2(i) xor cin;
    cin := cout;
end loop lp1;
retval(4):=cout;
return retval;
end add4;

-- Function for falling edge
function falling_edge(signal clock:bit)
    return Boolean is
begin
    return clock'event and clock = '0';
end falling_edge;

-- other functions and procedure declarations go here

end bit_pack
```

Appendix B Bit Package (iv)

Components in Library BITLIB include:


-- 3 input AND gate

```
entity And3 is  
    generic(DELAY:time);  
    port (A1,A2, A3: in bit; Z: out bit);  
end And3;  
architecture concur of And3 is  
begin  
    Z <= A1 and A2 and A3 after DELAY;  
end;
```

-- D Flip-flop

```
entity DFF is  
    generic(DELAY:time);  
    port (D, CLK: in bit;  
        Q: out bit; QN: out bit := '1');  
    -- initialize QN to '1' since bit signals are initialized to '0' by default  
end DFF;  
architecture SIMPLE of DFF is  
begin  
    process(CLK)  
    begin  
        if CLK = '1' then --rising edge of clock  
            Q <= D after DELAY;  
            QN <= not D after DELAY;  
        end if;  
    end process;  
end SIMPLE;
```

Figure 2-24 Two 74163 Counters Cascaded to Form an 8-bit Counter

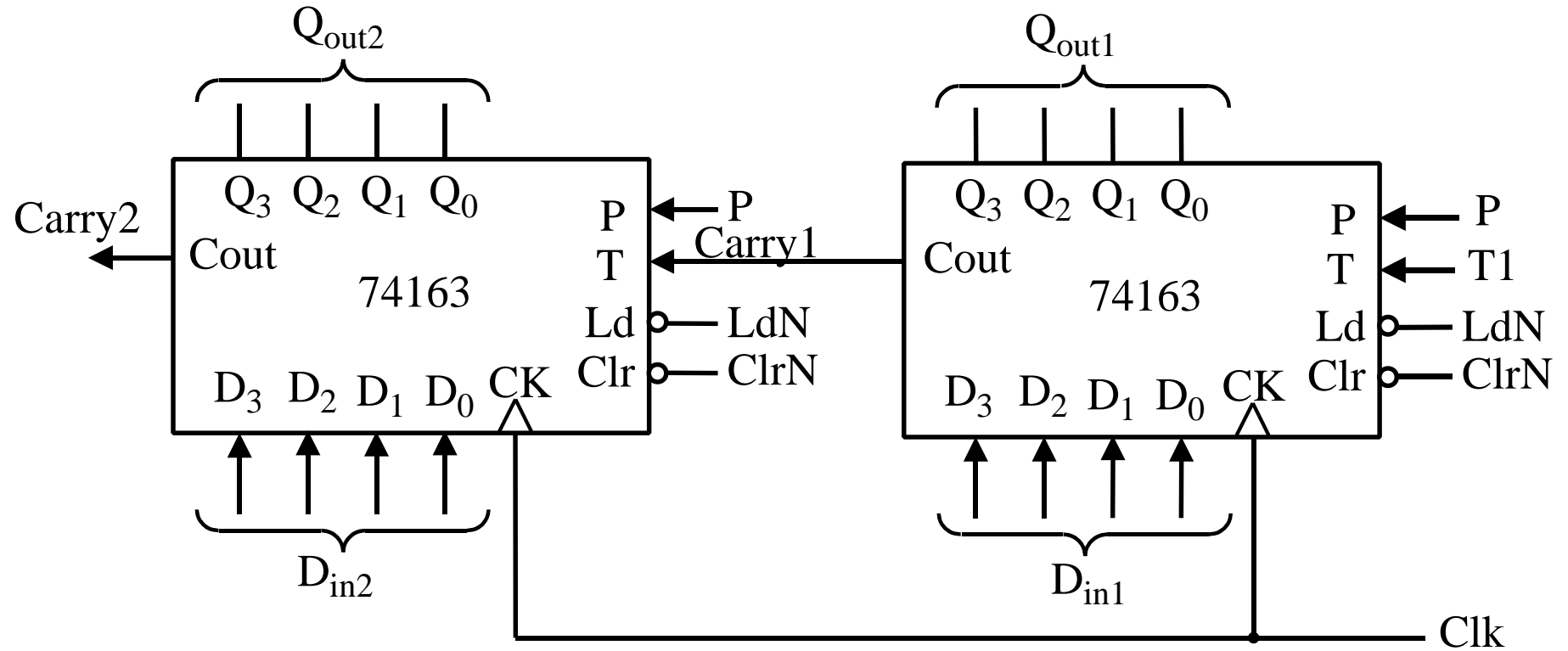

Control Signals			Next State				
$ClrN$	LdN	$P \cdot T$	Q_3^+	Q_2^+	Q_1^+	Q_0^+	
0	X	X	0	0	0	0	(clear)
1	0	X	D_3	D_2	D_1	D_0	(parallel load)
1	1	0	Q_3	Q_2	Q_1	Q_0	(no change)
1	1	1	present state + 1				(increment count)

Figure 2-25 74163 Counter Model

-- 74163 FULLY SYNCHRONOUS COUNTER

```
library BITLIB;                                -- contains int2vec and vec2int functions
use BITLIB.bit_pack.all;
```

```
entity c74163 is
    port(LdN, ClrN, P, T, CK: in bit; D: in bit_vector(3 downto 0);
        Cout: out bit; Q: inout bit_vector(3 downto 0) );
end c74163;
```

```
architecture b74163 of c74163 is
begin
```

```
    Cout <= Q(3) and Q(2) and Q(1) and Q(0) and T;
```

```
    process
```

```
    begin
```

```
        wait until CK = '1';                    -- change state on rising edge
```

```
        if ClrN = '0' then Q <= "0000";
```

```
            elsif LdN = '0' then Q <= D;
```

```
            elsif (P and T) = '1' then
```

```
                Q <= int2vec(vec2int(Q)+1,4);
```

```
            end if;
```

```
    end process;
```

```
end b74163;
```

Figure 2-26 VHDL for 8-bit Counter

```
library BITLIB;
use BITLIB.bit_pack.all;

entity c74163test is
    port(ClrN,LdN,P,T1,Clk: in bit;
        Din1, Din2: in bit_vector(3 downto 0);
        Qout1, Qout2: inout bit_vector(3 downto 0);
        Carry2: out bit);
end c74163test;

architecture tester of c74163test is
    component c74163
        port(LdN, ClrN, P, T, CK: in bit; D: in bit_vector(3 downto 0);
        Cout: out bit; Q: inout bit_vector(3 downto 0) );
    end component;
    signal Carry1: bit;
    signal Count: integer;
    signal temp: bit_vector(7 downto 0);
begin
    ct1: c74163 port map (LdN,ClrN,P,T1,Clk,Din1,Carry1,Qout1);
    ct2: c74163 port map (LdN,ClrN,P,Carry1,Clk,Din2,Carry2,Qout2);
    temp <= Qout2 & Qout1;
    Count <= vec2int(temp);
end tester;
```