
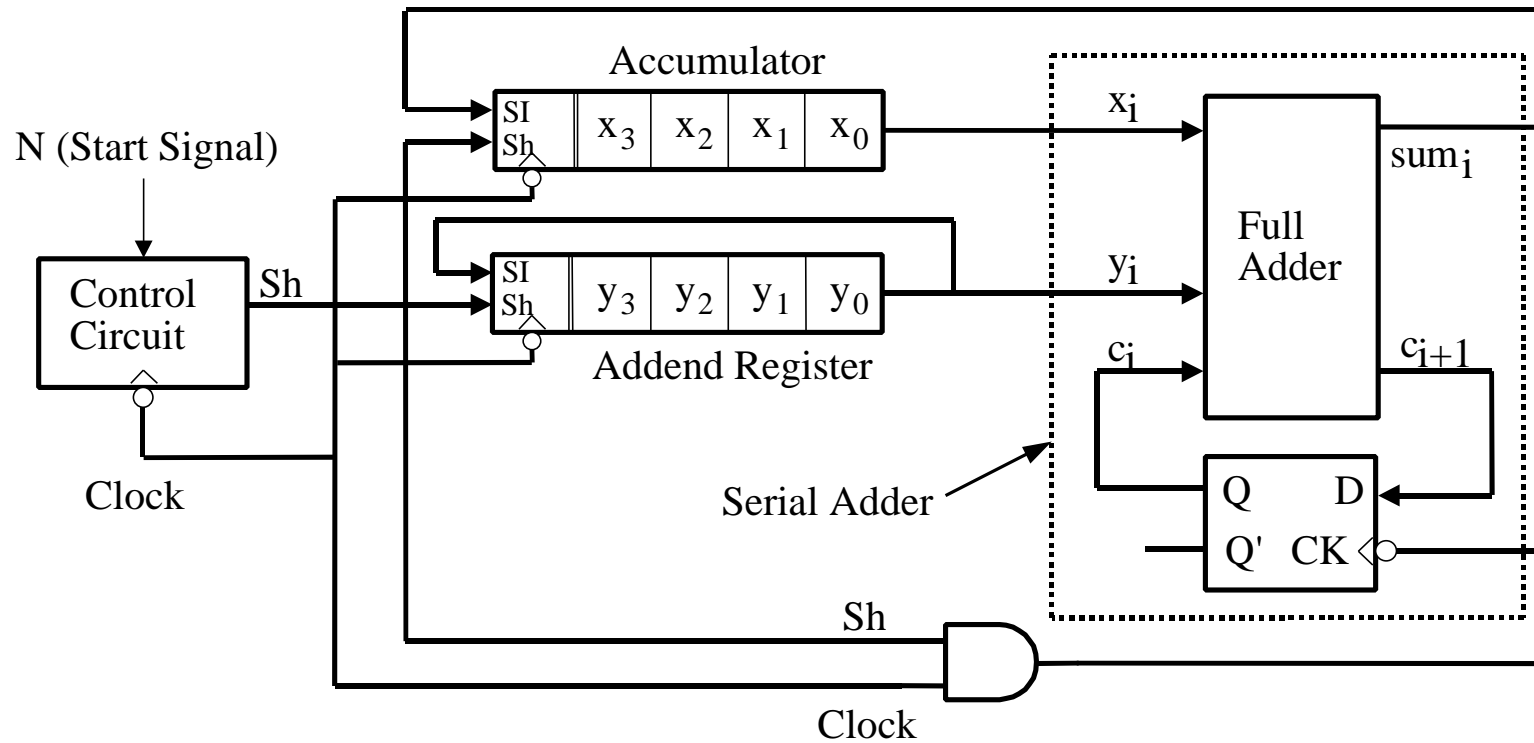


**Figure 4-1 Serial Adder with Accumulator**

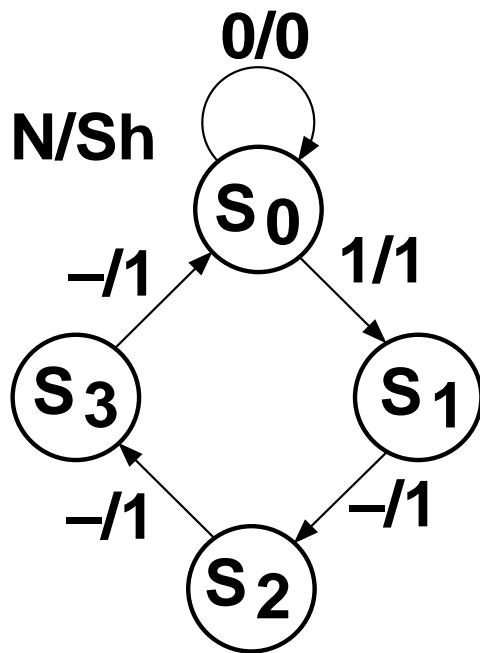

	X	Y	$c_i$	$sum_i$	$c_{i+1}$
$t_0$	0101	0111	0	0	1
$t_1$	0010	1011	1	0	1
$t_2$	0001	1101	1	1	1
$t_3$	1000	1110	1	1	0
$t_4$	1100	0111	0	(1)	(0)


**Figure 4-2 Control State Graph and Table for Serial Adder**




Present State	Next State		Present Output (Sh)	
	N=0	N=1	N=0	N=1
S0	S0	S1	0	1
S1	S2	S2	1	1
S2	S3	S3	1	1
S3	S0	S0	1	1

## Constraints on Input Labels for Every State $S_k$ (From Page 123-124)

 1. If  $I_i$  and  $I_j$  are any pair of input labels on arcs exiting state  $S_k$ , then  $I_i I_j = 0$  if  $i \neq j$ .
2. If  $n$  arcs exit state  $S_k$  and the  $n$  arcs have input labels  $I_1, I_2, \dots, I_n$ , respectively, then  $I_1 + I_2 + \dots + I_n = 1$ .


 
$$\begin{aligned}
 (X_1)(X_1'X_2') &= 0 \\
 (X_1)(X_1'X_2) &= 0 \\
 (X_1'X_2')(X_1'X_2) &= 0 \\
 X_1 + X_1'X_2' + X_1'X_2 &= 1
 \end{aligned}$$



Inputs are  $X_1 X_2 X_3$   
 $(X_1 = X_2 = 1)$  not allowed

	000	001	010	011	100	101	110	111
$S_k$	$S_k$	$S_k$	$S_q$	$S_q$	$S_p$	$S_p$	-	-


## Multiplication of $13_{10}$ by $11_{10}$ In Binary – From Page 124

$$\begin{array}{r}
 \text{Multiplicand} \longrightarrow 1101 \quad (13) \\
 \text{Multiplier} \longrightarrow \underline{1011} \quad (11) \\
 \hline
 \text{Partial Products} \left\{ \begin{array}{l} \longrightarrow 1101 \\ \longrightarrow \underline{1101} \\ \longrightarrow 100111 \\ \longrightarrow \underline{0000} \\ \longrightarrow 100111 \\ \longrightarrow \underline{1101} \end{array} \right. \\
 \hline
 10001111 \quad (143)
 \end{array}$$


initial contents of product register	0 0 0 0 0   1 0 1 1 ← M (11)	
(add multiplicand since M=1)	1 1 0 1	(13)
after addition	0 1 1 0 1   1 0 1 1	
after shift	0 0 1 1 0 1   1 0 1 ← M	
(add multiplicand since M=1)	1 1 0 1	
after addition	1 0 0 1 1 1   1 0 1	
after shift	0 1 0 0 1 1 1   1 0 ← M	
(skip addition since M=0)		
after shift	0 0 1 0 0 1 1 1   1 ← M	
(add multiplicand since M=1)	1 1 0 1	
after addition	1 0 0 0 1 1 1 1   1	
after shift (final answer)	0 1 0 0 0 1 1 1 1	(143)

dividing line between product and multiplier

**Figure 4-3 Block Diagram for Binary Multiplier**

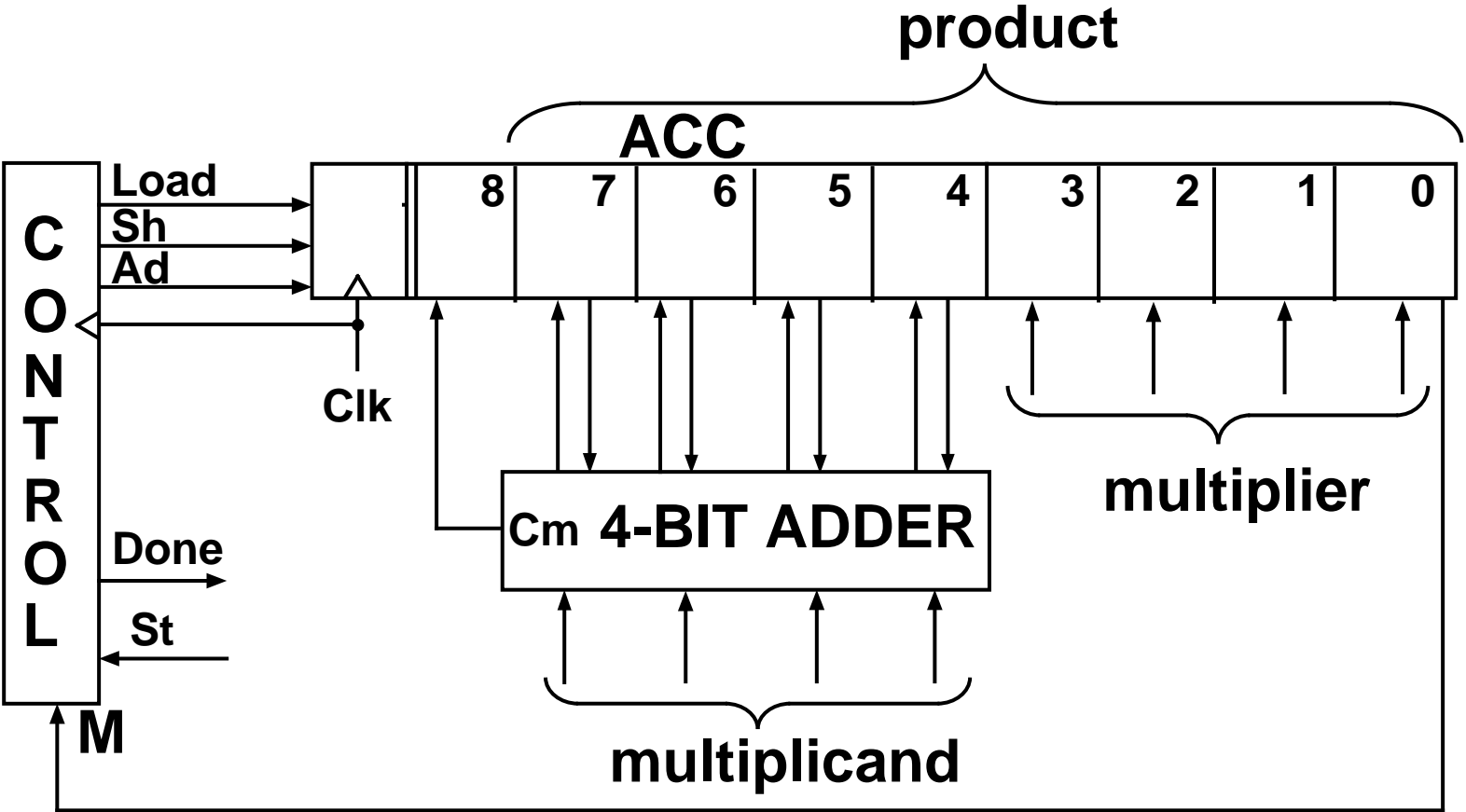

**Figure 4-4 State graph for Binary Multiplier Control**

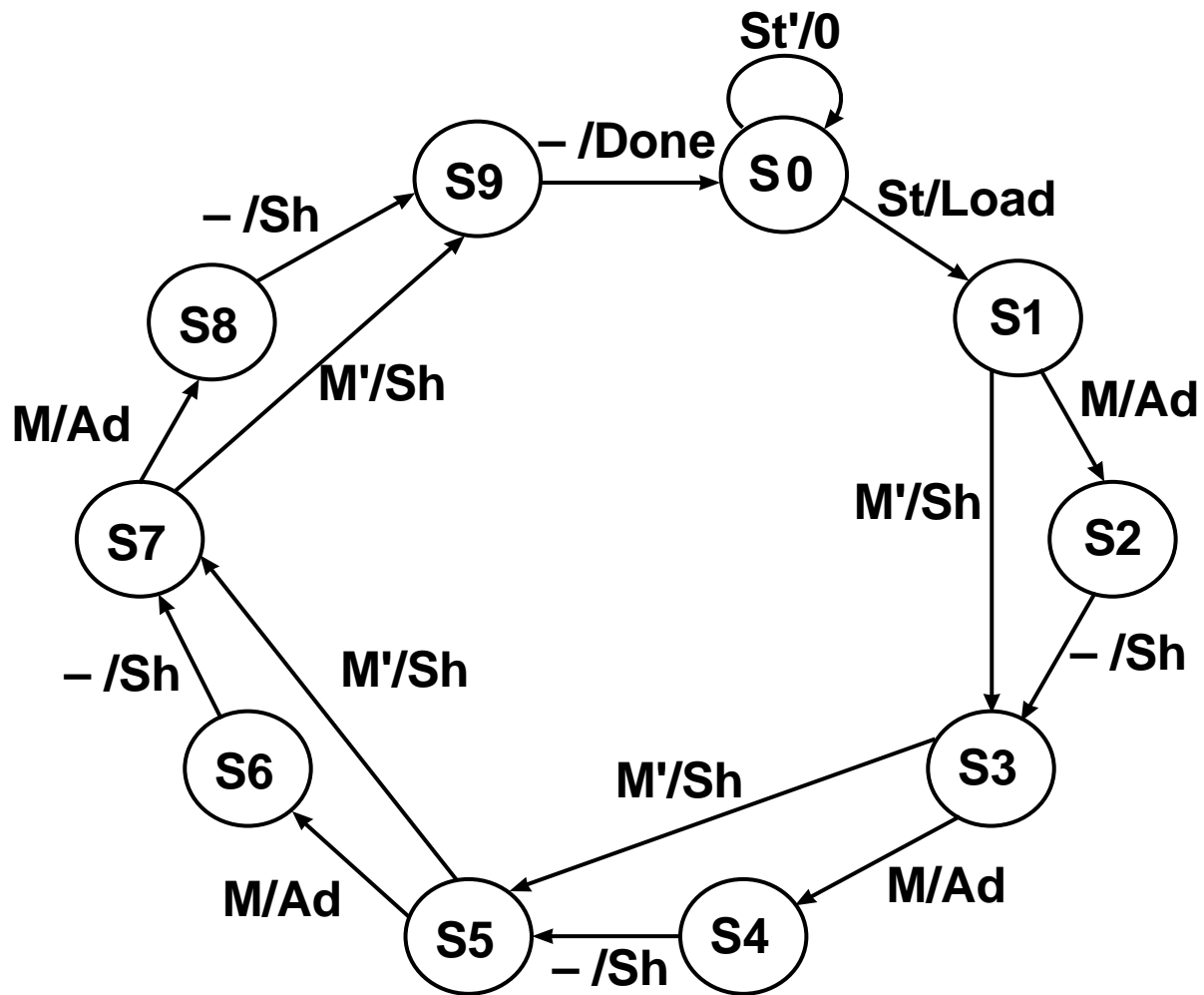

## Figure 4-5(a) Behavioral Model for 4 x 4 Binary Multiplier

- This is a behavioral model of a multiplier for unsigned binary numbers. It multiplies a
- 4-bit multiplicand by a 4-bit multiplier to give an 8-bit product.
- The maximum number of clock cycles needed for a multiply is 10.


```
library BITLIB;
use BITLIB.bit_pack.all;
entity mult4X4 is
    port (Clk, St: in bit;
          Mplier,Mcand : in bit_vector(3 downto 0);
          Done: out bit);
end mult4X4;
architecture behave1 of mult4X4 is
    signal State: integer range 0 to 9;
    signal ACC: bit_vector(8 downto 0);           -- accumulator
    alias M: bit is ACC(0);                       -- M is bit 0 of ACC
begin
    process
    begin
        wait until Clk = '1';                     -- executes on rising edge of clock
        case State is
            when 0=>                                -- initial State
                if St='1' then
                    ACC(8 downto 4) <= "00000";    -- Begin cycle
                    ACC(3 downto 0) <= Mplier;     -- load the multiplier
                    State <= 1;
                end if;
            end case;
        end process;
    end behave1;
```

## Figure 4-5(b) Behavioral Model for 4 x 4 Binary Multiplier


```
when 1 | 3 | 5 | 7 => -- "add/shift" State
  if M = '1' then -- Add multiplicand
    ACC(8 downto 4) <= add4(ACC(7 downto 4), Mcand, '0');
    State <= State + 1;
  else
    ACC <= '0' & ACC(8 downto 1); --Shift accumulator right
    State <= State + 2;
  end if;
when 2 | 4 | 6 | 8 => -- "shift" State
  ACC <= '0' & ACC(8 downto 1); -- Right shift
  State <= State + 1;
when 9 => -- End of cycle
  State <= 0;
end case;
end process;
Done <= '1' when State = 9 else '0';
end behave1;
```



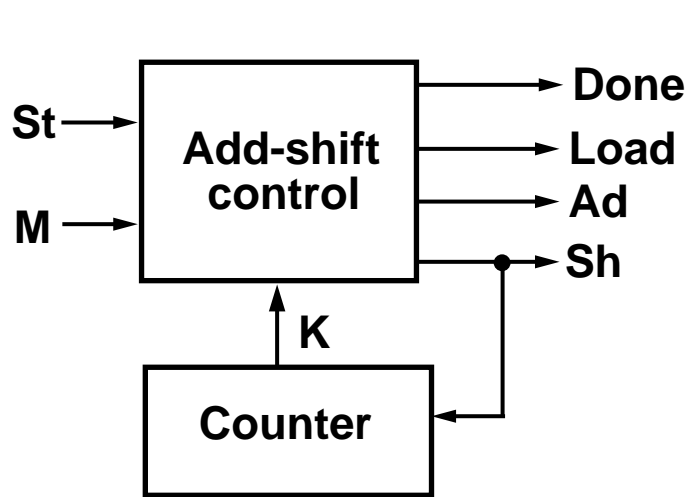
# Figure 4-6 Multiplier Control with Counter



(a) Multiplier control

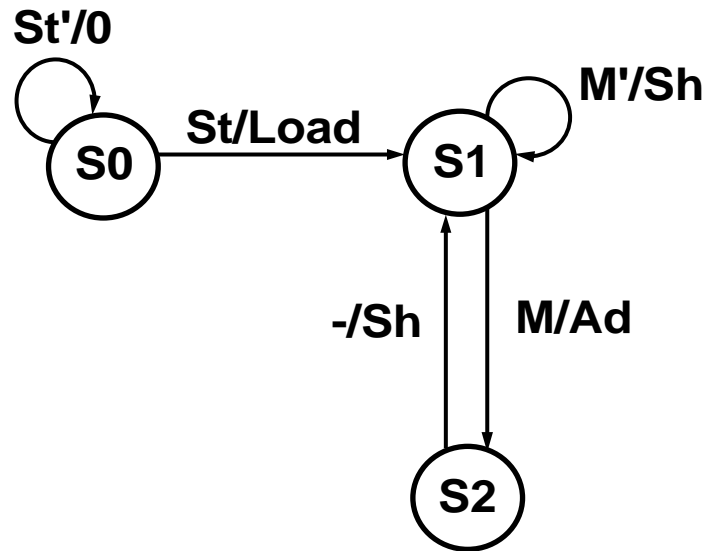

(b) State graph for add-shift control

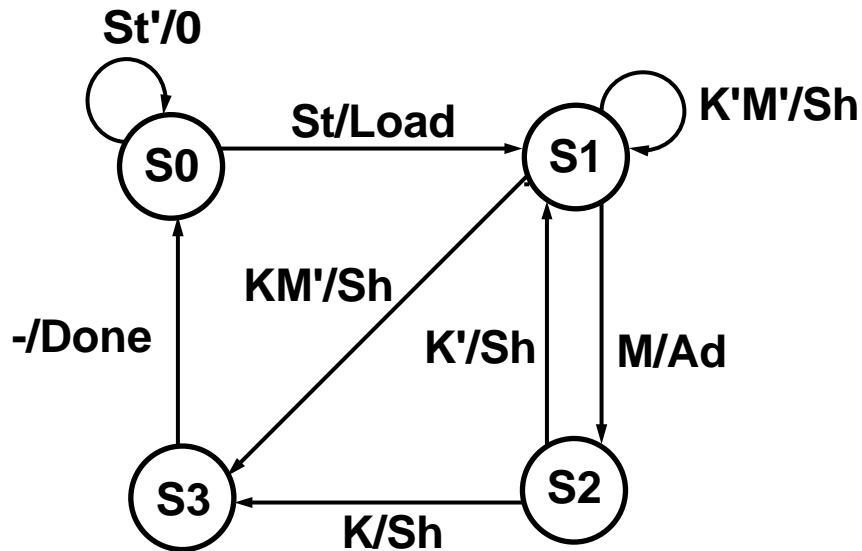


(c) Final state graph for add-shift control

**Table 4-2 Operation of Multiplier Using a Counter**

Time	State	Counter	Product Register	St	M	K	Load	Ad	Sh	Done
t0	S0	00	000000000	0	0	0	0	0	0	0
t1	S0	00	000000000	1	0	0	1	0	0	0
t2	S1	00	000001011	0	1	0	0	1	0	0
t3	S2	00	011011011	0	1	0	0	0	1	0
t4	S1	01	001101101	0	1	0	0	1	0	0
t5	S2	01	100111101	0	1	0	0	0	1	0
t6	S1	10	010011110	0	0	0	0	0	1	0
t7	S1	11	001001111	0	1	1	0	1	0	0
t8	S2	11	100011111	0	1	1	0	0	1	0
t9	S3	00	010001111	0	1	0	0	0	0	1



**Figure 4-7 Block Diagram of 4 x 4 Array Multiplier**

 

## From Page 133

0. 1 1 1	(+7/8)	←	Multiplicand
X 0. 1 0 1	(+5/8)	←	Multiplier
(0. 0 0) 0 1 1 1	(+7/64)	←	<i>Note:</i> The proper representation of the fractional partial products requires extension of the sign bit past the binary point, as indicated in parentheses. (Such extension is not necessary in the hardware.)
(0.)0 1 1 1	(+7/16)	←	
0. 1 0 0 0 1 1	(+35/64)		

1. 1 0 1	(-3/8)	
X 0. 1 0 1	(+5/8)	
(1. 1 1) 1 1 0 1	(-3/64)	←
(1.)1 1 0 1	(-3/16)	←
1. 1 1 0 0 0 1	(-15/64)	


*Note:* The extension of the sign bit provides proper representation of the negative products.

**From Pages 133 – 134**


	0. 1 0 1	(+5/8)	
X	1. 1 0 1	(-3/8)	
(0. 0 0)	0 1 0 1	(+5/64)	
(0.)	0 1 0 1	(+5/16)	
(0.)	0 1 1 0 0 1		
1. 0 1 1		(-5/8)	← Note: The two's complement of the multiplicand is added at this point.
1. 1 1 0 0 0 1		(-15/64)	

	1. 1 0 1	(-3/8)	
X	1. 1 0 1	(-3/8)	
(1. 1 1)	1 1 0 1	(-3/64)	
(1.)	1 1 0 1	(-3/16)	
(1.)	1 1 0 0 0 1		
0. 0 1 1		(+3/8)	← Add the two's complement of the multiplicand
0. 0 0 1 0 0 1		(+9/64)	

**Figure 4-8 Block Diagram for 2's Complement Multiplier**

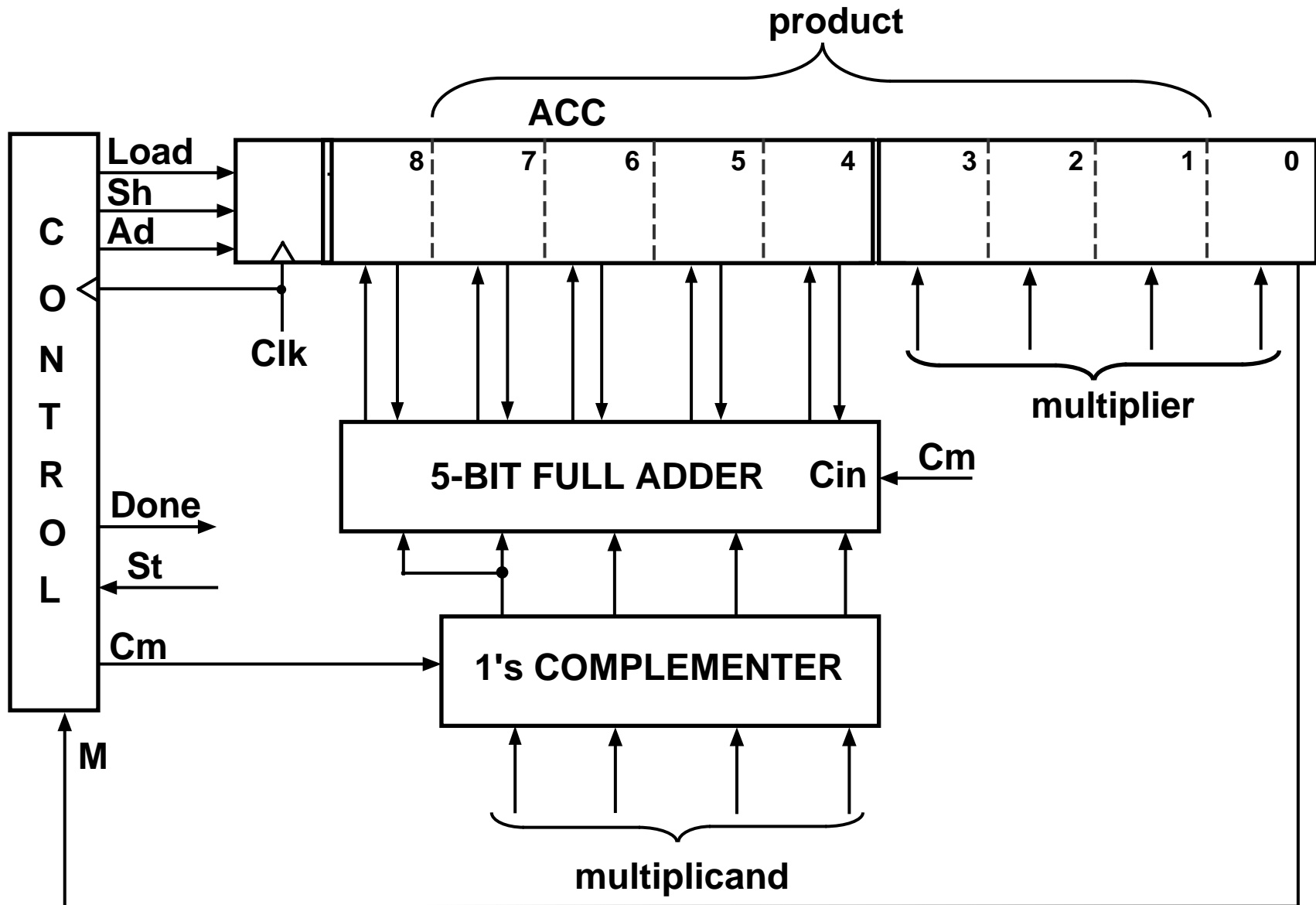


**Figure 4-9 State Graph for 2's Complement Multiplier**

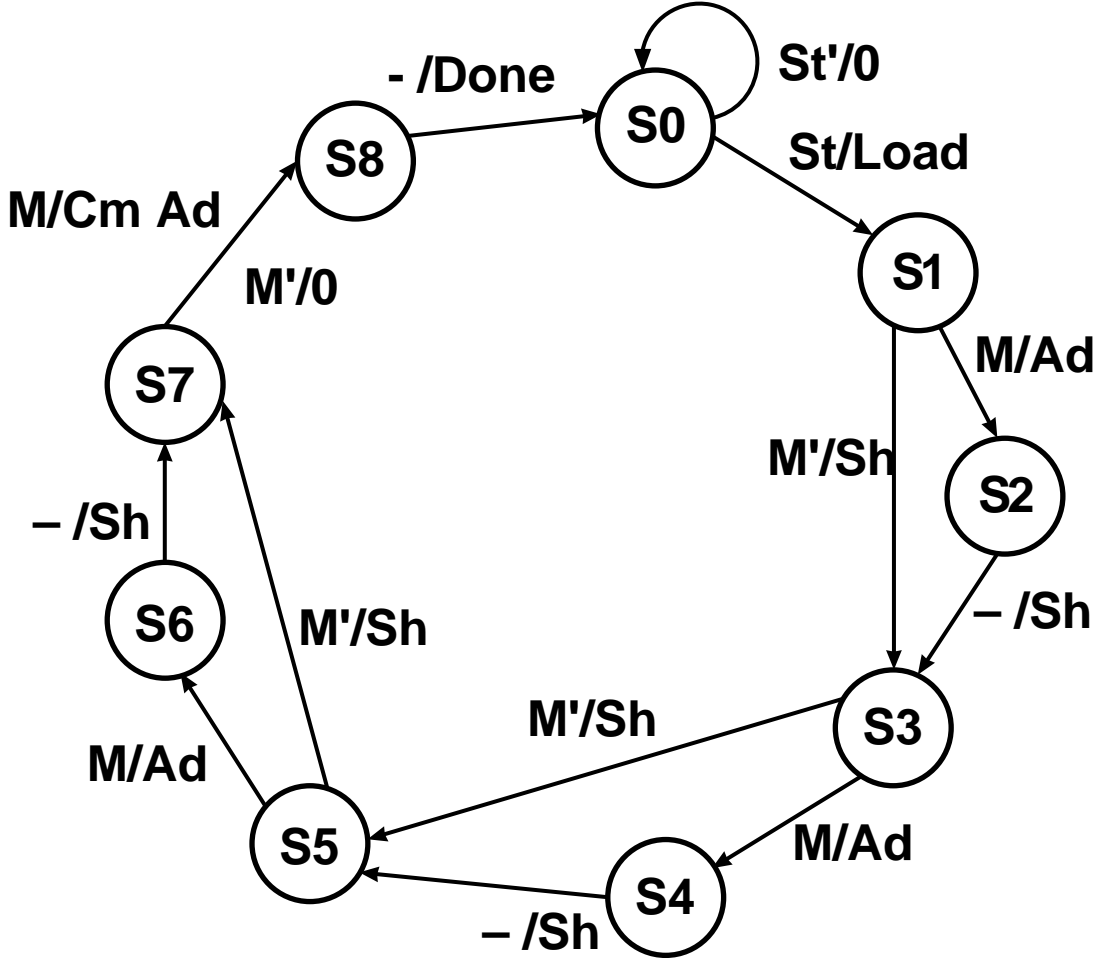




**Figure 4-10 Block Diagram for Faster Multiplier**

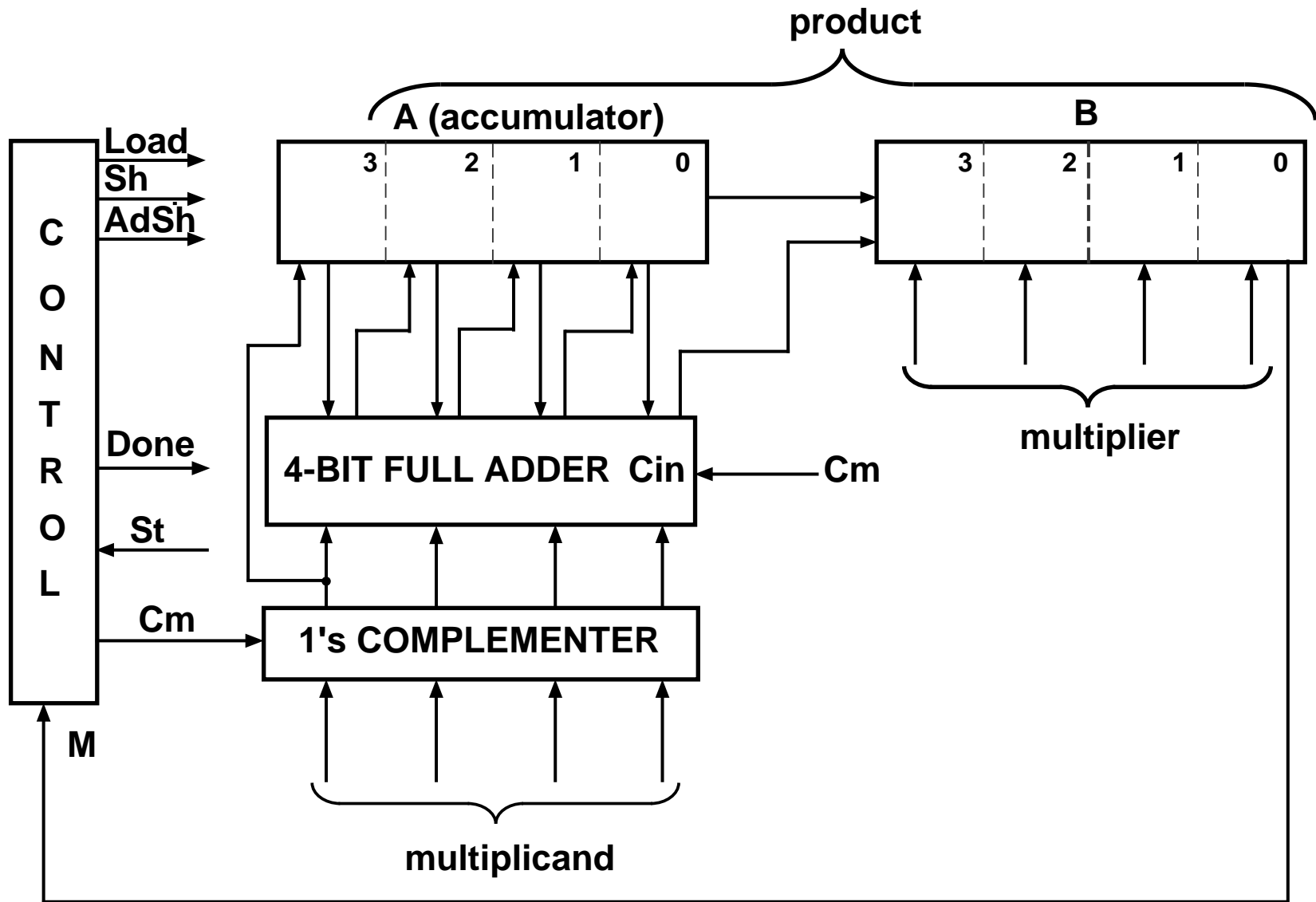

**Figure 4-11 State Graph for Faster Multiplier**

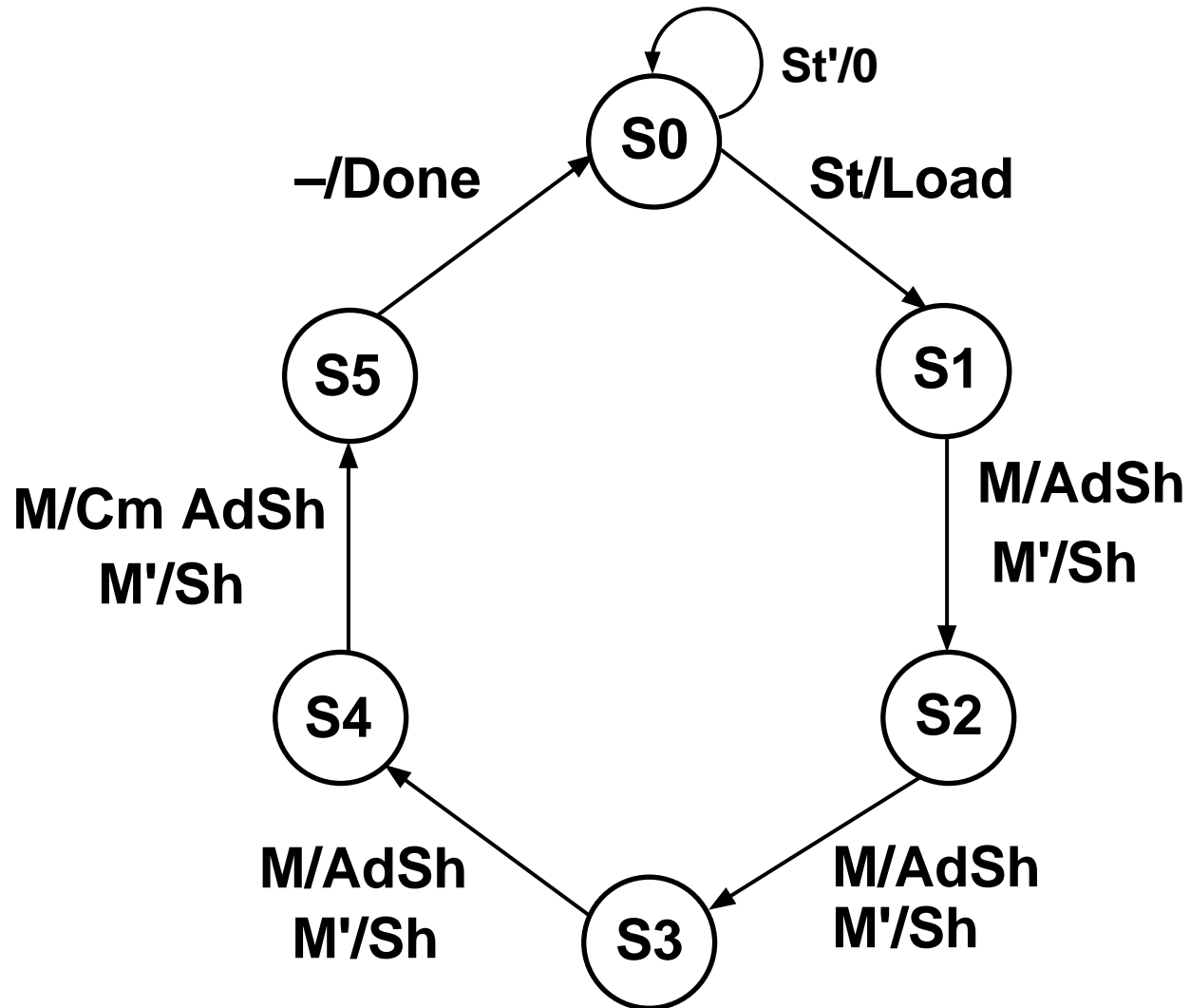

## Figure 4-12(a) Behavioral Model for 2's Complement Multiplier

```
library BITLIB;
use BITLIB.bit_pack.all;

entity mult2C is
    port (CLK, St: in bit;
          Mplier,Mcand : in bit_vector(3 downto 0);
          Product: out bit_vector (6 downto 0);
          Done: out bit);
end mult2C;

architecture behave1 of mult2C is
    signal State : integer range 0 to 5;
    signal A, B: bit_vector(3 downto 0);
    alias M: bit is B(0);
begin
    process
        variable addout: bit_vector(4 downto 0);
    begin
        wait until CLK = '1';
        case State is
            when 0=> -- initial State
                if St='1' then
                    A <= "0000"; -- Begin cycle
                    B <= Mplier; -- load the multiplier
                    State <= 1;
                end if;
            end case;
        end process;
    end architecture;
```

## Figure 4-12(b) Behavioral Model for 2's Complement Multiplier

```
when 1 | 2 | 3 => -- "add/shift" State
  if M = '1' then
    addout := add4(A,Mcand,'0'); -- Add multiplicand to A and shift
    A <= Mcand(3) & addout(3 downto 1);
    B <= addout(0) & B(3 downto 1);
  else
    A <= A(3) & A(3 downto 1); -- Arithmetic right shift
    B <= A(0) & B(3 downto 1);
  end if;
  State <= State + 1;
when 4 => -- add complement if sign bit
  if M = '1' then -- of multiplier is 1
    addout := add4(A, not Mcand,'1');
    A <= not Mcand(3) & addout(3 downto 1);
    B <= addout(0) & B(3 downto 1);
  else
    A <= A(3) & A(3 downto 1); -- Arithmetic right shift
    B <= A(0) & B(3 downto 1);
  end if;
  State <= 5; wait for 0 ns;
  Done <= '1'; Product <= A(2 downto 0) & B;
when 5 => -- output product
  State <= 0;
  Done <= '0';
end case;
end process;
end behave1;
```

### Figure 4-13 Command File and Simulation Results for (+5/8 by -3/8)

```
-- command file to test signed multiplier
list CLK St State A B Done Product
force st 1 2, 0 22
force clk 1 0, 0 10 - repeat 20
-- (5/8 * -3/8)
force Mcand 0101
force Mplier 1101
run 120
```

ns	delta	CLK	St	State	A	B	Done	Product
0	+1	1	0	0	0000	0000	0	0000000
2	+0	1	1	0	0000	0000	0	0000000
10	+0	0	1	0	0000	0000	0	0000000
20	+1	1	1	1	0000	1101	0	0000000
22	+0	1	0	1	0000	1101	0	0000000
30	+0	0	0	1	0000	1101	0	0000000
40	+1	1	0	2	0010	1110	0	0000000
50	+0	0	0	2	0010	1110	0	0000000
60	+1	1	0	3	0001	0111	0	0000000
70	+0	0	0	3	0001	0111	0	0000000
80	+1	1	0	4	0011	0011	0	0000000
90	+0	0	0	4	0011	0011	0	0000000
100	+2	1	0	5	1111	0001	1	1110001
110	+0	0	0	5	1111	0001	1	1110001
120	+1	1	0	0	1111	0001	0	1110001

## Figure 4-14 Test Bench for Signed Multiplier

```
library BITLIB;
use BITLIB.bit_pack.all;
entity testmult is end testmult;

architecture test1 of testmult is
component mult2C
    port(CLK, St: in bit;
        Mplier,Mcand : in bit_vector(3 downto 0);
        Product: out bit_vector (6 downto 0);
        Done: out bit);
end component;
    constant N: integer := 11; type arr is array(1 to N) of bit_vector(3 downto 0);
    constant Mcandarr: arr := ("0111", "1101", "0101", "1101", "0111", "1000", "0111",
        "1000", "0000", "1111", "1011");
    constant Mplierarr: arr := ("0101", "0101", "1101", "1101", "0111", "0111", "1000",
        "1000", "1101", "1111", "0000");
    signal CLK, St, Done: bit; signal Mplier, Mcand: bit_vector(3 downto 0);
    signal Product: bit_vector(6 downto 0);
begin
    CLK <= not CLK after 10 ns;
    process
    begin
        for i in 1 to N loop
            Mcand <= Mcandarr(i); Mplier <= Mplierarr(i); St <= '1';
            wait until rising_edge(CLK); St <= '0'; wait until falling_edge(Done);
        end loop;
    end process;
    mult1: mult2c port map(Clk, St, Mplier, Mcand, Product, Done);
end test1;
```

## Figure 4-15 Command File and Simulation of Signed Multiplier

-- Command file to test results of signed multiplier

```
list -NOtrigger Mplier Mcand product -Trigger done  
run 1320
```

ns	delta	mplier	mcand	product	done	
0	+1	0101	0111	0000000	0	
90	+2	0101	0111	0100011	1	$5/8 * 7/8 = 35/64$
110	+2	0101	1101	0100011	0	
210	+2	0101	1101	1110001	1	$5/8 * -3/8 = -15/64$
230	+2	1101	0101	1110001	0	
330	+2	1101	0101	1110001	1	$-3/8 * 5/8 = -15/64$
350	+2	1101	1101	1110001	0	
450	+2	1101	1101	0001001	1	$-3/8 * -3/8 = 9/64$
470	+2	0111	0111	0001001	0	
570	+2	0111	0111	0110001	1	$7/8 * 7/8 = 49/64$
590	+2	0111	1000	0110001	0	
690	+2	0111	1000	1001000	1	$7/8 * -1 = -7/8$
710	+2	1000	0111	1001000	0	
810	+2	1000	0111	1001000	1	$-1 * 7/8 = -7/8$
830	+2	1000	1000	1001000	0	
930	+2	1000	1000	1000000	1	$-1 * -1 = -1$ (error)
950	+2	1101	0000	1000000	0	
1050	+2	1101	0000	0000000	1	$-3/8 * 0 = 0$
1070	+2	1111	1111	0000000	0	
1170	+2	1111	1111	0000001	1	$-1/8 * -1/8 = 1/64$
1190	+2	0000	1011	0000001	0	
1290	+2	0000	1011	0000000	1	$0 * -3/8 = 0$
1310	+2	0101	0111	0000000	0	

## Figure 4-16(a) [revised] Model for 2's Complement Multiplier with Control Signals

```
library BITLIB;
use BITLIB.bit_pack.all;

entity mult2Cs is
port (CLK, St: in bit;
      Mplier,Mcand : in bit_vector(3 downto 0);
      Product: out bit_vector (6 downto 0); Done: out bit);
end mult2Cs;

architecture behave2 of mult2Cs is
  signal State, Nextstate: integer range 0 to 5; signal A, B: bit_vector(3 downto 0);
  signal AdSh, Sh, Load, Cm: bit; signal addout: bit_vector(4 downto 0);
  alias M: bit is B(0);
begin
  process (state, st, M)
  begin
    Load <= '0'; AdSh <= '0'; Sh <= '0'; Cm <= '0'; Done <= '0';
    case State is
      when 0=> -- initial State
        if St='1' then Load <= '1'; Nextstate <= 1; end if;
      when 1 | 2 | 3 => -- "add/shift" State
        if M = '1' then AdSh <= '1'; else Sh <= '1'; end if;
        Nextstate <= State + 1;
      when 4 => -- add complement if sign
        if M = '1' then Cm <= '1'; AdSh <= '1'; -- bit of multiplier is 1
        else Sh <= '1'; end if;
        nextstate <= 5;
```



**Figure 4-16(b) [revised] Model for 2's Complement Multiplier with Control Signals**

```


        when 5 =>                                -- Output product
            done <= '1';
            nextstate <= 0;
        end case;
    end process;

    addout <= add4(A, Mcand, '0') when Cm = '0' else add4(A, not Mcand, '1');

    process
    begin
        wait until CLK = '1';                    -- executes on rising edge
        if Load = '1' then                       -- Load the multiplier
            A <= "0000";
            B <= Mplier;
        end if;
        if AdSh = '1' then                       -- Add multiplicand to A and Shift
            A <= (Mcand(3) xor Cm) & addout(3 downto 1);
            B <= addout(0) & B(3 downto 1);
        end if;
        if Sh = '1' then
            A <= A(3) & A(3 downto 1); B <= A(0) & B(3 downto 1);
        end if;
        State <= Nextstate;
    end process;

    Product <= A(2 downto 0) & B;
end behave2;
```

**Figure 4-17 Realization of Multiplier Control Network**

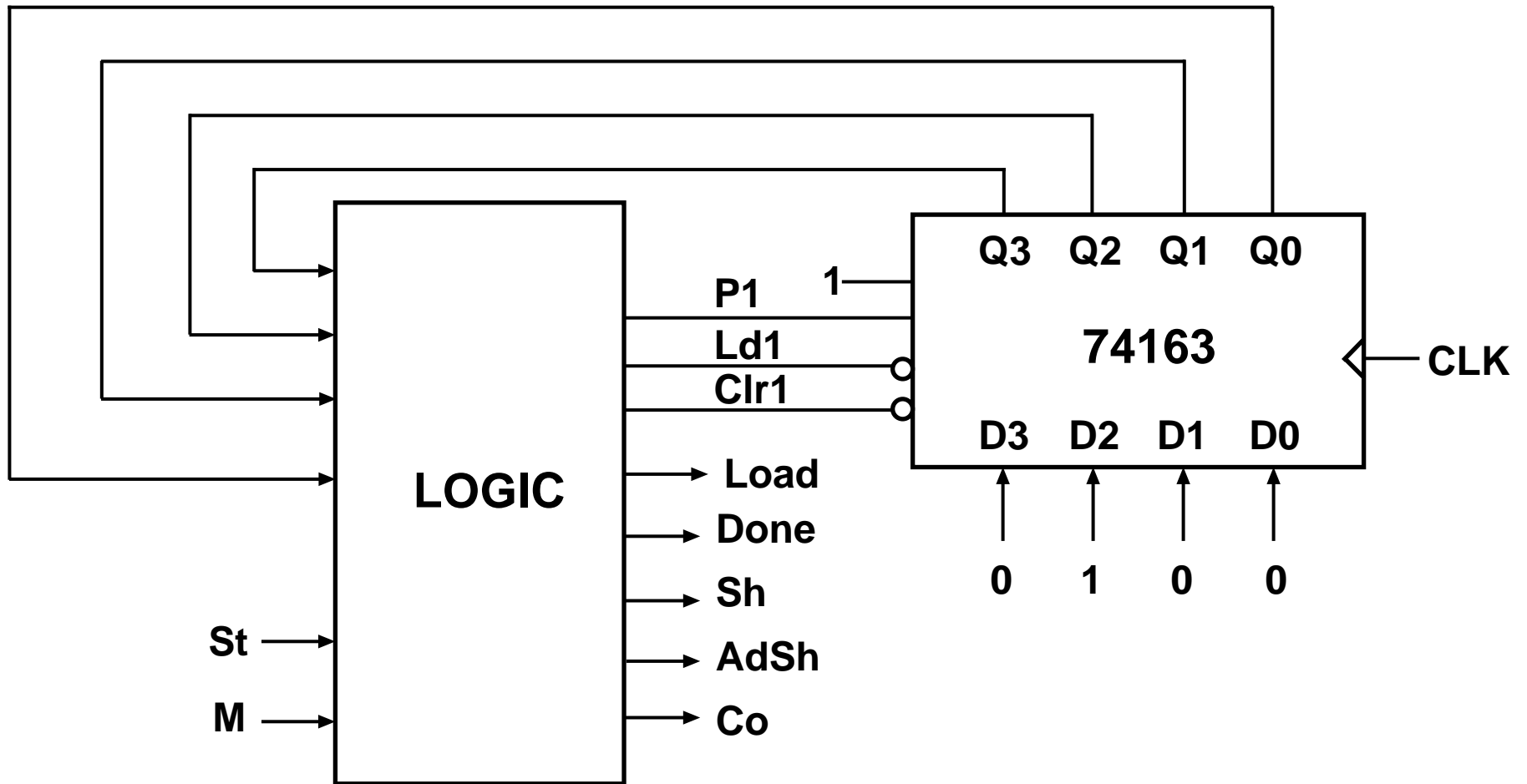

## Figure 4-18(a) Model for 2's Complement Multiplier Using Control Equations

-- This model of a 4-bit multiplier for 2's complement numbers  
-- implements the controller using a counter and logic equations.

**library** BITLIB;

**use** BITLIB.bit\_pack.all;

**entity** mult2CEQ **is**

**port**(CLK, St: **in** bit;

        Mplier, Mcand: **in** bit\_vector(3 **downto** 0);

        Product: **out** bit\_vector(6 **downto** 0));

**end** mult2CEQ;

**architecture** m2ceq **of** mult2CEQ **is**

**signal** A, B, Q, Comp: bit\_vector(3 **downto** 0);

**signal** addout: bit\_vector(4 **downto** 0);

**signal** AdSh, Sh, Load, Cm, Done, Ld1, CLR1, P1: bit;

**Signal** One: bit:='1';

**Signal** Din: bit\_vector(3 **downto** 0) := "0100";

**alias** M: bit **is** B(0);

**begin**

    Count1: C74163 **port** map (Ld1, CLR1, P1, One, CLK, Din, **open**, Q);

    P1 <= Q(2); CLR1 <= **not** Q(3); Done <= Q(3); Sh <= **not** M **and** Q(2);

    AdSh <= M **and** Q(2); Cm <= Q(1) **and** Q(0) **and** M;

    Load <= **not** Q(3) **and** **not** Q(2) **and** St; Ld1 <= **not** Load;

    Comp <= Mcand **xor** (Cm & Cm & Cm & Cm);      -- complement Mcand if Cm='1'


    addout <= add4(A, Comp, Cm);                    -- add complementer output to A

## Figure 4-18(b) Model for 2's Complement Multiplier Using Control Equations


```
process
begin
    wait until CLK = '1';           -- executes on rising edge
    if Load = '1' then           -- load the multiplier
        A <= "0000";
        B <= Mplier;
    end if;
    if AdSh = '1' then           -- Add multiplicand to A and shift
        A <= (Mcand(3) xor Cm) & addout(3 downto 1);
        B <= addout(0) & B(3 downto 1);
    end if;
    if Sh = '1' then           -- Right shift with sign extend
        A <= A(3) & A(3 downto 1);
        B <= A(0) & B(3 downto 1);
    end if;
    if Done = '1' then
        Product <= A(2 downto 0) & B;
    end if;
end process;
end m2ceq;
```

## Parallel Divider for Positive Binary Numbers – From Page 144


divisor	<u>1101</u>	$\overline{1010}$ $\overline{10000111}$	quotient dividend
		$\overline{1101}$ $\overline{0111}$ $\overline{0000}$ $\overline{1111}$ $\overline{1101}$ $\overline{0101}$ $\overline{0000}$ $\overline{0101}$	
(135 ÷ 13 = 10 with a remainder of 5)			remainder

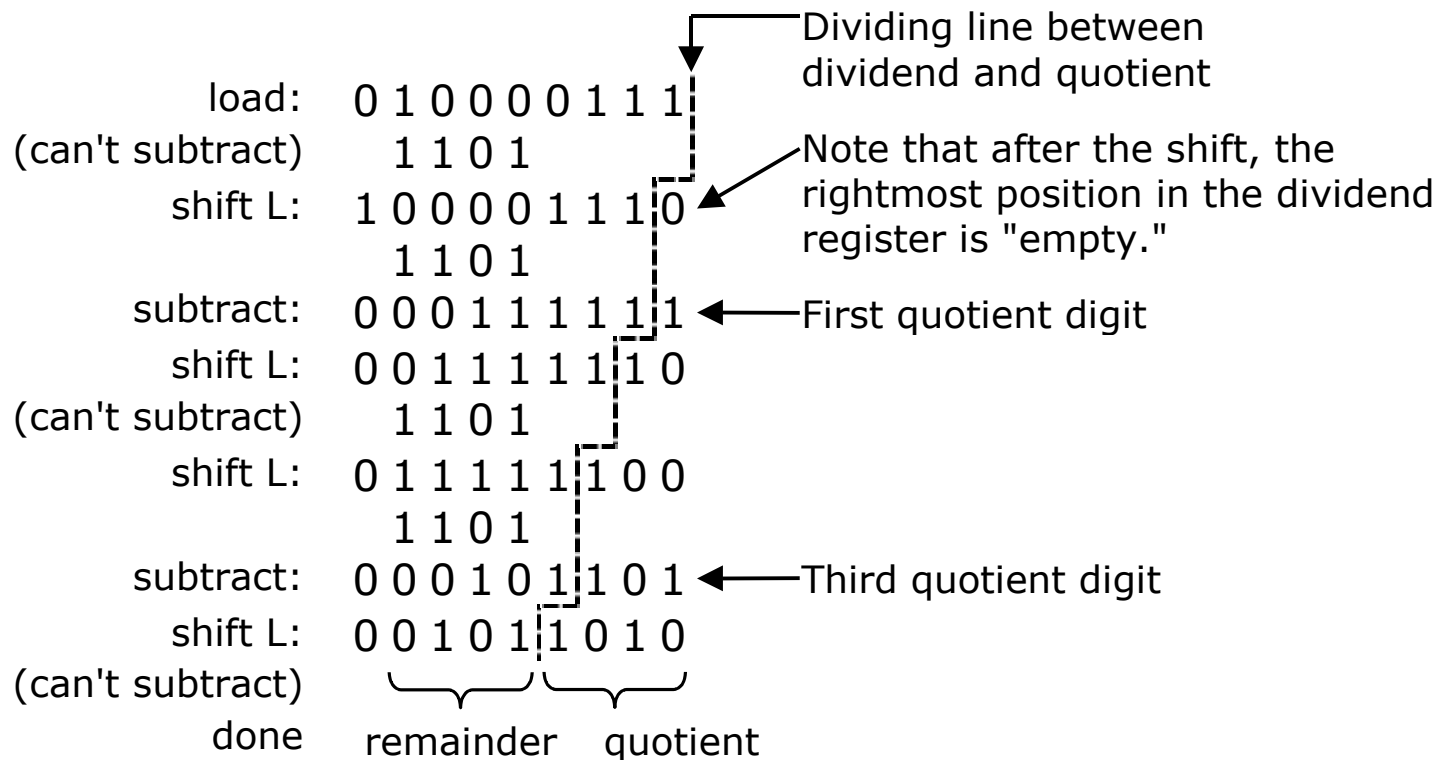

**Figure 4-19 Block Diagram for Parallel Binary Divider**

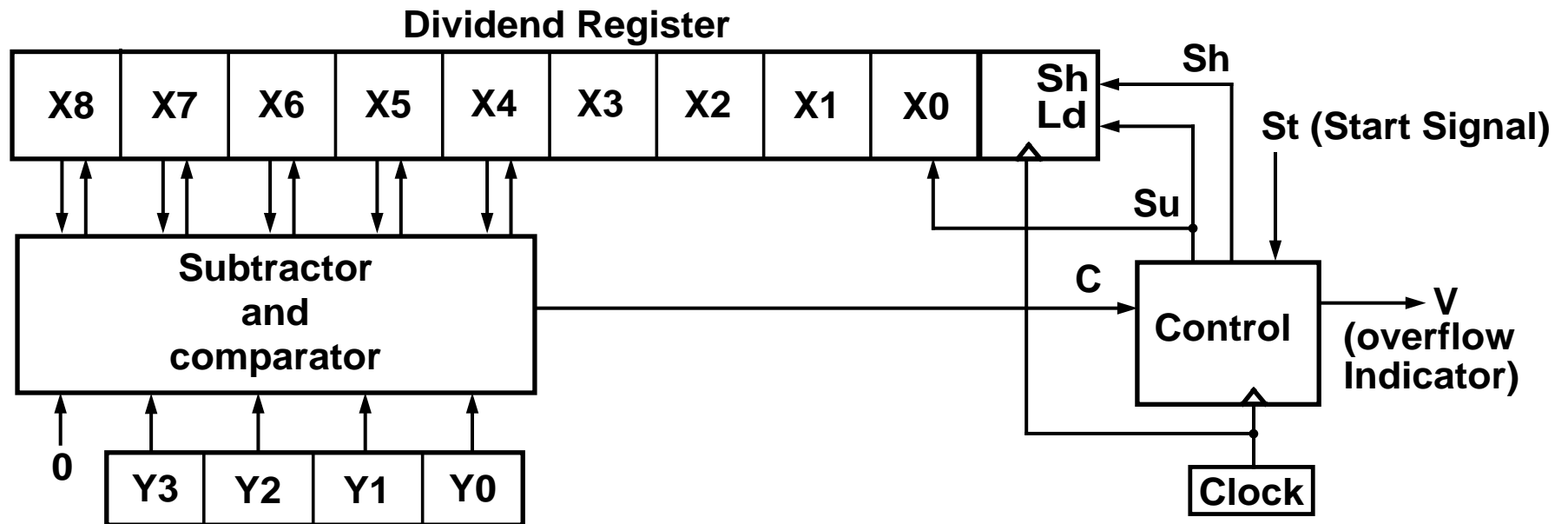

**Figure 4-20 State Diagram for Divider Control Circuit**

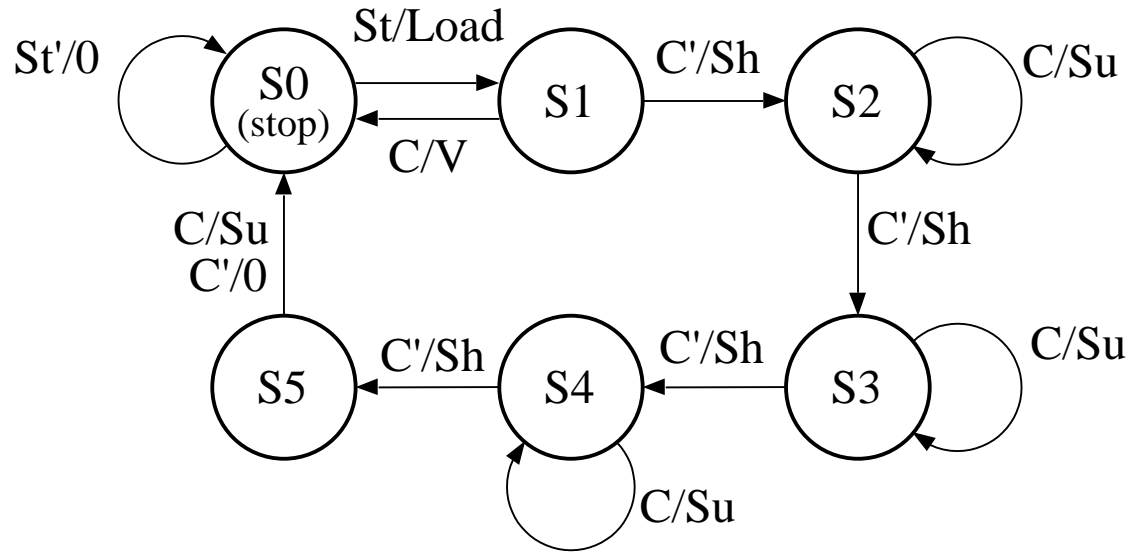


State	StC				StC			
	00	01	11	10	00	01	11	10
S0	S0	S0	S1	S1	0	0	Load	Load
S1	S2	S0	-	-	Sh	V	-	-
S2	S3	S2	-	-	Sh	Su	-	-
S3	S4	S3	-	-	Sh	Su	-	-
S4	S5	S4	-	-	Sh	Su	-	-
S5	S0	S0	-	-	0	Su	-	-

## Control Signals for Signed Divider


<i>LdU</i>	Load upper half of dividend from bus
<i>LdL</i>	Load lower half of dividend from bus
<i>Lds</i>	Load sign of dividend into sign flip-flop
<i>S</i>	Sign of dividend
<i>Cm1</i>	Complement dividend register (2's complement)
<i>Ldd</i>	Load divisor from bus
<i>Su</i>	Enable adder output onto bus (Ena) and load upper half of dividend from bus
<i>Cm2</i>	Enable complemeter (Cm2 equals the complement of the sign bit of the divisor, so that a positive divisor is complemented and a negative divisor is not)
<i>Sh</i>	Shift the dividend register left one place and increment the counter
<i>C</i>	Carry output from adder (If $C = 1$ , the divisor can be subtracted from the upper dividend.)
<i>St</i>	Start
<i>V</i>	Overflow
<i>Qneg</i>	Quotient will be negative ( $Qneg = 1$ when sign of dividend and divisor are different)



# Figure 4-21 Block Diagram for Signed Divider

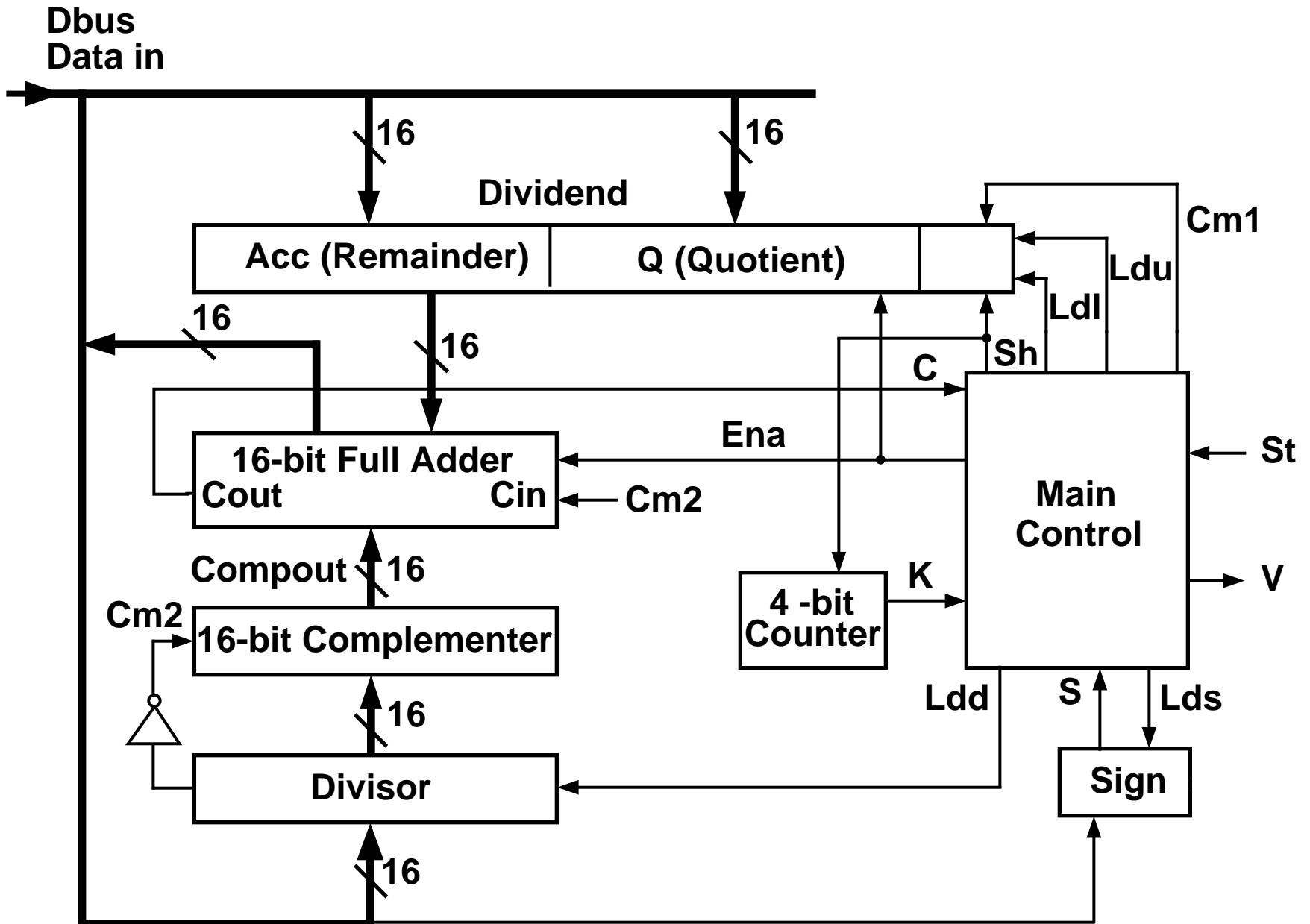

**Figure 4-22 State Graph for Signed Divider Control Network**

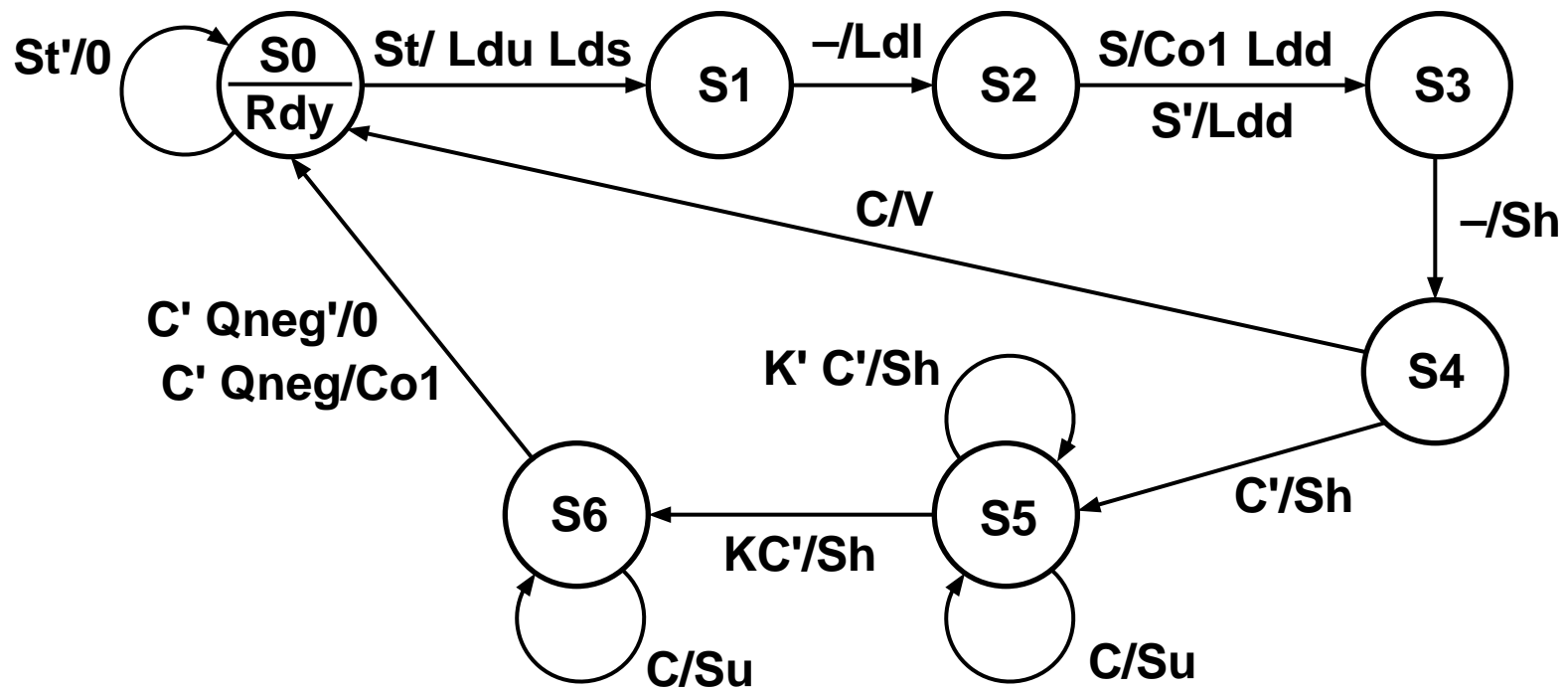

## Figure 4-23(a) VHDL Model of 32-bit Signed Divider

```
library BITLIB;
use BITLIB.bit_pack.all;
entity sdiv is
    port(Clk,St: in bit;
         Dbus: in bit_vector(15 downto 0); Quotient: out bit_vector(15 downto 0);
         V, Rdy: out bit);
end sdiv;
architecture Signdiv of Sdiv is
    constant zero_vector: bit_vector(31 downto 0):=(others=>'0');
    signal State: integer range 0 to 6; signal Count : integer range 0 to 15;
    signal Sign,C,NC: bit; signal Divisor,Sum,Compout: bit_vector(15 downto 0);
    signal Dividend: bit_vector(31 downto 0);
    alias Q: bit_vector(15 downto 0) is Dividend(15 downto 0);
    alias Acc: bit_vector(15 downto 0) is Dividend(31 downto 16);
begin
    compout <= divisor when divisor(15) = '1' -- concurrent statements
    else not divisor; -- 1's complementer
    Addvec(Acc,compout,not divisor(15),Sum,C,16); -- 16-bit adder
    Quotient <= Q; Rdy <= '1' when State=0 else '0';
```

## Figure 4-23(b) VHDL Model of 32-bit Signed Divider

```
process
begin
    wait until Clk = '1';           -- wait for rising edge of clock
    case State is
        when 0=>
            if St = '1' then
                Acc <= Dbus;         -- load upper dividend
                Sign <= Dbus(15); State <= 1;
                V <= '0'; Count <= 0; -- initialize overflow// initialize counter
            end if;
        when 1=>
            Q <= Dbus; State <= 2;   -- load lower dividend
        when 2=>
            Divisor <= Dbus;
            if Sign = '1' then       -- two's complement Dividend if necessary
                addvec(not Dividend,zero_vector,'1',Dividend,NC,32);
            end if; State <= 3;
        when 3=>
            Dividend <= Dividend(30 downto 0) & '0'; -- left shift
            Count <= Count+1; State <= 4;
        when 4 =>
            if C = '1' then         -- C
                v <= '1'; State <= 0;
            else                    -- C'
                Dividend <= Dividend(30 downto 0) & '0'; -- left shift
                Count <= Count+1; State <= 5;
            end if;
    end case;
end process;
```

## Figure 4-23(c) VHDL Model of 32-bit Signed Divider

```
    when 5 =>
        if C = '1' then
            ACC <= Sum;
            Q(0) <= '1';
        else
            Dividend <= Dividend(30 downto 0) & '0';
            if Count = 15 then
                count <= 0; State <= 6;
            else Count <= Count+1;
            end if;
        end if;
    when 6 =>
        if C = '1' then
            Acc <= Sum;
            Q(0) <= '1';
        else if (Sign xor Divisor(15)) = '1' then
            addvec(not Dividend, zero_vector, '1', Dividend, NC, 32);
        end if;
        state <= 0;
    end if;
end case;
end process;
end signdiv;
```

## Figure 4-24(a) Test Bench for Signed Divider

```
library BITLIB;
use BITLIB.bit_pack.all;
entity testsdiv is
end testsdiv;
architecture test1 of testsdiv is
component sdiv
    port(Clk,St: in bit;
        Dbus: in bit_vector(15 downto 0); Quotient: out bit_vector(15 downto 0);
        V, Rdy: out bit);
end component;
constant N: integer := 12;                                -- test sdiv1 N times
type arr1 is array(1 to N) of bit_vector(31 downto 0);
type arr2 is array(1 to N) of bit_vector(15 downto 0);
constant dividendarr: arr1 := (X"0000006F",X"07FF00BB",X"FFFFFFE08",
    X"FF80030A",X"3FFF8000",X"3FFF7FFF",X"C0008000",X"C0008000",
    X"C0008001",X"00000000",X"FFFFFFFF",X"FFFFFFFF");
constant divisorarr: arr2 := (X"0007", X"E005", X"001E", X"EFFA", X"7FFF", X"7FFF", X"7FFF",
    X"8000", X"7FFF", X"0001", X"7FFF", X"0000");
signal CLK, St, V, Rdy: bit; signal Dbus, Quotient, divisor: bit_vector(15 downto 0);
signal Dividend: bit_vector(31 downto 0); signal count: integer range 0 to N;
```

## Figure 4-24(b) Test Bench for Signed Divider

```
begin
  CLK <= not CLK after 10 ns;
  process
  begin
    for i in 1 to N loop
      St <= '1';
      Dbus <= dividendarr(i) (31 downto 16);
      wait until rising_edge(CLK);
      Dbus <= dividendarr(i) (15 downto 0);
      wait until rising_edge(CLK);
      Dbus <= divisorarr(i);
      St <= '0';
      dividend <= dividendarr(i);           -- save dividend for listing
      divisor <= divisorarr(i);           -- save divisor for listing
      wait until (Rdy = '1');
      count <= i;                          -- save index for triggering
    end loop;
  end process;
  sdiv1: sdiv port map(Clk, St, Dbus, Quotient, V, Rdy);
end test1;
```

## Figure 4-25 Simulation Test Results for Signed Divider

-- Command file to test results of signed divider  
list -hex -Notrigger dividend divisor Quotient V -Trigger count  
run 5300

ns	delta	dividend	divisor	quotient	v	count
0	+0	00000000	0000	0000	0	0
470	+3	0000006F	0007	000F	0	1
910	+3	07FF00BB	E005	BFFE	0	2
1330	+3	FFFFFFE08	001E	FFF0	0	3
1910	+3	FF80030A	EFFA	07FC	0	4
2010	+3	3FFF8000	7FFF	0000	1	5
2710	+3	3FFF7FFF	7FFF	7FFF	0	6
2810	+3	C0008000	7FFF	0000	1	7
3510	+3	C0008000	8000	7FFF	0	8
4210	+3	C0008001	7FFF	8001	0	9
4610	+3	00000000	0001	0000	0	A
5010	+3	FFFFFFFF	7FFF	0000	0	B
5110	+3	FFFFFFFF	0000	0002	1	C