

Figure 5-1 Components of an SM Chart

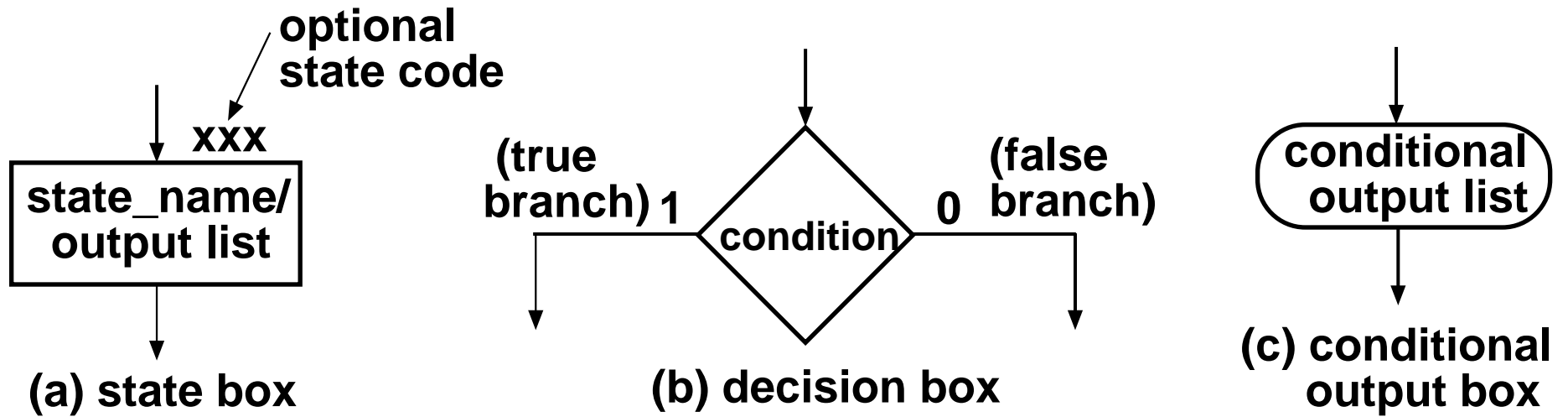


Figure 5-2 Example of an SM Block



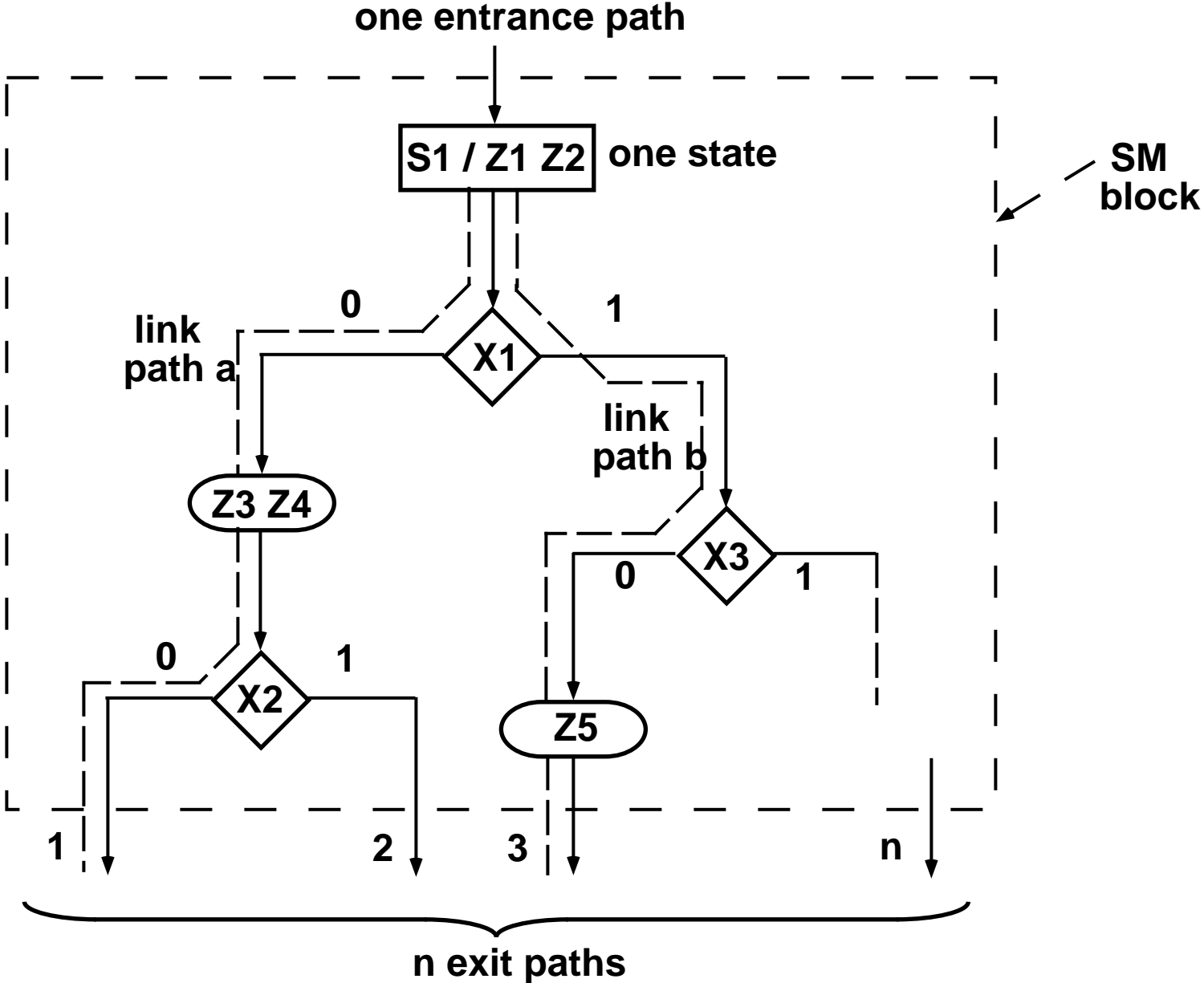


Figure 5-3 Equivalent SM Blocks

 

(a)

 

(b)

Figure 5-4: Equivalent SM Chart for a Combinational Network



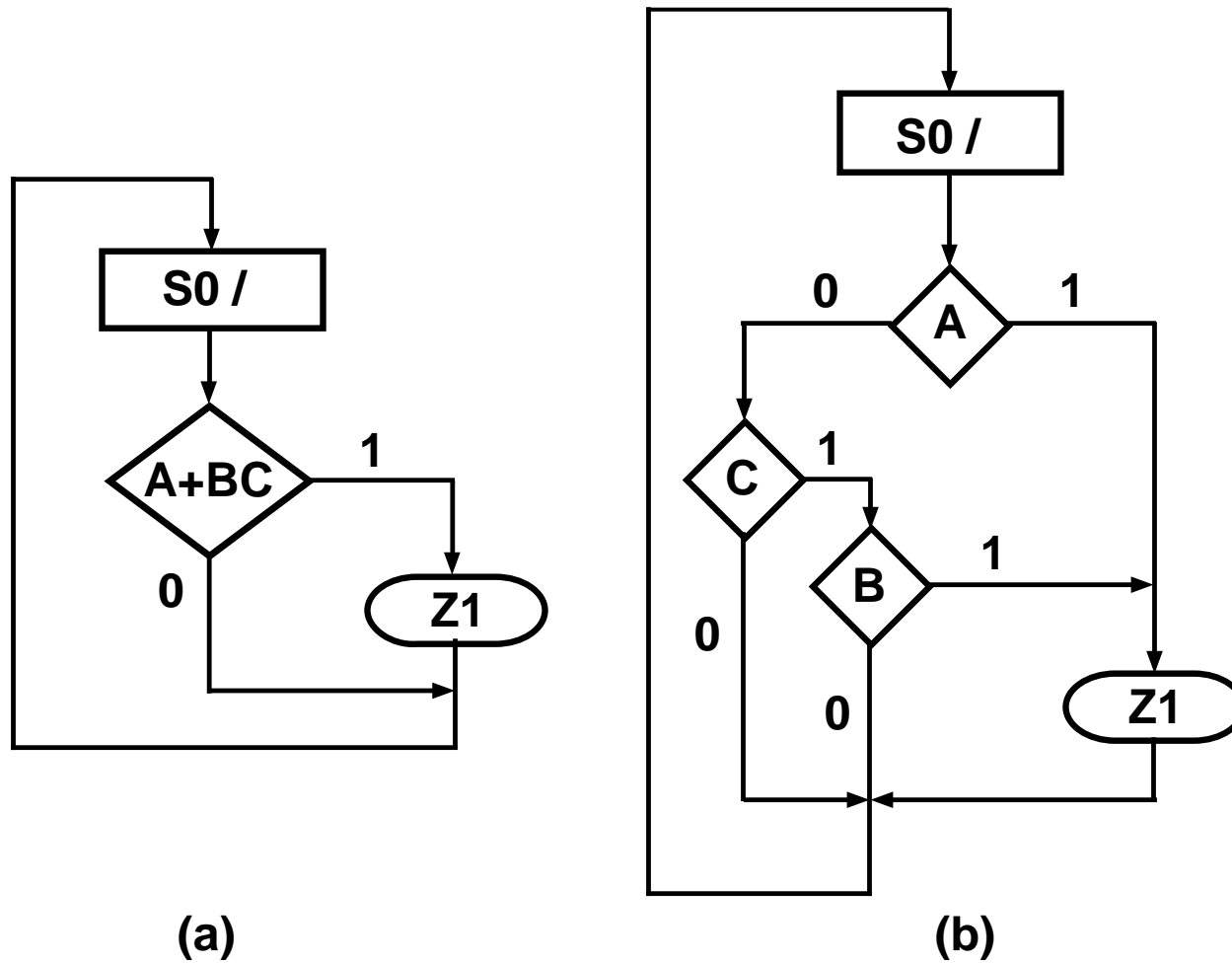


Figure 5-5 SM Block with Feedback

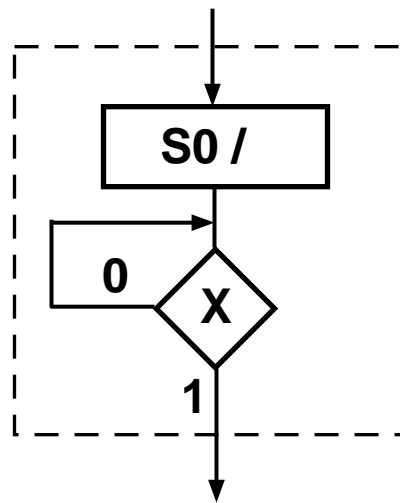


(a) incorrect

 


(b) correct

Figure 5-6 Equivalent SM Blocks

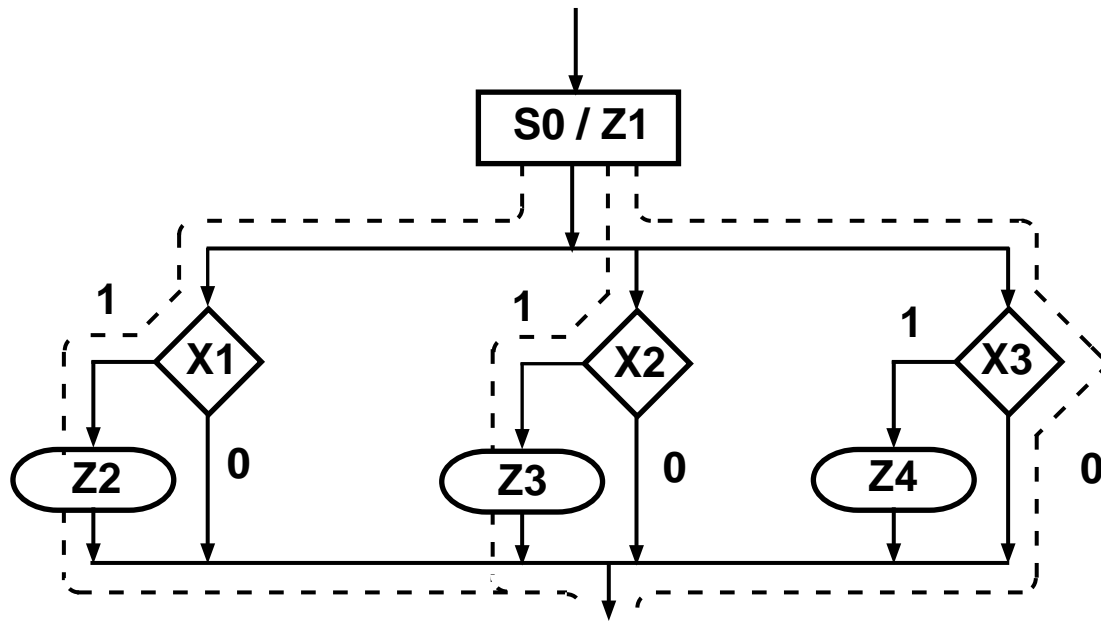

(a) Parallel form

 

(b) Serial form

Figure 5-7 Conversion of State Graph to an SM Chart

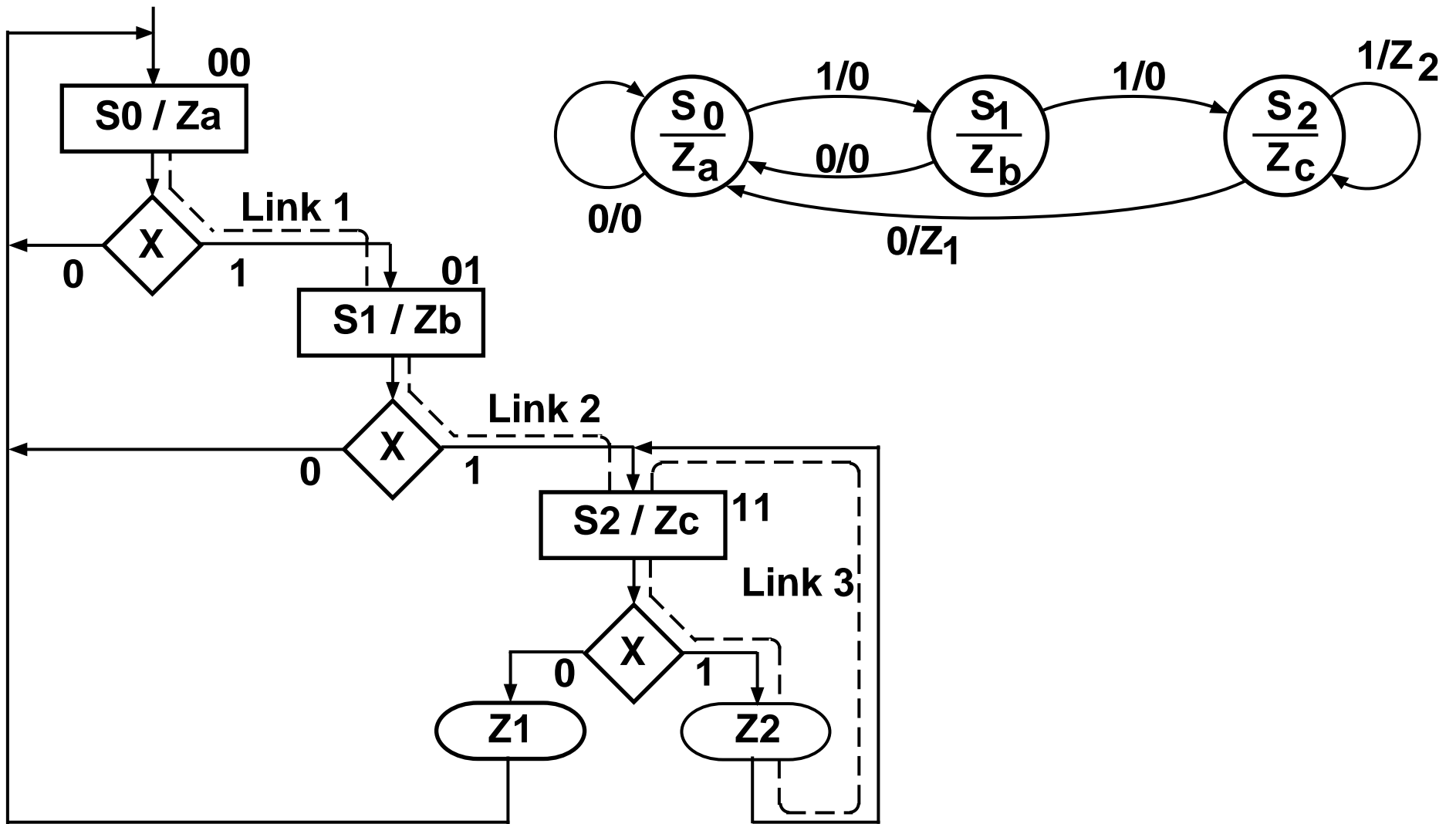


Figure 5-8 Timing Chart for Figure 5-7

 


Figure 5-9 SM Chart for Binary Multiplier

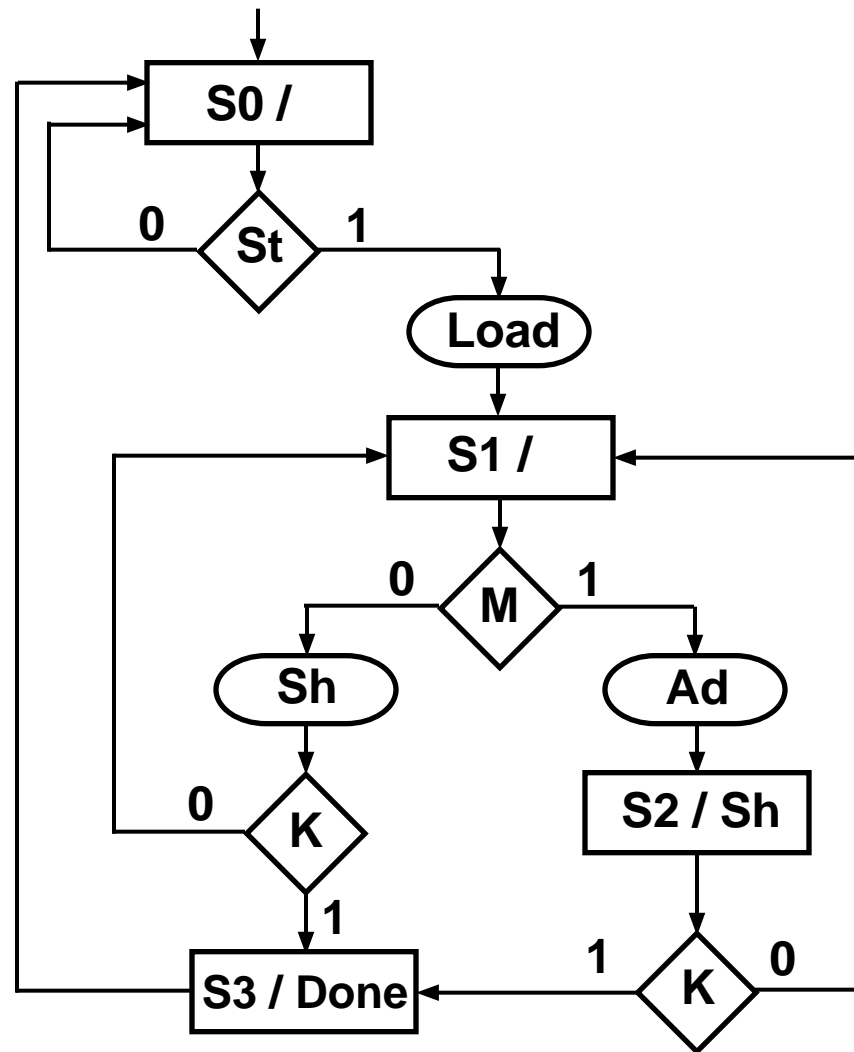


Figure 5-10(a) VHDL for SM Chart of Figure 5-9

```
entity Mult is
  port(CLK,St,K,M: in bit;
        Load,Sh,Ad,Done: out bit);
end mult;

architecture SMbehave of Mult is
  signal State, Nextstate: integer range 0 to 3;
begin
  process(St, K, M, State)                                -- start if state or inputs change
  begin
    Load <= '0'; Sh <= '0'; Ad <= '0';
    case State is
      when 0 => if St = '1' then                          -- St (state 0)
        Load <= '1'; Nextstate <= 1;
      else Nextstate <= 0;                                -- St'
      end if;
      when 1 => if M = '1' then                            -- M (state 1)
        Ad <= '1'; Nextstate <= 2;
      else                                              -- M'
        Sh <= '1'; if K = '1' then Nextstate <= 3;      -- K
      else Nextstate <= 1;                                -- K'
      end if;
      end if;
      when 2 => Sh <= '1';                                  -- (state 2)
        if K = '1' then Nextstate <= 3;                -- K
      else Nextstate <= 1;                                -- K'
      end if;
    end case;
  end process;
end SMbehave;
```

Figure 5-10(b) VHDL for SM Chart of Figure 5-9

```
        when 3 => Done <= '1';           -- (state 3)
            Nextstate <= 0;
        end case;
    end process;
    process(CLK)
    begin
        if CLK = '1' then
            State <= Nextstate;         -- update state on rising edge
        end if;
    end process;
end SMbehave;
```

Figure 5-11 Block Diagram for Dice Game

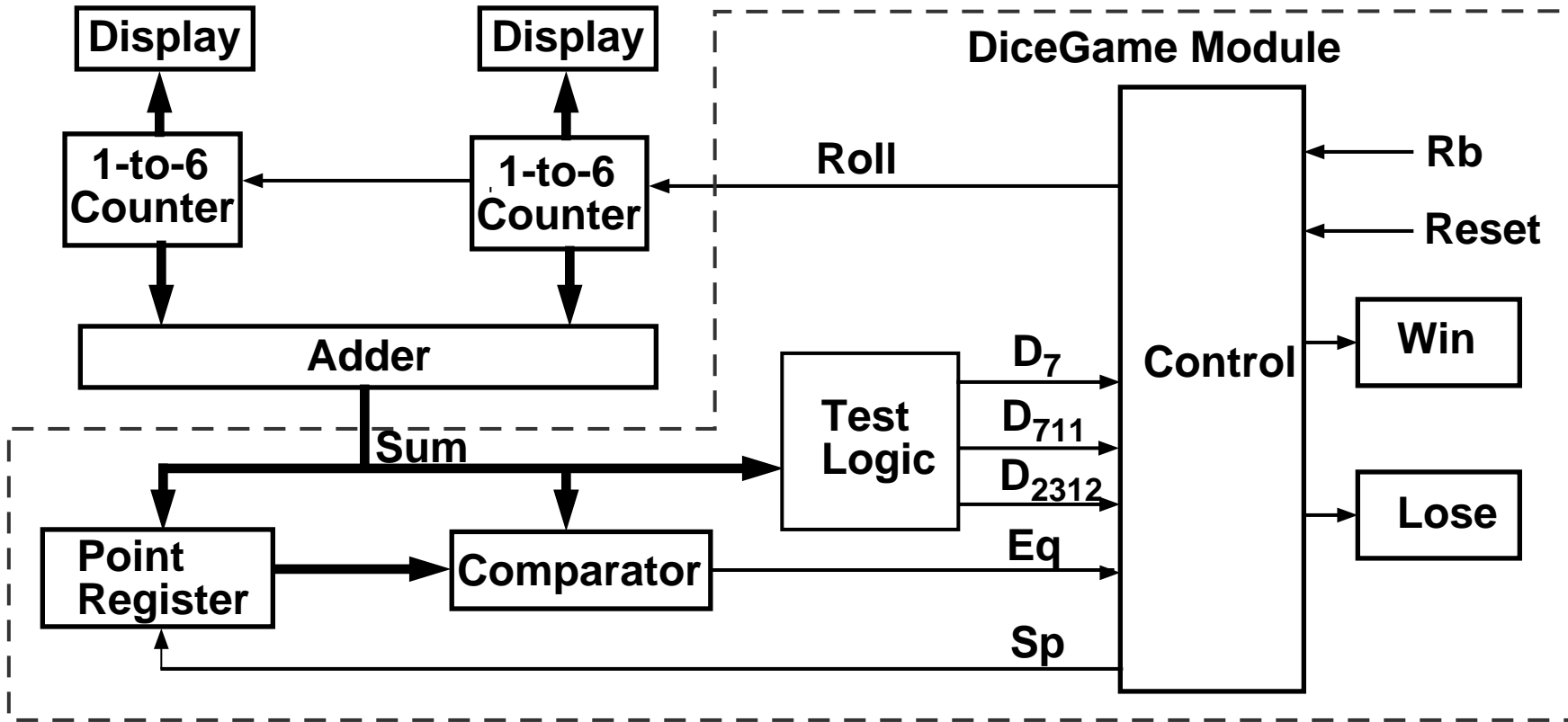


Figure 5-12 Flowchart for Dice Game

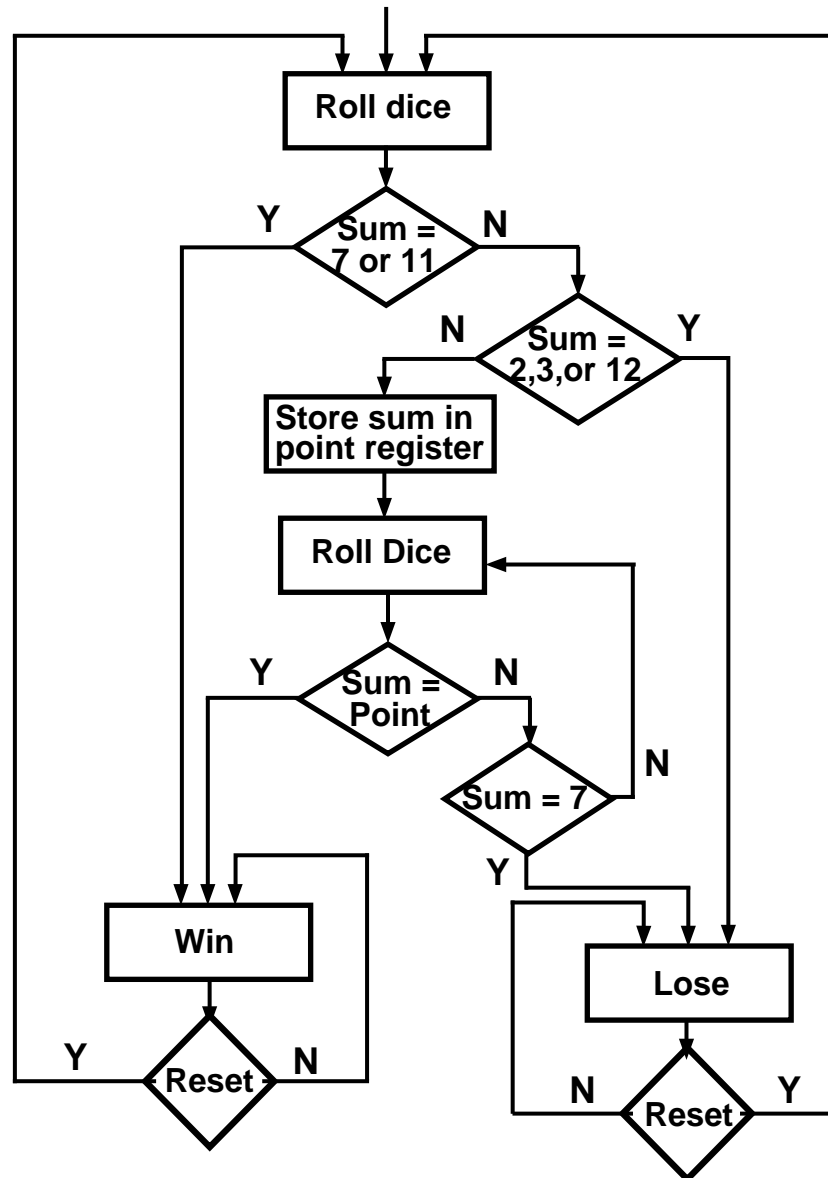


Figure 5-13 SM Chart for Dice Game

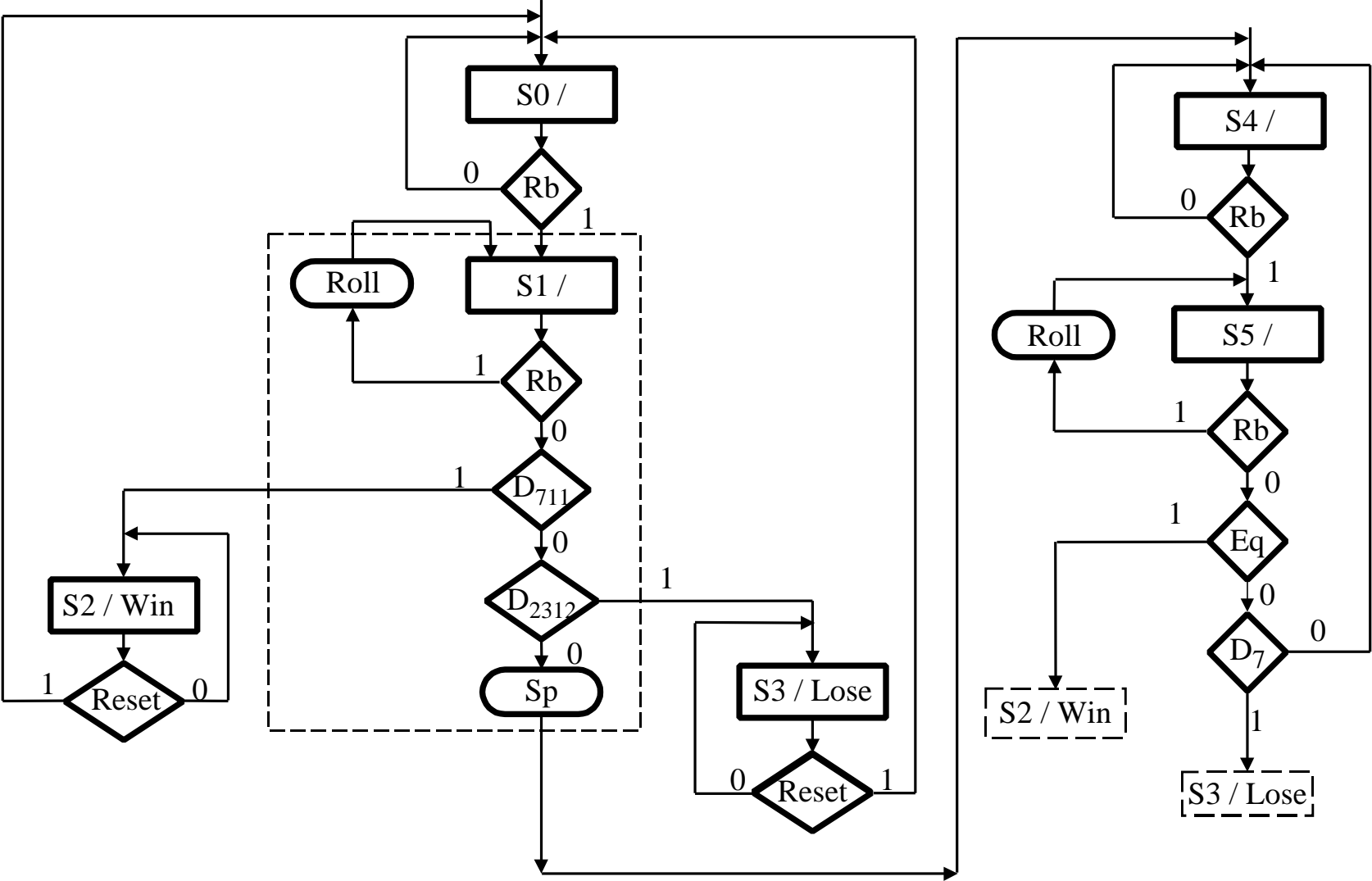


Figure 5-14 State Graph for Dice Game Controller

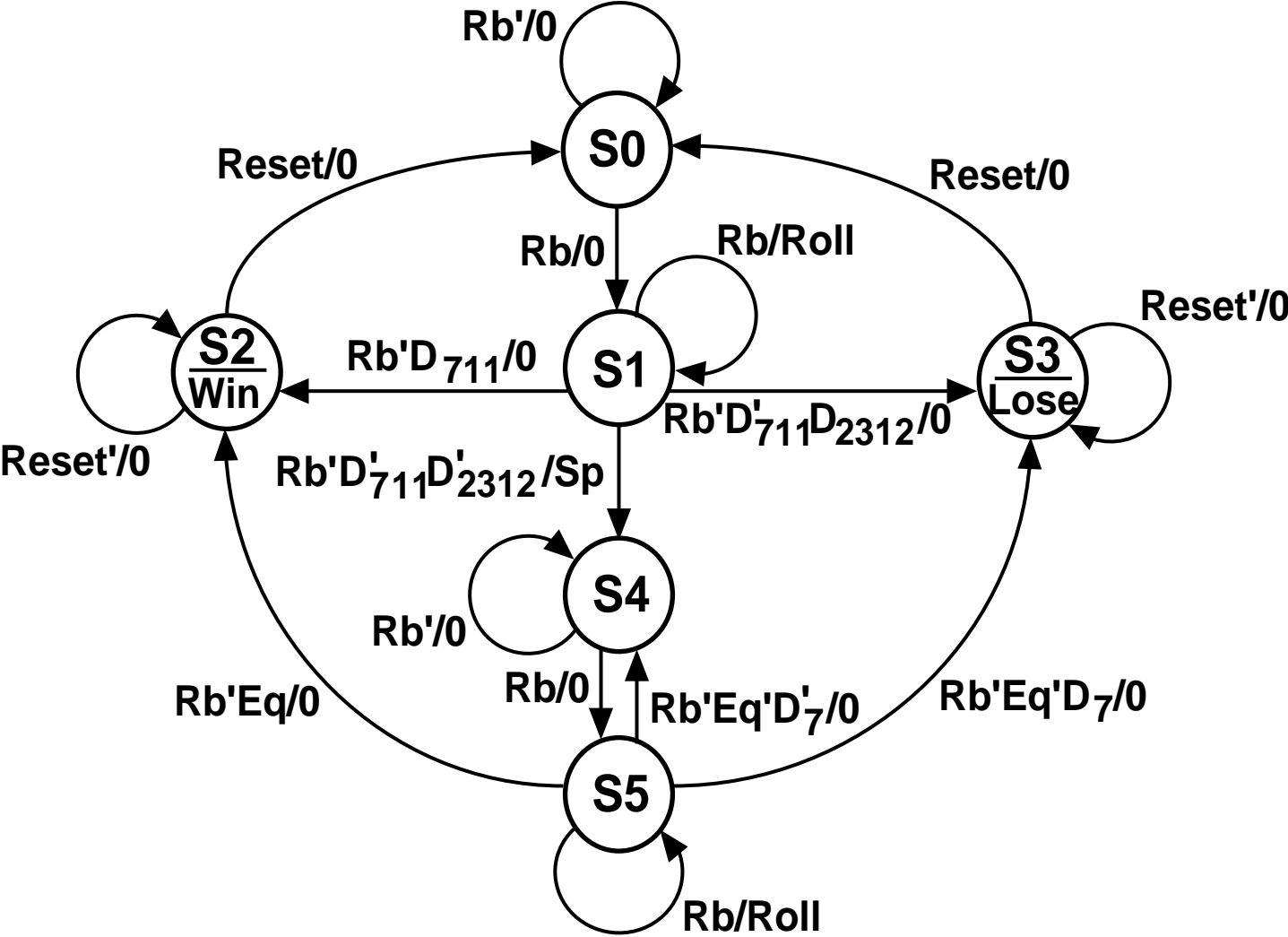


Figure 5-15(a) Behavioral Model for Dice Game

```
entity DiceGame is
    port (Rb, Reset, CLK: in bit;
          Sum: in integer range 2 to 12;
          Roll, Win, Lose: out bit);
end DiceGame;

library BITLIB;
use BITLIB.bit_pack.all;

architecture DiceBehave of DiceGame is
    signal State, Nextstate: integer range 0 to 5;
    signal Point: integer range 2 to 12;
    signal Sp: bit;
begin
    process(Rb, Reset, Sum, State)
    begin
        Sp <= '0'; Roll <= '0'; Win <= '0'; Lose <= '0';
        case State is
            when 0 => if Rb = '1' then Nextstate <= 1; end if;
            when 1 =>
                if Rb = '1' then Roll <= '1';
                    elsif Sum = 7 or Sum = 11 then Nextstate <= 2;
                    elsif Sum = 2 or Sum = 3 or Sum = 12 then Nextstate <= 3;
                    else Sp <= '1'; Nextstate <= 4;
                end if;
            when 2 => Win <= '1';
                if Reset = '1' then Nextstate <= 0; end if;
```


Figure 5-15(b) Behavioral Model for Dice Game

```
when 3 => Lose <= '1';  
    if Reset = '1' then Nextstate <= 0; end if;  
when 4 => if Rb = '1' then Nextstate <= 5; end if;  
when 5 =>  
    if Rb = '1' then Roll <= '1';  
        elsif Sum = Point then Nextstate <= 2;  
        elsif Sum = 7 then Nextstate <= 3;  
        else Nextstate <= 4;  
    end if;  
end case;  
end process;  
process(CLK)  
begin  
    if rising_edge(CLK) then  
        State <= Nextstate;  
        if Sp = '1' then Point <= Sum; end if;  
    end if;  
end process;  
end DiceBehave;
```

Figure 5-16 Dice Game with Test Bench

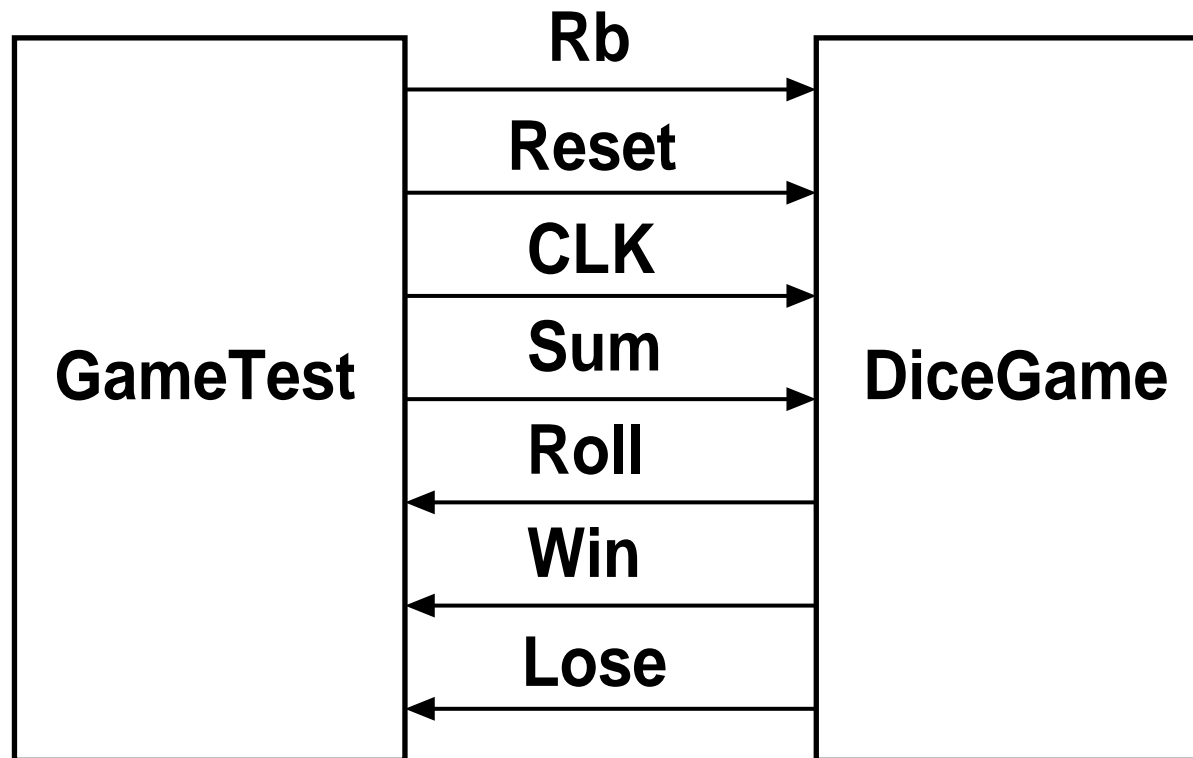


Figure 5-17 SM Chart for Dice Game Test

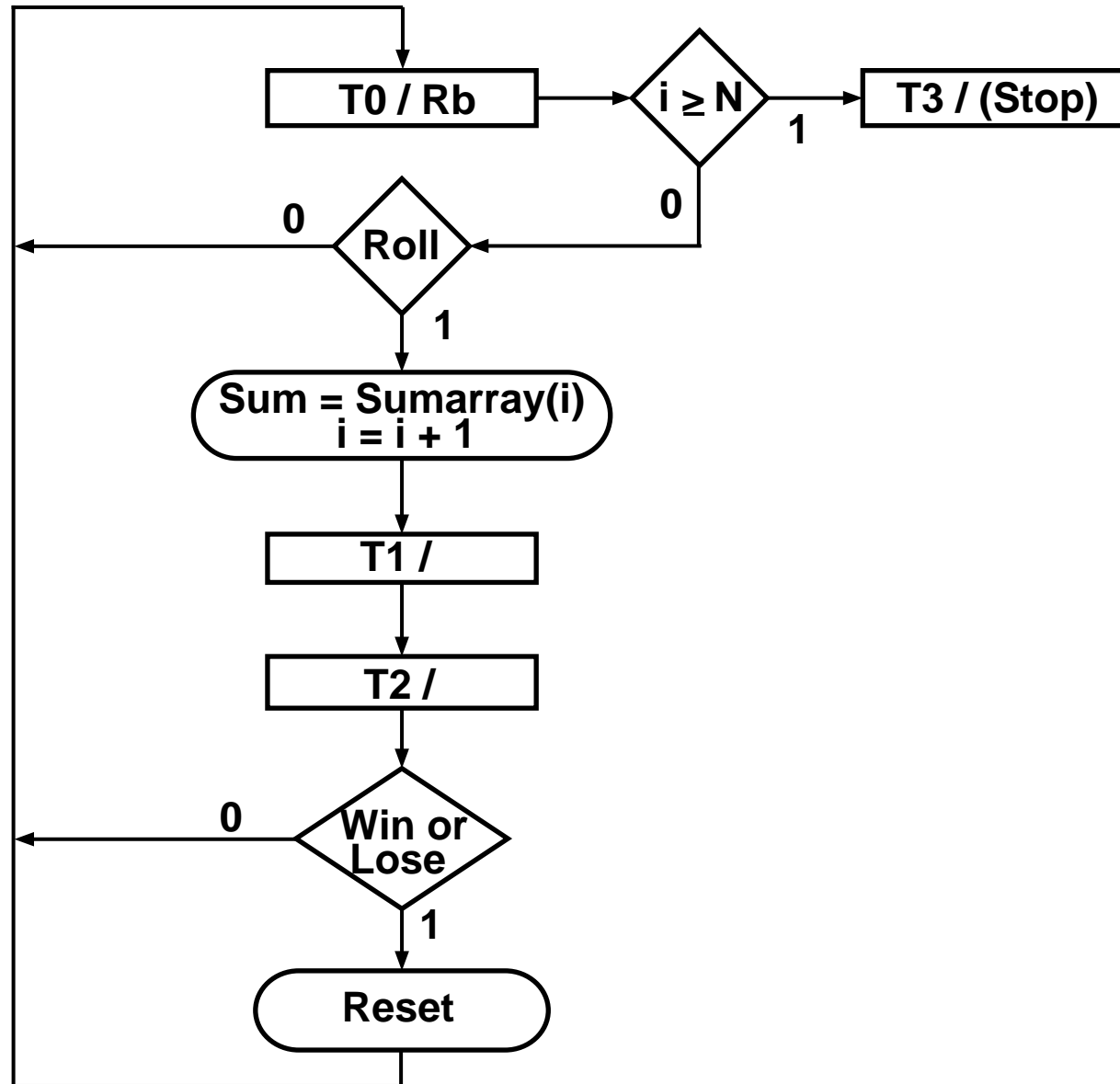


Figure 5-18(a) Dice Game Test Module

```
entity GameTest is  
    port(Rb, Reset: out bit; Sum: out integer range 2 to 12;  
        CLK: inout bit; Roll, Win, Lose: in bit);  
end GameTest;  
  
library BITLIB;  
use BITLIB.bit_pack.all;  
  
architecture dicetest of GameTest is  
    signal Tstate, Tnext: integer range 0 to 3;  
    signal Trig1: bit;  
    type arr is array(0 to 11) of integer;  
    constant Sumarray:arr := (7,11,2,4,7,5,6,7,6,8,9,6);  
    begin  
        CLK <= not CLK after 20 ns;
```

Figure 5-18(b) Dice Game Test Module

```
process(Roll, Win, Lose, Tstate)
  variable i: natural;                                -- i is initialized to 0
  begin
    case Tstate is
      when 0 => Rb <= '1';                            -- wait for Roll
        Reset <='0';
        if i>=12 then Tnext <= 3;
        elsif Roll = '1' then
          Sum <= Sumarray(i);
          i:=i+1;
          Tnext <= 1;
        end if;
      when 1 => Rb <= '0'; Tnext <= 2;
      when 2 => Tnext <= 0;
        Trig1 <= not Trig1;                            -- toggle Trig1
        if (Win or Lose) = '1' then Reset <= '1'; end if;
      when 3 => null;                                  -- Stop state
    end case;
  end process;
process(CLK)
  begin
    if CLK = '1' then
      Tstate <= Tnext;
    end if;
  end process;
end dicetest;
```

Figure 5-19 Tester for Dice Game

```
entity tester is  
end tester;  
architecture test of tester is  
component GameTest  
    port(Rb, Reset: out bit;  
        Sum: out integer range 2 to 12; CLK: inout bit; Roll, Win, Lose: in bit);  
end component;  
component DiceGame  
    port (Rb, Reset, CLK: in bit; Sum: in integer range 2 to 12 ; Roll, Win, Lose: out bit);  
end component;  
signal rb1, reset1, clk1, roll1, win1, lose1: bit; signal sum1: integer range 2 to 12;  
begin  
    Dice: Dicegame port map(rb1,reset1,clk1,sum1,roll1,win1,lose1);  
    Dicetest: GameTest port map(rb1,reset1,sum1,clk1,roll1,win1,lose1);  
end test;
```

Figure 5-20 Simulation and Command File for Dice Game Tester

```
list /dicetest/ trig1 -NOTrigger sum1 win1 lose1 /dice/point  
run 2000
```

ns	delta	trig1	sum1	win1	lose1	point
0	+0	0	2	0	0	2
100	+3	0	7	1	0	2
260	+3	0	11	1	0	2
420	+3	0	2	0	1	2
580	+2	1	4	0	0	4
740	+3	1	7	0	1	4
900	+2	0	5	0	0	5
1060	+2	1	6	0	0	5
1220	+3	1	7	0	1	5
1380	+2	0	6	0	0	6
1540	+2	1	8	0	0	6
1700	+2	0	9	0	0	6
1860	+3	0	6	1	0	6

Table 5-1 PLA Table for Multiplier Control

	A	B	St	M	K	A ⁺	B ⁺	Load	Sh	Ad	Done
S0	0	0	0	-	-	0	0	0	0	0	0
	0	0	1	-	-	0	1	1	0	0	0
S1	0	1	-	0	0	0	1	0	1	0	0
	0	1	-	0	1	1	1	0	1	0	0
	0	1	-	1	-	1	0	0	0	1	0
S2	1	0	-	-	0	0	1	0	1	0	0
	1	0	-	-	1	1	1	0	1	0	0
S3	1	1	-	-	-	0	0	0	0	0	1

$$A^+ = A'BM'K + A'BM + AB'K = A'B(M + K) + AB'K$$

$$B^+ = A'B'St + A'BM'(K'+K) + AB'(K'+K) = A'B'St + A'BM' + AB'$$

$$Sh = A'BM'(K'+K) + AB'(K'+K) = A'BM' + AB'$$

$$Load = A'B'St \quad Ad = A'B M \quad Done = A B$$

Figure 5-21 PLA Realization of Dice Game Controller

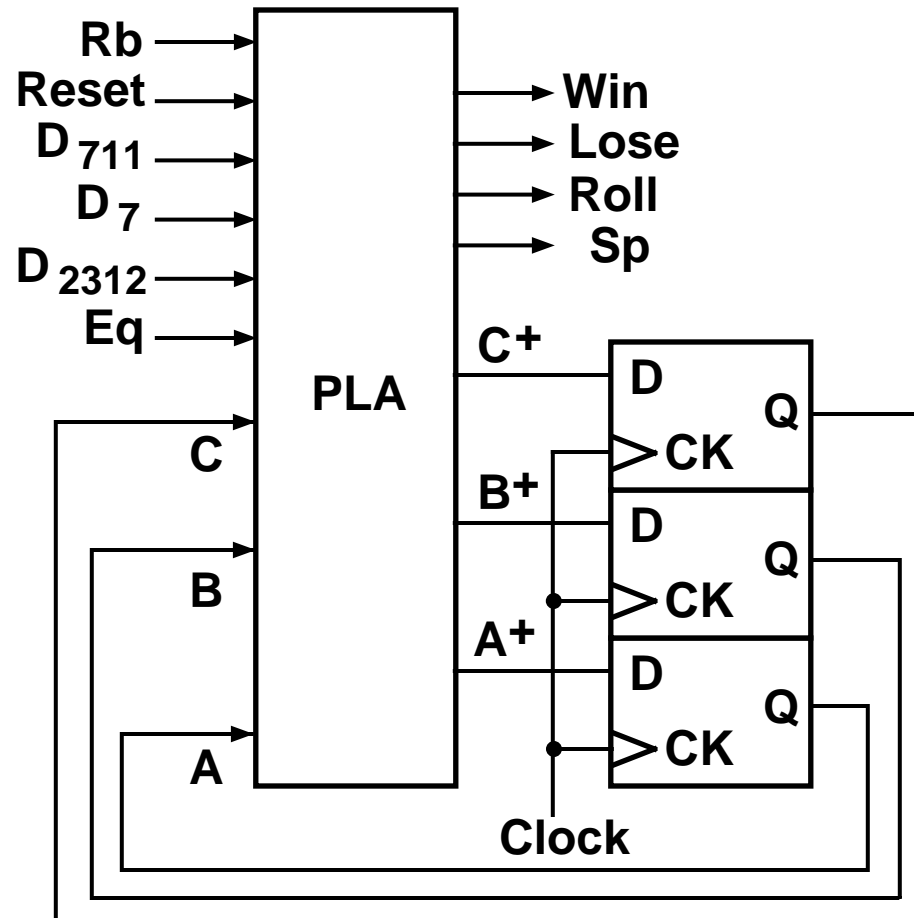


Figure 5-22 Maps Derived from Table 5-2

		AB			
		00	01	11	10
CRb	00			X	1
	01			X	1
	11			X	1
	10	E ₁		X	E ₂

$$E_1 = D'_{711} D'_{2312}$$

$$E_2 = D'_7 E_q'$$

		AB			
		00	01	11	10
CRb	00		R'	X	
	01		R'	X	
	11		R'	X	
	10	E ₃	R'	X	E ₄

R = Reset

$$E_3 = D_{711} + D'_{711} D'_{2312} = D_{711} + D'_{2312}$$

$$E_4 = E_q + D_7 E_q' = E_q + D_7$$

		AB			
		00	01	11	10
CRb	00		1	X	
	01		1	X	
	11			X	
	10			X	

Figure 5-23 Data Flow Model for Dice Game

```
library BITLIB;
use BITLIB.bit_pack.all;

architecture Dice_Eq of DiceGame is
    signal Sp,Eq,D7,D711,D2312: bit:= '0'; signal DA,DB,DC,A,B,C :bit:= '0';
    signal Point: integer range 2 to 12;
begin
process(Clk)
begin
    if rising_edge(Clk) then
        A <= DA; B <= DB; C <= DC;
        if Sp = '1' then Point <= Sum; end if;
    end if;
end process;
Win <= B and not C;
Lose <= B and C;
Roll <= not B and C and Rb;
Sp <= not A and not B and C and not Rb and not D711 and not D2312;
D7 <= '1' when Sum = 7 else '0';
D711 <= '1' when (Sum = 11) or (Sum = 7) else '0';
D2312 <= '1' when (Sum = 2) or (Sum = 3) or (Sum = 12) else '0';
Eq <= '1' when Point=Sum else '0';
DA <= (not A and not B and C and not Rb and not D711 and not D2312) or
    (A and not C) or (A and Rb) or (A and not D7 and not Eq);
DB <= ( (not A and not B and C and not Rb) and (D711 or D2312) )
    or (B and not Reset) or ( (A and C and not Rb) and (Eq or D7) );
DC <= (not B and Rb) or (not A and not B and C and not D711 and D2312) or
    (B and C and not Reset) or (A and C and D7 and not Eq);
end Dice_Eq;
```

Figure 5-24 Counter for Dice Game

```
entity Counter is  
    port(Clk, Roll: in bit;  
        Sum: out integer range 2 to 12);  
end Counter;  
  
architecture Count of Counter is  
signal Cnt1,Cnt2: integer range 1 to 6 := 1;  
begin  
    process (Clk)  
    begin  
        if Clk='1' then  
            if Roll='1' then  
                if Cnt1=6 then Cnt1 <= 1; else Cnt1 <= Cnt1+1; end if;  
                if Cnt1=6 then  
                    if Cnt2=6 then Cnt2 <= 1; else Cnt2 <= Cnt2+1; end if;  
                end if;  
            end if;  
        end process;  
        Sum <= Cnt1 + Cnt2;  
end Count;
```

Figure 5-25 Complete Dice Game

```
entity Game is  
    port (Rb, Reset, Clk: in bit;  
          Win, Lose: out bit);  
end Game;  
  
architecture Play1 of Game is  
    component Counter  
        port(Clk, Roll: in bit;  
            Sum: out integer range 2 to 12);  
    end component;  
    component DiceGame  
        port (Rb, Reset, CLK: in bit;  
            Sum: in integer range 2 to 12;  
            Roll, Win, Lose: out bit);  
    end component;  
    signal roll1: bit;  
    signal sum1: integer range 2 to 12;  
begin  
    Dice: Dicegame port map(Rb,Reset,Clk,sum1,roll1,Win,Lose);  
    Count: Counter port map(Clk,roll1,sum1);  
end Play1;
```

Figure 5-26 Control Network Using an input Mux to Select the Next State

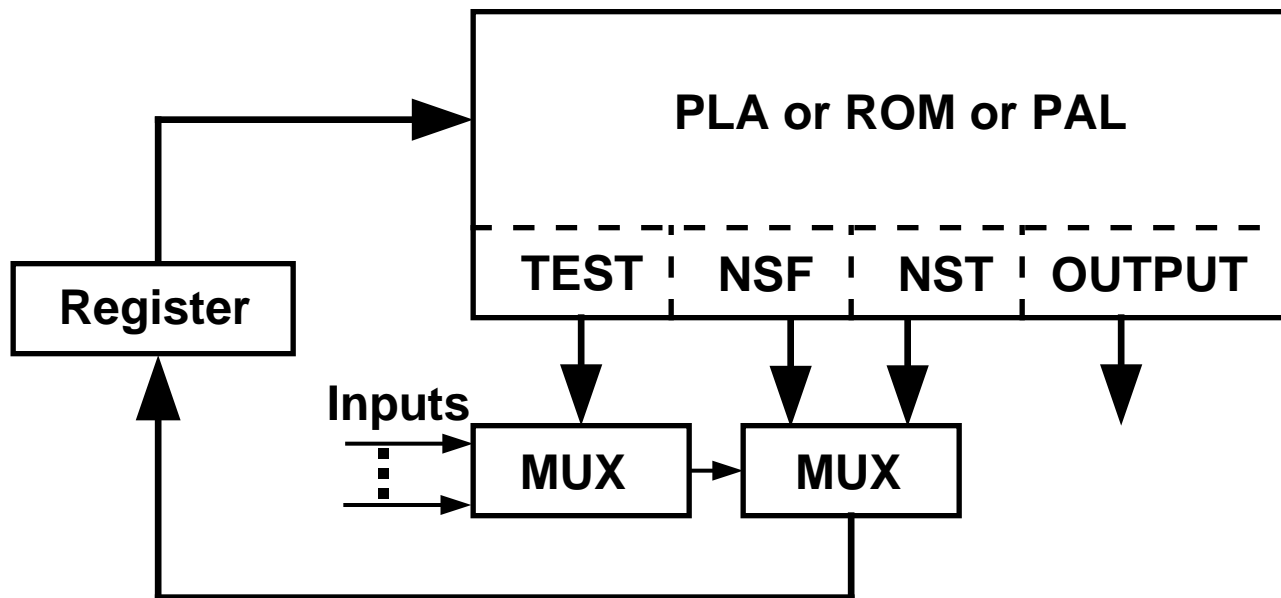


Figure 5-27(a) SM Chart with Moore Outputs and One Test per State

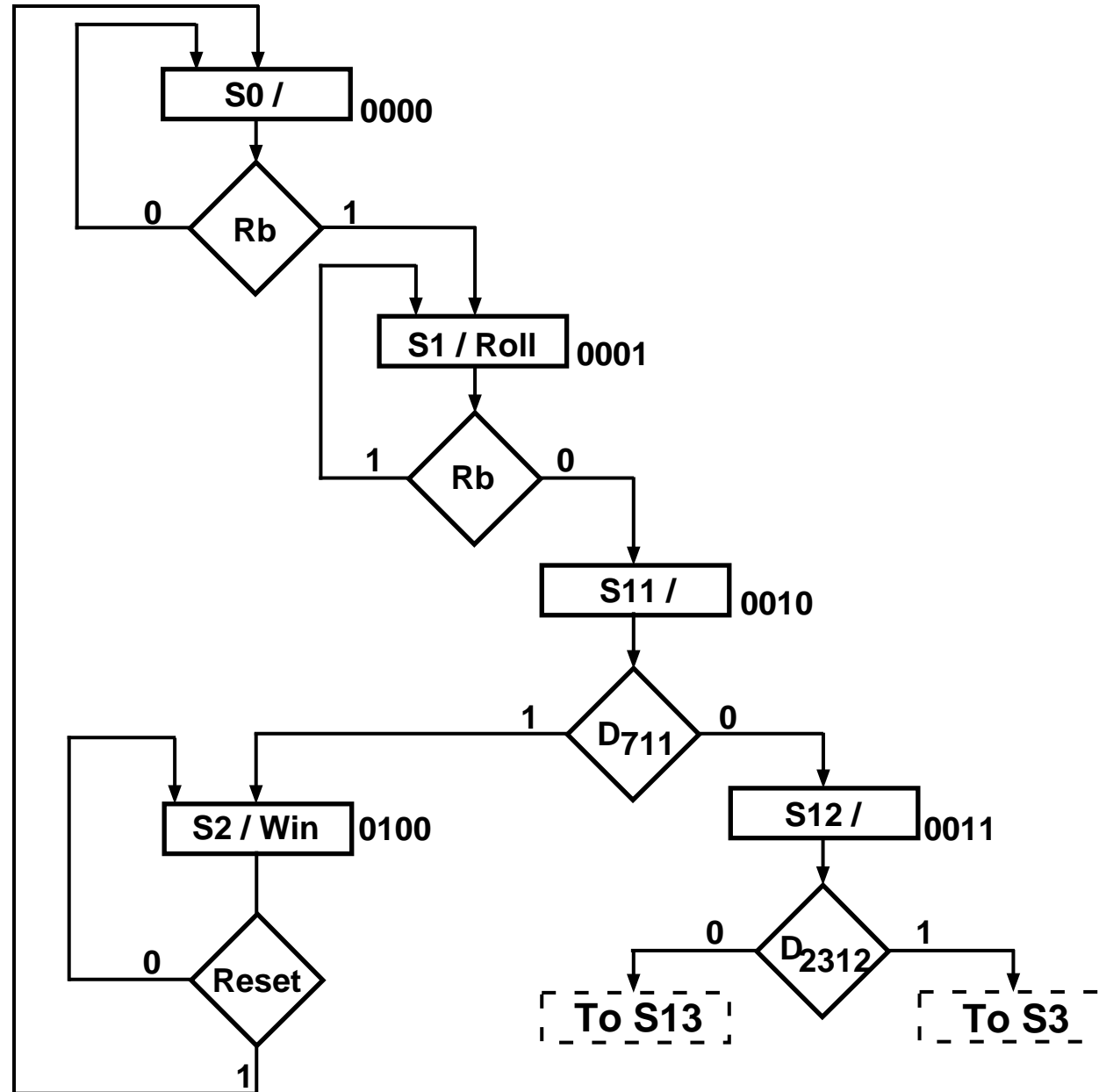


Figure 5-27(b) Chart with Moore Outputs and One Test per State

 


Figure 5-28 MUX for SM Chart of Figure 5-27

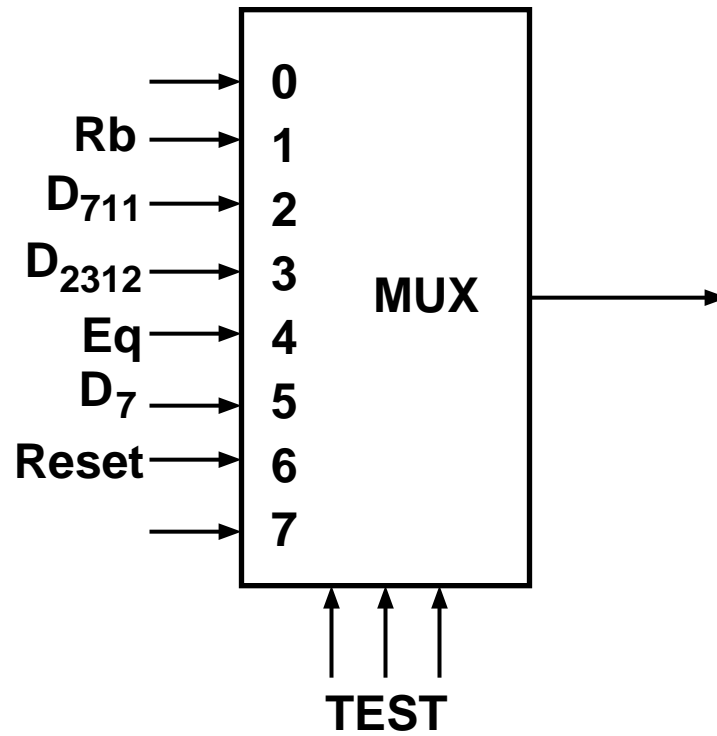


Table 5-3 PLA/ ROM Table for Figure 5-27

State	ABCD	TEST	NSF	NST	ROLL	Sp	Win	Lose
S0	0000	001	0000	0001	0	0	0	0
S1	0001	001	0010	0001	1	0	0	0
S11	0010	010	0011	0100	0	0	0	0
S12	0011	011	0101	0110	0	0	0	0
S2	0100	110	0100	0000	0	0	1	0
S13	0101	xxx	0111	0111	0	1	0	0
S3	0110	110	0110	0000	0	0	0	1
S4	0111	001	0111	1000	0	0	0	0
S5	1000	001	1001	1000	1	0	0	0
S51	1001	100	1010	0100	0	0	0	0
S52	1010	101	0111	0110	0	0	0	0

Figure 5-29 Control Network Using a Counter for the State Register

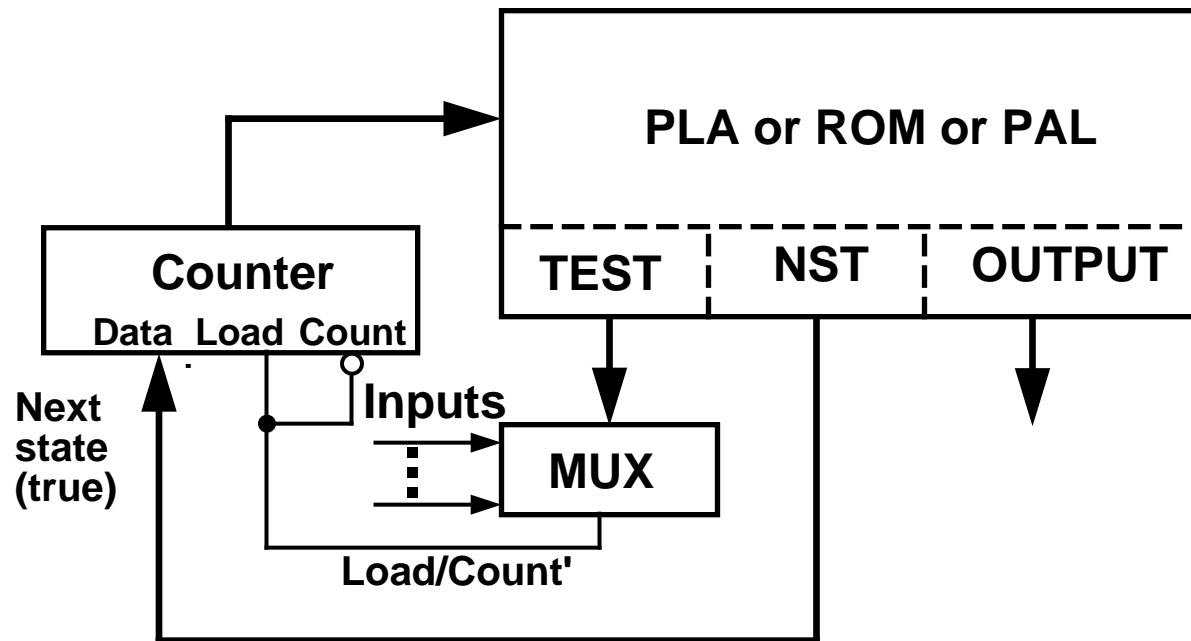


Figure 5-30(a) SM chart with Serial State Assignment and Added X-states

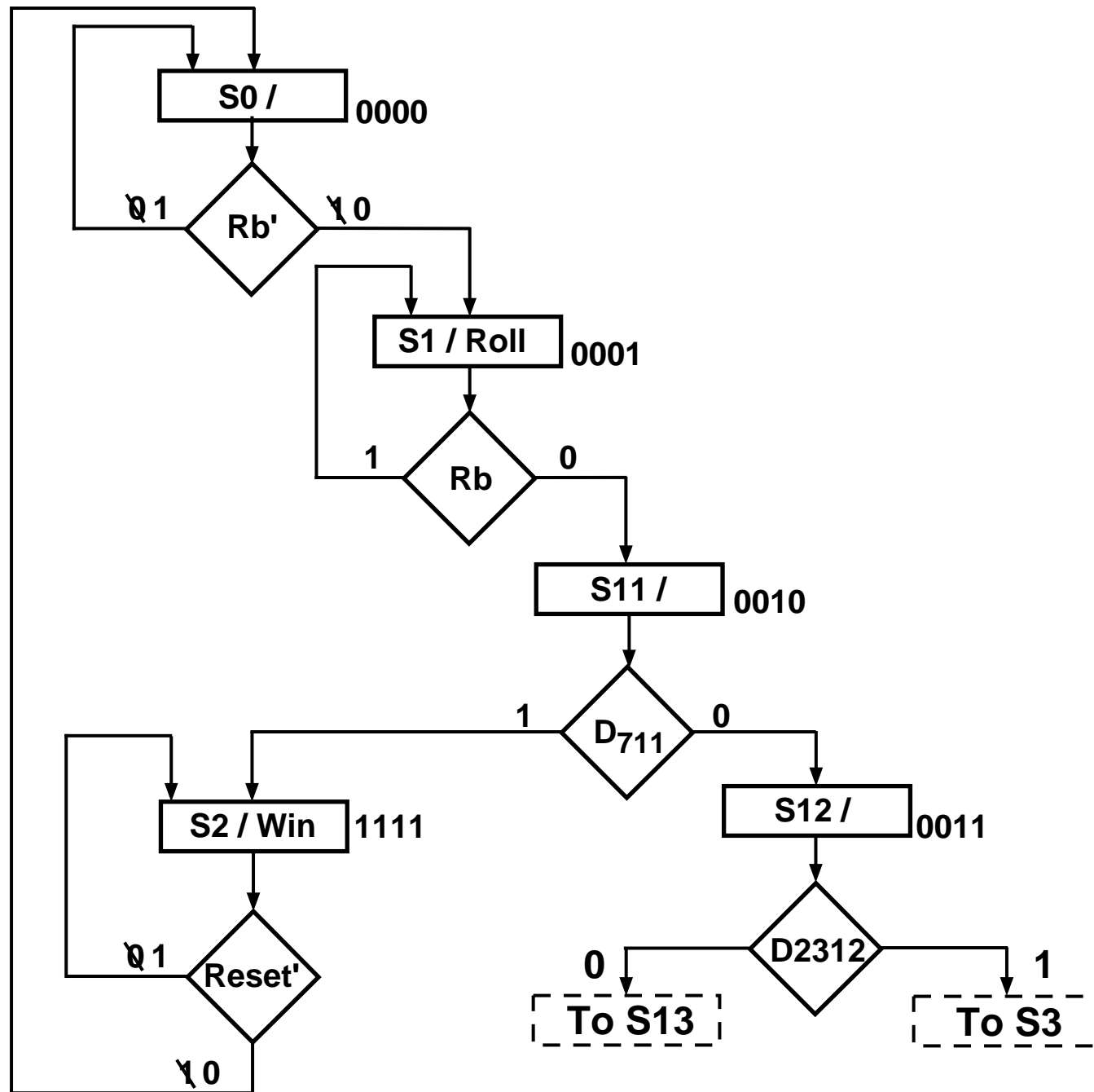


Figure 5-30(b) SM Chart with Serial State Assignment and Added X-state

 


Figure 5-31 MUX for SM chart of Figure 5-30

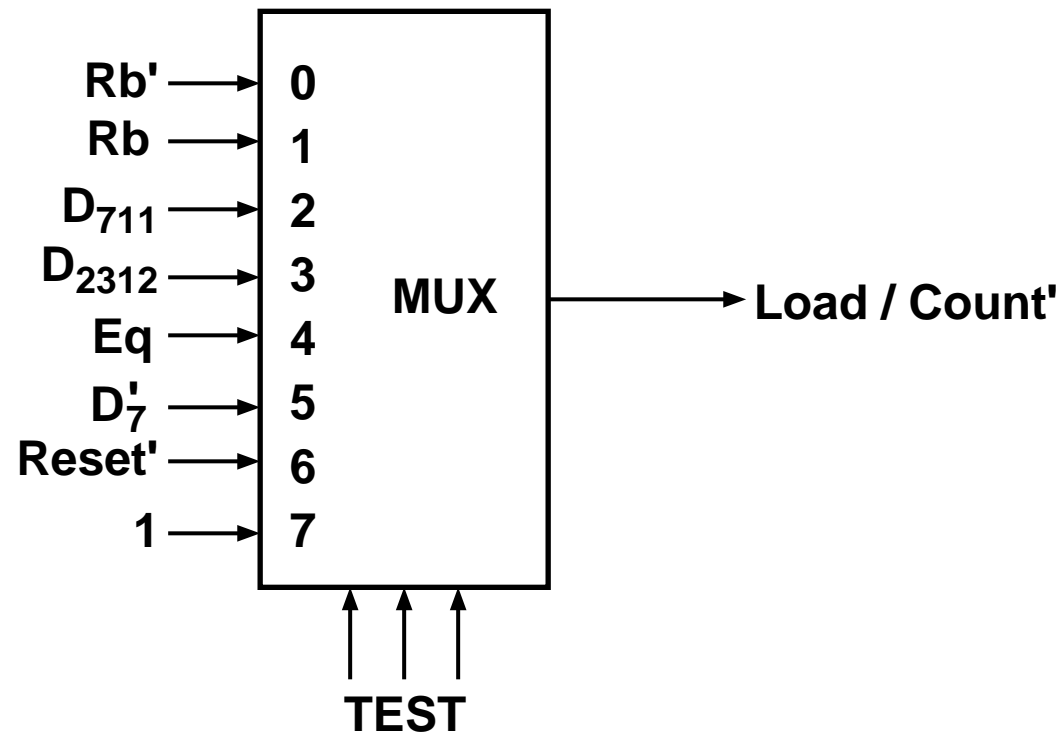


Table 5-4 PLA Table for Figure 5-31

State	ABCD	TEST	NST	ROLL	Sp	Win	Lose
S0	0000	000	0000	0	0	0	0
S1	0001	001	0001	1	0	0	0
S11	0010	010	1111	0	0	0	0
S12	0011	011	1001	0	0	0	0
S13	0100	111	0101	0	1	0	0
S4	0101	000	0101	0	0	0	0
S5	0110	001	0110	1	0	0	0
S51	0111	100	1111	0	0	0	0
S52	1000	101	0101	0	0	0	0
S3	1001	110	1001	0	0	0	1
Sx	1010	111	0000	0	0	0	0
S2	1111	110	1111	0	0	1	0

$$\text{Test}(2) = B C'D' + B C D + A$$

$$\text{Test}(1) = B'C + B C'D' + A D$$

$$\text{Test}(0) = A'B'D + B D' + A D'$$

$$\text{NST}(3) = A'B'C + C D + A D$$

$$\text{NST}(2) = A'C D' + B + A C'D'$$

$$\text{NST}(1) = A'C D' + B C$$

$$\text{NST}(0) = D + A'B'C + B C' + A C'$$

$$\text{Roll} = A'B'C'D + B C D'$$

$$\text{SP} = B C'D'$$

$$\text{Win} = A B$$

$$\text{Lose} = A B'D$$

Figure 5-32 SM Charts for Serially Linked State Machine

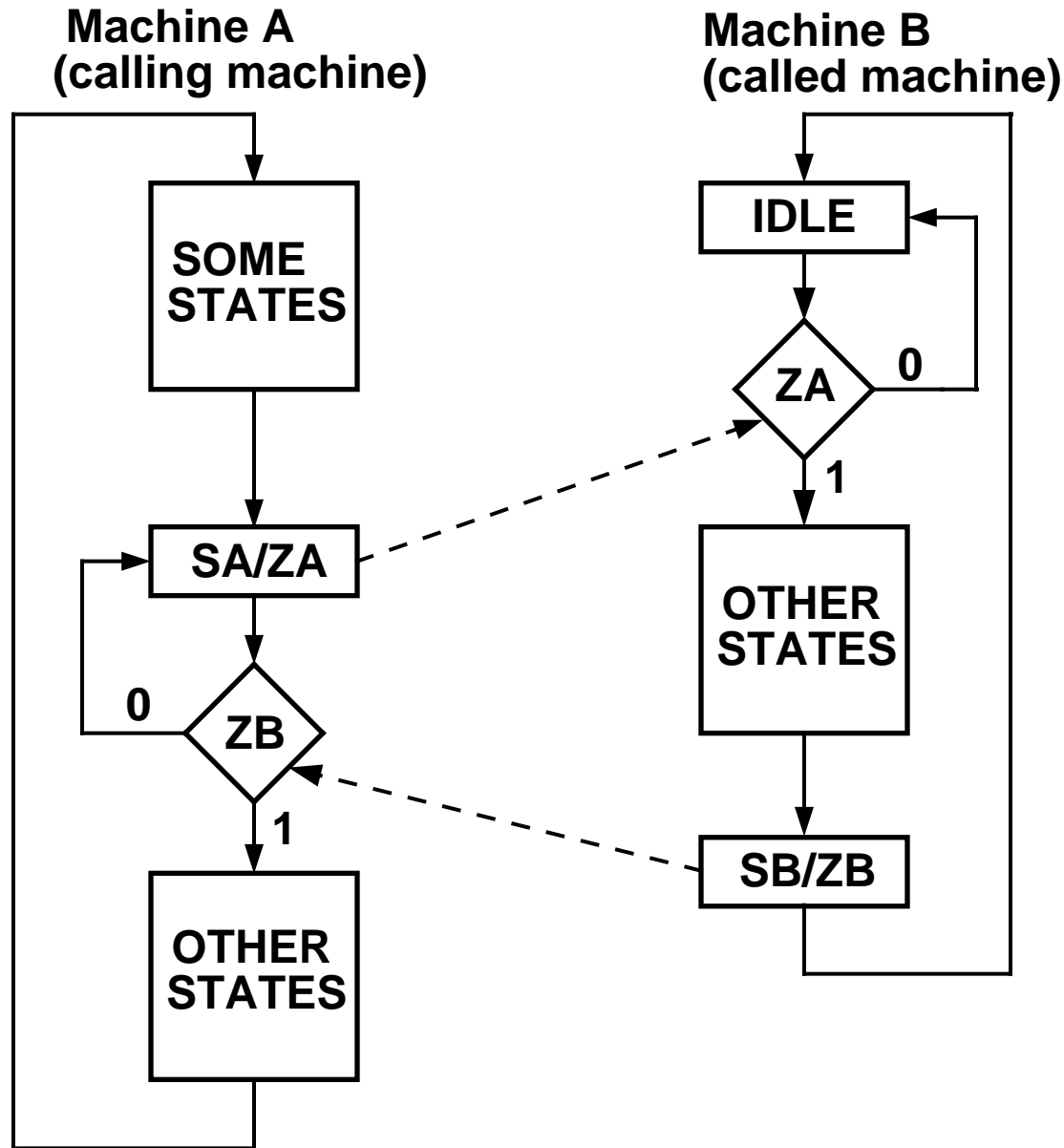


Figure 5-33a Linked SM Charts for Dice Game


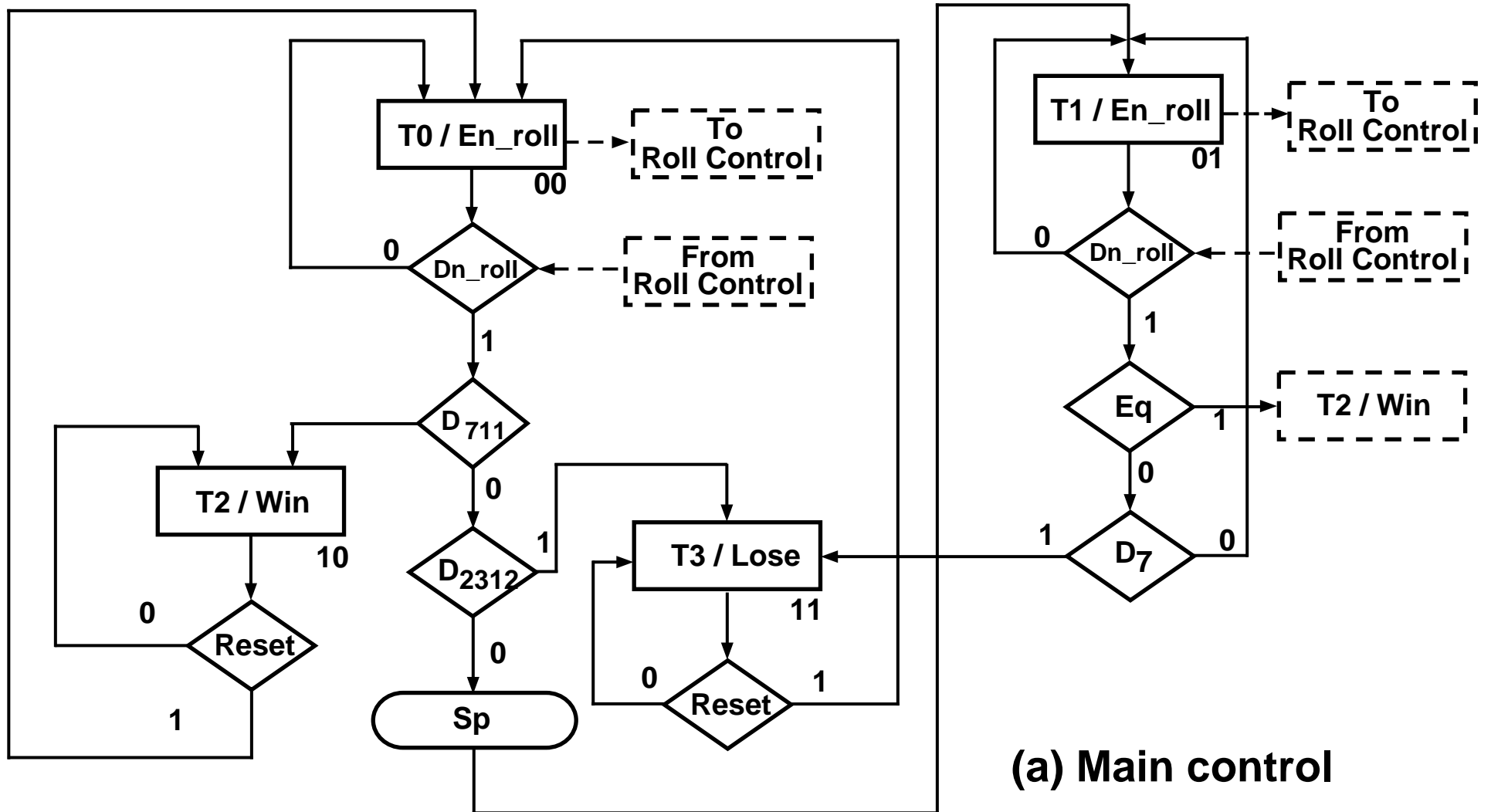


Figure 5-33b Linked SM Charts for Dice Game

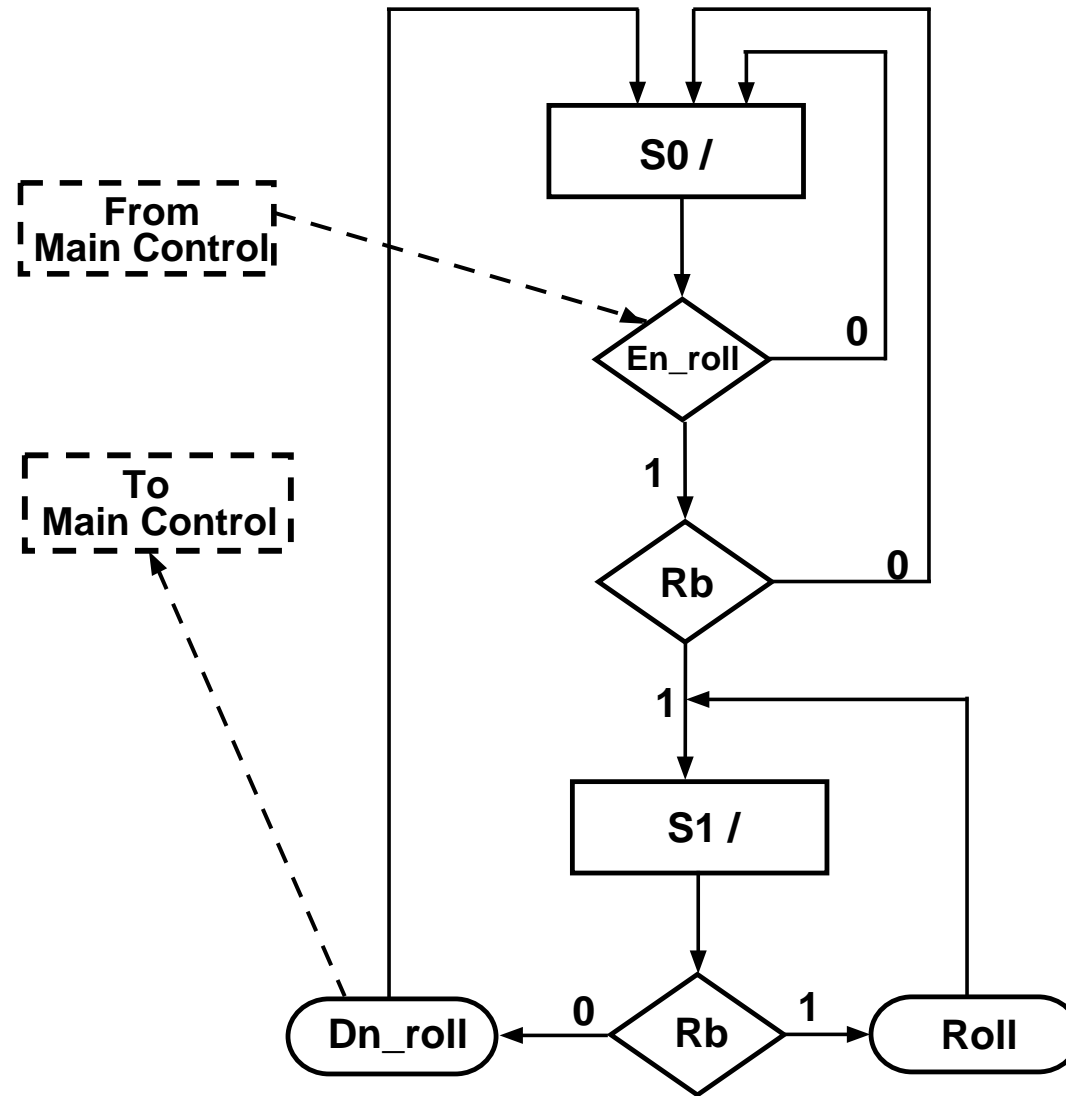

(b) Roll Control