

7.1 REPRESENTATION OF FLOATING-POINT NUMBERS

$$N = F \times 2^E$$

Examples of floating-point numbers using a 4-bit fraction and 4-bit exponent:

$$\begin{aligned} F = 0.101 \quad E = 0101 \quad N &= 5/8 \times 2^5 \\ F = 1.011 \quad E = 1011 \quad N &= -5/8 \times 2^{-5} \\ F = 1.000 \quad E = 1000 \quad N &= -1 \times 2^{-8} \end{aligned}$$

Normalization

$$\begin{aligned} \text{Unnormalized:} \quad F = 0.0101 \quad E = 0011 \quad N &= 5/16 \times 2^3 = 5/2 \\ \text{Normalized:} \quad F = 0.101 \quad E = 0010 \quad N &= 5/8 \times 2^2 = 5/2 \end{aligned}$$

$$\begin{aligned} \text{Unnormalized:} \quad F = 1.11011 \quad E = 1100 \quad N &= -5/32 \times 2^{-4} = -5 \times 2^{-9} \\ \text{(shift F left)} \quad F = 1.1011 \quad E = 1011 \quad N &= -5/16 \times 2^{-5} = -5 \times 2^{-9} \\ \text{Normalized} \quad F = 1.011 \quad E = 1010 \quad N &= -5/8 \times 2^{-6} = -5 \times 2^{-9} \end{aligned}$$

Representation of Zero

$$F = 0.000, \quad E = 1000 \quad \text{or} \quad 0.000 \times 2^{-8}$$

Figure 7-1 Flowchart for Floating-Point Multiplication

 


Figure 7-2(a) Exponent Adder and Fraction Multiplier

 


Figure 7-2(b) Exponent Adder and Fraction Multiplier

 


Figure 7-3 SM Chart for floating-Point Multiplication

 


Figure 7-4 State Graph for Multiplier Control

 


Figure 7-5(a) VHDL Code for Floating-Point Multiplier

```
library BITLIB;
use BITLIB.bit_pack.all;
entity FMUL is
    port (CLK, St: in bit; F1,E1,F2,E2: in bit_vector(3 downto 0);
          F: out bit_vector(6 downto 0); V, done:out bit);
end FMUL;
architecture FMULB of FMUL is
    signal A, B, C: bit_vector(3 downto 0);           -- fraction registers
    signal X, Y: bit_vector(4 downto 0);           -- exponent registers
    signal Load, Adx, Mdone, SM8, RSF, LSF, NC: bit; signal AdSh, Sh, Cm: bit;
    signal PS1, NS1: integer range 0 to 3;         -- present and next state
    signal State, Nextstate: integer range 0 to 4; -- mulitplier control state
    alias M: bit is B(0); constant one:bit_vector(4 downto 0):="00001";
    constant neg_one:bit_vector(4 downto 0):="11111";
begin
main_control: process
    begin
    Load <= '0'; Adx <= '0';                       -- clear control signals
    SM8 <= '0'; RSF <= '0'; LSF <= '0';
    case PS1 is
        when 0 => done<='0'; V<='0';              -- clear outputs
            if St = '1' then Load <= '1'; NS1 <= 1; F <= "0000000"; end if;
        when 1 => Adx <= '1'; NS1 <= 2;
```

Figure 7-5(b) VHDL Code for Floating-Point Multiplier

```
when 2 => if Mdone = '1' then -- wait for multiply
    if A = "0000" then SM8 <= '1'; -- zero fraction
    elsif A = "0100" and B = "0000" then -- fraction overflow
        RSF <= '1'; -- shift AB right
    elsif A(2) = A(1) then -- test for unnormalized
        LSF <= '1'; -- shift AB left
    end if; NS1 <= 3;
end if;
when 3 => --test for exp overflow
    if X(4) /= X(3) then V <= '1'; else V <= '0'; end if;
done <= '1';
F <= A(2 downto 0) & B; --output fraction
if ST = '0' then NS1<=0; end if;
end case;
wait until rising_edge(CLK);
PS1 <= NS1;
wait for 0 ns; --wait for state change
end process main_control;
mul2c: process --2's complement multiply
begin
AdSh <= '0'; Sh <= '0'; Cm <= '0'; --clear control signals
case State is
when 0=> Mdone <= '0'; --start multiply
if Adx='1' then
    if M = '1' then AdSh <= '1'; else Sh <= '1'; end if;
    Nextstate <= 1;
end if;
```

Figure 7-5(c) VHDL Code for Floating-Point Multiplier

```
    when 1 | 2 => --add/shift state
    if M = '1' then AdSh <= '1'; else Sh <= '1'; end if;
    Nextstate <= State + 1;
    when 3 =>
    if M = '1' then Cm <= '1'; AdSh <= '1'; else Sh <='1'; end if;
    Nextstate <= 4;
    when 4 => Mdone <= '1'; Nextstate <= 0;
end case;
wait until rising_edge(CLK);
State <= Nextstate;
wait for 0 ns; --wait for state change
end process mul2c;

update: process --update registers
variable addout: bit_vector(4 downto 0);
begin
wait until rising_edge(CLK);
if Cm = '0' then addout := add4(A,C,'0');
    else addout := add4(A, not C,'1'); end if; --add 2's comp. of C
if Load = '1' then X <= E1(3)&E1; Y <= E2(3)&E2;
    A <= "0000"; B <= F2; C <= F1; end if;
if ADX = '1' then addvec(X,Y,'0',X,NC,5); end if;
if SM8 = '1' then X <= "11000"; end if;
if RSF = '1' then A <= '0'&A(3 downto 1);
    B <= A(0)&B(3 downto 1);
    addvec(X,one,'0',X,NC,5); end if; -- increment X
```

Figure 7-5(d) VHDL Code for Floating-Point Multiplier

```
if LSF = '1' then  
    A <= A(2 downto 0)&B(3); B <= B(2 downto 0)&'0';  
    addvec(X,neg_one,'0',X,NC,5); end if;           -- decrement X  
if AdSh = '1' then  
    A <= (C(3) xor Cm) & addout(3 downto 1);      -- load shifted adder  
    B <= addout(0) & B(3 downto 1); end if;      -- output into A & B  
if Sh = '1' then  
    A <= A(3) & A(3 downto 1);                    -- right shift A & B  
    B <= A(0) & B(3 downto 1);                    -- with sign extend  
end if;  
end process update;  
end FMULB;
```

Figure 7-6(a) Test Data for Floating-Point Multiply

```
list f x f1 e1 f2 e2 v done
force f1 0111 0, 1001 200, 1000 400, 0000 600, 0111 800
force e1 0001 0, 1001 200, 0111 400, 1000 600, 0111 800
force f2 0111 0, 1001 200, 1000 400, 0000 600, 1001 800
force e2 1000 0, 0001 200, 1001 400, 1000 600, 0001 800
force st 1 0, 0 20, 1 200, 0 220, 1 400, 0 420, 1 600, 0 620, 1 800, 0 820
force clk 0 0, 1 10 -repeat 20
run 1000
```

Figure 7-6(b) Simulation Results for Floating-Point Multiply

ns	delta	f	x	f1	e1	f2	e2	v	done	
0	+0	0000000	00000	0000	0000	0000	0000	0	0	
0	+1	0000000	00000	0111	0001	0111	1000	0	0	$(0.111 \times 2^1) \times (0.111 \times 2^{-8})$
10	+1	0000000	00001	0111	0001	0111	1000	0	0	
30	+1	0000000	11001	0111	0001	0111	1000	0	0	
150	+2	0110001	11001	0111	0001	0111	1000	0	1	$= 0.110001 \times 2^{-7}$
170	+2	0000000	11001	0111	0001	0111	1000	0	0	
200	+0	0000000	11001	1001	1001	1001	0001	0	0	$(1.001 \times 2^{-7}) \times (1.001 \times 2^1)$
250	+1	0000000	11010	1001	1001	1001	0001	0	0	
370	+2	0110001	11010	1001	1001	1001	0001	0	1	$= 0.110001 \times 2^{-6}$
390	+2	0000000	11010	1001	1001	1001	0001	0	0	
400	+0	0000000	11010	1000	0111	1000	1001	0	0	$(1.000 \times 2^7) \times (1.000 \times 2^{-7})$
430	+1	0000000	00111	1000	0111	1000	1001	0	0	
450	+1	0000000	00000	1000	0111	1000	1001	0	0	
570	+1	0000000	00001	1000	0111	1000	1001	0	0	
570	+2	0100000	00001	1000	0111	1000	1001	0	1	$= 0.100000 \times 2^1$
590	+2	0000000	00001	1000	0111	1000	1001	0	0	
600	+0	0000000	00001	0000	1000	0000	1000	0	0	$(0.000 \times 2^{-8}) \times (0.000 \times 2^{-8})$
630	+1	0000000	11000	0000	1000	0000	1000	0	0	
650	+1	0000000	10000	0000	1000	0000	1000	0	0	
770	+1	0000000	11000	0000	1000	0000	1000	0	0	
770	+2	0000000	11000	0000	1000	0000	1000	0	1	$= 0.0000000 \times 2^{-8}$
790	+2	0000000	11000	0000	1000	0000	1000	0	0	
800	+0	0000000	11000	0111	0111	1001	0001	0	0	$(0.111 \times 2^7) \times (1.001 \times 2^1)$
830	+1	0000000	00111	0111	0111	1001	0001	0	0	
850	+1	0000000	01000	0111	0111	1001	0001	0	0	
970	+2	1001111	01000	0111	0111	1001	0001	1	1	$= 1.001111 \times 2^8$ (overflow)
990	+2	0000000	01000	0111	0111	1001	0001	0	0	

Figure 7-7 Bus Structure for Floating-Point Multiplier

 


Figure 7-8(a) Top-level Schematic for Floating-Point Multiplier

 


Figure 7-8(b) Top-level Schematic for Floating-Point Multiplier

 


Figure 7-9 Main Control for Floating-Point Multiplier

 


Figure 7-11 A Register

 


Figure 7-12 E1 Register


 


Figure 7-13 Exponent Adder

 

FLOATING POINT ADDITION *(from page 259)*

$$(F_1 \times 2^{E_1}) + (F_2 \times 2^{E_2}) = F \times 2^E$$

Example 1: Add $F_1 \times 2^{E_1} = 0.111 \times 2^5$ and $F_2 \times 2^{E_2} = 0.101 \times 2^3$
Unnormalize $0.101 \times 2^3 = 0.0101 \times 2^4 = 0.00101 \times 2^5$
Add fractions $(0.111 \times 2^5) + (0.00101 \times 2^5) = 01.00001 \times 2^5$
Fix Overflow $F \times 2^E = 0.100001 \times 2^6$

Example 2: $(1.100 \times 2^{-2}) + (0.100 \times 2^{-1})$
 $= (1.110 \times 2^{-1}) + (0.100 \times 2^{-1})$ (after shifting F_1)
 $= 0.010 \times 2^{-1}$ (result of adding fractions is unnormalized)
 $= 0.100 \times 2^{-2}$ (normalized by shifting left and subtracting one from exponent)

FLOATING POINT ADDITION SUMMARY *(from page 260)*

- 1) If exponents are not equal, shift the fraction with the smallest exponent right and add 1 to its exponent; repeat until the exponents are equal.
- 2) Add the fractions.
- 3)
 - (a) If fraction overflow occurs, shift right and add 1 to the exponent to correct the overflow.
 - (b) If the fraction is unnormalized, shift left and subtract 1 from exponent until the fraction is normalized.
 - (c) If the fraction is 0, set the exponent to the appropriate value.
- 4) Check for exponent overflow.