- (4) Question 2. Because of all the calculations, use B) Binary fixed-point
- (4) Question 3. To increase  $V_{OH}$  C) No, add a resistor to +5V (it will effect  $I_{OL}$ )
- (4) Question 4. ADC range is 2V, Precision is 2V/0.001V, which is 2000 alternatives.

Use an **11-bit ADC**, which has a precision of 2048 alternatives.

- (4) Question 5. Need NPN to sink current, need resistor to set LED current (C)
- (4) Question 6. Slowing down the 9S12 will B) make the batteries last longer
- (4) Question 7. Because the Fifo is empty, the software is not putting much data into itA) The system is CPU bound
- (4) Question 8. Because the Fifo is empty, the input rate is slow

C) The system is I/O bound

(4) **Question 9.** *Functional debugging* means we are interested in the input/output data. *minimally intrusive* means the debugging instrument needs to execute fast as compared to the time between interrupt calls. The dump is the fastest way to collect data

D) asm sei if(n<100){BufX[n]=x; BufY[n]=y; n++;} asm cli

(4) Question 10. Start with coworkers (you probably measured something wrong), then go to your boss, then go to the safety officer at the company. As a last resort, contact federal safety commissions.

(5) Question 11. Clock is normally high (CPOL=1), 9S12 needs to latch on the falling edge (other edge from the input device) (CPHA=0). See book figure 7.40

(10) Question 12. Use +12V supply because it is a 12V motor. Use a NPN, because it is simpler to interface a current sink to the 9S12 (they share common ground, but do share a common supply). Need  $12V/10\Omega = 1.2A$ , so use a TIP120, which has a maximum ICE of 3A. The hFE=1000 of the TIP120 means the IIH of the 9S12 will only be 1.2mA. The resistor can be added to limit the base current to a maximum of 1.2mA. The snubber diode (1N914) prevents back EMF.



(15) Question 13. Address decoder is A15, output positive logic, synchronized to E



Part b) The delays on first start of the interval are maximums, and at the end we use minimums. **Read Data Available** = [250+15+15+60,500+5+5+10] = [340,520]

(15) Question 14. A data acquisition system to measure angle.

Part a) Good CMRR and differential means use instrumentation amp. Need gain = 5 (no Rf is needed, leave pins 1,8 open)



```
Count = 5; // fifth rising edge
dummy = SCISR1; // read status with TDRE set
SCIDRL = 0x56; // output 'V'
```

} }