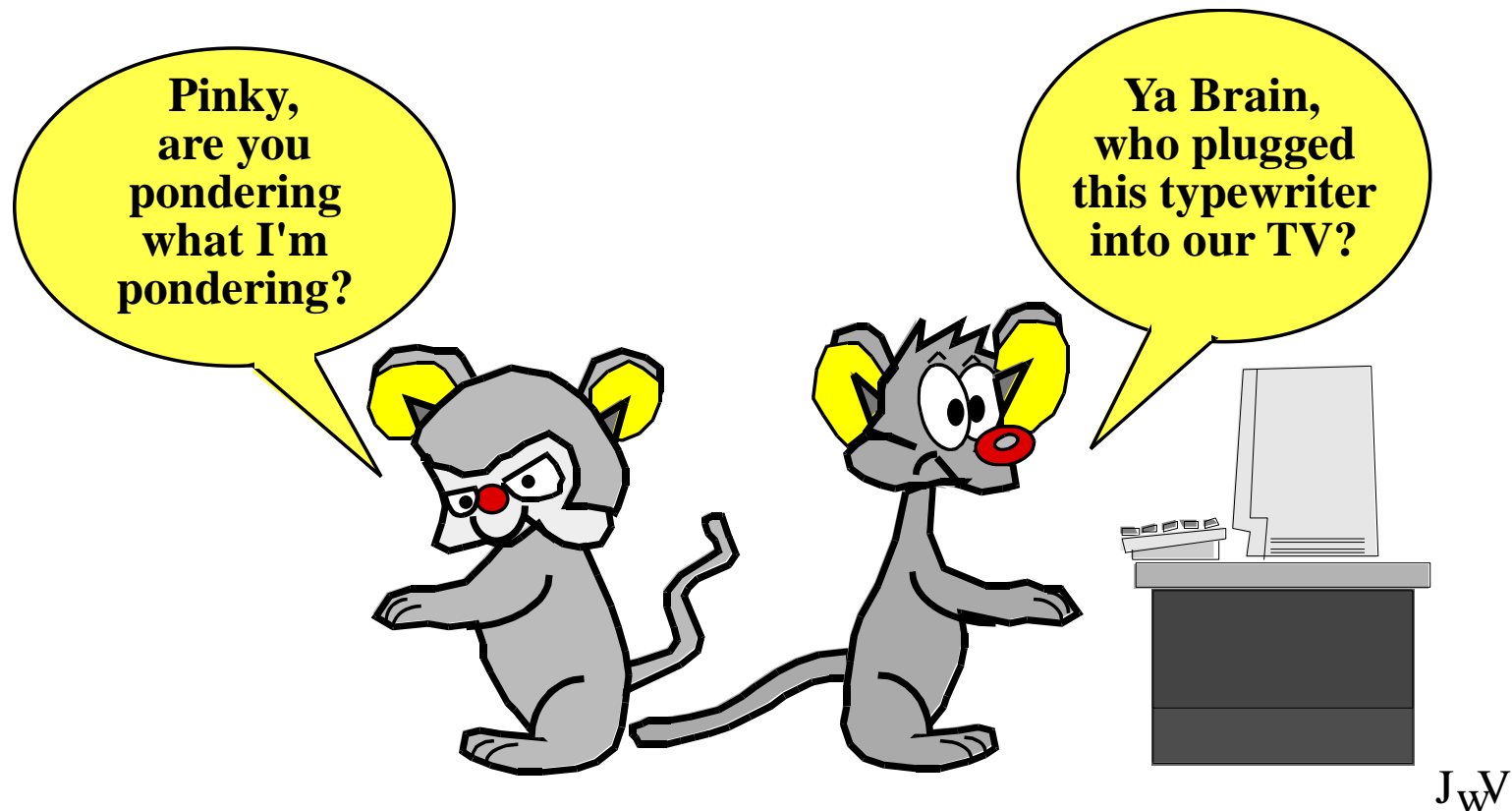


# 19. Motor Interfacing

- Motor physics
- Transistor-level interface



# Digital Interfacing

$V_{OL}$  is defined as the voltage at maximum  $I_{OL}$


<i>Family</i>	<i>Example</i>	$I_{OH}$	$I_{OL}$	$I_{IH}$	$I_{IL}$	<i>fan out</i>
Standard TTL	7404	0.4 mA	16 mA	40 $\mu$ A	1.6 mA	10
Schottky TTL	74S04	1 mA	20 mA	50 $\mu$ A	2 mA	10
Low Power Schottky	74LS04	0.4 mA	4 mA	20 $\mu$ A	0.4 mA	10
High speed CMOS	74HC04	4 mA	4 mA	1 $\mu$ A	1 $\mu$ A	
LM3S/LM4F 2mA-drive	LM3S811	2 mA	2 mA	2 $\mu$ A	2 $\mu$ A	
LM3S/LM4F 4mA-drive	LM3S811	4 mA	4 mA	2 $\mu$ A	2 $\mu$ A	
LM3S/LM4F 8mA-drive	LM3S811	8 mA	8 mA	2 $\mu$ A	2 $\mu$ A	

## Electrical specifications


- See Chapter 24 of TM4C123
- 5V tolerant?
- PD0, PD1  $\Leftrightarrow$  PB7, PB6

All GPIO signals are 5-V tolerant when configured as inputs except for PD4, PD5, PB0 and PB1, which are limited to 3.6 V.





# Motor Physics

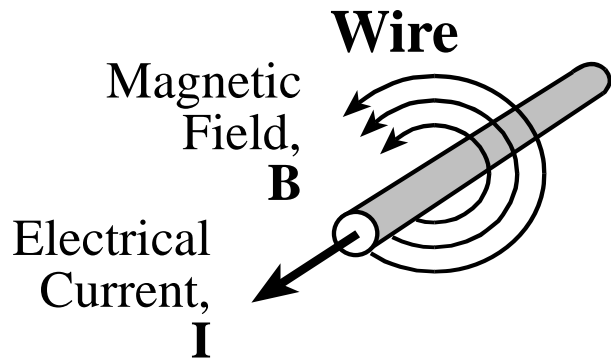

**Electromagnet**

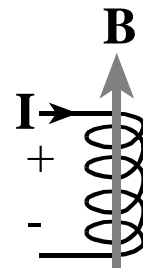

**Electrical Model**

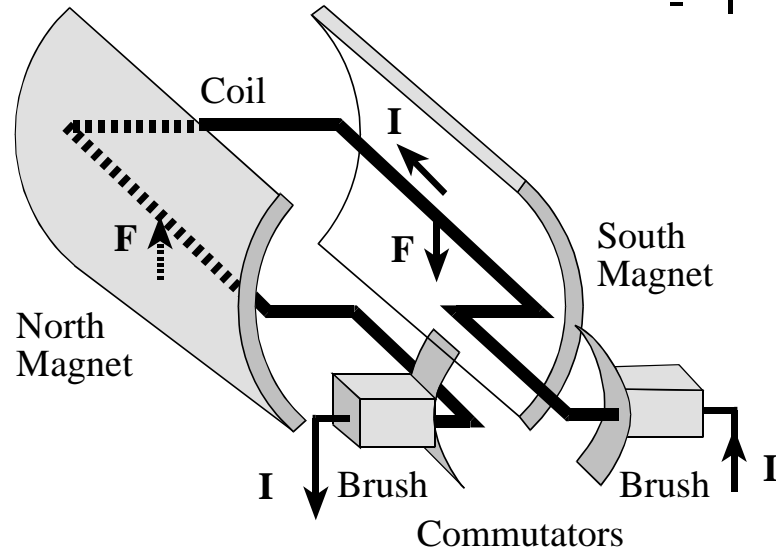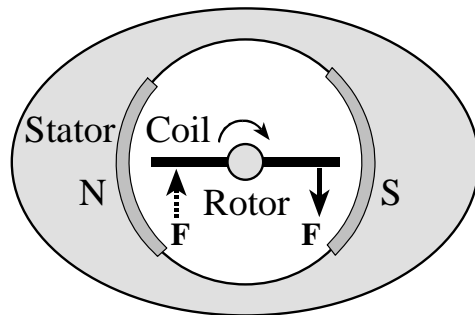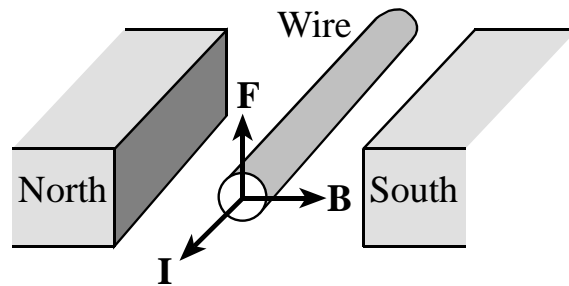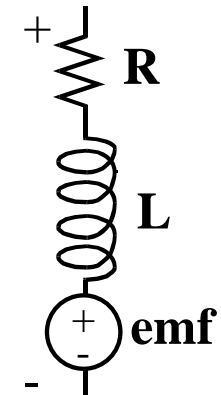

# Darlington Transistor


- TIP120 (NPN)
- $h_{fe} = 1000$
- $I_{ce} = 3A$

$$I_b = I_{coil} / h_{fe} = 1A / 1000 = 1mA$$

$$R_b \leq (V_{OH} - V_{be}) / I_b = (3 - 2.5) / 1mA = 0.5 \text{ k}\Omega$$



$$R_b = 100 \Omega$$

$V_{CE}$  depends on current

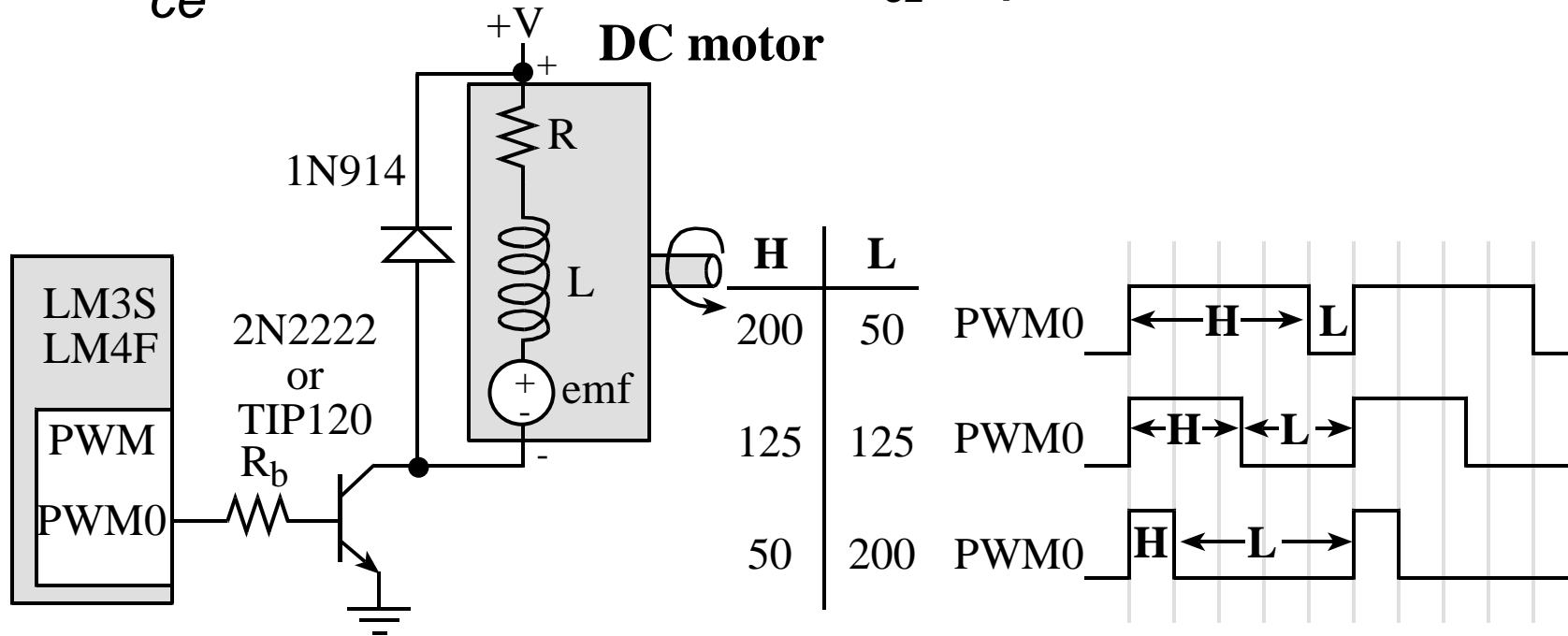

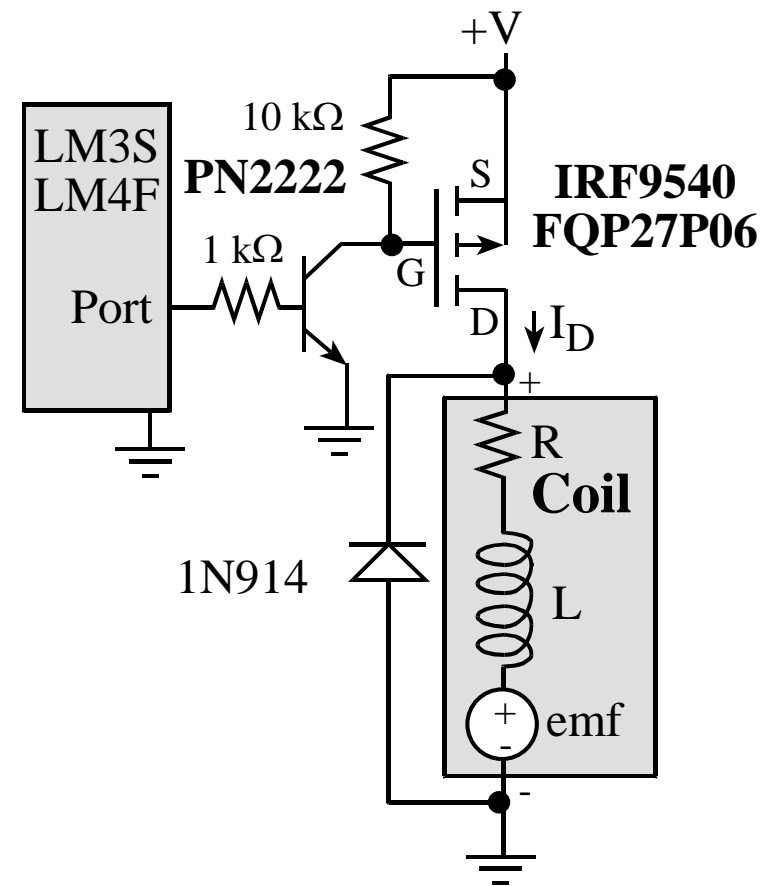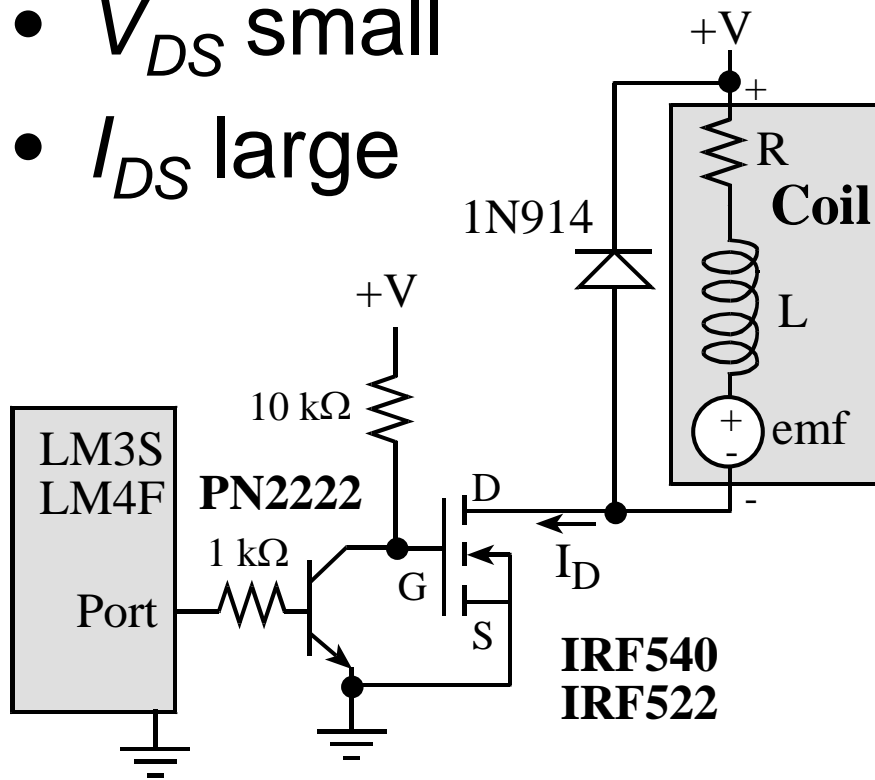
# MOSFET Interface

- $V_{GS}$  turns on
- $V_{DS}$  small
- $I_{DS}$  large



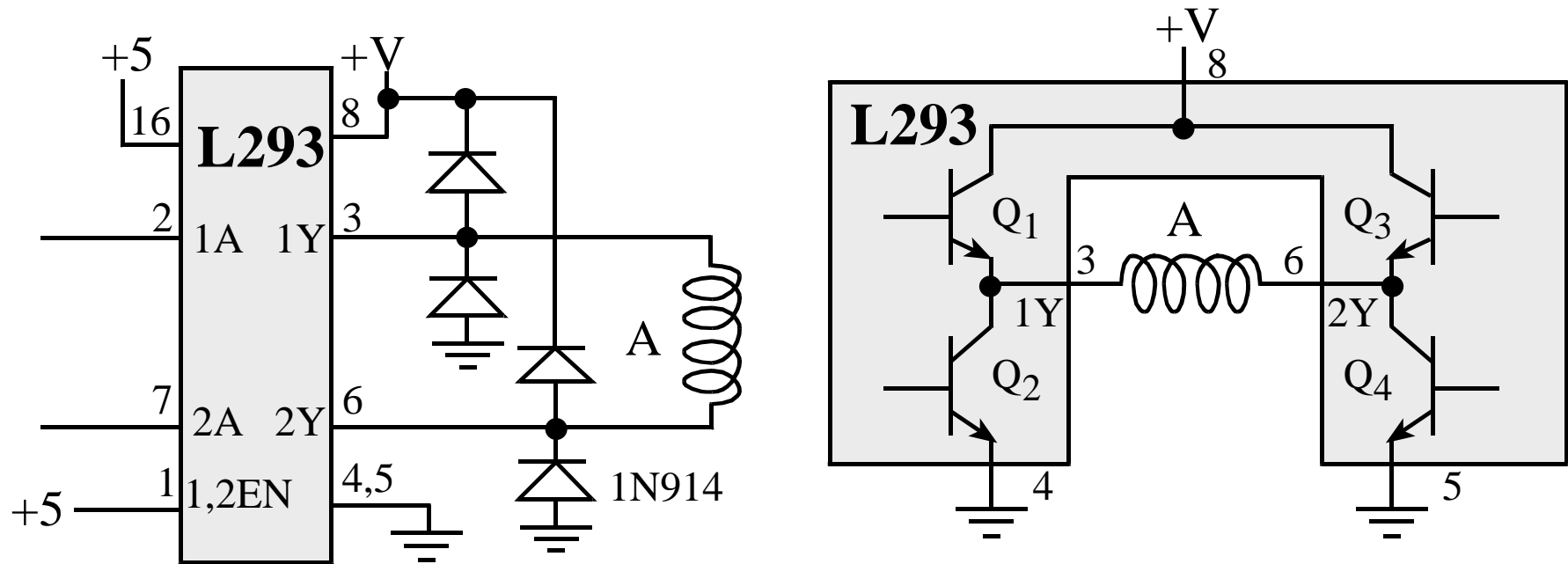
# H-bridge Interface

- Both directions
- $V_{OH} = +V - 1.4$ ,  $V_{OL} = 1.2$



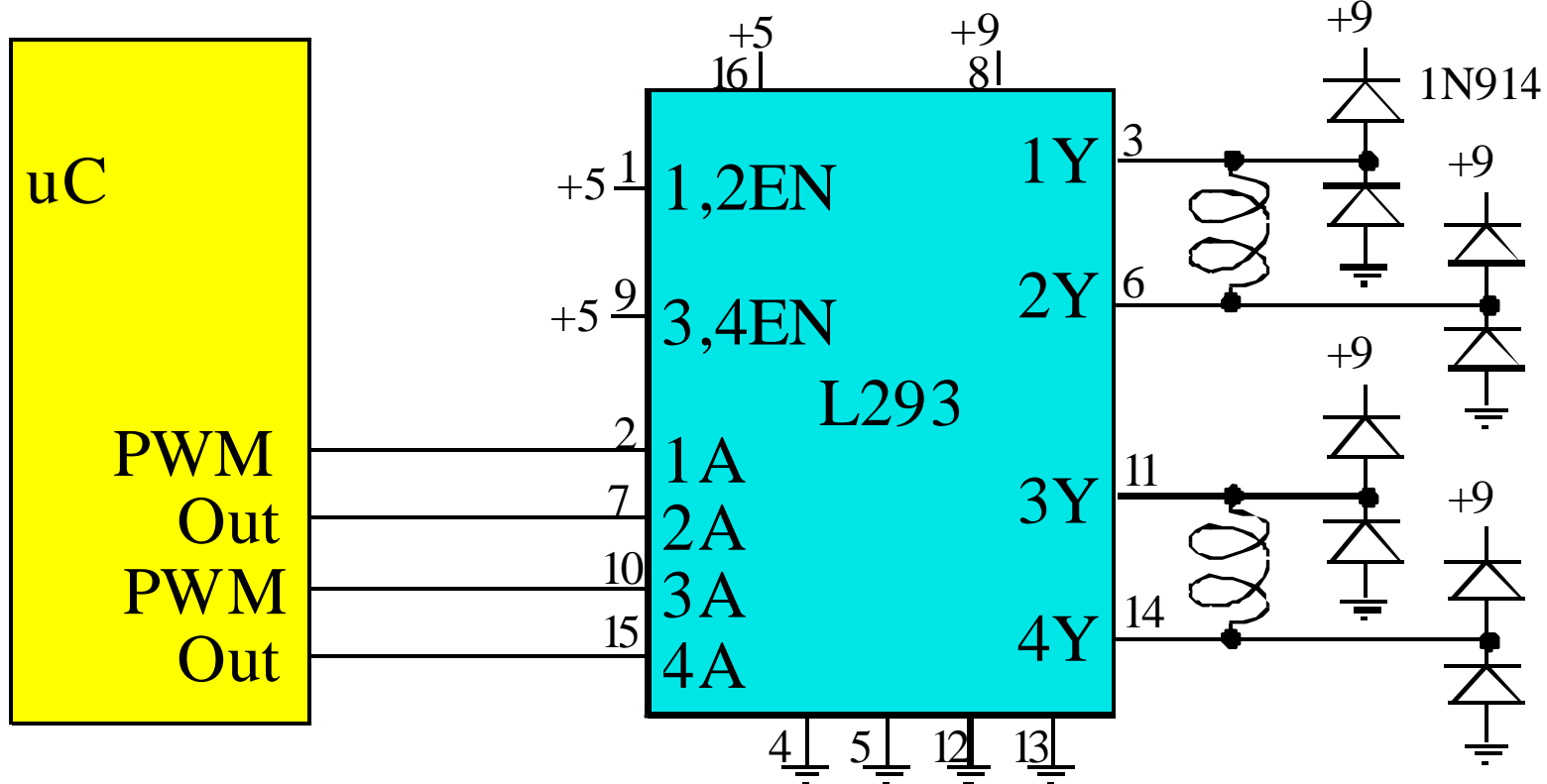
# H-bridge Interface

- PWM controls power
- Out controls direction


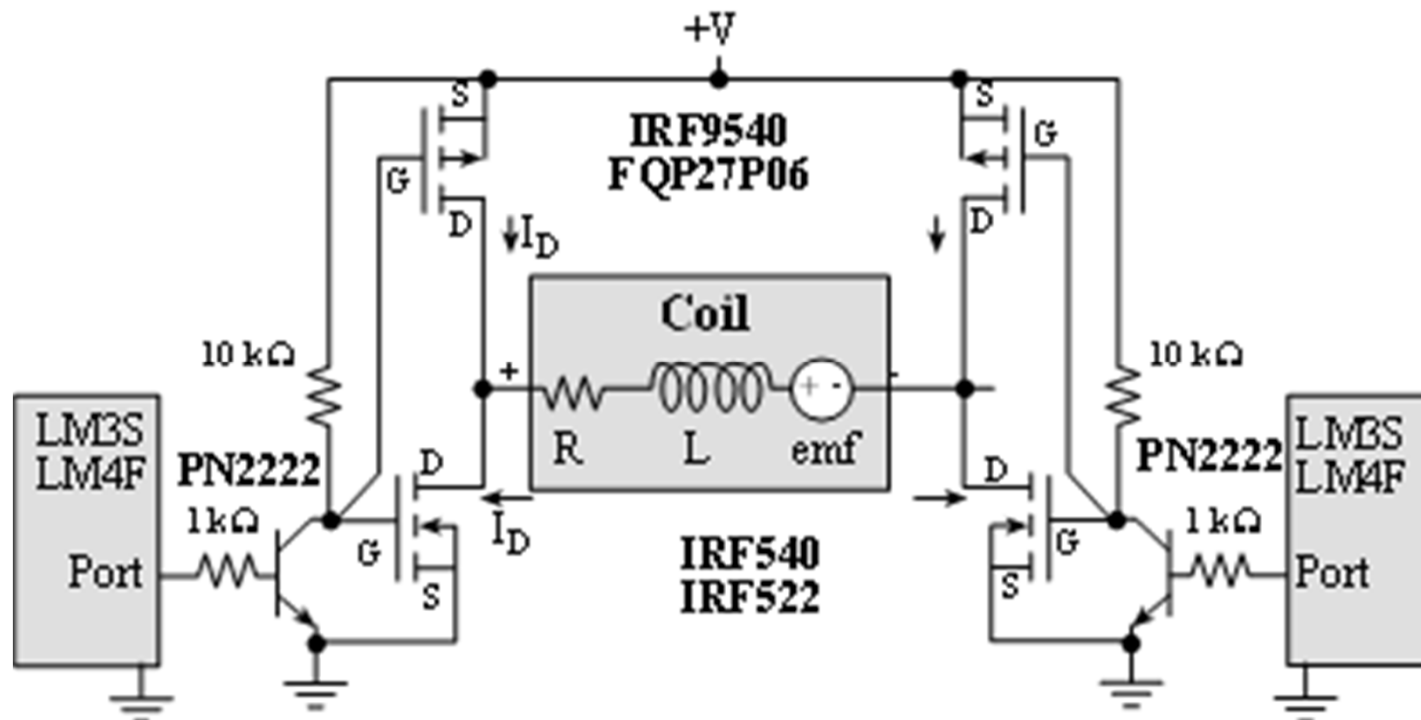
# H-bridge Interface


- One Port is PWM controlling power
- Other port controls direction






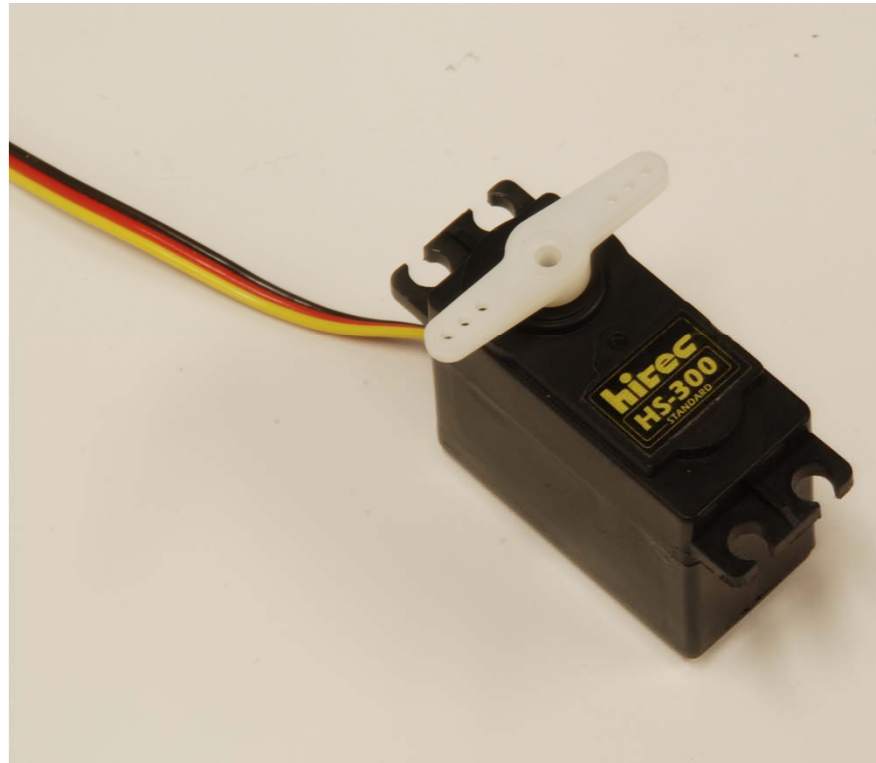
# Servo Motor

- Simple digital interface (built in controller)
- Duty cycle controls angle



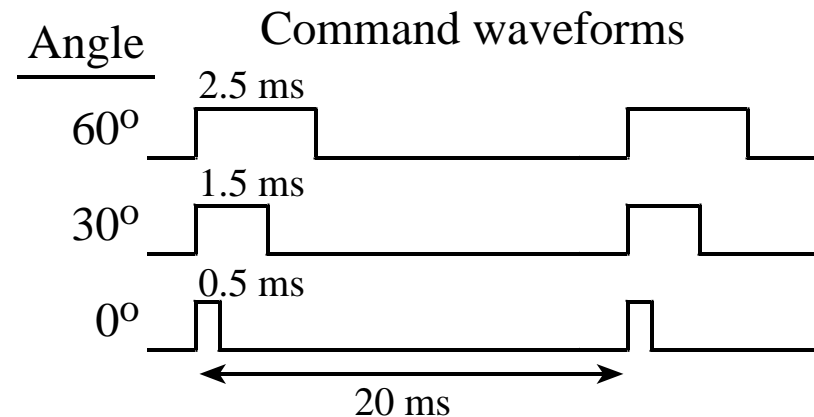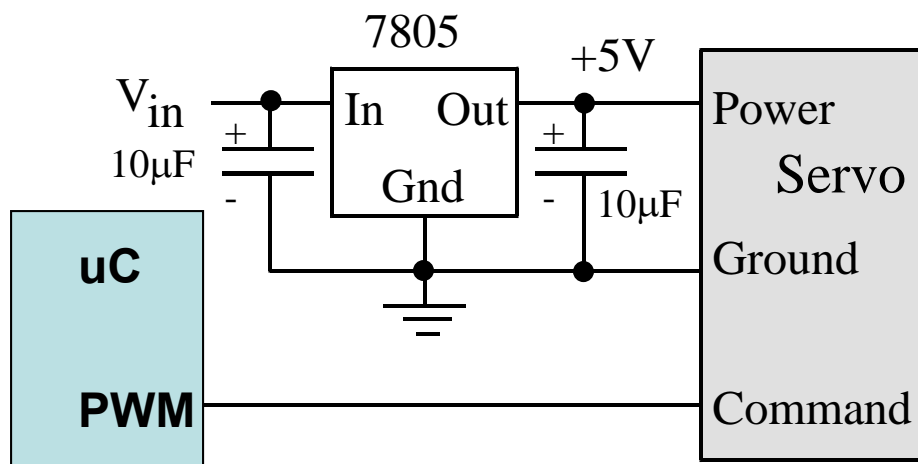
# Servo Interface

- Needs its own +5V regulator
- Duty cycle controls angle



# Servo Software

- Duty cycle controls angle

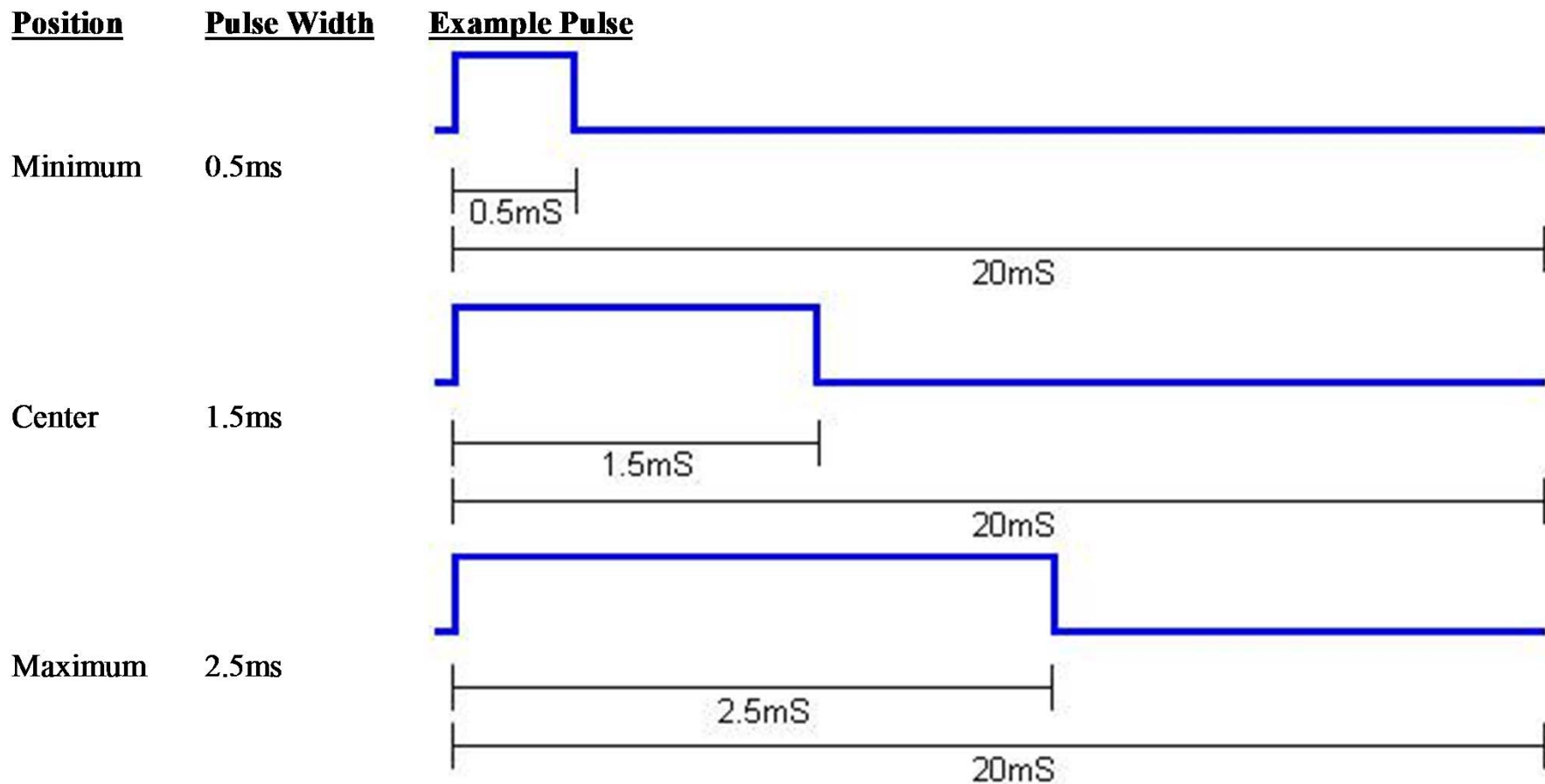

# Summary

- Be careful of the currents
- Sensors are noisy
- Time lag makes it unstable
- Component testing
- Visualization and control