

①

The Cascode ~~Transistor~~ Amplifier

Pio Balmeili
2/13/07


Motivation

- Transistors are mainly used as amplifiers
- One of the main function of a transistor is the amplifier
- * ~~But~~ transistors are not linear ($I_c \propto e^{V_{be}}$, $I_D \propto (V_{GS} - V_T)^2$)
 - transistor gain cannot not well controlled, ~~can not be controlled well~~
 - ex.: ~~gain~~ depends on the bias conditions
 - ~~gain~~ can vary by $> 2x$ over process corners and Temp.

Q: How can we build reliable amplifiers despite these drawbacks?

A: We build circuits that do not rely on the the Operational Amplifier

ex.

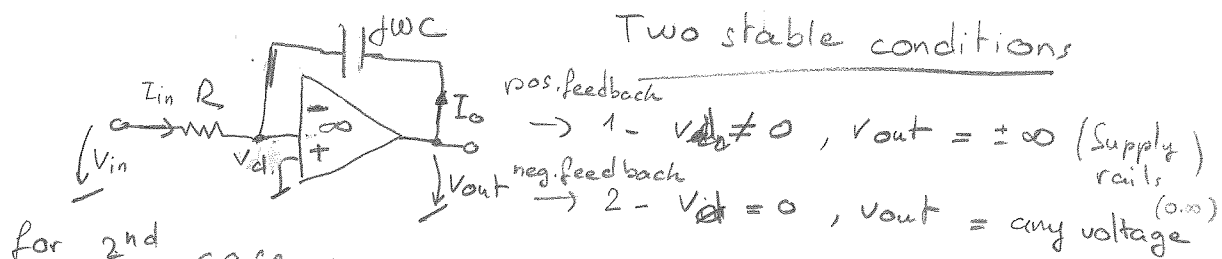

for 2nd case :

$$\begin{cases} I_{in} = V_{in}/R \\ I_o = -I_{in} \\ V_{out} = \frac{I_o}{j\omega C} \end{cases}$$

$$V_{out} = \frac{-V_{in}/R}{j\omega C}$$


$$\frac{V_{out}}{V_{in}} = \frac{1}{j\omega RC}$$

The integrator

$\rightarrow$ The function of the stage (Integrator) does not depend on the amplifier gain but on more stable, more linear passive components.

Q: How can we build amplifiers with high gain?

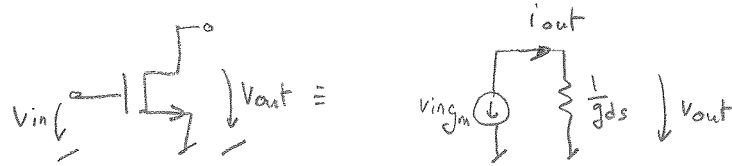The simple transistor in common source ~~can~~ configuration does not have enough gain.




$$\frac{V_{out}}{V_{in}} \approx 10 \dots 40$$

gain:

$$\begin{cases} V_{out} = i_{out} \cdot \frac{1}{g_{ds}} \\ i_{out} = -V_{in} \cdot g_m \\ \Rightarrow \frac{V_{out}}{V_{in}} = -\frac{g_m}{g_{ds}} \end{cases}$$

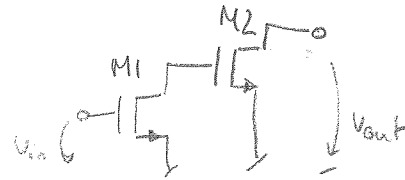A1: ~~We boost the gm~~. Ex. we cascade stages





$$\frac{V_{out}}{V_{in}} = \left(-\frac{g_{m1}}{g_{ds1}} \right) \cdot \left(-\frac{g_{m2}}{g_{ds2}} \right) = \frac{g_{m1} g_{m2}}{g_{ds1} g_{ds2}}$$

A2: We lower the g_{ds} (~~increase~~ ^{boost} output impedance)

The source degeneration technique

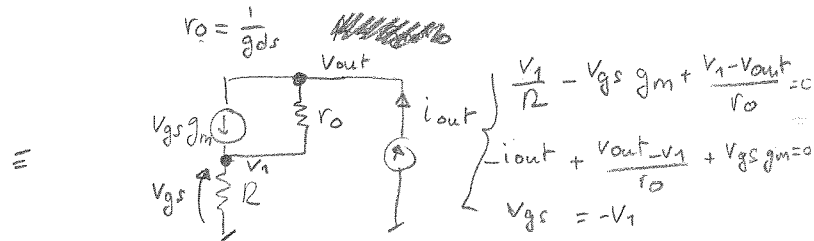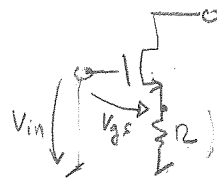Output Impedance ($\frac{V_{out}}{I_{out}}$)



$$\frac{V_{gs} (1/r_o + g_m)}{V_{gs} (1/R + g_m + 1/r_o)} = \frac{i_{out} - \frac{V_{out}}{r_o}}{-\frac{V_{out}}{r_o}}$$

$$\frac{1/r_o + g_m}{1/R + g_m + 1/r_o} = 1 - \frac{i_{out}}{V_{out}} r_o$$

$$\text{Subs. } \begin{cases} \textcircled{1} \quad -\frac{V_{gs}}{R} - V_{gs} g_m - \frac{V_{gs} V_{out}}{r_o} = 0 \\ \textcircled{2} \quad -i_{out} + \frac{V_{out} + V_{gs}}{r_o} + V_{gs} g_m = 0 \end{cases}$$

$$\text{isol } \begin{cases} \textcircled{1} \quad V_{gs} (1/R + g_m + 1/r_o) = -\frac{V_{out}}{r_o} \\ \textcircled{2} \quad V_{gs} (1/r_o + g_m) = i_{out} - \frac{V_{out}}{r_o} \end{cases}$$

$$\boxed{\frac{V_{out}}{i_{out}} = r_o + R + R \cdot g_m r_o}$$


Unfortunately the stage ^{equivalent} transconductance is: $g_m' = \frac{g_m r_o}{r_o + R + g_m R r_o} (< g_m)$

and the total gain is: $g_m' r_o' = g_m r_o \frac{r_o + R + R g_m r_o}{r_o + R + R g_m r_o} = \underline{\underline{g_m r_o}}$
unchanged!


The cascode transistor

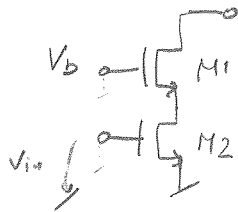(B) 1

- beside the unchanged gain the source degeneration technique has the disadvantage that the max R is limited by large signal considerations.
- Substitute the degeneration resistance with a transistor in saturation region:




Output Impedance

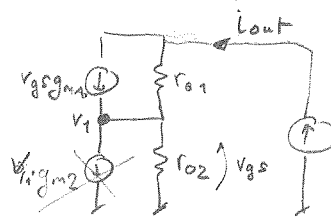

the small signal circuit is the same as the prev one therefore:

$$r_o' = \frac{V_{out}}{I_{out}} = r_{o1} + r_{o2} + r_{o2} g_{m1} r_{o1}$$

The effective g_m' is different:

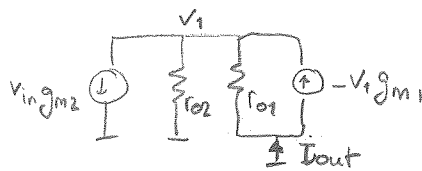

$$\begin{cases} \textcircled{1} \quad \begin{cases} I_{out} = -V_1 g_{m1} - \frac{V_1}{r_{o1}} \\ V_{in} g_{m2} + \frac{V_1}{r_{o2}} + \frac{V_1}{r_{o1}} + V_1 g_{m1} = 0 \end{cases} \\ \textcircled{2} \quad \begin{cases} V_1 (g_{m1} + \frac{1}{r_{o1}}) = -I_{out} \\ V_1 (\frac{1}{r_{o2}} + \frac{1}{r_{o1}} + g_{m1}) = -V_{in} g_{m2} \end{cases} \end{cases}$$


$$\textcircled{3} \quad \frac{V_1 (g_{m1} + \frac{1}{r_{o1}})}{V_1 (\frac{1}{r_{o2}} + \frac{1}{r_{o1}} + g_{m1})} = \frac{+I_{out}}{+V_{in} g_{m2}} \quad ; \quad \textcircled{4}$$

$$\frac{I_{out}}{V_{in}} = g_{m2} \frac{g_{m1} + \frac{1}{r_{o1}}}{g_{m1} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}} \approx g_{m2}$$

Therefore the gain is:

$$A = g_{m2} \cdot (r_{o1} + r_{o2} + r_{o2} g_{m1} r_{o1}) \approx g_{m2} r_{o2} g_{m1} r_{o1}$$

Intuitive explanation

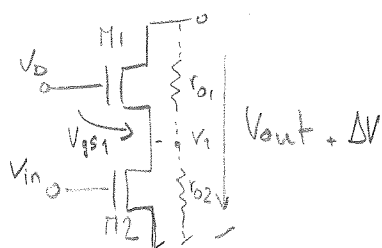


- when V_{out} changes, V_1 tends to follow it over the r_{o1}/r_{o2} voltage divider. However, V_1 activates Transistor M1 that provides additional current that flows through r_{o1} therefore most of the voltage drop is on r_{o1} and r_{o2} is kept stable reducing the net current and hence increasing the impedance

Derivatives of the basic cascode

52


1) The double cascode

- recursive use of the cascode idea

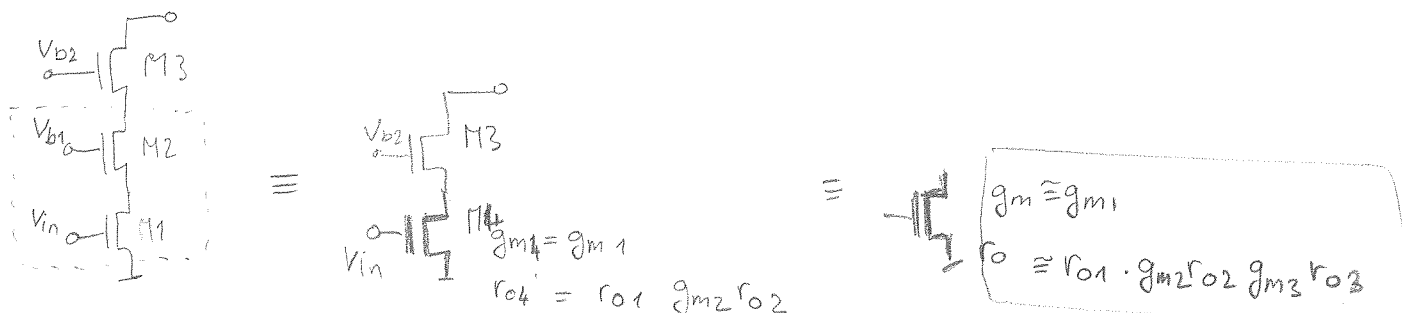

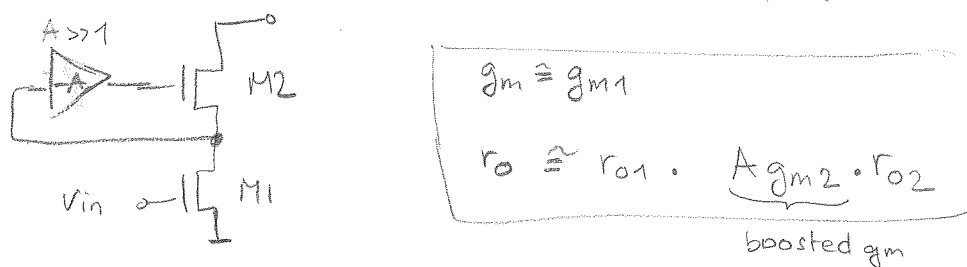
2) The regulated cascode

- g_{m2} is boosted by an operational amplifier



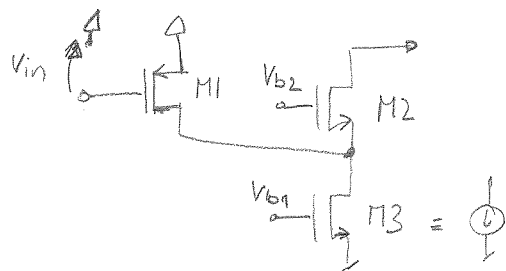3) The folded cascode

- PMOS input transistor and NMOS cascode transistor give more freedom in the choice of the common mode voltages




(assuming M3 is an ideal current sink)

$$\begin{cases}
 g_m = g_{m1} \\
 r_o = r_{o1} \cdot g_{m2} r_{o2}
 \end{cases}$$

© 1

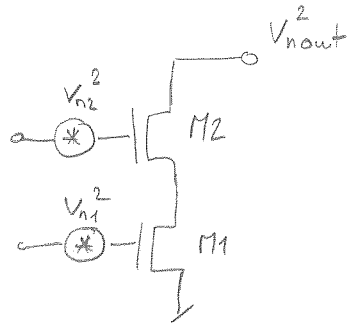Noise contribution of the cascode transistor



$$V_{nout}^2 = V_{n2}^2 \cdot (g_m r_{o2})^2 + V_{n1}^2 (g_{m2} r_{o2} g_{m1} r_{o1})^2$$

Input referred noise :

$$\begin{aligned} V_{nin}^2 &= \frac{V_{nout}^2}{(g_{m2} r_{o2} g_{m1} r_{o1})^2} \\ &= \frac{V_{n2}^2 (g_m r_{o2})^2 + V_{n1}^2 (g_{m2} r_{o2} g_{m1} r_{o1})^2}{(g_{m2} r_{o2} g_{m1} r_{o1})^2} \\ &= V_{n2}^2 \frac{1}{(g_{m1} r_{o1})^2} + V_{n1}^2 \end{aligned}$$

⚠ The noise contribution of M2 is scaled by the square of the gain of M1.

⇒ M2 is usually a negligible source of noise!

Conclusion

©2

- 1) The cascode ~~circuit~~ is a very common and useful topology in CMOS analog circuits
- 2) The g_m of the circuit is the same as the one of bottom transistor. The output impedance is the r_o of the bottom transistor ~~boosted~~ by the gain of the upper transistor.
- 3) The upper transistor does usually not contribute to the total noise

⑦

Notation

NMOS Transistor :  , 

PMOS Transistor :  , 

current source :  

voltage source :  

voltage controlled current source (g_m) : 

~~noise source~~ : 

gnd



Vdd

