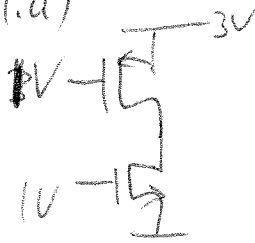


3.1.a)



assume both devices are saturated

$$I_{DP} = \frac{K_p'}{2} \left(\frac{W}{L} \right)_p (2V - 0.8V) = 200 \cdot 1.44 \mu A = 288 \mu A$$

$$I_{DN} = \frac{K_n'}{2} \left(\frac{W}{L} \right)_n (1V - 0.7V) = \frac{600 \cdot 0.09 \mu A}{300 \cdot 0.09} = 27 \mu A$$

$I_{DN} < I_{DP} \Rightarrow$ p device is ohmic

$$I_{DP} = I_{DN} = K_p' \frac{W}{L} \left((V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right)$$

$$V_{DS}^2 - 2(V_{GS} - V_T) V_{DS} + \frac{2I_{DN}}{K_p' \frac{W}{L}} = 0$$


$$V_{DS} = (V_{GS} - V_T) \pm \sqrt{(V_{GS} - V_T)^2 - \frac{2I_{DN}}{K_p' \frac{W}{L}}} = 251 mV \Rightarrow V_{out} = 2.749V$$

1.2V + $\sqrt{0.9}$ would get us into saturation $V_{out} = 2.882V$

linear ohmic equation only

$$V_{DS} = \frac{I_{DN}}{K_p' \frac{W}{L} (V_{GS} - V_T)} = 225 mV$$

3.1.b)

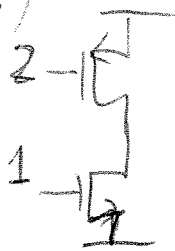

assume both in saturation

$$I_{DN} = 54 \mu A \sim$$

$$I_{DP} = \frac{100 \cdot (0.2)^2}{200} = 8 \mu A = 4 \mu A$$

therefore N device is ohmic


$$I_{DN} = I_{DP} = K_n' \frac{W}{L} \left((V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right)$$

$$V_{DS} = (V_{GS} - V_T) \pm \sqrt{(V_{GS} - V_T)^2 - \frac{2I_{DP}}{K_n' \frac{W}{L}}} = 483 mV$$

if I used linear only

$$V_{DS} = V_{out} = 44.4 mV = 23 mV$$

3.1 a small signal model

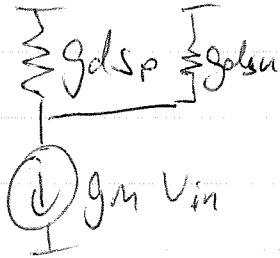

$$\text{gain } A = \frac{v_{out}}{v_{in}} = -g_m / (g_{dsp} + g_{dsn})$$

N-device saturation $g_m = \sqrt{2K_n' \frac{W}{L} I_D}$ ohmic $g_m = K_n' \frac{W}{L} V_{DS}$

P-device ohmic $g_{ds} = K_p' \left(\frac{W}{L} \right)_p (V_{DS} - V_T)$ sat. $g_{ds} = \lambda_p \cdot I_D$

$$a) \quad \frac{v_{out}}{v_{in}} = - \frac{\sqrt{2K_n' \left(\frac{W}{L} \right)_n I_D}}{K_p' \left(\frac{W}{L} \right)_p (V_{DS} - V_T)} = - \frac{\sqrt{1200 \cdot 54} \rightarrow 27}{200 \cdot 1.2 + g_{dsn}} = -1.06 =$$

$$b) \quad \frac{v_{out}}{v_{in}} = - \frac{K_n' \frac{W}{L} V_{DS}}{\lambda_p I_D + K_n' \left(\frac{W}{L} \right)_n (V_{DSn} - V_T)} = - \frac{600 \cdot 48.3 \cdot 10^{-3}}{0.03 \cdot 8 + 600 \cdot 0.3} = -1.58$$

3.2

output impedance requires cascoding


assume $V_{outmin} = 2V_{DSmin} = 2V_{on}$

$$N_{device}: V_{on} = \sqrt{\frac{I_D}{\frac{K'_1 W}{2L}}} = \sqrt{\frac{10\mu A}{75\mu A/V^2 \frac{W}{L}}} = 0.2V$$

$$\Rightarrow \frac{W}{L} = \frac{10\mu A}{75\mu A/V^2 (0.2V)^2} = 3.33$$

P_{device} W must be $3\times$ larger $\Rightarrow \frac{W}{L} = 10$
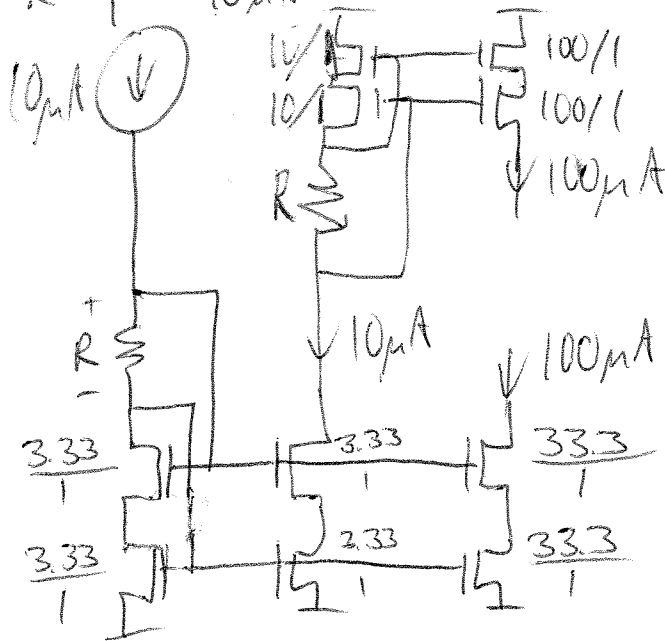
$$R = \frac{V}{I} = \frac{200mV}{10\mu A} = 20k\Omega$$



3.3

from lecture $G = \sqrt{k' \frac{W}{L} I_D} = 1 \text{ mS}$

make $I_D = 100 \mu\text{A} \Rightarrow \frac{W}{L} = \frac{(1 \text{ mS})^2}{k' I_D} = 66.66$


look at $V_{\text{min}} = 1 \text{ V}$

$$V_{\text{min}} = V_T + V_{\text{outtail}} + V_{\text{outdiffpair}}$$

$$V_{\text{outdiff}} = \sqrt{\frac{I_D}{\frac{k'}{2} \frac{W}{L}}} = \sqrt{\frac{50 \mu\text{A}}{75 \mu\text{A/V}^2 \cdot 66.66}} = 100 \text{ mV}$$

$$V_{\text{outtail}} = \sqrt{\frac{I_D}{\frac{k'}{2} \frac{W}{L}}} = 200 \text{ mV} \Rightarrow \frac{W}{L} = \frac{100 \mu\text{A}}{75 \mu\text{A/V}^2 \cdot (0.2)^2} = 33.33$$
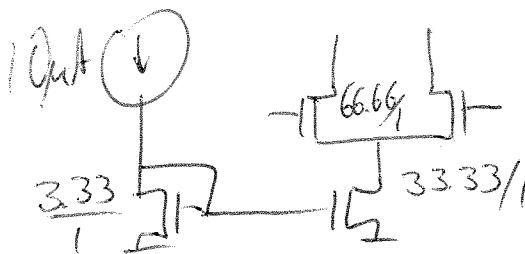
$$V_{\text{out min}} = V_{\text{min max}} + V_T = 0.8 \text{ V}$$



3.4

N current mirror takes in $10 \mu\text{A}$, produces $I_1 = 20 \mu\text{A}$, $30 \mu\text{A}$, $40 \mu\text{A}$

balanced diffpair splits current evenly $I_2 = I_3 = 10 \mu\text{A}$

P current mirror takes in $10 \mu\text{A}$, produces $50 \mu\text{A}$

$$I_5 = 50 \mu\text{A} - 40 \mu\text{A} = 10 \mu\text{A}$$

unbalanced diffpair: all current goes through M_2

$$I_4 = 0 \quad \text{if} \quad \sqrt{\frac{30 \mu\text{A}}{\frac{k'}{2} \frac{W}{L}}} < 2 \text{ V}$$