

Solution

$$(5) \quad I_{in} = \frac{K'_n W}{2 L} (1V - 0.54V)^2 (1 + \lambda(1V)) = 170.9728 \mu A$$

$$I_{out} = \frac{K'_n W}{2 L} (1V - 0.5V)^2 (1 + \lambda(2V)) = 204 \mu A$$

$$\begin{array}{l} V_{OS} \text{ mismatch} \quad 1.01 \text{ vs } 1.02 \\ V_T \text{ mismatch} \quad 0.46^2 \text{ vs } 0.5^2 \\ \quad \quad \quad = 0.2116 \text{ vs } 0.25 \text{ and bigger} \end{array}$$

$$\begin{array}{l} (4) \quad I_1 = 10 \mu A \\ I_2 = 40 \mu A \\ I_3 = 160 \mu A \\ I_4 = 60 \mu A \\ I_5 = 100 \mu A \end{array}$$

$$(3) \quad V_{a(load)} = 0.5V \Rightarrow 0.5V = \sqrt{\frac{I_D}{\frac{K'_n W}{2 L}}} \Rightarrow 0.25 \frac{I_D}{(W/L)_{load}} = \frac{I_D}{(W/L)_{load}} = \frac{4I_D}{25\mu} \\ \frac{g_{min}}{I_D} = \frac{\sqrt{2K'_n \frac{W}{L} I_D}}{I_D} = 20 \Rightarrow \frac{2 \cdot 160\mu \cdot (W/L)_n}{I_D} = 400 \Rightarrow (W/L)_n = \frac{5}{4} I_D$$

$$(40 \mu V / \sqrt{Hz})^2 = \frac{8}{3} kT \frac{1}{g_{min}} \left(1 + \frac{g_{mload}}{g_{min}} \right)$$

$$= \frac{8}{3} \cdot 1.38 \cdot 10^{-23} \cdot 300 \frac{1}{\sqrt{2K'_n \frac{W}{L} I_D}} \left(1 + \frac{\sqrt{2K'_p \frac{W}{L} I_D}}{\sqrt{2K'_n \frac{W}{L} I_D}} \right)$$

$$= (0.011 n) \frac{1}{\sqrt{2 \cdot 160\mu \cdot \frac{5}{4} \mu} I_D} \left(1 + \frac{\sqrt{100\mu \cdot \frac{4}{25} \mu}}{\sqrt{32\mu \cdot \frac{5}{4} \mu}} \right) \Rightarrow I_D = 4.44 \mu A$$


27.75 μA
41.8 μA

$$\textcircled{3} \Rightarrow \frac{W}{L}_{in} = 2051.56$$

$$\frac{W}{L}_{load} = 4.56 \cdot 6$$

check $g_{min} = 288 \mu S$ $825 \mu S$ $V_{ov_{in}} = 50mV < 0.5V$ ok
 $g_{nload} = 11.75 \mu S$ $165 \mu S$ $V_{ov_{load}} = 0.5V$

$\textcircled{2}$

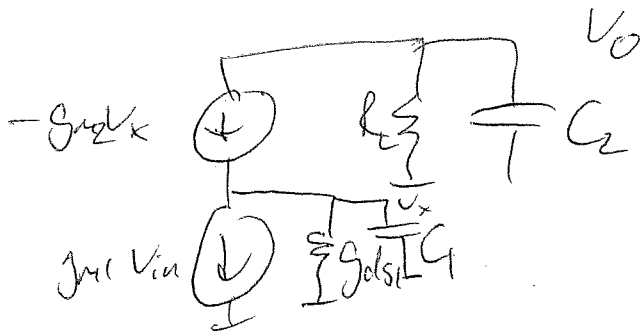

$$-g_{m2}v_x + v_0 \left(\frac{1}{R_L} + sC_2 \right) = 0$$

$$\Rightarrow v_x = + v_0 \frac{\left(\frac{1}{R_L} + sC_2 \right)}{g_{m2}}$$

$$g_{m1}v_{in} + g_{m2}v_x + g_{ds1}v_x + sC_1v_x = 0$$

$$\Rightarrow g_{m1}v_{in} + v_0 \left(g_{m2} + g_{ds1} + sC_1 \right) \cdot \frac{\frac{1}{R_L} + sC_2}{g_{m2}} = 0$$

$$\frac{v_0}{v_{in}} = - \frac{g_{m1}g_{m2}}{\left(\frac{1}{R_L} + sC_2 \right) \left(g_{m2} + g_{ds1} + sC_1 \right)}$$

$$DC \text{ gain: } g_{m1}R_L \cdot \frac{g_{mL}}{g_{m2} + g_{ds1}}$$

v_{in}

① Assume all saturated

$$M1: I_D = \frac{K'}{2} \frac{W}{L} (V_{GS} - V_T)^2 = 80\mu \cdot 4 \cdot 0.25 = 80\mu A$$

$$M3: I_D = \frac{K'}{2} \frac{W}{L} (V_{GS} - V_T)^2 = 25\mu \cdot 16 \cdot 6.25 = 2500\mu A$$

$$M2 \text{ is a cascode: } V_{GS} = V_T + \sqrt{\frac{I_D}{\frac{K'W}{2L}}} = 0.85V \quad \text{will go ohmic} \quad \swarrow$$

$$V_X = 2V - V_{GS2} = 1.15V$$

$$V_{DS1} = 1.15V > V_{DS1} = 0.5V$$

$$V_{out} = V_{DD} - V_{DS3}$$

$$V_{DS3} = \frac{I_D}{K' \frac{W}{L} V_{GS3}} = \frac{80\mu A}{50\mu A \cdot 16 \cdot 2.5V} = 40mV$$

$$V_{out} = 2.96V$$

$$V_{DS2} = 1.81V > 0.35V \Rightarrow \text{saturated}$$

M3: ohmic

M2: sat

M1: sat

$$I_D = 80\mu A$$

$$V_X = 1.15V$$

$$V_{out} = 2.96V$$