

23. Design for Low Power

- Previous Unit:
 - Circuit optimization overview
- This Unit
 - Power and Energy
 - Dynamic Power
 - Static Power
 - Low Power Design

D. Z. Pan

23. Design for Low Power

Power and Energy

- Power is drawn from a voltage source attached to the V_{DD} pin(s)

- Instantaneous Power: $P(t) = i_{DD}(t)V_{DD}$

- Energy:
$$E = \int_0^T P(t)dt = \int_0^T i_{DD}(t)V_{DD}dt$$

- Average Power:
$$P_{avg} = \frac{E}{T} = \frac{1}{T} \int_0^T i_{DD}(t)V_{DD}dt$$


April 16, 2008

D. Z. Pan

 23. Design for Low Power

Dynamic Power

- Dynamic power required to charge and discharge load capacitances when transistors switch
- One cycle involves a rising and falling output
- On rising output, charge $Q = CV_{DD}$ is required
- On falling output, charge is dumped to GND
- This repeats Tf_{sw} times over an interval of T




April 16, 2008

D. Z. Pan

 23. Design for Low Power

Dynamic Power Cont.

$$\begin{aligned} P_{dynamic} &= \frac{1}{T} \int_0^T i_{DD}(t)V_{DD}dt \\ &= \frac{V_{DD}}{T} \int_0^T i_{DD}(t)dt \\ &= \frac{V_{DD}}{T} [Tf_{sw}CV_{DD}] \\ &= CV_{DD}^2 f_{sw} \end{aligned}$$



April 16, 2008

D. Z. Pan

23. Design for Low Power

Activity Factor

- Suppose the system clock frequency = f
- Let $f_{sw} = \alpha f$, where α = activity factor
 - If the signal is a clock, $\alpha = 1$
 - If the signal switches once per cycle, $\alpha = 1/2$
 - Dynamic gates:
 - Switch either 0 or 2 times per cycle, $\alpha = 1/2$
 - Static gates:
 - Depends on design, but typically $\alpha = 0.1$
- Dynamic power: $P_{dynamic} = \alpha CV_{DD}^2 f$

April 16, 2008

D. Z. Pan

23. Design for Low Power

Short Circuit Current

- When transistors switch, both nMOS and pMOS networks may be momentarily ON for a short period of time
- Leads to a blip of “short circuit” current.
- < 10% of dynamic power if rise/fall times are comparable for input and output

April 16, 2008

D. Z. Pan

23. Design for Low Power

Example

- 200M transistor chip
 - 20M logic transistors
 - Average width: 12λ
 - 180M memory transistors
 - Average width: 4λ
 - 1.2 V 100 nm process
 - $C_g = 2 \text{ fF}/\mu\text{m}$

April 16, 2008

D. Z. Pan

23. Design for Low Power

7

Dynamic Power Example

- Static CMOS logic gates: activity factor = 0.1
- Memory arrays: activity factor = 0.05 (many banks!)
- Estimate dynamic power consumption per MHz (neglect wire capacitance)

April 16, 2008

D. Z. Pan

23. Design for Low Power

8

Dynamic Power Example

- Static CMOS logic gates: activity factor = 0.1
- Memory arrays: activity factor = 0.05 (many banks!)
- Estimate dynamic power consumption per MHz (neglect wire capacitance)

$$C_{\text{logic}} = (20 \times 10^6)(12\lambda)(0.05\mu\text{m}/\lambda)(2\text{fF}/\mu\text{m}) = 24\text{nF}$$

$$C_{\text{mem}} = (180 \times 10^6)(4\lambda)(0.05\mu\text{m}/\lambda)(2\text{fF}/\mu\text{m}) = 72\text{nF}$$

$$P_{\text{dynamic}} = [0.1C_{\text{logic}} + 0.05C_{\text{mem}}](1.2)^2 f = 8.6 \text{ mW/MHz}$$

April 16, 2008

D. Z. Pan

23. Design for Low Power

9

Static Power

- Static power is consumed even when chip is quiescent.
 - Ratioed circuits burn power in fight between ON transistors
 - Leakage draws power from nominally OFF devices

$$I_{ds} = I_{ds0} e^{\frac{V_{gs} - V_t}{nV_T}} \left[1 - e^{-\frac{V_{ds}}{V_T}} \right]$$

$$V_t = V_{t0} - \eta V_{ds} + \gamma \left(\sqrt{\phi_s + V_{sb}} - \sqrt{\phi_s} \right)$$

April 16, 2008

D. Z. Pan

23. Design for Low Power

10

Ratio Example

- The chip contains a 32 word x 48 bit ROM
 - Uses pseudo-nMOS decoder and bitline pullups
 - On average, one wordline and 24 bitlines are high
- Find static power drawn by the ROM
 - $\beta = 75 \mu\text{A}/\text{V}^2$
 - $V_{tp} = -0.4\text{V}$

April 16, 2008

D. Z. Pan

23. Design for Low Power

11

Ratio Example

- The chip contains a 32 word x 48 bit ROM
 - Uses pseudo-nMOS decoder and bitline pullups
 - On average, one wordline and 24 bitlines are high
- Find static power drawn by the ROM
 - $\beta = 75 \mu\text{A}/\text{V}^2$
 - $V_{tp} = -0.4\text{V}$
- Solution:

$$I_{\text{pull-up}} = \beta \frac{(V_{DD} - |V_{tp}|)^2}{2} = 24\mu\text{A}$$

$$P_{\text{pull-up}} = V_{DD} I_{\text{pull-up}} = 29\mu\text{W}$$

$$P_{\text{static}} = (31 + 24)P_{\text{pull-up}} = 1.6 \text{ mW}$$

April 16, 2008

D. Z. Pan

23. Design for Low Power

12

Leakage Example

- Process has two threshold voltages and two oxide thicknesses
- Subthreshold leakage:
 - 20 nA/ μm for low V_t
 - 0.02 nA/ μm for high V_t
- Gate leakage:
 - 3 nA/ μm for thin oxide
 - 0.002 nA/ μm for thick oxide
- Memories use low-leakage transistors everywhere
- Gates use low-leakage transistors on 80% of logic

April 16, 2008

D. Z. Pan

23. Design for Low Power

13

Leakage Example Cont.

- Estimate static power:
 - High leakage: $(20 \times 10^6)(0.2)(12\lambda)(0.05\mu\text{m}/\lambda) = 2.4 \times 10^6 \mu\text{m}$
 - Low leakage: $(20 \times 10^6)(0.8)(12\lambda)(0.05\mu\text{m}/\lambda) + (180 \times 10^6)(4\lambda)(0.05\mu\text{m}/\lambda) = 45.6 \times 10^6 \mu\text{m}$
- $$I_{\text{static}} = (2.4 \times 10^6 \mu\text{m})[(20\text{nA}/\mu\text{m})/2 + (3\text{nA}/\mu\text{m})] + (45.6 \times 10^6 \mu\text{m})[(0.02\text{nA}/\mu\text{m})/2 + (0.002\text{nA}/\mu\text{m})]$$
- $$= 32\text{mA}$$
- $$P_{\text{static}} = I_{\text{static}} V_{DD} = 38\text{mW}$$
- If no low leakage devices, $P_{\text{static}} = 749\text{mW}$

April 16, 2008


D. Z. Pan

23. Design for Low Power

14

Gloom and Doom predictions

Closer look at the power

 

Source: Shekhar Borkar, Intel


April 16, 2008

D. Z. Pan

23. Design for Low Power

15

Power density will increase

 

Power density too high to keep junctions at low temp

Source: Shekhar Borkar, Intel


April 16, 2008

D. Z. Pan

23. Design for Low Power

16

VDD, Power and Current Trend

 

International Technology Roadmap for Semiconductors 1999 update sponsored by the Semiconductor Industry Association in cooperation with European Electronic Component Association (EECA), Electronic Industries Association of Japan (EIAJ), Korea Semiconductor Industry Association (KSIA), and Taiwan Semiconductor Industry Association (TSIA) (* Taken from Sakurai's ISSCC 2001 presentation)


April 16, 2008

D. Z. Pan

 23. Design for Low Power

17

Power Delivery Problem (not just California)



Your car starter!

Source: Shekhar Borkar, Intel

April 16, 2008


D. Z. Pan

23. Design for Low Power

18

Why is Excessive Leakage an Issue?

 - Leakage component to active power becomes significant % of total power
- Approaching ~10% in 0.18 μm technology
- Acceptable limit less than ~10%, implies serious challenge in V_T scaling!



D. Z. Pan

23. Design for Low Power

19

Low Power Design

- Reduce dynamic power
 - α : clock gating, sleep mode
 - C: small transistors (esp. on clock), short wires
 - V_{DD} : lowest suitable voltage
 - f: lowest suitable frequency
- Reduce static power
 - Selectively use ratioed circuits
 - Selectively use low V_t devices
 - Leakage reduction: stacked devices, body bias, low temperature


April 16, 2008

D. Z. Pan

23. Design for Low Power

20

Low Power Design Techniques

 

- Need combination of techniques at all levels

April 16, 2008

D. Z. Pan

23. Design for Low Power

21