

6. Logical Effort

- Last module:
 - DC Response
 - Logic Levels and Noise Margins
 - Transient Response
 - Delay Estimation
- This module:
 - Delay in logic **networks**
 - Choosing the best number of stages

D. Z. Pan

6. Logical Effort 1

Introduction


- Chip designers face a bewildering array of choices
 - What is the best circuit topology for a function?
 - How many stages of logic give least delay?
 - How wide should the transistors be?
- Logical effort is one method to make these decisions
 - Uses a simple model of delay
 - Allows back-of-the-envelope calculations
 - Helps make rapid comparisons between alternatives
 - Emphasizes remarkable symmetries

D. Z. Pan

6. Logical Effort 2

 Example

- Design the decoder for a register file.
- Decoder specifications:
 - 16 word register file
 - Each word is 32 bits wide
 - Each bit presents load of 3 unit-sized transistors
 - True and complementary address inputs A[3:0]
 - Each input may drive 10 unit-sized transistors
- Need to decide:
 - How many stages to use?
 - How large should each gate be?
 - How fast can decoder operate?



D. Z. Pan

6. Logical Effort 3

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

$\tau = 3RC$
 $\approx 12 \text{ ps in } 180 \text{ nm process}$
 $40 \text{ ps in } 0.6 \mu\text{m process}$

- Delay has two components, $d = f + p$
- Effort delay $f = gh$ (a.k.a. stage effort)

g : logical effort

Measures relative ability
of gate to deliver current
 $g = 1$ for inverter

h : electrical effort = C_{out} / C_{in}

Ratio of output to input caps.
Sometimes called fanout
effort

- Parasitic delay p

- Represents delay of gate driving no load
- Set by internal parasitic capacitance

D. Z. Pan


6. Logical Effort 4

Delay Plots

$$d = f + p$$

$$= gh + p$$

- What about
NOR2?

 


D. Z. Pan

6. Logical Effort 5

Computing Logical Effort

- Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current

 - Measure from delay vs. fanout plots
- Or estimate by counting transistor widths



D. Z. Pan

6. Logical Effort 6

Catalog of Gates

- Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		4/3	5/3	6/3	$(n+2)/3$
NOR		5/3	7/3	9/3	$(2n+1)/3$
Tristate / mux	2	2	2	2	2
XOR, XNOR		4, 4	6, 12, 6	8, 16, 16, 8	

D. Z. Pan

6. Logical Effort 7

Catalog of Gates

- Parasitic delay of common gates
– In multiples of p_{inv} (≈ 1)


Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	

D. Z. Pan

6. Logical Effort 8

 Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



- Logical Effort: $g = 1$
- Electrical Effort: $h = 1$
- Parasitic Delay: $p = 1$
- Stage Delay: $d = 2$
- Frequency: $f_{osc} = 1/(2 \cdot N \cdot d) = 1/4N$


31 stage ring oscillator in
0.6 μm process has
frequency of ~ 200 MHz

D. Z. Pan

6. Logical Effort 9

 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



- Logical Effort: $g = 1$
- Electrical Effort: $h = 4$
- Parasitic Delay: $p = 1$
- Stage Delay: $d = 5$

The FO4 delay is about
200 ps in 0.6 μm process
60 ps in a 180 nm process
 $f/3$ ns in an f μm process
($f/3$ ps in an f nm process)

D. Z. Pan


6. Logical Effort 10

Multistage Logic Networks

- Logical effort generalizes to multistage networks
- Path Logical Effort $G = \prod g_i$

- Path Electrical Effort $H = \frac{C_{out-path}}{C_{in-path}}$

 - Path Effort $F = \prod f_i = \prod g_i h_i$



- Can we write $F = GH$ in general?


D. Z. Pan

6. Logical Effort 11

Paths that Branch

- No! Consider paths that branch:
 
$$\begin{aligned}
 G &= 1 \\
 H &= 90 / 5 = 18 \\
 GH &= 18 \\
 h_1 &= (15 + 15) / 5 = 6 \\
 h_2 &= 90 / 15 = 6 \\
 F &= g_1 g_2 h_1 h_2 = 36 = 2GH
 \end{aligned}$$



D. Z. Pan

6. Logical Effort 12

Branching Effort

- Introduce *branching effort*
 - Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- Now we compute the path effort
 - $F = GBH$

D. Z. Pan

6. Logical Effort 13

Multistage Delays

- Path Effort Delay $D_F = \sum f_i$
- Path Parasitic Delay $P = \sum p_i$
- Path Delay $D = \sum d_i = D_F + P$

D. Z. Pan

6. Logical Effort 14

Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is

$$D = NF^{\frac{1}{N}} + P$$

- This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes

D. Z. Pan

6. Logical Effort 15

Gate Sizes

- How wide should the gates be for least delay?

$$\hat{f} = gh = g \frac{C_{\text{out}}}{C_{\text{in}}}$$

$$\Rightarrow C_{\text{in}_i} = \frac{g_i C_{\text{out}_i}}{\hat{f}}$$


- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives
- Check work by verifying input cap spec is met

D. Z. Pan

6. Logical Effort 16

 Example: 3-stage path


- Select gate sizes x and y for least delay from A to B



D. Z. Pan

6. Logical Effort 17

Example: 3-stage path

 


Logical Effort	$G = (4/3) * (5/3) * (5/3) = 100/27$
Electrical Effort	$H = 45/8$
Branching Effort	$B = 3 * 2 = 6$
Path Effort	$F = GBH = 125$
Best Stage Effort	$\hat{f} = \sqrt[3]{F} = 5$
Parasitic Delay	$P = 2 + 3 + 2 = 7$
Delay	$D = 3 * 5 + 7 = 22 = 4.4 \text{ FO4}$

D. Z. Pan

6. Logical Effort 18

 Example: 3-stage Path

- Work backward for sizes
 $y = 45 * (5/3) / 5 = 15$
 $x = (15*2) * (5/3) / 5 = 10$



D. Z. Pan


6. Logical Effort 19

Best Number of Stages

- How many stages should a path use?
 – Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

$$D = NF^{1/N} + P$$

$$= N(64)^{1/N} + N$$

 

D. Z. Pan

6. Logical Effort 20

Derivation

- Consider adding inverters to end of path
 – How many give least delay?

$$D = NF^{1/N} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$

$$\frac{\partial D}{\partial N} = -F^{1/N} \ln F^{1/N} + F^{1/N} + p_{inv} = 0$$

- Define best stage effort $\rho = F^{1/N}$
 $p_{inv} + \rho(1 - \ln \rho) = 0$

D. Z. Pan

6. Logical Effort 21

Best Stage Effort


- $p_{inv} + \rho(1 - \ln \rho) = 0$ has no closed-form solution
- Neglecting parasitics ($p_{inv} = 0$), we find $\rho = 2.718$ (e)
- For $p_{inv} = 1$, solve numerically for $\rho = 3.59$

D. Z. Pan

 6. Logical Effort 22

Sensitivity Analysis

- How sensitive is delay to using exactly the best number of stages?



- $2.4 < \rho < 6$ gives delay within 15% of optimal
 – We can be sloppy!
 – For example, use $\rho = 4$

D. Z. Pan

6. Logical Effort 23

Decoder Ex: Number of Stages

- Decoder effort is mainly electrical and branching
 Electrical Effort: $H = (32*3) / 10 = 9.6$
 Branching Effort: $B = 8$

- If we neglect logical effort (assume $G = 1$)
 Path Effort: $F = GBH = 76.8$

$$\text{Number of Stages: } N = \log_4 F = 3.1$$

- Try a 3-stage design based on rough estimation

D. Z. Pan

6. Logical Effort 24

Decoder: Gate Sizes & Delay


Logical Effort: $G = 1 * 6/3 * 1 = 2$ (not estimation)

Path Effort: $F = GBH = 154$

Stage Effort: $\hat{f} = F^{1/3} = 5.36$

Path Delay: $D = 3\hat{f} + 1 + 4 + 1 = 22.1$

 Gate sizes: $z = 96 * 1/5.36 = 18$; $y = 18 * 2/5.36 = 6.7$



D. Z. Pan

6. Logical Effort 25

Decoder: Comparison

- Compare many alternatives with a spreadsheet

Design	N	G	P	D
NAND4-INV	2	2	5	29.8
NAND2-NOR2	2	20/9	4	30.1
INV-NAND4-INV	3	2	6	22.1
NAND4-INV-INV-INV	4	2	7	21.1
NAND2-NOR2-INV-INV	4	20/9	6	20.5
NAND2-INV-NAND2-INV	4	16/9	6	19.7
INV-NAND2-INV-NAND2-INV	5	16/9	7	20.4
NAND2-INV-NAND2-INV-INV-INV	6	16/9	8	21.6

D. Z. Pan

6. Logical Effort 26

Review of Definitions

Term	Stage	Path
number of stages	1	N
logical effort	g	$G = \prod g_i$
electrical effort	$h = \frac{C_{out}}{C_{in}}$	$H = \frac{C_{out-path}}{C_{in-path}}$
branching effort	$b = \frac{C_{out-path} + C_{in-path}}{C_{in-path}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	f	$D_f = \sum f_i$
parasitic delay	p	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_f + P$

D. Z. Pan

6. Logical Effort 27

Method of Logical Effort

- 1) Compute path effort $F = GBH$
- 2) Estimate best number of stages $N = \log_4 F$
- 3) Sketch path with N stages
- 4) Estimate least delay $D = NF^{\frac{1}{N}} + P$
- 5) Determine best stage effort $\hat{f} = F^{\frac{1}{N}}$

- 6) Find gate sizes $C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$

D. Z. Pan

6. Logical Effort 28

Limits of Logical Effort

- Chicken and egg problem
 - Need path to compute G
 - But don't know number of stages without G
- Simplistic delay model
 - Neglects input rise time effects
- Interconnect
 - Iteration required in designs with wire
- Maximum speed only
 - Not minimum area/power for constrained delay

D. Z. Pan

6. Logical Effort 29

Summary

- Logical effort is useful for thinking of delay in circuits
 - Numeric logical effort characterizes gates
 - NANDs are faster than NORs in CMOS
 - Paths are fastest when effort delays are ~ 4
 - Path delay is weakly sensitive to stages, sizes
 - But using fewer stages doesn't mean faster paths
 - Delay of path is about $\log_4 F$ FO4 inverter delays
 - Inverters and NAND2 best for driving large caps
- Provides language for discussing fast circuits
 - But requires practice to master

D. Z. Pan

6. Logical Effort 30