

9. Datapath Design

- Last module:
 - Adder circuits
 - Simple adders
 - Fast addition
- This module
 - Comparators
 - Shifters
 - Multi-input Adders
 - Multipliers

D. Z. Pan

9. Datapath Design 1

Comparators


- 0's detector: $A = 00\dots000$
- 1's detector: $A = 11\dots111$
- Equality comparator: $A = B$
- Magnitude comparator: $A < B$

D. Z. Pan

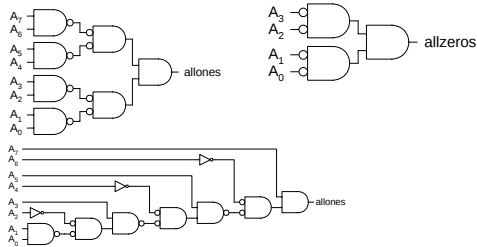9. Datapath Design 2

1's & 0's Detectors

- 1's detector: N-input AND gate
- 0's detector: NOTs + 1's detector (N-input NOR)




D. Z. Pan

 9. Datapath Design 3

Equality Comparator

- Check if each bit is equal (XNOR, or "equality gate")
- 1's detect on bitwise equality




D. Z. Pan

 9. Datapath Design 4

Magnitude Comparator

- Compute $B-A$ and look at sign
- $B-A = B + \sim A + 1$
- For unsigned numbers, carry out is sign bit



D. Z. Pan

9. Datapath Design 5

Signed vs. Unsigned

- For signed numbers, comparison is harder
 - C: carry out
 - Z: zero (all bits of A-B are 0)
 - N: negative (MSB of result)
 - V: overflow (inputs had different signs, output sign $\neq$ B)

Table 10.4 Magnitude comparison		
Relation	Unsigned Comparison	Signed Comparison
$A = B$	Z	Z
$A \neq B$	$\bar{Z}$	Z
$A < B$	$\bar{C} + \bar{Z}$	$(N \oplus V) + \bar{Z}$
$A > B$	$\bar{C}$	$(N \oplus V)$
$A \leq B$	C	$(N \oplus V)$
$A \geq B$	$\bar{C} + Z$	$(N \oplus V) + Z$

D. Z. Pan

9. Datapath Design 6

Shifters


- Logical Shift:
 - Shifts number left or right and fills with 0's
 - 1011 LSR 1 = 0101 1011 LSL 1 = 0110
- Arithmetic Shift:
 - Shifts number left or right. Rt shift sign extends
 - 1011 ASR 1 = 1101 1011 ASL 1 = 0110
- Barrel Shift (Rotate):
 - Shifts number left or right and fills with lost bits
 - 1011 ROR 1 = 1101 1011 ROL 1 = 0111

D. Z. Pan

 9. Datapath Design 7

Funnel Shifter

- A funnel shifter can do all six types of shifts
- Selects N-bit field Y from 2N-bit input
 - Shift by k bits ($0 \leq k < N$)



D. Z. Pan

9. Datapath Design 8

Funnel Shifter Operation

Table 10.10 Funnel shifter operation

Shift Type	B	C	Offset
Logical Right	$0 \dots 0$	$A_{N-1} \dots A_0$	k
Logical Left	$A_{N-1} \dots A_0$	$0 \dots 0$	$N-k$
Arithmetic Right	$A_{N-1} \dots A_{N-1}$ (sign extension)	$A_{N-1} \dots A_0$	k
Arithmetic Left	$A_{N-1} \dots A_0$	0	$N-k$
Rotate Right	$A_{N-1} \dots A_0$	$A_{N-1} \dots A_0$	k
Rotate Left	$A_{N-1} \dots A_0$	$A_{N-1} \dots A_0$	$N-k$

- Computing N-k requires an adder

D. Z. Pan

9. Datapath Design 9

Simplified Funnel Shifter

- Optimize down to 2N-1 bit input

Table 10.11 Simplified funnel shifter


Shift Type	Z	Offset
Logical Right	$0..0, A_{N-1} \dots A_0$	k
Logical Left	$A_{N-1} \dots A_0, 0..0$	$\bar{k}$
Arithmetic Right	$A_{N-1} \dots A_{N-1}, A_{N-1} \dots A_0$	k
Arithmetic Left	$A_{N-1} \dots A_0, 0..0$	$\bar{k}$
Rotate Right	$A_{N-2} \dots A_0, A_{N-1} \dots A_0$	k
Rotate Left	$A_{N-1} \dots A_0, A_{N-1} \dots A_1$	$\bar{k}$

D. Z. Pan

 9. Datapath Design 10

Funnel Shifter Design 1

- N N-input multiplexers
 - Use 1-of-N hot select signals for shift amount
 - nMOS pass transistor design (V_t drops!)




D. Z. Pan

 9. Datapath Design 11

Funnel Shifter Design 2

- Log N stages of 2-input MUXes
 - No select decoding needed




D. Z. Pan

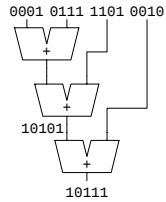9. Datapath Design 12

Multi-input Adders

- Suppose we want to add k N-bit words
 - Ex: 0001 + 0111 + 1101 + 0010 = 10111
- Straightforward solution: k-1 N-input CPAs
 - Large and slow




D. Z. Pan

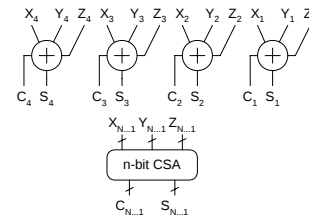9. Datapath Design 13

Carry Save Addition

- Full adder sums 3 inputs, produces 2 outputs
 - Carry output has twice *weight* of sum output
- N full adders in parallel: *carry save adder*
 - Produce N sums and N carry outs




D. Z. Pan

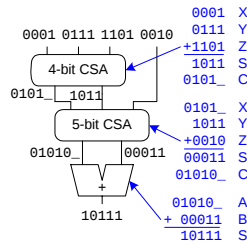9. Datapath Design 14

CSA Application

- Use k-2 stages of CSAs
 - Keep result in carry-save redundant form
- Final CPA computes actual result



D. Z. Pan

9. Datapath Design 15

Multiplication

- Example:

$$\begin{array}{r}
 1100 : 12_{10} \\
 0101 : 5_{10} \\
 \hline
 1100 \\
 0000 \\
 1100 \\
 0000 \\
 \hline
 00111100 : 60_{10}
 \end{array}$$

multiplicand
 multiplier
 partial products
 product

- M x N-bit multiplication
 - Produce N M-bit partial products
 - Sum these to produce M+N-bit product

D. Z. Pan

9. Datapath Design 16

General Form

- Multiplicand: $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$
- Multiplier: $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$
- Product: $P = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$

$$\begin{array}{r}
 y_5 \ y_4 \ y_3 \ y_2 \ y_1 \ y_0 \\
 x_5 \ x_4 \ x_3 \ x_2 \ x_1 \ x_0 \\
 \hline
 x_5 y_5 \ x_5 y_4 \ x_5 y_3 \ x_5 y_2 \ x_5 y_1 \ x_5 y_0 \\
 x_4 y_5 \ x_4 y_4 \ x_4 y_3 \ x_4 y_2 \ x_4 y_1 \ x_4 y_0 \\
 x_3 y_5 \ x_3 y_4 \ x_3 y_3 \ x_3 y_2 \ x_3 y_1 \ x_3 y_0 \\
 x_2 y_5 \ x_2 y_4 \ x_2 y_3 \ x_2 y_2 \ x_2 y_1 \ x_2 y_0 \\
 x_1 y_5 \ x_1 y_4 \ x_1 y_3 \ x_1 y_2 \ x_1 y_1 \ x_1 y_0 \\
 x_0 y_5 \ x_0 y_4 \ x_0 y_3 \ x_0 y_2 \ x_0 y_1 \ x_0 y_0 \\
 \hline
 p_{11} \ p_{10} \ p_9 \ p_8 \ p_7 \ p_6 \ p_5 \ p_4 \ p_3 \ p_2 \ p_1 \ p_0
 \end{array}$$


multiplicand
 multiplier
 partial products
 product

D. Z. Pan

9. Datapath Design 17



Dot Diagram

- Each dot represents a bit

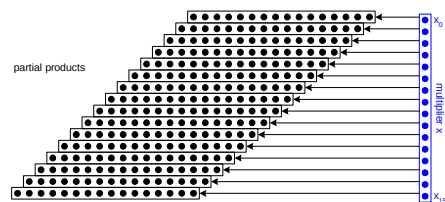

D. Z. Pan

9. Datapath Design 18

  

Fewer Partial Products

- Array multiplier requires N partial products
- If we looked at groups of r bits, we could form N/r partial products.
 - Faster and smaller?
 - Called radix- 2^r encoding
- Ex: $r = 2$: look at pairs of bits
 - Form partial products of 0, Y , $2Y$, $3Y$
 - First three are easy, but $3Y$ requires adder ☹



D. Z. Pan 9. Datapath Design 21

Booth Encoding

- Instead of $3Y$, try $-Y$, then increment next partial product to add $4Y$
- Similarly, for $2Y$, try $-2Y + 4Y$ in next partial product


Inputs			Partial Product	Booth Selects		
x_{2i+1}	x_{2i}	x_{2i-1}	PP_i	X'_i	$2X'_i$	M_i
0	0	0	0	0	0	0
0	0	1	Y'	1	0	0
0	1	0	Y'	1	0	0
0	1	1	$2Y'$	0	1	0
1	0	0	$-2Y'$	0	1	1
1	0	1	$-Y'$	1	0	1
1	1	0	$-Y'$	1	0	1
1	1	1	$-0 (= 0)$	0	0	1

D. Z. Pan 9. Datapath Design 22

  

Simplified Sign Extension

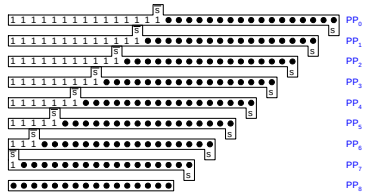- Sign bits are either all 0's or all 1's
 - Note that all 0's is all 1's + 1 in proper column
 - Use this to reduce loading on MSB




D. Z. Pan

 9. Datapath Design 25

Even Simpler Sign Extension

- No need to add all the 1's in hardware
 - Precompute the answer!



D. Z. Pan

9. Datapath Design 26

Advanced Multiplication

- Signed vs. unsigned inputs
- Higher radix Booth encoding
- Array vs. tree CSA networks
- Serial Multiplication

D. Z. Pan

9. Datapath Design 27


Serial Multiplication

- Lower area at expense of speed
 - signal processing on bit streams
- Delay for $n \times n$ multiply
 - $2n$ bit product with $2n$ bit delay
 - Additional n -bit delay to shift n bits
 - Total delay of $3n$ bits
- Pipelined multiplier:** possible to produce a new $2n$ bit product every $2n$ bit times after initial n bit delay
 - Only interest in high-order bits: n bit delay for n bit product

D. Z. Pan

9. Datapath Design 28

Serial Multiplier Architecture

 


Pipeline multiplier accumulates partial product sums starting with the least significant partial product (result is n -bit number which is truncated to $n-1$ bits before the next partial product)

D. Z. Pan

9. Datapath Design 29

Division

 

- To divide A by B
 - Shift P and A one bit left
 - Subtract B from P, put the result back
 - If result is negative, additional steps, set low order bits of A to 0, otherwise to 1
 - “restoring” or “non-restoring” division to fix negative result

D. Z. Pan

9. Datapath Design 30

SRT Division

- Divide A by B (n-bits)(view numbers as fractions between $\frac{1}{2}$ and 1)
1. If B has k leading 0s when expressed using n bits, shift all registers by k bits
 2. For i = 0 to (n-1)
 1. If top 3 bits of P equal, set $q_i = 0$, shift (P,A) one bit left
 2. If top 3 bits of P not all equal, and P negative, set $q_i = -1$, (written as $\bar{1}$, shift (P,A) one bit left and add B
 3. Otherwise, set $q_i = 1$, shift (P,A) one bit left, subtract B
 3. If the final remainder is negative, correct by adding B, correct quotient by subtracting 1; finally, shift remainder k bits right
 4. Radix-4 SRT algorithm used in Pentium chip

D. Z. Pan

9. Datapath Design 31

Floating Point (IEEE 754-1985)

Special values NaN, ∞ , $-\infty$

Rounds to nearest by default, but three other rounding modes

"Halfway" result rounded to nearest even floating point number

"Denormal" numbers to represent results of computations

 $< 1.0 \times 2^{E_{min}}$

Sophisticated facilities for handling exceptions

D. Z. Pan

9. Datapath Design 32

Iterative Division

- Newton's iteration: finding the 0 of a function
 - starting from a guess for the 0, approximate function by its tangent at the guess, form new guess based on where tangent has a 0
- Goldschmidt's method
 - To compute a/b , iteratively, multiply both numerator and denominator by r with $r.b = 1$
 - Set $x_0 = a$, $y_0 = b$ and write $b = 1 - \delta$ where $|\delta| < 1$
 - If we pick $r_0 = 1 + \delta$, then $y_1 = r_0 y_0 = 1 - \delta^2$
 - Next, pick $r_1 = 1 + \delta^2$, etc., and $y_i \rightarrow 1$
 - Used in the TI 8847 chip

D. Z. Pan

9. Datapath Design 33