

EE 302, Introduction to Electrical and Computer Engineering

Dr. Archie Holmes, Jr.

Exam #1

Solution



Class Average = _____

Standard Deviation = _____

PROBLEM #1. SHORT ANSWER (10 POINTS)

- a) Explain the advantages and disadvantages of protecting intellectual property with a trade secret

Advantages: Protection last forever if secret is not divulged; Do not have to disclosure idea/procedure like in patent

Disadvantages: No protection if independently discovered or reverse engineered

- b) Explain the differences between patents and copyrights.


Patents provide protection for an idea while copyrights protect the expression of an idea

- c) You have three resistors with values of 500Ω , 600Ω , and $1.2\text{ k}\Omega$. How can these resistors be combined to maximize and minimize the total (i.e., equivalent) resistance? Draw each resistor combination and provide a value for the equivalent resistance.

Minimum: Place resistors in parallel. $R_{eq} = 222\Omega$

Maximum: Place resistors in series. $R_{eq} = 2.3\text{ k}\Omega$.

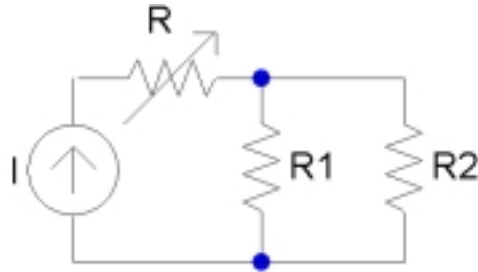PROBLEM #2. CONCEPTUAL PROBLEMS (15 POINTS)




- a) When resistor R is increased in the above circuit, determine if the quantities below increases (I), decreases (D), or stays the same (S).

Power dissipated by resistor $R1$: S

Power dissipated by resistor $R2$: S

Power supplied by the current source: I

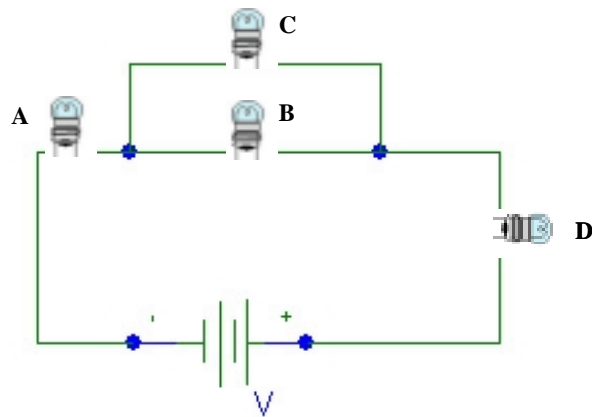
- b) The circuit below has four identical light bulbs connected to an ideal battery.



- (i) How do the brightnesses of these bulbs compare? **$(A=D) > (B=C)$**
(ii) Which light bulb(s) draws the least amount of current? **C & B**
(iii) What happens to the brightness of the remaining light bulbs when light bulb C is removed **A & D decreases, B increases**
(iv) What happens to the brightness of the remaining light bulbs when light bulb D is removed. **All go out (decrease) since there is no current flow.**


PROBLEM #3. VOLTAGE AND CURRENT DIVISION (20 POINTS)

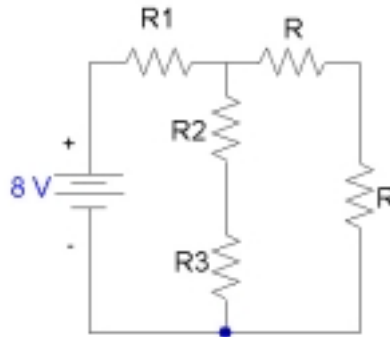- a) Calculate the value of R in the circuit below so that resistor R_1 dissipates 2 mW of power. Assume $R_1 = 8\text{k}\Omega$, $R_2 = 4\text{k}\Omega$, and $R_3 = 6\text{k}\Omega$ in your calculation.



$R = 20\Omega$

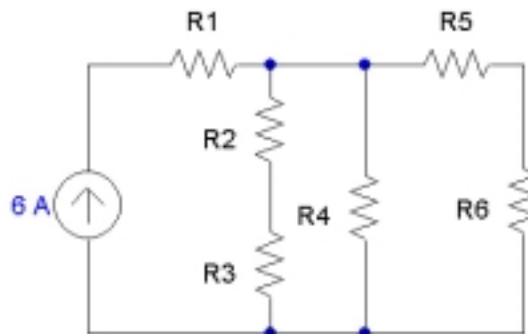
- c) Calculate the current through resistor R_4 and the voltage across resistor R_3 in the circuit below. Assume $R_1 = 12\Omega$, $R_2 = 7\Omega$, $R_3 = 3\Omega$, $R_4 = 10\Omega$, $R_5 = 6\Omega$, and $R_6 = 4\Omega$ in your calculations. **Make sure** you clearly identify your reference directions for each of these quantities!!



Current through $R_4 = \pm 2\text{ A}$ (depending on direction assumed)

Voltage across resistor $R_3 = \pm 6\text{V}$ (depending on direction assumed)

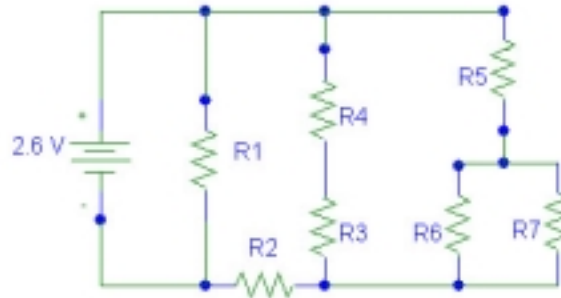PROBLEM #4. POWER DISSIPATION IN ELECTRIC CIRCUITS (30 POINTS)



- a) If all of the resistors in the above circuit have the same value (i.e., R), select the resistance value such that the source provides 1.3 W of power to the circuit. **$R = 8\Omega$**
- b) Calculate the power being dissipated by resistors R2, R4, and R7

Power dissipated by R2 = 245 mW

Power dissipated by R4 = 45 mW

Power dissipated by R7 = 20 mW

- c) If all the resistors are to have the same power rating, what minimum power rating is required in this circuit. Assume that the power rating can change by 1/8-W increments (e.g., 1/8-W, 1/4-W, 3/8-W, etc.)

R1 dissipates the most power (= 0.845 W). Therefore I need 7/8-W power rating.

PROBLEM #5 THREE-WAY LIGHT BULB DESIGN (25 POINTS)



A light bulb which provides a single intensity of light consists of a single filament as shown above. When a voltage is applied to the leads, the filament dissipates power and this power dissipation leads to light being emitted (measured in watts).

Your task in this problem is to design a three-way light bulb. This light bulb uses two filaments to produce three different levels of light output. Your light bulb is to emit light a 50, 100, and 150 W when a voltage of 120 V is applied. In your design provide the following:

- The resistance value of each filament. **The resistance for 50 W is 288 Ω . The resistance for 100 W is 144 Ω . These are placed in parallel to give the resistance for 150 W.**
- Diagrams showing how the filaments are connected to the 120-V supply (assume an ideal battery) to produce each light output value. **See above.**
- The range of expected annual energy costs of operating this light bulb for 100 hours a month. Assume that the cost of electricity is \$0.0355 per kW-hr. **Minimum \$2.13; Maximum is \$6.39**

Bonus (10 points). If this light bulb is powered by thirteen 9-V batteries, the 50-W setting produces 45 watts of power. How much power is produced in the other two settings?

The batteries have an internal resistance of 0.615 Ω . Therefore the other powers are 85.32 W and 121.5 W.

EXTRA CREDIT (3 POINTS TOTAL)

- 1) Who are the two major political parties' candidates for Vice President

Dick Cheney and Joe Lieberman

- 2) Where did your instructor attend college? Graduate school?

University of Texas at Austin; University of California at Santa Barbara