

## EE394V Homework Assignment #4

Due date: 11/23/2011

For all questions elaborate some few conclusions or comments about the results. For all questions you are free to make further, but logical, assumptions you consider necessary

- 1) Consider a buck-boost converter with  $L = 500 \mu\text{H}$ ,  $C = 1 \text{ mF}$ ,  $R = 10 \Omega$ ,  $E = 30 \text{ V}$ . Simulate an hysteresis control that achieves a voltage output of  $40 \text{ V}$  with a current ripple of  $1 \text{ Amp}$ . Plot the state variables in time domain and on a phase portrait.
- 2) Now, try regulating the output with a PI controller. For the PI controller choose some suitable gains and simulate the resulting system. Plot the state variables in time domain and on a phase portrait.
- 3) Consider a buck converter with  $L=500 \mu\text{H}$ ,  $C= 1000 \mu\text{F}$ ,  $E = 20\text{V}$ , and a constant-power load of  $50 \text{ W}$ . Now simulate the buck converter with a PID controller with  $k_d=0.001$ ,  $k_p=0.01$ , and  $k_i=1$ . What happens if you make  $k_d=0$ ?