



Snubbers

"A snubber is a circuit connected around a power semiconductor device (switch) for the purpose of altering its switching trajectory. Snubbers usually have the objective of reducing power loss in the semiconductor device."

from kereh

The idea is that the commutation becomes more linear

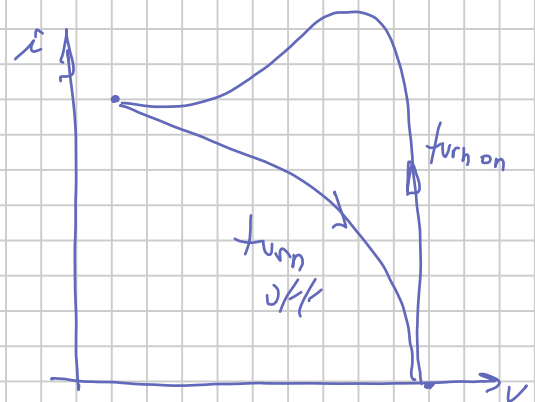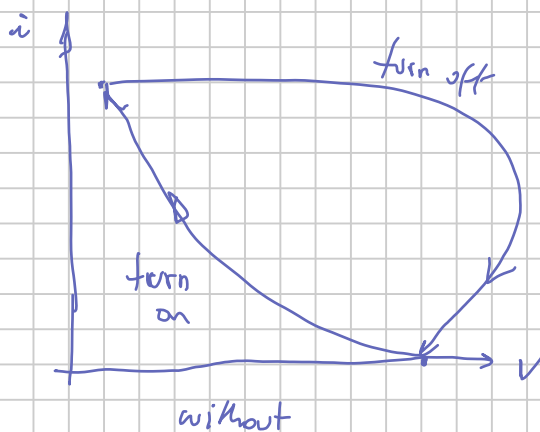Simplest example \rightarrow with inductive load a capacitor can eliminate the voltage overshoot during turn off but the "price" to pay is now a current overshoot.




Additional issue: I can't always add the clamping diode

so I can do something like this:



But this circuit doesn't work because I can't discharge the capacitor

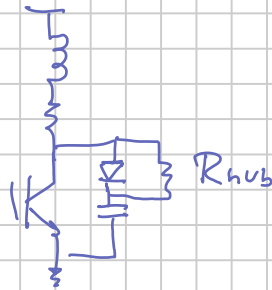
One alternative is to add a resistor to discharge the capacitor:



Lossy shubber

Switching losses are traded off for resistive losses

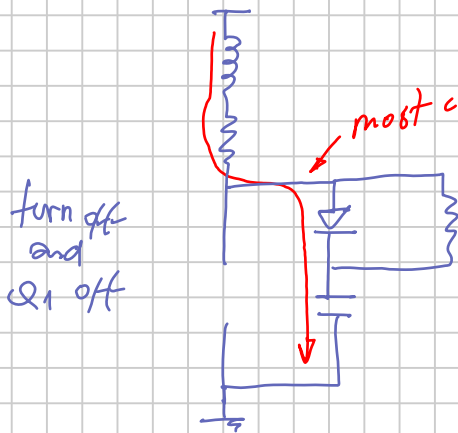
But if capacitor is sized correctly then it may be worth.



most current flows like this until the capacitor is charged and current stops to flow


oscillatory RLC circuit

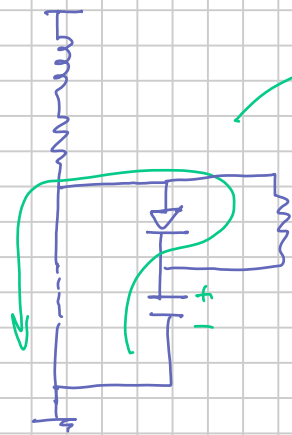so current flows mostly during turn-off if capacitor is sized properly



During turn-on the capacitor discharges through the resistance. Hence, current overshoot is reduced (no short-circuit)

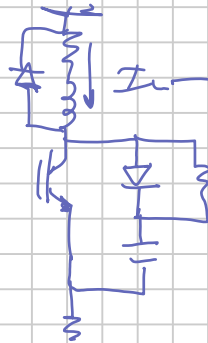For simplicity consider a damped RL load with real diode:



I_L assumed to be constant

turn off shubber

The design must achieve 2 objectives → 1) The capacitor should be big enough to avoid voltage overshoot during turn-off
2) $\tau = RC$ should be short enough so the capacitor discharges completely before the switch turns off and starts to get charged again

As seen before the current changes linearly during turn off



$$i_{sw}(t) = I_L - \frac{I_L}{t_{off}} t$$

During turn off $i_c = I_L - i_{sw} = \frac{I_L t}{t_{off}}$

$$V_c = \int_0^{t_{off}} \frac{i_c}{C} dt = \int_0^{t_{off}} \frac{I_L t}{t_{off} C} dt = \frac{I_L t^2}{2 t_{off} C} \Big|_0^{t_{off}} = \frac{I_L t_{off}}{2C}$$

$V_c(t) \Big|_{t_{off}}$

$$U_{sw, t_{off}} = \int_0^{t_{off}} V_c(t) i_{sw}(t) dt = \int_0^{t_{off}} \left(\frac{I_L t^2}{2C t_{off}} \right) \left(I_L - \frac{I_L t}{t_{off}} \right) dt$$

$$U_{sw, t_{off}} = \frac{I_L^2}{24C} t_{off}^2$$

The capacitor will be charged until it reaches V_{off} ; hence, it accumulates an energy of

$$U_c = \frac{1}{2} C V_{off}^2$$

← This energy is dissipated in the resistance during turn on:

Recall that inductive commutation has a loss of

$$P_{sw} \Big|_{I_c} = \frac{V_{off} I_c t_{sw} f}{a} \quad \begin{cases} a=2 \text{ ideal diode} \\ a=1.5 \text{ real diode} \end{cases}$$

With a snubber


$$P_{sw} \Big|_{snub} = \left(\underbrace{\frac{I_L^2 t_{off}^2}{24C}}_{P_{off}} + \underbrace{\frac{1}{2} C V_{off}^2}_{P_{on}} \right) f$$

We want that


$$P_{sw} \Big|_{I_c} > P_{sw} \Big|_{snub}$$

↙ If $a=2$ (ideal diode)
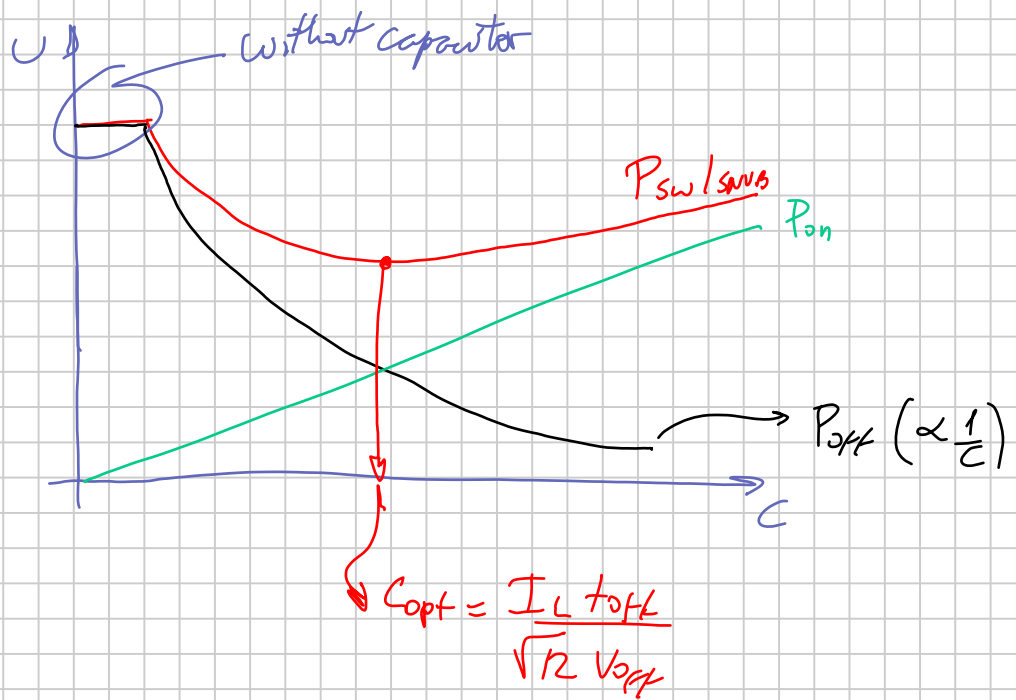
$$\frac{I_L^2 t_{off}^2}{24C} + C V_{off}^2 < I_L V_{off} t_{sw}$$



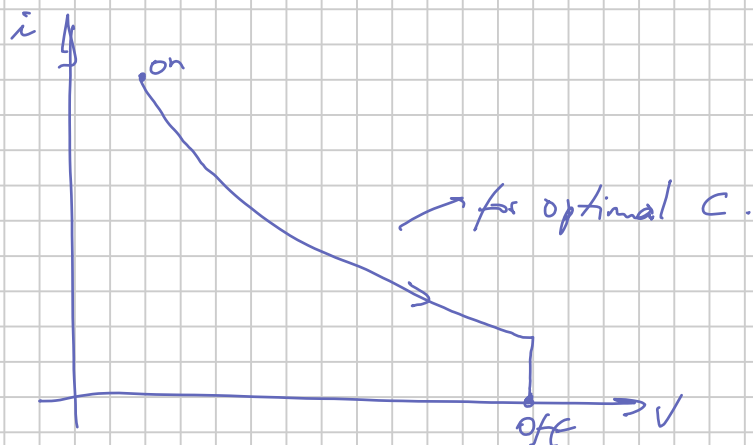With optimal snubber $a \approx 3.5$ ($a = \sqrt{12}$)



From condition (2) above:

If $\tau = RC < \frac{t_{cond}}{2} \rightarrow$ More than 98% of the capacitor energy is discharged before turn-off

$$\text{Thus } \rightarrow RC < \frac{DT}{2} \rightarrow RC < \frac{DT}{2C}$$

The resistor power rating is the average power given by the energy stored in the capacitor


$$P_r = \frac{1}{2} C V_{off}^2 f$$

The capacitor serves to avoid overshoots during turn off, so it reduces losses during turn off

For turn on transitions the dual circuit is needed.

Dual of capacitor \rightarrow inductor

Turn-on snubber

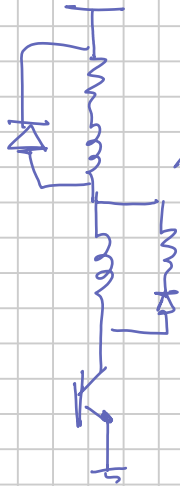

Snubber's inductor limits the rate of rise of switch current during switching

After the switch turns off the energy dissipates through the diode and resistance

Assuming linear voltage transient

$$V_L = V_{off} \frac{t}{t_{on}}$$

$$U_{sw} = \int_0^{t_{on}} V_{sw} i_{sw} dt = \int_0^{t_{on}} V_{off} \left(1 - \frac{t}{t_{on}}\right) \left(\frac{V_{off}}{L} \frac{t^2}{2t_{on}}\right) dt$$

Hence

$$P_{sw|snub} = \left(\frac{V_{off}^2 t_{on}^2}{24L} + \frac{1}{2} L I_{on}^2 \right) f$$

Optimal $\rightarrow L_{opt} = \frac{V_{off} t_{on}}{\sqrt{2} I_{on}}$

Additional condition: $\frac{L}{R} < \frac{(1-D)T}{2} \rightarrow R > \frac{2L}{(1-D)T}$




Combined snubbers



Must dissipate $\rightarrow \frac{1}{2} C V_{off}^2 + \frac{1}{2} L I_{on}^2$

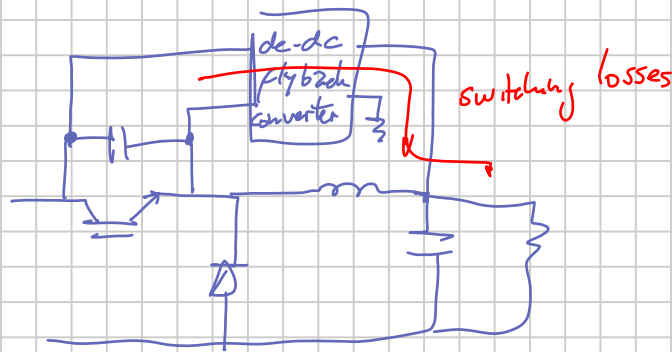Lossless snubbers \rightarrow losses are re injected to the output
(like a car turbo charger)



Additional techniques \rightarrow resonant methods