
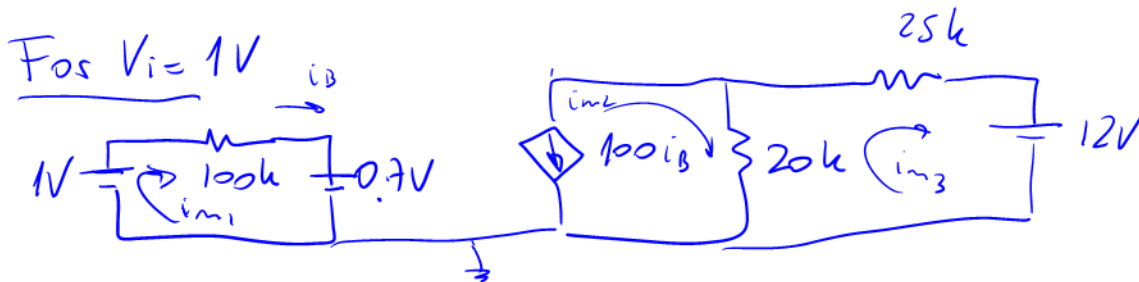


EE411 – Fall 2009, Test 1

Please, show all your work on the test sheets. A correct answer without supporting work gets no credit. One sheet of notes is permitted. Write your name in all pages. Do not unstaple. You have 60 minutes to complete the test.

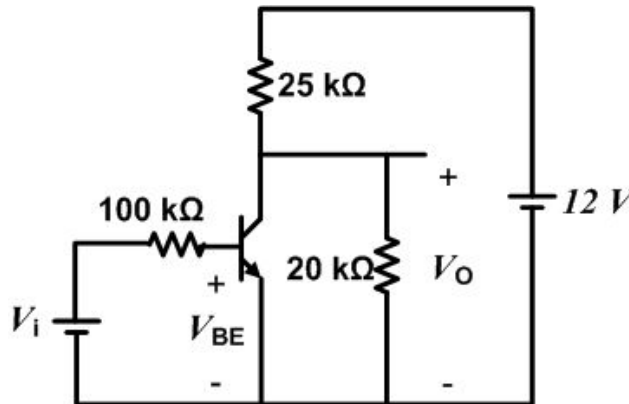Problem 1 (30 points)

For the circuit in the figure below find V_O / V_i for $V_i = 1\text{ V}$ and $V_i = 0.5\text{ V}$. Consider that $\beta = 100$, $V_{BE} = 0.7\text{ V}$.



#1 $1 - 0.7 = 1.10^5 i_{m1} \rightarrow i_{m1} = \frac{0.3}{1.10^5} = 3\mu\text{A}$

#2 $i_{m2} = -100 i_B = -100 i_{m1} = -300\mu\text{A}$

#3 $12 + 25000 i_{m3} + 20000 i_{m3} - 20000 i_{m2} = 0$


$$45000 i_{m3} = -6 - 12 = -18$$

$$i_{m3} = \frac{-18}{45000} = -\frac{2}{5000} = -0.2 \cdot 10^{-3} = -400\mu\text{A}$$

$$V_O = 20000 (i_{m2} - i_{m3}) = 20,000 \Omega 100\mu\text{A} = 2 \cdot 10^4 \cdot 1 \cdot 10^{-4} = 2\text{V}$$

$$\frac{V_O}{V_i} = 2$$

For $V_i = 0.5V$

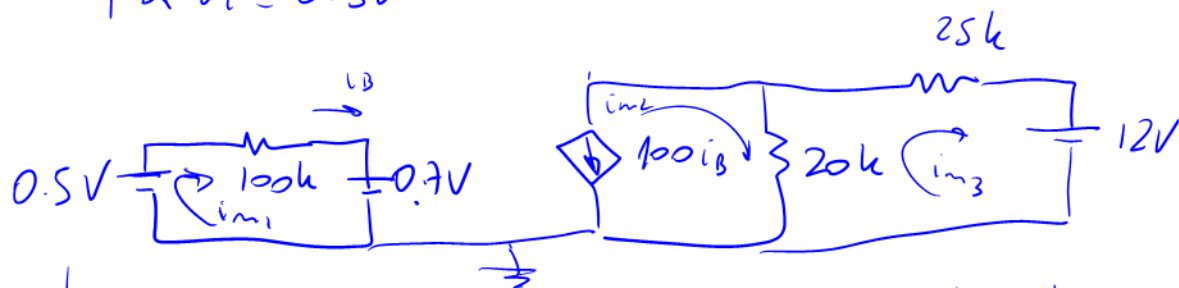

→ In reality a BJT transistor will not operate appropriately with this input voltage because it is less than $0.7V$. But for the sake of completing the calculations let's solve the circuit:

#1 $0.5 - 0.7 = 100000 i_{m1} \rightarrow i_{m1} = \frac{-0.2}{1 \cdot 10^{-5}} = -2 \mu A$

#2 $i_{m2} = -100 i_B = 200 \mu A$


#3 $12 + 45000 i_{m3} - 20000 i_{m2} = 0$

→ $i_{m3} = \frac{4 - 12}{45000} = -177.7 \mu A$


$V_o = 20000 (i_{m2} - i_{m3}) = 7.554 V$

$\frac{V_o}{V_i} = 15.11$


EE411 – Fall 2009, Test 1

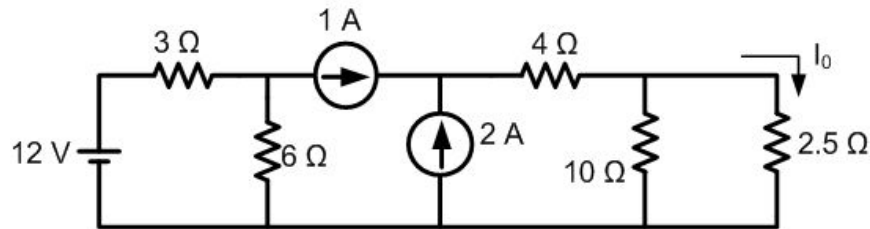Problem 2 (25 points)Apply superposition in order to obtain I_0 .


a) 12V voltage source on, rest off

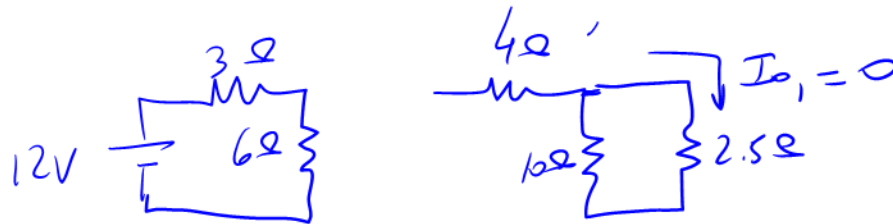

b) 2A current source on, the rest off

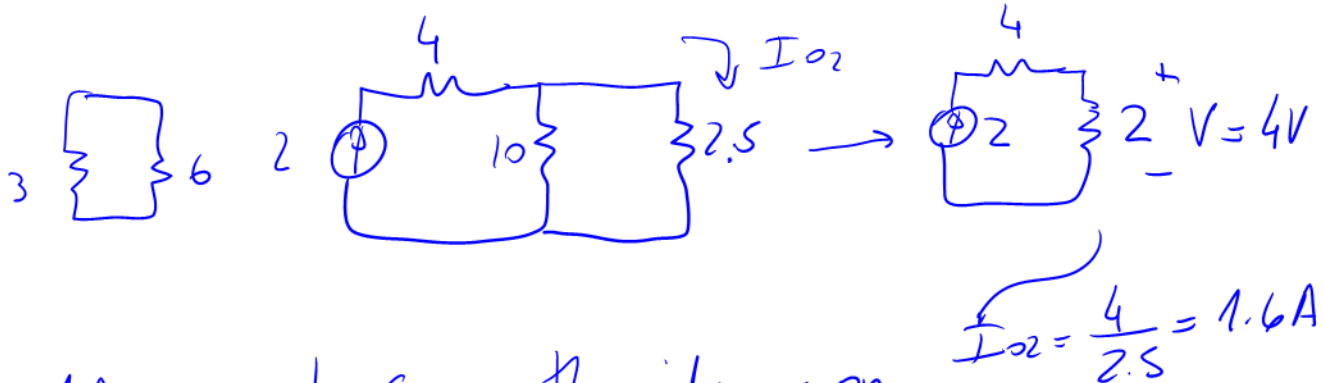

c) 1A current source the only one on

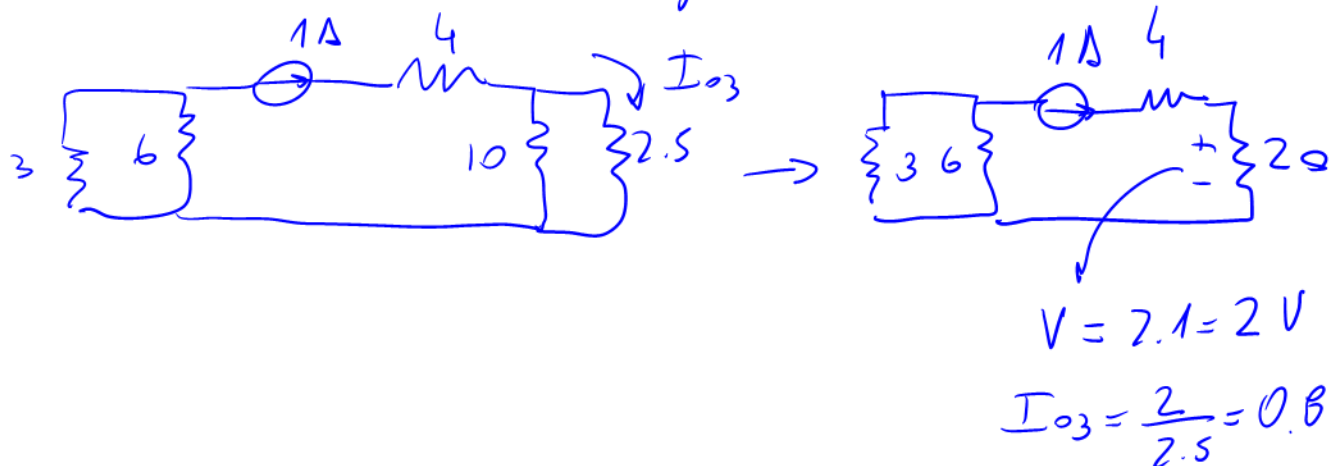


$$I_0 = 1.6 + 0.8 = 2.4 \text{ A}$$

EE411 – Fall 2009, Test 1

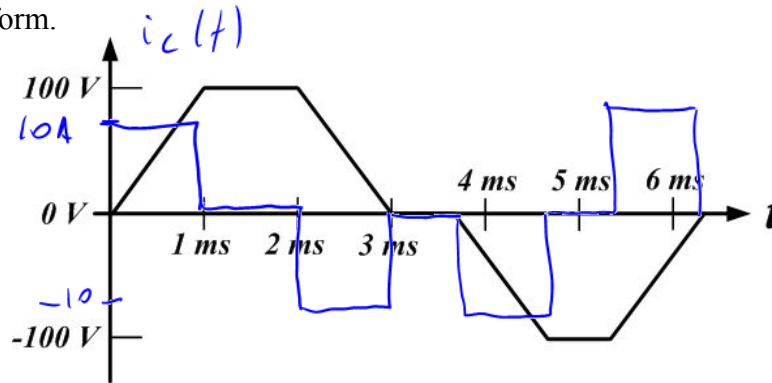Problem 3 (15 points)

The figure shows the voltage waveform for a $100\ \mu\text{F}$ capacitor. Sketch the capacitor current waveform.



$$i_c = C \frac{dV_c}{dt}$$

$$0 \leq t \leq 1\text{ ms} \rightarrow i_c = 100 \times 10^{-6} \frac{100}{1 \cdot 10^{-3}} = 10\text{ A}$$


$$1 \leq t \leq 2\text{ ms} \rightarrow i_c = 0$$

| the rest follows the same idea


EE411 – Fall 2009, Test 1

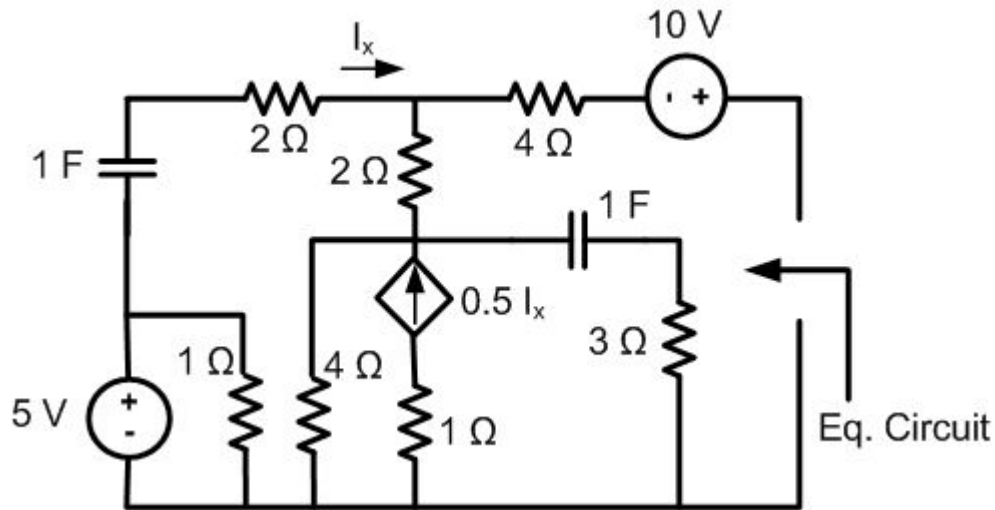Problem 4 (30 points)

Find the Thevenin and Norton equivalents for the circuit in the next figure under dc conditions.



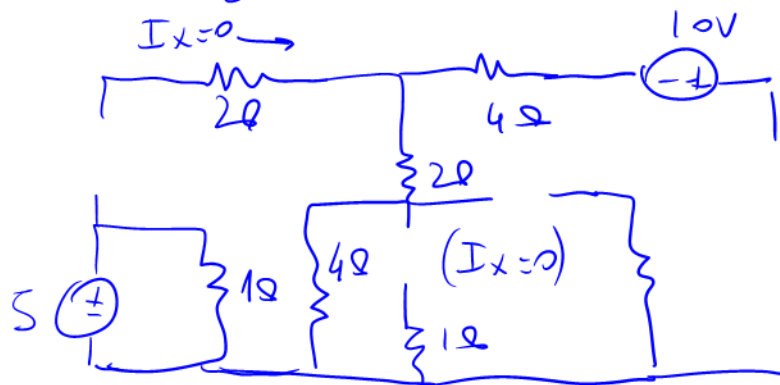Since in dc $i_C = 0$ then the circuit is



Thus, the simplified circuit is

